

E11 Lecture 12: Diodes & Transistors


Profs. David Money Harris & Sarah Harris
Fall 2011

Outline

- Semiconductors
- Diodes
- Transistors


Semiconductors

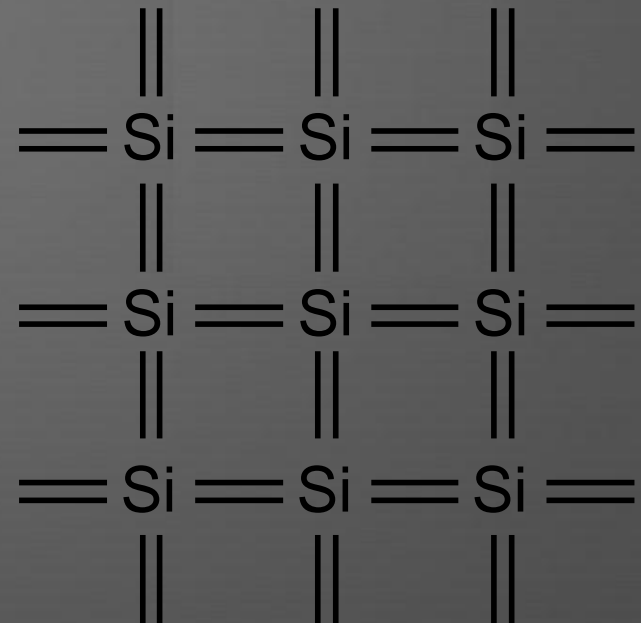- Silicon is a Group IV Material
- Forms tetrahedral crystal with bonds to four neighbors
- Adjustable conductivity





Dopants

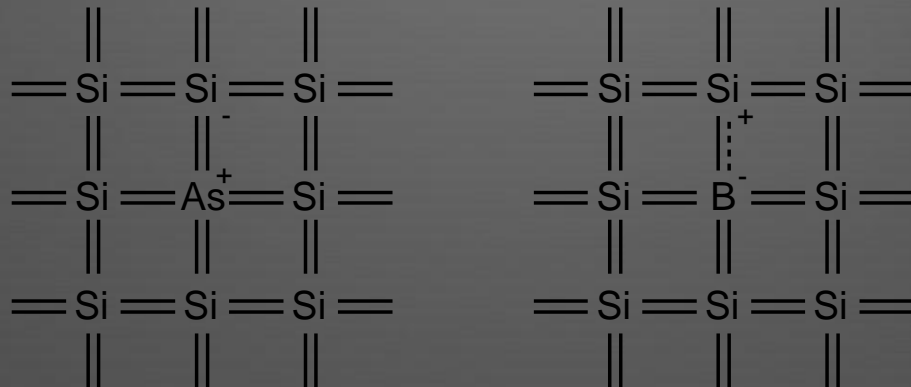- Silicon is a semiconductor
- Pure silicon has no free carriers and conducts poorly
- Adding dopants increases the conductivity
- Group V: extra electron (n-type)
- Group III: missing electron, called hole (p-type)



Diodes

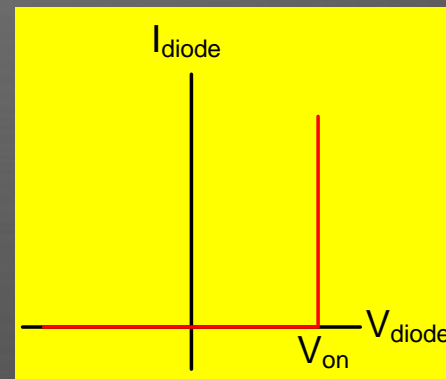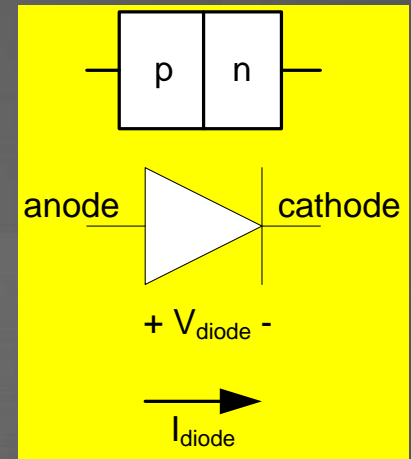- A p-n junction is called a *diode*
 - p side is called *anode*
 - n side is called *cathode*
- Current only flows from anode to cathode
 - When $V_{\text{diode}} > V_{\text{on}}$
 - $V_{\text{on}} \approx 0.7 \text{ V}$ for silicon diodes
- Approximate I-V behavior




Light Emitting Diode

- Electron-hole recombination in a diode releases photons
- Wavelength of photons depends on semiconductor's bandgap
- GaAs and related materials glow red, yellow, green, or blue
- V_{on} depends on material, typically ~ 1.7 V
- Typically 5-20 mA gives satisfactory brightness



Nick Holonyak

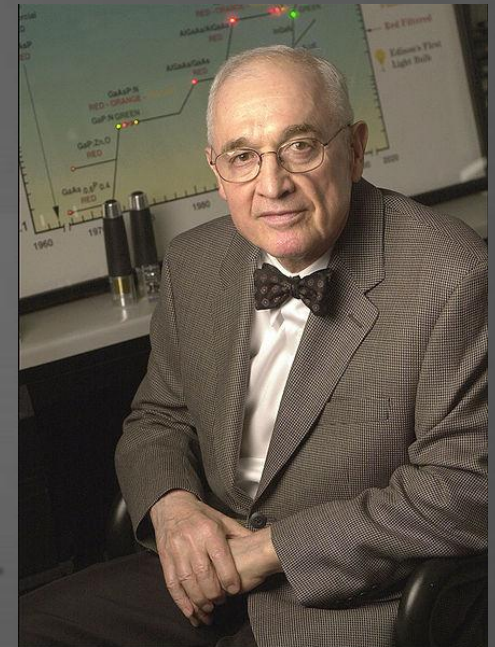
- 1928-
- Invented the first practical visible LED in 1962 while at GE
- EE Prof at University of Illinois
- Also invented laser diode and light dimmer



en.wikipedia.org/wiki/File:Nick_Holonyak_Jr.jpg


LED Circuit Analysis

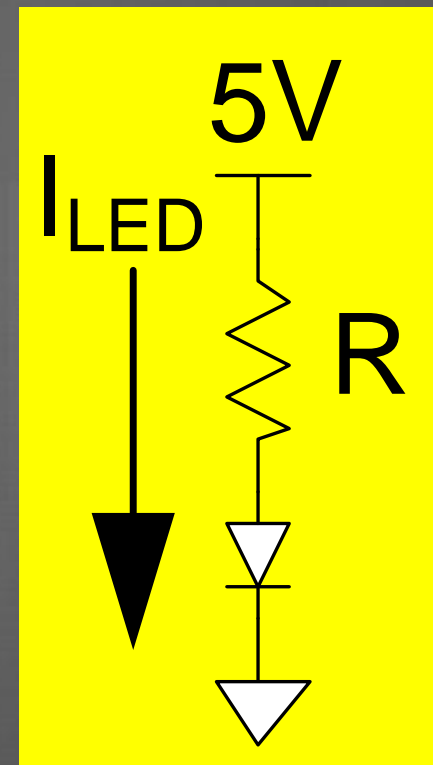- What value of R makes $I_{LED} = 10 \text{ mA}$?
- a) 10Ω
- b) 100Ω
- c) 330Ω
- d) $3 \text{ k}\Omega$




npn Bipolar Junction Transistor

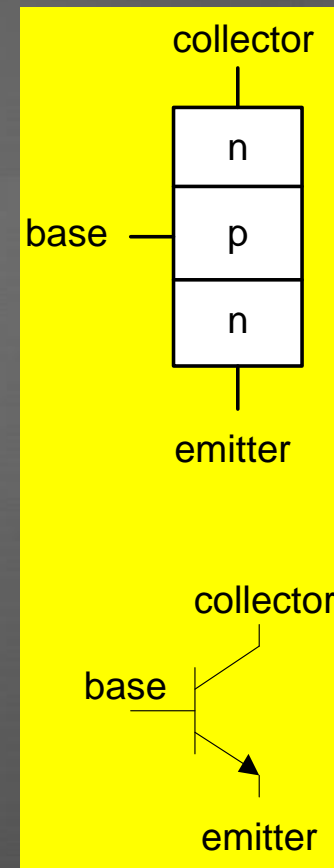- Made of two back-to-back diodes
- Behaves as a current-controlled switch
- 3 Terminals
 - Base (control)
 - Emitter (negative switch terminal)
 - Collector (positive switch terminal)



William Shockley

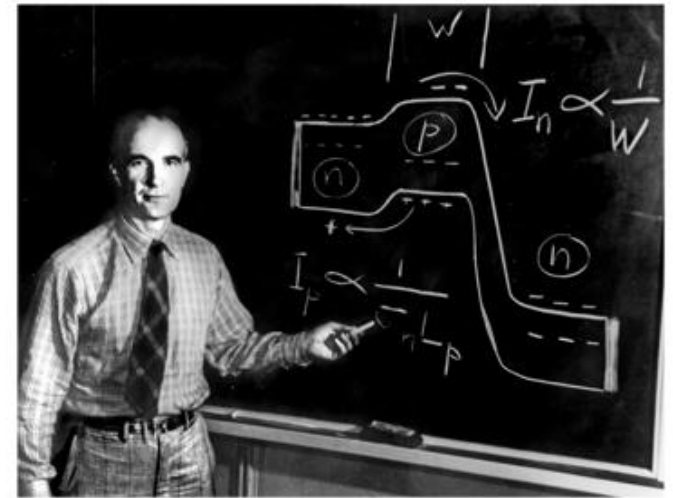- 1910-1989
- Son of a mining engineer
- B.S. Caltech, Ph.D. MIT
- Invented BJT in 1948 @ Bell Labs
- Supervised Bardeen & Brattain
 - who invented first transistor in 1947
 - The three received the Nobel Prize in Physics in 1956



computerhistory.org

npn Transistor Behavior

- Base-to-emitter junction is a diode
- Small base current allows larger collector current to flow
- Three operating regions:
 - Cutoff:
 - no current flows
 - Linear:
 - collector current proportional to base current
 - Saturation:
 - collector current ceases to increase with base current

Operating Regions

- Three operating regions:

- Cutoff:

- base-emitter diode off
 - no current flows

$$V_{be} < V_{on}$$
$$I_c = 0$$

- Linear:

- base-emitter diode on
 - collector current proportional to base current


β typically around 100, but highly variable

$$V_{be} = V_{on}, V_{ce} > 0$$
$$I_c = \beta I_b$$

- Saturation:

- base-emitter diode on
 - collector current independent of base current
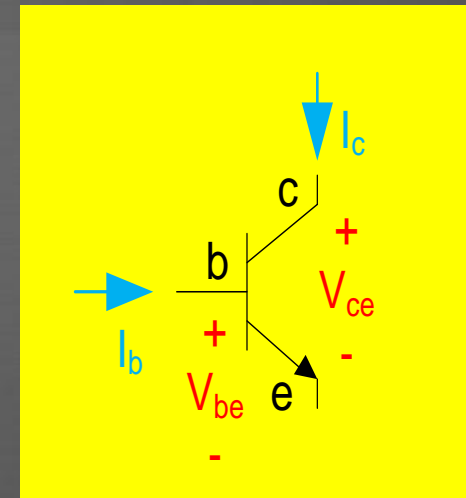
$$V_{be} = V_{on}, V_{ce} \approx 0$$
$$I_c \text{ const}$$




Linear and Saturation Models

- When $V_{be} \approx 0.7V$, transistor turns ON
- If $V_{ce} > 0$, transistor behaves as a current amplifier

$$I_c = \beta I_b$$

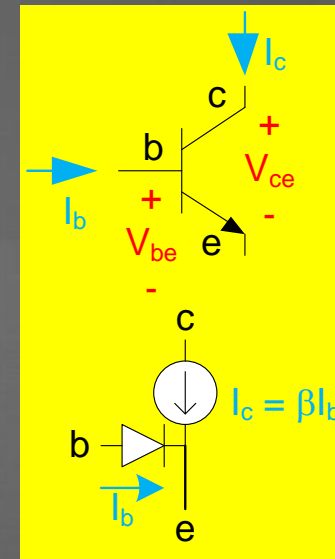- If V_{ce} falls to 0, I_c ceases to rise with I_b
 - Saturation



Transistor Applications

- Amplifiers
- Switches

Transistor Amplifier

- For $V_{in} < 0.7$, Cutoff, $I_c = 0$, $V_{out} = V_{cc}$
- For $V_{in} > 0.7$, linear mode of operation


$$I_b = \frac{V_{in} - 0.7}{R_b}$$

$$I_c = \beta I_b$$


$$V_{out} = V_{cc} - I_c R_c = V_{cc} - \beta \frac{R_c}{R_b} (V_{in} - 0.7)$$

$$Gain = \frac{dV_{out}}{dV_{in}} = -\beta \frac{R_c}{R_b}$$

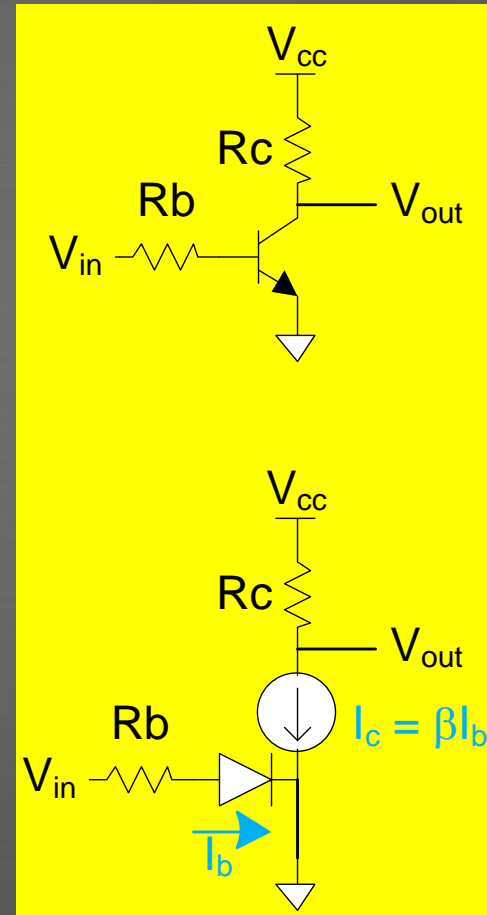- But V_{out} never falls below 0
 - Transistor saturates first



Amplifier Behavior

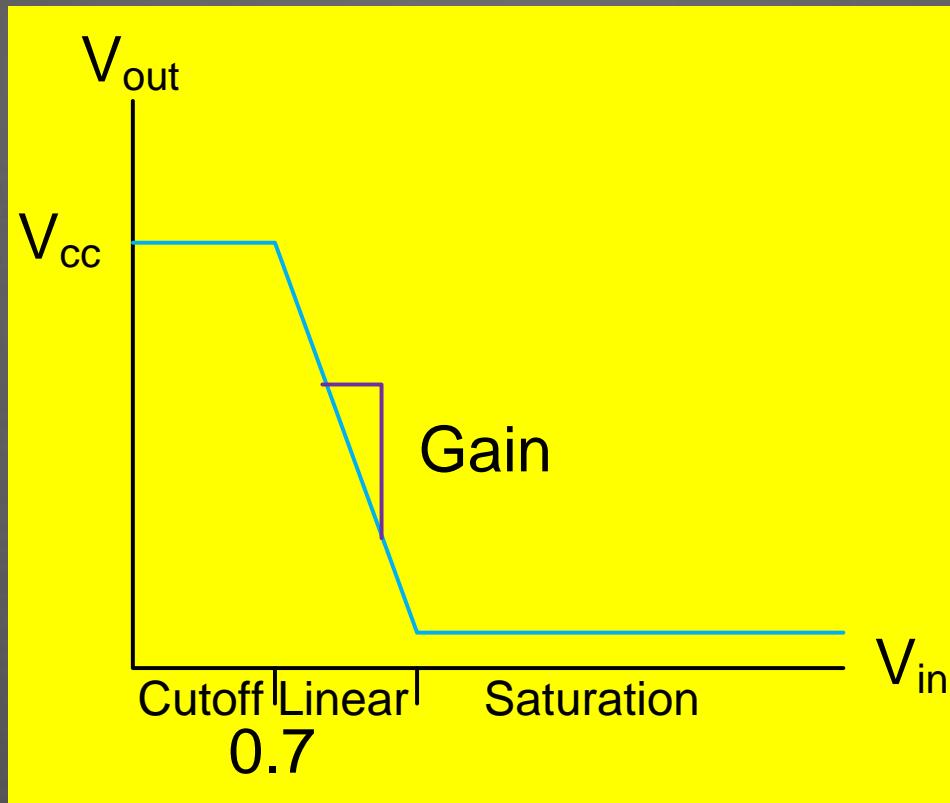

Transistor as Switch

- Turn on or off a high-current load
 - Such as the motor
 - Needs more current than digital I/O
- If $D_2 = 0$, transistor is cutoff
 - No current flows to load
- If $D_2 = 1$ (5V), transistor saturates
 - $I_b = (5 - 0.7) / 215 = 20 \text{ mA}$
 - I_c of up to $\sim 2\text{A}$ flows to load
 - Enough to pull x down close to 0

