

E11 Lecture 14: Capacitors & Inductors

Profs. David Money Harris & Sarah Harris
Fall 2011

Outline


- Frequencies
- Capacitors
- Inductors
- 1st order systems
 - DC Response
 - Step Response

Frequencies

- Consider a signal $x(t) = \cos(\omega t)$
- ω is the frequency of the signal (in units of radians/sec)
- If $\omega = 0$, $x(t) = 1$
 - Zero frequency is a constant signal, called *DC* (direct current)
- If ω is relatively small, signal is called *low frequency*
- If ω is relatively large, signal is called *high frequency*


Capacitor

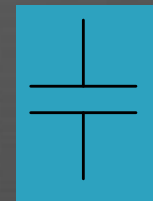- A capacitor consists of two conductors separated by an insulator.
- When a voltage V is applied, positive charge $+Q$ accumulates on one plate and negative charge $-Q$ accumulates on the other.
- The capacitance is the ratio of charge to voltage:
 - $Q = CV$
- Units of Farads (farad = coulomb / volt)



Michael Faraday

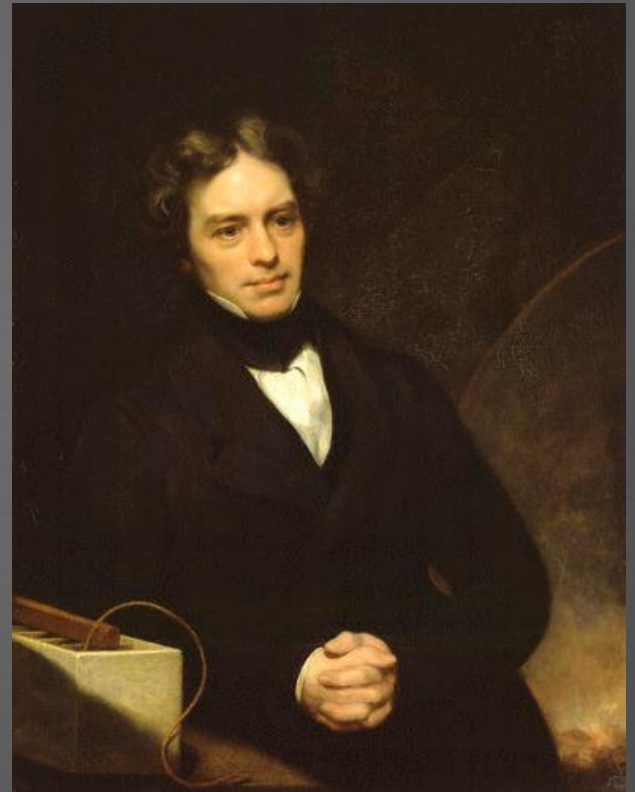- 1791-1867
- English chemist and physicist
- Poor family, little formal education
 - Didn't know calculus
- One of history's best experimentalists
- Professor at the Royal Institution
- Inventor of motors
- Established the basis for concept of electromagnetic field




en.wikipedia.org/wiki/File:Michael_Faraday_001.jpg

Capacitor I-V Relationship

- $Q = CV$
- Current is $I = dQ/dt$
- Hence

$$I = C \frac{dV}{dt}$$

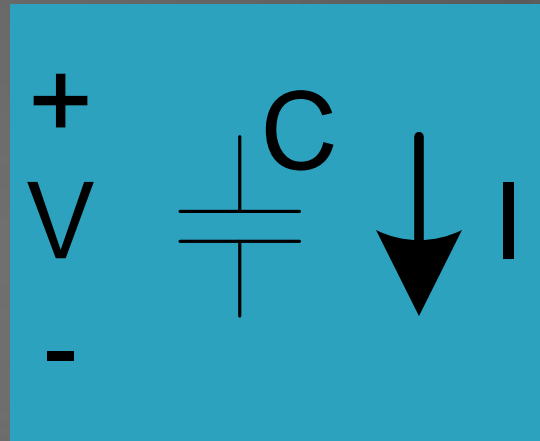

Capacitor Energy Storage

- A capacitor stores energy in the form of the electric field created by the charge.
- If a capacitor is charged from 0 to V_{DD} , the energy stored is

$$\begin{aligned} E &= \int_0^T P dt \\ &= \int_0^T VI dt \\ &= \int_0^T CV \frac{dV}{dt} dt \\ &= \int_0^{V_{DD}} CV dV \\ &= \frac{1}{2} CV_{DD}^2 \end{aligned}$$

Capacitor Behavior


- A capacitor doesn't like to change its voltage instantly.
 - Requires current
 - Requires energy
- Capacitor looks like:
 - Open circuit at low frequency
 - Short circuit at high frequency

Capacitor Applications

- Store electrical energy
- Stabilize a voltage (such as the power supply)
 - Capacitor opposes changes to its voltage
- Passing only high frequency signals

Capacitor Types

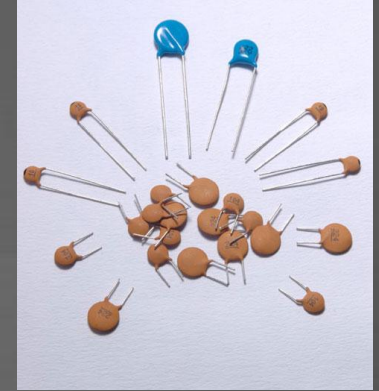- **Ceramic Disk**
 - Typical values of 10 pF – 100 nF
 - Cheap and reliable
 - No polarity
- **Electrolytic**
 - Popular for values $> 1 \mu\text{F}$
 - Cheap
 - Wide tolerances ($\sim -50\% / +100\%$)
 - Polarized, can explode if hooked backward
- **Tantalum**
 - Similar to electrolytic, but smaller and more expensive



leds-capacitors-manufacturer.com




diytrade.com

Inductor

- An inductor consists of a coil of wire.
- Current flowing in the wire induces a magnetic field
- Changing the magnetic field induces a voltage

$$V = L \frac{dI}{dt}$$

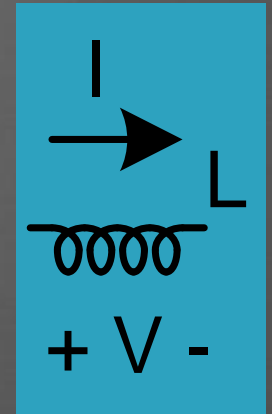

- Inductance L has units of Henries (Volts / (Amperes/sec))

Joseph Henry

- 1797-1878
- American scientist
- Poor family, father died young
- Research was the basis of the telegraph
- First secretary of the Smithsonian



www.photolib.noaa.gov/bigs/perso124.jpg

Inductor Energy Storage

- An inductor stores energy in the form of the magnetic field created by the current.
- If an inductor has current I flowing, the energy stored is

$$\begin{aligned} E &= \int_0^T P dt \\ &= \int_0^T IV dt \\ &= \int_0^T IL \frac{dI}{dt} dt \\ &= \int_0^I LI dI \\ &= \frac{1}{2} LI^2 \end{aligned}$$

Inductor Behavior

- An inductor doesn't like to change its current instantly.
 - Requires voltage
 - Requires energy
- Inductor looks like:
 - Short circuit at low frequency
 - Open circuit at high frequency

Inductor Applications

- Store magnetic energy
- Magnetically operate electromechanical systems
- Passing only low frequency signals

Inductor Types

- Coils
 - Often wound on iron core to increase magnetic field
 - Typical values of $10 \mu\text{H}$ – 100 mH
 - Relatively expensive compared to capacitors



<http://personal.ee.surrey.ac.uk/Personal/H.M/UG/Labs/components/inductors.htm>

First Order Systems

- A 1st order system is described by a 1st order differential eq
 - An equation with just a first derivative
- Systems with a single energy storage element are 1st order
 - e.g. a single inductor or capacitor

Example: RC Circuit


- Apply KCL to find governing equation

$$I_1 = \frac{V - x}{R}$$

$$I_2 = C \frac{dx}{dt}$$


$$I_1 = I_2$$
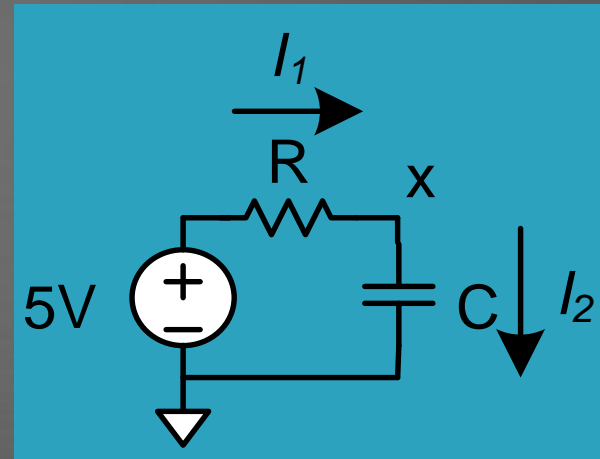
$$\frac{dx}{dt} + \frac{x}{RC} = \frac{V}{RC}$$



RC Circuit DC Response

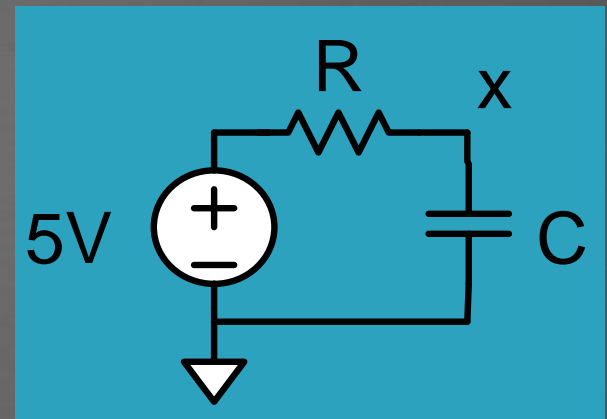- What is the voltage at node x?
- A) 0 V
- B) 2.5 V
- C) 5 V
- D) infinity



Differential Equations

- This is a 1st order differential equation
 - An equation involving a single derivative

$$\frac{dx}{dt} + \frac{x}{RC} = \frac{V}{RC}$$

- Solving differential equations
 - Need to know the initial condition (value of x at the start)
 - Guess the form of the answer
 - Use intuition about functions, or past experience
 - All 1st order DiffEqs have solution of the form
 - Substitute the guess into the equation and check
 - Use initial condition to solve for free variable

$$x(t) = Ae^{\frac{-t}{\tau}} + B$$

RC Circuit DC Response

- Two ways to analyze

- Formal: $\frac{dx}{dt} + \frac{x}{RC} = \frac{V}{RC}$

- $V = \text{constant } 5\text{ V}$


- x must be constant $\rightarrow dx/dt = 0$

- $x = V = 5\text{ V}$

- Intuitive


- Capacitor looks like open circuit at DC

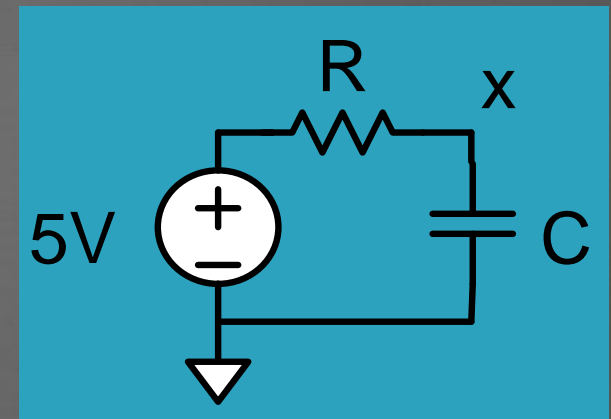- By voltage divider, $x = V \frac{\infty}{\infty + R} = V$





RC Circuit DC Response

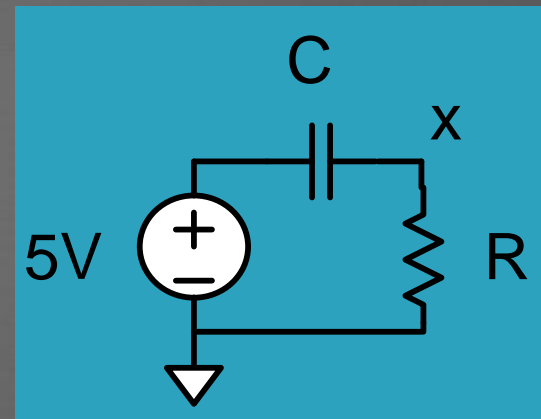- What is the voltage at node x?
- A) 0 V
- B) 2.5 V
- C) 5 V
- D) infinity



RC Circuit Step Response

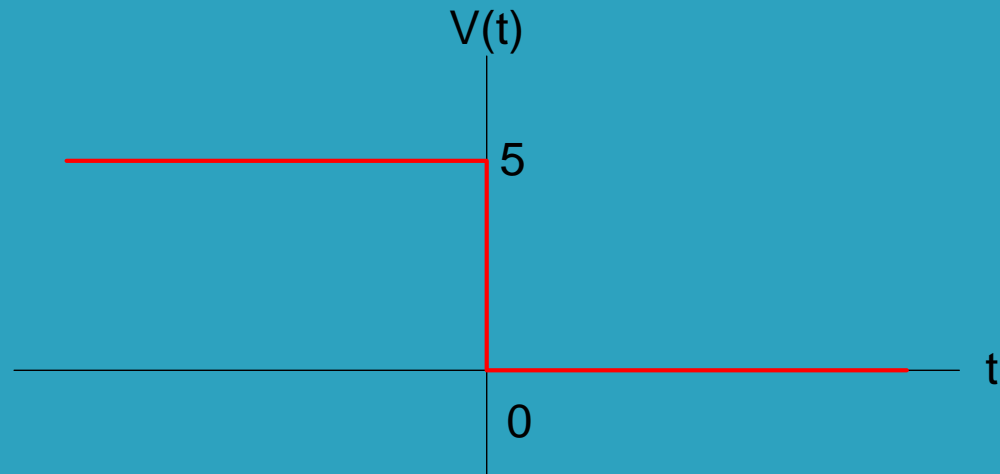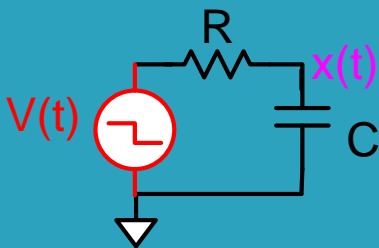- A step is an abrupt change from one value to another.
- What happens if the input voltage steps from 5 to 0 at time $t = 0$?



RC Circuit Step Response

$$\frac{dx}{dt} + \frac{x}{RC} = \frac{V(t)}{RC}$$

$$V(t) = \begin{cases} 5 & t < 0 \\ 0 & t > 0 \end{cases}$$

- $x(t) = 5$ for $t < 0$ (initial condition)
- $x(t)$ for $t > 0$ must be a function whose derivative is of the same form so it can cancel

- Guess $x(t) = Ae^{\frac{-t}{\tau}} + B$

- Initial condition: $x(0) = 5 \rightarrow A+B = 5$

- Hence $x(t) = 5e^{\frac{-t}{RC}}$

After step


$$\frac{d}{dt} \left(Ae^{\frac{-t}{\tau}} + B \right) + \frac{Ae^{\frac{-t}{\tau}} + B}{RC} = 0$$

$$\frac{-1}{\tau} Ae^{\frac{-t}{\tau}} + \frac{Ae^{\frac{-t}{\tau}} + B}{RC} = 0$$

$$\tau = RC; B = 0$$

RC Circuit Response

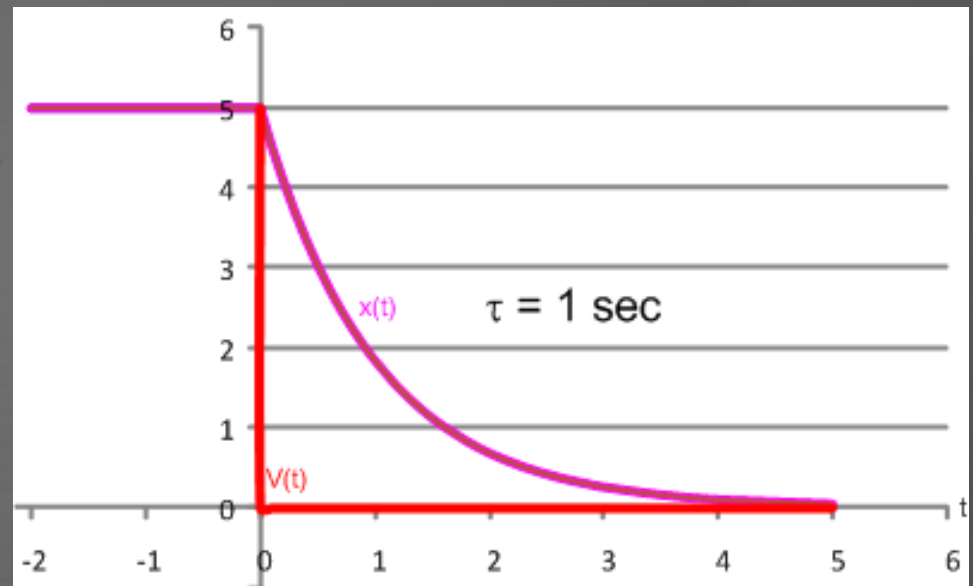- τ is the *time constant*
- Capacitor won't change voltage instantaneously
- τ describes how fast exponential approaches final value




- After 3τ , output is ~ 0
- All 1st order systems have a response in the form of an exponential approaching the final value


Step Response

- What would the RC circuit be to a rising step?


(a)

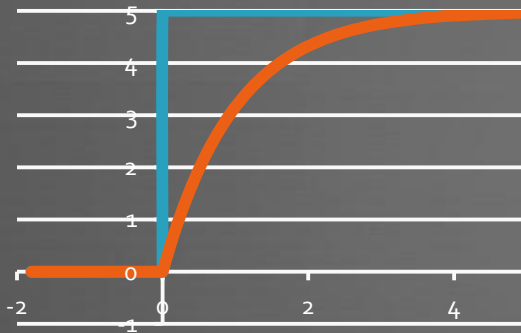


(b)

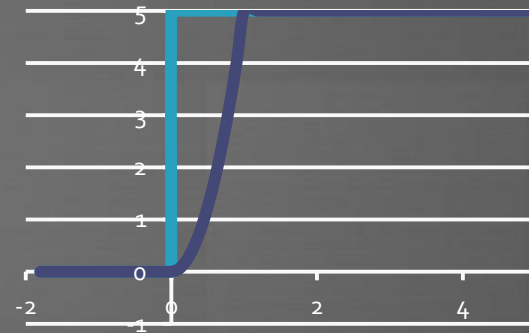

(c)

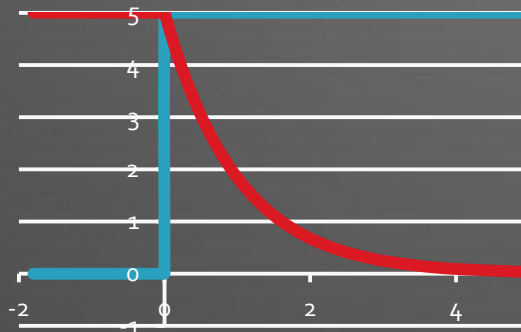

(d)

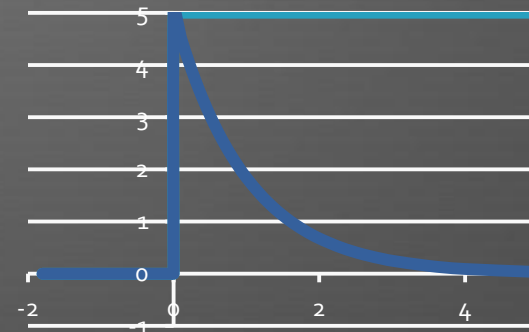

RC Circuit Step Response

$$\frac{dx}{dt} + \frac{x}{RC} = \frac{V(t)}{RC}$$

$$V(t) = \begin{cases} 0 & t < 0 \\ 5 & t > 0 \end{cases}$$

- Solution is of the form $x(t) = Ae^{\frac{-t}{\tau}} + B$

- Initial condition: $x(0) = 0 \rightarrow A+B = 0$

- After step:

$$\frac{d}{dt} \left(Ae^{\frac{-t}{\tau}} + B \right) + \frac{Ae^{\frac{-t}{\tau}} + B}{RC} = 5$$

$$\frac{-1}{\tau} Ae^{\frac{-t}{\tau}} + \frac{Ae^{\frac{-t}{\tau}} + B}{RC} = 5$$

$$\tau = RC; B = 5$$

- Hence,

$$x(t) = 5 - 5e^{\frac{-t}{RC}} = 5 \left(1 - e^{\frac{-t}{RC}} \right)$$