

E11 Lecture 9-10: Circuits

Profs. David Money Harris & Sarah Harris
Fall 2011

Outline

- Voltage, Current, Resistance
- Ohm's Law
- Kirchoff's Current Law
- Resistor Combinations
- Power
- Multimeters
- Ideal and Real Power Supplies

Voltage

- The electric force to drive electricity between two points
- Units: Volts (V)
- Technically:
 - energy / unit charge (Volt = Joule / Coulomb; $V = J/C$)
- Informally:
 - how hard the circuit wants to push electrons...
- Voltage is always measured between two points
 - Meaningless without a reference point
 - We typically call the reference point *ground*
 - If the ground is connected well across the system, we can treat it as **0V**

Allesandro Volta

- 1745-1827
- Invented the first battery
- Granted title as Count by Napoleon in 1810 in honor of his work



en.wikipedia.org/wiki/File:Volta_A.jpg

Current

- The amount of electric charge flowing through a circuit per time.
- Unit: Amperes
 - (Amperes = Coulombs / Sec, A = C/s)
- Technically:
 - $I = dQ/dt$

Andre-Marie Ampere

- 1775-1836
- French physicist and mathematician
- A main discoverer of electromagnetism



en.wikipedia.org/wiki/File:Ampere_Andre_1825.jpg

Resistance

- A measure of the opposition to the flow of electric current
- Units: Ohm (Ω)
 - $\Omega = V/A$
- A material with high resistance is called an *insulator*
- A material with low resistance is called a *conductor*

Georg Ohm

- 1789 – 1854
- German high school teacher
- Later joined Jesuit College in Colonge
- Determined relationship between voltage and current in a conductor
- College unsatisfied with his research and he resigned



en.wikipedia.org/wiki/File:Ohm3.gif

“Resistance is Useless”

- Prostetnic Vogon Jeltz, *Hitchhiker's Guide to the Galaxy*




Circuits

- Circuits consist of nodes and elements
- Nodes:
 - Wires, at a particular voltage relative to ground
- Elements
 - Voltage sources
 - Resistors, capacitors, inductors
 - Diodes, transistors
 - Motors
 - Other sensors ...

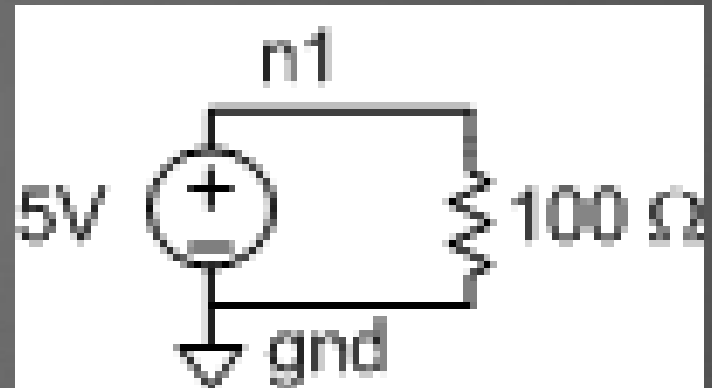Example

- This circuit has two nodes
 - n_1 , gnd
- Two elements
 - A 5V voltage source
 - A $100\ \Omega$ resistor




Ohm's Law

- Voltage = Current \times Resistance ($V = IR$)
 - Or $I = V/R$

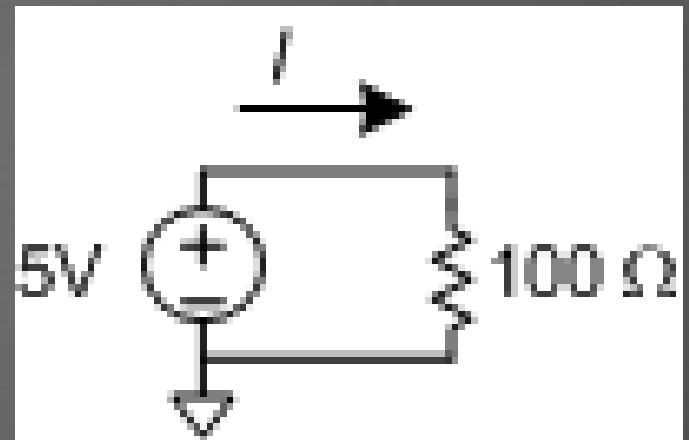Example

- A 5 V power supply is connected to a 100 Ω resistor. How much current flows?
- A) 500 A
- B) 20 A
- C) 50 mA
- D) 5 mA




Kirchoff's Current Law (KCL)

- Charge is conserved
- It doesn't accumulate on circuit nodes
- Hence, the **current flowing into a circuit node equals the current out of the node.**

KCL Example

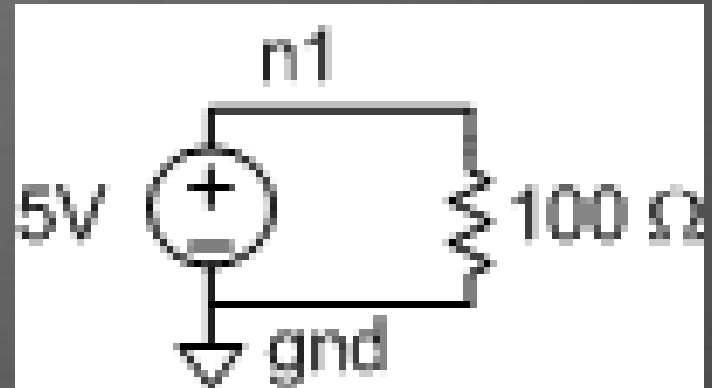- Current flowing out of 5V supply into n1: 50 mA
- Current flowing out of n1 into resistor: 50 mA
- KCL: 50 mA = 50 mA 😊



Voltage Divider

- Compute voltage at x:


- Ohm's Law: $I_1 = \frac{5-x}{R_1}$

$$I_2 = \frac{x-0}{R_2}$$

- KCL: $I_1 = I_2$

- Solve for x:
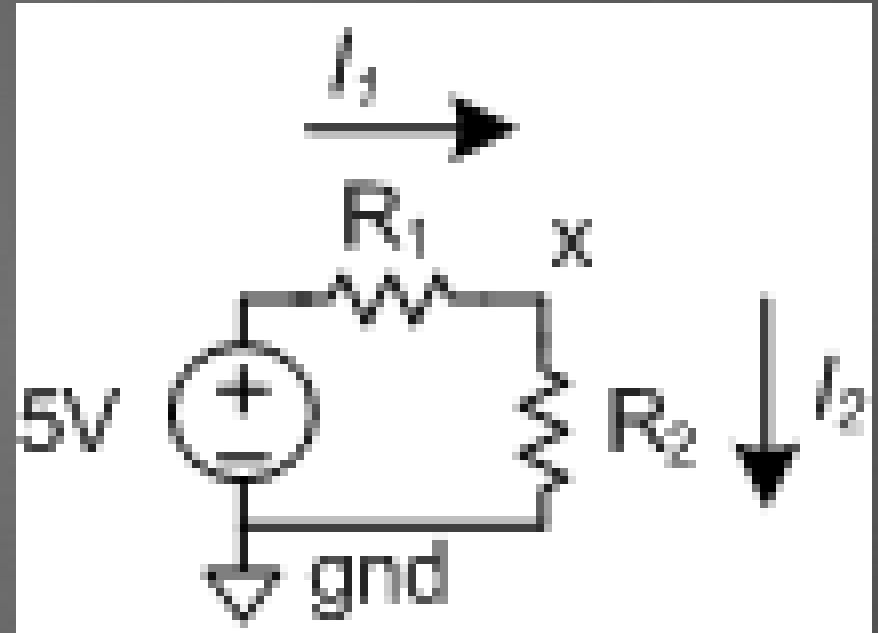
$$\frac{5-x}{R_1} = \frac{x}{R_2} \Rightarrow x = 5 \left(\frac{R_2}{R_1 + R_2} \right)$$



Example

- What is the voltage at x if $R_1 = R_2 = 100 \Omega$?
- A) 100 V
- B) 5 V
- C) 2.5 V
- D) 0.5 V

Ex: Potentiometer


- A potentiometer (pot) is a variable resistor with an adjustable tap
- Can be used as a voltage divider
 - As tap slides from top to bottom, V_{out} varies from 5V to 0V.



Series Resistors

- Two resistors in series are equivalent to one larger one

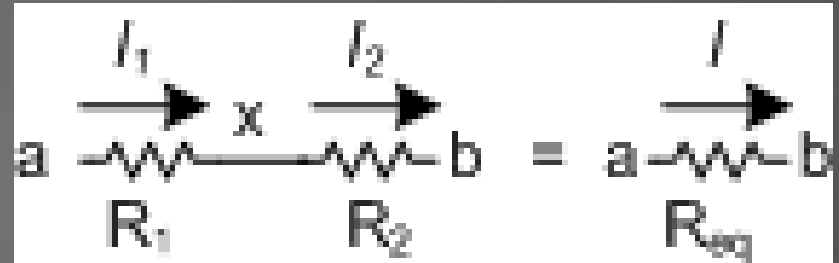- Ohm's Law:
$$I_1 = \frac{a-x}{R_1}$$
$$I_2 = \frac{x-b}{R_2}$$



- KCL: $I = I_1 = I_2$

- Solve for I :
$$I = \frac{a-b}{R_1 + R_2}$$

- Hence, $R_{eq} = R_1 + R_2$

Series Resistors

- In general, any collection of resistors in series is equivalent to a single resistor with a value equal to the sum of the resistances.

Example


- What is the equivalent resistance of the circuit below?
- A) $300\ \Omega$
- B) $200\ \Omega$
- C) $100\ \Omega$
- D) $33\ \Omega$



Parallel Resistors

- Two resistors in parallel are equivalent to one smaller one

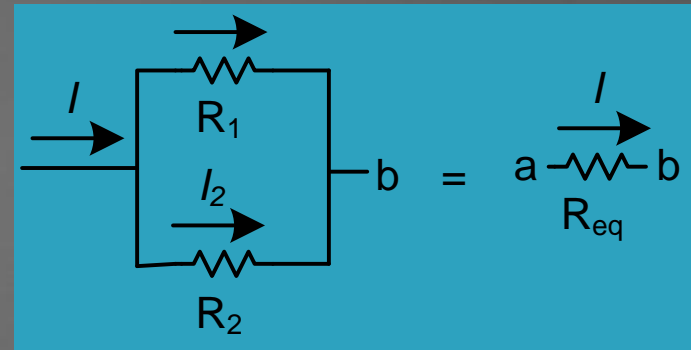- Ohm's Law:
$$I_1 = \frac{a-b}{R_1}$$
$$I_2 = \frac{a-b}{R_2}$$




- KCL: $I = I_1 + I_2$

- Solve for I :
$$I = \frac{a-b}{R_1} + \frac{a-b}{R_2} = \frac{a-b}{\frac{R_1 R_2}{R_1 + R_2}}$$

- Hence, $R_{eq} = R_1 R_2 / (R_1 + R_2) \equiv R_1 \parallel R_2$

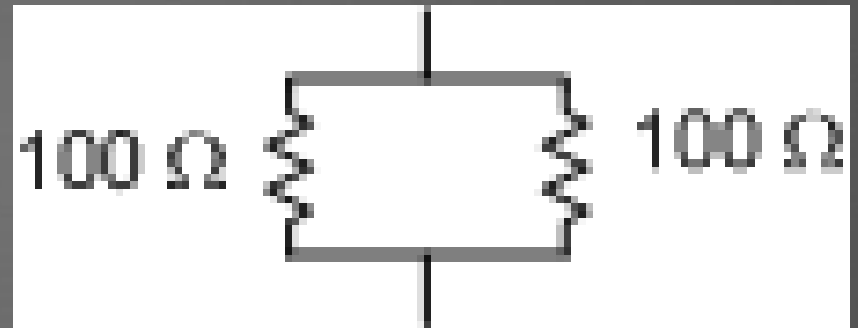Example

- What is the equivalent resistance of the circuit below?
- A) $200\ \Omega$
- B) $100\ \Omega$
- C) $50\ \Omega$
- D) $33\ \Omega$



Example


- You have a large drawer of $100\ \Omega$ resistors, but you need a $250\ \Omega$ resistor. Invent a circuit with the required resistance.

Power

- The amount of energy flowing through a circuit per time.
- Unit: Watts
 - (Watts= Joules / Sec, $W = J/s$)
- Technically:
 - $P = dE/dt$

James Watt

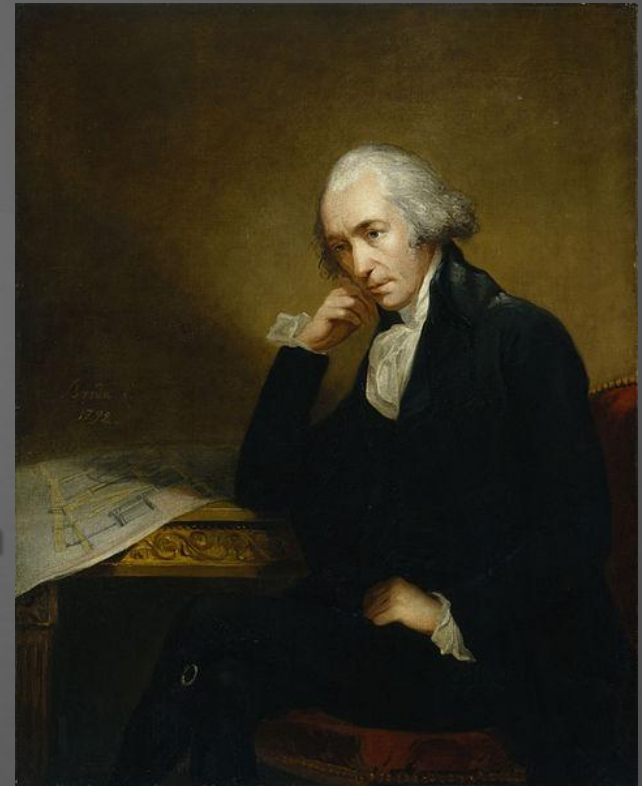- 1736-1819
- Scottish engineer and inventor
- Home schooled
- Revolutionized steam engines
 - Condenser improved power generation



en.wikipedia.org/wiki/File:Watt_James_von_Breda.jpg


Power

- The power dissipated in a component is $P = IV$
 - Derivation:
 - $E = QV$ because Volts = Joules / Coulomb
 - $dE/dt = (dQ/dt) V$ differentiate both sides, assuming V const
 - $P = IV$ dE/dt is power, dQ/dt is current
- $E = QV$
 - For a resistor, V and I are related by Ohm's law, $V = IR$
 - Hence, $P_{\text{resistor}} = I^2R = V^2/R$

Is this a paradox that P is directly and inversely proportional to R ?

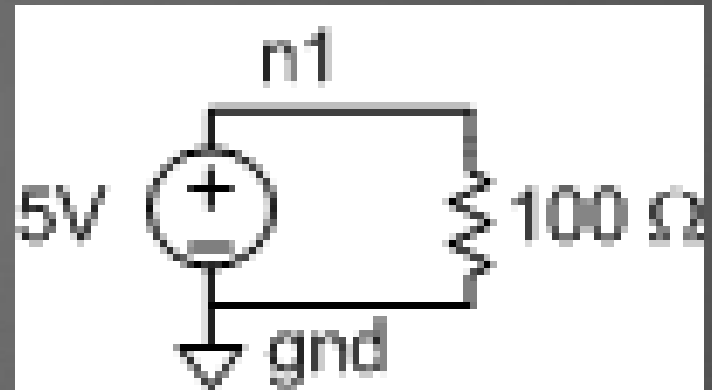Example

- How much power is delivered to the resistor?
- A) 2500 W
- B) 0.25 W
- C) 0.04 W
- D) 0.01 W



Open Circuit

- An open circuit is a circuit with no connection
 - Usually where a connection was intended
- Resistance = ∞
- No current flows

Short Circuit

- An short circuit is a circuit where two nodes are connected
 - Usually where a connection was NOT intended
- Resistance = 0
- Ex: short circuit across a power supply causes huge amounts of current to flow, might blow a fuse or start a fire!

Multimeter

- Multimeters measure:
 - Voltage (voltmeter)
 - Current (ammeter)
 - Resistance (ohmmeter)
- Some do autoscaling while cheaper ones require that you choose the right scale



fluke.com

Voltmeter

- Place meter in parallel with circuit
- Meters may be digital or analog
 - Most today are digital for cost, accuracy
- Digital:
 - A/D converter
- Analog:
 - Galvanometer
 - Resistor in series with a coil of wire in a fixed magnetic field
 - Current through coil creates a torque that rotates the coil and deflects a needle

Ammeter


- Place meter in series with circuit
- Meter includes small precision internal resistor
 - Measure voltage across the resistor
 - Deduce current
- Most multimeters have a separate terminal for measuring current
- Fuse in meter will blow if the current is too large

Ohmmeter

- Place in parallel with the resistor being measured
- Apply a small known voltage or current to the resistor
- Measure the current or voltage that flows
- Deduce resistance from Ohm's Law
- Unreliable if the resistor is in situ in a live circuit that distorts the measurements

Power Demo

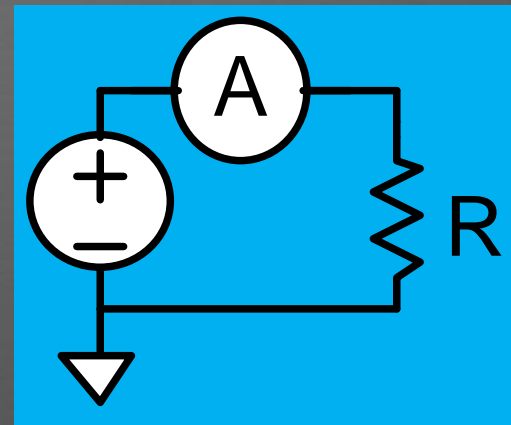- Resistors are rated for a certain amount of power
 - Typical small resistors are $\frac{1}{4}$ Watt
 - Resistors can overheat and change if power is exceeded
- Ex: $5\ \Omega$ resistor connected to a variable power supply
 - Use ammeter to measure current




- Plot I vs. V ; compute P and R

A Caution about Modeling

- We have assumed that our components are ideal.
 - This is not a bad approximation for electrical components in their usual operating range.
 - If you push them too hard, they violate the assumptions.
 - Mechanical and chemical systems rarely match ideal models as electrical systems.


Power Supply Model

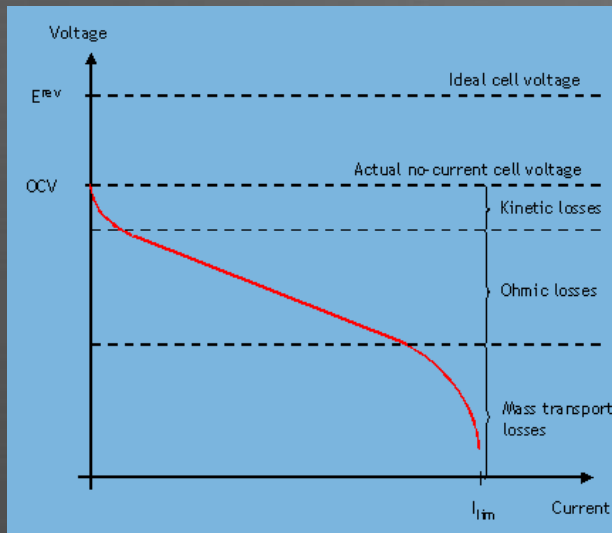- A typical power supply is not an ideal voltage source
 - Can provide a finite amount of output current
 - Voltage droops as you pull more current
 - Examples: fuel cell, solar cell, battery



Power Supply Model

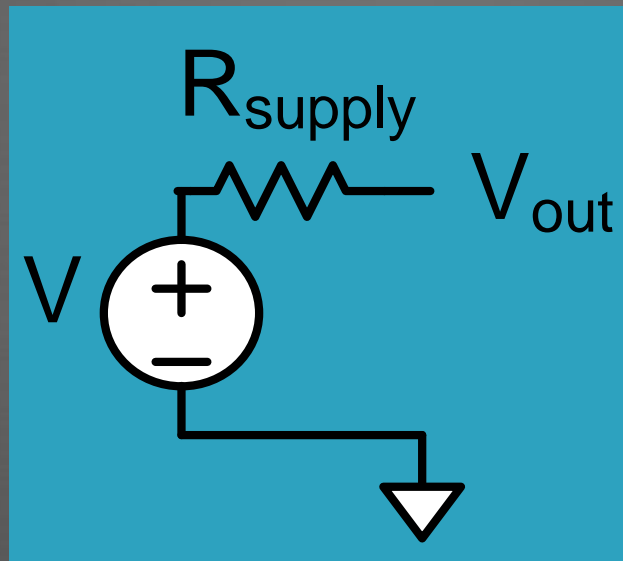
- Model power supply as ideal voltage source in series with nonzero output resistance.



Loaded Nonideal Supply

- Suppose the load on the supply is varied. How does current and voltage change? How does power supplied to the load resistor change?
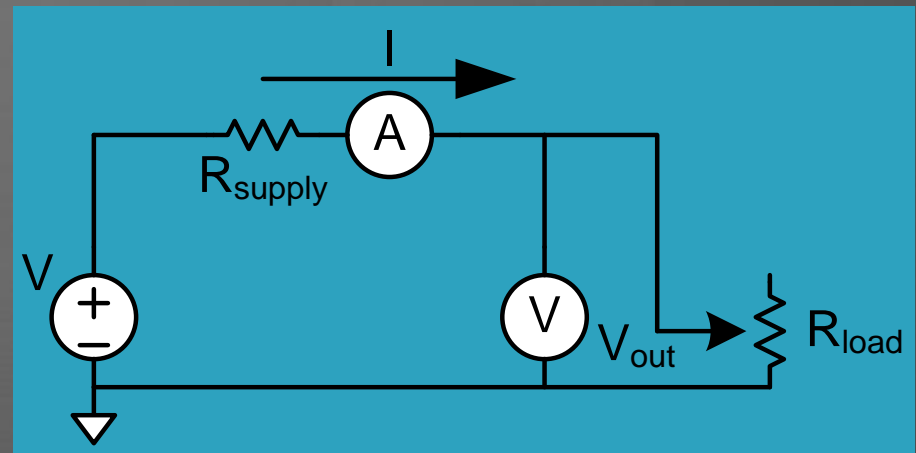
$$I = \frac{V}{R_{supply} + R_{load}}$$
$$V_{out} = V \frac{R_{load}}{R_{supply} + R_{load}}$$
$$P_{load} = \frac{V_{out}^2}{R_{load}} = V^2 \frac{R_{load}}{(R_{supply} + R_{load})^2}$$



Matched Load

- What load resistance draws maximum power? How much power?

$$P_{load} = \frac{V_{out}^2}{R_{load}} = V^2 \frac{R_{load}}{(R_{supply} + R_{load})^2}$$

$$\frac{dP_{load}}{dR_{load}} = \frac{(R_{supply} + R_{load})^2 - R_{load} \cdot 2(R_{supply} + R_{load})}{(R_{supply} + R_{load})^4} = 0$$

$$R_{supply}^2 + 2R_{supply}R_{load} + R_{load}^2 - 2R_{supply}R_{load} - 2R_{load}^2 = 0$$

$$R_{load} = R_{supply}$$

$$V_{out} = V / 2$$

$$P_{load} = \frac{V^2}{4R_{load}}$$

Open and Short Loads

- Open Circuit Load

- $R_{\text{load}} = \infty$
- $V_{\text{out}} = V$
- $I = 0$
- $P = 0$


- Short Circuit Load

- $R_{\text{load}} = 0$
- $V_{\text{out}} = 0$
- $I = V / R_{\text{supply}}$
- $P = 0$

Example

- A fuel cell has an open circuit voltage of 0.9 V and an effective output resistance of $2\ \Omega$. How much power can it deliver to a matched load?
- A) 101 mW
- B) 810 mW
- C) 405 mW
- D) 1620 mW

Fuel Cell Model Predictions

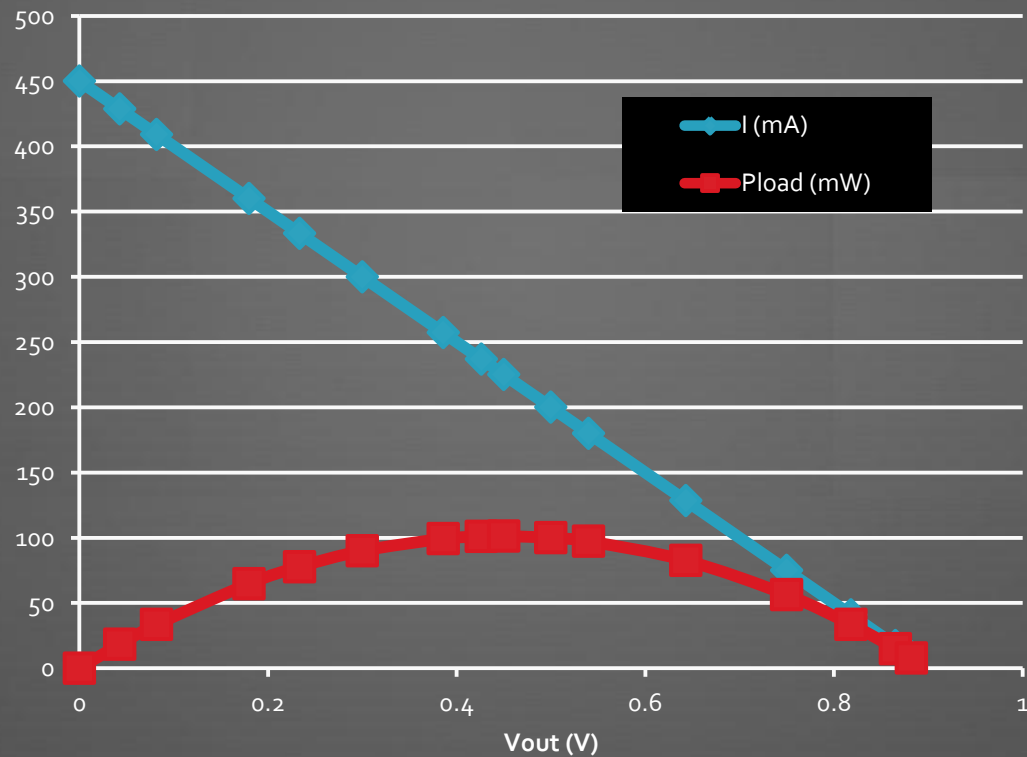

Nonlinear Circuits

- In a nonlinear circuit, voltage and current are not proportional
- But nevertheless $P = IV$
- Ex: Fuel cell

