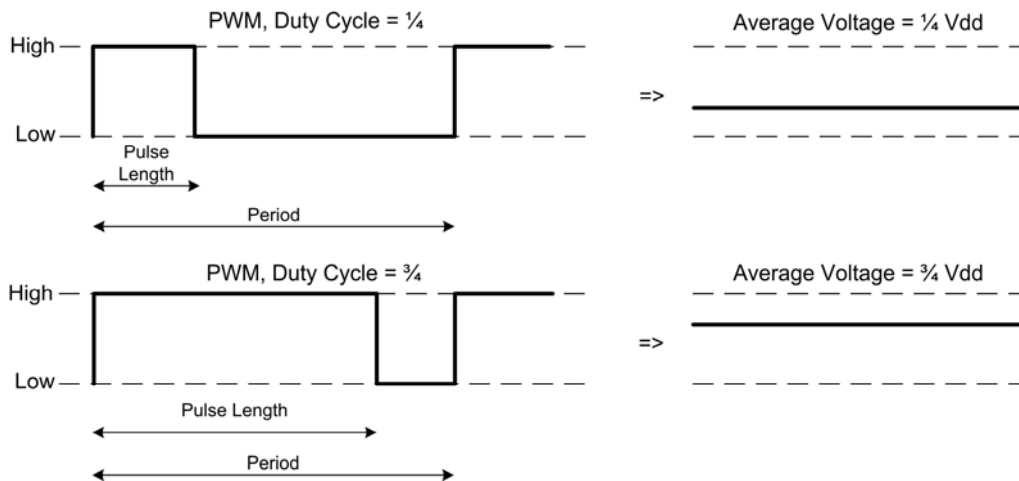


## Introduction

Three types of motors are applicable to small projects: DC brushed motors, stepper motors, and servo motors. DC brushed motors simply rotate in a direction dependent on the flow of current. Servo motors move to an angular location dependent on the duty cycle of a pulse width modulated (PWM) input signal. Stepper motors rotate in discrete steps. Motors require large currents to operate, exceeding the drive of most digital logic; therefore, H-bridges are used to supply the high currents under the control of digital signals. Motor design and torque/speed considerations are beyond the scope of this documentation.

## Pulse Width Modulation

Torque of most electrical motors is dependent on the power ( $P = I * V$ ) being used to drive the motor. The easiest solution to vary the power of a digital signal is by using a method called Pulse Width Modulation (PWM). A pulse width modulated signal is a square wave, which, when sufficiently fast, creates an effective average voltage on the line. The ratio of high pulse length to period of the signal is called the duty cycle. By varying the duty cycle you can vary the average voltage. Hence, to give the motor more power, you should increase the duty cycle, as shown in Figure 1.




**Figure 1: Pulse Width Modulation**

The PIC18F452 includes a built-in PWM module that supports a period up to 819.2  $\mu\text{s}$  (see page 122 of the PIC datasheet for how this is calculated) using a 20 MHz oscillator (409.6  $\mu\text{s}$  with a 40 MHz oscillator). Sometimes the period for a PWM you wish to generate is too long for the PWM module. To work around this limitation you can use the PIC18F452's interrupt system to generate the PWM signal. An interrupt request handler (a procedure executed when an interrupt occurs) is called when a timer overflows, giving a predictable delay between calls to the handler. The interrupt request handler would then compare a "count" with a maximum period length variable and a high pulse length variable. A pin would be driven high when count is less than the high pulse

length variable and the count is reset when it exceeds the maximum period length. Both methods free the majority of processor time for other tasks. The PWM module drives a single pin, PORTC<2>. With the interrupt driven method you can drive any pin, as well as do more complex tasks beyond generating a simple PWM signal. Examples of both methods are given in the sample code section.

## H-Bridges

The PIC output drivers are only rated for 25 mA, and most other digital chips provide less than 20mA. Motors draw more current than a PIC can provide. One exception is the servo, which has separate control and power inputs, so current draw is not an issue. Also, motors may operate at different voltage levels than a PIC. A common drive circuit, called an H-bridge, can be used to provide higher current and isolate voltage levels. An H-bridge consists of four switches/transistors/relays/etc: two switches go to VCC and two go to ground, as shown in Figure 2. By closing switches 1 and 4, current flows through the motor from left to right in the figure, hence the motor will turn one direction. By closing switches 2 and 3, the motor will turn the other direction. To apply braking to the motor, by induction, close switches 2 and 4. To allow the motor shaft to rotate freely, do not close any switches. The voltage VCC of the h-bridge may be larger than the logic levels of the control device you are using.

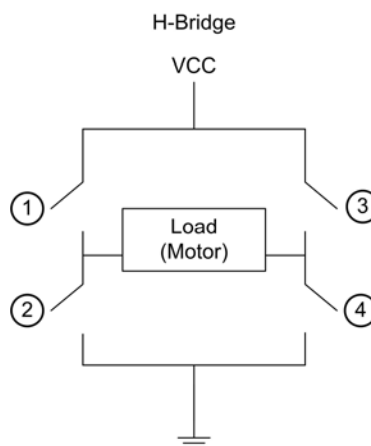

**Figure 2: H-Bridge**

H-bridges are often packaged in an IC form. Some come in half-h driver form, which is one side of an h-bridge (i.e. will drive a lead high, low, or high-impedance). The SN754410NE has four half-h drivers, which can be paired, so it can drive two motors with two separate H-bridges. It is rated for 1.1A continuous output at up to 36V. Although the input pins are specified for 4.5V control, they are also specified for TTL levels, and so appear to work at 3.3V. The SN754410NE has four input pins and two enable pins. When an enable pin is high, the two corresponding drivers are high or low depending on their input pins (when input pin is high, driver is high. Otherwise driver is low). When the enable pin is low, both drivers controlled by the enable pin are high-impedance.

## DC Brushed Motors

Many motors use coils at fixed symmetrical angles to attract magnets on a motor shaft to different positions. When current is applied to the coils in the correct sequence, rotation occurs. A DC brushed motor automatically supplies current to the correct coils, often by using spring-loaded “brushes” which touch a contact, on the shaft, connected to a coil. As the shaft rotates, the contact the brush touches changes, keeping the shaft rotating without the need for more complex control circuitry. All that is needed to drive a brushed motor is current flow through the leads of the motor, as shown in Figure 3. Brushed motors are ideal for situations where high-speed/torque rotation is needed. However, the motor does not directly indicate velocity or shaft position. (A device called a *shaft encoder* may be used to optically determine the amount of rotation of the motor shaft, to determine the shaft position or velocity, but it is beyond the scope of this documentation.)

 


Figure 3: Driving a DC Brushed Motor

The speed/torque of the motor is determined by the electrical power ( $I \cdot V$ ) supplied and the direction of rotation is determined by the direction that current flows through the motor. To control the speed using the PIC, pulse width modulation is used. One motor lead is connected to `PORTC<2>`, which is the output for the PIC’s built-in PWM generation module. The duty cycle determines the average voltage delivered to the motor and hence the speed of the motor. If speed control is not needed, or interrupt-based PWM is used, you do not need to use the PIC’s built-in PWM and another pin may be used to control the motor.

To control directions, an arbitrary port, in the example code `PORTC<1>`, is connected to the other lead of the motor. Normally `PORTC<1>` is low, causing current to flow through the motor from `PORTC<2>` (when high) to `PORTC<1>`. When `PORTC<1>` goes high, current instead flows from `PORTC<1>` to `PORTC<2>` (when low), effectively reversing the direction of the shaft rotation.

Since the RS-550PF motor draws up to 29.1 A at 5VDC to 12VDC, more current than the PIC can provide, it is connected to a quadruple half-h driver, as shown in Schematic 1 on page 7 in the example schematic section. It is often desirable to give the motor more current than a single H-bridge can provide, so you may use multiple H-bridges attached to the same lead, or, of course, use a more powerful H-bridge.

## Stepper Motors

Stepper motors have coils, connected directly to the external motor leads, which align the motor shaft to discrete positions or “steps”. To rotate the motor shaft in a direction,

current must be sent through the motor leads in proper sequence. The stepper motor demonstrated in this paper is a bipolar stepper motor, which has two coils, perpendicular to each other, and multiple permanent magnets on the shaft. The Airpax LB82773-M1 stepper motor rotates 7.5 degrees per step. Stepper motors are ideal when precise control over amount of rotation is needed, but provide less speed and torque than a DC brushed motor would.

The sequence in which the motor leads are driven is called the stepping sequence. There are different stepping sequences depending on different factors such as power consumption, torque, and granularity of angle. For example, with a half-step stepping sequence, two leads could be driven simultaneously, which provides more torque than a simple one-phase sequence, which is discussed below, but requires more power to operate. The speed of rotation is determined by the delay between changing steps in the sequence. When starting at maximum speed the shaft will not rotate into position before the sequence progresses a step, causing the shaft to jitter but not rotate, therefore you should not start the sequence at maximum speed but instead gradually increase the stepping speed. To reverse direction of rotation just reverse the sequence. For this documentation we implement a simple one-phase (only one coil has current at a time) sequence. The stepping sequence as implemented in the sample code is shown in Table 1. As power is switched from one coil to another coil the motor moves a step. The process repeats causing continuous rotation in the direction indicated.

|        | ← Counter-Clockwise |     | Clockwise → |     |
|--------|---------------------|-----|-------------|-----|
|        | 1                   | 2   | 3           | 4   |
| Grey   | ON                  | OFF | OFF         | OFF |
| Black  | OFF                 | OFF | ON          | OFF |
| Red    | OFF                 | ON  | OFF         | OFF |
| Yellow | OFF                 | OFF | OFF         | ON  |

Table 1: Sample Airpax LB82773-M1 Stepping Sequence


Controlling a stepper motor using the 18F452 PIC is achieved using interrupts. First an initial bit-pattern is loaded onto PORTD. After a specific delay, which in the sample code is determined by the *speed* register, PORTD is rotated right or left depending on the direction desired of the motor shaft. For more complex stepping sequences, as discussed earlier, either modify the bit pattern on PORTD or implement an algorithm to determine which leads should be driven.

## Servos

Servos are motor devices which can be positioned to a specific absolute angle. The servo can be viewed as a DC motor with a built-in controller. Internally servos use a device such as a potentiometer to measure the angle of the shaft, by using the voltage from the potentiometer. The servo's circuitry internally generates a signal from the voltage of the potentiometer, and then compares it to the input signal and matches the two by moving the DC motor accordingly. The speed at which the servo moves to the new position is proportional to the distance it needs to travel, so as the servo becomes closer to the target angle it will gradually slow. Servos are similar to stepper motors in that a specific amount of rotation can be achieved, but servos allow you to control an absolute angular

position instead of a relative amount of angular rotation. Additionally, servos often have finer granularity of amount of rotation than stepper motors, but are limited to a maximum angle of rotation, often not exceeding 360 degrees. Servos are ideal when absolute positioning of a shaft is desired.

The HS-322HD servo has three pins: VCC (Red), GND (Black), and SIGNAL (Yellow). Typically servos require a PWM signal with a 20ms period of a pulse length between 0.9ms and 2.1ms. 0.9ms corresponds to zero angle and 2.1ms corresponds to the maximum angle, as shown in Figure 4. Therefore, middle position is 1.5ms (the average of the pulse lengths). The HS-322HD has a maximum angle of 180 degrees. Servos only move a finite angular amount per cycle of the signal, so multiple cycles must be sent before the servo arrives at the correct angle. The number of cycles needed is dependent on the distance it must move. The servo will resist change away from the designated angle as long as signal is applied. The servo draws its power from VCC and the signal needs no more than 20 mA of current while running at 3VDC to 5VDC. Hence, it can be driven directly by the PIC without the need of an H-bridge. The voltage of the signal appears to not affect the angular position of the servo, as long as the voltage is within the 3VDC to 5VDC range. The HS-322HD specifications define VCC to be between 4.8VDC and 6VDC (though the servo appears to work at 3.3VDC). In the sample code the PWM is generated using interrupts, therefore the signal input on the servo can be connected to any arbitrary output pin on the PIC.

 

**Figure 4: Controlling a HS-322HD Servo with PWM**

**Specifications**

PIC18CXX2 Data Sheet

<http://ww1.microchip.com/downloads/en/DeviceDoc/39026c.pdf>

Mabuchi RS-550PF VDC Motor

<http://cvhsrobotics.org/files/2003/mabuchi.pdf>

Hitec HS-322HD Servo Motor

[http://www.hitecrd.com/Servos/spec\\_sheets/HS322HD.pdf](http://www.hitecrd.com/Servos/spec_sheets/HS322HD.pdf)

Airpax LB82773-M1 Stepper Motor

<http://www.allelectronics.com/pdf/32.pdf>

Texas Instruments SN754410NE Quadruple Half-H Driver

<http://www-s.ti.com/sc/ds/sn754410.pdf>

**Supplier**

| Part                 | Vendor          | Part #        | Price   |
|----------------------|-----------------|---------------|---------|
| Mabuchi RS-550PF     | All Electronics | DCM-104       | \$3.50  |
| Airpax LB82773-M1    | All Electronics | SMT-75        | \$2.75  |
| SN754410NE H-Bridge  | Digi-Key        | 296-9911-5-ND | \$1.88  |
| Hitec HS-322HD Servo | Hitec RCD USA   | HS-322HD      | \$11.49 |

[www.allelectronics.com](http://www.allelectronics.com)

[www.digikey.com](http://www.digikey.com)

[www.hitecrd.com](http://www.hitecrd.com)

**Additional Resources**

PICmicro® DC Motor Control Tips ‘n Tricks

<http://ww1.microchip.com/downloads/en/DeviceDoc/41233A.pdf>

Brushed DC Motor Fundamentals

<http://ww1.microchip.com/downloads/en/AppNotes/00905a.pdf>

Stepper Motor Theory – Haydon Switch and Instrument

<http://www.hsimotors.com/technical-data/theory.htm>

Jones on Stepping Motor


<http://www.cs.uiowa.edu/~jones/step/>

What’s a servo: A quick tutorial


<http://www.seattlerobotics.org/guide/servos.html>

### Schematics


#### Schematic 1: Brushed DC Motor

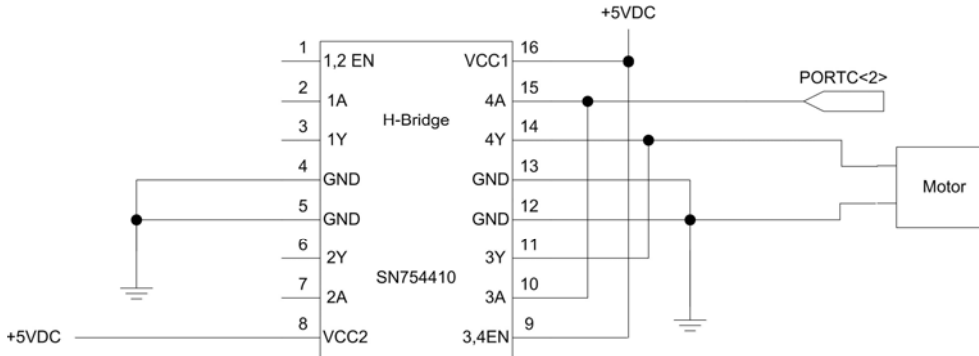

#### Schematic 2: Stepper Motor

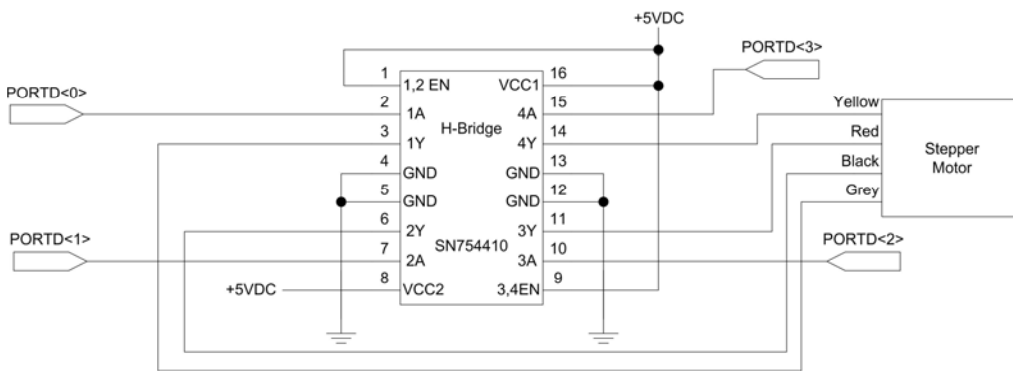

#### Schematic 3: Servo

 

## Sample Code

### Listing 1: brushed.asm

```
; brushed.asm: Demonstrates how to drive a dc brushed motor.
; 2005 Nathaniel Pinckney <npinckney@hmc.edu>
; Takes advantage of 18F452's builtin PWM module. Assumes 20Mhz clock.
;
; PORTC<1> is always 0 or 1, which will set direction by flipping polarity.
; PORTC<2> is controlled by PWM module.

LIST p=18F452
include "p18f452.inc"

org 0x0

start:
    clrf TRISC           ; PORTC as output

    call init_pwm
    movlw b'01100100'   ; Speed. MSB is direction.
    btfss WREG,7        ; Check direction.
    bcf PORTC,1         ; Set direction.
    btfsc WREG,7
    bsf PORTC,1
    btfsc WREG,7        ; Also, if opposite direction,
    negf WREG           ; negate speed so pulse length is the same
    rlc WREG            ; Multiply by 2, since speed is really on 7-bits.
    movwf CCP1L        ; Move into PWM module's pulse length reg.
    goto $             ; $ is current address. Loop endlessly.
                    ; (Your code would replace goto loop.)

; Initializes the PWM module for DC Brushed motor control.
init_pwm:
    setf PR2           ; Give us a period of (255+1)*4 cycles.
    clrf CCP1L        ; MSB of duty cycle, initially 0.
    movlw b'00000100' ; 0 postscale, PWM on, 0 prescale
    movwf T2CON
    movlw b'00001100' ; LSB of duty cycle, PWM Mode
    movwf CCP1CON
    return

end
```



**Listing 2: stepper.asm**

```

; stepper.asm: Control a stepper motor.
; 2005 Nathaniel Pinckney <npinckney@hmc.edu>
; Assumes 20Mhz clock.
; Overview:
; * Configure interrupt on TMR0 overflow. This slows us down some.
; * Configure and enable TMR0.
; * Move a bit pattern of wires activated to PORTD. To cycle through
; wires in sequence all we must do is rotate PORTD.
; * Interrupt handler counts number of overflows in 'count' register and
; compares to 'speed' register. If count > speed then rotate
; our PORTD which will activate correct wires in sequence. Also,
; count is then reset.
; * Speed's MSB is the direction. Rest of the bits are multiplied by 2
; to determine delay.

LIST p=18F452
include "p18f452.inc"

; Registers
W_TEMP      equ 0x01      ; Save state, used in ISR.
STATUS_TEMP equ 0x02      ; Save state, used in ISR.
count       equ 0x03      ; Keeps track for timing/speed.
speed       equ 0x04      ; Speed/delay of stepper motor.

org 0x0      ; Reset vector.
goto start
org 0x08     ; Interrupt vector.
goto TMR0_ISR ; goto TMR0 ISR (Interrupt Service Request)

start:
clrf TRISD      ; PORTD is output.
movlw b'11100000' ; Set our speed/delay. MSB is direction.
movwf speed

movlw b'10100000' ; Enable all interrupts, and TMR0 overflow as
                 ; an interrupt.
movwf INTCON
movlw b'11000000' ; Setup TMR0, 8-bit mode, no prescaler.
movwf T0CON

movlw b'00010001' ; Stepping sequence pattern.
movwf PORTD

goto $          ; $ is current address. Loop endlessly.
                 ; (Your code would replace goto loop.)

TMR0_ISR:      ; TMR0 ISR Handler.
movwf W_TEMP   ; Save WREG
movff STATUS,STATUS_TEMP ; Save Status
incf count     ; Increment count.
movf speed,w
rlcf WREG      ; Shift speed by 1 (multiply by two)
cpfsqt count   ; Check if we hit our upper-bound of count.
goto _then
clrf count     ; Reset count
btfsc speed,7 ; Rotate our output in direction
rlncf PORTD    ; determined by MSB of speed.
btfss speed,7
rrncf PORTD

_then:
bcf INTCON,TMR0IF ; We handled the interrupt.
movf W_TEMP,w     ; Restore WREG
movff STATUS_TEMP,STATUS ; Restore Status
retfie           ; Return from interrupt handler.

end

```

**Listing 3: servo.asm**

```

; servo.asm: Control a servo.
; 2005 Nathaniel Pinckney <npinckney@hmc.edu>
; Assume 20Mhz clock.
; Overview:
; * Configure interrupt to trigger on TMR0 overflow.
;   Interrupt will trigger approximately every 0.1ms.
; * Configure TMR0.
; * On interrupt check if pwm >= pwm_count, if true turn PORTD<7> on,
;   else turn PORTD<7> off.
; * Check if we reach 20ms by comparing pwm_count to 200.
;   If so reset to 0.

LIST p=18F452
include "p18f452.inc"

; Constants to test with.
ANGLE      equ .15          ; This is really pulse length in 0.1 ms, which
                           ; translates to angle. 15 (1.5 ms) is center position,
                           ; 9 (0.9 ms) is ~0 degrees, and 21 (2.1 ms) is ~180
                           ; degrees.

; Registers
W_TEMP     equ 0x01         ; Save state, used in ISR.
pwm_count  equ 0x02         ; Keeps track if TMR0 overflows, for pwm generation.
pwm        equ 0x03         ; Pulse length of pwm.

org 0x00    ; Reset vector.
goto start
org 0x08    ; Interrupt vector.
goto TMR0_ISR

start:
clrf TRISD      ; PORTD is output.
movlw ANGLE     ; Pulse length (/ a period of 200)
movwf pwm

movlw b'10100000' ; Enable all interrupts, and TMR0 overflow as an
                  ; interrupt.
movwf INTCON
movlw b'11000000' ; Setup TMR0, 8-bit mode, no prescaler.
movwf TOCON

goto          $      ; $ is current address. Loop endlessly.
                  ; (Your code would replace goto loop.)

TMR0_ISR:
movwf W_TEMP     ; TMR0 ISR (Interrupt Service Request) Handler.
                  ; Save WREG

movf  pwm_count,w
cpfslt pwm        ; Compare pwm to pwm_count.
bsf  PORTD,7      ; >= PORTD<7> = 1
cpfsgt pwm
bcf  PORTD,7      ; <= PORTD<7> = 0

incfsz pwm_count ; incfsz does not modify STATUS (unlike incf)
movlw .200       ; and since we don't save STATUS...
cpfslt pwm_count ; 200 is selected because TMR0 overflows
clrf  pwm_count  ; once every 0.1ms, and we want a 20ms period.

bcf  INTCON,TMR0IF ; We handled the interrupt.
movf W_TEMP,w      ; Restore WREG
retfie             ; Return from interrupt handler.

end

```