

Introduction to CMOS VLSI Design (E158)

Lecture 20: Low Power Design

David Harris

Harvey Mudd College

David_Harris@hmc.edu

Based on EE271 developed by Mark Horowitz, Stanford University

Overview

Reading


W&E 4.7.1 - 4.7.3 Power Dissipation

Introduction

In addition to performance, power is becoming a significant concern for designers. CMOS was originally a low power technology, but it is not low power any more. CMOS chips can dissipate 50Watts. This power comes from charging and discharging capacitors and is fundamental to all circuits that drive wires. This lecture will look at power dissipation in CMOS circuits, and discuss various proposed methods for reducing the power. The key areas are technology, and algorithm. Both can make a huge difference in power.

Power

 Trend in CMOS power dissipation is a little frightening



Power seems to be proportional to area and frequency

Power Issues

Three reasons that power is important:

1. Hard to get large current into a chip (Amps of current)

50W at 2.5V is 20Amps

2. Cheap device

Must use plastic package, in a low-cost box

No fans, so thermal resistance is high (35°C/Watt)


Power must be under 2W

3. For a portable system

Need to carry the energy (Power * Time) you use

Energy is heavy (20 Wh / lb)

Lower power means less battery weight

 

Power

Power is current times voltage – iV


There are two types of current that need to be considered

- Static
 - Current caused by a resistor between the supply
 - nMOS style circuits
 - Current easy to estimate, V/R
- Dynamic
 - Current used to charge and discharge capacitors
 - Current depends on how often the capacitor changes state
 - Dominant current in CMOS chips (sometimes only current)

Static Power

Current flows whenever the output is low

 - Assume that the output is low 50% of the time.




In a 1μ technology, the current is $170\mu\text{A}/\mu$ of width for the pMOS. This means that the current for a 4:2 device would be around $340\mu\text{A}$, and the power would be 1.7mWatts (on average) for the gate. 10K gates -- 17Watts

- Sometimes do this in CMOS to get large fanin gates.

Also occurs in analog like circuits


Memory, PLL, V_{bb} generators, etc.

 Leakage is another source of static power




Dynamic Power

 Takes current from the power supply to charge up the capacitor. When the capacitor is discharged the current does not get put back to the supply. The amplitude of the current spike when charging the capacitor depends on the resistance of the switch ($i = V/R$). But the total charge required does not depend on the switch, since must be equal to $C\Delta V$.



Dynamic Power

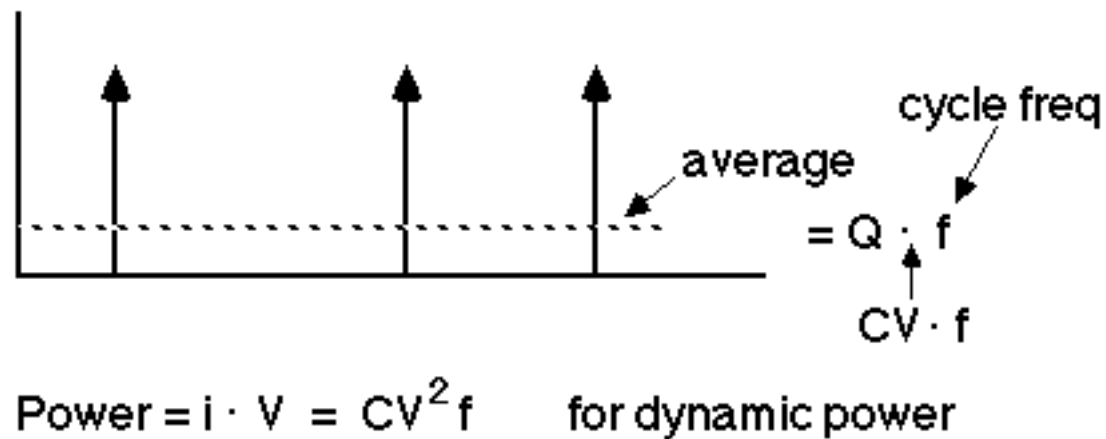
The average current that the 'capacitor' needs is just equal to the charge required to switch the capacitor time the number of times per second the capacitor switches. The latter term is just the frequency that the line is toggling at.



This is a fundamental power that is needed to switch capacitors (without inductors).

Dynamic (Short Circuit) Power

 Short Circuit current occurs when the input of a gate is in transition and both the P-channel and N-channel devices are conducting at the same time. (see W&E 4.7.3 for derivation)



In general the percentage of the total dynamic power due to the short circuit current is much smaller than that used to charge and discharge the capacitive loads. Very slow rise and fall times on the inputs could however make this current significant, and must be considered for gates at the end of long wires with large RC delays. In a well designed circuit, this current is small. To first order it can be ignored.

Dynamic Power

Total Power

$$P = \sum_n \frac{1}{2} C_n \Delta V V_{dd} \alpha_n F$$

'n' ranges over all nodes
in the circuit

α_n = average number of times that node n transitions/cycle¹

Generally the signal swing is equal to Vdd

$$P = C_{eff} V^2 F$$

Dominate power in CMOS circuits

- Static power is usually pretty small
- If the circuit is idle most of the time, the static power can still be important, since it uses energy whether the circuit is doing anything or not.

1. The 1/2 in the formula is because signal must make two transitions (up and down) for a cycle

Low Power Design

Need to:

- Understand the basic trade-offs
- Make low power a design objective
 - Along with design time, and performance
- Don't be stupid

Find smart ways to reduce power

- Slower is usually lower power
 - CV^2F , lower F lower power
- Need some metrics for low power designs
 - Provides a way to compare designs
 - Which design / style is better
 - What should a designer expect


Metrics - Power

Obvious choice

- Sets battery life in hours, packaging limits

Problem

- Dynamic power proportional to F

 


Often want to do more, not have it take longer

- Comparing the power of two designs can be misleading
- Lower power design could simply be slower

Metric - Energy / Operation

Rather than look at power, look at the total energy needed to complete some operation. Fixes obvious problems with the energy metric, since changing the operating frequency does not change the answer
 
$$\text{Energy/Op} = \text{Power} * \text{Delay/Op} = kC\Delta VV_{dd}$$




The energy is the area under the curve. While this metric looks promising, the problem is that one can decrease the energy/op by doing stuff that will slow down the chip -- like lowering the supply voltage, or using small transistors.

Metric - Energy/Op and Delay/Op

Since lower energy solutions might simply be lower performance, we need to have a metric that includes both energy and performance.

 One solution is to think about a 2-D solution space:




Clearly 'b' is lower power than 'c'. But can we say anything about 'b' and 'd'? While 'd' is slightly lower power, it is also much slower.

Proposal: Energy/Op * Delay/Op

$$\text{Energy} * \text{delay} = \text{Power} * (\text{Delay/Op})^2$$

 Constant energy-delay products are straight-lines in the graph:



Implies one can trade lower energy/op for increased delay

- Try to show you why this is true

Voltage Scaling

Changing power supply voltage:

- Has a large effect on power, since $P = CV^2F$
- Affects performance too

$$t_d = \frac{CV}{k(V - V_{th})^\alpha}$$


Energy * Delay is:

$$ED = \gamma \frac{V^3}{(V - V_{th})^\alpha}$$

(α is between 1-2 and models velocity saturation)

Voltage Scaling

 For quadratic device it is often drawn as:




Looks like this is an important optimal point

- But you should be cautious:

No labels on the graph


Energy-Delay for Quadratic Devices

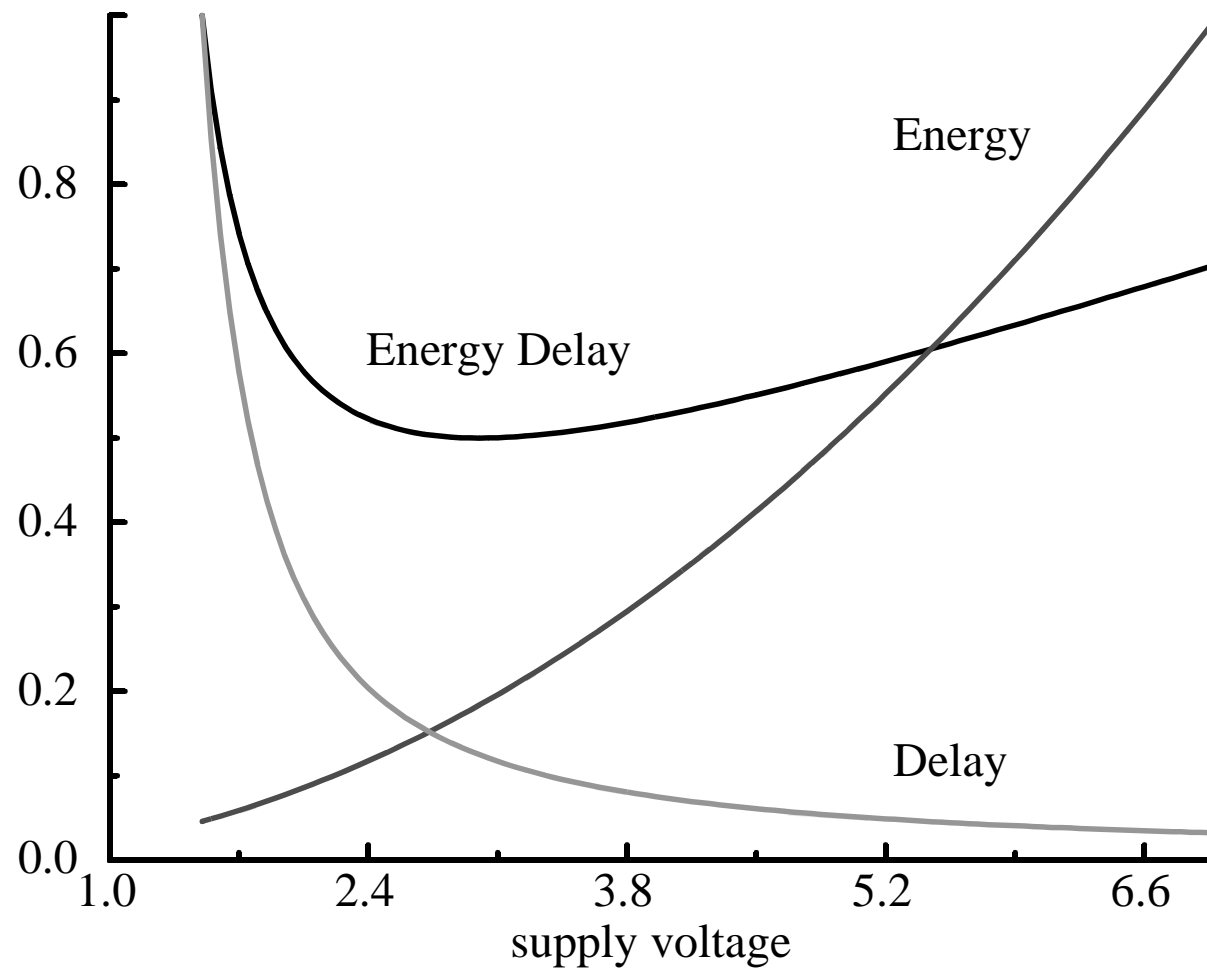

Energy-delay is pretty flat.


Another View of Voltage Scaling

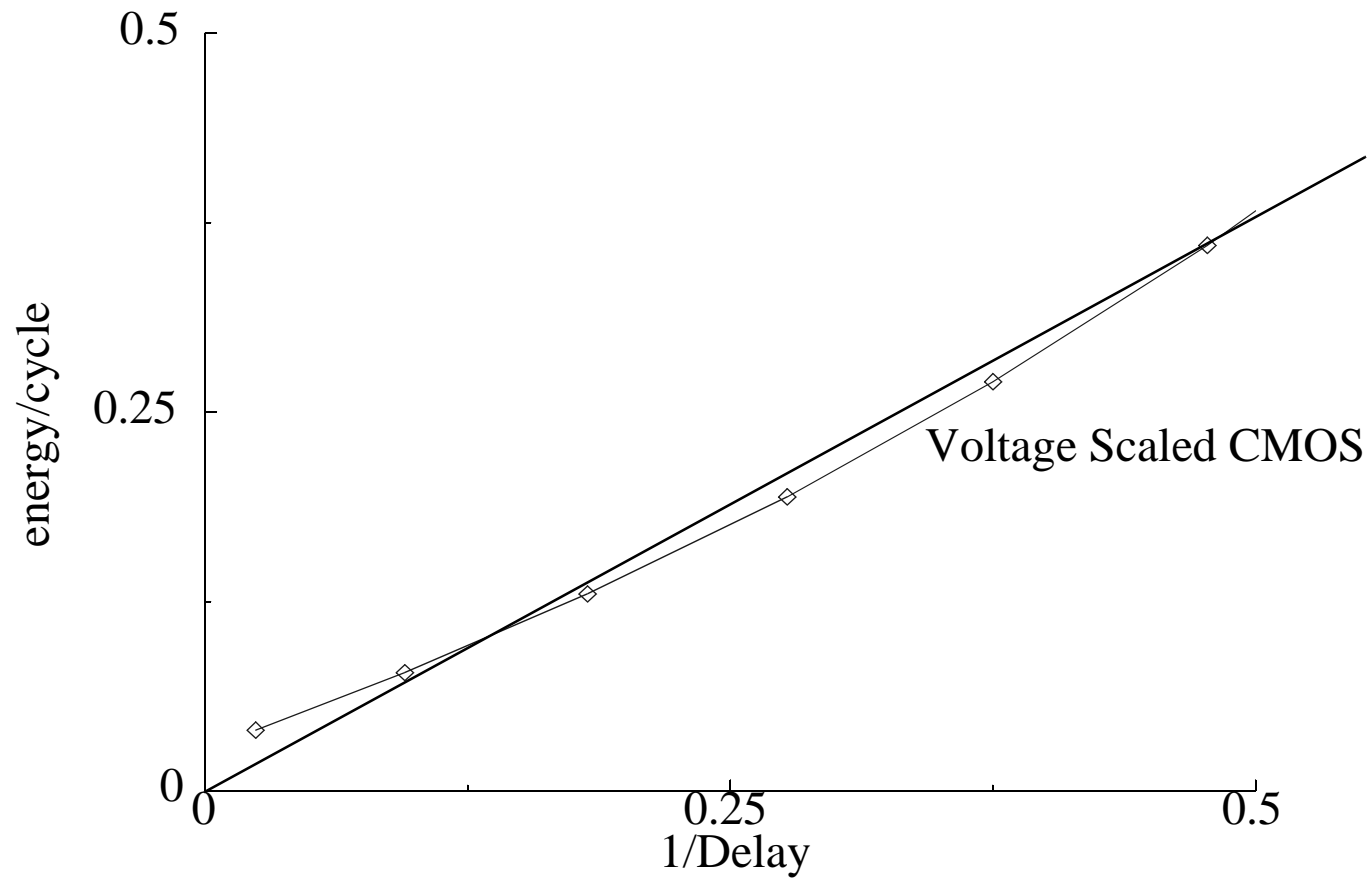Voltage scaling is pretty straight on the Energy 1/Delay plot



Plots energy of quadratic inverter, versus its performance (1/delay)


Energy Delay for 'Real' Devices

 

Data from a real 0.35μ technology.

Voltage Scaling of a Real Device

 E*D product changes by +/- 30% over voltage operating range



With modern technologies, max operating voltages is not very energy efficient

- Reason modern processors are using aggressively scaled supplies

Transistor Sizing


Using smaller transistors is another method of reducing the power

- Power decreases since the low capacitance decreases
- Delay increases since the driving resistance increases


Modeling is a little difficult, since not all path are critical

- Making transistors on non-critical paths smaller is good -- lower power and no delay change

Simple example of critical path changes

 

Sizing Energy Delay

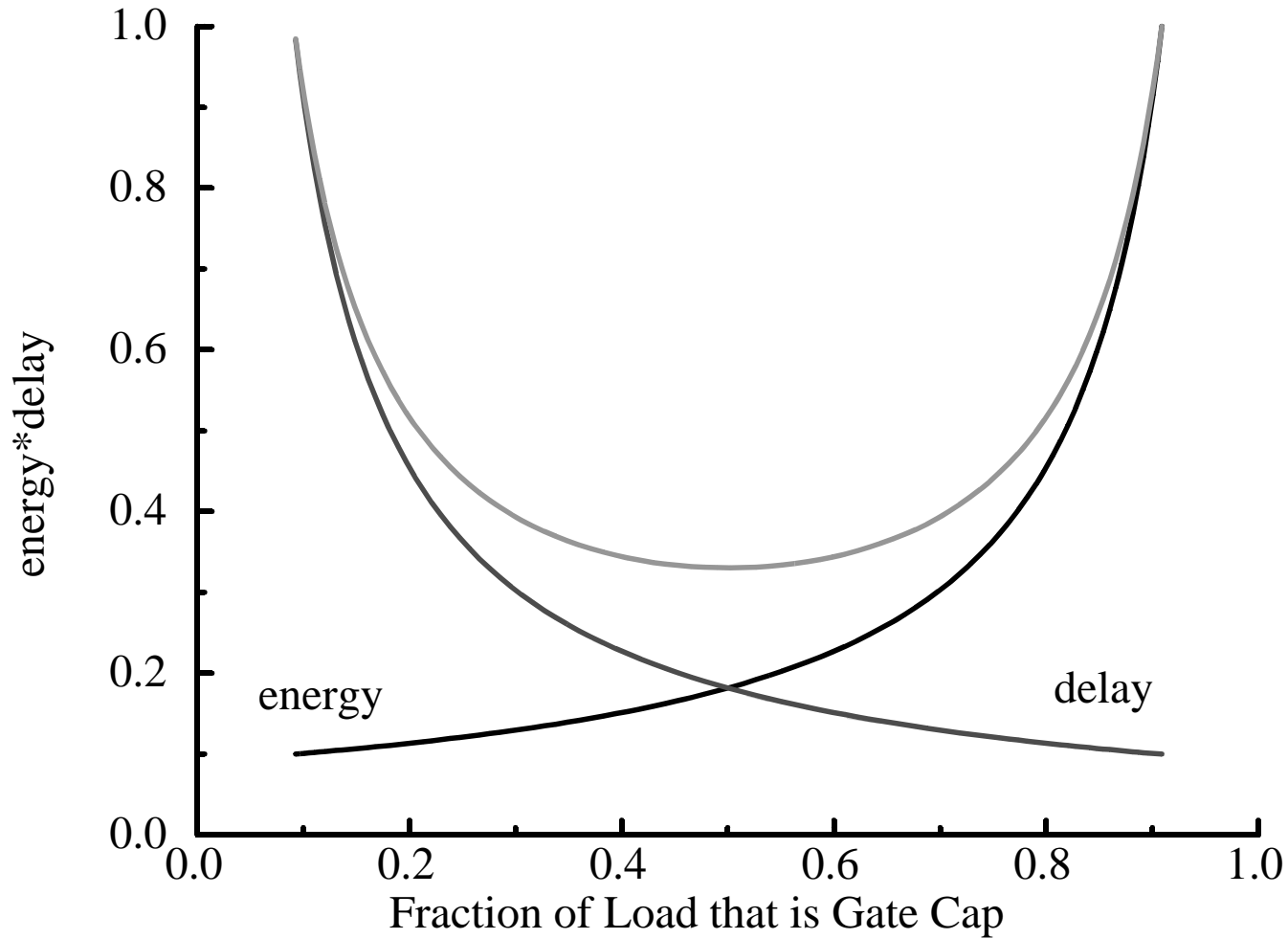

Over a reasonable set of load ratios, the energy-delay is pretty constant

Energy Delay

Good metric

- Models intrinsic trade-off of technology
- Flat for a factor of 10 in voltage scaling
- Flat for a factor of 4 in transistor sizing

Implies

- Optimized Power is proportional to $(1/\text{Delay})^2$
- $1/2$ Speed \Rightarrow Energy/Op = $1/2$, Ops/sec = $1/2$
- Slower peak performance will be lower Energy/Op

MIPS/Watt should be smaller for slower processors

- Performance is expensive!

Lower Energy Delay

Some techniques:

- Better fabrication technology

Helps both performance and energy

Mostly need to normalize it out

- Dynamic Power Reduction

Selective Activation

Swing Reduction

- Problem reformulation

This is where the greatest leverage is

Redefine / code problem to reduce energy/delay

Technology

Two kinds of technology scaling:

- Constant voltage (what we used to do)
- Scaled voltage (what we seem to be doing now)

Constant Voltage:

- $L = \alpha L$; $V = V$

C falls as α^1

- Energy/Op = $k_1 CV^2$ falls as α
- Delay = CV/i

falls as α to α^2 depending on whether the transistors are velocity saturated

- Energy delay falls as α^2 to α^3

1. $C/\mu\text{m}$ remains the same, but the wires get shorter. This is true even with fringing capacitance

Ideal Scaling

Ideal scaling:

- $L = \alpha L$; $V = \alpha V$
- Energy/Op = $k_1 CV^2$
falls as α^3
- Delay = CV/i
falls as α
- Energy delay falls as α^4

Better than constant voltage scaling ...

Extra factor of α


Optimal Energy-Delay product

$$= k V_{th}$$

Scaling V_{th} reduces dynamic power

Minimum V_{th} set by static leakage power

 - When you turn a transistor off, there is still some leakage
- Leakage current is exponential on $(V_{th} - V_{gs})$
- Since minimum of $V_{gs} = 0$, need some V_{th} to turn devices off



$$I_{ds} \sim \frac{W}{L} I_s \times \exp\left(\frac{V_{gs} - V_{th}}{av_T}\right)$$

Dynamic Power Reduction

Try to prevent useless transitions

- Use selective activation

 If block is not being used, turn off the clock

 This will force the latches to hold their values

 Most of the signals will not change

- Try to reduce transitions on large capacitance nodes

 Prevent glitches when possible

But this is mostly small changes, a factor or two if you are lucky

Big Wins

The major way to reduce power is to rethink about the problem at the high level. Like most things, this is where the leverage is. There are two general techniques that will help with power:

Use parallelism

- Improve delay, and thus energy * delay
- Use voltage scaling / transistor sizing
 convert excess speed to low power

Reformulate the problem

- Reduce required computation
- Improves energy/op and delay/op

Parallelism

If the problem can be solved in a parallel fashion



- $\text{Energy/Op} = 1 + \Delta_e$
Have a small amount of overhead in distributing the operands
- $\text{Delay/Op} = 1/n + \Delta_d$
Again small overhead in making the solution parallel
- $\text{Energy delay} = 1/n + \text{overhead}$

Problem Reformulation

Assume operation needs 100 instructions

- Energy = $100 E_{\text{inst}}$
- Delay = $100 T_{\text{inst}}$

If another algorithm only needs 50 instructions

- Energy delay = 1/4 Old solution
- Could use a slower, lower power processor

Works for hardware too

- Remove multiplies, need for FP, etc.
- Reduce the energy needed for operation, and time required

Low Power Design

Good design has always meant careful trade-offs

- Used to worry about performance, area, and design time
- Need to consider energy too

Energy delay metric is helpful in making these trade-offs

- Reminds about the trade-off between performance and power
- High speed techniques good for low power

Parallelism very helpful

Leverage is at the top and bottom

- Better technologies have much better energy-delay products

Same performance at α^2 - α^4 the power

- Key is to think about the system-level problem

Here one can make order of magnitude changes