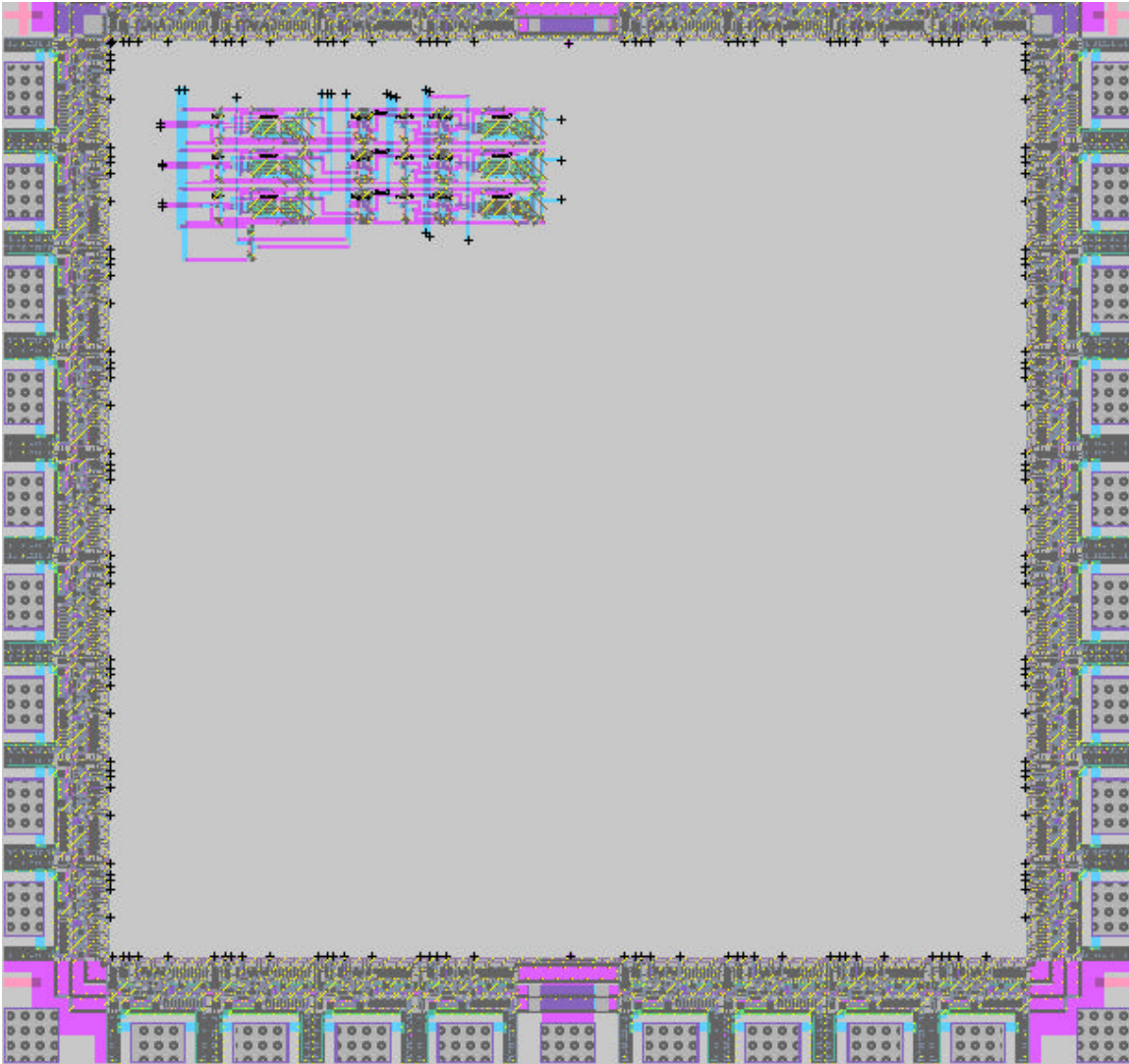


Final Report  
Intro to CMOS VLSI Design  
E158




## 8 Bit Floating Point Adder/ Subtractor

11 April 2001  
Andrew Ingram  
Ronalee Lo

# Table of Contents

<b>Section</b>	<b>page</b>
<b>Color Chip Plots</b>	1
<b>Functional Overview</b>	2-3
<b>Chip Floorplan</b>	4-5
<b>Area and Design Time Data</b>	6
<b>Simulation Results</b>	7
1) Verilog waveforms	8-13
2) IRSim simulation	14-16
<b>Verification Results</b>	17
<b>Postfabrication Test Plan</b>	18-25
<b>Schematics/ Verilog</b>	26
1) Readable Verilog Code	26-36
2) Verilog Code for Electric	37-47
3) Leaf Cell: Mux2 (schematic)	48
4) Leaf Cell: Full adder (schematic)	48
5) Hand layout of the Exponent Bitslice (schematic)	49
6) Hand layout of Exponent Datapath (schematic)	49
7) Synthesized and hand layout of full datapath (schematic)	50
<b>Layout</b>	
1) Leaf Cell: Mux2 (layout)	51
2) Leaf Cell: Full Adder (layout)	51
3) Hand layout of Exponent Datapath (layout)	52
4) Synthesized and hand layout of full datapath (layout)	52

# Color Chip Plot

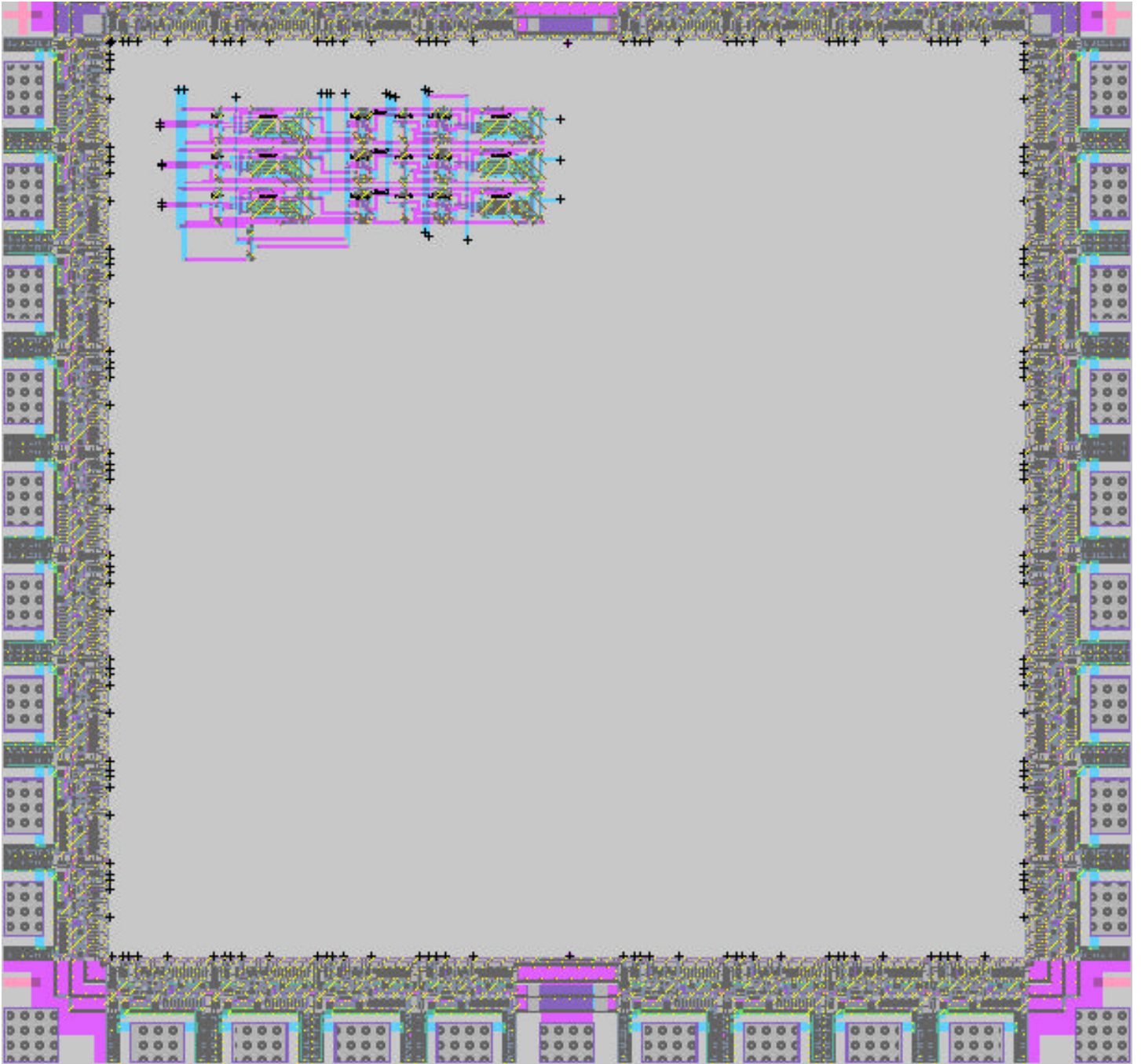

# Functional Overview:

## Two Function Calculator

The motivation for this project began at almost the very beginning of our HMC careers. During the freshman year we worked on the giant calculator that was given to Professor Benjamin. We used the logic from a hand-held calculator to generate the results. For this project we would like to actually construct the logic on the transistor level for a subset of the calculator functions.

Specifically, we propose to build an 8 bit floating point adder. Floating point numbers allow computers to perform operations on numbers other than simple integers. According to the IEEE standards, floating point numbers are of the form  $(-1)^S * 2^E * M$ . Here,  $S$  is the sign bit, which determines whether the number is positive or negative. The mantissa,  $M$ , holds the significant bits of the floating point number. Using a notation similar to scientific notation,  $E$  is the exponent that the mantissa is raised to.

A 32 bit floating point number is standard, but due to size limitations in our design, both in available I/O pins, and chip area, we will be using an 8 bit representation. We will have a sign bit, 3 bits available for the exponent, and the remaining 4 bits will be devoted to the mantissa. This will allow us to represent a resolution as small as  $1/128$  when the implicit leading 1 is taken into account. However the smallest number we can represent is  $1/8$

We are aware that 8 bits are not terribly useful for performing extremely accurate calculations, but it does demonstrate the operation of a floating point adder. The design methodology is nearly identical for an 8 bit adder as for the larger adders, and the learning gained from the 8 bit version will be just as valuable.

Our adder should perform correctly in the normal cases, but for extreme cases we have devised ways of handling exceptions. For the subtraction of two equal numbers, the result should be zero. For our implementation, zero will be denoted on a separate zero-detect pin on the chip. When a calculation results in zero, that pin will be at logical 1. When adding numbers that produce a result out of range, an overflow occurs. For this exception, we will have a separate signal that indicates that an overflow has occurred, and that the result [0:7] is not reliable.


Data will be loaded into our adder using 16 parallel inputs, [7:0] for  $A$  and [16:8] for  $B$  and the result [7:0] will also be 8 bits in parallel. We will also need to assign a pin to be function select. This selects whether we are performing subtraction or addition.

This project will be implemented in two different software packages. We first designed the entire project in verilog to ensure that the logic was correct. The formal layout for this project is quite large, so given the time constraints we will be laying out the exponent datapath and synthesizing the mantissa datapath from the generated verilog code. We will join the exponent datapath with the mantissa datapath to create the final chip design.


The final test to see whether our design meets the specs in this proposal is simple: can it correctly add and subtract two floating point numbers? Does it handle the exceptions correctly, as described herein? Finally, although neither of us be here next year, this might be something that would be useful to add to a micro-p's project in the future.

Inputs	Outputs
A[0:7]	Result[0:7]
B[0:7]	Zero detect
Clk	Overflow
Function select	
Power	
Ground	

# Chip Floorplan: Block Diagram

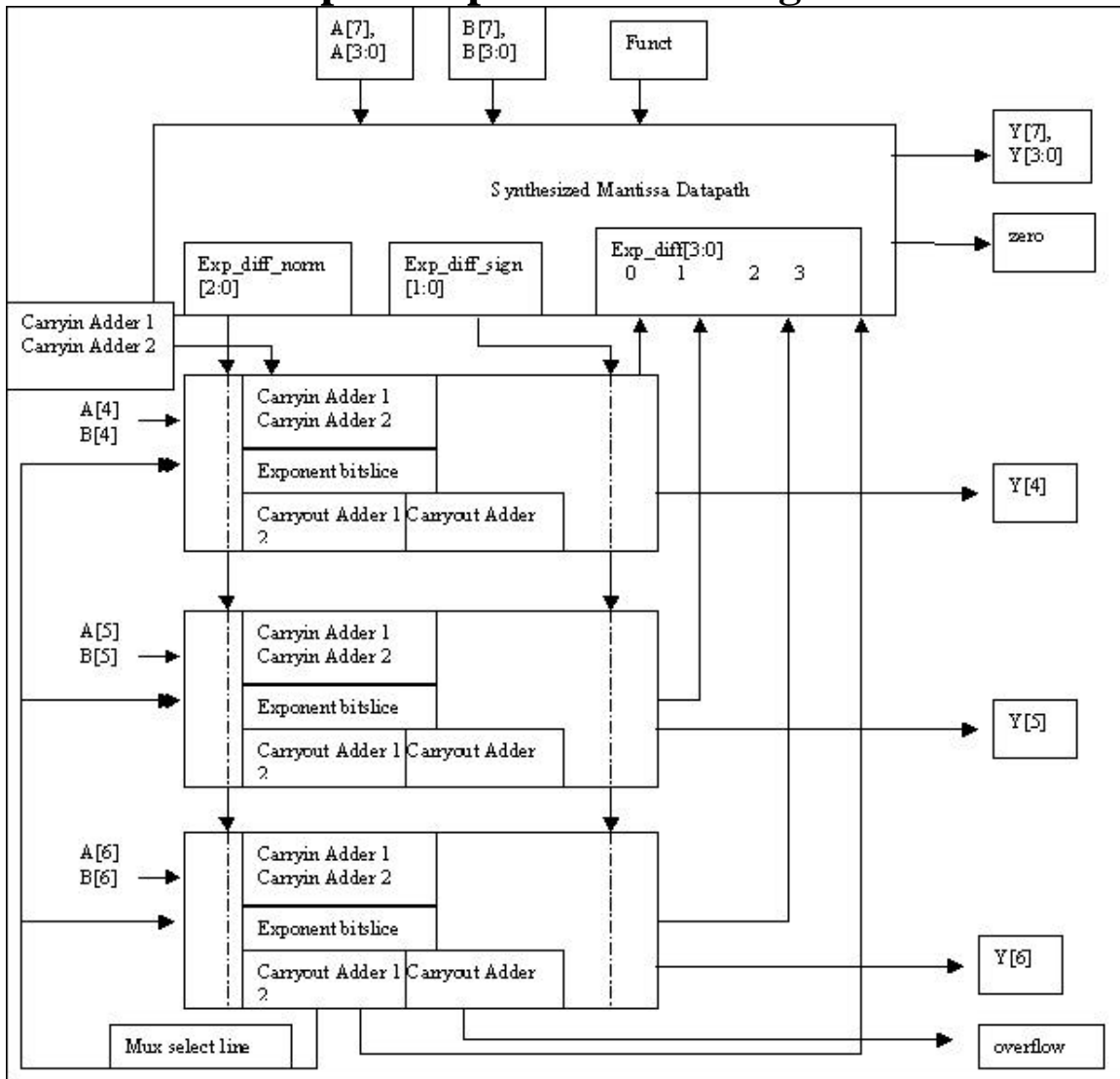

# Chip Area Estimate

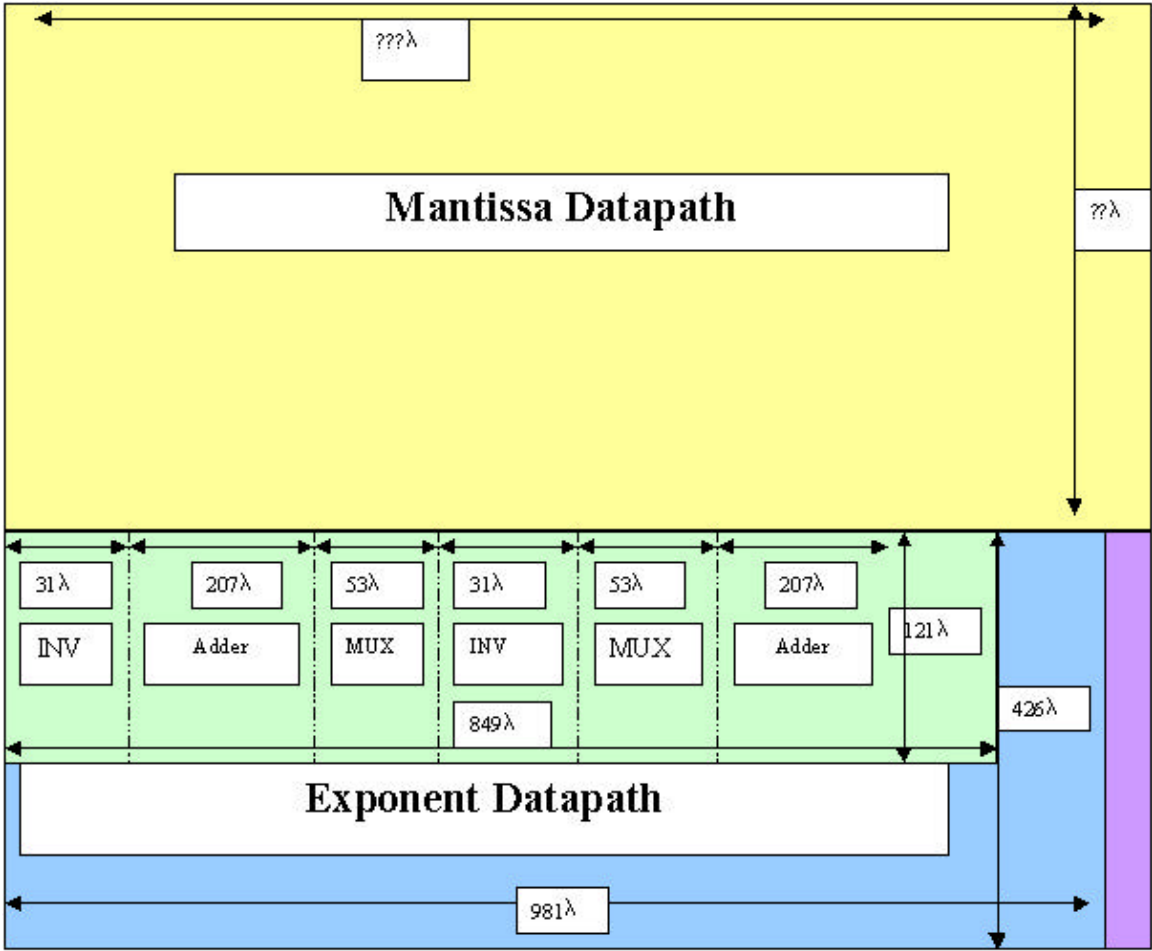

Note: Figure not drawn to scale

## Area and Design Time Data

Cell Name	Area	Design Time	Comments
2-Input Mux	$4982\lambda^2$	1 hour	Modified a design found in an existing library
INV	$3007\lambda^2$	5 minutes	Taken from another library
Adder	$20286\lambda^2$	4 hours	Metal modifications to an existing design
Exponent Bitslice	$102729\lambda^2$	9 hours	Assembled various parts, required a lot of updating as designs changed
Exponent Datapath	$477252\lambda^2$	3 hours	Assembled bitslices, also took a lot of updating and modifications
Synthesized Datapath	NA	See below	
Complete layout	NA		

## Other Time Considerations

Task	Time	Comments
Conceptual Design	8 hours	Visualizing the data path, identifying the inputs and outputs to each module
Verilog Code	40-45 hours	Many attempts to get a working code. Had to gain a clear understanding of how a floating-point adder works. Commenting and rewriting code to accommodate Electric
Verification of Exponent Datapath	4 hours	Getting DRC, ERC, and NCC to pass in Electric for the hand-layout of the exponent datapath layout and schematic. Some time was spent trying to get NCC to pass in Electric but ended up verifying using Gemini.
Simulation of Exponent Datapath	14 hours	Electric has a lot of trouble generating a .sim file for both the layout and schematic datapath, see Simulation section for more details
Synthesize Mantissa Datapath	7 hours	Design Analyzer could not make a non-hierarchical .vhdl file for Electric
Final Report	10 hours	



## **Simulation Results**

Many simulation tests were performed on this project during various stages in the development. The first set of waveforms following this section is the simulation done on the complete Verilog code using the Xilinx simulation tool. The complete code includes both the exponent and mantissa datapaths. By proving that the code is simulating properly, we are fairly confident that the synthesized mantissa datapath will be correct, but that we can also use the exponent datapath code as a guide for the hand drawn exponent datapath. We tested the code with all of the cases listed in the testing protocol.














The next set of tests would have been to use IRSim to test the full schematic datapath. This test could not be completed because Electric could not generate a .sim file for the layout. It was unable to place two of our exports from the layout into the .sim file. Below is a screen shot of the list of exports for the layout and also the error given when IRSim is trying to generate the .sim file for the layout.

Export list of the exponent datapath layout:

Thumbnail	Export Name	Connects to
	Input port 'a0'	connects at [-186.251, 60.8319] to Metal-2
	Input port 'a1'	connects at [-182.189, -37.0681] to Metal-2
	Input port 'a2'	connects at [-181.672, -134.293] to Metal-2
	Input port 'b0'	connects at [-185.232, 52.6656] to Metal-2
	Input port 'b1'	connects at [-182.08, -45.1481] to Metal-2
	Input port 'b2'	connects at [-181.525, -142.287] to Metal-2
	Input port 'cinadder1'	connects at [-1.75688, 122.579] to Metal-1
	Input port 'exp_diff_norm0'	connects at [385.871, 123.464] to Metal-1
	Input port 'exp_diff_norm1'	connects at [376.052, 127.391] to Metal-1
	Input port 'exp_diff_norm2'	connects at [366.467, 133.218] to Metal-1
	Input port 'exp_diff_sign'	connects at [468.743, 136.757] to Metal-1
	Input port 'exp_diff_signb'	connects at [459.743, 143.832] to Metal-1
	Output port 'exp_diff0'	connects at [205.243, 133.931] to Metal-1
	Output port 'exp_diff1'	connects at [221.271, 133.153] to Metal-1
	Output port 'exp_diff2'	connects at [229.639, 133.43] to Metal-1
	Output port 'exp_diff3'	connects at [266.699, 132.931] to Metal-1
	Output port 'overflow'	connects at [563.127, -223.189] to Metal-1
	Output port 'signout'	connects at [469.072, -215] to Metal-1
	Output port 'signoutb'	connects at [460.072, -206] to Metal-1
	Output port 'y4'	connects at [791.483, 69.5581] to Metal-1
	Output port 'y5'	connects at [790.901, -28.3419] to Metal-1
	Output port 'y6'	connects at [789.154, -125.567] to Metal-1
	Power port 'vdd'	connects at [-140.738, 141.515] to Metal-1
	Ground port 'gnd'	connects at [-127.819, 141.403] to Metal-1



## Screen shot of IRSim error message

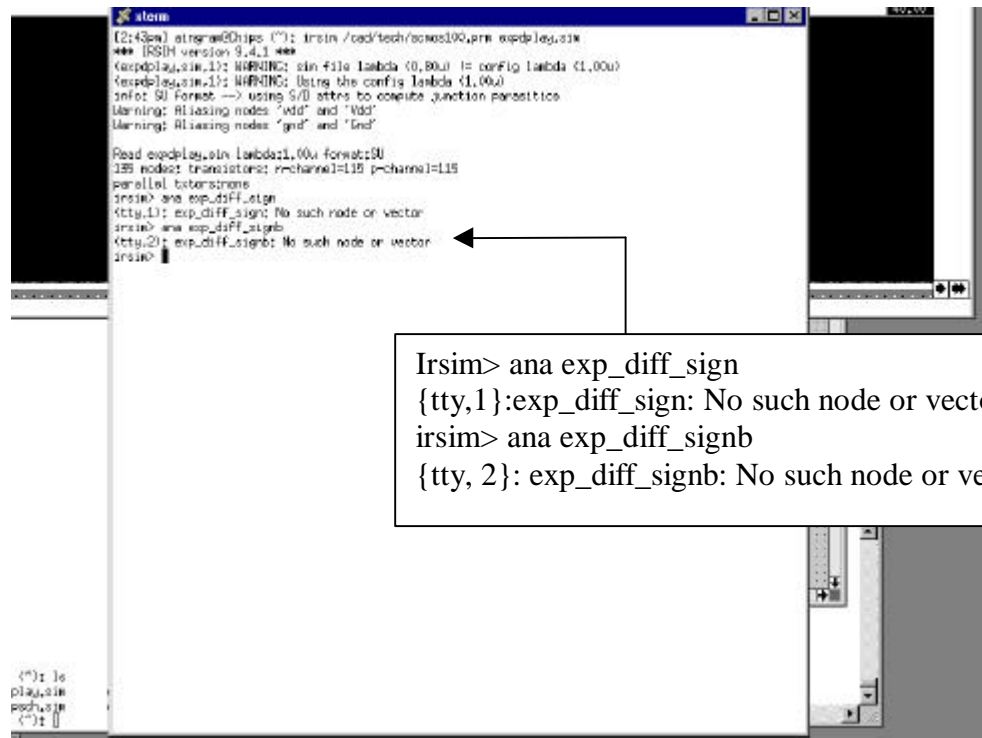

```
stern
[2:43pm] atreg@Ochip: C:\: irsim /cd/tech/sonos190.prm expd1eg.sim
*** IIRSim version 9.4.1 ***
<expd1eg.sim.1> WARNING: sin file lambda (0.800) != config lambda (1.000)
<expd1eg.sim.1> WARNING: Using the config lambda (1.000)
infor: SU Forest --> using S/D attrs to compute junction parasitics
Warning: Aliasing nodes "vdd" and "Vdd"
Warning: Aliasing nodes "gnd" and "Gnd"

Read expd1eg.sim lambda21.000 forest:SU
135 nodes: transitions: rchannel=115 pchannel=115
parallel transitions
irsim> ana exp_diff_sign
{tty,1}: exp_diff_sign: No such node or vector
irsim> ana exp_diff_signb
{tty,2}: exp_diff_signb: No such node or vector
irsim>
```

Callout box content:

```
Irsim> ana exp_diff_sign
{tty,1}:exp_diff_sign: No such node or vector
irsim> ana exp_diff_signb
{tty, 2}: exp_diff_signb: No such node or vector
```

As you can see, Electric clearly knows that the exports exist but when we looked in the generated .sim file, there were no connected or even mention of exp\_diff\_sign or exp\_diff\_signb.

We were told that since we managed to get NCC to check on Gemini if we can prove that the simulation works on the schematic datapath then we can safely assume that the simulation of the layout would also be successful. However when we tried to run the generated .sim file for the schematic datapath of the exponent we were given the following error.

## Screen shot of IRSim message window

```
infat SU format -> using S/3 attrx to compute junction parasitics
(expdpsch, sin.5): Wrong number of args for 'n' (12)
n b0 gnd slicel /net4 vdd 2 2 4.8 46.1 g=5_gnd s=R_12,P_14 d=R_12,P_14
(expdpsch, sin.7): Wrong number of args for 'p' (12)
p b0 slicel /net4 vdd 2 2 4.8 22.1 g=5_vdd s=R_12,P_14 d=R_12,P_14
(expdpsch, sin.9): Wrong number of args for 'n' (12)
p slicel /adder1/coutb net4 vdd 2 2 47.2 12.3 g=5_vdd s=R_12,P_14 d=R_12,P_14
(expdpsch, sin.11): Wrong number of args for 'n' (12)
n slicel /adder1/coutb gnd net4 2 2 47.2 5.9 g=5_gnd s=R_12,P_14 d=R_12,P_14
(expdpsch, sin.13): Wrong number of args for 'p' (12)
p slicel /adder1/sub exp_diff0 vdd 2 2 39.2 11.9 g=5_vdd s=R_12,P_14 d=R_12,P_14
(expdpsch, sin.15): Wrong number of args for 'n' (12)
n slicel /adder1/sub gnd exp_diff0 2 2 39.2 5.9 g=5_gnd s=R_12,P_14 d=R_12,P_14
(expdpsch, sin.17): Wrong number of args for 'p' (12)
p s0 slicel /adder1/net10 vdd 2 2 31.2 22.3 g=5_vdd s=R_12,P_14 d=R_12,P_14
(expdpsch, sin.19): Wrong number of args for 'p' (14)
p cinadder1 slicel /adder1/sub slicel /adder1/net11 2 2 31.2 12.9 g=5_vdd s=R_12,P_14 d=R_12,P_14
(expdpsch, sin.21): Wrong number of args for 'p' (14)
p slicel /net4 slicel /adder1/net10 slicel /adder1/net11 2 2 31.2 17.9 g=5_vdd s=R_12,P_14 d=R_12,P_14
(expdpsch, sin.23): Wrong number of args for 'p' (12)
p cinadder1 slicel /adder1/net12 vdd 2 2 26.2 17.9 g=5_vdd s=R_12,P_14 d=R_12,P_14
(expdpsch, sin.25): Wrong number of args for 'p' (13)
p slicel /net4 slicel /adder1/net12 vdd 2 2 21.2 17.9 g=5_vdd s=R_12,P_14 d=R_12,P_14
(expdpsch, sin.27): Wrong number of args for 'p' (12)
p s0 slicel /adder1/net12 vdd 2 2 49.2 17.9 g=5_vdd s=R_12,P_14 d=R_12,P_14
(expdpsch, sin.29): Wrong number of args for 'p' (14)
p slicel /adder1/coutb slicel /adder1/sub slicel /adder1/net12 2 2 21.2 11.9 g=5_vdd s=R_12,P_14 d=R_12,P_14
(expdpsch, sin.31): Wrong number of args for 'p' (12)
p s0 slicel /adder1/net7 vdd 2 2 6.2 17.9 g=5_vdd s=R_12,P_14 d=R_12,P_14
(expdpsch, sin.33): Wrong number of args for 'p' (14)
p slicel /net4 slicel /adder1/coutb slicel /adder1/net7 2 2 6.2 11.9 g=5_vdd s=R_12,P_14 d=R_12,P_14
(expdpsch, sin.35): Wrong number of args for 'p' (13)
p slicel /net4 slicel /adder1/net8 vdd 2 2 1.2 17.9 g=5_vdd s=R_12,P_14 d=R_12,P_14
(expdpsch, sin.37): Wrong number of args for 'p' (12)
p s0 slicel /adder1/net8 vdd 2 2 -5.8 17.9 g=5_vdd s=R_12,P_14 d=R_12,P_14
(expdpsch, sin.39): Wrong number of args for 'p' (13)
p cinadder1 slicel /adder1/coutb slicel /adder1/net9 2 2 -0.9 11.9 g=5_vdd s=R_12,P_14 d=R_12,P_14
(expdpsch, sin.41): Wrong number of args for 'n' (14)
n slicel /adder1/coutb slicel /adder1/net3 slicel /adder1/sub 2 2 21.2 5.9 g=5_gnd s=R_12,P_14 d=R_12,P_14
(expdpsch, sin.43): Wrong number of args for 'n' (13)
n cinadder1 slicel /adder1/net4 slicel /adder1/sub 2 2 31.2 4.9 g=5_gnd s=R_12,P_14 d=R_12,P_14
(expdpsch, sin.45): Wrong number of args for 'n' (12)
n s0 gnd slicel /adder1/net5 2 2 31.2 -5.1 g=5_gnd s=R_12,P_14 d=R_12,P_14
Too many errors in sim file (expdpsch.sim)
(2:47m) singra@0chip (~):
```

Too many errors in sim file <expdpsch.sim>

Since neither datapath was able to generate a proper .sim file, the full datapath could not be simulated. We attempted to track down the bug which prevented Electric from generating a correct .sim file. We check other facets such as INV and AND using IRSim to simulate their functionality. Both gates simulated properly. In the end we still could not find the problem.

## Verification Results

DRC, ERC, and NCC verification was done in separate stages as our project progressed. We verified DRC, ERC, and NCC on many smaller layouts and schematics to make sure that our design was not going awry without us realizing it. DRC, ERC, and NCC passed on the MUX and Adder. We also verified DRC and ERC on the exponent datapath bitslice. However, we ran into some problems when we tried to verify NCC. We eventually used Gemini to determine why NCC was not passing. We also used Gemini to verify NCC on the full datapath of the exponent layout and schematic. Gemini did identify minor modifications that needed to be made to our design. However, even though Gemini verified both the bitslice and the datapath, Electric would not pass NCC on either. We were told that Gemini is more reliable so we did not spend any more time trying to get Electric to pass NCC for the exponent bitslice and the datapath.

After the rest of the datapath for a floating-point adder was synthesized, we performed more verification tests on the full design. NCC was not expected to pass using Electric since the exponent datapath did not pass. Again, we used Gemini to verify NCC on the full datapath.

Results:

Cell	DRC	ERC	NCC
MUX	Pass	Pass	Pass
INV	Pass	Pass	Pass
Adder	Pass	Pass	Pass
Exponent Bitslice	Pass	Pass	Pass in Gemini
Exponent Datapath	Pass	Pass	Pass in Gemini
Full Datapath			

# Post-Fabrication Test Plan

Testing the chip just calls for enough runs to test a fair portion of the capabilities of the chip and a few special cases. To test the chip, one can hook the chip to a protoboard. Note the physical locations of each input and output pin. Once you have verified the pin locations, hook dip switches to the inputs and LEDs to the outputs. The dip switches will allow you to manually apply high and low values to each input pin. For quick verification, the LEDs should light if the desired output is high.

Note that the test plan does not call for a test of every possible combination of numbers. Each 8 bit floating point number can represent  $2^8$  different numbers. So it would require  $2^{17}$  tests to check all possible combinations(including the function choice). So instead of testing  $2^{17}$  different cases, we will only test the boundary cases.

Listed below are equations that should be applied and why it is important.

1) **Same exponent, same mantissa value- these tests will verify if the chip is functioning properly when no original shifting is required to add or subtract two identical numbers.**

- Addition of two identical numbers (but more importantly, since they have the same exponent value, the mantissa does not need to be shifted)

**5 + 5 = 10**

Input		Output	
A[7:0]	01010100	Y[7:0]	01100100
B[7:0]	01010100	Zero	0
Funct	0	Overflow	0

\*Also try this equivalent case **[5 - (-5)] = 10\***

Input		Output	
A[7:0]	01010100	Y[7:0]	01100100
B[7:0]	11010100	Zero	0
Funct	1	Overflow	0

- Subtraction of two identical numbers (assert the zero pin)

$$5 - 5 = 0$$

Input		Output	
A[7:0]	01010100	Y[7:0]	XXXXXXXXXX
B[7:0]	01010100	Zero	1
Funct	0	Overflow	0

\*Equivalent cases  $(-5 + 5)$ ,  $[-5 - (-5)]$ \*

\*X denotes "don't care"\*

$$(-5 + 5) = 0$$

Input		Output	
A[7:0]	11010100	Y[7:0]	XXXXXXXXXX
B[7:0]	01010100	Zero	1
Funct	0	Overflow	0

$$[(-5) - (-5)] = 0$$

Input		Output	
A[7:0]	11010100	Y[7:0]	XXXXXXXXXX
B[7:0]	11010100	Zero	1
Funct	1	Overflow	0

- 2) **The next few cases will be used to determine if the shifting functions are working properly. The shifting functions will be used since the exponents are not equal, therefore the smaller mantissa will need to be shifted in order to perform the calculation.**

- Adding two positive numbers

$$18 + 7 = 25$$

Input		Output	
A[7:0]	01110010	Y[7:0]	01111001
B[7:0]	01011100	Zero	0
Funct	0	Overflow	0

\*note: the values given to input A and input B can be switched in order to do a more thorough check, the output values should remain unchanged\*

- Adding two negative numbers

$$(-18) + (-7) = (-25)$$

Input		Output	
A[7:0]	11110010	Y[7:0]	11111001
B[7:0]	11011100	Zero	0
Funct	0	Overflow	0

\*note: the values given to input A and input B can be switched in order to do a more thorough check, the output values should remain unchanged\*

- Adding a positive and negative number where the positive number is bigger

$$18 + (-7) = 11$$

Input		Output	
A[7:0]	01110010	Y[7:0]	01100110
B[7:0]	11011100	Zero	0
Funct	0	Overflow	0

\*note: the values given to input A and input B can be switched in order to do a more thorough check, the output values should remain unchanged\*

- Adding a positive and negative number where the negative number is bigger

$$(-18) + 7 = -11$$

Input		Output	
A[7:0]	11110010	Y[7:0]	11100110
B[7:0]	01011100	Zero	0
Funct	0	Overflow	0

\*note: the values given to input A and input B can be switched in order to do a more thorough check, the output values should remain unchanged\*

- Subtracting two positive numbers, where the larger positive is given to input A

$$18 - 7 = 11$$

Input		Output	
A[7:0]	01110010	Y[7:0]	01100110
B[7:0]	01011100	Zero	0
Funct	1	Overflow	0

- Subtracting two positive numbers, where the larger positive is given to input B

$$7 - 18 = -11$$

Input		Output	
A[7:0]	01011100	Y[7:0]	11100110
B[7:0]	01110010	Zero	0
Funct	1	Overflow	0

- Subtracting two negative numbers, where the larger positive is given to input A

$$(-18) - (-7) = -11$$

Input		Output	
A[7:0]	11110010	Y[7:0]	11100110
B[7:0]	11011100	Zero	0
Funct	1	Overflow	0

- Subtracting two negative numbers, where the larger positive is given to input B

$$(-7) - (-18) = 11$$

Input		Output	
A[7:0]	11011100	Y[7:0]	01100110
B[7:0]	11110010	Zero	0
Funct	1	Overflow	0

- Subtracting a positive number from a negative number where the absolute value of the positive number is smaller than the absolute value of the negative number

$$(-18) - 7 = -25$$

Input		Output	
A[7:0]	11110010	Y[7:0]	11111001
B[7:0]	01011100	Zero	0
Funct	1	Overflow	0

- Subtracting a positive number from a negative number where the absolute value of the positive number is larger than the absolute value of the negative number

$$(-7) - 18 = -25$$

Input		Output	
A[7:0]	11011100	Y[7:0]	11100110
B[7:0]	01110010	Zero	0
Funct	1	Overflow	0

- Subtracting a negative number from a positive number where the absolute value of the positive number is smaller than the absolute value of the negative number

$$7 - (-18) = 25$$

Input		Output	
A[7:0]	01011100	Y[7:0]	01100110
B[7:0]	11110010	Zero	0
Funct	1	Overflow	0

- Subtracting a negative number from a positive number where the absolute value of the positive number is larger than the absolute value of the negative number

$$18 - (-7) = 25$$

Input		Output	
A[7:0]	01110010	Y[7:0]	01111001
B[7:0]	11011100	Zero	0
Funct	1	Overflow	0

- 3) **Overflow case: this case just checks to see if the resulting number cannot be represented in the 8 bits provided. (i.e. the absolute value of the number is greater than 31)**

$$31 + 1 = 32$$

Input		Output	
A[7:0]	01111111	Y[7:0]	XXXXXXXX
B[7:0]	00110000	Zero	0
Funct	0	Overflow	1

- 4) **Normalization of Exponent: These cases will check the different possibilities for normalizing the final exponent value**

- Changing the exponent value by 4

$$31 - 30 = 1$$

Input		Output	
A[7:0]	01111111	Y[7:0]	00110000
B[7:0]	01111110	Zero	0
Funct	1	Overflow	0



- Changing the exponent value by 3

$$15 - 14 = 1$$

Input		Output	
A[7:0]	01101110	Y[7:0]	00110000
B[7:0]	01101100	Zero	0
Funct	1	Overflow	0

- Changing the exponent value by 2

$$7 - 6 = 1$$

Input		Output	
A[7:0]	01011100	Y[7:0]	00110000
B[7:0]	01011000	Zero	0
Funct	1	Overflow	0

- Changing the exponent value by 1

$$3 - 2 = 1$$

Input		Output	
A[7:0]	01001000	Y[7:0]	00110000
B[7:0]	01000000	Zero	0
Funct	1	Overflow	0

5) **Lowest number representation: These cases test the decimal numbers that can be represented in an 8-bit floating-point scheme.**

- Adding the smallest numbers that can be represented as inputs

$$0.125 + 0.125 = 0.25$$

Input		Output	
A[7:0]	00000000	Y[7:0]	00010000
B[7:0]	00000000	Zero	0
Funct	0	Overflow	0

- Adding two fractions which result in a whole number, note also the ability to express the smallest resolution in the output (the 1/16 bit location)

$$0.5 + 0.5 = 1$$

Input		Output	
A[7:0]	00100000	Y[7:0]	00110000
B[7:0]	00100000	Zero	0
Funct	0	Overflow	0

- Adding a whole number and a fraction to get a mixed number, note also the ability to express the smallest resolution in the output (the 1/16 bit location)

$$1 + 0.1875 = 1.1875$$

Input		Output	
A[7:0]	00110000	Y[7:0]	00110011
B[7:0]	00001000	Zero	0
Funct	0	Overflow	0

- 6) **Shifting mantissa: These cases require varying amount of initial shifting of the Mantissa to add two numbers. It is important to note that if two numbers are added where the difference in their exponents is greater than 4, the resulting output is incorrect. (i.e.  $30 + \frac{1}{2} = 30$ )**

- Shifting the mantissa by 4

$$30 + 1 = 31$$

Input		Output	
A[7:0]	01111110	Y[7:0]	01111111
B[7:0]	00110000	Zero	0
Funct	0	Overflow	0

- Shifting the mantissa by 3

$$14 + 1 = 15$$

Input		Output	
A[7:0]	01101100	Y[7:0]	01101110
B[7:0]	00110000	Zero	0
Funct	0	Overflow	0

- Shifting the mantissa by 2

$$6 + 1 = 7$$

Input		Output	
A[7:0]	01011000	Y[7:0]	01011100
B[7:0]	00110000	Zero	0
Funct	0	Overflow	0

- Shifting the mantissa by 1

$$2 + 1 = 3$$

Input		Output	
A[7:0]	01000000	Y[7:0]	01001000
B[7:0]	00110000	Zero	0
Funct	0	Overflow	0

## Schematics and Verilog

In this section you will find versions of the same Verilog code. The first code is a more readable version. It still have module separations and busses which represent various inputs. This is also the code with comments since it is easier to follow.

The second code is the version of code with all of the busses flattened so that Electric can handle the synthesized module. The hierarchy of this code was later removed since the data analyzer outputs a hierarchical vhdl file which also cannot be handled in Electric.

### Readable Verilog Code

```
//This is not the code that was synthesized
//Electric does not recognize busses so the code was redone with all of the
// busses flattened

//Also, this code contains verilog code for both the exponent and mantissa datapaths

module topadder(A, B, funct, zero, Y);

input [7:0] A ; //Input number A
input [7:0] B ; //Input number B
input funct ; // funct=0 is add, and funct=1 is subtract

output zero ; //the output at Y is not corrent for cases that
result //in zero so a seperate output pin is assigned
//for zero cases
// zero = 1 when result is zero, zero = 0 for
//nonzero results

output [7:0] Y ; //answer

wire [2:0] exp_A; //internal wires for easier coding, represent
wire [2:0] exp_B; // theexponential values for A, B, and Y
wire [2:0] exp_Y;

wire sign_Y; //sign bit of Y

wire [3:0] mant_Y; //mantissa bits of Y

wire [2:0] exp_diff_norm; //used in the normalization module, tells the module
//what value to add or subtract to a temp exponent
//value
```

```

wire [1:0] exp_diff_sign;           //tells the normalize module to add or subtract the
exp_diff_norm                       //value from the temp exp. value
wire [3:0] exp_diff;                //result of exp_A - exp_B

assign exp_A = A[6:4];              //exponent bits of an 8-bit floating point number is
                                   //in bits 4-6
assign exp_B = B[6:4];

assign Y = {sign_Y, exp_Y, mant_Y}; //initial value of Y

//module call to the synthesized mantissa datapath
synth_part get_mant(A, B, funct, zero, exp_diff_norm, exp_diff_sign, exp_diff, sign_Y,
mant_Y);

//module call to the exponent datapath (this module was used as a guide to hand draw the
//exponent datapath
exp_part get_exp(exp_A, exp_B, exp_diff_norm, exp_diff_sign, exp_diff, exp_Y);

endmodule

//*****
//Module: top level module for the synthesis mantissa datapath
module synth_part (A, B, funct, zero, exp_diff_norm, exp_diff_sign, exp_diff, sign_Y,
mant_Y);

input [3:0] exp_diff;              //exp_A - exp_B
input [7:0] A;                     //number A
input [7:0] B;                     //number B
input funct;                       // funct=0 is add, and funct=1 is subtract

output zero;                       //assert zero if the result is zero
output sign_Y;                     //resultant number
output [3:0] mant_Y;               //mantissa bits of Y

output [2:0] exp_diff_norm;        //amount to add/sub to temp. exp to normalize
output [1:0] exp_diff_sign;        //tells normalize to add or sub the exp_diff_norm to
                                   //get the right output exponent value

wire sign_A;                       //sign bits of A, B, and Y
wire sign_B;
wire sign_Y;

```

```

wire temp_sign; //helps with holding sign_B value in case the bit
                //needs to be swizzled to accommodate subtraction
                //calls

wire [3:0] mant_A; //mantissa bits of A, B, and Y
wire [3:0] mant_B;
wire [3:0] mant_Y;
wire [5:0] temp_mant_Y; //holds the sum of the two mantissa before
                        //normalization

wire [3:0] exp_diff; //amount to shift smaller mantissa by
                    //is the value of the smaller of the
                    //two input exponents
wire exp_diffsig; //most significant bit in the exp_diff value,
                 //this will check for neg. values

wire [4:0] mant_diff; //mant_A - mant_B
wire mant_diffsig; //most significant bit of mant_diff will be a
                  //quick check to determine
                  //which mantissa value was larger,
                  //if the bit is 0, A is larger
                  //if the bit is 1, B is larger

wire [3:0] small_mant; //holds the mantissa of the number with the
                      //smaller exponent
                      //if the exponent value is equal, it is
                      //arbitrarily set to the mantissa of A
wire [2:0] shift_amount; //amount to shift the small_mant (equal to
                        //exp_diff) this shift is necessary in order to
                        //produce a correct output

wire [5:0] shifted_mant; //small mantissa shifted by shift amount,
                        //also appended with the
                        //implied leading one
wire [3:0] big_mant; //mantissa of the number with the bigger
                    //exponent

wire temp_sign_B; //holds the final value of B's sign, needed to
                 //help in case
                 //of bit swizzling in the case of subtraction

wire [5:0] twos_small_mant; //possible two's compliment of the shifted
                            //mantissa, two's compliment

```

```

//used if subtraction is used

wire [1:0] exp_diff_sign; //tells normalize whether to add or subtract a
//certain value in
//order to properly normalize the exponent
wire [2:0] exp_diff_norm; //the value to add or subtract to normalize
//the exponent

//CODE BEGINS HERE
//divide inputs into Floating Point fields

assign sign_A = A[7]; //assign the sign bit of A, B
assign sign_B = B[7];

assign mant_A = A[3:0]; //assign mantissa bits of A, B
assign mant_B = B[3:0];

assign exp_diffsig = exp_diff[3]; //exp_diff is an input so set the highest bit
// 1 => exp_B is larger than exp_A
// 0 => exp_A is larger than exp_B

//find mantissa difference
assign mant_diff = mant_A - mant_B;
assign mant_diffsig = mant_diff[4]; //mant_diff
// 1 => mant_B is larger than mant_A
// 0 => mant_A is larger than mant_B

//assign small_mant to be the value of the mantissa of the number with the smaller of the
//two exponents
big_small_mants(mant_A, mant_B, exp_diff, exp_diffsig, mant_diffsig, big_mant,
small_mant);

//assign the shift amount, don't need the highest bit of exp_diff since it just tells you
//which exponent is larger. Also, if exp_B is larger, the exp_diff is in two's compliment
//form so perform another two's compliment to get a positive shift value
assign shift_amount = (exp_diffsig)? ~(exp_diff[2:0]): exp_diff[2:0];

//code for addition or subtraction, if subtraction is being done, swizzle the sign bit of B
assign temp_sign = funct? ~sign_B: sign_B;
assign temp_sign_B = temp_sign;

//shift mantissa to align decimal points

```

```

right_shifter shift_mantissa(small_mant, shift_amount, shifted_mant);

//calculate the two's compliment of the shifted mant, only needed in the case of
//subtraction or equivalent case (i.e. adding a negative number to a positive number)
twos_comp twos_small_mant(sign_A, sign_B, funct, shifted_mant, twos_small_mant);

//add the two mantissas together
assign temp_mant_Y = {1'b1, big_mant} + twos_small_mant;

//assign zero detect
zero_detect zero_find(sign_A, sign_B, funct, exp_diff, mant_diff, zero);

//normalize the mantissa and exponent value so it's back in floating point representation
normalize normal(temp_mant_Y, mant_Y, exp_diff_norm, exp_diff_sign);

//determine sign of the final value
final_sign sign_find(exp_diffsig, mant_diffsig, exp_diff, sign_A, temp_sign_B, sign_Y);

endmodule

//*****
//Module: see if the result of the operation results in a zero

module zero_detect (sign_A, sign_B, funct, exp_diff, mant_diff, zero);
input sign_A, sign_B, funct; //sign bits of A and B, and function being
//performed
input [3:0] exp_diff; //exponential difference (exp_A - exp_B)
input [4:0] mant_diff; //mantissa difference (mant_A - mant_B)
output zero; //assert true when result is zero

reg zero;

always@(sign_A or sign_B or funct or exp_diff or mant_diff)

//((sign_A^sign_B)^funct) is 1 when after you convert the operation to addition
//((i.e. a - b => a + (-b) OR a - (-b) => a + b) if the signs of A and B are different
if((((sign_A^sign_B)^funct)&(exp_diff == 4'b0000)&(mant_diff == 5'b00000))
    zero <= 1; //zero asserted if the signs of A and B are
//different and there is no
//difference in the mantissa and exponent

```



```

else
    zero <= 0;

endmodule

// a number plus a conjugate

//*****
//Module: perform two's compliment if subtraction operation is called for

module twos_comp (sign_A, sign_B, funct, shifted_mant, twos_small_mant);
input sign_A, sign_B, funct;           //sign bits of A and B, function being
                                       //performed
input [5:0] shifted_mant;             //the smaller mantissa shifted so that the
                                       //numbers are aligned in order to do the
                                       //operation
output [5:0] twos_small_mant;         //result either same as input or the two's
                                       //compliment of input

//two's compliment of shifted mantissa if numbers are being subtracted or adding
//a negative number
assign twos_small_mant = ((sign_A^sign_B)^funct)? -(shifted_mant): shifted_mant;

endmodule

//*****
//Module: Normalize the final exponent and mantissa value so it can be represented in
//floating point format

module normalize (in_mant, out_mant, exp_diff_norm, exp_diff_sign);

input [5:0] in_mant;                 //input sign_A, sign_B, funct;

output [3:0] out_mant;               //normalized mantissa value
output [1:0]exp_diff_sign;          //tells the exponent normalization module
                                       //whether the exponent value
                                       //needs a value added or subtracted in order
                                       //to be normalized, this is a 2 bit bus because
                                       //it simplifies the exponent datapath layout

output [2:0]exp_diff_norm;          //the value that needs to be added or
                                       //subtracted

reg [5:0] in_mant;
reg [3:0] out_mant;
reg [2:0]exp_diff_sign;

```

```

reg [2:0]exp_diff_norm;

//find the first "1" (i.e. locate a one and shift accordingly in order to get the implicate
//leading one for floating point representation
always@(in_mant)
begin

    if (in_mant[5])
        begin
            out_mant <= in_mant[4:1];
            exp_diff_norm <= 3'b001;
            exp_diff_sign <= 2'b01;           //0 means add to in_exp
                                           //the value in exp_diff_sign[1] can
                                           //be decoded to determine the
                                           //operation
                                           // 0 => add
                                           // 1 => subtract
                                           //the other bit is used in the exponent
                                           //datapath for the select_bar line of a
                                           //mux

        end
    else if (in_mant[4])
        begin
            out_mant <= in_mant[3:0];
            exp_diff_norm <= 3'b000;
            exp_diff_sign <=2'b01;

        end
    else if (in_mant[3])
        begin
            out_mant <= {in_mant[2:0], 1'b0};
            exp_diff_norm <= 3'b001;           //1
            exp_diff_sign <= 2'b10;           // 1 means to subtract

        end
    else if (in_mant[2])
        begin
            out_mant <= {in_mant[1:0], 2'b00};
            exp_diff_norm <= 3'b010;           //2
            exp_diff_sign <= 2'b10;           //subtract

        end
    else if (in_mant[1])
        begin
            out_mant <= {in_mant[0], 3'b000};
            exp_diff_norm <= 3'b011;           //3
            exp_diff_sign <= 2'b10;           //subtract

        end
    else if (in_mant[0])

```

```

        begin
            out_mant <= 4'b0000;
            exp_diff_norm <= 3'b100;           //4
            exp_diff_sign <= 2'b10;           //subtract
        end
    else
        begin
            out_mant <= in_mant;
            exp_diff_norm <= 3'b001;         //1
            exp_diff_sign <= 2'b01;         //add
        end
    end

end

endmodule

//*****
//Module: Determines the sign of the resulting value
module final_sign (exp_diffsig, mant_diffsig, exp_diff, sign_A, sign_B, sign_Y);

input exp_diffsig;                // 0 => exp_A is greater than or equal to
                                  //exp_B
                                  // 1 => exp_A is less than exp_B
input mant_diffsig;              // 0 => mant_A is greater than or equal to
                                  //mant_B
                                  // 1 => mant_A is less than mant_B
input [3:0]exp_diff;             //the exponent difference (exp_A - exp_B)
input sign_A;                    //sign bits of A, B, and Y
input sign_B;
output sign_Y;

reg sign_Y;

always@(exp_diffsig or mant_diffsig or exp_diff or sign_B or sign_A)
begin
    if (exp_diffsig)
        sign_Y <= sign_B;        //if the exp_diffsig is 1 (number B is bigger)
                                  //give sign_Y the sign of B
    else
        begin
            if (exp_diff == 4'b0000) //if the exp_diff is 0 (the two exp are
                                  //equal), check the mantissa values
                begin
                    if (mant_diffsig) //if the mant_diffsig is 1 (number B is
                                      //bigger)
                        sign_Y <= sign_B; //give sign_Y the sign //of B
                    else

```

```

        sign_Y <= sign_A;           //if the exp_diff is 0 and the
    end                               //mant_diffsig != 1
                                       //A and B have the same exponent but the
                                       //difference in the mantissas are zero or
                                       //greater
    else sign_Y <= sign_A;           //give sign_Y the sign of A
end                                     //give sign_Y the sign of A
                                       //if exp_diffsig != 1
                                       //(exp_A is bigger) and exp_diff is greater
                                       //than zero

end

endmodule

//*****
//Module: find which mantissa is bigger
module big_small (mant_A, mant_B, exp_diff, exp_diffsig, mant_diffsig, big_mant,
small_mant);

input [3:0]mant_A, mant_B, exp_diff;   //mantissa bits of A, B and the difference in /
                                       //the exponents (exp_A -exp_B)
input exp_diffsig, mant_diffsig;      //bits which tell which mantissa and
                                       //exponent value was larger for exp_diffsig
                                       // 0 => exp_A is greater than or equal to
                                       //exp_B
                                       // 1 => exp_A is less than exp_B
                                       //for mant_diffsig
                                       // 0 => mant_A is greater than or equal to
                                       //mant_B
                                       // 1 => mant_A is less than mant_B

output [3:0] big_mant, small_mant;    //the larger exponent's mantissa
                                       //and the smaller exponent's mantissa

reg [3:0]mant_A, mant_B, exp_diff;
reg exp_diffsig;
reg [3:0] big_mant, small_mant;

always@(mant_A or mant_B or exp_diff or exp_diffsig or mant_diffsig)

//if there exponents are equal
    if (exp_diff == 4'b0000)
        begin
            big_mant <= (mant_diffsig)? mant_B: mant_A;
            //assign based on which mantissa value is larger

```

```

        small_mant <= (mant_diffsig)? mant_A: mant_B;
    end
//if the exponents are not equal
    else
        begin
            big_mant <= (exp_diffsig)? mant_B: mant_A;
            //big mant is the mantissa of the number with the larger exponent
            small_mant <= (exp_diffsig)? mant_A: mant_B;
        end
        //small mant is the other mantissa
endmodule

//*****
//Module: Shifts a given number to the right by an amount (shift_amt)
module right_shifter(small_mant, shift_amt, shifted_mant);

input [3:0] small_mant;           //the smaller exponent's mantissa
input [2:0] shift_amt;           //the amount to right shift
output [5:0] shifted_mant;       //resulted shifted mantissa

reg [3:0] small_mant;
reg [5:0] shifted_mant;

//shift and append the implicit leading one
always@(small_mant or shift_amt)
    case (shift_amt)
        3'b000:    shifted_mant <= {2'b01, small_mant[3:0]};
        3'b001:    shifted_mant <= {3'b001, small_mant[3:1]};
        3'b010:    shifted_mant <= {4'b0001, small_mant[3:2]};
        3'b011:    shifted_mant <= {5'b00001, small_mant[3]};
        3'b100:    shifted_mant <= 6'b000001;

        default:    shifted_mant <= 6'b000000;

    endcase

endmodule

//*****
//Module: Verilog representation of the exponent datapath

```

```

module exp_part(exp_A, exp_B, exp_diff_norm, exp_diff_sign, exp_diff, exp_Y);

input [2:0] exp_A, exp_B, exp_diff_norm; //exponent values of A, B and the
//normalization number
input [1:0]exp_diff_sign; //operation in order to normalize

output [3:0] exp_diff; //the difference between exp_A - exp_B
output [2:0] exp_Y; //final exponent value

wire exp_diffsig; //0 => exp_A is greater than or equal to
//exp_B
// 1 => exp_A is less than exp_B
wire [2:0] temp_exp_Y; //holds the larger exponent value

reg [2:0] exp_Y;

//find exponent difference

assign exp_diff = exp_A - exp_B; //find the exponent difference
assign exp_diffsig = exp_diff[3];

//give temp_exp_Y the exp value of the bigger exp value
assign temp_exp_Y = (exp_diffsig)? exp_B: exp_A;

//normalizing the exponent value
always@(exp_diff_norm or exp_diff_sign or temp_exp_Y)

    if(exp_diff_sign[1]) //if =1 subtract
        exp_Y <= (temp_exp_Y) - (exp_diff_norm);

    else
        //if =0 add
        exp_Y <= (temp_exp_Y) + (exp_diff_norm);

endmodule

```

## Flatten Code

//Same code but with flattened busses for Electric

//Not as many comments since it's already hard to read

```
module topadder(A7, A6, A5, A4, A3, A2, A1, A0, B7, B6, B5, B4, B3, B2, B1, B0,  
funcnt, zero, Y7, Y6, Y5, Y4, Y3, Y2, Y1, Y0);
```

```
input funcnt; // funcnt=0 is add, and funcnt=1 is subtract
```

```
input A0;
```

```
input A1;
```

```
input A2;
```

```
input A3;
```

```
input A4;
```

```
input A5;
```

```
input A6;
```

```
input A7;
```

```
input B0;
```

```
input B1;
```

```
input B2;
```

```
input B3;
```

```
input B4;
```

```
input B5;
```

```
input B6;
```

```
input B7;
```

```
output zero ;
```

```
output Y0;
```

```
output Y1;
```

```
output Y2;
```

```
output Y3;
```

```
output Y4;
```

```
output Y5;
```

```
output Y6;
```

```
output Y7;
```

```
wire sign_Y;
```

```
wire exp_diff_norm0;
```

```
wire exp_diff_norm1;
```

```
wire exp_diff_norm2;
```

```
wire exp_diff_sign0;
```

```
wire exp_diff_sign1;
```

```

wire exp_diff0;
wire exp_diff1;
wire exp_diff2;
wire exp_diff3;

```

```

synth_part get_mant(A7, A3, A2, A1, A0, B7, B3, B2, B1, B0, funct, zero,
exp_diff_norm2, exp_diff_norm1, exp_diff_norm0, exp_diff_sign1, exp_diff_sign0,
exp_diff3, exp_diff2, exp_diff1, exp_diff0, Y7, Y3, Y2, Y1, Y0);

```

```

exp_part get_exp(A6, A5, A4, B6, B5, B4, exp_diff_norm2, exp_diff_norm1,
exp_diff_norm0, exp_diff_sign1, exp_diff_sign0, exp_diff3, exp_diff2, exp_diff1,
exp_diff0, Y6, Y5, Y4);

```

```

endmodule

```

```

//*****

```

```

module synth_part (A7, A3, A2, A1, A0, B7, B3, B2, B1, B0, funct, zero,
exp_diff_norm2, exp_diff_norm1, exp_diff_norm0, exp_diff_sign1, exp_diff_sign0,
exp_diff3, exp_diff2, exp_diff1, exp_diff0, Y7, Y3, Y2, Y1, Y0);

```

```

input exp_diff3, exp_diff2, exp_diff1, exp_diff0 ;
input A7, A3, A2, A1, A0;
input B7, B3, B2, B1, B0;
input funct;

```

```

// funct=0 is add, and funct=1 is subtract

```

```

output zero;
output Y7, Y3, Y2, Y1, Y0;
output exp_diff_norm2, exp_diff_norm1, exp_diff_norm0;
output exp_diff_sign1, exp_diff_sign0;

```

```

wire temp_sign;

```

```

wire temp_mant_Y5;
wire temp_mant_Y4;
wire temp_mant_Y3;
wire temp_mant_Y2;
wire temp_mant_Y1;
wire temp_mant_Y0;

```

```

wire mant_diff4;
wire mant_diff3;
wire mant_diff2;
wire mant_diff1;
wire mant_diff0;

```



```

wire    mant_diffsig;

wire small_mant3;
wire small_mant2;
wire small_mant1;
wire small_mant0;

wire shift_amount0;
wire shift_amount1;
wire shift_amount2;

wire shifted_mant5;           //small mantissa shifted
wire shifted_mant4;
wire shifted_mant3;
wire shifted_mant2;
wire shifted_mant1;
wire shifted_mant0;

wire big_mant3;              //bigger of the two mantissas
wire big_mant2;
wire big_mant1;
wire big_mant0;

wire temp_sign_B;
wire twos_small_mant5;
wire twos_small_mant4;
wire twos_small_mant3;
wire twos_small_mant2;
wire twos_small_mant1;
wire twos_small_mant0;

wire exp_diff_sign1;
wire exp_diff_sign0;
wire exp_diff_norm2;
wire exp_diff_norm1;
wire exp_diff_norm0;

//divide inputs into FP fields

//find mantissa difference

assign { mant_diff4, mant_diff3, mant_diff2, mant_diff1, mant_diff0 } = { A3, A2, A1,
A0 } - { B3, B2, B1, B0 } ;

assign mant_diffsig = mant_diff4;

```

```

//assign small_mant to be the value of the mantissa of the number with the smaller of the
//two exponents
big_small_mants(A3, A2, A1, A0, B3, B2, B1, B0, exp_diff3, exp_diff2, exp_diff1,
exp_diff0, mant_diffsig, big_mant3, big_mant2, big_mant1, big_mant0, small_mant3,
small_mant2, small_mant1, small_mant0);

assign {shift_amount2, shift_amount1, shift_amount0} = (exp_diff3)? -({exp_diff2,
exp_diff1, exp_diff0}): {exp_diff2, exp_diff1, exp_diff0};

//code for addition or subtraction

assign temp_sign = funct? ~B7: B7;
assign temp_sign_B = temp_sign;

//shift mantissa to align decimal points
right_shifter shift_mantissa(small_mant3, small_mant2, small_mant1, small_mant0,
shift_amount2, shift_amount1, shift_amount0, shifted_mant5, shifted_mant4,
shifted_mant3, shifted_mant2, shifted_mant1, shifted_mant0);

twos_comp two_small_mant(A7, B7, funct, shifted_mant5, shifted_mant4,
shifted_mant3, shifted_mant2, shifted_mant1, shifted_mant0, twos_small_mant5,
twos_small_mant4, twos_small_mant3, twos_small_mant2, twos_small_mant1,
twos_small_mant0);

//add the two mantissas together

assign {temp_mant_Y5, temp_mant_Y4, temp_mant_Y3, temp_mant_Y2,
temp_mant_Y1, temp_mant_Y0} =
    {1'b1, {big_mant3, big_mant2, big_mant1, big_mant0}} +
    {twos_small_mant5, twos_small_mant4, twos_small_mant3, twos_small_mant2,
twos_small_mant1, twos_small_mant0};

//assign zero detect
zero_detect zero_find(A7, B7, funct, exp_diff3, exp_diff2, exp_diff1, exp_diff0,
mant_diff4, mant_diff3, mant_diff2, mant_diff1, mant_diff0, zero);

normalize normal(temp_mant_Y5, temp_mant_Y4, temp_mant_Y3, temp_mant_Y2,
temp_mant_Y1, temp_mant_Y0, Y3, Y2, Y1, Y0, exp_diff_norm2, exp_diff_norm1,
exp_diff_norm0, exp_diff_sign1, exp_diff_sign0);

final_sign sign_find(mant_diffsig, exp_diff3, exp_diff2, exp_diff1, exp_diff0, A7,
temp_sign_B, Y7);

endmodule

```

```

//*****
module zero_detect (A7, B7, funct, exp_diff3, exp_diff2, exp_diff1, exp_diff0,
    mant_diff4, mant_diff3, mant_diff2, mant_diff1, mant_diff0, zero);
    input A7, B7, funct;

    input exp_diff3, exp_diff2, exp_diff1, exp_diff0;
    input mant_diff4, mant_diff3, mant_diff2, mant_diff1, mant_diff0;

    output zero;
    reg zero;

    always@(A7 or B7 or funct or exp_diff3 or exp_diff2 or exp_diff1 or exp_diff0 or
    mant_diff4 or mant_diff3 or
        mant_diff2 or mant_diff1 or mant_diff0)
    if(((A7^B7)^funct)&({exp_diff3, exp_diff2, exp_diff1, exp_diff0} == 4'b0000) &
        ({mant_diff4, mant_diff3, mant_diff2, mant_diff1, mant_diff0} == 5'b00000))
        zero <= 1;
    else
        zero <= 0;

endmodule

//*****
module twos_comp (A7, B7, funct, shifted_mant5, shifted_mant4, shifted_mant3,
    shifted_mant2, shifted_mant1, shifted_mant0, twos_small_mant5, twos_small_mant4,
    twos_small_mant3, twos_small_mant2, twos_small_mant1, twos_small_mant0);

    input A7, B7, funct;
    input shifted_mant5, shifted_mant4, shifted_mant3, shifted_mant2, shifted_mant1,
        shifted_mant0;

    output twos_small_mant5, twos_small_mant4, twos_small_mant3, twos_small_mant2,
        twos_small_mant1, twos_small_mant0;

    //two's compliment of shifted mantissa if numbers are being subtracted or adding
    //a negative number

    assign {twos_small_mant5, twos_small_mant4, twos_small_mant3, twos_small_mant2,
    twos_small_mant1, twos_small_mant0} =
        ((A7^B7)^funct)? -({shifted_mant5, shifted_mant4, shifted_mant3,
    shifted_mant2, shifted_mant1, shifted_mant0}):
        {shifted_mant5, shifted_mant4, shifted_mant3, shifted_mant2, shifted_mant1,
    shifted_mant0};

```

```

endmodule

//*****
module normalize (in_mant5, in_mant4, in_mant3, in_mant2, in_mant1, in_mant0,
                 out_mant3, out_mant2, out_mant1, out_mant0, exp_diff_norm2,
                 exp_diff_norm1, exp_diff_norm0, exp_diff_sign1, exp_diff_sign0);

input in_mant5, in_mant4, in_mant3, in_mant2, in_mant1, in_mant0;

output out_mant3, out_mant2, out_mant1, out_mant0;
output exp_diff_sign1, exp_diff_sign0;
output exp_diff_norm2, exp_diff_norm1, exp_diff_norm0;

reg in_mant5, in_mant4, in_mant3, in_mant2, in_mant1, in_mant0;
reg out_mant3, out_mant2, out_mant1, out_mant0;
reg exp_diff_sign1, exp_diff_sign0;
reg exp_diff_norm2, exp_diff_norm1, exp_diff_norm0;

always@(in_mant5 or in_mant4 or in_mant3 or in_mant2 or in_mant1 or in_mant0)
begin
    if (in_mant5)
        begin
            {out_mant3, out_mant2, out_mant1, out_mant0} <= {in_mant4,
                in_mant3, in_mant2, in_mant1};
            {exp_diff_norm2, exp_diff_norm1, exp_diff_norm0} <= 3'b001;
            {exp_diff_sign1, exp_diff_sign0} <= 2'b01;
        end
    else if (in_mant4)
        begin
            {out_mant3, out_mant2, out_mant1, out_mant0} <= {in_mant3,
                in_mant2, in_mant1, in_mant0};
            {exp_diff_norm2, exp_diff_norm1, exp_diff_norm0} <= 3'b000;
            {exp_diff_sign1, exp_diff_sign0} <= 2'b01;
        end
    else if (in_mant3)
        begin
            {out_mant3, out_mant2, out_mant1, out_mant0} <=
                {{in_mant2, in_mant1, in_mant0}, 1'b0};
            {exp_diff_norm2, exp_diff_norm1, exp_diff_norm0} <= 3'b001;
            {exp_diff_sign1, exp_diff_sign0} <= 2'b10;
        end
    else if (in_mant2)
        begin
            {out_mant3, out_mant2, out_mant1, out_mant0} <= {{in_mant1,
                in_mant0}, 2'b00};
        end
end

```

```

        {exp_diff_norm2, exp_diff_norm1, exp_diff_norm0} <= 3'b010;
        {exp_diff_sign1, exp_diff_sign0} <= 2'b10;
    end
else if (in_mant1)
    begin
        {out_mant3, out_mant2, out_mant1, out_mant0} <= {in_mant0,
        3'b000};
        {exp_diff_norm2, exp_diff_norm1, exp_diff_norm0} <= 3'b011;
        {exp_diff_sign1, exp_diff_sign0} <= 2'b10;
    end
else if (in_mant0)
    begin
        {out_mant3, out_mant2, out_mant1, out_mant0} <= 4'b0000;
        {exp_diff_norm2, exp_diff_norm1, exp_diff_norm0} <= 3'b100;
        {exp_diff_sign1, exp_diff_sign0} <= 2'b10;
    end
else
    begin
        {out_mant3, out_mant2, out_mant1, out_mant0} <= {in_mant3,
        in_mant2, in_mant1, in_mant0};
        {exp_diff_norm2, exp_diff_norm1, exp_diff_norm0} <= 3'b001;
        {exp_diff_sign1, exp_diff_sign0} <= 2'b01;
    end
end
end
endmodule

```

```

//*****
module final_sign (mant_diffsig, exp_diff3, exp_diff2, exp_diff1, exp_diff0, sign_A,
sign_B, sign_Y);

input mant_diffsig;
input exp_diff3, exp_diff2, exp_diff1, exp_diff0;
input sign_A;
input sign_B;

output sign_Y;

reg sign_Y;

always@(mant_diffsig or exp_diff3 or exp_diff2 or exp_diff1 or exp_diff0 or sign_B or
sign_A)
begin
    if (exp_diff3)
        sign_Y <= sign_B;           //if the exp_diffsig is 1 (number B is bigger)
                                   //give sign_Y the sign of B

```

```

else
    begin
        if ({exp_diff3, exp_diff2, exp_diff1, exp_diff0} == 4'b0000)
            //if the exp_diff is 0 (the two exp are equal),
            begin //check the mantissa values
                if (mant_diffsig) //if the mant_diffsig is 1 (B is bigger)
                    sign_Y <= sign_B; //give sign_Y the sign
                                        //of B

                else
                    sign_Y <= sign_A; //if the exp_diff is 0
                                        //and the mant_diffsig
                                        //!= 1

                end //((A and B have the
                    //same exponent but
                    //the difference in the
                    //mantissas are zero or
                    //greater

            else sign_Y <= sign_A;
                //give sign_Y the sign of A
            end //give sign_Y the sign of A if exp_diffsig !=
                //1 (exp_A is bigger)
                //and exp_diff is greater than zero

    end

end

endmodule

//*****
//find which mantissa is bigger

module big_small (A3, A2, A1, A0, B3, B2, B1, B0, exp_diff3, exp_diff2, exp_diff1,
exp_diff0, mant_diffsig, big_mant3, big_mant2, big_mant1, big_mant0, small_mant3,
small_mant2, small_mant1, small_mant0);

input A3, A2, A1, A0;
input B3, B2, B1, B0;
input exp_diff3, exp_diff2, exp_diff1, exp_diff0;
input mant_diffsig;

output big_mant3, big_mant2, big_mant1, big_mant0;
output small_mant3, small_mant2, small_mant1, small_mant0;

reg A3, A2, A1, A0, B3, B2, B1, B0, exp_diff3, exp_diff2, exp_diff1, exp_diff0;
reg big_mant3, big_mant2, big_mant1, big_mant0, small_mant3, small_mant2,
small_mant1, small_mant0;

```

```

always@(A3 or A2 or A1 or A0 or B3 or B2 or B1 or B0 or exp_diff3 or exp_diff2 or
exp_diff1
    or exp_diff0 or mant_diffsig)

    if ({exp_diff3, exp_diff2, exp_diff1, exp_diff0} == 4'b0000)
        begin
            {big_mant3, big_mant2, big_mant1, big_mant0} <=
            (mant_diffsig)? {B3, B2, B1, B0}: {A3, A2, A1, A0};
            {small_mant3, small_mant2, small_mant1, small_mant0} <=
            (mant_diffsig)? {A3, A2, A1, A0}: {B3, B2, B1, B0};
        end
    else
        begin
            {big_mant3, big_mant2, big_mant1, big_mant0} <= (exp_diff3)?
            {B3, B2, B1, B0}: {A3, A2, A1, A0};
            {small_mant3, small_mant2, small_mant1, small_mant0} <=
            (exp_diff3)? {A3, A2, A1, A0}: {B3, B2, B1, B0};
        end
endmodule

```

```

//*****
module right_shifter(small_mant3, small_mant2, small_mant1, small_mant0,
shift_amount2, shift_amount1, shift_amount0, shifted_mant5, shifted_mant4,
shifted_mant3, shifted_mant2, shifted_mant1, shifted_mant0);

input small_mant3, small_mant2, small_mant1, small_mant0;
input shift_amount2, shift_amount1, shift_amount0;

output shifted_mant5, shifted_mant4, shifted_mant3, shifted_mant2, shifted_mant1,
shifted_mant0;

reg small_mant3, small_mant2, small_mant1, small_mant0;
reg shifted_mant5, shifted_mant4, shifted_mant3, shifted_mant2, shifted_mant1,
shifted_mant0;

always@(small_mant3 or small_mant2 or small_mant1 or small_mant0 or shift_amount2
or shift_amount1 or shift_amount0)
    case ({shift_amount2, shift_amount1, shift_amount0})
        3'b000: {shifted_mant5, shifted_mant4, shifted_mant3,
                shifted_mant2, shifted_mant1, shifted_mant0} <=
                {2'b01, {small_mant3, small_mant2, small_mant1,
                small_mant0}};
    endcase

```

```

3'b001:    {shifted_mant5, shifted_mant4, shifted_mant3,
            shifted_mant2, shifted_mant1, shifted_mant0} <=
            {3'b001, {small_mant3, small_mant2, small_mant1}}};

3'b010:    {shifted_mant5, shifted_mant4, shifted_mant3,
            shifted_mant2, shifted_mant1, shifted_mant0} <=
            {4'b0001, {small_mant3, small_mant2}}};

3'b011:    {shifted_mant5, shifted_mant4, shifted_mant3,
            shifted_mant2, shifted_mant1, shifted_mant0} <=
            {5'b00001, small_mant3};

3'b100:    {shifted_mant5, shifted_mant4, shifted_mant3,
            shifted_mant2, shifted_mant1, shifted_mant0} <=
            6'b000001;

default:   {shifted_mant5, shifted_mant4, shifted_mant3,
            shifted_mant2, shifted_mant1, shifted_mant0} <=
            6'b000000;

```

```

    endcase

```

```

endmodule

```

```

//*****

```

```

//exponent stuff

```

```

module exp_part(A6, A5, A4, B6, B5, B4, exp_diff_norm2, exp_diff_norm1,
exp_diff_norm0, exp_diff_sign1, exp_diff_sign0, exp_diff3, exp_diff2, exp_diff1,
exp_diff0, Y6, Y5, Y4);

```

```

input A6, A5, A4, B6, B5, B4, exp_diff_norm2, exp_diff_norm1, exp_diff_norm0;
input exp_diff_sign1, exp_diff_sign0;

```

```

output exp_diff3, exp_diff2, exp_diff1, exp_diff0;
output Y6, Y5, Y4;

```

```

wire exp_diffsig;
wire temp_exp_Y2;
wire temp_exp_Y1;
wire temp_exp_Y0;

```

```

reg Y6, Y5, Y4;

```



```

//find exponent difference

assign {exp_diff3, exp_diff2, exp_diff1, exp_diff0} = {A6, A5, A4} - {B6, B5, B4};

//give the exp_Y the exp value of the bigger exp value
assign {temp_exp_Y2, temp_exp_Y1, temp_exp_Y0} = (exp_diff3)? {B6, B5, B4}: {A6,
A5, A4};

always@(exp_diff_norm2 or exp_diff_norm1 or exp_diff_norm0 or exp_diff_sign1 or
exp_diff_sign0 or
temp_exp_Y2 or temp_exp_Y1 or temp_exp_Y0)

    if(exp_diff_sign1) //if =1 subtract
        {Y6, Y5, Y4} <= ({temp_exp_Y2, temp_exp_Y1, temp_exp_Y0}) -
({exp_diff_norm2, exp_diff_norm1, exp_diff_norm0});


    else //if =0 add
        {Y6, Y5, Y4} <= ({temp_exp_Y2, temp_exp_Y1, temp_exp_Y0}) +
({exp_diff_norm2, exp_diff_norm1, exp_diff_norm0});

endmodule


```



## Exponent Bitslice Schematic

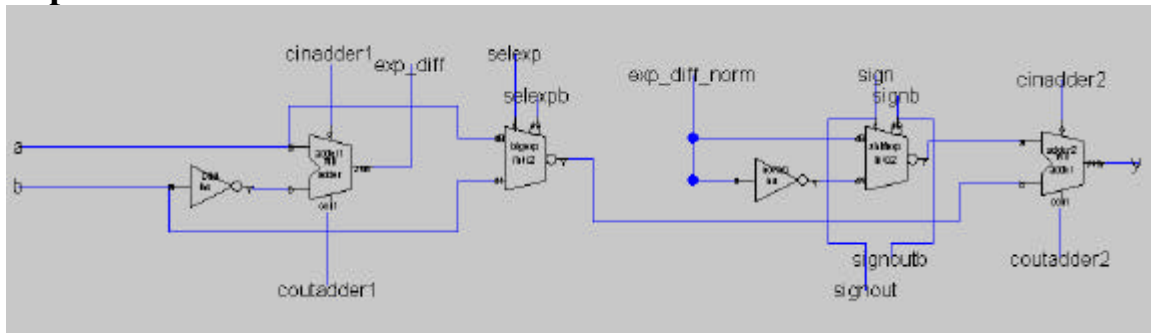

## Exponent Datapath Schematic

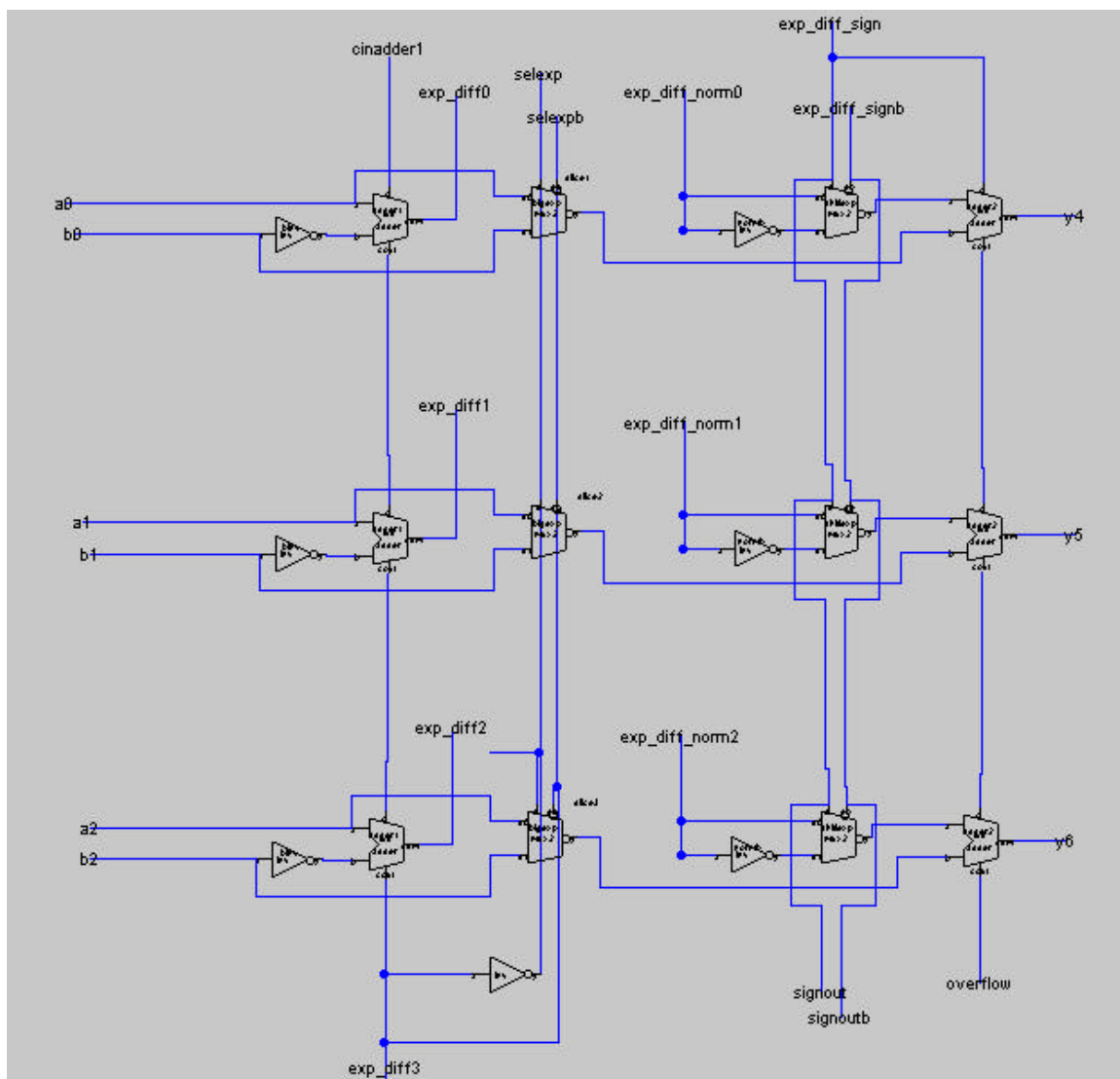


## Exponent and Mantissa Datapath Schematic


You will note that the schematic for the mantissa is missing. A program called data analyzer is supposed to be able to generate a schematic and layout from Verilog code. However, the code cannot contain any hierarchy or busses for data lines. The entire Verilog code was rewritten to accommodate Electric. However, even though the Verilog code does not contain any module calls, it implies an adder and a subtractor. The Data Analyzer program created an adder and a subtractor in submodules. The Data Analyzer has a “Flatten Hierarchy” option, however, when we applied it to the design it said that the operation to flatten hierarchy was too expensive. The Data Analyzer creates a .vhdl file which is supposed to be imported into the Silicon Compiler option in Electric. Electric then reads the .vhdl netlist to create a layout and a schematic of your code. On the off chance that Electric would be able to handle the adder and subtractor submodules, we imported the Data Analyzer result to Electric. However, Electric was unable to create the desired designs since it was unable to handle the .vhdl file sent by the Data Analyzer. There is a slight possibility that one could trick the Data Analyzer into creating the adder without generating a submodule. This would require someone to layout the result of each bit on an adder using logic gates. This problem quickly turns into a gigantic undertaking.

# Layout


## Leaf Cell: Mux2

 

## Leaf Cell: Full Adder Layout

 

## Exponent Bitslice Layout

 

## Exponent Datapath Layout

