

# Logical Effort\*

## Designing for Speed on the Back of an Envelope

David Harris  
David\_Harris@hmc.edu

Harvey Mudd College  
Claremont, CA

\* Based on a book by Ivan Sutherland, Bob Sproull, and David Harris published by Morgan Kaufman, 1999.

## Outline

- Introduction
- Delay in a Logic Gate
- Multi-stage Logic Networks
- Choosing the Best Number of Stages
- Example
- Summary

## Introduction

Chip designers face a bewildering array of choices.

- What is the best circuit topology for a function?
- How large should the transistors be?
- How many stages of logic give least delay?



Logical Effort is a method of answering these questions:


- Uses a very simple model of delay
- Back of the envelope calculations and tractable optimization
- Gives new names to old ideas to emphasize remarkable symmetries

Who cares about logical effort?

- Circuit designers waste too much time simulating and tweaking circuits
- High speed logic designers need to know where time is going in their logic
- CAD engineers need to understand circuits to build better tools
 
## Example

Ben Bitdiddle is the memory designer for the Motorola 68W86, an embedded processor for automotive applications. Help Ben design the decoder for a register file:



Decoder specification:

- 16 word register file
- Each word is 32 bits wide
- Each bit presents a load of 3 unit-sized transistors
- True and complementary inputs of address bits  $a\langle 3:0 \rangle$  are available
- Each input may drive 10 unit-sized transistors

Ben needs to decide:

- How many stages to use?
- How large should each gate be?
- How fast can the decoder operate?

## Outline

- Introduction
- Delay in a Logic Gate**
- Multi-stage Logic Networks
- Choosing the Best Number of Stages
- Example
- Summary

## Delay in a Logic Gate

Let us express delays in a process-independent unit:

$$d = \frac{d_{abs}}{\tau}$$

$\tau \approx 20$  ps  
in  $0.25 \mu\text{m}$   
technology

Delay of logic gate has two components:

$$d = f + p$$

↖ effort delay, a.k.a. stage effort  
↖ parasitic delay

Effort delay again has two components:


$$f = gh$$

↖ logical effort  
↖ electrical effort =  $C_{out}/C_{in}$

electrical effort is sometimes called "fanout"

- Logical effort describes relative ability of gate topology to deliver current (defined to be 1 for an inverter)
- Electrical effort is the ratio of output to input capacitance

## Delay Plots

 


How about a 2-input NOR?

- $d = f + p = gh + p$
- Delay increases with electrical effort
- More complex gates have greater logical effort and parasitic delay
 
## Computing Logical Effort

DEF: Logical effort is the ratio of the input capacitance of a gate to the input capacitance of an inverter delivering the same output current.

- Measured from delay vs. fanout plots of simulated or measured gates
- Or estimated, counting capacitance in units of transistor width:



## A Catalog of Gates

**Table 1: Logical effort of static CMOS gates**

Gate type	Number of inputs					
	1	2	3	4	5	$n$
inverter	1					
NAND		4/3	5/3	6/3	7/3	$(n+2)/3$
NOR		5/3	7/3	9/3	11/3	$(2n+1)/3$
multiplexer		2	2	2	2	2
XOR, XNOR		4	12	32		


**Table 2: Parasitic delay of static CMOS gates**

Gate type	Parasitic delay
inverter	$p_{inv}$
$n$ -input NAND	$np_{inv}$
$n$ -input NOR	$np_{inv}$
$n$ -way multiplexer	$2np_{inv}$
2-input XOR, XNOR	$4np_{inv}$

$p_{inv} \approx 1$   
parasitic delays  
depend on diffusion  
capacitance
 
## Example

Estimate the frequency of an  $N$ -stage ring oscillator:



Logical Effort:  $g =$

Electrical Effort:  $h =$


Parasitic Delay:  $p =$

Stage Delay:  $d =$

Oscillator Frequency:  $F =$
 
## Example

Estimate the delay of a fanout-of-4 (FO4) inverter:



Logical Effort:  $g =$

Electrical Effort:  $h =$

Parasitic Delay:  $p =$


Stage Delay:  $d =$

## Outline

- Introduction
- Delay in a Logic Gate
- Multi-stage Logic Networks**
- Choosing the Best Number of Stages
- Example
- Summary
 
## Multi-stage Logic Networks

Logical effort extends to multi-stage networks:




$$\begin{array}{llll} g_1 = 1 & g_2 = 5/3 & g_3 = 4/3 & g_4 = 1 \\ h_1 = x/10 & h_2 = y/x & h_3 = z/y & h_4 = 20/z \end{array}$$

- Path Logical Effort:  $G = \prod g_i$
  - Path Electrical Effort:  $H = \frac{C_{out}(path)}{C_{in}(path)}$
  - Path Effort:  $F = \prod f_i = \prod g_i h_i$
- Don't define  $H = \prod h_i$  because we don't know  $h_i$  until the design is done

Can we write  $F = GH$ ?

## Branching Effort

No! Consider circuits that branch:

 

$$\begin{array}{l} G = \\ H = \\ GH = \\ h_1 = \\ h_2 = \\ F = \end{array} = GH?$$

## Delay in Multi-stage Networks

We can now compute the delay of a multi-stage network:

- Path Effort Delay:  $D_F = \sum f_i$
- Path Parasitic Delay:  $P = \sum p_i$
- Path Delay:  $D = \sum d_i = D_F + P$

We can prove that delay is minimized when each stage bears the same effort:

$$\hat{f} = g_i h_i = F^{1/N}$$

Therefore, the minimum delay of an  $N$ -stage path is:

$$\boxed{NF^{1/N} + P}$$

- This is a **key** result of logical effort. Lowest possible path delay can be found without even calculating the sizes of each gate in the path.

## Determining Gate Sizes

Gate sizes can be found by starting at the end of the path and working backward.


- At each gate, apply the capacitance transformation:

$$C_{in_i} = \frac{C_{out_i} \cdot g_i}{\hat{f}}$$

- Check your work by verifying that the input capacitance specification is satisfied at the beginning of the path.
 
## Example

Select gate sizes  $y$  and  $z$  to minimize delay from  $A$  to  $B$



Logical Effort:  $G =$

Electrical Effort:  $H =$

Branching Effort:  $B =$

Path Effort:  $F =$

Best Stage Effort:  $\hat{f} =$

Delay:  $D =$

Work backward for sizes:

$z =$

$y =$


## Outline

- Introduction
- Delay in a Logic Gate
- Multi-stage Logic Networks
- Choosing the Best Number of Stages**
- Example
- Summary
 
## Choosing the Best Number of Stages

How many stages should a path use?

- Delay is not always minimized by using as few stages as possible
- Example: How to drive 64 bit datapath with unit-sized inverter




$$D = NF^{1/N} + P = N(64)^{1/N} + N \text{ assuming polarity doesn't matter}$$
 
## Derivation of the Best Number of Stages

Suppose we can add inverters to the end of a path without changing its function.

- How many stages should we use? Let  $\hat{N}$  be the value of  $N$  for least delay.



$$D = NF^{1/N} + \sum_1^{n_1} p_i + (N - n_1) p_{inv}$$

$$\frac{\partial D}{\partial N} = -F^{1/N} \ln(F^{1/N}) + F^{1/N} + p_{inv} = 0$$

- Define  $\rho \equiv F^{1/\hat{N}}$  to be the best stage effort. Substitute and simplify:


$$p_{inv} + \rho(1 - \ln \rho) = 0$$

## Best Number of Stages (continued)

$p_{inv} + \rho(1 - \ln p) = 0$  has no closed form solution.

- Neglecting parasitics (i.e.  $p_{inv} = 0$ ), we get the familiar result that  $\rho = 2.718$  (e)
- For  $p_{inv} = 1$ , we can solve numerically to obtain  $\rho = 3.59$

 How sensitive is the delay to using exactly the best number of stages?




- $2.4 < \rho < 6$  gives delays within 15% of optimal -> we can be sloppy

## Outline

- Introduction
- Delay in a Logic Gate
- Multi-stage Logic Networks
- Choosing the Best Number of Stages
- Example**
- Summary
 
## Example

Let's revisit Ben Bitdiddle's decoder problem using logical effort:



Decoder specification:

- 16 word register file
- Each word is 32 bits wide
- Each bit presents a load of 3 unit-sized transistors
- True and complementary inputs of address bits  $a\langle 3:0 \rangle$  are available
- Each input may drive 10 unit-sized transistors

Ben needs to decide:

- How many stages to use?
- How large should each gate be?
- How fast can the decoder operate?

## Example: Number of Stages

How many stages should Ben use?

- Effort of decoders is dominated by electrical and branching portions
- Electrical Effort:  $H =$
- Branching Effort:  $B =$

If we neglect logical effort (assume  $G = 1$ ),


- Path Effort:  $F =$

Remember that the best stage effort is about  $\rho = 4$

- Hence, the best number of stages is:  $N =$
 
## Example: Gate Sizes & Delay

Lets try a 3-stage design using 16 4-input NAND gates with  $G =$



- Actual path effort is:  $F =$
- Therefore, stage effort should be:  $f =$
- Gate sizes:  $z =$   $y =$
- Path delay:  $D =$

## Example: Alternative Decoders

Table 3: Comparison of Decoder Designs

Design	Stages	G	P	D
NAND4; INV	2	2	5	29.8
INV; NAND4; INV	3	2	6	22.1
INV; NAND4; INV; INV	4	2	7	21.1
NAND2; INV; NAND2; INV	4	16/9	6	19.7
INV; NAND2; INV; NAND2; INV	5	16/9	7	20.4
NAND2; INV; NAND2; INV; INV; INV	6	16/9	8	21.6
INV; NAND2; INV; NAND2; INV; INV; INV	7	16/9	9	23.1
NAND2; INV; NAND2; INV; INV; INV; INV; INV	8	16/9	10	24.8

We underestimated the best number of stages by neglecting the logical effort.

- Logical effort facilitates comparing different designs before selecting sizes
- Using more stages also reduces G and P by using multiple 2-input gates
- Our design was about 10% slower than the best

## Outline

- Introduction
- Delay in a Logic Gate
- Multi-stage Logic Networks
- Choosing the Best Number of Stages
- Example
- Summary**

## Summary

Table 4: Key Definitions of Logical Effort

Term	Stage expression	Path expression
Logical effort	$g$ (see Table 1)	$G = \prod g_i$
Electrical effort	$h = \frac{C_{out}}{C_{in}}$	$H = \frac{C_{out (path)}}{C_{in (path)}}$
Branching effort	n/a	$B = \prod b_i$
Effort	$f = gh$	$F = GBH$
Effort delay	$f$	$D_F = \sum f_i$
Number of stages	1	$N$
Parasitic delay	$p$ (see Table 2)	$P = \sum p_i$
Delay	$d = f + p$	$D = D_F + P$

## Method of Logical Effort

Logical effort helps you find the best number of stages, the best size of each gate, and the minimum delay of a circuit with the following procedure:

- ❑ Compute the path effort:  $F = GBH$
- ❑ Estimate the best number of stages:  $\hat{N} \approx \log_4 F$
- ❑ Estimate the minimum delay:  $D = \hat{N}F^{1/\hat{N}} + P$
- ❑ Sketch your path using the number of stages computed above
- ❑ Compute the stage effort:  $\hat{f} = F^{1/\hat{N}}$
- ❑ Starting at the end, work backward to find transistor sizes:

$$C_{in_i} = \frac{C_{out_i} \cdot g_i}{\hat{f}}$$

## Limitations of Logical Effort

Logical effort is not a panacea. Some limitations include:

- ❑ **Chicken & egg problem**  
how to estimate G and best number of stages before the path is designed
- ❑ **Simplistic delay model**  
neglects effects of input slopes
- ❑ **Interconnect**  
iteration required in designs with branching and non-negligible wire C or RC  
same convergence difficulties as in synthesis / placement problem
- ❑ **Maximum speed only**  
optimizes circuits for speed, not area or power under a fixed speed constraint

## Conclusion

Logical effort is a useful concept for thinking about delay in circuits:

- ❑ Facilitates comparison of different circuit topologies
- ❑ Easily select gate sizes for minimum delay
- ❑ Circuits are fastest when effort delays of each stage are equal and about 4
- ❑ Path delay is insensitive to modest deviations from optimal sizes


Some further results from logical effort include:

- ❑ Logical effort can be applied to domino, pass gate, and other logic families
- ❑ Logic gates can be skewed to favor one input or edge at the cost of another
- ❑ While the logical effort of a multiplexer is independent of the number of inputs, parasitic delay increases with size, so 4-way multiplexers are best
- ❑ Circuits that fork should equalize delays between legs of the fork

A book on Logical Effort will be available in Feb. 1999 from Morgan Kaufmann

[http://www.mkp.com/Logical\\_Effort](http://www.mkp.com/Logical_Effort)

## Delay Plots

 


- ❑  $d = f + p = gh + p$
- ❑ Delay increases with electrical effort
- ❑ More complex gates have greater logical effort and parasitic delay


 
## Example

Estimate the frequency of an  $N$ -stage ring oscillator:



Logical Effort:  $g \equiv 1$

Electrical Effort:  $h = \frac{C_{out}}{C_{in}} = 1$

Parasitic Delay:  $p = p_{inv} \approx 1$


Stage Delay:  $d = gh + p = 2$

Oscillator Frequency:  $F = \frac{1}{2Nd_{abs}} = \frac{1}{4N\tau}$

A 31 stage ring oscillator in a  $0.25 \mu\text{m}$  process oscillates at about 400 MHz.
 
## Example

Estimate the delay of a fanout-of-4 (FO4) inverter:



Logical Effort:  $g \equiv 1$

Electrical Effort:  $h = \frac{C_{out}}{C_{in}} = 4$

Parasitic Delay:  $p = p_{inv} \approx 1$

Stage Delay:  $d = gh + p = 5$


The FO4 inverter delay is a useful metric to characterize process performance.

1 FO4 delay =  $5\tau$

This is about 100 ps in a  $0.25 \mu\text{m}$  process.

## Branching Effort

No! Consider circuits that branch:

 

$$\begin{aligned} G &= 1 \\ H &= 90 / 5 = 18 \\ GH &= 18 \\ h_1 &= (15+15) / 5 = 6 \\ h_2 &= 90 / 15 = 6 \\ F &= 36, \text{ not } 18! \end{aligned}$$

Introduce new kind of effort to account for branching within a network:

Branching Effort:  $b = \frac{C_{on\ path} + C_{off\ path}}{C_{on\ path}}$

Path Branching Effort:  $B = \prod b_i$

Note:

$$\prod h_i = BH \neq H$$


in circuits that branch

Now we can compute the path effort:

Path Effort:  $F = GBH$
 
## Example

Select gate sizes  $y$  and  $z$  to minimize delay from  $A$  to  $B$



Logical Effort:  $G = (4/3)^3$

Electrical Effort:  $H = \frac{C_{out}}{C_{in}} = 4.5$

Branching Effort:  $B = 2 \cdot 3 = 6$

Path Effort:  $F = GHB = 64$

Best Stage Effort:  $\hat{f} = F^{1/3} = 4$

Delay:  $D = 3 \cdot 4 + 3 \cdot 2 = 18$

Work backward for sizes:

$$z = \frac{4.5C \cdot (4/3)}{4} = 1.5C$$

$$y = \frac{3z \cdot (4/3)}{4} = 1.5C$$

## Example: Number of Stages

How many stages should Ben use?

- ❑ Effort of decoders is dominated by electrical and branching portions
- ❑ Electrical Effort:  $H = \frac{32 \cdot 3}{10} = 9.6$
- ❑ Branching Effort:  $B = 8$  because each address input controls half the outputs

If we neglect logical effort,


- ❑ Path Effort:  $F = GBH = 8 \cdot 9.6 = 76.8$

Remember that the best stage effort is about  $\rho = 4$

- ❑ Hence, the best number of stages is:  $N = \log_4 76.8 = 3.1$
- ❑ Let's try a 3-stage design
 
## Example: Gate Sizes & Delay

Lets try a 3-stage design using 16 4-input NAND gates with  $G = 1 \cdot 2 \cdot 1 = 2$



- ❑ Actual path effort is:  $F = 2 \cdot 8 \cdot 9.6 = 154$
- ❑ Therefore, stage effort should be:  $f = (154)^{1/3} = 5.36$  ← Close to 4, so  $f$  is reasonable
- ❑  $z = 96 \cdot 1/5.36 = 18$       $y = 18 \cdot 2/5.36 = 6.7$
- ❑  $D = 3f + P = 3 \cdot 5.36 + 1 + 4 + 1 = 22.1$