


Lecture 11: Sequential Circuit Design

Outline

- Sequencing
- Sequencing Element Design
- Max and Min-Delay
- Clock Skew
- Time Borrowing
- Two-Phase Clocking

Sequencing

 - ❑ *Combinational logic*
 - output depends on current inputs
- ❑ *Sequential logic*
 - output depends on current and previous inputs
 - Requires separating previous, current, future
 - Called *state* or *tokens*
 - Ex: FSM, pipeline



Sequencing Cont.


- ❑ If tokens moved through pipeline at constant speed, no sequencing elements would be necessary
- ❑ Ex: fiber-optic cable
 - Light pulses (tokens) are sent down cable
 - Next pulse sent before first reaches end of cable
 - No need for hardware to separate pulses
 - But *dispersion* sets min time between pulses
- ❑ This is called *wave pipelining* in circuits
- ❑ In most circuits, dispersion is high
 - Delay fast tokens so they don't catch slow ones.

Sequencing Overhead

- ❑ Use flip-flops to delay fast tokens so they move through exactly one stage each cycle.
- ❑ Inevitably adds some delay to the slow tokens
- ❑ Makes circuit slower than just the logic delay
 - Called sequencing overhead
- ❑ Some people call this clocking overhead
 - But it applies to asynchronous circuits too
 - Inevitable side effect of maintaining sequence

Sequencing Elements

 - ❑ **Latch:** Level sensitive
 - a.k.a. transparent latch, D latch
- ❑ **Flip-flop:** edge triggered
 - A.k.a. master-slave flip-flop, D flip-flop, D register
- ❑ **Timing Diagrams**
 - Transparent
 - Opaque
 - Edge-trigger



Latch Design

- ❑ Pass Transistor Latch

- ❑ Pros

 - +

 - +

- ❑ Cons

 -


 -

 -

 -

 -

 -

 


Used in 1970's

Latch Design

□ Transmission gate

+


-

 

Latch Design

❑ Inverting buffer

- + -
- + -
- + Fixes either
 - -
 - -
-

 


Latch Design

❑ Tristate feedback

+

-

 ❑ Static latches are now essential because of leakage




Latch Design

□ Buffered input

+

+

 


Latch Design

❑ Buffered output

+

❑ Widely used in standard cells

 
- + Very robust (most important)
- Rather large
- Rather slow (1.5 – 2 FO4 delays)
- High clock loading



Latch Design


□ Datapath latch

- +
- +
-

 


Flip-Flop Design

 - ❑ Flip-flop is built as pair of back-to-back latches




Enable

 - ❑ Enable: ignore clock when $en = 0$
 - Mux: increase latch D-Q delay
 - Clock Gating: increase en setup time, skew




Reset

 - ❑ Force output low when reset asserted
- ❑ Synchronous vs. asynchronous




Set / Reset

 - ❑ Set forces output high when enabled
- ❑ Flip-flop with asynchronous set and reset



Sequencing Methods






 
- ❑ Flip-flops
- ❑ 2-Phase Latches
- ❑ Pulsed Latches



Timing Diagrams


Contamination and Propagation Delays

t_{pd}	Logic Prop. Delay
t_{cd}	Logic Cont. Delay
t_{pcq}	Latch/Flop Clk->Q Prop. Delay
t_{ccq}	Latch/Flop Clk->Q Cont. Delay
t_{pdq}	Latch D->Q Prop. Delay
t_{cdq}	Latch D->Q Cont. Delay
t_{setup}	Latch/Flop Setup Time
t_{hold}	Latch/Flop Hold Time

      


Max-Delay: Flip-Flops
 
$$t_{pd} \leq T_c - \underbrace{\quad}_{\text{sequencing overhead}}$$




Max Delay: 2-Phase Latches
 
$$t_{pd} = t_{pd1} + t_{pd2} \leq T_c - \underbrace{\quad}_{\text{sequencing overhead}}$$





Max Delay: Pulsed Latches
 
$$t_{pd} \leq T_c - \underbrace{\max(\quad)}_{\text{sequencing overhead}}$$



Min-Delay: Flip-Flops

$$t_{cd} \geq$$

  


Min-Delay: 2-Phase Latches

$$t_{cd1}, t_{cd2} \geq$$

Hold time reduced by nonoverlap

Paradox: hold applies twice each cycle, vs. only once for flops.


But a flop is made of two latches!

 

Min-Delay: Pulsed Latches

$$t_{cd} \geq$$


Hold time increased
by pulse width

 

Time Borrowing

- ❑ In a flop-based system:
 - Data launches on one rising edge
 - Must setup before next rising edge
 - If it arrives late, system fails
 - If it arrives early, time is wasted
 - Flops have hard edges
- ❑ In a latch-based system
 - Data can pass through latch while transparent
 - Long cycle of logic can borrow time into next
 - As long as each loop completes in one cycle

Time Borrowing Example

 


How Much Borrowing?

2-Phase Latches

$$t_{\text{borrow}} \leq \frac{T_c}{2} - (t_{\text{setup}} + t_{\text{nonoverlap}})$$

Pulsed Latches
 
$$t_{\text{borrow}} \leq t_{pw} - t_{\text{setup}}$$





Clock Skew

- ❑ We have assumed zero clock skew
- ❑ Clocks really have uncertainty in arrival time
 - Decreases maximum propagation delay
 - Increases minimum contamination delay
 - Decreases time borrowing

Skew: Flip-Flops

$$t_{pd} \leq T_c - \underbrace{(t_{pcq} + t_{setup} + t_{skew})}_{\text{sequencing overhead}}$$
  
$$t_{cd} \geq t_{hold} - t_{ccq} + t_{skew}$$




Skew: Latches

2-Phase Latches

$$t_{pd} \leq T_c - \underbrace{(2t_{pdq})}_{\text{sequencing overhead}}$$

$$t_{cd1}, t_{cd2} \geq t_{\text{hold}} - t_{ccq} - t_{\text{nonoverlap}} + t_{\text{skew}}$$
 
$$t_{\text{borrow}} \leq \frac{T_c}{2} - (t_{\text{setup}} + t_{\text{nonoverlap}} + t_{\text{skew}})$$



Pulsed Latches

$$t_{pd} \leq T_c - \underbrace{\max(t_{pdq}, t_{pcq} + t_{\text{setup}} - t_{pw} + t_{\text{skew}})}_{\text{sequencing overhead}}$$

$$t_{cd} \geq t_{\text{hold}} + t_{pw} - t_{ccq} + t_{\text{skew}}$$


$$t_{\text{borrow}} \leq t_{pw} - (t_{\text{setup}} + t_{\text{skew}})$$

Two-Phase Clocking

- ❑ If setup times are violated, reduce clock speed
- ❑ If hold times are violated, chip fails at any speed
- ❑ In this class, working chips are most important
 - No tools to analyze clock skew
- ❑ An easy way to guarantee hold times is to use 2-phase latches with big nonoverlap times
- ❑ Call these clocks ϕ_1 , ϕ_2 (ph1, ph2)

Safe Flip-Flop


 
- ❑ Past years used flip-flop with nonoverlapping clocks
 - Slow – nonoverlap adds to setup time
 - But no hold times
- ❑ In industry, use a better timing analyzer
 - Add buffers to slow signals if hold time is at risk



Adaptive Sequencing

❑ Designers include timing margin

  - Voltage
- Temperature
- Process variation
- Data dependency
- Tool inaccuracies



❑ Alternative: run faster and check for near failures

- Idea introduced as “Razor”
 - Increase frequency until at the verge of error
 - Can reduce cycle time by ~30%

Summary

- ❑ Flip-Flops:
 - Very easy to use, supported by all tools
- ❑ 2-Phase Transparent Latches:
 - Lots of skew tolerance and time borrowing
- ❑ Pulsed Latches:
 - Fast, some skew tol & borrow, hold time risk

	Sequencing overhead ($T_c - t_{pd}$)	Minimum logic delay t_{cd}	Time borrowing t_{borrow}
Flip-Flops	$t_{pcq} + t_{setup} + t_{skew}$	$t_{hold} - t_{ccq} + t_{skew}$	0
Two-Phase Transparent Latches	$2t_{pdq}$	$t_{hold} - t_{ccq} - t_{nonoverlap} + t_{skew}$ in each half-cycle	$\frac{T_c}{2} - (t_{setup} + t_{nonoverlap} + t_{skew})$
Pulsed Latches	$\max(t_{pdq}, t_{pcq} + t_{setup} - t_{p\omega} + t_{skew})$	$t_{hold} - t_{ccq} + t_{p\omega} + t_{skew}$	$t_{p\omega} - (t_{setup} + t_{skew})$