 


SHA-1 Cryptographic Hash Unit

Kyle Baran and Will Buik

E158

April 19, 2010



Introduction

The goal of this project was to create a functioning implementation of the SHA-1 cryptographic hash algorithm. The SHA-1 algorithm takes in a message of up to $2^{64}-1$ bits and produces a unique 160-bit hash code. The hash code is computed through a series of nonlinear functions and rotations of temporary 32-bit values until the entire message has been encoded. This design was intended to be implemented on a 1.5x1.5 mm 40-pin MOSIS “TinyChip” fabricated in a 0.6 μm process.

Specifications

The SHA-1 cryptographic hash algorithm operates on 32-bit words, and processes 16 word long message blocks in an iterative process consisting of 80 rounds. The algorithm maintains a five word state that each round modifies to produce the final hash. To process each message block, the five word state is copied, each round modifies the copy, and it is then added to the original state. The algorithm extends the 16 word message into an 80 word message, but since each extended message word depends only on the previous 16, only 16 words of storage are needed to handle the message extension. The algorithm as implemented requires 16 words of storage for the message block, ten words of storage for the state, two words of storage for temporary values, and ten hard coded constant values. Further details of the SHA1 algorithm may be found in Appendix C.

Architecture

The core is broken down into three top level cells: a controller, counter bank, and datapath. The controller was synthesized from Verilog code, while the counter bank and datapath, both of which express a higher degree of regularity, were laid out by hand. The datapath contains two memory banks, a ROM, a single temporary register implemented as a flip flop, an ALU, and an input output direction selector. The counter bank consists of three five-bit counters and are used by the controller to keep track of rounds and memory locations. Finally, the controller directs the multiplexors and tristates in the datapath and interfaces the counters to coordinate the SHA-1 algorithm.

Since the SHA-1 algorithm operates on 32-bit words, it was decided that the inputs and outputs would also be 32 bits wide. Because there are only 40 pins on the TinyChip, it was determined that the input and output words would have to share the same pins. This was found to not be a problem since the design uses additional pins to control whether it is inputting or outputting data, making it impossible for data to be moving in both directions at the same time. Table 1 shows the inputs and outputs of the chip.

Pin Name	Direction	Width
vdd	Input	1
gnd	Input	1
io	Input/Output	32
ph1	Input	1
ph2	Input	1
Reset	Input	1

Block	Input	1
Hash	Output	1
Ready	Output	1

Table 1: Listing of SHA-1 Inputs and Outputs

VDD and GND are the power and ground lines for the chip. IO is the shared input and output pins. Ph1 and Ph2 are two-phase non-overlapping clocks. Reset is the global reset for all of the cells. Block signals that the chip should input a sixteen word message block on the subsequent sixteen cycles. Hash signals that the chip should output the five word hash on the subsequent five cycles. Ready indicates that the chip can accept a message block or output the hash. In addition, Ready indicates the direction of the input output pins. When Ready is high, the io pins are in input mode.

SRAM

The SRAM was responsible for storing the sixteen 32-bit words that make up the 512-bit message block. This cell contained an address buffer and 16 single-word SRAM cells.

Memory and Constant Bank

The memory and constant bank was responsible for storing the words of state as well as the constants used in the algorithm. It contained a ROM/RAM block made up of a 9-word mask ROM and an 11-element SRAM block; a flip-flop to control the data flow into the SRAM; and a 2-input mux to choose between the SRAM and ROM outputs. Though the SHA-1 algorithm uses 10 constants, one of those constants is zero, which does not need to be masked. The SRAM and ROM cells are interlaced to share the SRAM decoders.

ALU

The ALU was responsible for performing all of the calculations for the algorithm. It contained a “Shift A” cell that selected between unshifted, 5-bit left shifted, or 30-bit left shifted values of data coming from the temporary flip-flop, a “Shift B” cell that selected between unshifted and 1-bit left shifted values of data from either the SRAM or Memory and Constant Bank, an inverter, an inverting xnor cell, an inverting fulladder, a nand gate, and multiplexors to select the operation.

Flip-Flop

The flip-flop was used to hold temporary values outputted by the ALU. These values would later be passed back into the ALU for further processing.

I/O Selection Block

The I/O select block determined whether to pass the data coming out of the ALU back into the datapath or to the output pins.

The schematics and layouts of all custom blocks may be seen in Appendix B.

Floor Plan:

The final floor plan consumed almost twice as much area as the initial estimate, as seen in Figure 1. This was due primarily to the decision to implement the full SHA1 algorithm instead of the initially proposed version which would have acted on 8-bit data words. The final controller became larger because more states were required to handle the full algorithm and the datapath grew as it became 32 bits wide rather than 8. In addition, the initial estimate did not integrate the 16 Word Shift Register into the datapath and the final version of the chip separated the three counters from the synthesized controller.

The controller and counter bank both used standard muddlib10 cells, inverting every other row to share VDD and ground lines. These blocks had a pitch of 90 lambda and were six rows and five rows tall respectively. The datapath, however, could not use standard muddlib10 cells as they were too large to fit all 32 slices reasonably onto the chip. As such, reduced height cells were designed with to be six wiring tracks tall rather than eight. The datapath consisted of three zipper rows using muddlib10 cells at 110 lambda pitch, and 32 rows of reduced height cells at a 70 lambda pitch by inverting every other row. The ground plane for the first zipper row was shared with the 32nd row of reduced height cells.

The third row of zippers was used for write address decoding and buffering, the second row of zippers was used for read address decoding and buffering, and the first row of zippers was general purpose. Except for the memories, all word slices had a single row of zipper logic. The memory banks required all three rows for address decoding, and had address line buffers hanging off to the side. These address line buffers fit over the other word slice zippers since they only used the first zipper row.

The sliceplans of the datapath, ALU, and IOSelect modules are shown in Figure 2. The pinout of the chip can be seen in Figure 3.



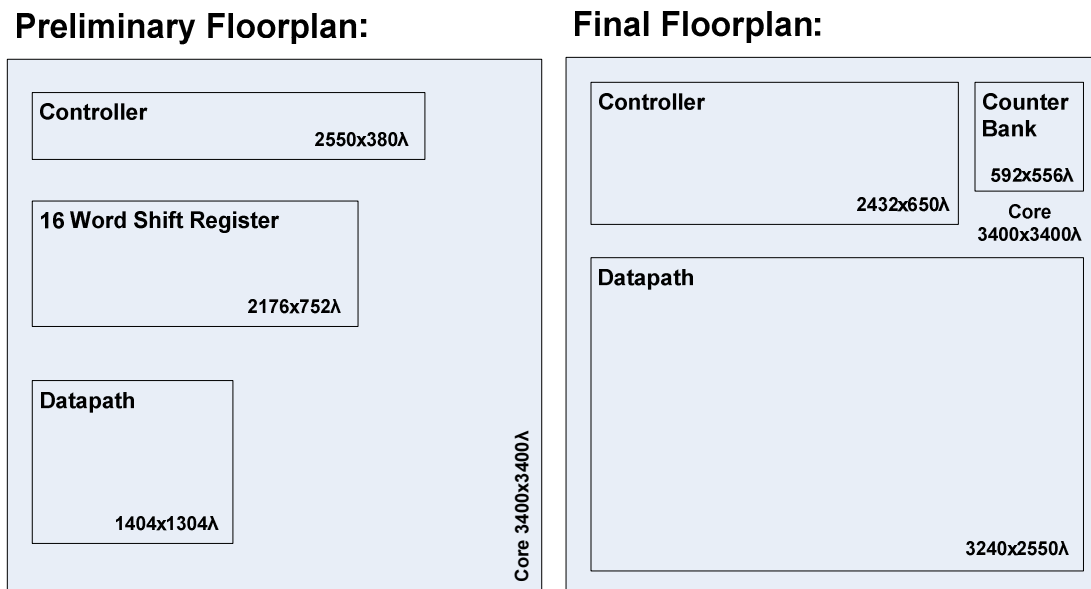


Figure 1: Preliminary and Final Floorplans.


Datapath Slice Plan

 

ALU Slice Plan

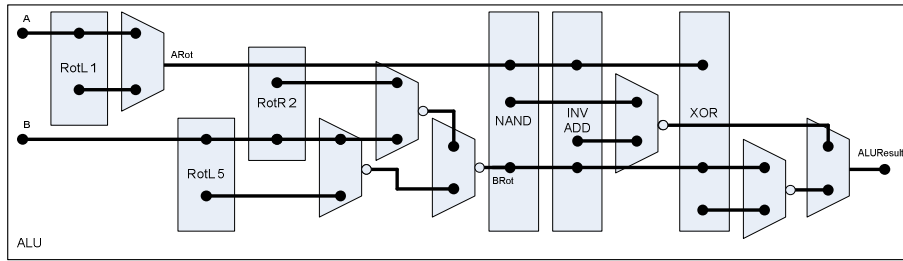

IOSelect Slice Plan

 

Slice plan of Datapath, ALU, and IOSelect.

Figure 2: Slice Plans of the Datapath, ALU and IOSelect.

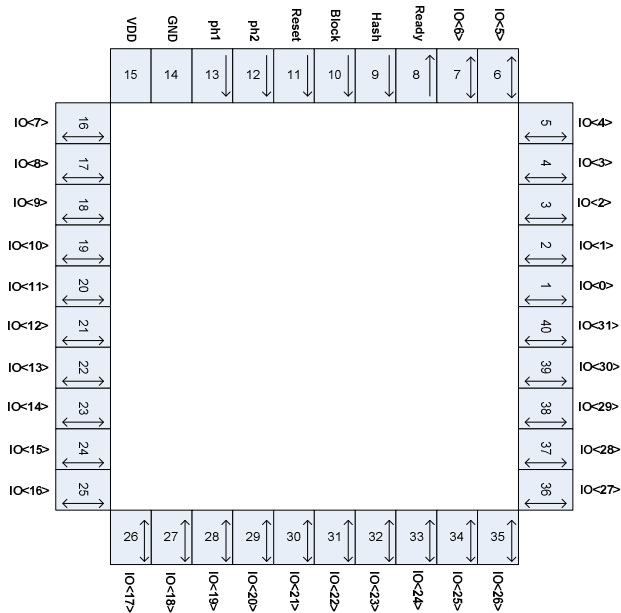


Figure 3: Pinout Diagram

Verification:

The design was first verified as a Verilog model. A test bench generator was written, the code for which is in Appendix D. This generator was verified against a known working implementation of the SHA-1 algorithm. A self checking test bench was designed to test the Verilog model. It tested only a single random message block, but due to the nature of the SHA-1 algorithm any small error propagates to the final hash, often drastically changing the result. The Verilog model was designed to be as close to the actual design as possible, and can be found in Appendix A.

Next, the schematics of each cell were designed using the Virtuoso Schematic Editor. Each was netlisted and plugged in individually to the Verilog model to verify functionality. The controller was synthesized from the Verilog model since it had little regularity and would not benefit from being constructed by hand. Once the design was completed up to the core schematic, the netlisted design could be tested alone with the same self checking test bench used to verify the Verilog model.

The only discrepancy in net listing was an intermittent error that caused the inverting 32 bit full adder to sometimes not netlist correctly. Sometimes invalid verilog code for this schematic was generated, that cut off before the proper end of the line. To handle this, a working copy of the inverting 32 bit full adder netlist was saved from one of the times it netlisted properly and used in the event that it did not.

Next, each cell was laid out using layout of the chip using the Virtuoso Layout Editor. The controller layout was synthesized using SOC Encounter. DRC and LVS were used to ensure that the layouts did not violate design rules and that logical netlist and transistor parameters matched the schematics.

All cells passed DRC, and all cells except the datapath passed LVS. The team ran out of time while wiring the datapath, and as a result it did not pass LVS. Since the datapath layout was not complete, the core layout was not auto routed or placed into a padframe. As such a CIF could not be created.

Had the datapath been completed, the core layout would have been auto routed and placed into a padframe. To verify the function of the chip, the top level chip schematic containing padframe and core would have been netlisted and verified against the same self checking test bench used for the core. Assuming the chip layout passed DRC and LVS, it would have been exported to a CIF, and then re-imported to verify that DRC and LVS still passed.

Post-Fabrication Test Plan:

Due to the tight spacing of elements on the chip, adding a self testing feature to the device was infeasible. As such, the chip must be tested using its standard operating procedure. To do this, the chip must be restarted, a sample message loaded into its memory, and the hash value compared to a known value. A programmable microcontroller may be used to test the chip. Due to the iterative and cryptographic natures of the SHA1 algorithm, a single sample message is sufficient to test all facilities of the chip. Since each of the 80 rounds is designed to introduce a high degree of entropy into the algorithm's state, this single test message will likely hit all corner cases of the device. Additionally, any

error that occurs during the progress of the algorithm will propagate to the final hash output, making failures simple to detect.

Errors in the controller or counters will cause the hash output to be incorrect if they cause the controller to improperly control the datapath. If the next state logic fails, the hash output will either be incorrect, or the chip will never reach the ready state to load the data or to output the hash. Errors in the datapath will cause the hash value to be incorrect.

By carefully selecting the test message, which consists of 16 32-bit words of input and five 32-bit words of expected output, stuck at failures for the input-output pins can be detected. The test input should ensure that every pin is asserted high and low, and should be chosen such that the hash produced causes the pins to be asserted both high and low when outputting the five result words. If any of the controller input or output pins are stuck, the chip will fail to output the hash.

Design Time

The team allocated the following person-hours to the project:

Project Proposal:	12 Hours
Verilog Model:	24 Hours
Schematics:	28 Hours
Layout:	80 Hours
Final Report:	14 Hours

File Locations:

Verilog Code:	/home/wbuik/project2_final/sha1full.sv
Test Vectors:	/home/wbuik/project2_final/sha1full.sv
Synthesis Results:	/home/wbuik/project2_final/core_run1/
Cadence Libraries:	/home/wbuik/project2_final/sha1/ /home/wbuik/project2_final/sha1_alu/
CIF:	N/A (<i>Image on cover page is unrouted core plot not CIF chip plot.</i>)
PDF Core Plot:	/home/wbuik/project2_final/core.pdf
PDF of Report:	/home/wbuik/project2_final/finalreport.pdf

Appendix A (Verilog Code and Test Vectors)

```
typedef enum logic [4:0] {
    H0 = 5'b00000,
    H1 = 5'b00001,
    H2 = 5'b00010,
    H3 = 5'b00011,
    H4 = 5'b00100,
    A = 5'b00101,
    B = 5'b00110,
    C = 5'b00111,
    D = 5'b01000,
    E = 5'b01001,
    T2 = 5'b01010,

    AInit = 5'b10000,
    BInit = 5'b10001,
    CInit = 5'b10010,
    DInit = 5'b10011,
    EInit = 5'b10100,
    K1 = 5'b10101,
    K2 = 5'b10110,
    K3 = 5'b10111,
    K4 = 5'b11000,
    ZERO = 5'b11001
} regreadaddr;

typedef enum logic [3:0] {
    H0W = 4'b0000,
    H1W = 4'b0001,
    H2W = 4'b0010,
    H3W = 4'b0011,
    H4W = 4'b0100,
    AW = 4'b0101,
    BW = 4'b0110,
    CW = 4'b0111,
    DW = 4'b1000,
    EW = 4'b1001,
    T2W = 4'b1010
} regwriteaddr;

typedef enum logic [1:0] {
    NONE = 2'b00,
    THIRTY_B = 2'b10,
    FIVE_B = 2'b01,
    ONE_A = 2'b11
} alushift;

typedef enum logic [1:0] {
    PASS = 2'b00,
    ADD = 2'b10,
    XOR = 2'b01,
    AND = 2'b11
} aluop;

typedef enum logic {
    RegOut = 1'b0,
    WOut = 1'b1
} srcb;

module controller(
    // Clock Inputs
    input logic ph1, ph2, Reset,
    // Chip Inputs
    input logic Block, Hash,
    // Chip Outputs
    output logic Ready,
    // Datapath Control
    output logic [3:0] WAddr,
    output logic WEn,
    output regreadaddr RegReadAddr,
    output regwriteaddr RegWriteAddr,
    output logic RegWrite,
    output logic TempWrite,
    output srcb SrcB,
    output alushift ALUShift,
    output aluop ALUOp,
    output logic CounterAReset,
    output logic CounterAInc,
    input logic [4:0] CounterA,
```



```

output logic CounterBReset,
output logic CounterBInc,
input logic [1:0] CounterB,
output logic CounterCReset,
input logic [3:0] CounterC,
output logic [5:0] state);

// WAddr calculation
logic [1:0] WOutSel;
logic [3:0] WOffset0;
logic [3:0] WOffset1;
logic [3:0] WOffset2;
logic [3:0] WOffset3;
logic [3:0] WOffset;
assign WOffset0 = 0;
assign WOffset1 = 2;
assign WOffset2 = 8;
assign WOffset3 = 13;
mux4 #(4) woffsetmux(WOffset0, WOffset1, WOffset2, WOffset3, WOutSel, WOffset);
assign WAddr = CounterC + WOffset;

// Debugging
/*always @(posedge ph2)
begin
if(WEn == 1 || SrcB == WOut) begin
    $display("%d: %d, %b, %d", state, CounterC, WOutSel, WAddr);
end
end*/

// State
//logic [5:0] state;
logic [5:0] nextstate;
logic [5:0] stateplusone;
assign stateplusone = state + 1;

// State Register
flop #(6) statereg(ph1, ph2, nextstate, state);

// Next State Logic
always_comb
begin
    if(Reset == 1) nextstate = 0;
    else begin
        case(state)
            5: // Ready
                if (Hash == 1) nextstate = 57; // Ready -> Hash
                else if (Block == 1) nextstate = 6; // Ready -> Read Block
                else nextstate = 5; // Ready -> Ready

            6: // Read Block
                if (CounterA == 15) nextstate = 7; // Read Block -> Block Init
                else nextstate = 6; // Read Block -> Read Block

            12:
                case (CounterB)
                    0: nextstate = 13; // Round Init -> RoundA
                    1: nextstate = 18; // Round Init -> RoundB
                    2: nextstate = 22; // Round Init -> RoundC
                    3: nextstate = 29; // Round Init -> RoundD
                endcase

            17:
                nextstate = 33; // RoundA -> Round Cleanup

            21:
                nextstate = 33; // RoundB -> Round Cleanup

            28:
                nextstate = 33; // RoundC -> Round Cleanup

            32:
                nextstate = 33; // RoundD -> Round Cleanup

            45:
                if (CounterA == 19) nextstate = 46; // MessageExtension -> Next Round Class
                else nextstate = 12; // MessageExtension -> Round Init

            46:
                if (CounterB == 3) nextstate = 47; // Next Round Class -> Block Cleanup
                else nextstate = 12; // Next Round Class -> Round Init

            56:
                nextstate = 5; // Block Cleanup -> Ready

            61:
                nextstate = 5; // Hash -> Ready

            default:

```

```

        nextstate = stateplusone;
    endcase
end
end

// Output Logic
always_comb
begin
    Ready = 0;
    WOutSel = 2'b00;
    WEn = 0;
    RegReadAddr = H0;
    RegWriteAddr = HOW;
    RegWrite = 0;
    TempWrite = 0;
    SrcB = RegOut;
    ALUShift = NONE;
    ALUOp = PASS;
    CounterAReset = 0;
    CounterBReset = 0;
    CounterCReset = 0;
    CounterAInc = 0;
    CounterBInc = 0;

    case (state)
        // Init Chip
        0: begin
            RegReadAddr = AInit;
            RegWriteAddr = HOW;
            RegWrite = 1;
        end
        1: begin
            RegReadAddr = BInit;
            RegWriteAddr = H1W;
            RegWrite = 1;
        end
        2: begin
            RegReadAddr = CInit;
            RegWriteAddr = H2W;
            RegWrite = 1;
        end
        3: begin
            RegReadAddr = DInit;
            RegWriteAddr = H3W;
            RegWrite = 1;
        end
        4: begin
            RegReadAddr = EInit;
            RegWriteAddr = H4W;
            RegWrite = 1;
        end

        // Ready
        5: begin
            CounterAReset = 1;
            CounterCReset = 1;
            Ready = 1;
        end

        // Read Block
        6: begin
            WEn = 1;
            CounterAInc = 1;
            Ready = 1;
        end

        // Block Init
        7: begin
            RegReadAddr = H0;
            RegWriteAddr = AW;
            RegWrite = 1;
        end
        8: begin
            RegReadAddr = H1;
            RegWriteAddr = BW;
            RegWrite = 1;
        end
        9: begin
            RegReadAddr = H2;
            RegWriteAddr = CW;
            RegWrite = 1;
        end
    endcase
end

```

```

    end
10: begin
    RegReadAddr = H3;
    RegWriteAddr = DW;
    RegWrite = 1;
    end
11: begin
    RegReadAddr = H4;
    RegWriteAddr = EW;
    RegWrite = 1;
    CounterBReset = 1;
    CounterAReset = 1;
    end

// Round Init
//12:

// RoundA
13: begin
    RegReadAddr = D;
    TempWrite = 1;
    end
14: begin
    RegReadAddr = C;
    TempWrite = 1;
    ALUOp = XOR;
    end
15: begin
    RegReadAddr = B;
    TempWrite = 1;
    ALUOp = AND;
    end
16: begin
    RegReadAddr = D;
    TempWrite = 1;
    ALUOp = XOR;
    end
17: begin
    RegReadAddr = K1;
    TempWrite = 1;
    ALUOp = ADD;
    end

// RoundB
18: begin
    RegReadAddr = B;
    TempWrite = 1;
    end
19: begin
    RegReadAddr = C;
    TempWrite = 1;
    ALUOp = XOR;
    end
20: begin
    RegReadAddr = D;
    TempWrite = 1;
    ALUOp = XOR;
    end
21: begin
    RegReadAddr = K2;
    TempWrite = 1;
    ALUOp = ADD;
    end

// RoundC
22: begin
    RegReadAddr = C;
    TempWrite = 1;
    end
23: begin
    RegReadAddr = D;
    RegWriteAddr = T2W;
    RegWrite = 1;
    ALUOp = AND;
    end
24: begin
    RegReadAddr = C;
    TempWrite = 1;
    end
25: begin

```

```

    RegReadAddr = D;
    TempWrite = 1;
    ALUOp = XOR;
end
26: begin
    RegReadAddr = B;
    TempWrite = 1;
    ALUOp = AND;
end
27: begin
    RegReadAddr = T2;
    TempWrite = 1;
    ALUOp = XOR;
end
28: begin
    RegReadAddr = K3;
    TempWrite = 1;
    ALUOp = ADD;
end

// RoundD
29: begin
    RegReadAddr = B;
    TempWrite = 1;
end
30: begin
    RegReadAddr = C;
    TempWrite = 1;
    ALUOp = XOR;
end
31: begin
    RegReadAddr = D;
    TempWrite = 1;
    ALUOp = XOR;
end
32: begin
    RegReadAddr = K4;
    TempWrite = 1;
    ALUOp = ADD;
end

// Round Cleanup
33: begin
    RegReadAddr = E;
    TempWrite = 1;
    ALUOp = ADD;
end
34: begin
    RegReadAddr = A;
    TempWrite = 1;
    ALUOp = ADD;
    ALUShift = FIVE_B;
end
35: begin
    SrcB = WOut;
    TempWrite = 1;
    ALUOp = ADD;
end
36: begin
    RegReadAddr = D;
    RegWriteAddr = EW;
    RegWrite = 1;
    ALUOp = PASS;
end
37: begin
    RegReadAddr = C;
    RegWriteAddr = DW;
    RegWrite = 1;
    ALUOp = PASS;
end
38: begin
    RegReadAddr = B;
    RegWriteAddr = CW;
    RegWrite = 1;
    ALUOp = PASS;
    ALUShift = THIRTY_B;
end
39: begin
    RegReadAddr = A;
    RegWriteAddr = BW;
    RegWrite = 1;

```

```

        ALUOp = PASS;
    end
40: begin
    RegReadAddr = ZERO;
    RegWriteAddr = AW;
    RegWrite = 1;
    ALUOp = ADD;
    end

// Message Extension
41: begin
    SrcB = WOut;
    TempWrite = 1;
    end
42: begin
    WOutSel = 2'b01;
    SrcB = WOut;
    TempWrite = 1;
    ALUOp = XOR;
    end
43: begin
    WOutSel = 2'b10;
    SrcB = WOut;
    TempWrite = 1;
    ALUOp = XOR;
    end
44: begin
    WOutSel = 2'b11;
    SrcB = WOut;
    TempWrite = 1;
    ALUOp = XOR;
    end
45: begin
    RegReadAddr = ZERO;
    TempWrite = 1;
    ALUOp = ADD;
    ALUShift = ONE_A;
    WEn = 1;
    CounterAInc = 1;
    end

// Next Round Class
46: begin
    CounterBInc = 1;
    CounterAReset = 1;
    end

// Block Cleanup
47: begin
    RegReadAddr = A;
    TempWrite = 1;
    end
48: begin
    RegReadAddr = H0;
    RegWriteAddr = HOW;
    RegWrite = 1;
    ALUOp = ADD;
    end
49: begin
    RegReadAddr = B;
    TempWrite = 1;
    end
50: begin
    RegReadAddr = H1;
    RegWriteAddr = H1W;
    RegWrite = 1;
    ALUOp = ADD;
    end
51: begin
    RegReadAddr = C;
    TempWrite = 1;
    end
52: begin
    RegReadAddr = H2;
    RegWriteAddr = H2W;
    RegWrite = 1;
    ALUOp = ADD;
    end
53: begin
    RegReadAddr = D;
    TempWrite = 1;

```

```

        end
54: begin
    RegReadAddr = H3;
    RegWriteAddr = H3W;
    RegWrite = 1;
    ALUOp = ADD;
    end
55: begin
    RegReadAddr = E;
    TempWrite = 1;
    end
56: begin
    RegReadAddr = H4;
    RegWriteAddr = H4W;
    RegWrite = 1;
    ALUOp = ADD;
    end

    // Output Hash
57: RegReadAddr = H0;
58: RegReadAddr = H1;
59: RegReadAddr = H2;
60: RegReadAddr = H3;
61: RegReadAddr = H4;
endcase
end

endmodule

//
// Counter/Adder Bank
// Since the three counters never need to be reset or
// incremented at the same time, share the adder logic.
// Also share adder logic with WAddr calculation.
//
//module counterAdderBank
//    (input logic ph1, ph2,
//     input logic inc, reset,
//     input logic [1:0] counterSel
//     input logic [1:0] WOutSel,
//     output logic [4:0] counterOut);
//
//    input logic [4:0] ca, cb, cc, counter;
//    assign cb[4:2] = 0;
//    assign cc[4] = 0;
//
//    mux3 #(5) (ca, cb, cc, counterSel, counter);
//
//    assign counterOut = 1 + counter;
//
//    flopen #(5) counterareg(ph1, ph2, ~(counterSel[0] | counterSel[1]), counterOut, ca);
//    flopen #(2) counterbreg(ph1, ph2, counterSel[0], counterOut, cb[1:0]);
//    flopen #(4) countercreg(ph1, ph2, counterSel[1], counterOut, cc[3:0]);
//
//endmodule

module counter #(parameter WIDTH = 8)
    (input logic ph1, ph2,
     input logic reset,
     input logic en,
     output logic [WIDTH-1:0] y);

    logic [WIDTH-1:0] yplusone;
    assign yplusone = y + 1;

    flopenr #(WIDTH) counterreg(ph1, ph2, reset, en, yplusone, y);
endmodule

module datapath
    #(parameter WIDTH = 32)
    (input logic ph1,
     input logic ph2,
     input logic [3:0] WAddr,
     input logic WEn,
     input logic [4:0] RegReadAddr,
     input logic [3:0] RegWriteAddr,
     input logic RegWriteEn,
     input logic TempWrite,
     input logic SrcB,
     input logic [1:0] ALUshift,

```

```

input logic [1:0] ALUop,
input logic IOSel,
inout [WIDTH-1:0] io);

logic [WIDTH-1:0] A;
logic [WIDTH-1:0] B;
logic [WIDTH-1:0] Wout;
logic [WIDTH-1:0] RegOut;
logic [WIDTH-1:0] ALUresult;
logic [WIDTH-1:0] WriteData;

//instantiate modules
mux2 #(WIDTH) Bsource (RegOut, Wout, SrcB, B);
flopen #(WIDTH) t1reg(ph1, ph2, TempWrite, WriteData, A);
FinalAlu #(WIDTH) alu (A, B, ALUshift, ALUop, ALUresult);
SRAM16 #(WIDTH) wmem (ph1, ph2, WAddr, WEn, WriteData, Wout);
MemConstBank #(WIDTH) bank (RegReadAddr, RegWriteAddr, RegWriteEn, WriteData, ph1, ph2,
RegOut);
ioselector #(WIDTH) ioselect (ALUresult, IOSel, WriteData, io);

endmodule

// Input Output Selector
module ioselector
#(parameter WIDTH = 8)
(input logic [WIDTH-1:0] ValueIn,
input logic IOSel,
output logic [WIDTH-1:0] ValueOut,
inout [WIDTH-1:0] IO);

mux2 #(WIDTH) wdmux (ValueIn, IO, IOSel, ValueOut);
tristate #(WIDTH) iotri (ValueIn, ~IOSel, IO);
endmodule

module tristate
#(parameter WIDTH = 8)
(input logic [WIDTH-1:0] in,
input logic en,
output logic [WIDTH-1:0] out);

assign out = en ? in : {(WIDTH){1'bz}};
endmodule

// SRAM Module for Message State, 16 Words
module SRAM16
#(parameter WIDTH = 8)
(input ph1, input ph2,
input [3:0] Addr,
input WriteEn,
input [WIDTH-1:0] DataIn,
output logic [WIDTH-1:0] DataOut);

logic [WIDTH-1:0] RAM [15:0];

always @ ( * )
if(ph2 & WriteEn) RAM[Addr] <= DataIn;

assign DataOut = RAM[Addr];
endmodule

//This module stores words and provides words and constants as needed
//These are the addresses of the variables used in the algorithm
//They are only 4 bits since they are used by RegWriteAddr, which is also 4 bits
//When used by RegReadAddr as a 5-bit number, they will have a 0 padded onto the front
module MemConstBank
#(parameter WIDTH = 8)
(input [4:0] RegReadAddr,
input [3:0] RegWriteAddr,
input RegWriteEn,
input [WIDTH-1:0] RegIn,
input ph1, input ph2,
output logic [WIDTH-1:0] RegOut);

logic [WIDTH-1:0] ROM [9:0];

```

```

assign ROM[0] = 32'h67452301;
assign ROM[1] = 32'hEFCDA89;
assign ROM[2] = 32'h98BADCFE;
assign ROM[3] = 32'h10325476;
assign ROM[4] = 32'hC3D2E1F0;
assign ROM[5] = 32'h5A827999;
assign ROM[6] = 32'h6ED9EBAl;
assign ROM[7] = 32'h8F1BBCDC;
assign ROM[8] = 32'hCA62C1D6;
assign ROM[9] = 32'b0;

// Flop for ram sequencing
logic [WIDTH-1:0] RegInSeq;
flop #(WIDTH) seq(ph2, ph1, RegIn, RegInSeq);

logic [WIDTH-1:0] RamData;
SRAM11 #(WIDTH) ram(ph1, ph2, RegReadAddr[3:0], RegWriteAddr, RegWriteEn, RegInSeq, RamData);

//always @(*)
//    if (ph2 & RegWriteEn) RAM[RegWriteAddr] <= RegInSeq;

assign RegOut = RegReadAddr[4] ? ROM[RegReadAddr[3:0]] : RamData;
endmodule

// SRAM Module for Message State, 16 Words
module SRAM11
#(parameter WIDTH = 8)
(input ph1, input ph2,
input [3:0] RAddr,
input [3:0] WAddr,
input WriteEn,
input [WIDTH-1:0] DataIn,
output logic [WIDTH-1:0] DataOut);

logic [WIDTH-1:0] RAM [10:0];

always @(negedge ph2)
    if (WriteEn) RAM[WAddr] <= DataIn;

assign DataOut = RAM[RAddr];
endmodule

/*This is the ALU used for the SHA algorithm
It can left-circular shift the "A" input by 0, 5, or 6 places,
and can left-circular shift the "B" input by 0 or 1 places
It can AND, XOR, or sum the shifted A and B, or it can directly pass
the shifted B
This was implemented using NAND, XNOR, an inverted sum, and an inverter,
with the output chosen by an inverting mux, to better reflect what the final
chip will look like
*/
module FinalAlu
#(parameter WIDTH = 8)
(input [WIDTH-1:0] A, input [WIDTH-1:0] B,
output [1:0] ALUrot, input [1:0] ALUop,
output reg [WIDTH-1:0] Y);

logic [WIDTH-1:0] Arot1;
logic [WIDTH-1:0] Brot5;
logic [WIDTH-1:0] BrotWMinus2;
logic [WIDTH-1:0] Arot;
logic [WIDTH-1:0] Brot;
logic [WIDTH-1:0] OpNand;
logic [WIDTH-1:0] OpXNOR;
logic [WIDTH-1:0] OpAdd;
logic [WIDTH-1:0] OpPass;
logic [WIDTH-1:0] OpNandAdd;
logic [WIDTH-1:0] OpXNORPass;

// Rotation functionality for A and B
rotl1 #(WIDTH) arot1(A, Arot1);
rotl5 #(WIDTH) brot5(B, Brot5);
rotr2 #(WIDTH) brot1(B, BrotWMinus2);
mux2 #(WIDTH) arotmux(A, Arot1, ALUrot[0] & ALUrot[1], Arot);
mux4 #(WIDTH) brotmux(B, Brot5, BrotWMinus2, B, ALUrot, Brot);

//These are the functions that the ALU can perform on the inputs
//They are inverted to better match how the final implementation will perform

```



```

    assign OpNand = ~(Arot & Brot);
    assign OpXNOR = ~(Arot ^ Brot);
    assign OpAdd = ~(Arot + Brot);
    assign OpPass = ~Brot;

    // Output selector mux
    mux2inv #(WIDTH) outmux1(OpAdd, OpNand, ALUop[0], OpNandAdd);
    mux2inv #(WIDTH) outmux2(OpPass, OpXNOR, ALUop[0], OpXNORPass);
    mux2 #(WIDTH) outmux3(OpXNORPass, OpNandAdd, ALUop[1], Y);
endmodule

//
// Circular rotation modules
//
module rotl1
    #(parameter WIDTH = 8)
    (input logic [WIDTH-1:0] a,
     output logic [WIDTH-1:0] y);

    assign y[WIDTH-1:1] = a[WIDTH-2:0];
    assign y[0] = a[WIDTH-1];
endmodule

module rotl5
    #(parameter WIDTH = 8)
    (input logic [WIDTH-1:0] a,
     output logic [WIDTH-1:0] y);

    assign y[4:0] = a[WIDTH-1:WIDTH-5];
    assign y[WIDTH-1:5] = a[WIDTH-6:0];
endmodule

module rotr2
    #(parameter WIDTH = 8)
    (input logic [WIDTH-1:0] a,
     output logic [WIDTH-1:0] y);

    assign y[WIDTH-1:WIDTH-2] = a[1:0];
    assign y[WIDTH-3:0] = a[WIDTH-1:2];
endmodule

//
// Memory Elements
//
module flop #(parameter WIDTH = 8)
    (input logic          ph1, ph2,
     input logic [WIDTH-1:0] d,
     output logic [WIDTH-1:0] q);

    logic [WIDTH-1:0] mid;

    latch #(WIDTH) master(ph2, d, mid);
    latch #(WIDTH) slave(ph1, mid, q);
endmodule

module flopenr #(parameter WIDTH = 8)
    (input logic          ph1, ph2, reset, en,
     input logic [WIDTH-1:0] d,
     output logic [WIDTH-1:0] q);

    logic [WIDTH-1:0] d2, resetval;

    assign resetval = 0;

    mux3 #(WIDTH) enrmux(q, d, resetval, {reset, en}, d2);
    flop #(WIDTH) f(ph1, ph2, d2, q);
endmodule

module flopen #(parameter WIDTH = 8)
    (input logic          ph1, ph2, en,
     input logic [WIDTH-1:0] d,
     output logic [WIDTH-1:0] q);

    logic [WIDTH-1:0] d2;

    mux2 #(WIDTH) enrmux(q, d, en, d2);
    flop #(WIDTH) f(ph1, ph2, d2, q);
endmodule

```

```

module latch #(parameter WIDTH = 8)
    (input logic ph,
     input logic [WIDTH-1:0] d,
     output logic [WIDTH-1:0] q);

    always_latch
        if (ph) q <= d;
endmodule

//
// Muxes
//
module mux2inv #(parameter WIDTH = 8)
    (input logic [WIDTH-1:0] d0,
     input logic [WIDTH-1:0] d1,
     input logic s,
     output logic [WIDTH-1:0] y);
    assign y = ~(s ? d1: d0);
endmodule

module mux2 #(parameter WIDTH = 8)
    (input logic [WIDTH-1:0] d0,
     input logic [WIDTH-1:0] d1,
     input logic s,
     output logic [WIDTH-1:0] y);
    assign y = (s ? d1: d0);
endmodule

module mux3 #(parameter WIDTH = 8)
    (input logic [WIDTH-1:0] d0, d1, d2,
     input logic [1:0] s,
     output logic [WIDTH-1:0] y);

    always_comb
        casez (s)
            2'b00: y = d0;
            2'b01: y = d1;
            2'b1?: y = d2;
        endcase
endmodule

module mux4 #(parameter WIDTH = 8)
    (input logic [WIDTH-1:0] d0, d1, d2, d3,
     input logic [1:0] s,
     output logic [WIDTH-1:0] y);

    always_comb
        case (s)
            2'b00: y = d0;
            2'b01: y = d1;
            2'b10: y = d2;
            2'b11: y = d3;
        endcase
endmodule

module SHA1 #(parameter WIDTH = 32)
    (input ph1, ph2, Reset, Block, Hash,
     inout [WIDTH-1:0] io,
     output Ready);

    // Datapath Control
    logic [3:0] WAddr;
    logic WEn;
    regreadaddr RegReadAddr;
    regwriteaddr RegWriteAddr;
    logic RegWrite;
    logic TempWrite;
    srcb SrcB;
    alushift ALUShift;
    aluop ALUOp;

    // Counter Control
    logic CounterAReset;
    logic CounterBReset;
    logic CounterCReset;
    logic CounterAInc;
    //logic CounterBInc;
    logic [4:0] CounterA;
    logic [1:0] CounterB;

```

```

logic [3:0] CounterC;

// Debug Out
logic [5:0] state;

controller ctrl(
    ph1, ph2, Reset, Block, Hash, Ready, WAddr,
    WEn, RegReadAddr, RegWriteAddr, RegWrite, TempWrite,
    SrcB, ALUShift, ALUOp, CounterAReset, CounterAInc, CounterA,
    CounterBReset, CounterBInc, CounterB, CounterCReset, CounterC,
    state);

counter #(5) counter5(ph1, ph2, CounterAReset, CounterAInc, CounterA);
counter #(2) counter2(ph1, ph2, CounterBReset, CounterBInc, CounterB);
counter #(4) counter4(ph1, ph2, CounterCReset, WEn, CounterC);

datapath #(WIDTH) dp(ph1, ph2, WAddr, WEn, RegReadAddr, RegWriteAddr, RegWrite,
    TempWrite, SrcB, ALUShift, ALUOp, Ready, io);

endmodule

module testbench();
    // Clock
    logic ph1, ph2;

    // Chip Inputs
    logic Block, Hash, Reset;
    logic [31:0] DataIn;
    // Chip Outputs
    logic Ready;
    // ChipIO
    tri [31:0] DataIO;
    assign DataIO = Ready ? DataIn : 32'bz;
    SHA1 #(32) dut(ph1, ph2, Reset, Block, Hash, DataIO, Ready);

    // TV
    logic [2:0] testState;
    logic [10:0] vectornum;
    logic [31:0] TestVectors[100:0];
    logic [31:0] HashOut[4:0];

    assign TestVectors[0] = 32'h8A921FC4;
    assign TestVectors[1] = 32'h452C45D2;
    assign TestVectors[2] = 32'hABC243FE;
    assign TestVectors[3] = 32'hEC429CBD;
    assign TestVectors[4] = 32'h452C45D2;
    assign TestVectors[5] = 32'hEC429CBD;
    assign TestVectors[6] = 32'h452C45D2;
    assign TestVectors[7] = 32'hEC429CBD;
    assign TestVectors[8] = 32'h8A921FC4;
    assign TestVectors[9] = 32'h452C45D2;
    assign TestVectors[10] = 32'hABC243FE;
    assign TestVectors[11] = 32'h452C45D2;
    assign TestVectors[12] = 32'hEC429CBD;
    assign TestVectors[13] = 32'h452C45D2;
    assign TestVectors[14] = 32'h8A921FC4;
    assign TestVectors[15] = 32'h452C45D2;

    assign TestVectors[16] = 32'hFC258E41;
    assign TestVectors[17] = 32'hDFE90802;
    assign TestVectors[18] = 32'h64C65A1F;
    assign TestVectors[19] = 32'hDCB36023;
    assign TestVectors[20] = 32'h9FAEA24E;

    // generate clock to sequence tests
    always
    begin
        ph1 <= 0; ph2 <= 0; #1;
        ph1 <= 1; # 4;
        ph1 <= 0; #1;
        ph2 <= 1; # 4;
    end

    // Init chip
    initial begin
        //$readmemb("ctrl.tv", testvectors); // load test vectors
        testState = 0;
        Reset = 1; #17; Reset = 0; // come out of reset before cycle 2
        Block = 0;
        Hash = 0;
    end
endmodule

```

```

    DataIn = 0;
end

// Check results on ph2
always @(posedge ph2) begin
    if(Hash && Ready) begin
        // Verify Hash
        if(HashOut[0] != TestVectors[16] ||
           HashOut[1] != TestVectors[17] ||
           HashOut[2] != TestVectors[18] ||
           HashOut[3] != TestVectors[19] ||
           HashOut[4] != TestVectors[20]) begin
            $display("ERROR:");
            $display("EXPECTED: %H %H %H %H %H", TestVectors[16], TestVectors[17],
                    TestVectors[18], TestVectors[19], TestVectors[20]);
        end

        $display("HASHOUT: %H %H %H %H %H", HashOut[0], HashOut[1],
                HashOut[2], HashOut[3], HashOut[4]);
        $finish;
    end

    if(testState == 0) begin // wait for init
        if(Ready == 1) begin
            testState = 1;
            vectornum = 0;
            Block = 1;
        end
    end

    else if(testState == 1) begin // input msg block
        if(vectornum > 15) begin
            testState = 2;
        end
        vectornum += 1;
    end

    else if(testState == 2) begin // wait for hash result
        if(Ready == 1) begin
            Block = 0;
            Hash = 1;
            testState = 3;
            vectornum = 0;
        end
    end

    else if(testState == 3) begin // output hash data
        HashOut[vectornum] = DataIO;
        vectornum += 1;
        //$display("%h", DataIO);
    end
end

// Load data on ph1
always @(posedge ph1) begin
    if(testState == 1) DataIn = TestVectors[vectornum];
end
endmodule


```


Appendix B (Schematics and Layout of Custom Cells)

Library	Cell Name	Notes
shal	controller_fsm_synth	Layout only, schematic synthesized.
shal	core	Layout not routed.
shal	counter_bank	
shal	counter_cell	
shal	counter_zipper	
shal	counter5	
shal	datapath	Layout does not LVS.
shal	flopen_dp	
shal	flopen32_dp	
shal	flopr	
shal	halfadder_dp	
shal	inv_dp	
shal	ioselect	
shal	memconstbank	
shal	mux2_32	
shal	mux2_dp	
shal	nand4_1x	
shal	rom_bitcond	
shal	rom_bitcond32	
shal	rom_one	
shal	rom_word0	
shal	rom_word1	
shal	rom_word2	
shal	rom_word3	
shal	rom_word4	
shal	rom_word5	
shal	rom_word6	
shal	rom_word7	
shal	rom_word8	
shal	rom_zero	Layout only, schematic empty.
shal	sram_cell	
shal	sram11_addrbuf	
shal	sram11_word	
shal	sram11_zipper	
shal	sram11rom	
shal	sram16	
shal	sram16_addrbuf	
shal	sram16_word	
shal	sram16_zipper	
shal	tristate	
shal	xor2	
shal_alu	alu	


sha1_alu invadder_32
sha1_alu invfulladder
sha1_alu invmux2_32
sha1_alu invmux2_dp
sha1_alu nand2_1x
sha1_alu nand2_32x
sha1_alu shift_a
sha1_alu shift_b
sha1_alu xnor2
sha1_alu xnor2_32x


sha1.counter_bank

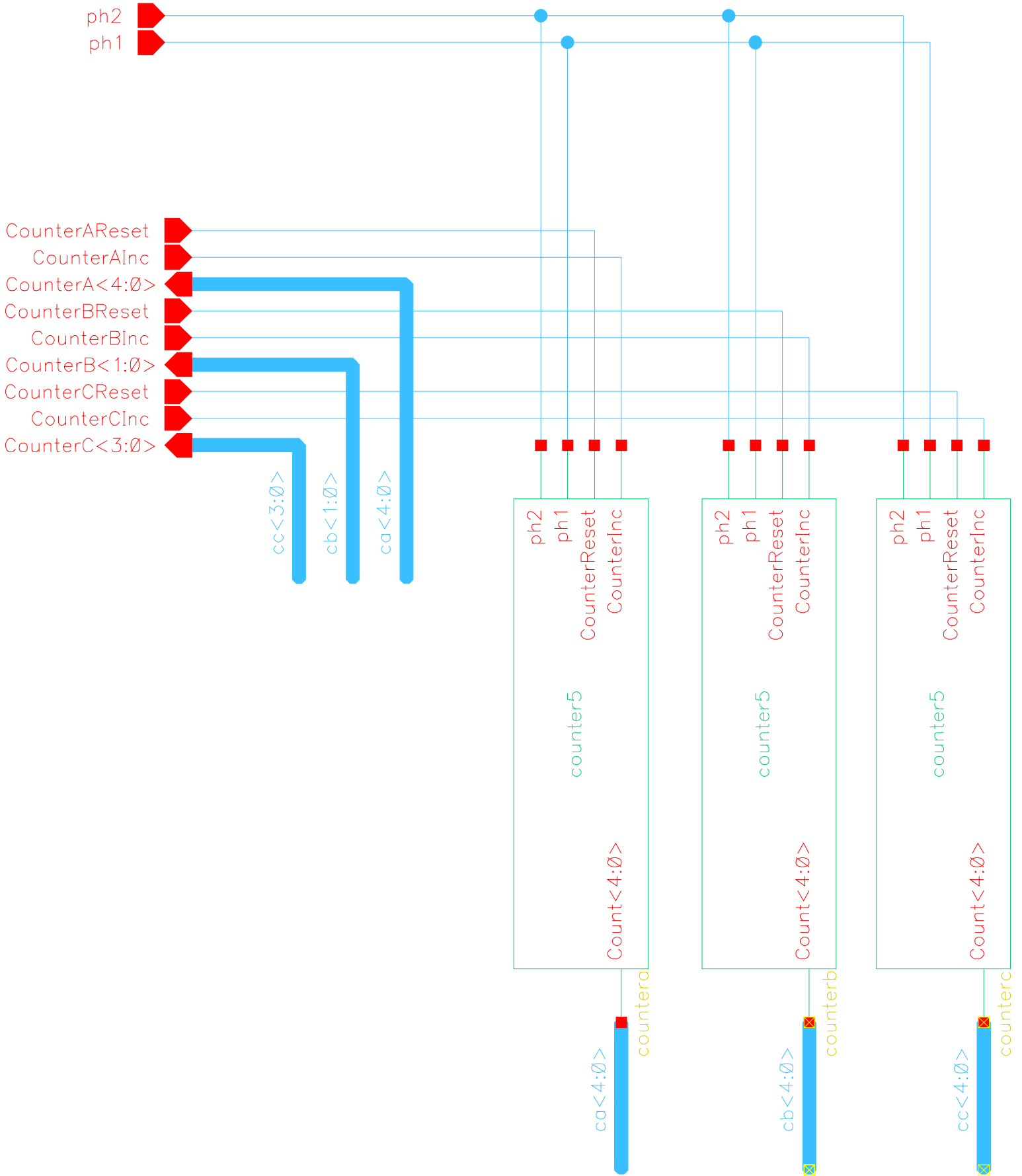


 



sha1.counter_cell

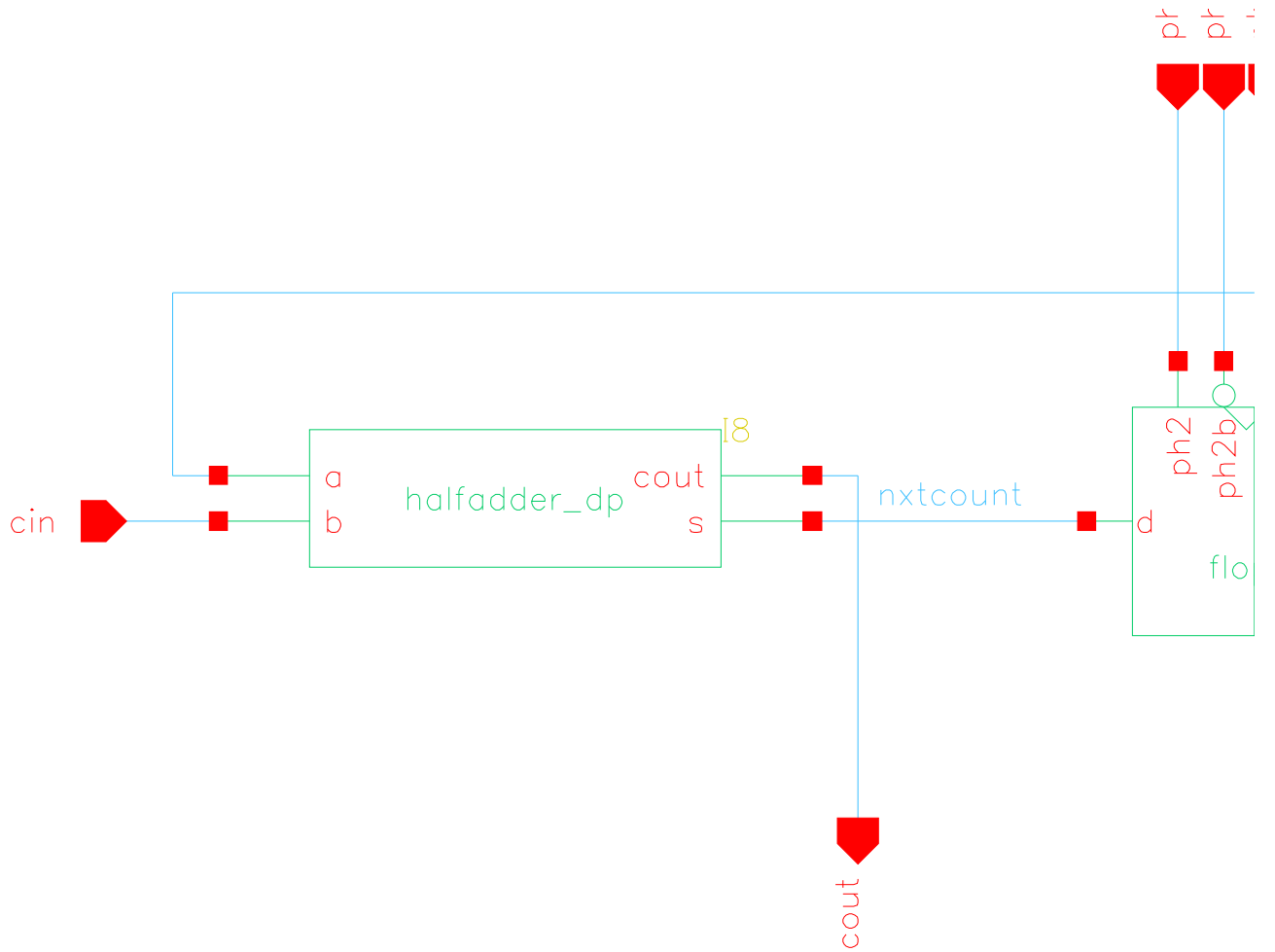


 

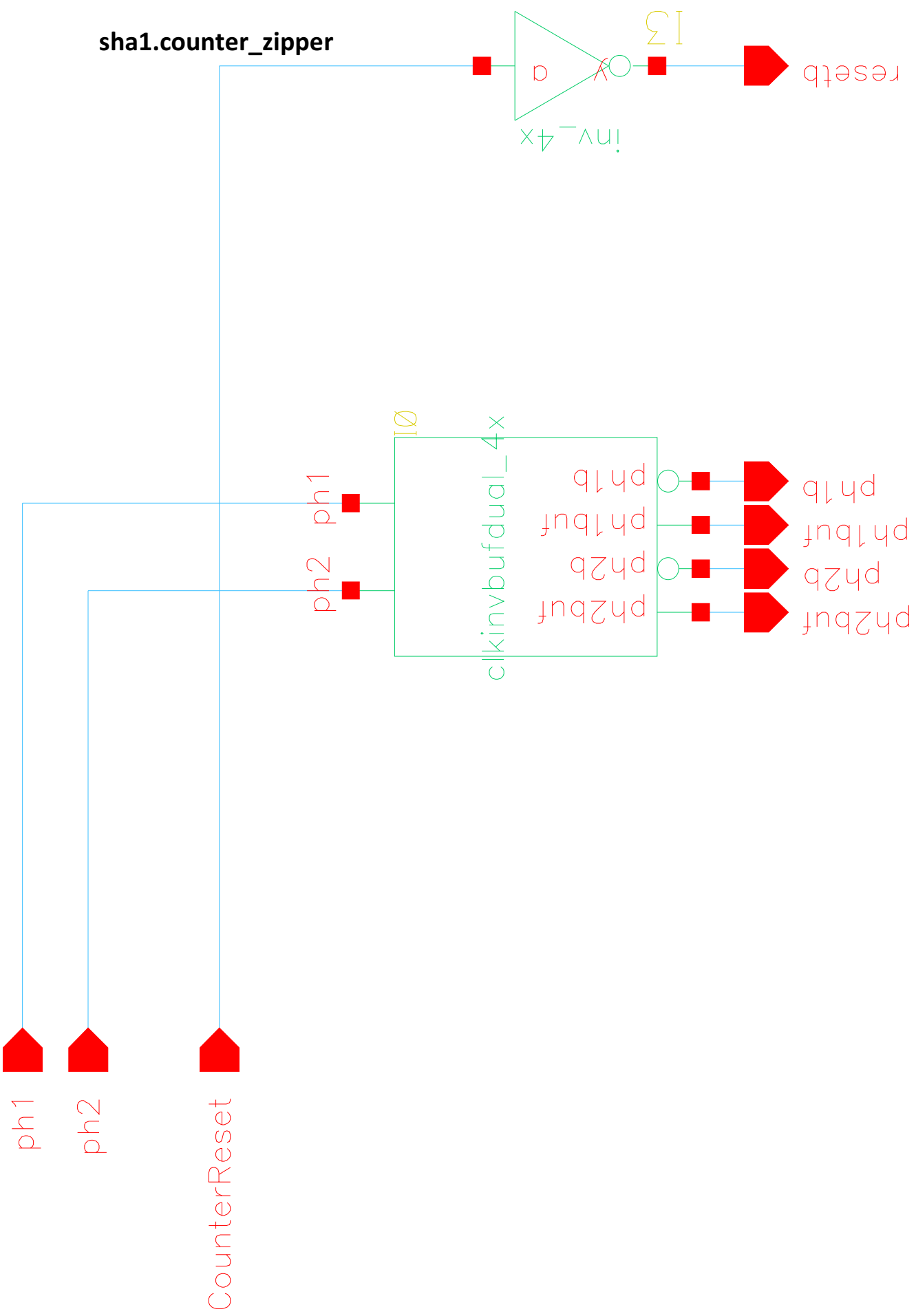

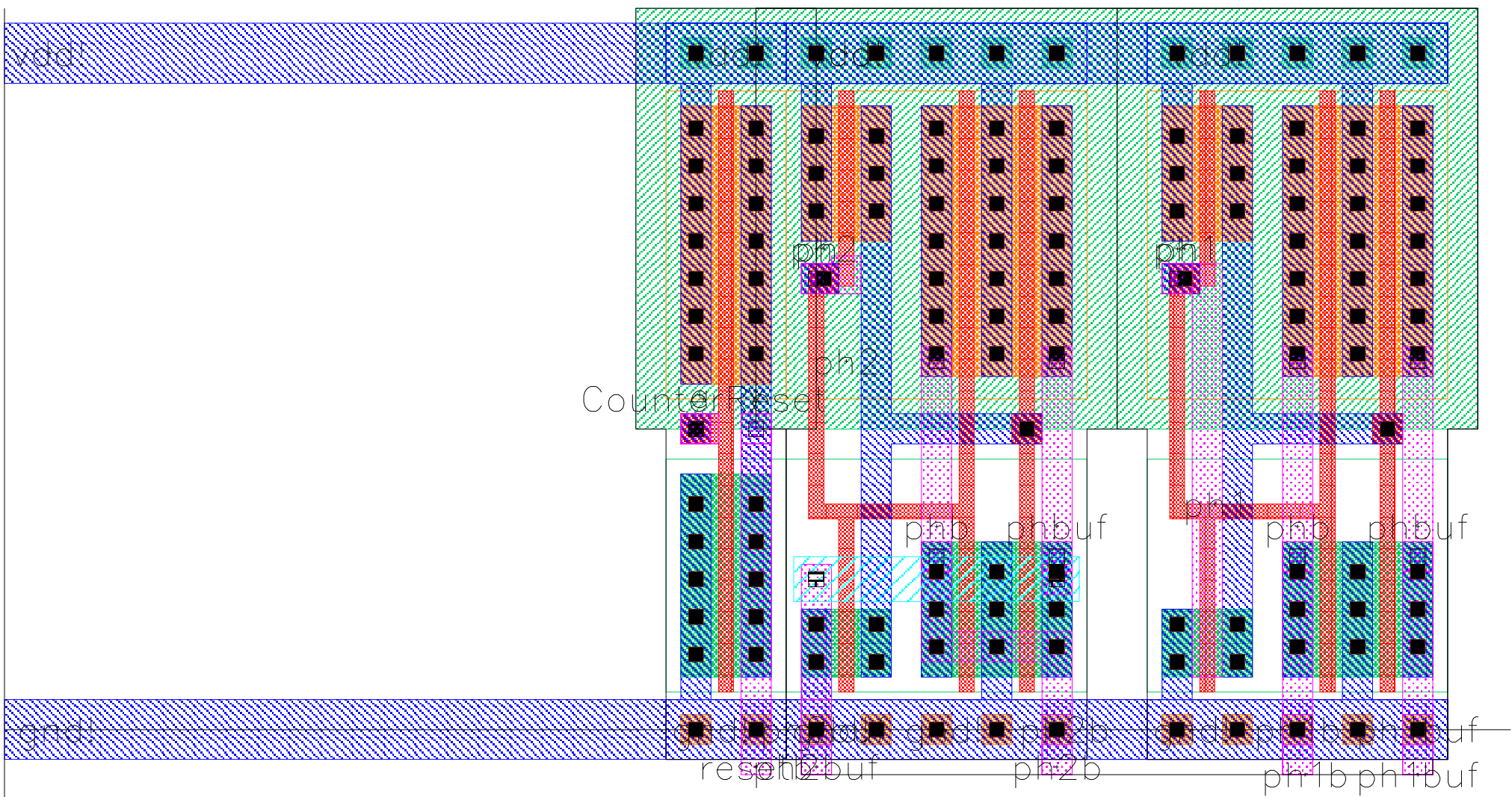


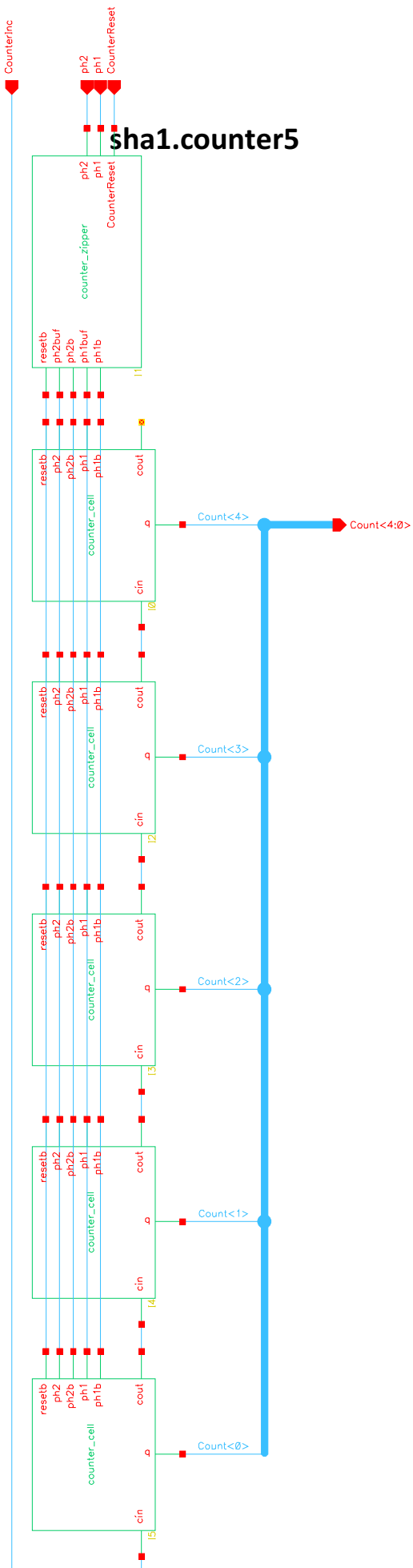


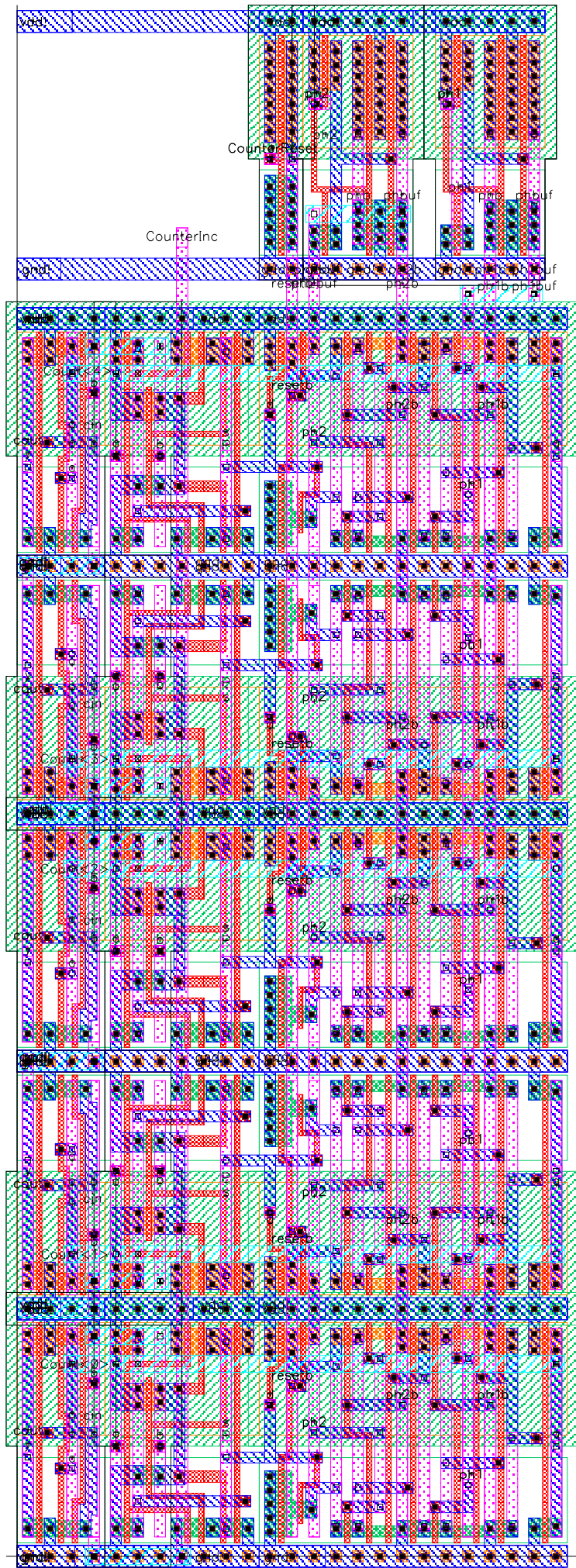

sha1_alu.alu


ALUrot<1:0>
ALUop<1:0>

 

 

sha1_alu.invadder_32

REVISIONS			
ZONE	REV	DESCRIPTION	DATE

 

Harvey Mudd College

UPDATED
Apr 14 02:47:32 2010

BY
wbuik


SIZE
A

REV

adder_8


SHEET

1 of 1

 

REVISIONS		DESCRIPTION	
ZONE	REV		

DATE sha1_alu.invfulladder

 

Harvey Mudd College


fulladder

UPDATED Apr 14 01:50:19 2010


BY wbuik

REV

SIZE A

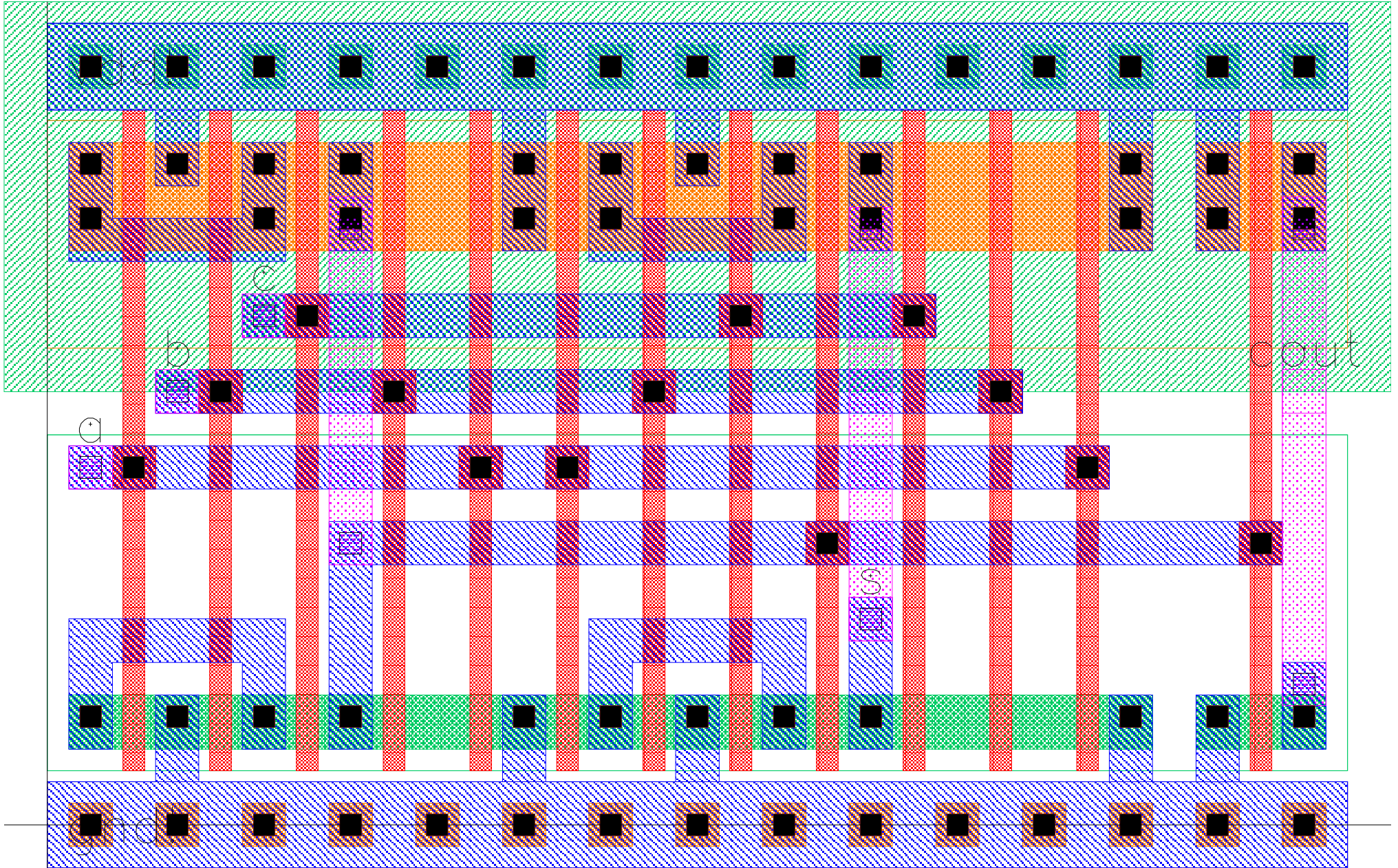


sha1_alu.invmux2_32

 



sha1_alu.invmux2_dp

REVISIONS			
ZONE	REV	DESCRIPTION	DATE

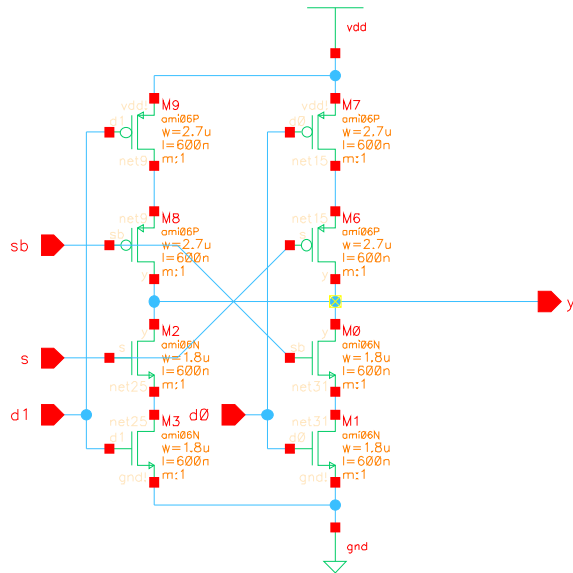

Harvey Mudd College

UPDATED
Mar 29 23:52:23 2010

BY
wbuik


SIZE
A

REV


mux2_dp_1x

SHEET

1 of 1



 


REVISIONS		DATE
ZONE	REV	sha1_alu.nand2_1x
DESCRIPTION		

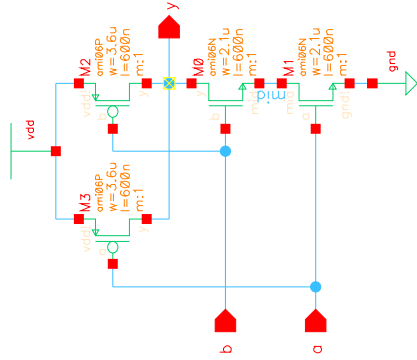



Harvey Mudd College

UPDATED	nand2_1x	
Apr 14 02:07:56 2010		
BY	wbuik	
SIZE	REV	SHEET
A		1 of 1

 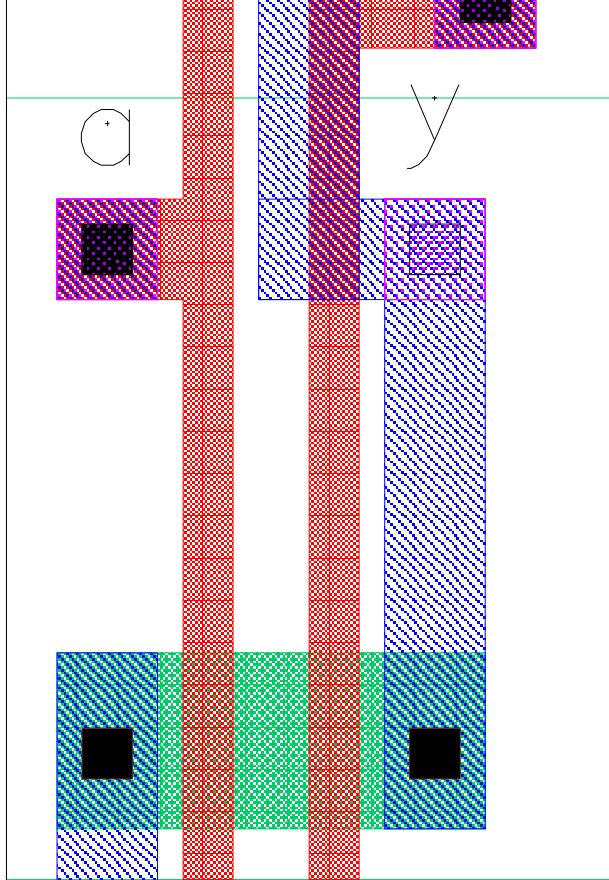 



sha1_alu.nand2_32x

 

 



sha1_alu.shift_a

 

 



sha1_alu.shift_b

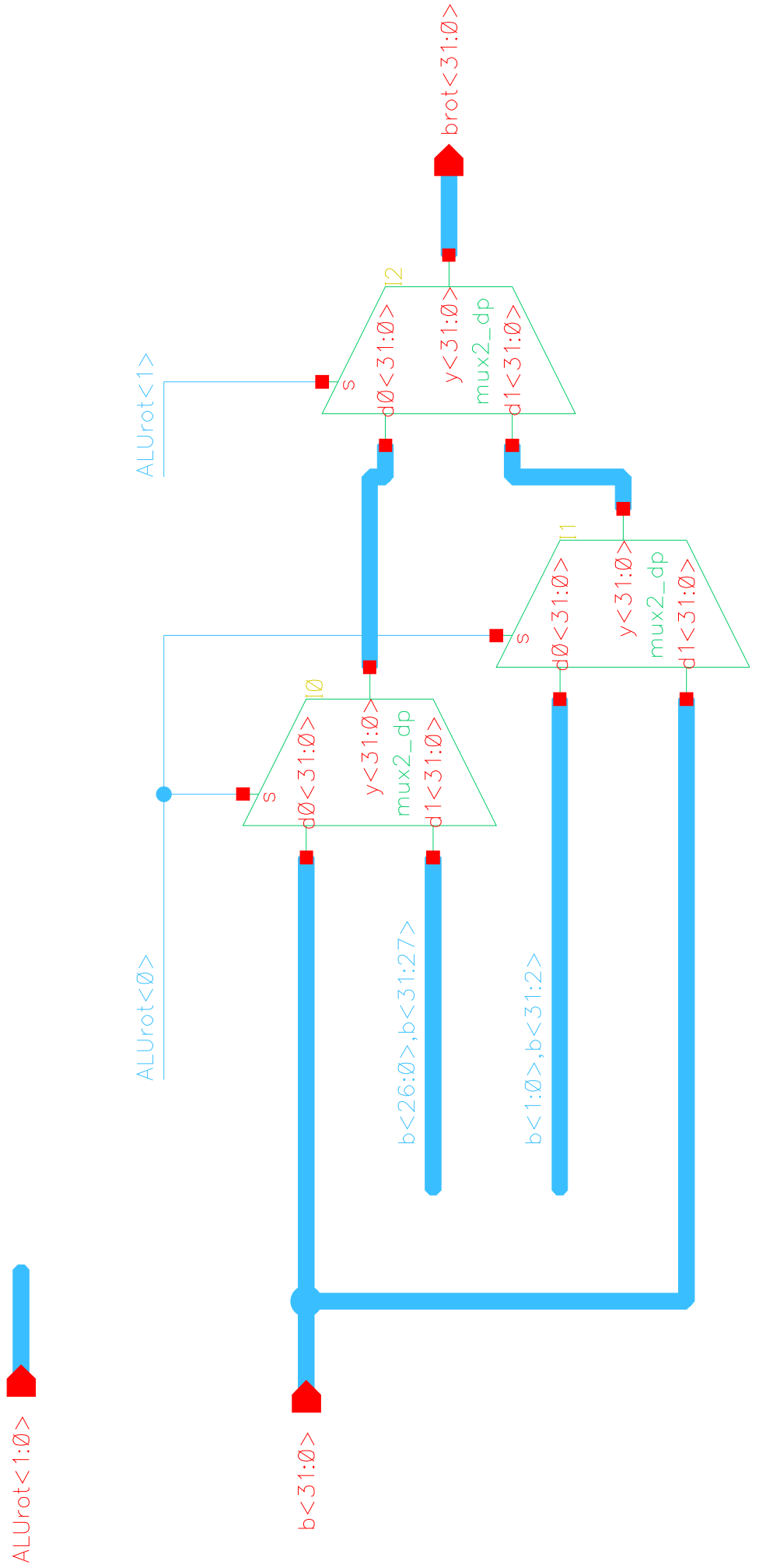

 



sha1_alu.xnor2

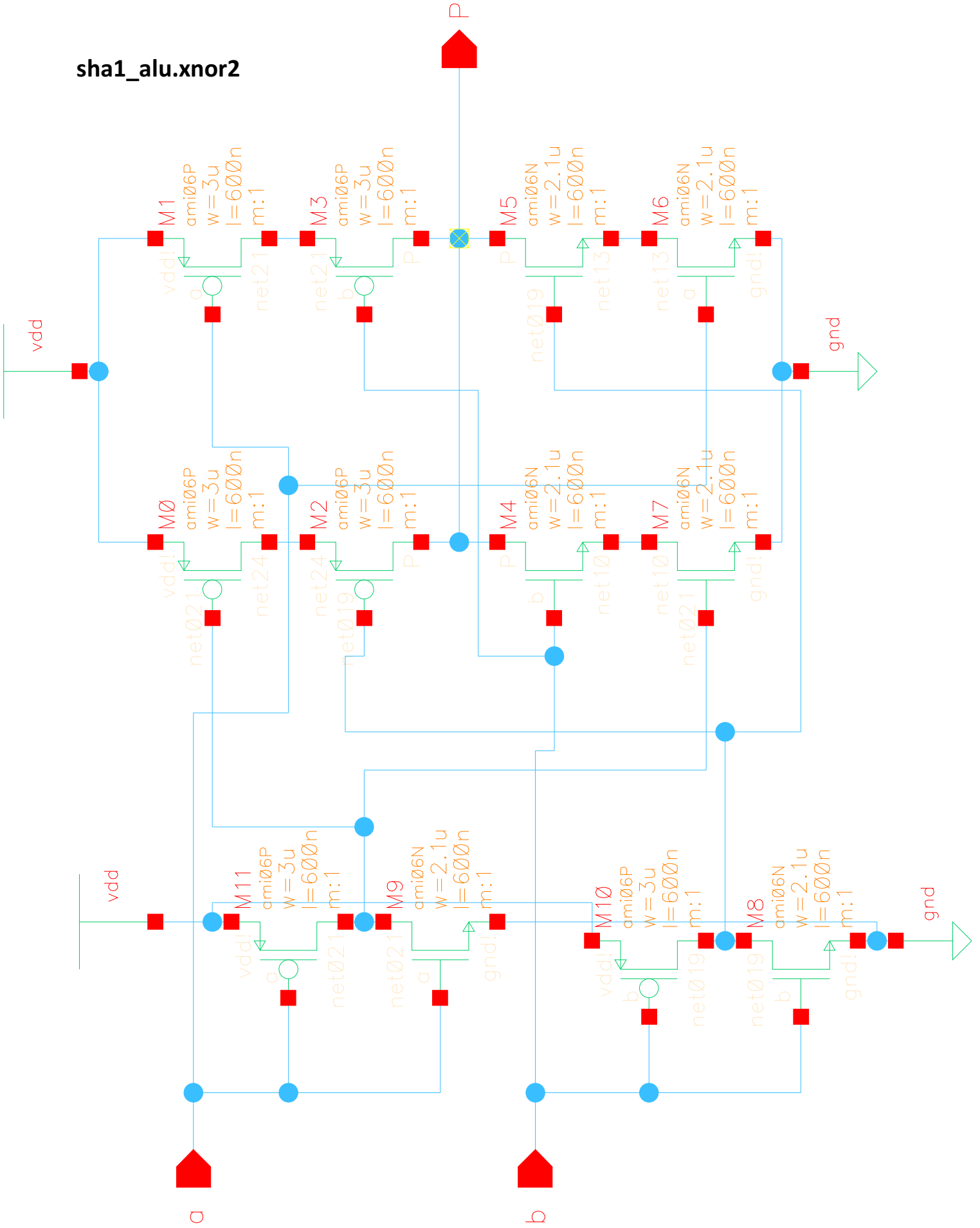


 

sha1_alu.xnor2_32x

 

 

 

REVISIONS

DESCRIPTION

ZONE

REV

DATE sha1.flopen_dp

Harvey Mudd College

UPDATED Jan 22 14:16:42 2010


BY wbuik


SIZE A REV


flopen_dp_1x


SHEET

1 of 1

 

 

 

 


Harvey Mudd College

flopr_dp_1x


UPDATED
Apr 5 19:08:17 2010


BY
wbui

SIZE
A

 


sha1.halfadder_dp

 







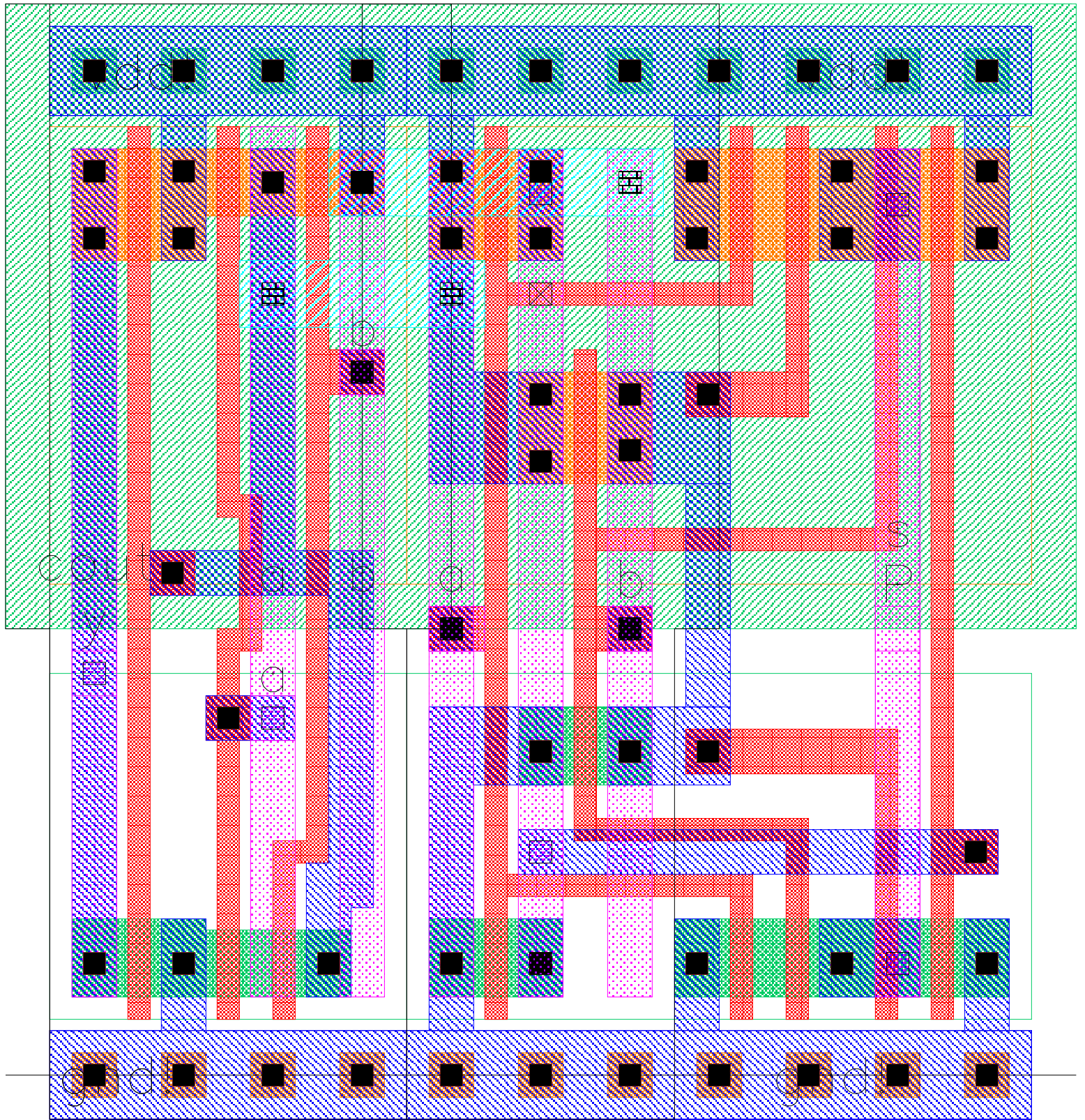


REVISIONS		DATE
ZONE	REV	sha1.inv_dp
DESCRIPTION		

 


Harvey Mudd College

UPDATED	inv_1x	
Mar 29 23:52:00 2010		
BY	wbuik	
SIZE	REV	
A		
SHEET		1 of 1

       



sha1.ioselect

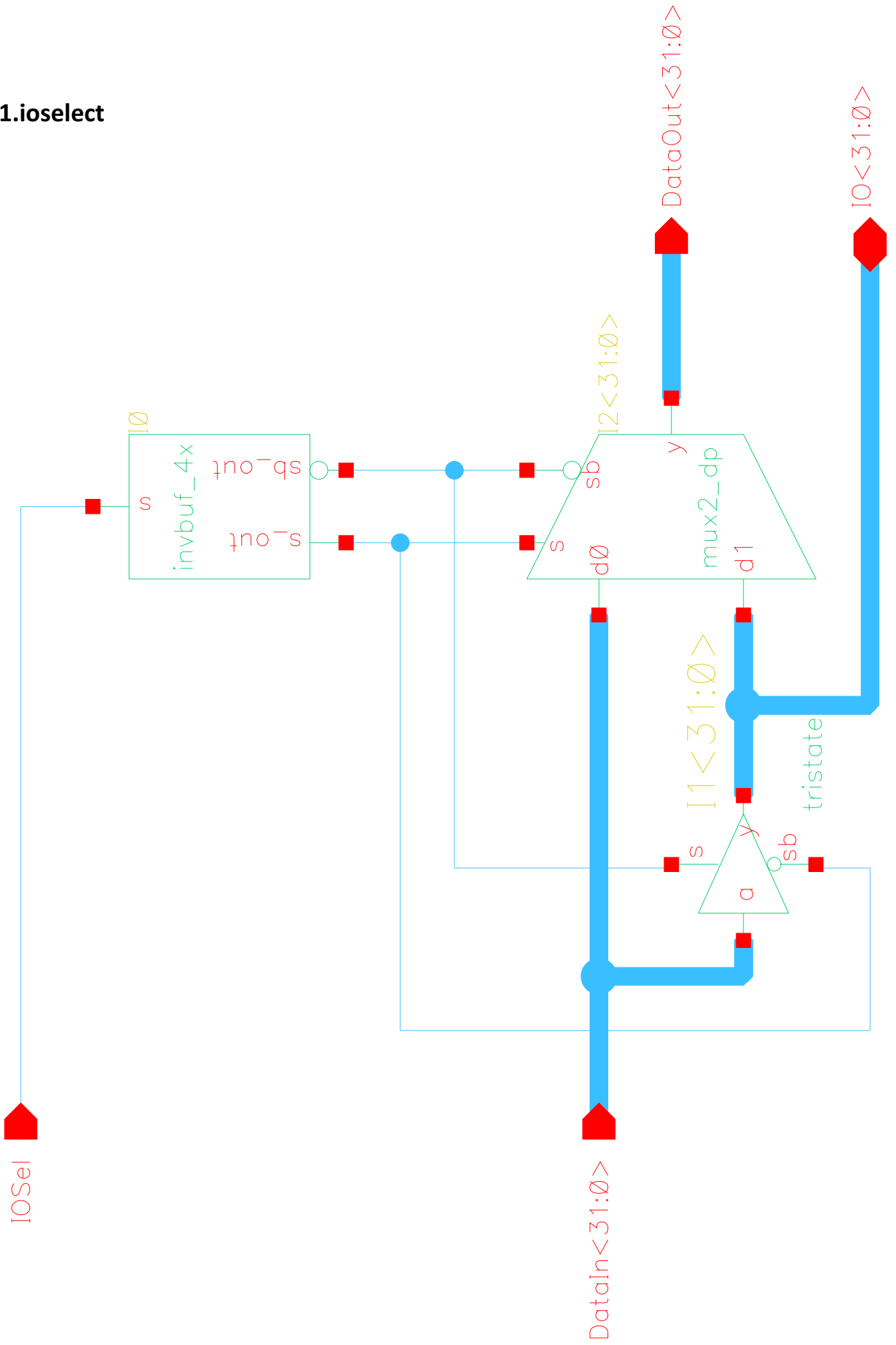




sha1.memconstbank

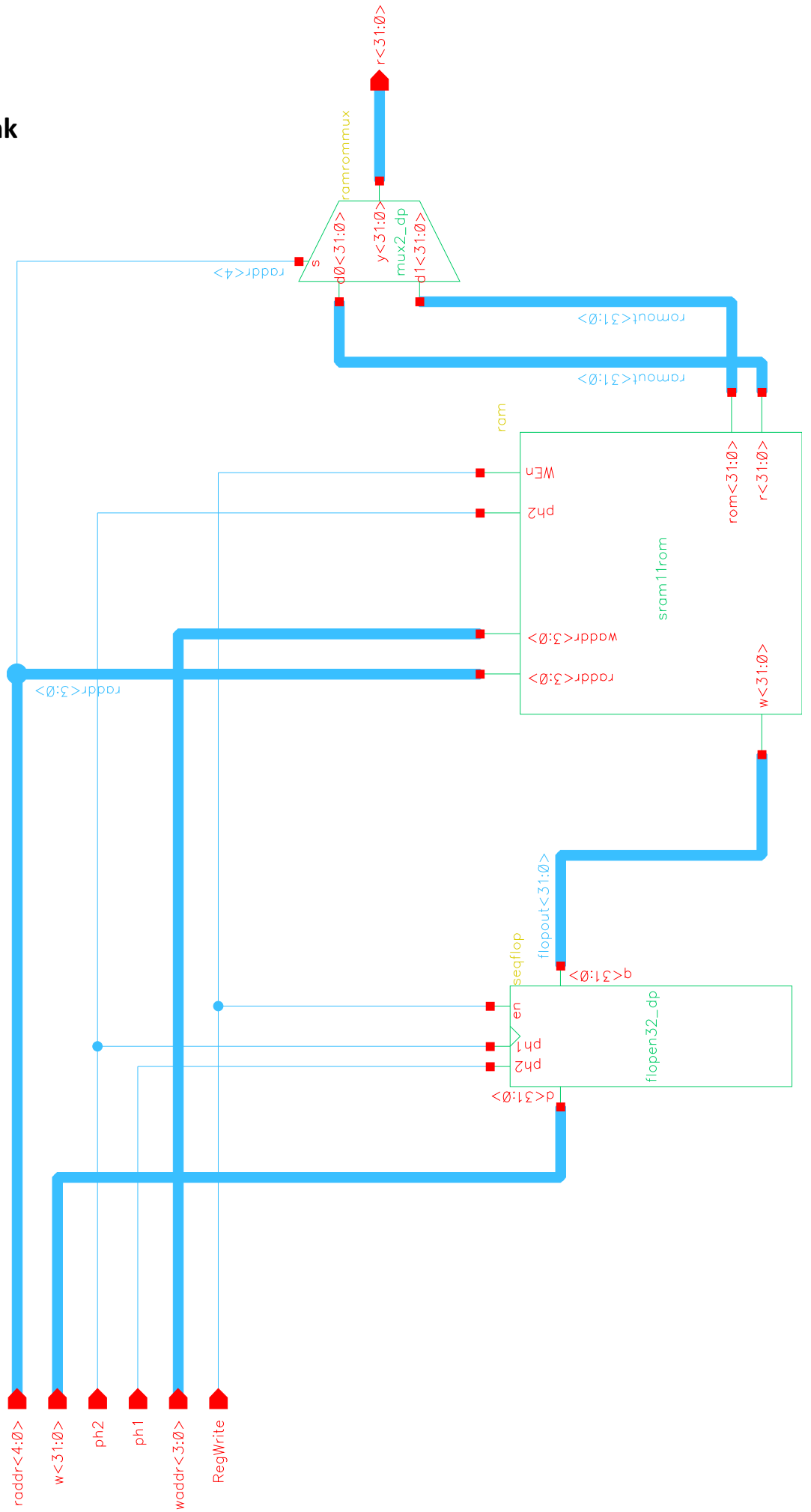

 


sha1.mux2_32

 



sha1.mux2_dp

REVISIONS			
ZONE	REV	DESCRIPTION	DATE

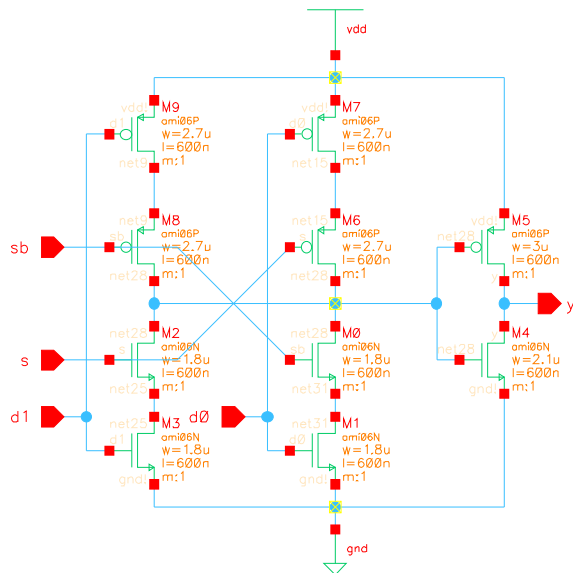

Harvey Mudd College

UPDATED
Mar 29 23:52:45 2010

BY
wbuk


SIZE
A

REV

mux2_dp_1x

SHEET

1 of 1

 


REVISIONS

DESCRIPTION

ZONE REV

DATE sha1.nand4_1x

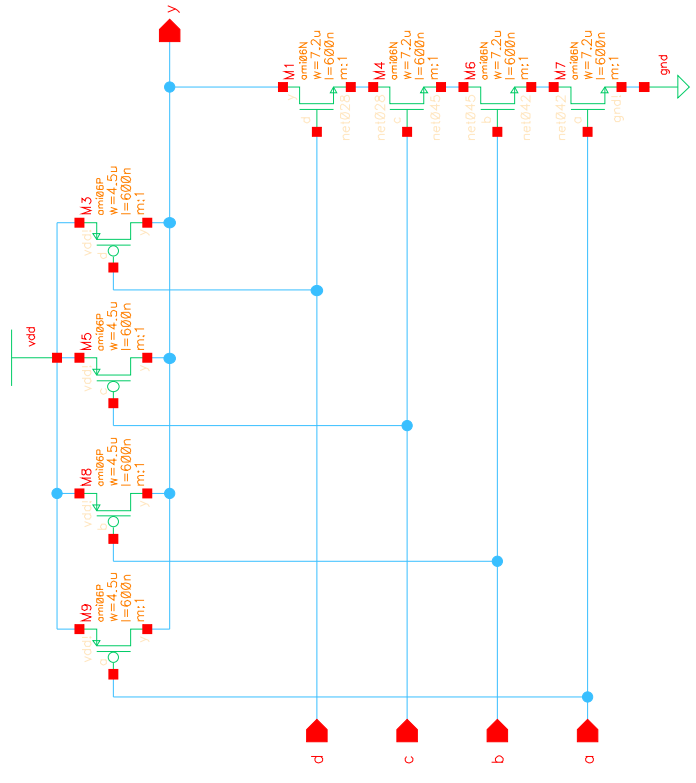


Harvey Mudd College

UPDATED Mar 29 23:53:14 2010


BY wbuik


SIZE A REV

nand5_1x

 


sha1.rom_bitcond

 

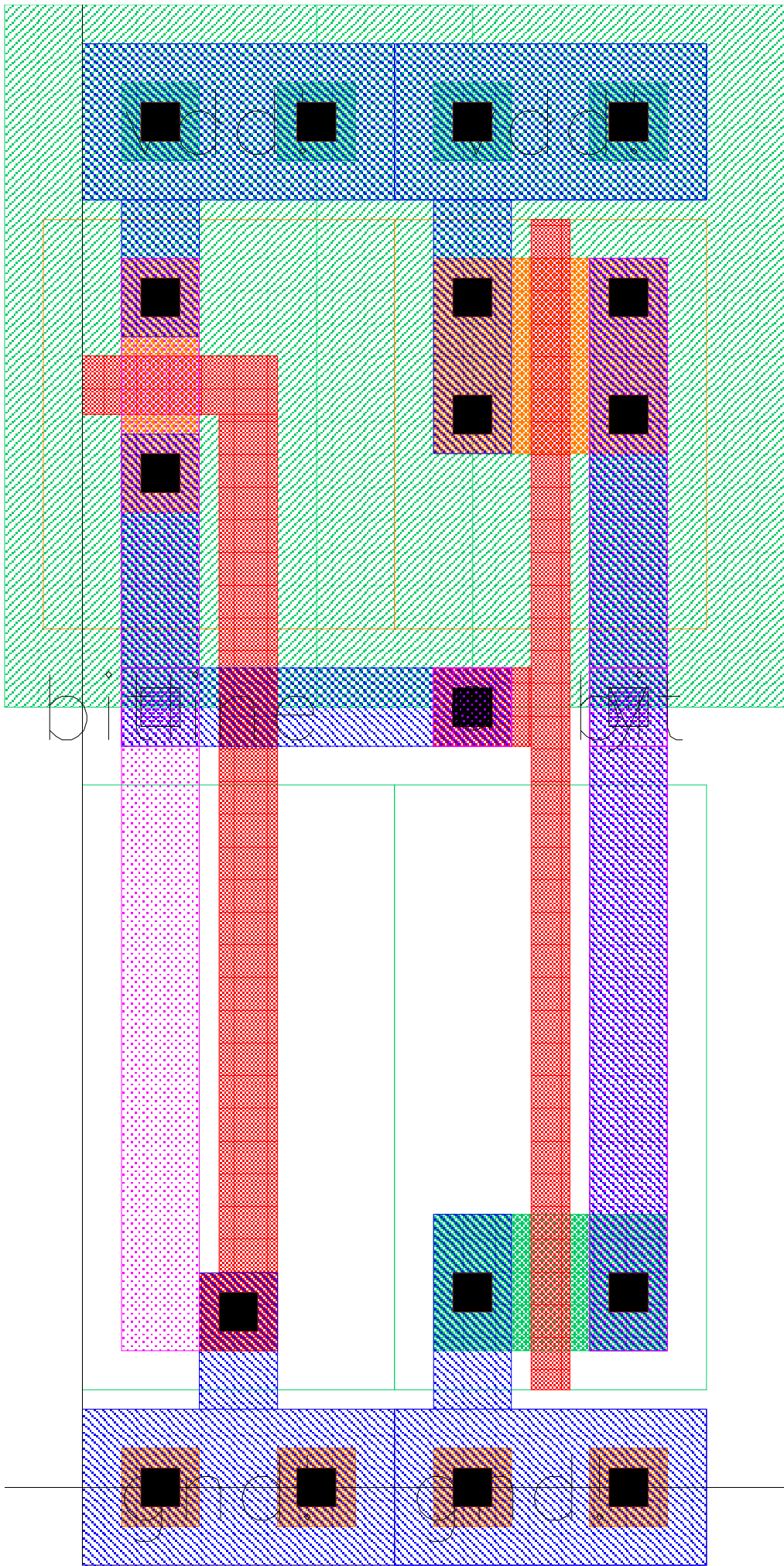




sha1.rom_bitcond32

 






sha1.rom_one

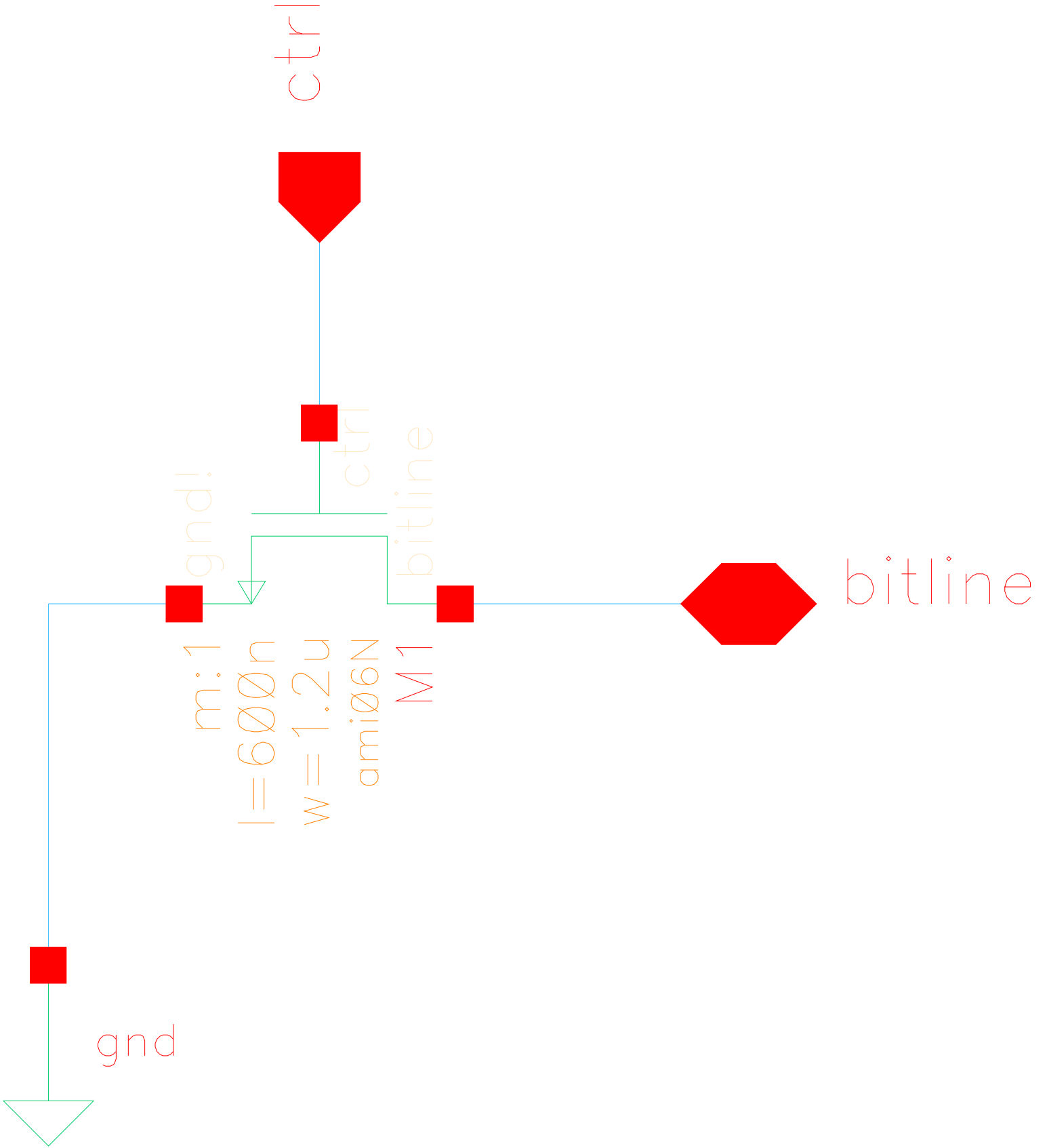

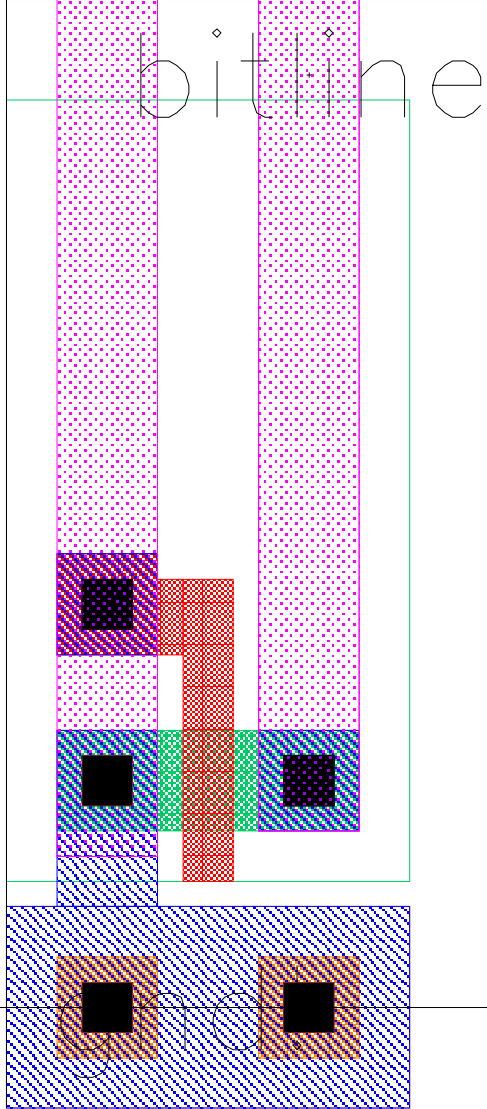 

 

 

 





read

rombit<31:0>

sha1_rom_word2

rombit<31>

rombit<30>

rombit<29>

rombit<28>

rombit<27>

rombit<26>

rombit<25>

rombit<24>

rombit<23>

rombit<22>

rombit<21>

rombit<20>

rombit<19>

rombit<18>

rombit<17>

rombit<16>

rombit<15>

rombit<14>

rombit<13>

rombit<12>

rombit<11>

rombit<10>

rombit<9>

rombit<8>

rombit<7>

rombit<6>

rombit<5>


rombit<4>

rombit<3>

rombit<2>

rombit<1>

rombit<0>

 






read

rombit<31:8>

sha1.rom_word3

 







read

rombit<31:0>

sha1.rom_word4

 



 





read

rombit<31:0>

sha1.rom_word6

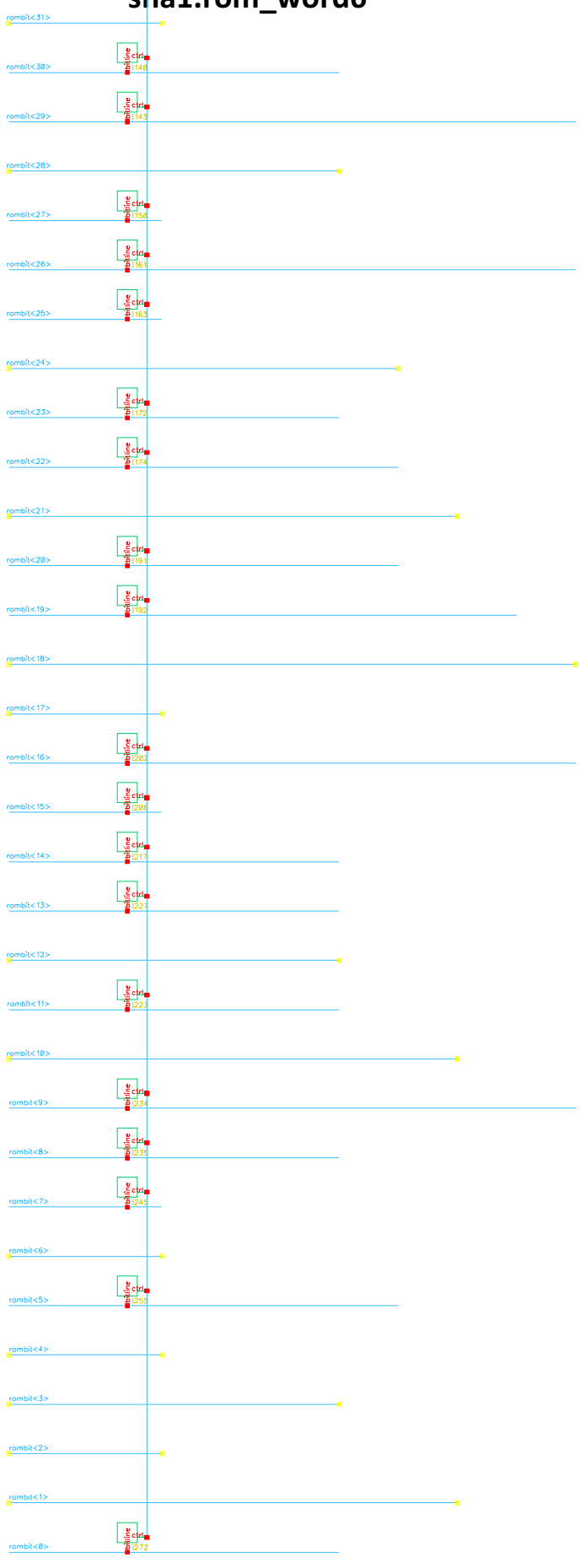



 










read

rombit<31:0>

sha1.rom_word8

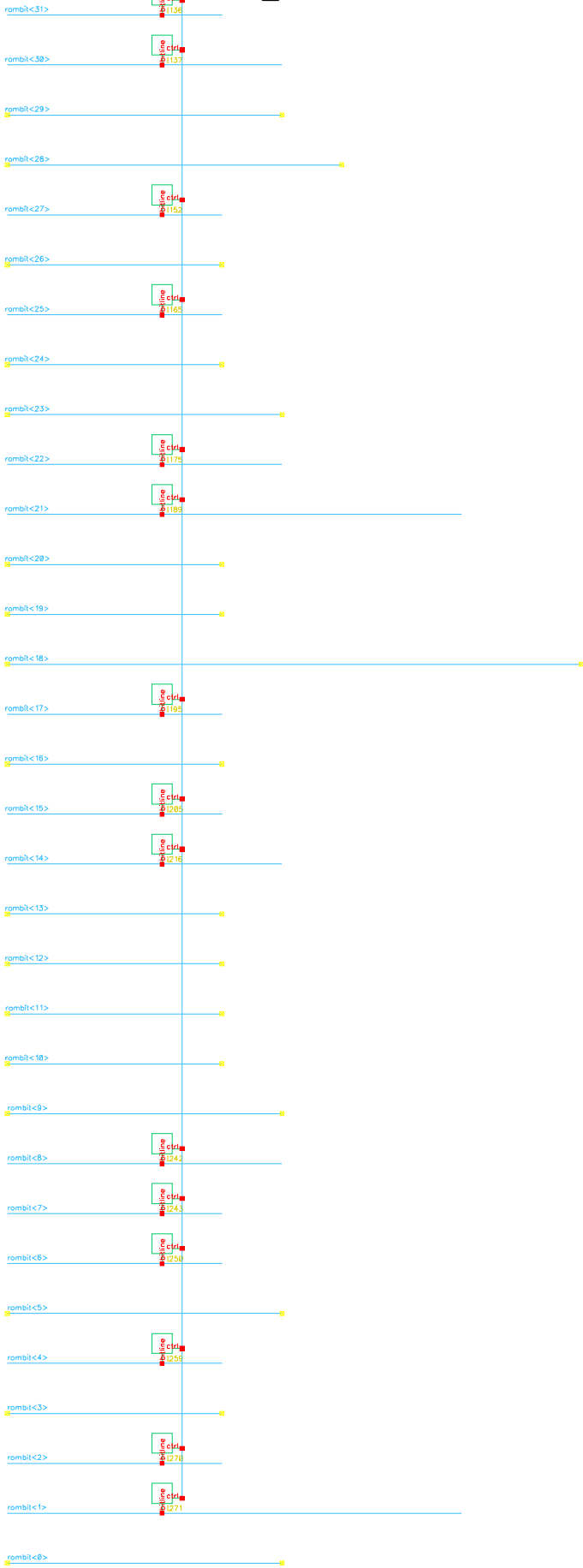




    

sha1.sram_cell

REVISIONS			
ZONE	REV	DESCRIPTION	DATE

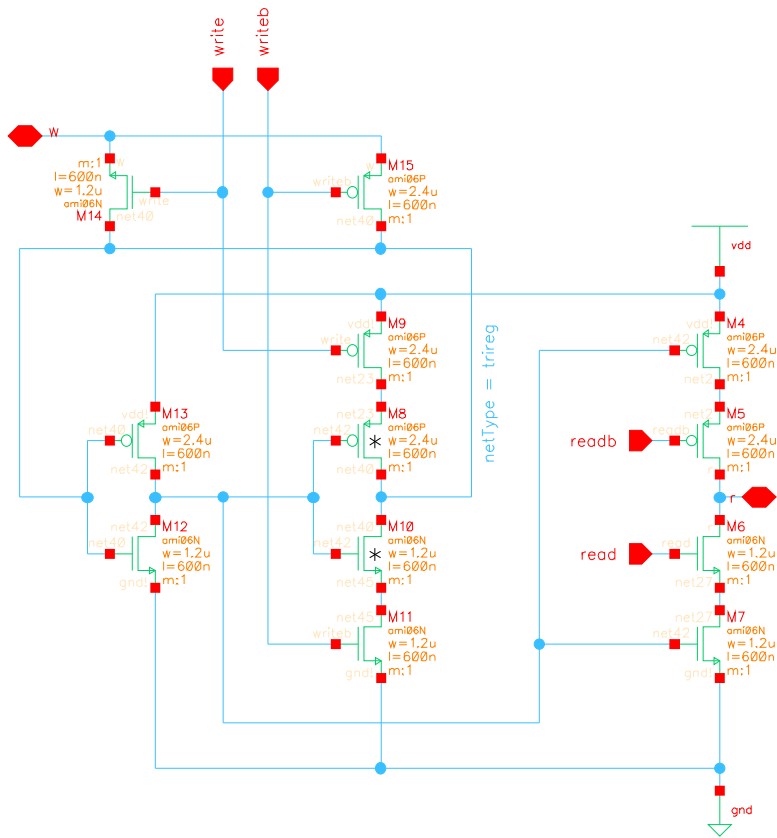

Harvey Mudd College

UPDATED
Apr 5 23:47:52 2010

BY
wbuik


SIZE
A

REV

regram_dp


SHEET

1 of 1

 

sha1.sram11_addrbuf

REVISIONS			
ZONE	REV	DESCRIPTION	DATE

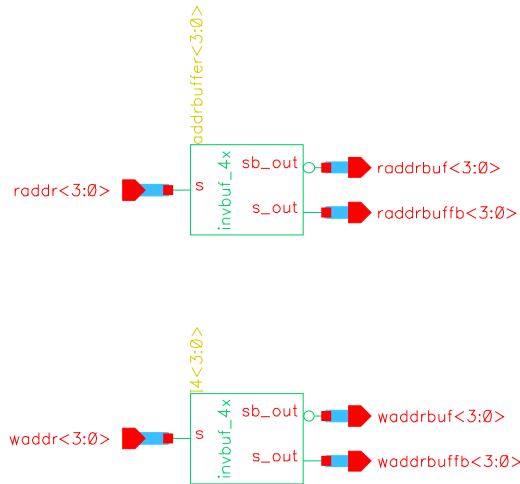

Harvey Mudd College

UPDATED
Mar 30 13:52:24 2010

BY
wbuik


SIZE
A

REV

regramadrbuf


SHEET

1 of 1

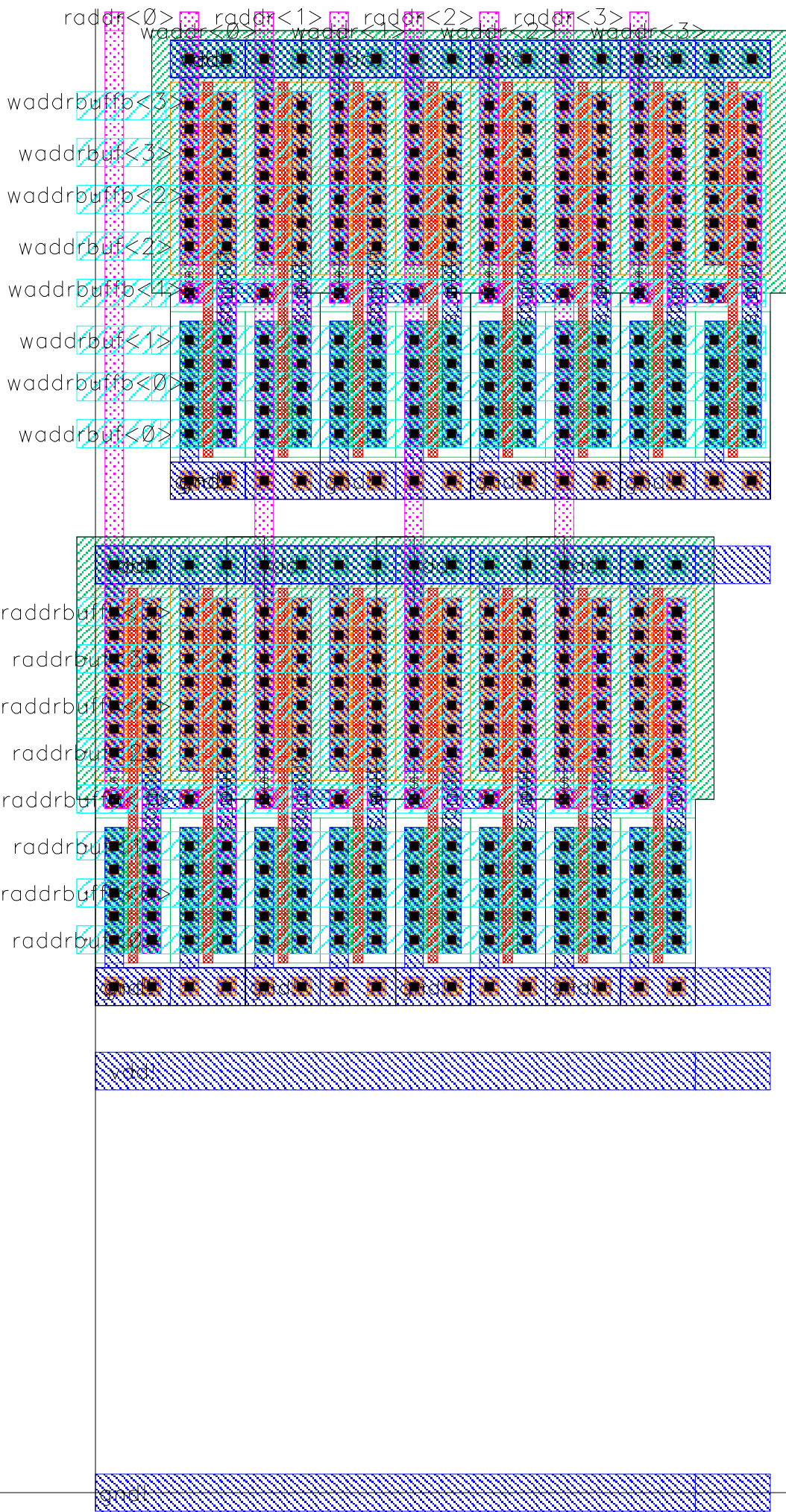

sha1.sram11_word

REVISIONS			
ZONE	REV	DESCRIPTION	DATE

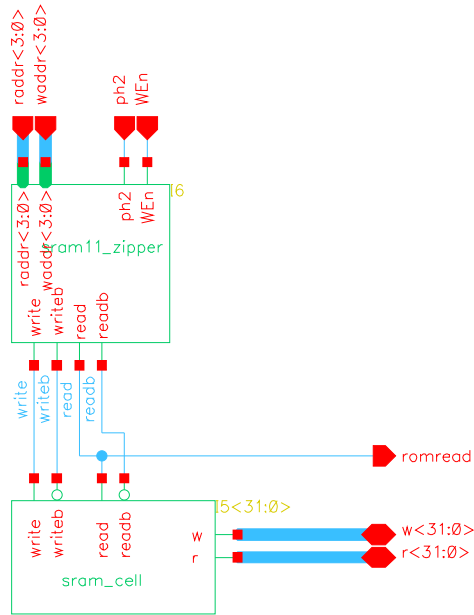

Harvey Mudd College

UPDATED
Apr 13 15:06:37 2010

BY
wbuik

SIZE
A

REV

regramvector_dp


SHEET

1 of 1



sha1.sram11_zipper

REVISIONS			
ZONE	REV	DESCRIPTION	DATE

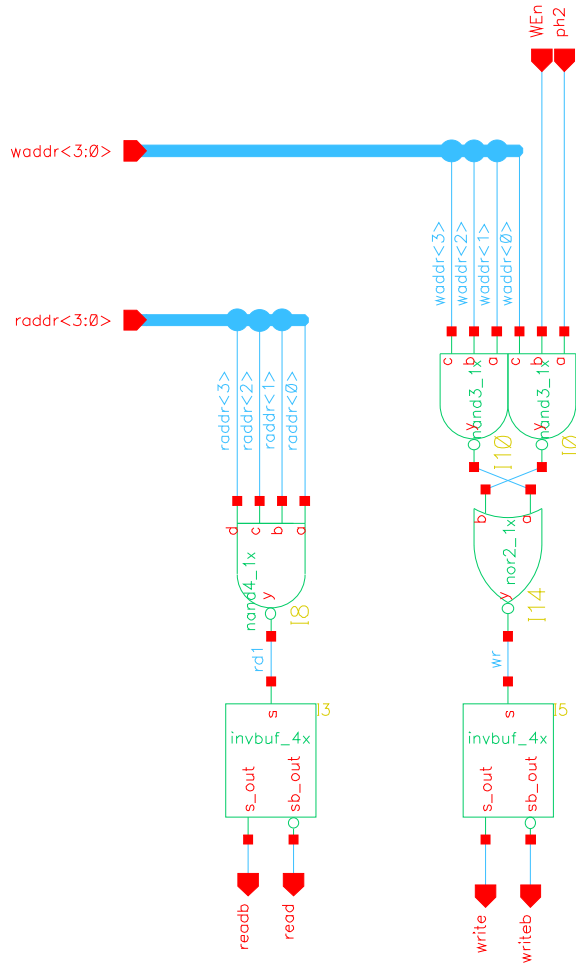

Harvey Mudd College

UPDATED
Apr 6 19:04:17 2010

BY
wbuik




SIZE
A

REV


regram_zipper


SHEET

1 of 1

 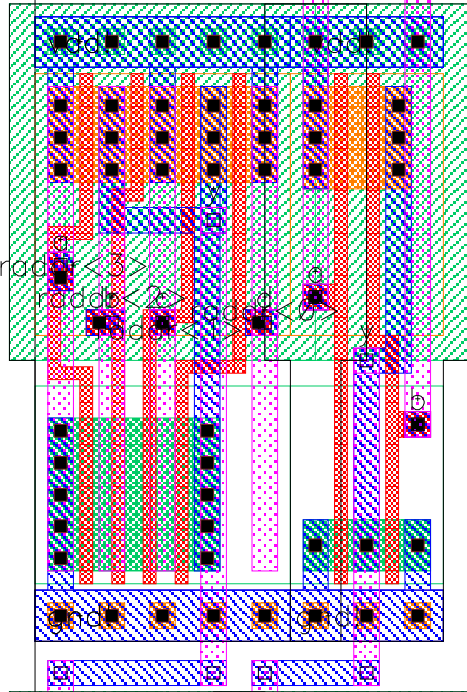 



sha1.sram1rom

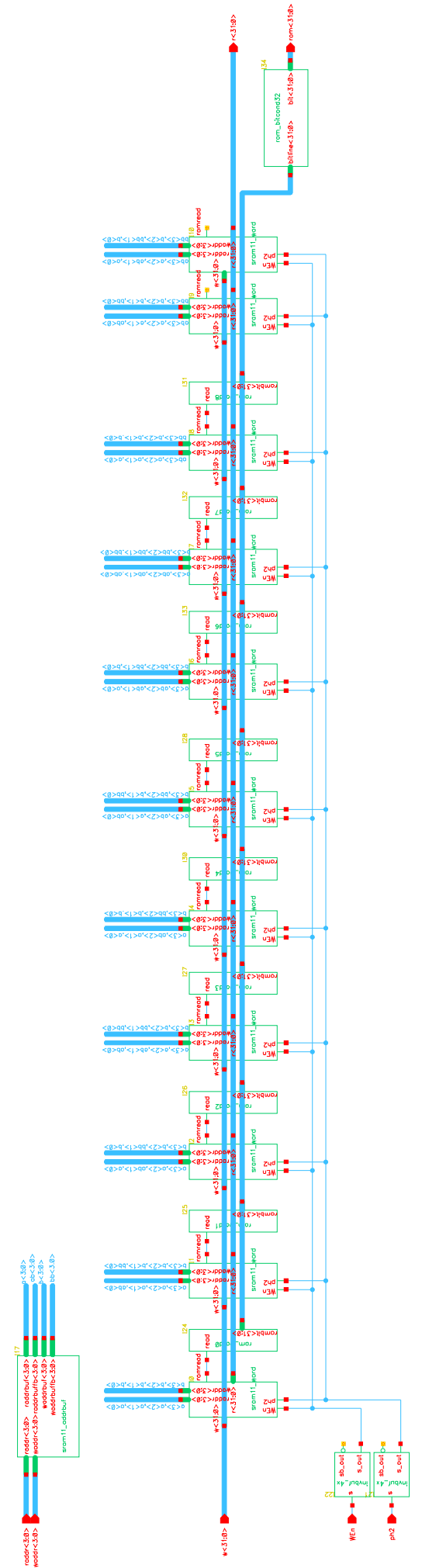

 


sha1.sram16

 

 

sha1.sram16_addrbuf

REVISIONS			
ZONE	REV	DESCRIPTION	DATE

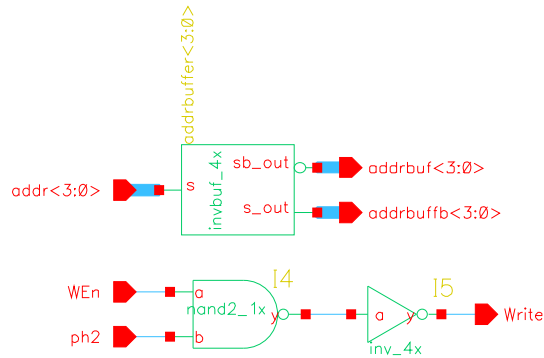

Harvey Mudd College

UPDATED
Apr 6 16:17:21 2010

BY
wbuik


SIZE
A

REV

regramadrbuf


SHEET

1 of 1

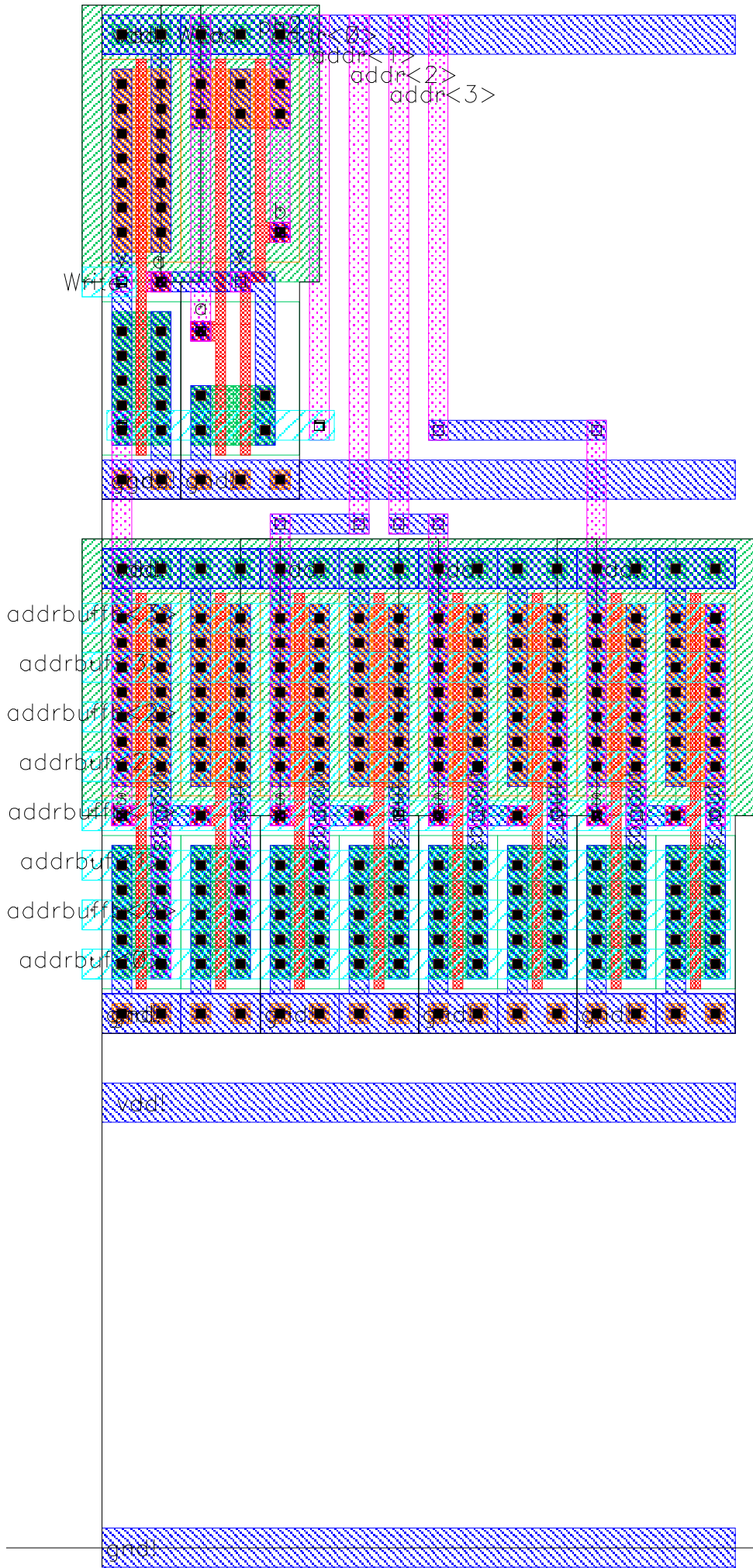

sha1.sram16_word

REVISIONS			
ZONE	REV	DESCRIPTION	DATE

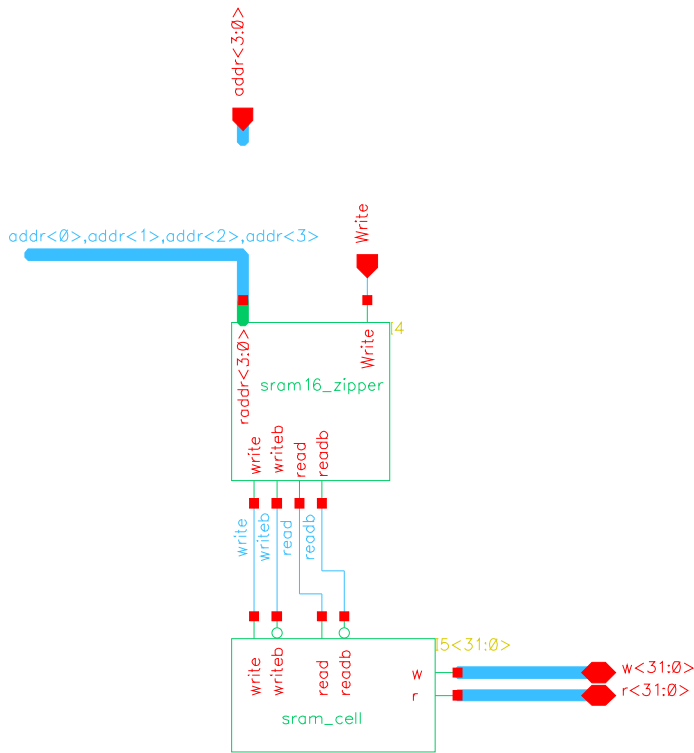

Harvey Mudd College

UPDATED
Apr 12 16:02:53 2010

BY
wbuik

SIZE
A

REV

regramvector_dp


SHEET

1 of 1



sha1.sram16_zipper

REVISIONS			
ZONE	REV	DESCRIPTION	DATE

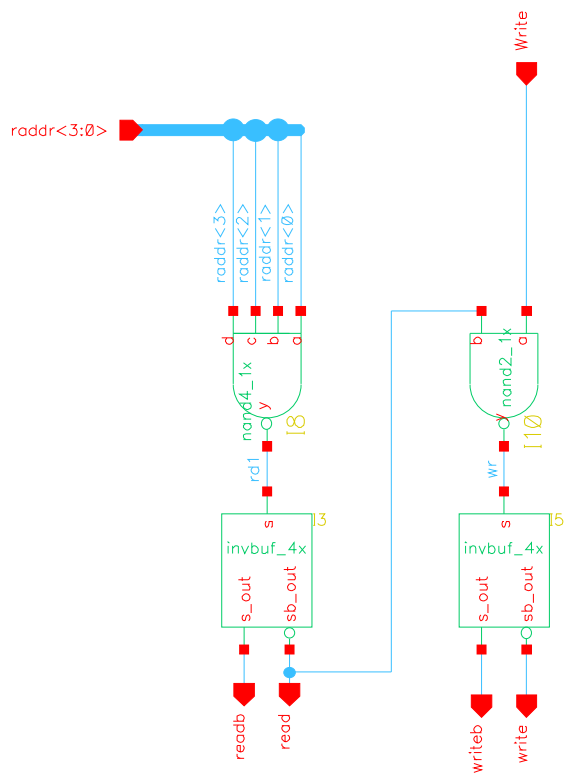

Harvey Mudd College

UPDATED
Apr 12 01:58:09 2010

BY
wbuik


SIZE
A

REV


regram_zipper

SHEET

1 of 1

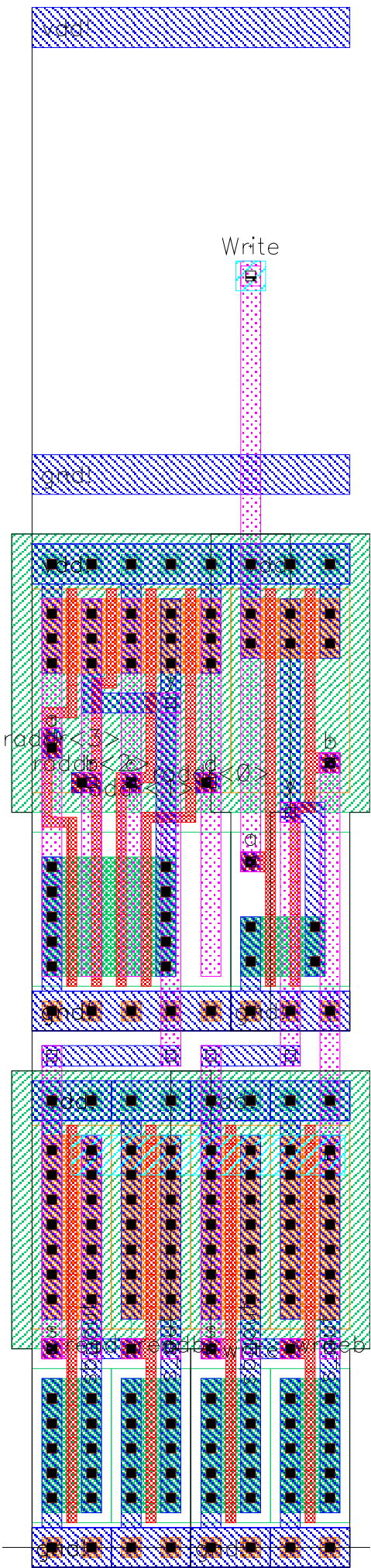


REVISIONS		DATE
ZONE	REV	sha1.tristate


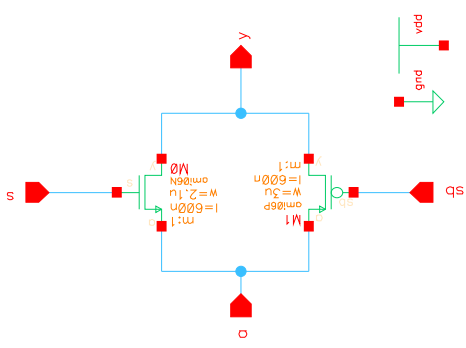



Harvey Mudd College

UPDATED	inv_1x	SHEET	1 of 1
Mar 29 20:43:00 2010			
BY	wbuiik		
SIZE	A		
REV			

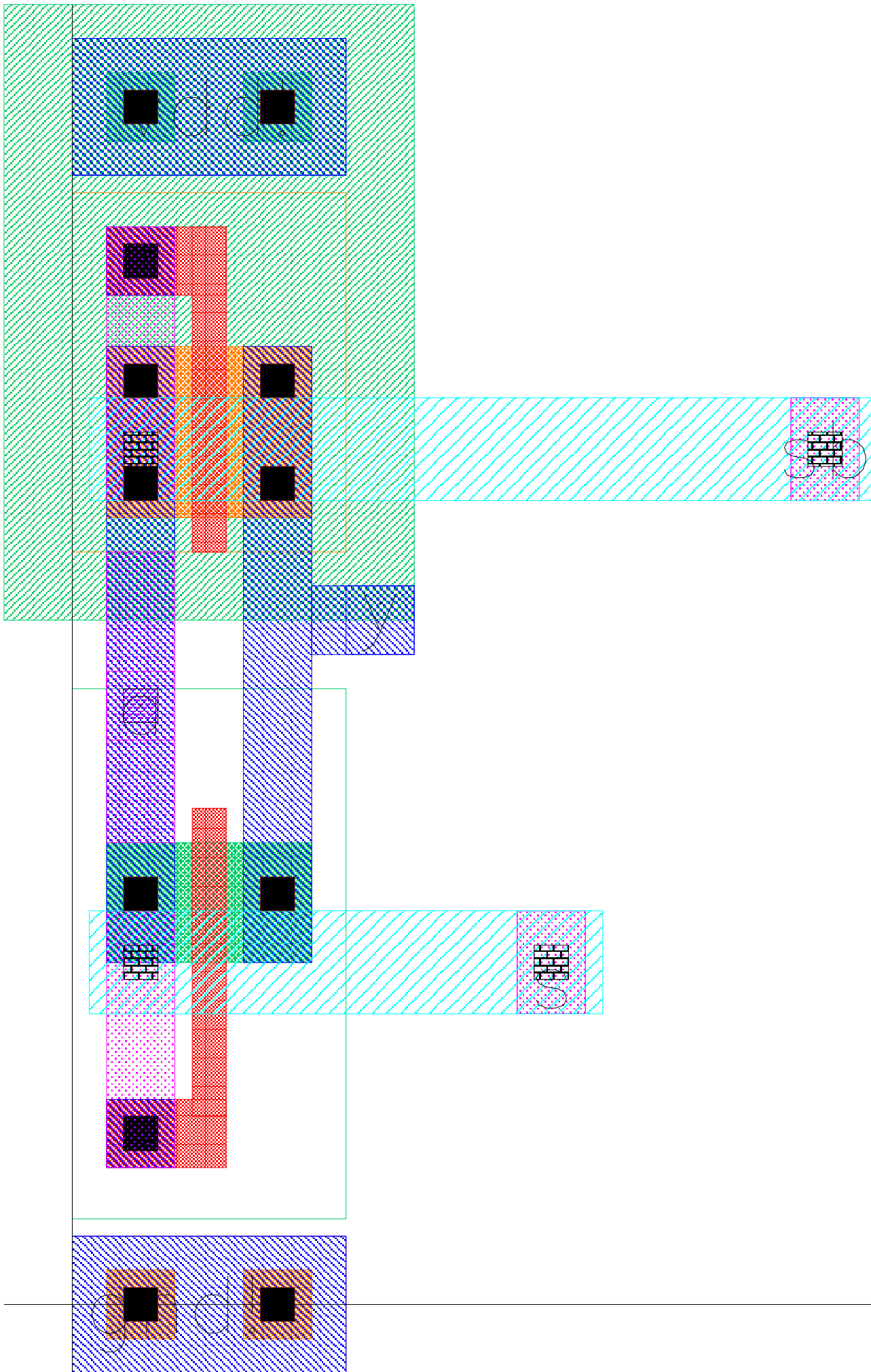


sha1.xor

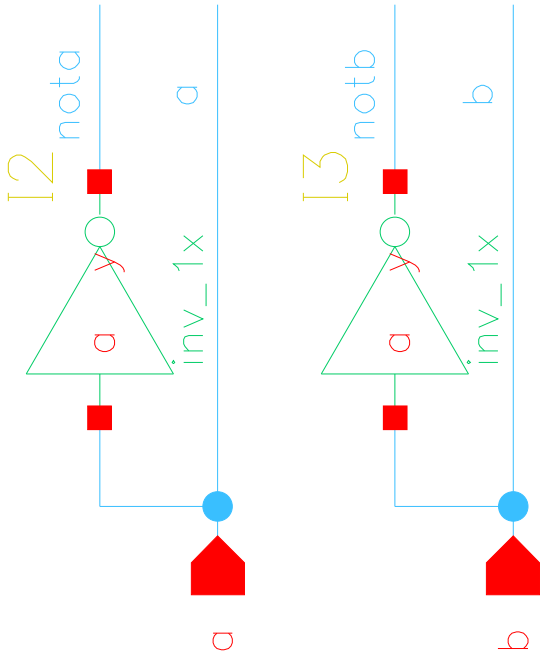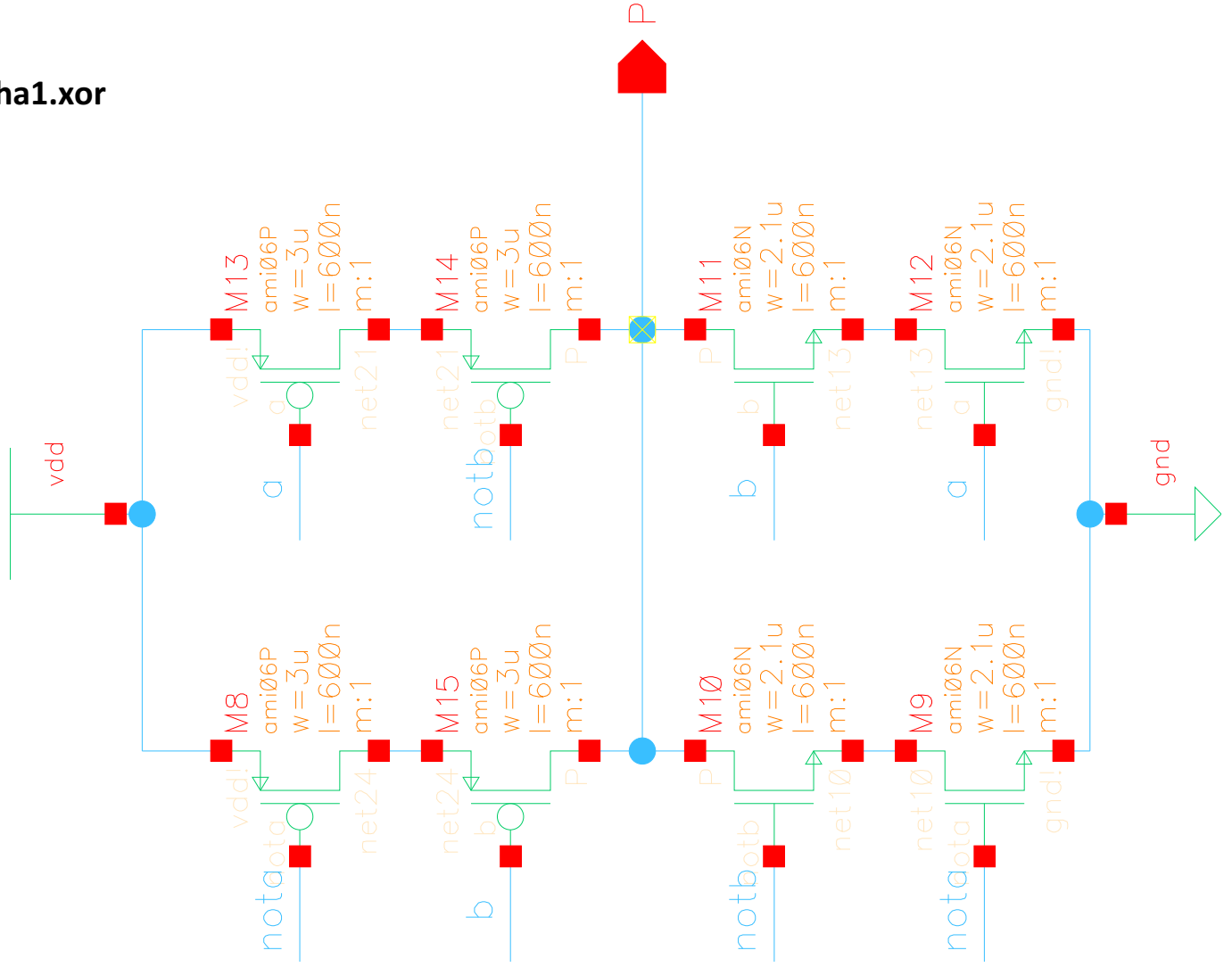


 

sha1_alu.alu


ALUrot<1:0>
ALUop<1:0>

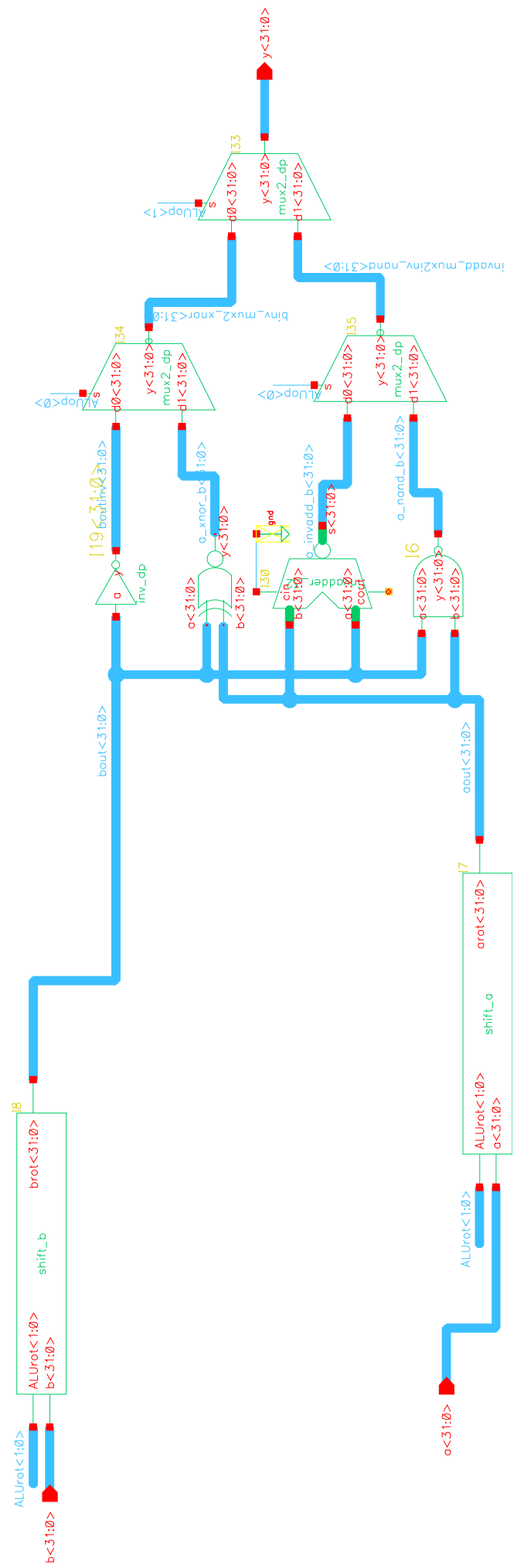

 

sha1_alu.invadder_32

REVISIONS			
ZONE	REV	DESCRIPTION	DATE

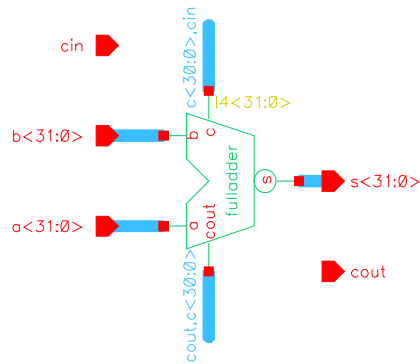

Harvey Mudd College

UPDATED
Apr 14 02:47:32 2010

BY
wbuik


SIZE
A

REV

adder_8


SHEET

1 of 1

 

REVISIONS		DESCRIPTION	
ZONE	REV		

DATE sha1_alu.invfulladder

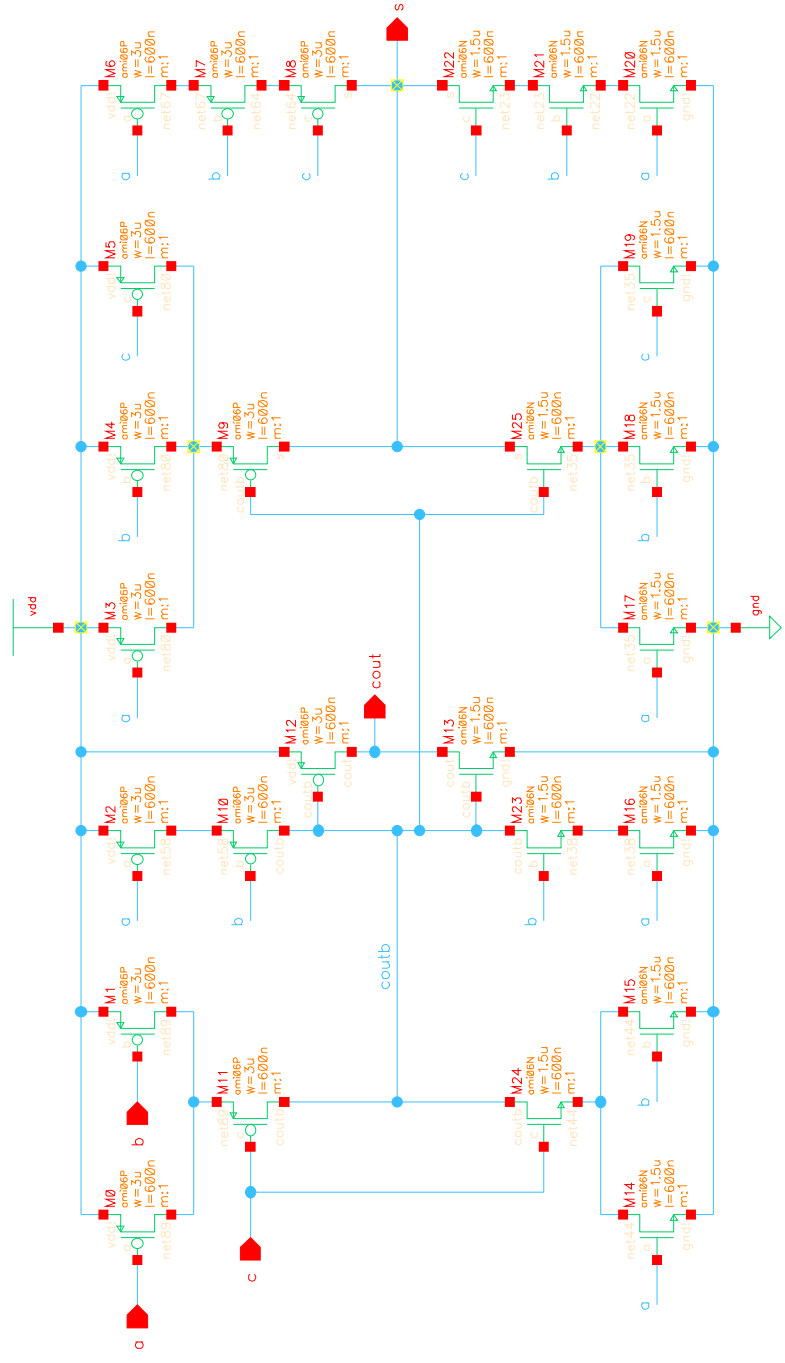


Harvey Mudd College

fulladder


UPDATED Apr 14 01:50:19 2010

BY wbuik

SIZE A REV

 


sha1_alu.invmux2_32

 



sha1_alu.invmux2_dp

REVISIONS			
ZONE	REV	DESCRIPTION	DATE

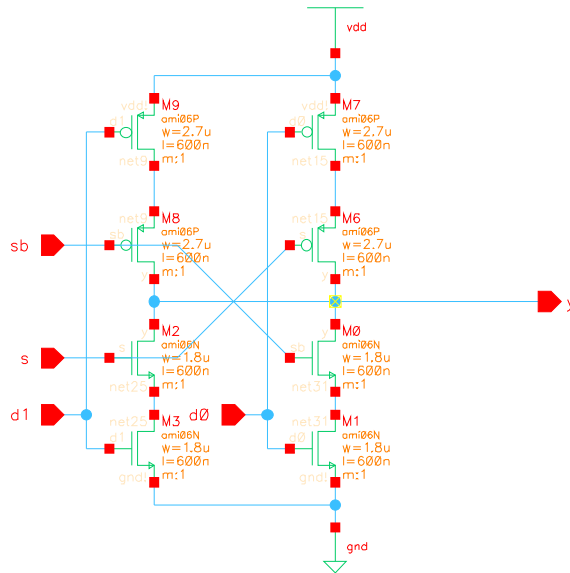

Harvey Mudd College

UPDATED
Mar 29 23:52:23 2010

BY
wbuik


SIZE
A

REV


mux2_dp_1x

SHEET

1 of 1



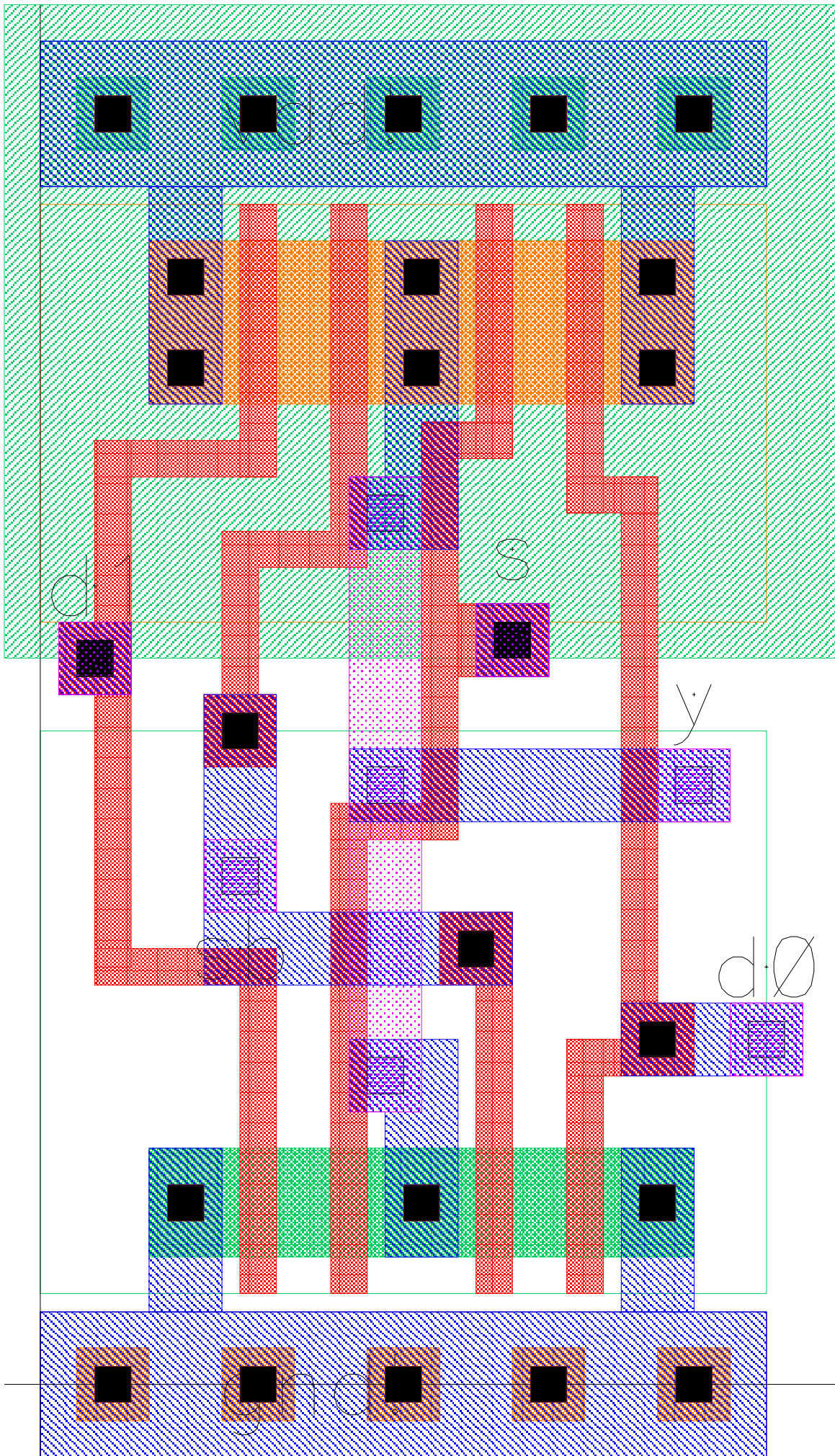


REVISIONS		DATE
ZONE	REV	sha1_alu.nand2_1x
DESCRIPTION		

 



Harvey Mudd College

UPDATED	nand2_1x	
Apr 14 02:07:56 2010		
BY	wbuik	
SIZE	REV	
A		
SHEET		1 of 1

  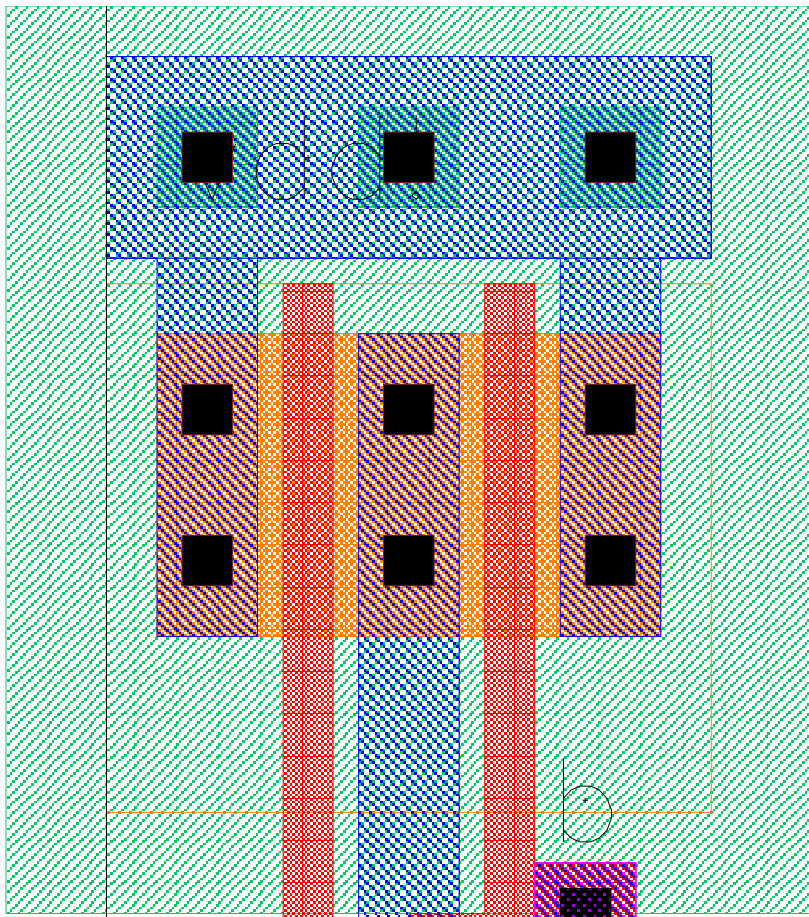



sha1_alu.nand2_32x

 

 



sha1_alu.shift_a

 

 



sha1_alu.shift_b

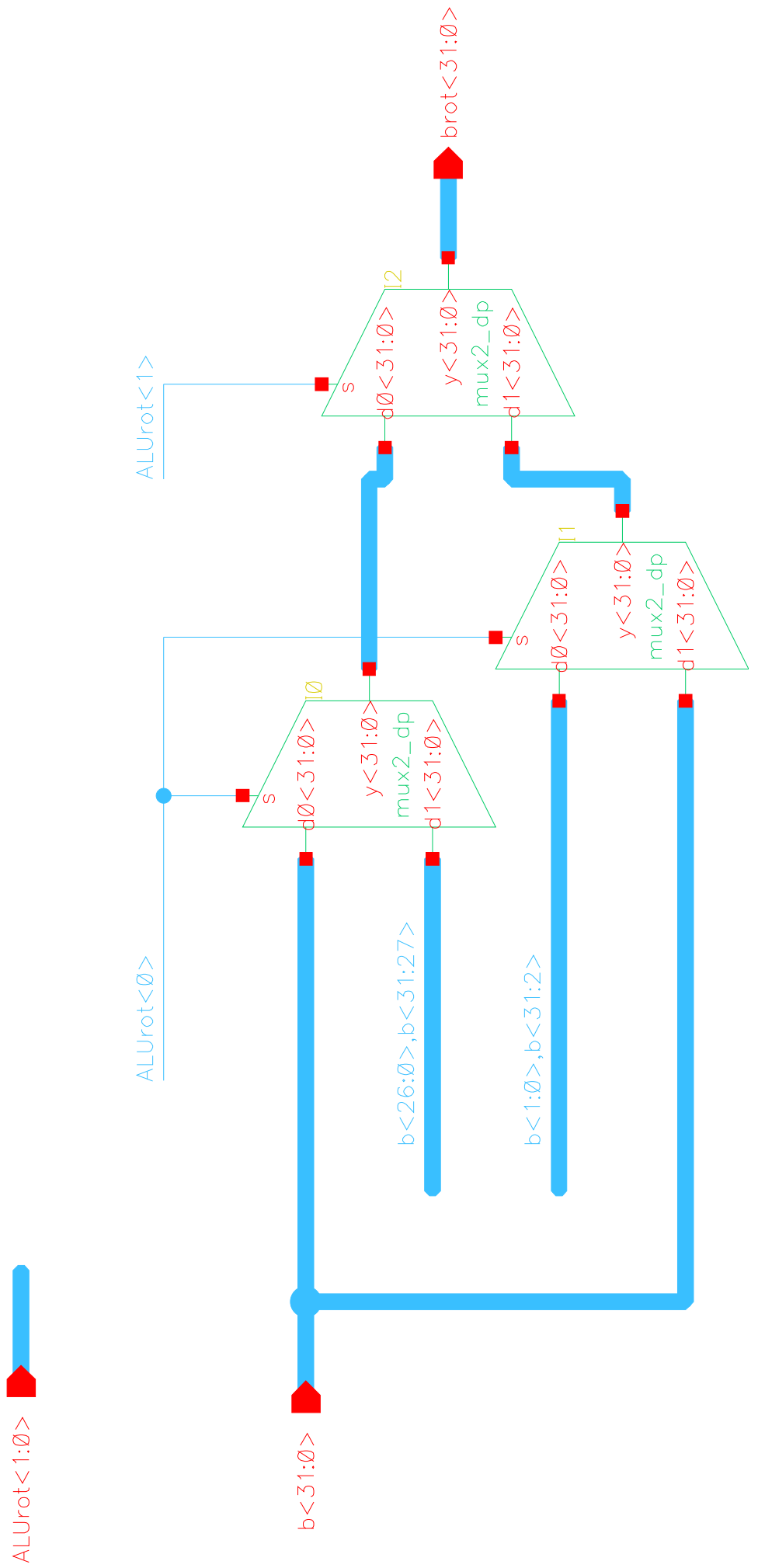

 



sha1_alu.xnor2

 

 

sha1_alu.xnor2_32x

 

 

Appendix C (SHA-1 Pseudocode)

Initialize variables:

```
h0 = 0x67452301
h1 = 0xEFCDAB89
h2 = 0x98BADCFE
h3 = 0x10325476
h4 = 0xC3D2E1F0
```

Pre-processing:

```
append the bit '1' to the message
append  $0 \leq k < 512$  bits '0', so that the resulting message length (in bits)
  is congruent to  $448 \equiv -64 \pmod{512}$ 
append length of message (before pre-processing), in bits, as 64-bit big-endian integer
```

Process the message in successive 512-bit chunks:

```
break message into 512-bit chunks
```

```
for each chunk
```

```
  break chunk into sixteen 32-bit big-endian words  $w[i]$ ,  $0 \leq i \leq 15$ 
```

Extend the sixteen 32-bit words into eighty 32-bit words:

```
for i from 16 to 79
   $w[i] = (w[i-3] \text{ xor } w[i-8] \text{ xor } w[i-14] \text{ xor } w[i-16])$  leftrotate 1
```

Initialize hash value for this chunk:

```
a = h0
b = h1
c = h2
d = h3
e = h4
```

Main loop:

```
for i from 0 to 79
  if  $0 \leq i \leq 19$  then
     $f = (b \text{ and } c) \text{ xor } ((\text{not } b) \text{ and } d)$ 
     $k = 0x5A827999$ 
  else if  $20 \leq i \leq 39$ 
     $f = b \text{ xor } c \text{ xor } d$ 
     $k = 0x6ED9EBA1$ 
  else if  $40 \leq i \leq 59$ 
     $f = (b \text{ and } c) \text{ xor } (b \text{ and } d) \text{ xor } (c \text{ and } d)$ 
     $k = 0x8F1BBCDC$ 
  else if  $60 \leq i \leq 79$ 
     $f = b \text{ xor } c \text{ xor } d$ 
     $k = 0xCA62C1D6$ 

  temp = (a leftrotate 5) + f + e + k + w[i]
  e = d
  d = c
  c = b leftrotate 30
  b = a
  a = temp
```

Add this chunk's hash to result so far:

```
h0 = h0 + a
h1 = h1 + b
h2 = h2 + c
h3 = h3 + d
h4 = h4 + e
```

Produce the final hash value (big-endian):

```
digest = hash = h0 append h1 append h2 append h3 append h4
```

Source: <http://en.wikipedia.org/wiki/Sha1>, accessed 4/19/2010.

Appendix D (Test Bench Generator)

C# code used to calculate the state of all registers for each round of the SHA1 algorithm as the chip implements it. Used to debug the Verilog implementation of the chip and to generate test benches.

```
using System;
using System.Collections.Generic;
using System.Linq;
using System.Text;

namespace SHATest {
    class Program {

        static UInt32 RotateLeft(UInt32 x, int num) {
            for (; num > 0; num--) {
                UInt32 temp = (x >> 31) & 0x00000001;
                x = (x << 1) | temp;
            }
            return x;
        }

        enum OP {
            PASS,
            ADD,
            AND,
            XOR
        }

        enum LROT : int {
            NONE = 0,
            ONE_A = 1,
            FIVE_B = 5,
            THIRTY_B = 30
        }

        static UInt32 ALU(UInt32 a, UInt32 b, OP op, LROT lrot) {

            if(lrot == LROT.FIVE_B || lrot == LROT.THIRTY_B)
                b = RotateLeft(b, (int)lrot);
            if (lrot == LROT.ONE_A)
                a = RotateLeft(a, (int)lrot);

            switch (op) {
                case OP.ADD:
                    return a + b;
                case OP.XOR:
                    return a ^ b;
                case OP.PASS:
                    return b;
                case OP.AND:
                    return a & b;
            }
            return 0;
        }

        static void Main(string[] args) {

            // Memory
            UInt32[] W = new UInt32[16];
            UInt32 A = 0, B = 0, C = 0, D = 0, E = 0, t2 = 0;
            UInt32 H0 = 0, H1 = 0, H2 = 0, H3 = 0, H4 = 0;
            UInt32 t1 = 0;

            UInt32 NULL = 0;

            // Constants
            UInt32 Zero = 0;
            UInt32 AInit = 0x67452301;
            UInt32 BInit = 0xEFCDAB89;
```

```

UInt32 CInit = 0x98BADCFE;
UInt32 DInit = 0x10325476;
UInt32 EInit = 0xC3D2E1F0;
UInt32 K1 = 0x5A827999;
UInt32 K2 = 0x6ED9EBA1;
UInt32 K3 = 0x8F1BBCDC;
UInt32 K4 = 0xCA62C1D6;

// Initilize
//for (int i = 0; i < 16; i++) W[i] = 0xFFFFFFFF;
//W[0] = 0x80000000;
//for (int i = 1; i < 14; i++) W[i] = 0;
//W[14] = 0;
//W[15] = 0;

W[0] = 0x8A921FC4;
W[1] = 0x452C45D2;
W[2] = 0xABC243FE;
W[3] = 0xEC429CBD;
W[4] = 0x452C45D2;
W[5] = 0xEC429CBD;
W[6] = 0x452C45D2;
W[7] = 0xEC429CBD;
W[8] = 0x8A921FC4;
W[9] = 0x452C45D2;
W[10] = 0xABC243FE;
W[11] = 0x452C45D2;
W[12] = 0xEC429CBD;
W[13] = 0x452C45D2;
W[14] = 0x8A921FC4;
W[15] = 0x452C45D2;

//for (int i = 0; i < 16; i++) W[i] = 0x8A921FC4;

H0 = AInit;
H1 = BInit;
H2 = CInit;
H3 = DInit;
H4 = EInit;

A = H0;
B = H1;
C = H2;
D = H3;
E = H4;

for (int i = 0; i < 80; i++) {
    // Crypto
    //

    //Calc f
    if (i >= 0 && i < 20) {
        //F = (B & C) ^ (~B & D);
        t1 = ALU(NULL, D, OP.PASS, LROT.NONE);
        t1 = ALU(t1, C, OP.XOR, LROT.NONE);
        t1 = ALU(t1, B, OP.AND, LROT.NONE);
        t1 = ALU(t1, D, OP.XOR, LROT.NONE);

        t1 = ALU(t1, K1, OP.ADD, LROT.NONE);
    } else if (i >= 20 && i < 40) {
        // F = B ^ C ^ D
        t1 = ALU(NULL, B, OP.PASS, LROT.NONE);
        t1 = ALU(t1, C, OP.XOR, LROT.NONE);
        t1 = ALU(t1, D, OP.XOR, LROT.NONE);

        t1 = ALU(t1, K2, OP.ADD, LROT.NONE);
    } else if (i >= 40 && i < 60) {
        //F = (B & C) ^ (B & D) ^ (C & D);
        t1 = ALU(NULL, C, OP.PASS, LROT.NONE);

```



```

        t2 = ALU(t1, D, OP.AND, LROT.NONE);
        t1 = ALU(NULL, C, OP.PASS, LROT.NONE);
        t1 = ALU(t1, D, OP.XOR, LROT.NONE);
        t1 = ALU(t1, B, OP.AND, LROT.NONE);
        t1 = ALU(t1, t2, OP.XOR, LROT.NONE);

        t1 = ALU(t1, K3, OP.ADD, LROT.NONE);
    } else if (i >= 60 && i < 80) {
        // F = B ^ C ^ D
        t1 = ALU(NULL, B, OP.PASS, LROT.NONE);
        t1 = ALU(t1, C, OP.XOR, LROT.NONE);
        t1 = ALU(t1, D, OP.XOR, LROT.NONE);

        t1 = ALU(t1, K4, OP.ADD, LROT.NONE); //(C & D) + (B & (C # D))
    }

    t1 = ALU(t1, E, OP.ADD, LROT.NONE);
    t1 = ALU(t1, A, OP.ADD, LROT.FIVE_B);
    t1 = ALU(t1, W[0], OP.ADD, LROT.NONE);

    // New state

    E = ALU(NULL, D, OP.PASS, LROT.NONE);
    D = ALU(NULL, C, OP.PASS, LROT.NONE);
    C = ALU(NULL, B, OP.PASS, LROT.THIRTY_B);
    B = ALU(NULL, A, OP.PASS, LROT.NONE);
    A = ALU(t1, Zero, OP.ADD, LROT.NONE); // Pass A

    string aa = String.Format("{0:X8}", A);
    string bb = String.Format("{0:X8}", B);
    string cc = String.Format("{0:X8}", C);
    string dd = String.Format("{0:X8}", D);
    string ee = String.Format("{0:X8}", E);

    //Console.WriteLine(aa + " " + bb + " " + cc + " " + dd + " " + ee);

    // Message Extension
    //
    t1 = ALU(NULL, W[0], OP.PASS, LROT.NONE);
    t1 = ALU(t1, W[2], OP.XOR, LROT.NONE);
    t1 = ALU(t1, W[8], OP.XOR, LROT.NONE);
    t1 = ALU(t1, W[13], OP.XOR, LROT.NONE);
    t1 = ALU(t1, Zero, OP.ADD, LROT.ONE_A);

    // Downshift W
    for (int j = 0; j < 15; j++) {
        W[j] = W[j + 1];
    }
    W[15] = t1;
}

t1 = ALU(NULL, A, OP.PASS, LROT.NONE);
H0 = ALU(t1, H0, OP.ADD, LROT.NONE);

t1 = ALU(NULL, B, OP.PASS, LROT.NONE);
H1 = ALU(t1, H1, OP.ADD, LROT.NONE);

t1 = ALU(NULL, C, OP.PASS, LROT.NONE);
H2 = ALU(t1, H2, OP.ADD, LROT.NONE);

t1 = ALU(NULL, D, OP.PASS, LROT.NONE);
H3 = ALU(t1, H3, OP.ADD, LROT.NONE);

t1 = ALU(NULL, E, OP.PASS, LROT.NONE);
H4 = ALU(t1, H4, OP.ADD, LROT.NONE);

string Ahex = String.Format("{0:X8}", H0);
string Bhex = String.Format("{0:X8}", H1);
string Chex = String.Format("{0:X8}", H2);
string Dhex = String.Format("{0:X8}", H3);

```

```
string Ehex = String.Format("{0:X8}", H4);

Console.WriteLine("");
Console.WriteLine(Ahex + " " + Bhex + " " + Chex + " " + Dhex + " " + Ehex);
//Console.WriteLine("da39a3ee 5e6b4b0d 3255bfef 95601890 afd80709".ToUpper());

Console.ReadKey();

}
}
}
```