

Conway's Game of Life

Narayan Propato
Nicholas Card

Contents

Introduction.....	3
Specifications.....	3
Floorplan.....	4
Verification.....	5
Postfabrication Test Plan.....	5
Design Time.....	6
References.....	6

Appendix

A1: Floorplan.....	7
A2: File Locations.....	11
A3: Verilog Code.....	13
A4: Test Materials.....	26
A5: Schematics and Layouts.....	31

Introduction

The goal of this project is to implement Conway's Game of Life on a 1.5 x 1.5 mm 40-pin MOSIS "TinyChip" fabricated in a 0.6 μm process. Conway's Game of Life consists of a matrix (8 by 8 in this project) consisting of dead and live cells. The user is able to provide a starting matrix, and then the chip will calculate subsequent iterations of the matrix according to a set of rules and output this data.

Specifications

The user is able to input rows of data making up the initial state of the 8 by 8 board. The user interface comprises a reset button, an enter button, and eight switches. Each switch corresponds to a cell in a row (0 for dead and 1 for alive), while the enter button is used to input the set of values on the switches into the currently selected row. When all row data has been entered, each press of the button causes the next iteration of the board to be calculated according to the following rules:

1. A live cell with fewer than 2 adjacent live cells dies.
2. A live cell with more than 3 adjacent live cells dies.
3. A live cell with 2 or 3 adjacent live cells continues to live.
4. A dead cell with exactly 3 adjacent live cells becomes a live cell ("Conway").

The reset button is used to start a new game. The board information is stored in an SRAM memory block and outputted via the ledpower[7:0] pins and ledcolumn[7:0] pins. The chip uses time multiplexing to quickly cycle power between the 8 ledpower signals, each of which will be connected to a row of an 8 by 8 dot-matrix LED display. The 8 ledcolumn signals will be connected to the columns of the display representing the values in the row that is

currently being powered. See Table 1 for a table of all the pins on the chip. The project uses 34 out of the 40 pins: 12 input pins, 16 output pins, and 6 bi-directional pins.

Input Pins	Output Pins
reset	power [7:0]
enter	column [7:0]
switch [7:0]	
ph1, ph2	
VDD/GND [5:0]	

Table 1. Table lists all 40 pins used in the design. Note that only one pair of VDD and GND pins are actually connected to the chip's core.

Floorplan

The proposed floorplan covered six modules: the *controller*, the *register*, the *bit selector*, the *hold mem*, the *output logic*, and the *temp mem*, as seen in Fig. A1.1(a). Other than the register, all modules would be automatically synthesized from Verilog modules. The register would be custom designed, including the *wordline* conditioning logic and the *bitline* conditioning logic (see the slice plan in Fig. A1.2). During further design iterations, all synthesized modules were instanced within a single top-level module, *gameoflife*, to optimize synthesis (see Fig. A1.1(b) for final floorplan and Fig. A1.3 for pinout diagram).

Originally, $4.56 \text{ k}\lambda^2$ was budgeted for all synthesized blocks combined, and the final *gameoflife* block uses $4.34 \text{ k}\lambda^2$, which is 4.9% smaller than expected. This difference is primarily due to the uncertainty in estimating the original controller size.

The custom block takes up $0.47 \text{ k}\lambda^2$, which is 2.15 times the allotted area of $0.22 \text{ k}\lambda^2$. Originally, the register used 6-transistor SRAM cells (Harris 504), but the extra design time required to properly adjust the width-ratio between the bitline conditioning logic and the memory cell proved prohibitive. The cell was thus changed to a 12-transistor version (Harris 506) during subsequent design iterations in order to reduce the design time burden. The area difference

between the proposed and final registers is due to the 12-transistor cell being approximately twice the size of the 6 transistor cell, as well as the extra wiring tracks needed for the extra signals in the 12-transistor cell.

Verification

The Verilog code (see A3.1) passes the testbench on the chosen test vectors (see A4 for testing materials). The schematic (including the register and synthesized logic) also passes the testbench. The layout passes DRC and LVS, confirming that it matches the schematic and therefore passes the testbench.

There is one caveat: due to an undetermined error in the synthesis process, an enable/reset flip-flop synthesizes in part to a mux that loops its output to its select signal. Since the output starts as a conflict \times , the mux never resolves the output. This means that any module with an enable/reset flip-flop will not simulate correctly. To fix this, the output of the latch in the flip-flop must be set to 1 on start. The netlist used to do this is in A3.2.

Postfabrication Test Plan

After fabrication, the chip's VDD and GND pins (pins 5 and 4, respectively) will be connected to a 5 V power supply. The ph1 and ph2 pins will be connected to the appropriate clock sources. The “enter” and “reset” pins will be connected to 1-bit buttons that pass 1 on press. The “switch” pins will be connected to an 8-position DIP switch such as Tyco Electronics' ADE0804 switch. Finally, the output pins will be connected to a dot-matrix LED display such as Avago Technologies' HDSP -S80E/S80G. The “ledpower” pins will be connected to the rows of the display, and the “ledcolumn” pins will be connected to the columns, such that ledpower[7] is connected to the top row and ledcolumn[7] is connected to the left-most

column. Once the circuit is assembled, testing will consist of inputting a test matrix, pressing the enter button to cause the chip to calculate new iterations, and then comparing the resulting matrix with the expected one. If the two match, the chip is fully functional.

Design Time

A breakdown of design time by category is shown in Fig. 1. Coding the Verilog and debugging it for synthesis made up 72% of the man-hours spent on the project.

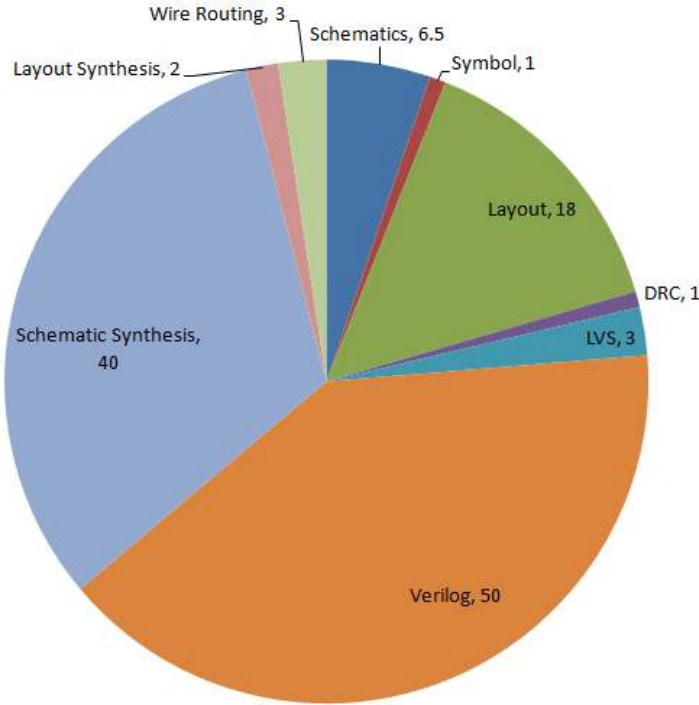


Fig. 1. A breakdown of design time for different design stages in man-hours.

References


“Conway’s Game of Life.” *LifeWiki*. Retrieved from http://www.conwaylife.com/wiki/index.php?title=Conway%27s_Game_of_Life.

Harris, David Money and Weste, Neil H. E. *CMOS VLSI Design*. Boston: Addison-Wesley, 2011.


Appendix 1:

Floorplan

A1.1: Floorplan

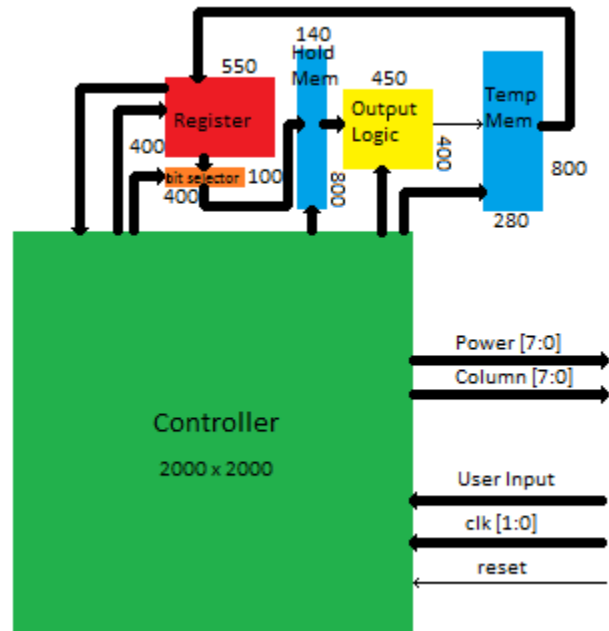

(a)

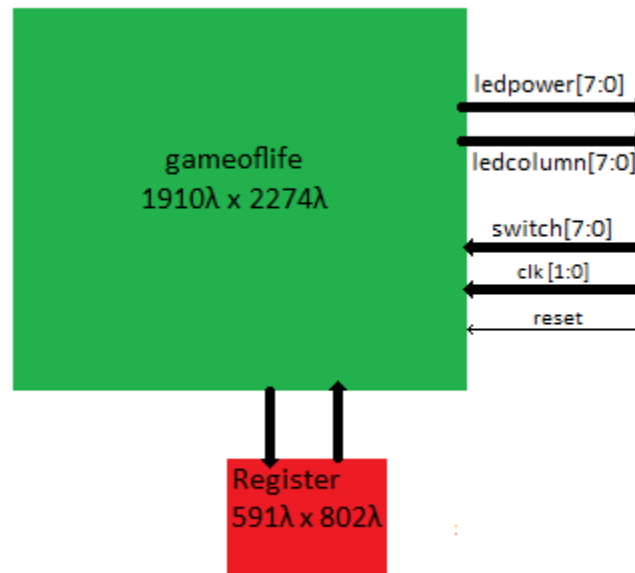

(b)

Figure A1.1. The floorplans from the proposal (a) and from the actual chip (b). The *gameoflife* module contains the *controller*, the *bit selector*, the *output logic*, the *temp mem*, and the *hold mem*.

A1.2: Array Plan

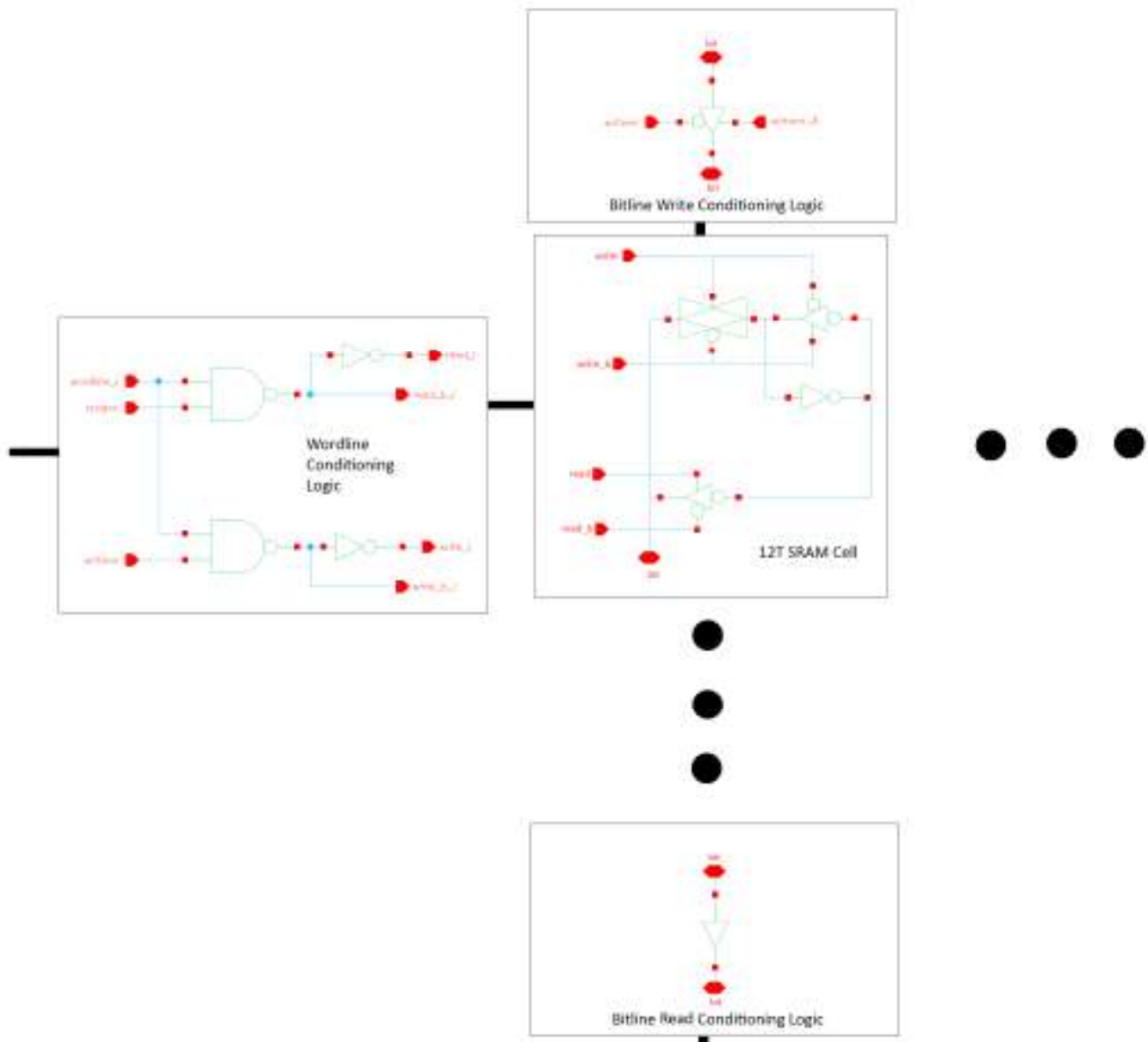


Fig A1.2. An Array Slice from the custom logic. The complete array is 8 x 8.

A1.3: Pinout

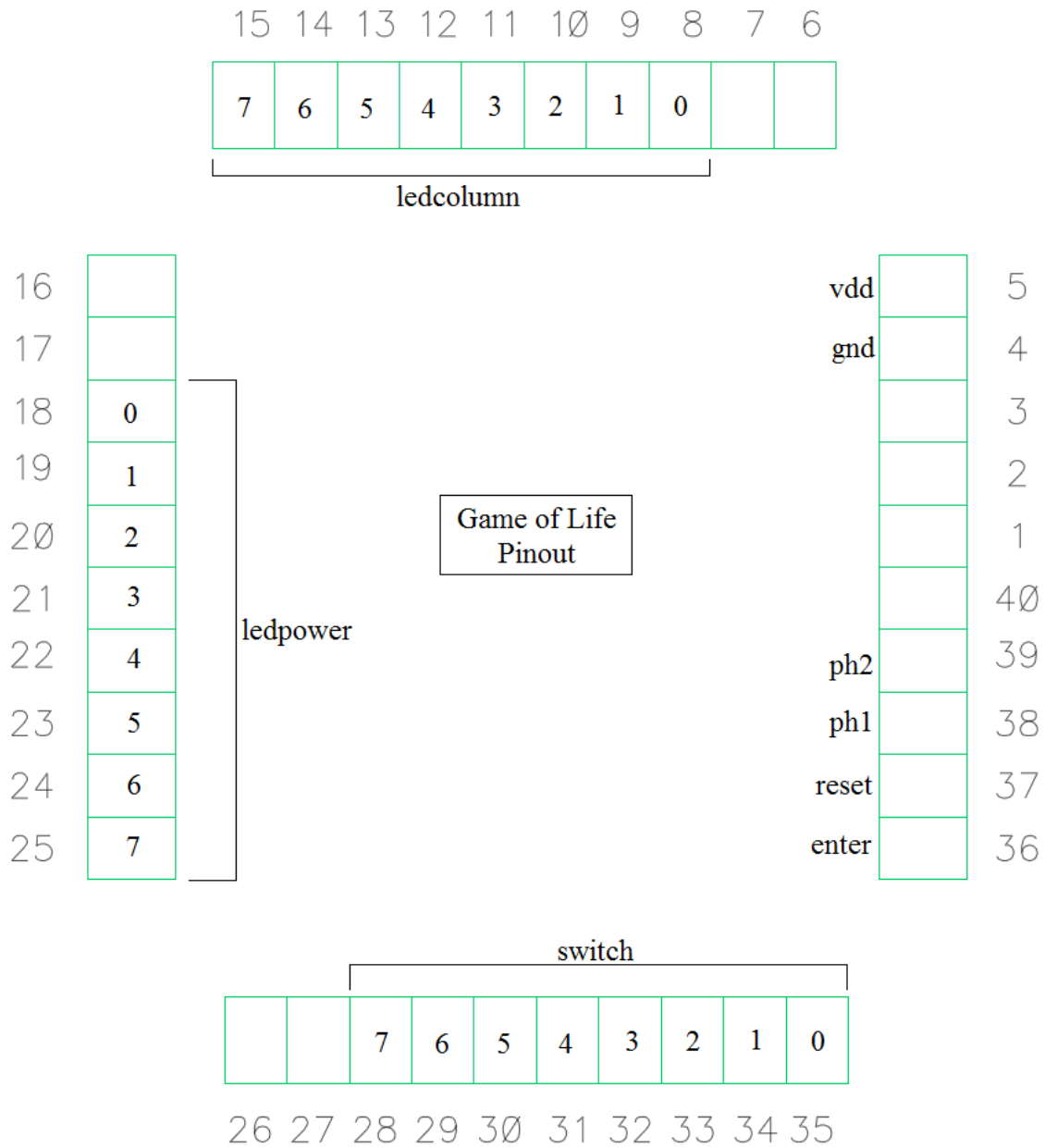


Figure A1.3. The pinout for the Game of Life cell. The number in the pins represents the bit of the signal.

Appendix 2:

File Locations

A2: File Locations

File	Location on Chips (chips.eng.hmc.edu)
Verilog Code	/home/ncard/gameoflife/gameoflife.v
Test Fixture	/home/ncard/gameoflife/verilogtestfixture.v
Test Vectors	/home/ncard/gameoflife/Testmatrixcompilation.txt
Synthesis Results	/home/ncard/gameoflife/gameoflife_syn.v
Cadence Libraries:	/home/ncard/IC_CAD/cadence/
project2_nc (contains custom blocks)	/home/ncard/IC_CAD/cadence/project2_nc/
gameoflife (contains chip and synthesized blocks)	/home/ncard/IC_CAD/cadence/gameoflife/
CIF	/home/ncard/gameoflife/chip.cif
PDF Chip Plot	/home/ncard/gameoflife/chip.pdf
PDF Copy of This Report	/home/ncard/gameoflife/report.pdf

Appendix 3:

Verilog Code

```
1      `timescale 1ns / 1ps
2      ////////////////////////////////////////////////////////////////////
3      // Company: Harvey Mudd College
4      // Engineer: Narayan Propato
5      // Create Date:    16:47:42 03/21/2010
6      // Design Name: Conway's Game of Life
7      // Module Name:    gameoflife
8      // Project Name: Conway's Game of Life
9      // Description: This is the Verilog module that will interface with the 64-bit
10     // memory module to make up the core of the chip. The module takes in the user
11     // inputs reset, enter, and switch and outputs ledpower and ledcolumn off the
12     // chip. It interfaces with the memory via bitlineread, bitlinewrite, wordline,
13     // writeen and readen. Note that core and the memory instance within it are only
14     // used for behavioral simulation. The actual chip only uses the gameoflife
15     // module and a custom-made memory. Please note that the modules flop, flopen,
16     // flopenr, latch, mux2, and mux3 were written by Professor Harris.
17     ////////////////////////////////////////////////////////////////////
18
19     // The core module is made up of the synthesizable module gameoflife and the
20     // non-synthesizable module memory. The latter is only used for running
21     // behavior simulations on the Verilog.
22     module core(input ph1,ph2,
23                 input reset,
24                 input enter,
25                 input [7:0] switch,
26                 output [7:0] ledpower,
27                 output [7:0] ledcolumn);
28
29         wire [7:0] bitlineread,bitlinewrite;
30         wire readen,writeen;
31         wire [7:0] wordline;
32
33         gameoflife gameoflifel(ph1,ph2,reset,enter,switch,bitlineread,ledpower,
34                               ledcolumn,writeen,readen,wordline,bitlinewrite);
35         memory memoryl(ph1, ph2, reset, writeen,readen, wordline, bitlinewrite,
36                       bitlineread);
37     endmodule
38
39     // The gameoflife module is the synthesizable module that will be used in the
40     // final design.
41     module gameoflife(input ph1,ph2,
42                      input reset,
43                      input enter,
44                      input [7:0] switch,
45                      input [7:0] bitlineread,
46                      output [7:0] ledpower,
47                      output [7:0] ledcolumn,
48                      output writeen,
49                      output readen,
50                      output [7:0] wordline,
51                      output [7:0] bitlinewrite);
52
53         wire [7:0] row2;
54         wire finalrowpipe;
55         wire leden;
56         wire [7:0] column;
57         wire zerorow;
58         wire threebitshift;
59         wire newbiten;
60         wire [2:0] threebits;
61         wire cellbit;
```

```

62     wire [7:0] eightbits;
63     wire newcellvalue;
64     wire [7:0] nledpower;
65     wire [7:0] nledcolumn;
66
67     flopenr #8 ledpowerreg(ph1,ph2,reset,leden,nledpower,ledpower);
68     flopenr #8 ledcolumnreg(ph1,ph2,reset,leden,nledcolumn,ledcolumn);
69
70     controller controller1(ph1,ph2,reset,enter,switch,bitlineread,row2,
71                             finalrowpipe,leden,nledpower,nledcolumn,
72                             writeen,readen,wordline,bitlinewrite,
73                             column,zerorow,threebitshift,newbiten);
74     bitselector bitselector1(column,zerorow,bitlineread,threebits);
75     holdmem holdmem1(ph1,ph2,reset,threebitshift,threebits,cellbit,eightbits);
76     outputlogic outputlogic1(cellbit,eightbits,newcellvalue);
77     tempmem tempmem1(ph1,ph2,reset,newbiten,finalrowpipe,newcellvalue,row2);
78 endmodule
79
80 // The controller is comprised of a finite state machine that handles user
81 // input, writes to and reads from memory, matrix iteration calculation, and
82 // matrix output (to an LED display). The controller first writes 8'b00000000
83 // to each address in the memory, resetting it. It then writes the values in
84 // switch to a row in memory each time the user presses enter. The controller
85 // outputs the matrix at all times, so the user is able to see the rows he or
86 // she has inputted throughout the input process. After the user presses the
87 // enter button for the ninth time, the controller will calculate the new matrix
88 // iteration and display it. It will continue doing this until the reset button
89 // is pressed, at which point the memory will be reset and user input will be
90 // accepted once again.
91 module controller(input ph1,ph2,
92                  input reset,
93                  input enter,
94                  input [7:0] switch,
95                  input [7:0] bitlineread,
96                  input [7:0] row2,
97                  output finalrowpipe,
98                  output reg leden,
99                  output reg [7:0] nledpower,
100                 output reg [7:0] nledcolumn,
101                 output writeenph2,
102                 output reg readen,
103                 output reg [7:0] wordline,
104                 output [7:0] bitlinewrite,
105                 output reg [7:0] column,
106                 output reg zerorow,
107                 output reg threebitshift,
108                 output newbiten);
109
110     wire en;
111     assign en = 1'b1;
112
113     //enter logic
114     // When the user presses enter, the value is held in a register
115     // until the input is processed.
116     wire enteren;
117     wire enterpipe;
118     reg checkedinput;
119
120     flopenr #1 enterreg(ph1,ph2,reset,enteren,enter,enterpipe);
121     assign enteren = ~enterpipe|checkedinput;
122

```

```

123 // userinputover logic
124 // Once the user sets the initial conditions, each subsequent press
125 // of the enter button will cause the matrix to be updated with a new
126 // iteration.
127 wire uioen;
128 reg userinputover;
129 wire uiopipe;
130
131 flopenr #1 userinputoverreg(ph1,ph2,reset,uioen,userinputover,uiopipe);
132 assign uioen = ~uiopipe;
133
134 // writeen logic
135 // To prevent glitches in the write signal which would corrupt the memory
136 // data, writes are only performed while ph2 is high and all signals are
137 // stable.
138 reg writeen;
139 assign writeenph2 = writeen & ph2;
140
141 // State Register
142 wire [4:0] state;
143 reg [4:0] nextstate;
144
145 flopenr #5 statereg(ph1,ph2,reset,en,nextstate,state);
146
147 wire iden;
148 reg iterationdone;
149 wire idpipe;
150 reg displayloop;
151
152 flopenr #1 iterationdonereg(ph1,ph2,reset,iden,iterationdone,idpipe);
153 assign iden = ~idpipe|displayloop;
154
155 reg nnewbiten;
156
157 flopenr #1 newbitenreg(ph1,ph2,reset,en,nnewbiten,newbiten);
158
159 reg nstorerow;
160 flopenrval #1 storerowreg(ph1,ph2,reset,en,1'b1,nstorerow,storerow);
161
162 reg finalrow;
163 flopenr #1 finalrowreg(ph1,ph2,reset,en,finalrow,finalrowpipe);
164
165 // FSM Next State Logic
166 always@(*)
167     casez (state)
168         5'b00000: nextstate = 5'b00001;
169         5'b????1: if (wordline[0])
170             nextstate = 5'b00010;
171             else
172                 nextstate = 5'b00001;
173         5'b????1?: if (displayloop&enterpipe)
174             if (uiopipe)
175                 nextstate = 5'b01000;
176             else
177                 nextstate = 5'b00100;
178             else
179                 nextstate = 5'b00010;
180         5'b??1??: nextstate = 5'b00010;
181         5'b?1??: if (storerow) nextstate = 5'b10000;
182             else nextstate = 5'b01000;
183         5'b1??: if (finalrow) nextstate = 5'b10000;

```



```
184         else if (idpipe) nextstate = 5'b00010;
185         else nextstate = 5'b01000;
186         default: nextstate = 5'bxxxxx;
187     endcase
188
189     // FSM Output Logic
190     wire [7:0] wordlinecounter;
191     reg [7:0] nwordlinecounter;
192     wire [7:0] columncounter;
193     reg [7:0] ncolumncounter;
194     wire [9:0] rowcounter;
195     reg [9:0] nrowcounter;
196     wire [7:0] rowinput;
197     reg [7:0] nrowinput;
198     reg colcounteren;
199     reg rowcounteren;
200     reg rowinputreset;
201
202     flopenrval #8 wordlinecounterreg(ph1,ph2,reset,en,8'b10000000,
203         nwordlinecounter, wordlinecounter);
204     flopenrval #8 columncounterreg(ph1,ph2,reset,colcounteren,8'b10000000,
205         ncolumncounter, columncounter);
206     flopenrval #10 rowcounterreg(ph1,ph2,reset,rowcounteren,10'b1000000000,
207         nrowcounter, rowcounter);
208
209     reg rowinputen;
210     reg [7:0] ncolumn;
211
212     flopenrval #8 rowinputreg(ph1,ph2,rowinputreset,rowinputen,8'b10000000,
213         nrowinput, rowinput);
214
215     reg [3:0] ncounter1;
216     wire [3:0] counter1;
217
218     flopenr #4 counter1reg(ph1,ph2,reset,en,ncounter1,counter1);
219
220     reg threerowsreset;
221     reg threerowsen;
222     wire [2:0] threerows;
223     reg [2:0] nthreerows;
224
225     flopenrval #3 threerowsreg(ph1,ph2,threerowsreset,threerowsen,3'b100,
226         nthreerows, threerows);
227
228     reg [7:0] bitlinez;
229     reg writenewrow;
230
231     always@(*)
232     begin
233         writeen = 0;
234         readen = 0;
235         leden = 0;
236         threebitshift = 0;
237         nnewbiten = 0;
238         bitlinez = 0;
239         wordline = 0;
240         nledpower = 0;
241         nledcolumn = 0;
242         displayloop = 0;
243         checkedinput = 0;
244         nwordlinecounter = wordlinecounter;
```

```
245     ncolumncounter = columncounter;
246     nrowcounter = rowcounter;
247     nrowinput = rowinput;
248     nthreerows = threerows;
249     ncounter1 = counter1;
250     userinputover = 0;
251     rowinputten = 0;
252     colcounteren = 0;
253     rowcounteren = 0;
254     zerorow = 0;
255     threerowsen = 0;
256     iterationdone = 0;
257     writenewrow = 0;
258     nstorerow = 0;
259     rowinputreset = 0;
260     finalrow = 0;
261     threerowsreset = 0;
262
263     case (state)
264     // Reset state
265     5'b00000: begin rowinputreset = 1;
266                 threerowsreset = 1;
267                 nwordlinecounter = wordlinecounter; end
268     // Memory reset state
269     5'b00001: begin nwordlinecounter = {wordlinecounter[0],
270                                         wordlinecounter[7:1]};
271                 wordline = wordlinecounter;
272                 writeen = 1'b1;
273                 bitlinez = 8'b00000000; end
274
275     // Display state
276     5'b00010: begin
277                 ncounter1 = counter1 + 1;
278                 if (counter1 == 4'b1111)
279                 begin
280                     nwordlinecounter = {wordlinecounter[0],
281                                         wordlinecounter[7:1]};
282                     if (wordlinecounter[0])
283                     begin
284                         displayloop = 1;
285                     end
286                 end
287                 else
288                 begin
289                     wordline = wordlinecounter;
290                     readen = 1'b1;
291                     leden = 1'b1;
292                     nledcolumn = bitlineread;
293                     nledpower = wordlinecounter;
294                 end
295             end
296
297     // Write user input to memory state
298     5'b00100: begin
299                 if (rowinput[0]) userinputover = 1;
300                 checkedinput = 1;
301                 nrowinput = {rowinput[0],rowinput[7:1]};
302                 wordline = rowinput;
303                 writeen = 1'b1;
304                 rowinputten = 1'b1;
305                 bitlinez = switch;
```

```

306             end
307
308         // Calculate new matrix state
309         5'b01000: begin
310             if (rowinput[7]) checkedinput = 1;
311             threerowsen = 1;
312             nthreerows = {threerows[0],threerows[2:1]};
313             column = columncounter;
314             threebitshift = 1;
315             readen = 1;
316             if ((rowinput[7]&threerows[2])|(rowinput[0]&threerows[0]))
317                 zerorow = 1;
318             if (threerows[0])
319                 begin
320                     nnewbiten = 1;
321                     colcounteren = 1;
322                     ncolumncounter = {columncounter[0],
323                                         columncounter[7:1]};
324                     if (columncounter[0])
325                         begin
326                             if (rowinput[0]) iterationdone = 1;
327                             if (~rowinput[7]) nstorerow = 1;
328                             else
329                                 begin
330                                     rowinputen = 1;
331                                     nrowinput = {rowinput[0],rowinput[7:1]};
332                                 end
333                             end
334                         end
335                     casez (threerows)
336                         3'b1??: wordline = {rowinput[6:0],rowinput[7]};
337                         3'b?1?: wordline = rowinput;
338                         3'b??1: wordline = {rowinput[0],rowinput[7:1]};
339                         default: wordline = 3'bxxx;
340                     endcase
341                 end
342             5'b10000: begin
343                 threerowsreset = 1;
344                 writeen = 1;
345                 wordline = {rowinput[6:0],rowinput[7]};
346                 writenewrow = 1;
347                 if (rowinput[0]) finalrow = 1;
348                 if (~rowinput[7])
349                     begin
350                         rowinputen = 1;
351                         nrowinput = {rowinput[0],rowinput[7:1]};
352                     end
353                 else if (rowinput[6]&idpipe) rowinputreset = 1;
354             end
355         endcase
356     end
357
358     assign bitlinewrite = writenewrow ? row2 : bitlinez;
359 endmodule
360
361 // Temporary module used for behavioral simulation purposes. Since the memory
362 // will ultimately be custom-made and not synthesized, this module can be ignored
363 // in the final design.
364 module memory(input ph1, ph2,
365              input reset,
366              input writeen,readen,

```

```

367         input [7:0] wordline,
368         input [7:0] bitlinewritez,
369         output [7:0] bitlineread);
370
371 wire [7:0] row1,row2,row3,row4,row5,row6,row7,row8;
372 reg [7:0] bitlinereadz;
373 wire [7:0] bitlinewrite;
374
375 assign bitlinewrite = writeen ? bitlinewritez : 8'bzzzzzzzz;
376
377 flopenrval #8 row1reg1(ph1,ph2,reset,wordline[7]&writeen,
378                       8'b10000000,bitlinewrite,row1);
379 flopenrval #8 row2reg1(ph1,ph2,reset,wordline[6]&writeen,
380                       8'b01000000,bitlinewrite,row2);
381 flopenrval #8 row3reg1(ph1,ph2,reset,wordline[5]&writeen,
382                       8'b00100000,bitlinewrite,row3);
383 flopenrval #8 row4reg1(ph1,ph2,reset,wordline[4]&writeen,
384                       8'b00010000,bitlinewrite,row4);
385 flopenrval #8 row5reg1(ph1,ph2,reset,wordline[3]&writeen,
386                       8'b00001000,bitlinewrite,row5);
387 flopenrval #8 row6reg1(ph1,ph2,reset,wordline[2]&writeen,
388                       8'b00000100,bitlinewrite,row6);
389 flopenrval #8 row7reg1(ph1,ph2,reset,wordline[1]&writeen,
390                       8'b00000010,bitlinewrite,row7);
391 flopenrval #8 row8reg1(ph1,ph2,reset,wordline[0]&writeen,
392                       8'b00000001,bitlinewrite,row8);
393
394 always@(*)
395     casez (wordline)
396         8'b1??????? : bitlinereadz = row1;
397         8'b?1??????? : bitlinereadz = row2;
398         8'b??1??????? : bitlinereadz = row3;
399         8'b???1??????? : bitlinereadz = row4;
400         8'b????1????? : bitlinereadz = row5;
401         8'b?????1??? : bitlinereadz = row6;
402         8'b???????1? : bitlinereadz = row7;
403         8'b????????1 : bitlinereadz = row8;
404         default: bitlinereadz = 8'bxxxxxxxx;
405     endcase
406
407     assign bitlineread = readen ? bitlinereadz : 8'bzzzzzzzz;
408 endmodule
409
410 // The bitselector module determines which set of three bits should be
411 // pulled from the row that was read from memory. The correct three bits
412 // are the bit currently being looked at, as well as the two to its left
413 // and right. If the current bit is located on the left or right edge, the
414 // first or third bit are set to zero, respectively. The zerorow input
415 // indicates that the row being looked at is outside the indexing of the
416 // matrix. In these case all three bits are set to zero.
417 module bitselector(input [7:0] en,
418                  input zerorow,
419                  input [7:0] d,
420                  output [2:0] q);
421
422     reg [2:0] m;
423
424     always@(*)
425         casez (en)
426             8'b1??????? : m = {1'b0,d[7:6]};
427             8'b?1??????? : m = d[7:5];

```

```

428         8'b???1?????: m = d[6:4];
429         8'b???1?????: m = d[5:3];
430         8'b????1????: m = d[4:2];
431         8'b?????1????: m = d[3:1];
432         8'b???????1?: m = d[2:0];
433         8'b???????1?: m = {d[1:0],1'b0};
434         default: m = 3'bxxx;
435     endcase
436
437     assign q = m&{~zerorow,~zerorow,~zerorow};
438 endmodule
439
440 // The holdmem module holds the sets of three bits outputted by the
441 // bitselector module until all nine bits are available, so that the
442 // correct input is provided to the output logic module.
443 module holdmem(input ph1,ph2,
444               input reset,
445               input en,
446               input [2:0] row,
447               output cellbit,
448               output [7:0] eightbits);
449     wire [2:0] row1, row2, row3;
450
451     flopenr #3 reg1(ph1,ph2,reset,en,row,row1);
452     flopenr #3 reg2(ph1,ph2,reset,en,row1,row2);
453     flopenr #3 reg3(ph1,ph2,reset,en,row2,row3);
454
455     assign cellbit = row2[1];
456     assign eightbits = {row1,row2[2],row2[0],row3};
457 endmodule
458
459 // The outputlogic module takes in the bit whose new value is being
460 // calculated, as well as the surrounding eight bits, and calculates
461 // the new cell value.
462 module outputlogic(input cellbit,
463                   input [7:0] eightbits,
464                   output newcellvalue);
465
466     wire [3:0] sum;
467
468     assign sum = eightbits[7]+eightbits[6]+eightbits[5]+eightbits[4]+
469                eightbits[3]+eightbits[2]+eightbits[1]+eightbits[0];
470     assign newcellvalue = ~(sum[3]|sum[2])&sum[1]&(~sum[0]&cellbit|sum[0]);
471 endmodule
472
473 // The tempmem module holds the new cell values outputted by outputlogic
474 // until the old values are no longer needed.
475 module tempmem(input ph1,ph2,
476               input reset,
477               input newbiten,
478               input finalrow,
479               input q,
480               output [7:0] row2);
481
482     wire [15:0] tworows;
483
484     flopenr #16 reg2(ph1,ph2,reset,newbiten,{tworows[14:0],q},tworows);
485
486     assign row2 = finalrow? tworows[7:0]: tworows[15:8];
487 endmodule
488

```

```
489 // The tristate module is only used in the memory module.
490 module tristate(input en,
491               input [2:0] d,
492               output [2:0] q);
493     assign q = en ? d : 3'bzzz;
494 endmodule
495
496 module flop #(parameter WIDTH = 8)
497     (input ph1, ph2,
498      input [WIDTH-1:0] d,
499      output [WIDTH-1:0] q);
500
501     wire [WIDTH-1:0] mid;
502
503     latch #(WIDTH) master(ph2, d, mid);
504     latch #(WIDTH) slave(ph1, mid, q);
505 endmodule
506
507 module flopen #(parameter WIDTH = 8)
508     (input ph1, ph2, en,
509      input [WIDTH-1:0] d,
510      output [WIDTH-1:0] q);
511
512     wire [WIDTH-1:0] d2;
513
514     mux2 #(WIDTH) enmux(q, d, en, d2);
515     flop #(WIDTH) f(ph1, ph2, d2, q);
516 endmodule
517
518 module flopenr #(parameter WIDTH = 8)
519     (input ph1, ph2, reset, en,
520      input [WIDTH-1:0] d,
521      output [WIDTH-1:0] q);
522
523     wire [WIDTH-1:0] d2, resetval;
524
525     assign resetval = 0;
526
527     mux3 #(WIDTH) enrmux(q, d, resetval, {reset, en}, d2);
528     flop #(WIDTH) f(ph1, ph2, d2, q);
529 endmodule
530
531 module flopenrval #(parameter WIDTH = 8)
532     (input ph1, ph2, reset, en,
533      input [WIDTH-1:0] resetval,
534      input [WIDTH-1:0] d,
535      output [WIDTH-1:0] q);
536
537     wire [WIDTH-1:0] d2;
538
539     mux3 #(WIDTH) enrmux(q, d, resetval, {reset, en}, d2);
540     flop #(WIDTH) f(ph1, ph2, d2, q);
541 endmodule
542
543 module latch #(parameter WIDTH = 8)
544     (input ph,
545      input [WIDTH-1:0] d,
546      output reg [WIDTH-1:0] q);
547
548     always@(*)
549         if (ph) q <= d;
```

```
550     endmodule
551
552     module mux2 #(parameter WIDTH = 8)
553         (input [WIDTH-1:0] d0, d1,
554          input s,
555          output [WIDTH-1:0] y);
556
557         assign y = s ? d1 : d0;
558     endmodule
559
560     module mux3 #(parameter WIDTH = 8)
561         (input [WIDTH-1:0] d0, d1, d2,
562          input [1:0] s,
563          output reg [WIDTH-1:0] y);
564
565         always@(*)
566             casez (s)
567                 2'b00: y = d0;
568                 2'b01: y = d1;
569                 2'b1?: y = d2;
570             endcase
571     endmodule
572
```

A3.2: Fixed Netlist for Latch

```
// Library - muddlib10, Cell - latch_c_1x, View - cmos_sch
// LAST TIME SAVED: Feb  4 13:25:38 2010
// NETLIST TIME: Apr  3 19:32:53 2010
`timescale 1ns / 100ps

module latch_c_1x ( q, d, ph );
output  q;

input  d, ph;
trireg  masterb;

//ADDED VARIABLE
reg rst;

specify
    specparam CDS_LIBNAME = "muddlib10";
    specparam CDS_CELLNAME = "latch_c_1x";
    specparam CDS_VIEWNAME = "cmos_sch";
endspecify

//THESE LINES ARE CHANGED FROM ORIGINAL LATCH
initial begin
    rst = 1; #5; rst = 0;
end

nmos jamb(masterb, cds_globals.gnd_, rst);
//END CHANGED SECTION

rnmos #(0.1)  M18( net030, masterb, phb);
rpmos #(0.1)  M15( net054, masterb, phbuf);
`switch default
nmos #(0.1)  (* const real width = 2.100, length = 0.600; *) M34( phb,
    cds_globals.gnd_, ph);
`switch default
nmos #(0.1)  (* const real width = 2.100, length = 0.600; *) M26( q,
    cds_globals.gnd_, masterb);
`switch default
nmos #(0.1)  (* const real width = 2.100, length = 0.600; *) M35(
    phbuf, cds_globals.gnd_, phb);
`switch default
nmos #(0.1)  (* const real width = 1.200, length = 0.600; *) M14(
    cds_globals.gnd_, net030, master);
`switch default
nmos #(0.1)  (* const real width = 1.800, length = 0.600; *) M32(
    masterinb, cds_globals.gnd_, d);
`switch default
nmos #(0.1)  (* const real width = 1.800, length = 0.600; *) M2(
    masterb, masterinb, phbuf);
`switch default
nmos #(0.1)  (* const real width = 1.800, length = 0.600; *) M1(
    master, cds_globals.gnd_, masterb);
`switch default
```



```

pmos #(0.1)    (* const real width = 3.000, length = 0.600; *) M30(
    masterinb, cds_globals.vdd_, d);
`switch default
pmos #(0.1)    (* const real width = 3.000, length = 0.600; *) M27( q,
    cds_globals.vdd_, masterb);
`switch default
pmos #(0.1)    (* const real width = 3.000, length = 0.600; *) M33( phb,
    cds_globals.vdd_, ph);
`switch default
pmos #(0.1)    (* const real width = 3.000, length = 0.600; *) M36(
    phbuf, cds_globals.vdd_, phb);
`switch default
pmos #(0.1)    (* const real width = 1.200, length = 0.600; *) M16(
    cds_globals.vdd_, net054, master);
`switch default
pmos #(0.1)    (* const real width = 1.800, length = 0.600; *) M3(
    masterb, masterinb, phb);
`switch default
pmos #(0.1)    (* const real width = 2.700, length = 0.600; *) M0(
    master, cds_globals.vdd_, masterb);

endmodule

```

Appendix 4:

Testing Materials

```
1      `timescale 1ns / 1ps
2
3      ////////////////////////////////////////////////////////////////////
4      // Company: Harvey Mudd College
5      // Engineer: Narayan Propato
6      // Create Date: 19:43:51 03/22/2010
7      // Design Name: gameoflife
8      // Module Name: C:/NP/Project 2/gameoflife/verilogtestfixture.v
9      // Project Name: gameoflife
10     // Description: This test fixture simulates user input comprised of setting the
11     // switch values to certain numbers and then pressing enter to input them. These
12     // values are obtained from the testmatrix.txt file. After three iterations, The
13     // values outputted by the chip to the LED matrix are then checked against the
14     // expected ones, which are also located in the testmatrix.txt file.
15     ////////////////////////////////////////////////////////////////////
16
17     module verilogtestfixture;
18
19         // Inputs
20         reg ph1,ph2;
21         reg reset;
22         reg enter;
23         reg [7:0] switch;
24
25         // Outputs
26         wire [7:0] ledpower;
27         wire [7:0] ledcolumn;
28
29         reg [7:0] testmatrix [16:0], currentrow;
30         reg [5:0] vectornum, errors;
31         reg [11:0] cyclea, cycleb;
32         reg ledoutputa,ledoutputb;
33
34         // Instantiate the Unit Under Test (UUT)
35         core dut (
36             .ph1(ph1),
37             .ph2(ph2),
38             .reset(reset),
39             .enter(enter),
40             .switch(switch),
41             .ledpower(ledpower),
42             .ledcolumn(ledcolumn));
43
44         // Initialize test
45         initial
46             begin
47                 $readmemb("testmatrix.txt", testmatrix);
48                 vectornum = 0; errors = 0;
49                 ph1 = 0;
50                 ph2 = 0;
51                 enter = 0;
52                 switch = 0;
53                 cyclea = 0;
54                 cycleb = 0;
55                 reset <= 1; # 11; reset <= 0;
56
57                 #36; enter <= 1; switch <= testmatrix[vectornum];
58                 vectornum = vectornum + 1; #12; enter <= 0;
59                 #1500; enter <= 1; switch <= testmatrix[vectornum];
60                 vectornum = vectornum + 1; #12; enter <= 0;
61                 #1500; enter <= 1; switch <= testmatrix[vectornum];
```

```
62     vectornum = vectornum + 1; #12; enter <= 0;
63     #1500; enter <= 1; switch <= testmatrix[vectornum];
64     vectornum = vectornum + 1; #12; enter <= 0;
65     #1500; enter <= 1; switch <= testmatrix[vectornum];
66     vectornum = vectornum + 1; #12; enter <= 0;
67     #1500; enter <= 1; switch <= testmatrix[vectornum];
68     vectornum = vectornum + 1; #12; enter <= 0;
69     #1500; enter <= 1; switch <= testmatrix[vectornum];
70     vectornum = vectornum + 1; #12; enter <= 0;
71     #1500; enter <= 1; switch <= testmatrix[vectornum];
72     vectornum = vectornum + 1; #12; enter <= 0;
73
74     #1500; enter <=1; switch <= 8'h00; #12; enter <=0;
75     #3000; enter <=1; switch <= 8'h00; #12; enter <=0;
76     #3000; enter <=1; switch <= 8'h00; #12; enter <=0;
77     end
78
79
80     // Generate clock to sequence tests
81     always
82     begin
83         ph1 <= 0; ph2 <= 0; #1;
84         ph1 <= 1; cyclea <= cyclea + 1; # 4;
85         ph1 <= 0; #1;
86         ph2 <= 1; cycleb <= cycleb + 1; # 4;
87     end
88
89     // ledoputa and ledoutputb are used to identify when a
90     // new row should be checked
91     always @(posedge ph1)
92         case (cyclea)
93             12'h886: ledoutputa = 1;
94             12'h896: ledoutputa = 1;
95             12'h8a6: ledoutputa = 1;
96             12'h8b6: ledoutputa = 1;
97             12'h8c6: ledoutputa = 1;
98             12'h8d6: ledoutputa = 1;
99             12'h8e6: ledoutputa = 1;
100            12'h8f6: ledoutputa = 1;
101            12'h906: ledoutputa = 1;
102            default: ledoutputa = 0;
103        endcase
104
105     always @(posedge ph2)
106         case (cycleb)
107             12'h886: ledoutputb = 1;
108             12'h896: ledoutputb = 1;
109             12'h8a6: ledoutputb = 1;
110             12'h8b6: ledoutputb = 1;
111             12'h8c6: ledoutputb = 1;
112             12'h8d6: ledoutputb = 1;
113             12'h8e6: ledoutputb = 1;
114             12'h8f6: ledoutputb = 1;
115             12'h906: ledoutputb = 1;
116             default: ledoutputb = 0;
117         endcase
118
119     always @(posedge ledoutputa) begin
120         currentrow = testmatrix[vectornum];
121     end
122
```

```
123 // check if test was successful and apply next one
124 always @(posedge ledoutputb) begin
125     if (currentrow === 8'bxxxxxxxx) begin
126         $display("Completed the test with %d errors.",
127                 errors);
128         $stop;
129     end
130     else if ((ledcolumn !== currentrow)) begin
131         $display("Error: output mismatches as %h (%h expected)",
132                 ledcolumn, currentrow);
133         errors = errors + 1;
134     end
135     vectornum = vectornum + 1;
136 end
137 endmodule
138
```


A4.2: Test Vectors

00000000	11111111	10011101
00000000	00000000	00110000
00000000	11111111	11011111
00000000	00000000	11011011
00000000	11111111	00111100
00000000	00000000	10110110
00000000	11111111	11111111
00000000	00000000	11001001
00000000	00011000	00100000
00000000	00000000	11000000
00000000	00011000	00000011
00000000	00000000	00100100
00000000	00011000	11000100
00000000	00111100	00000100
00000000	00000000	00000011
00000000	00000000	00000000
xxxxxxxx	xxxxxxxx	xxxxxxxx
11111111	11111001	
11111111	10001001	
11111111	11011001	
11111111	11110000	
11111111	01111101	
11111111	00000110	
11111111	01111110	
11111111	10100110	
00000000	01011010	
00000000	01000001	
00000000	00011001	
00000000	00001010	
00000000	00001000	
00000000	01010111	
00000000	10000011	
00000000	01010000	
xxxxxxxx	xxxxxxxx	


Appendix 5:

Schematics and Layout


A5.1.1: 12t_cell Schematic

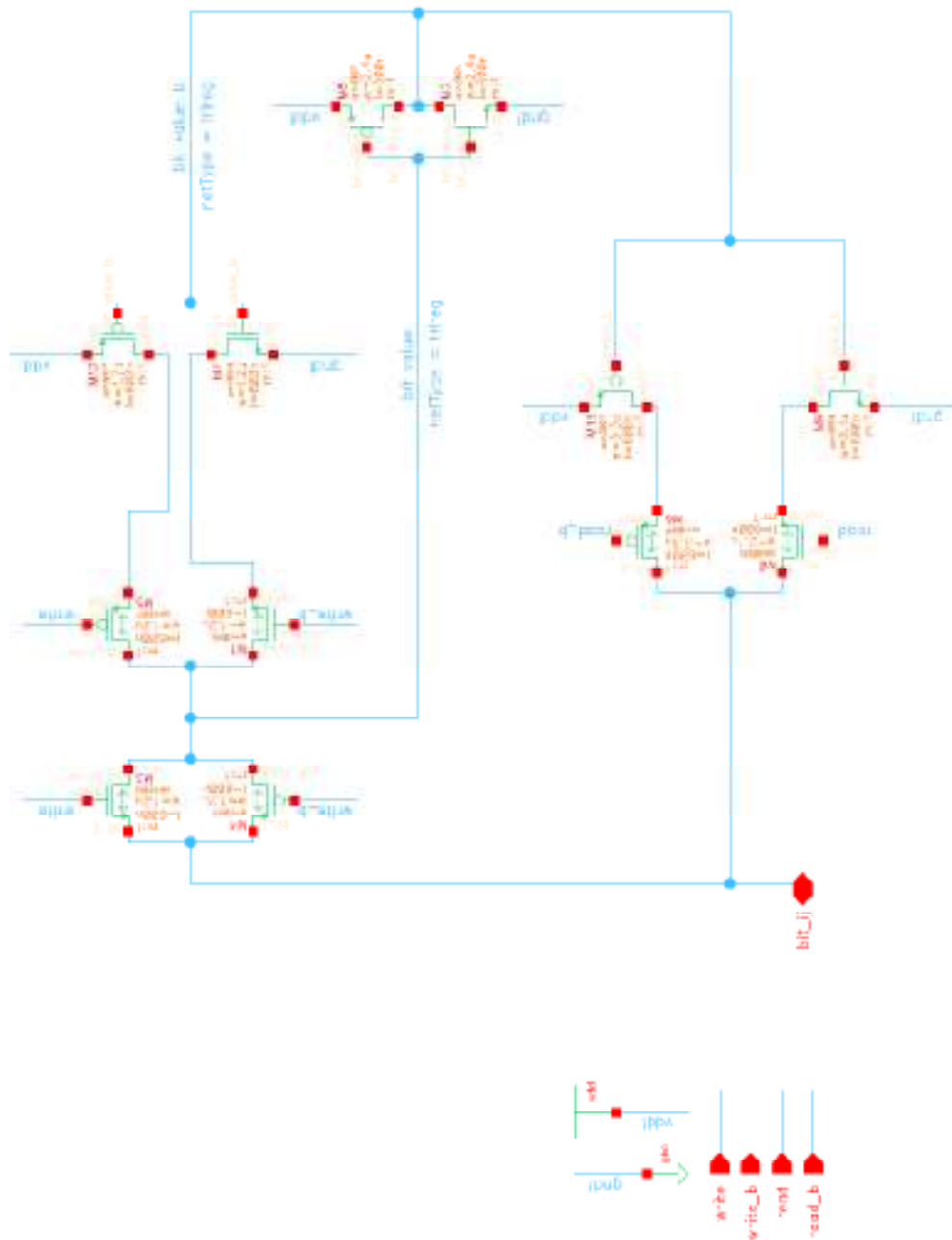


A5.1.1: 12t_cell Layout

 

A5.2.1: tri_buf Schematic

 


A5.2.2: tri_buf Layout


 


A5.3.1: wordline_bitcell and wordline_bitcell_odd Schematics


Both cells share the same schematic

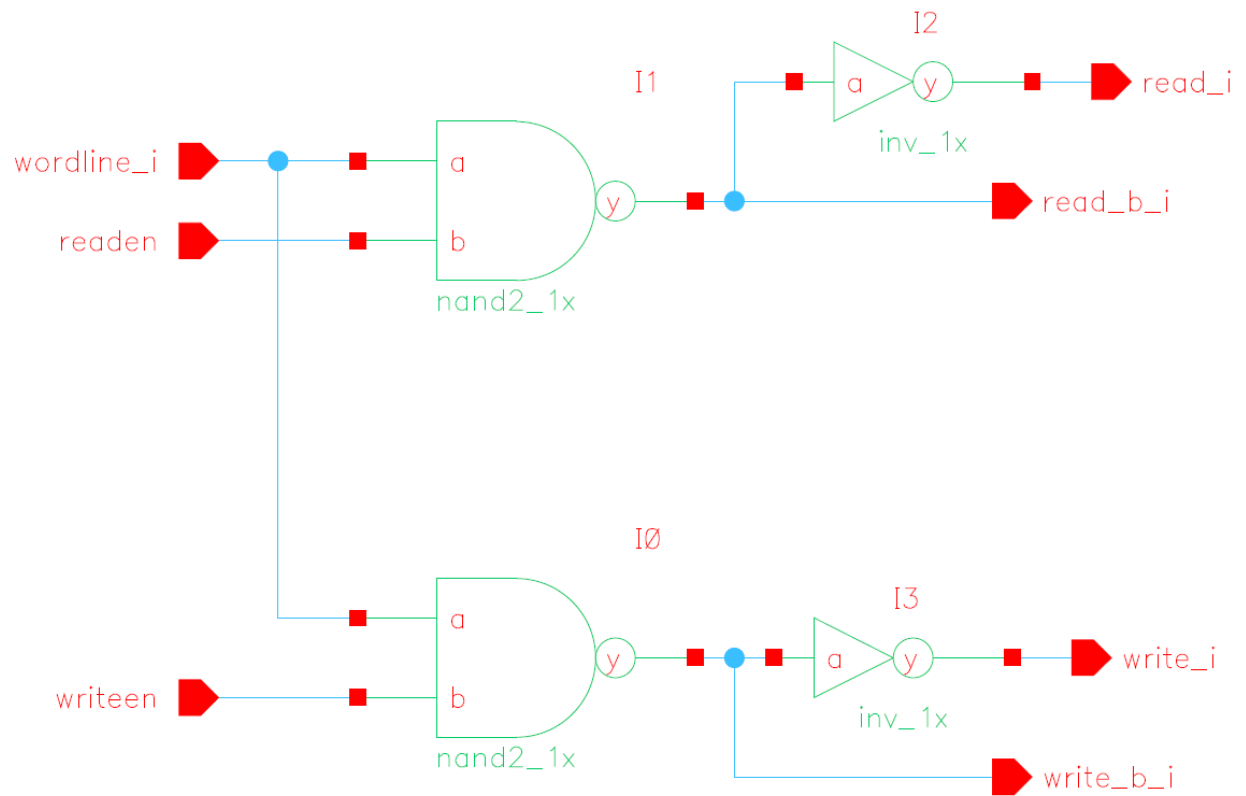

  
A5.3.2: wordline_bitcell (top) and wordline_bitcell_odd (bottom) Layouts




A5.4.1: wordline Schematic

 


A5.4.2: wordline Layout

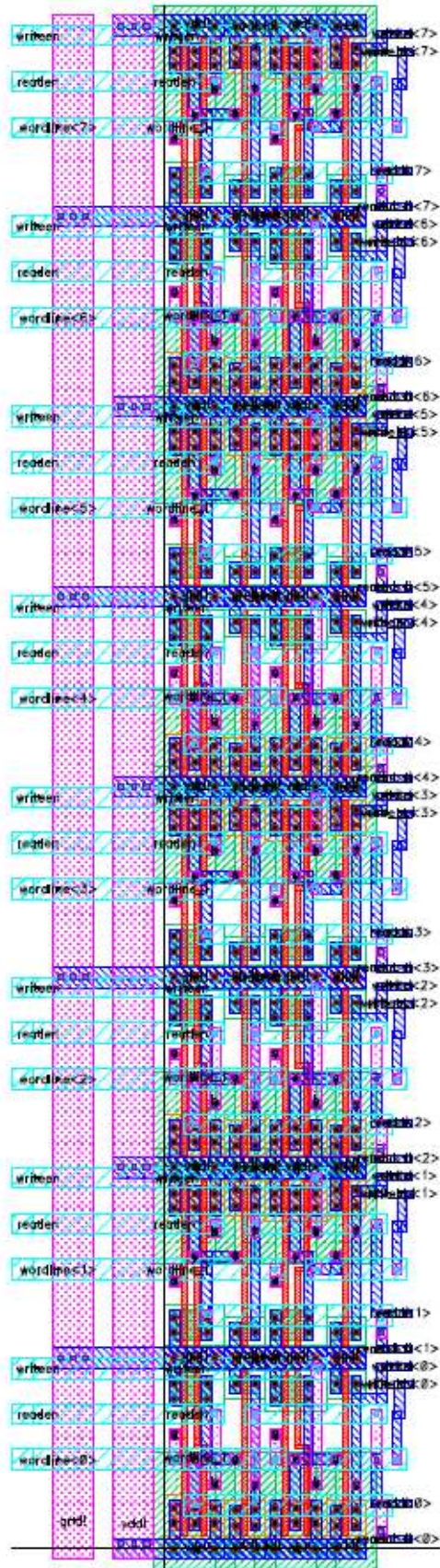

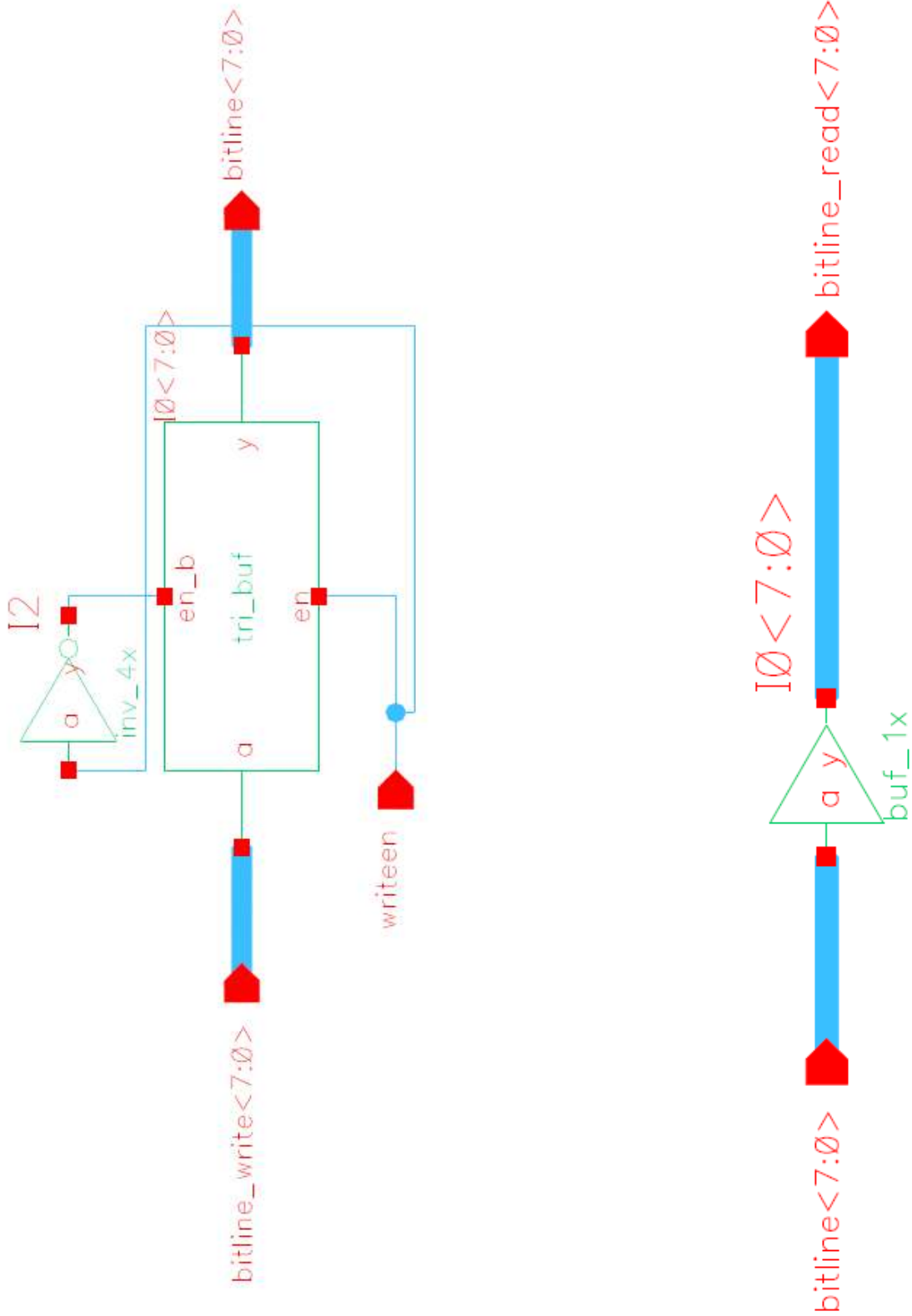
A5.5.1: bitline_write (left) and bitline_read (right) Schematics



 
A5.5.2: bitline_write (left) and bitline_read (right) Layouts




A5.6.1: 8bit_mem Schematic

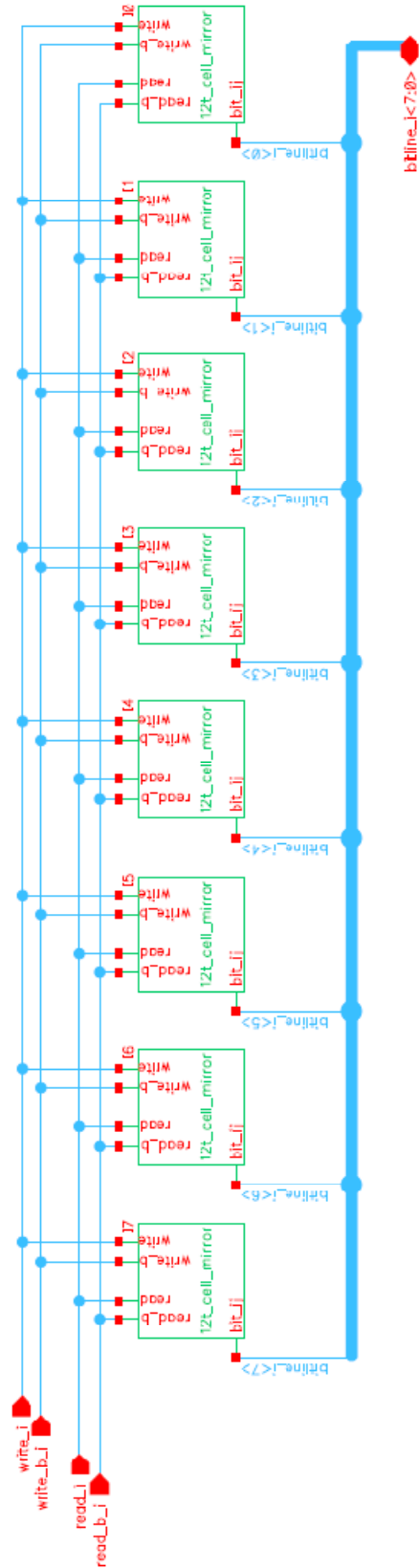

A5.6.2: 8bit_mem Layout

 


A5.7.1: 64bit_mem Schematic

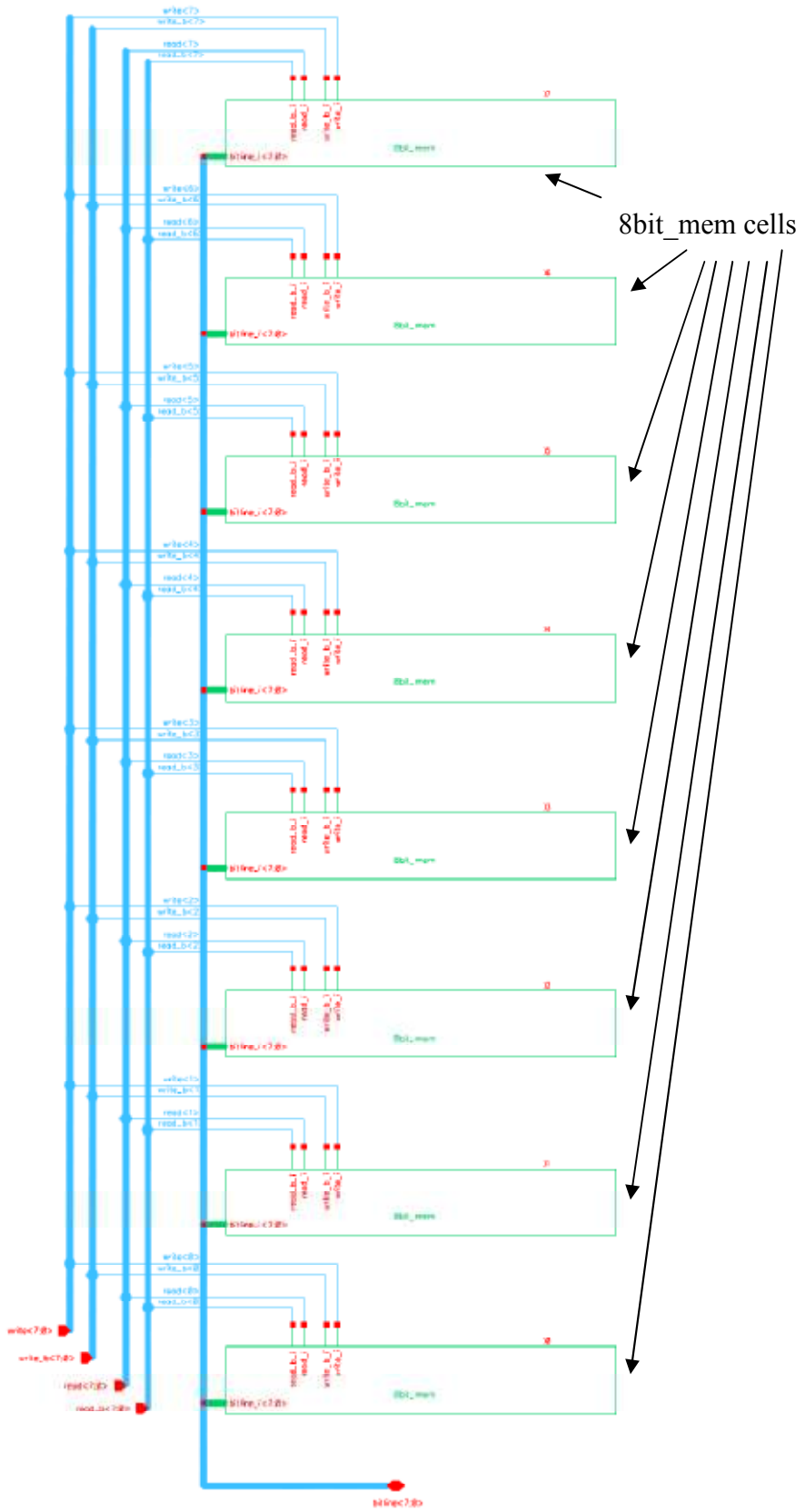


A5.7.2: 64bit_mem Layout




A5.8.1: register Schematic

 


A5.8.2: register Layout

 


A5.9: gameoflife Layout

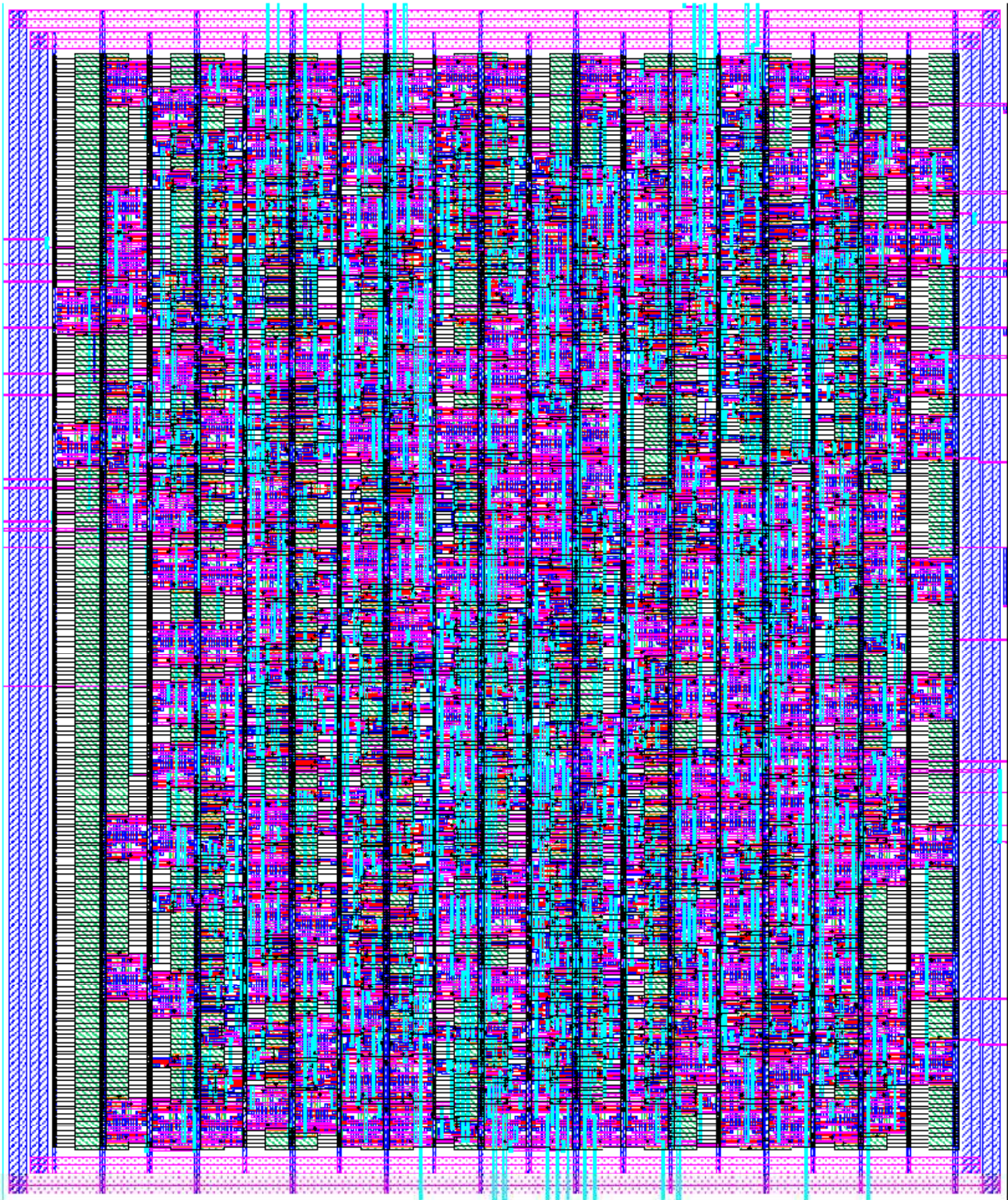

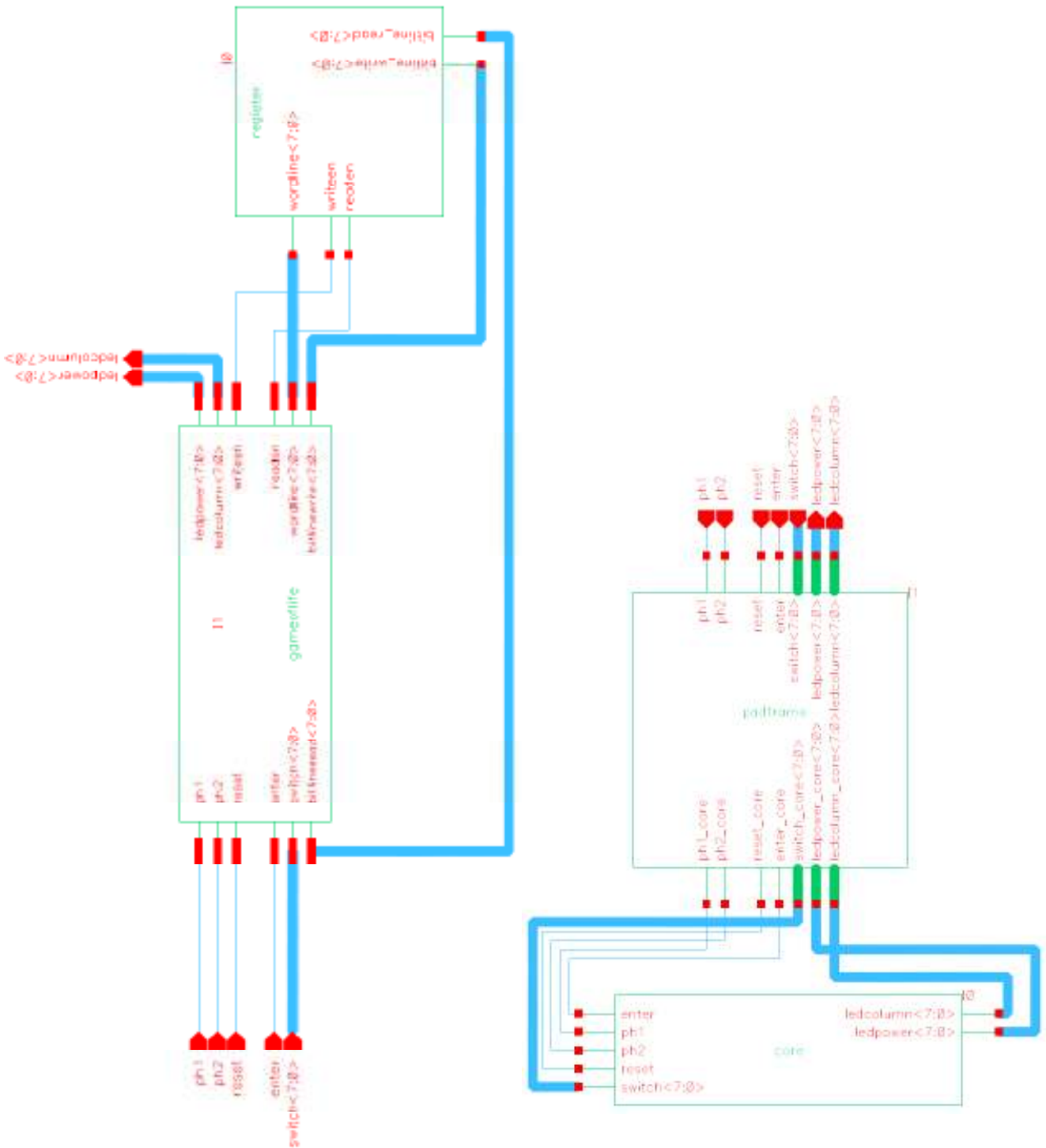A5.10.1: core (left) and chip (right) Schematics



A5.10.2: core Layout

 

A5.10.3: chip Layout

