

# CMOS VLSI Design

## Lab 3: Controller Design and Verification

The controller for your MIPS processor is responsible for generating the signals to the datapath to fetch and execute each instruction. It lacks the regular structure of the datapath. In the first section of the lab, you will design the ALU decoder control logic by hand. You will discover how this becomes tedious and error-prone even for small designs. For larger blocks, especially designs that might require bug fixes late in the design process, hand place and route becomes exceedingly onerous. Therefore, you will use Synopsys's Design Compiler to synthesize the combinational logic for the control FSM and Cadence's SOC Encounter to automatically place and route the controller.

### I. ALUDec Logic

The `aludec` logic is responsible for decoding a 2-bit `ALUOp` signal and a 6-bit `funct` field of the instruction to produce three multiplexer control lines for the ALU. Two of the signals select which type of ALU operation is performed and the third determines if input B is inverted.

The function of the `aludec` logic is defined in Chapter 1 of *CMOS VLSI Design*. The Verilog code in Figure 1 is an equivalent description of the logic. Note that the main controller will never produce an `aluop` of 11, so that case need not be considered. The processor only handles the five R-type instructions listed, so you can treat the result of other `funct` codes as don't cares and optimize your logic accordingly.

```
typedef enum logic [5:0] {ADD = 6'b100000,
                          SUB = 6'b100010,
                          AND = 6'b100100,
                          OR  = 6'b100101,
                          SLT = 6'b101010} functcode;

module aludec(input  logic [1:0] aluop,
             input  logic [5:0] funct,
             output logic [2:0] alucontrol);

    always_comb
    case (aluop)
        2'b00: alucontrol = 3'b010; // add for lb/sb/addi
        2'b01: alucontrol = 3'b110; // subtract (for beq)
        default: case(funct) // R-Type instructions
            ADD: alucontrol = 3'b010;
            SUB: alucontrol = 3'b110;
            AND: alucontrol = 3'b000;
            OR:  alucontrol = 3'b001;
            SLT: alucontrol = 3'b111;
            default: alucontrol = 3'b101; // should never happen
        endcase
    endcase
endmodule
```

Figure 1: System Verilog code for ALUDec module

Create a new library named `controller_xx`. Create an `aludec` schematic in your `controller_xx` library. Using the logic gates from `muddlib11`, design a combinational circuit to compute the `alucontrol[2:0]` signals from `aluop[1:0]` and `funct[5:0]`. Limit yourself to the `inv`, `nand2`, `nand3`, `nor2`, and `nor3` gates so that you gain experience designing with inverting gates. As `funct[5:4]` are always 10 for any instruction under consideration, you may omit them as don't cares. Try to minimize the number of gates required because that will save you time and space in the layout. Remember to name your busses with angle brackets (e.g. `aluop<1:0>`).

You will need to connect individual bits to your input and output busses. Draw the busses with a wide wire and connect a pin with the appropriate name. Then draw narrow wires from the bus to individual logic gates. Add a label for each of these wires with its name (e.g. `aluop<0>`).

Create a self-checking testbench for your `aludec`, as you did with the gates in Lab 1. Simulate your schematic and correct any errors.

Make a symbol for your `aludec`.

Next, create an `aludec` layout. Remember to use `metal2` vertically and `metal3` horizontally. When you are done, provide pins for `vdd!`, `gnd!`, the eight inputs and the three outputs.

Run DRC and LVS and fix any problems you might find.

## II. Controller Verilog

The MIPS controller is responsible for decoding the instruction and generating mux select and register enable signals for the datapath. In our multicycle MIPS design, it is implemented as a finite state machine, as shown in Figure 3.<sup>1</sup> The Verilog code describing this FSM is the `statellogic` and `outputlogic` modules in the RTL `mips.sv` that you worked with in Lab 2.

Look through the Verilog and identify the major portions. The top level module is called `controller`. It calls the `aludec`, which you just designed, and a `controller_synth` module that you are about to synthesize. The `controller_synth` module, in turn, has separate modules for the next state logic and the output logic of the FSM. The next state logic describes the state transitions of the FSM. The output logic determines which outputs will be asserted in each state. Note that the Verilog also contains the AND/OR gates required to compute `pcen`, the write enable to the program counter.

---

<sup>1</sup> This FSM is identical to that of the multicycle processors in Patterson & Hennessy *Computer Organization and Design* and in Harris and Harris *Digital Design and Computer Architecture*, save that `LW` and `SW` have been replaced by `LB` and `SB` and instruction fetch now requires four cycles to load instructions through a byte-wide interface.

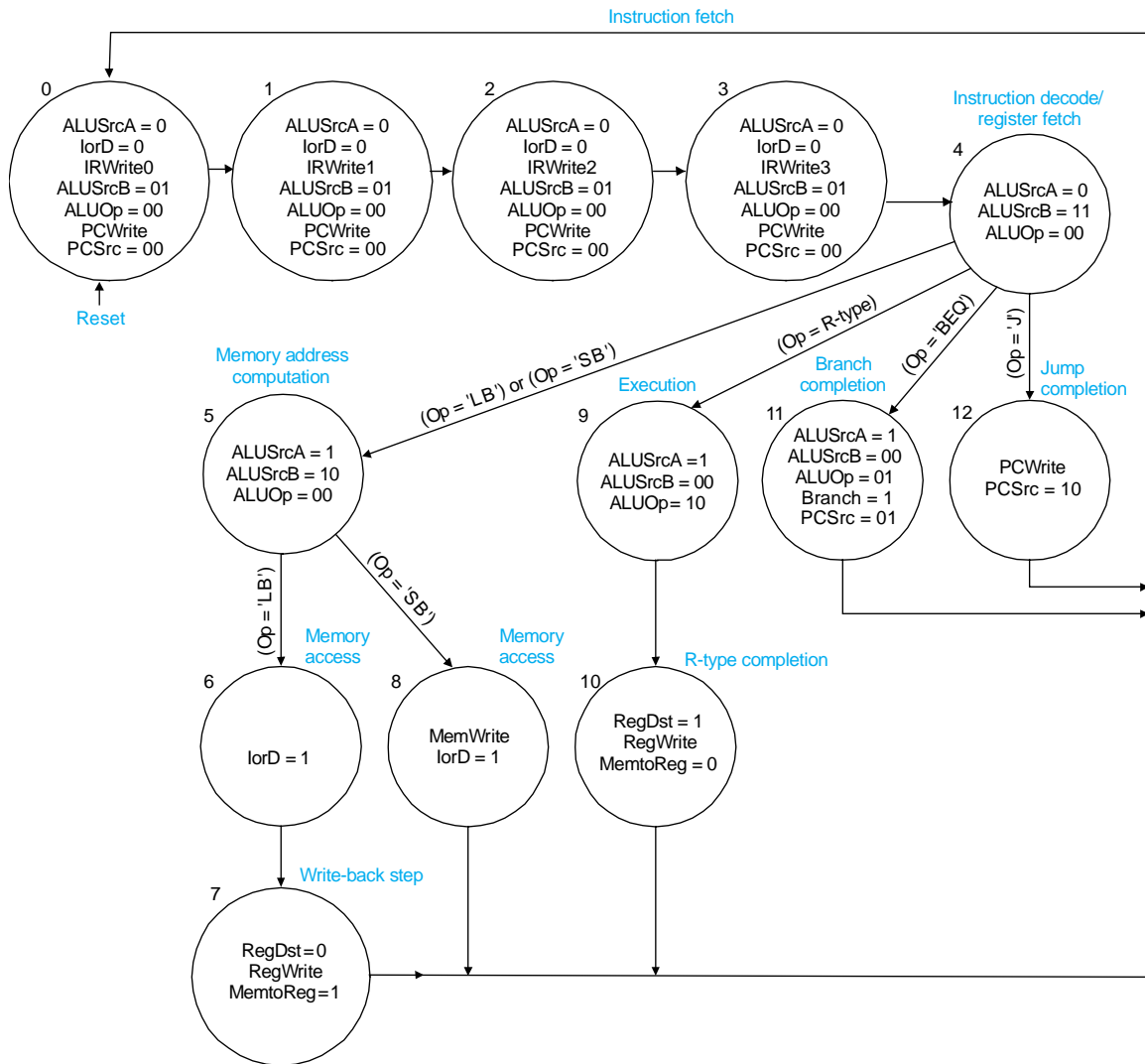


Figure 3: Controller FSM

### III. Controller Synthesis

In this section, you will use Synopsys Design Compiler to synthesize the `controller_synth` module into a gate-level netlist. Design Compiler is the industry-standard logic synthesis tool.

Create a new directory named `synth` in your `IC_CAD` directory. Design Compiler requires a configuration file in the directory where you will run. Copy it over using

```
cp /courses/e158/11/lab3/.synopsys_dc.setup ~/IC_CAD/synth
```

Look over the file to see how it defines some configuration for the Design Compiler.

Design Compiler can be driven at the command line, but it is easier to place all of the commands in a script. Copy a generic synthesis script from the class directory

```
cp /courses/e158/11/lab3/syndc.tcl ~/IC_CAD/synth
```

Look over the script. It is written in TCL (tool control language), with extensions that Design Compiler understands. Near the beginning of the file, it sets “myFiles” to `mips.sv` and the basename (the module you want to synthesize) to `controller_synth`. If you were synthesizing something else, you would need to change these lines.

Copy your `mips.sv` file from lab2 into the `synth` directory. While in the `synth` directory, invoke synthesis using the command

```
syn-dc -f syndc.tcl
```

You’ll get a bunch of messages that may scroll off the screen. It may be easier to pipe them to `more` so you get one screenful at a time:

```
syn-dc -f syndc.tcl | more
```

The first time that you run, Design Compiler will analyze the `muddlib.db` file to determine which cells are available in the cell library. Subsequent runs in the same directory will be much faster after this analysis is complete.

Check the report carefully. You should get many warnings in the first 100 lines of `mips.sv` because the testbench contains nonsynthesizable commands such as *initial* blocks, delays, assertions, and *\$finish*. You’ll also get warnings about driving cell attributes that you may ignore. You’ll also notice that certain unused bits are optimized out of the instruction register. Get a sense of what a good report looks like so you can recognize a bad one.

Inspect the output files named `controller_synth_syn.v`, `.rep`, `.pow`, and `.sdc`. The `.v` file is the structural netlist produced by synthesis. The `.rep` file is the synthesis report, including a summary of the critical path timing and the area. The `.pow` file has a power report. The `.sdc` file contains timing constraints.

#### **IV. Controller Place & Route with SOC Encounter**

Now, you can import the synthesized design back into the Cadence tools and place & route it into a layout using SOC Encounter. (SOC stands for System-On-Chip.)

Make another directory in `IC_CAD` called `soc` for your SOC Encounter runs. Then make a subdirectory within `soc` (e.g. `controller_xx`) for this particular run. Change into this new run directory.

You’ll need copies of your structural netlist and timing constraints files from synthesis. The best way to do this is to create a symbolic link so that if you change your synthesis results, the new netlist is automatically visible:

```
ln -s ~/IC_CAD/synth/controller_synth_syn.v .
ln -s ~/IC_CAD/synth/controller_synth_syn.sdc .
```

You'll also need links to `muddlib.lib` and `muddlib.lef`. `muddlib.db` is the Synopsys library file containing timing information about the cells used by synthesis. `muddlib.lef` is a Library Exchange Format file containing physical information about the cell sizes and pin locations.

```
ln -s /courses/e158/11/lab3/muddlib.lib .
ln -s /courses/e158/11/lab3/muddlib.lef .
```

Version 9.1 of SOC Encounter / Encounter Digital Implementation (EDI) is crashing Cygwin in 2011. Use a different program. \*\*\*

Invoke SOC Encounter at the command line by typing `cad-soc`. (Note that Encounter needs your terminal window and will crash if you try to run it in the background. Also, you may receive and ignore an error message about shared library `libfeoax22.so` and about Open Access features being disabled.) Encounter can also be driven with a GUI or with a script. In this lab, we'll use the GUI because there aren't too many commands to enter and you'll be able to see what is going on.

Invoke File • Import Design. Enter `controller_synth_syn.v` for your Verilog netlist and `controller_synth` as the top-level cell. Enter `muddlib.lib` as the Common Timing Library, `muddlib.lef` as the LEF file, and `controller_synth_syn.sdc` as the timing constraint file. Then, click on the Advanced tab. Click on Power and enter `vdd!` as the Power Net and `gnd!` as the Ground Net.

Watch for errors in the console. You may see and ignore warnings about layers, via rules, leakage power units, `fanout_load`, `set_input_delay`, and `set_units`. Encounter's internal state is easily corrupted when there are errors. If you get errors along the way, it is better to start over from scratch by reinvoking `cad-soc` rather than attempting to redo the command.

Choose Floorplan • Specify Floorplan. Set margins of 30 (microns) from the core to the left, right, top, and bottom sides to give room for a power ring later on. Under the Advanced tab, you can leave 0 spacing between pairs of rows for now. If you were building a more complex design and had trouble with insufficient space for routing, you might wish to increase the row spacing. After clicking OK, you'll see a window with some rows for standard cells and some space around the edge.

Use File • Save Design... and save the design as `controller_synth_floorplan.enc`. Encounter doesn't allow Undo, so if you goof a later step, you'll be able to revert to this step. In general, save often with different file names corresponding to the steps you are at so that you can revert to the last good place. If you need to reload a saved design, choose File • Restore Design....

Invoke **Power • Power Planning • Add Ring...** to add the power rings around the cells. Set the width of the top, bottom, left, and right rings to 9.9 (microns) and the spacing to 1.8 to provide fat wires that can carry plenty of current to the design. Click **Center in channel** at the **Offset** option to center the rings in the margin around the rows of cells. You'll see the power rings appear in the Encounter window.

Invoke **Route • Special Route...** to route power and ground to each row, and press **OK**. Notice that Encounter automatically flips cells between rows and overlaps the power and ground wires to save space. You may wish to save again now.

Invoke **Place • Place Standard Cell...** Turn off all optimization because you don't want Encounter to modify your design (which would cause LVS errors later). Click **OK** to place the cells in the design. It will appear that nothing happened. On the right end of the second row of the toolbar, click on the **Physical View** icon that looks like a transistor. This will bring you to a new view in which you can see the gates placed in the rows. Check the console window and look for errors. Ignore warnings about the scan chain because you don't have one, and about buffers because muddlib doesn't have them (it uses pairs of inverters). Encounter has a degree of randomness in cell placement and occasionally fails to place the cells. If you have an error, restore the last saved version and try again. If all is good, save again.

Invoke **Place • Physical Cells • Add Filler...** to add filler cells so there is a continuous n-well even where there are no logic gates. Click **select**, then choose both **fill\_1\_wide** and **fill\_2\_wide** and click **Add**. You'll see the gaps filled up.

Invoke **Route • Nanoroute • Route...** and click **OK** to route the design. Check the console to verify that the number of fails is 0 and the number of DRC violations is 0. Again, if it fails, restore and try again. Notice how the cells are routed together and connect to pins scattered randomly around the periphery. You may get six warnings about vdd and gnd, metal dimensions, and a capacitance table.

Invoke **Verify • Verify Geometry...** to do a basic design rule check. Make sure there are no violations. (You might get a warning about a filler cell pin on metal1 not connected to any net, and also see some violations. We're not sure why they show up, but your design is still ok if it passes DRC and LVS in the next section.)

Invoke **Verify • Verify Connectivity...** to ensure the design is really connected in the way that the structural netlist specified. Make sure there are no violations.

You are now done with place & route. Save once more. Then choose **File • Save • DEF** to save the output in Design Exchange Format that the Virtuoso Layout Editor will be able to read back in. Change to DEF version 5.5 and click **OK**.

Close Encounter.

## V. Import the Synthesized and Placed Controller

The next step is to import the schematic and layout for the controller back into the Cadence tools.

In the icfb window, choose File • Import • Verilog. Set the Target Library Name to `controller_xx`. Add `mudlib11` to Reference Libraries, along with `basic`. Set the Verilog Files to Import to `~/IC_CAD/synth/controller_synth_syn.v`. You'll see warnings about Verilog definitions for modules not being found. These are ok because the tool uses `muddlib11` cells. Open the `controller_synth` schematic. You should be able to identify the eight latches and a rat's nest of gates that make you thankful the FSM was synthesized rather than designed by hand.

In the icfb window, choose File • Import • DEF. Enter your library (e.g. `controller_xx`), `controller_synth` for the cell, and layout for the view. Click Use and enter `muddlib11` as the reference library to indicate where the standard cells are taken from. Enter `~/IC_CAD/soc/controller_xx/controller_synth.def` for the DEF file. In the icfb window, you should have warnings about failing to open the `techfile.cds` or the `controller_synth` layout and `viagen` layouts and finding the master core. Watch for other errors.

In the Library Manager, open the `controller_synth` layout that you just imported. The design will initially open in “Preview” mode without the usual set of menus. Choose Tools • Layout to return to your familiar layout model.

All of the cells are imported as “abstract” views with just port information but no real layout. You'll need to use find & replace to change these to “layout” views. Choose Edit • Search... Click Add Criteria. Change the criteria to view name. Set it equal to “abstract” Click Apply, and all the abstracts will be selected. At the bottom of the window, choose Replace -> view name -> and enter “layout” in the box. Click Replace All, and close the search box. Zoom in and inspect the layout that was just produced. Be sure to save the file.

Run DRC and LVS. There should be no errors.

Our Encounter flow is not entirely robust yet. If you get a small number of DRC or LVS errors, it may be easiest to fix them by hand in the Virtuoso layout editor.

## V. What to Turn In

Please provide a hard copy of each of the following items:

1. Please indicate how many hours you spent on this lab. This will not affect your grade, but will be helpful for calibrating the workload for the future.
2. A printout of the `aludec` schematics and layout.
3. Does your `aludec` pass your self-checking testbench?

4. A printout of the `controller_synth` schematics and layout.
5. What are the DRC and LVS status of `aludec` and `controller_synth`?