

# Lecture 18: Datapath Functional Units

# Outline




- Comparators
- Shifters
- Multi-input Adders
- Multipliers

# Comparators

- ❑ 0's detector:  $A = 00\dots000$
- ❑ 1's detector:  $A = 11\dots111$
- ❑ Equality comparator:  $A = B$
- ❑ Magnitude comparator:  $A < B$

   
# 1's & 0's Detectors

- ❑ 1's detector: N-input AND gate
- ❑ 0's detector: NOTs + 1's detector (N-input NOR)



 
# Equality Comparator

- ❑ Check if each bit is equal (XNOR, aka equality gate)
- ❑ 1's detect on bitwise equality


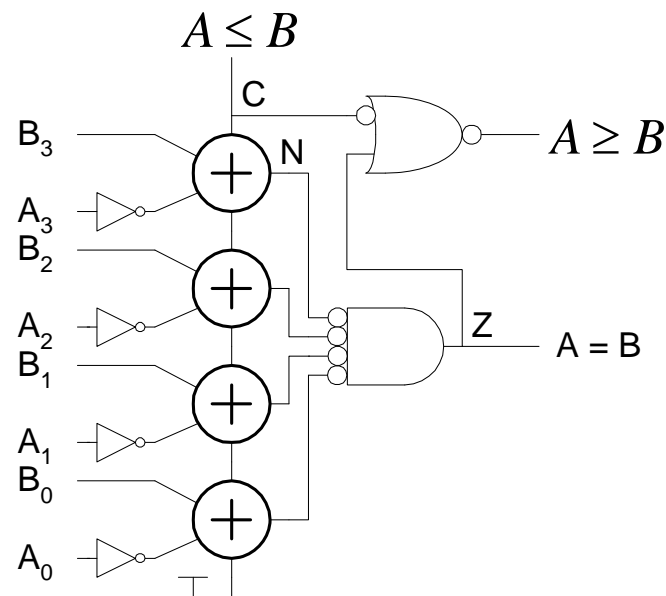
# Magnitude Comparator

- ❑ Compute  $B - A$  and look at sign
- ❑  $B - A = B + \sim A + 1$
- ❑ For unsigned numbers, carry out is sign bit



# Signed vs. Unsigned

- ❑ For signed numbers, comparison is harder
  - C: carry out
  - Z: zero (all bits of  $A - B$  are 0)
  - N: negative (MSB of result)
  - V: overflow (inputs had different signs, output sign  $\neq$  B)
  - S:  $N \text{ xor } V$  (sign of result)

| Relation   | Unsigned Comparison | Signed Comparison       |
|------------|---------------------|-------------------------|
| $A = B$    | $Z$                 | $Z$                     |
| $A \neq B$ | $\bar{Z}$           | $\bar{Z}$               |
| $A < B$    | $C \cdot \bar{Z}$   | $\bar{S} \cdot \bar{Z}$ |
| $A > B$    | $\bar{C}$           | $S$                     |
| $A \leq B$ | $C$                 | $\bar{S}$               |
| $A \geq B$ | $\bar{C} + Z$       | $S + Z$                 |

# Shifters

## ❑ Logical Shift:

– Shifts number left or right and fills with 0's

• 1011 LSR 1 =                      1011 LSL1 =

## ❑ Arithmetic Shift:

– Shifts number left or right. Rt shift sign extends

• 1011 ASR1 =                      1011 ASL1 =

## ❑ Rotate:


– Shifts number left or right and fills with lost bits

• 1011 ROR1 =                      1011 ROL1 =


 
# Funnel Shifter

- ❑ A funnel shifter can do all six types of shifts
- ❑ Selects  $N$ -bit field  $Y$  from  $2N-1$ -bit input
  - Shift by  $k$  bits ( $0 \leq k < N$ )
  - Logically involves  $N$   $N:1$  multiplexers




# Funnel Source Generator

| Shift Type              | $Z_{2N-2:N}$ | $Z_{N-1}$ | $Z_{N-2:0}$ | Offset    |
|-------------------------|--------------|-----------|-------------|-----------|
| Rotate Right            | $A_{N-2:0}$  | $A_{N-1}$ | $A_{N-2:0}$ | $k$       |
| Logical Right           | 0            | $A_{N-1}$ | $A_{N-2:0}$ | $k$       |
| Arithmetic Right        | sign         | $A_{N-1}$ | $A_{N-2:0}$ | $k$       |
| Rotate Left             | $A_{N-1:1}$  | $A_0$     | $A_{N-1:1}$ | $\bar{k}$ |
| Logical/Arithmetic Left | $A_{N-1:1}$  | $A_0$     | 0           | $\bar{k}$ |

 
# Array Funnel Shifter

- N N-input multiplexers
  - Use 1-of-N hot select signals for shift amount
  - nMOS pass transistor design ( $V_t$  drops!)




 
# Logarithmic Funnel Shifter

- Log N stages of 2-input muxes
  - No select decoding needed


 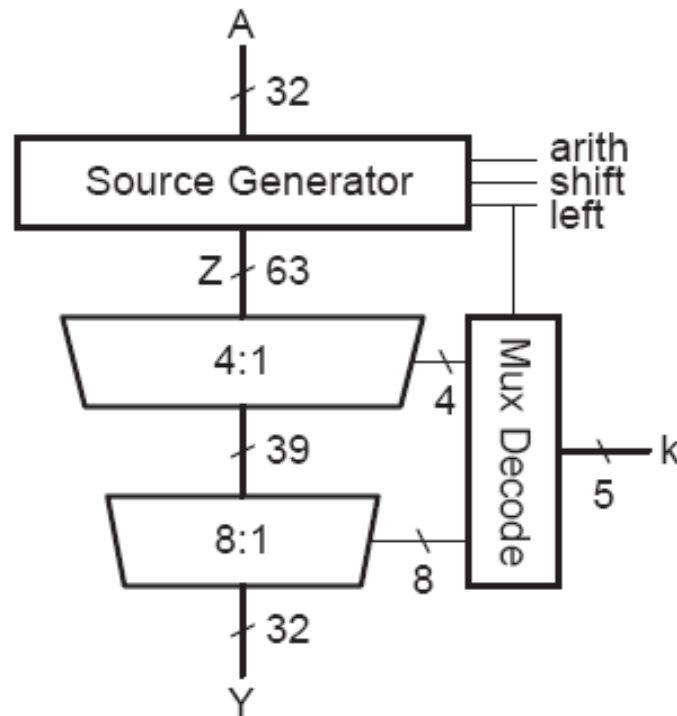
# 32-bit Logarithmic Funnel


- ❑ Wider multiplexers reduce delay and power
- ❑ Operands  $> 32$  bits introduce datapath irregularity




# Barrel Shifter

- ❑ Barrel shifters perform right rotations using wrap-around wires.
- ❑ Left rotations are right rotations by  $N - k = \bar{k} + 1$  bits.
- ❑ Shifts are rotations with the end bits masked off.


# Logarithmic Barrel Shifter

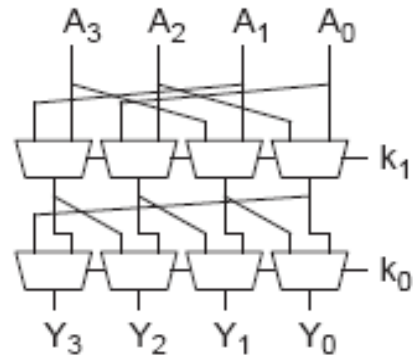

Right shift only

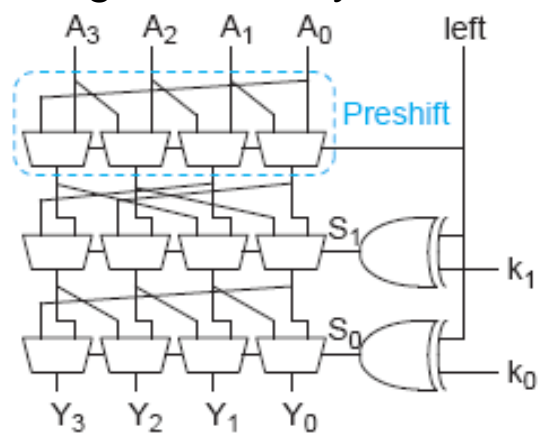


Right/Left shift

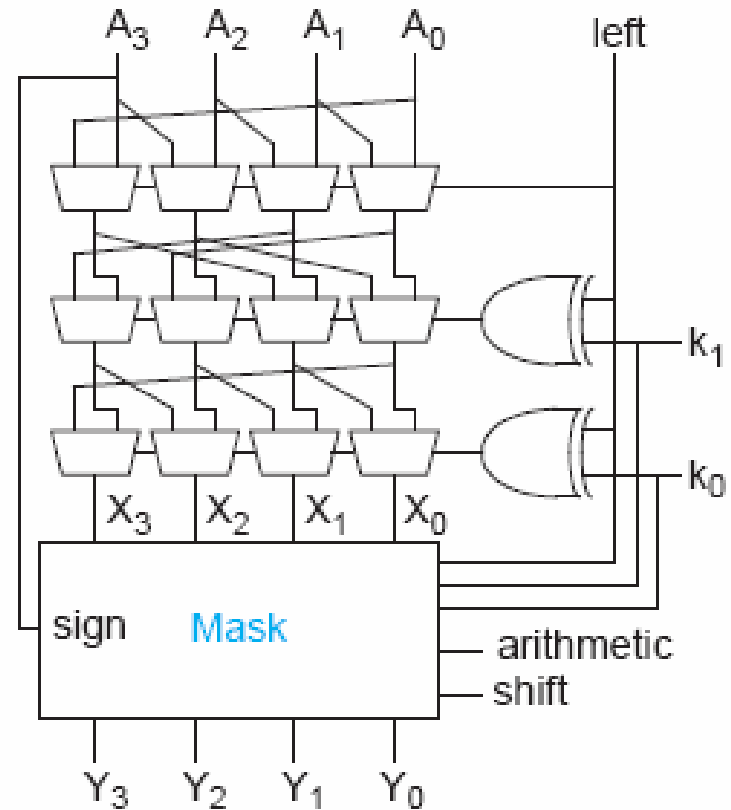

Right/Left Shift & Rotate
 
# 32-bit Logarithmic Barrel


- ❑ Datapath never wider than 32 bits
- ❑ First stage preshifts by 1 to handle left shifts





 
# Multi-input Adders

- ❑ Suppose we want to add  $k$   $N$ -bit words
  - Ex:  $0001 + 0111 + 1101 + 0010 = 10111$
- ❑ Straightforward solution:  $k-1$   $N$ -input CPAs
  - Large and slow



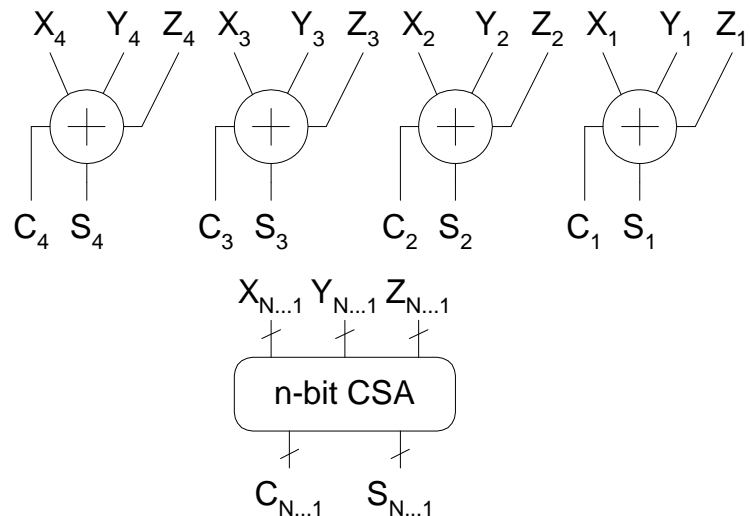
# Carry Save Addition

- ❑ A full adder sums 3 inputs and produces 2 outputs
  - Carry output has twice *weight* of sum output
- ❑ N full adders in parallel are called *carry save adder*
  - Produce N sums and N carry outs


 
# CSA Application

- ❑ Use k-2 stages of CSAs
  - Keep result in carry-save redundant form
- ❑ Final CPA computes actual result



# Multiplication

□ Example:

$$\begin{array}{r} 1100 : 12_{10} \\ \underline{0101} : 5_{10} \\ \hline \end{array}$$


multiplicand  
multiplier  
partial products  
product

- M x N-bit multiplication
- Produce N M-bit partial products
  - Sum these to produce M+N-bit product




# Dot Diagram

- Each dot represents a bit

 


# Array Multiplier

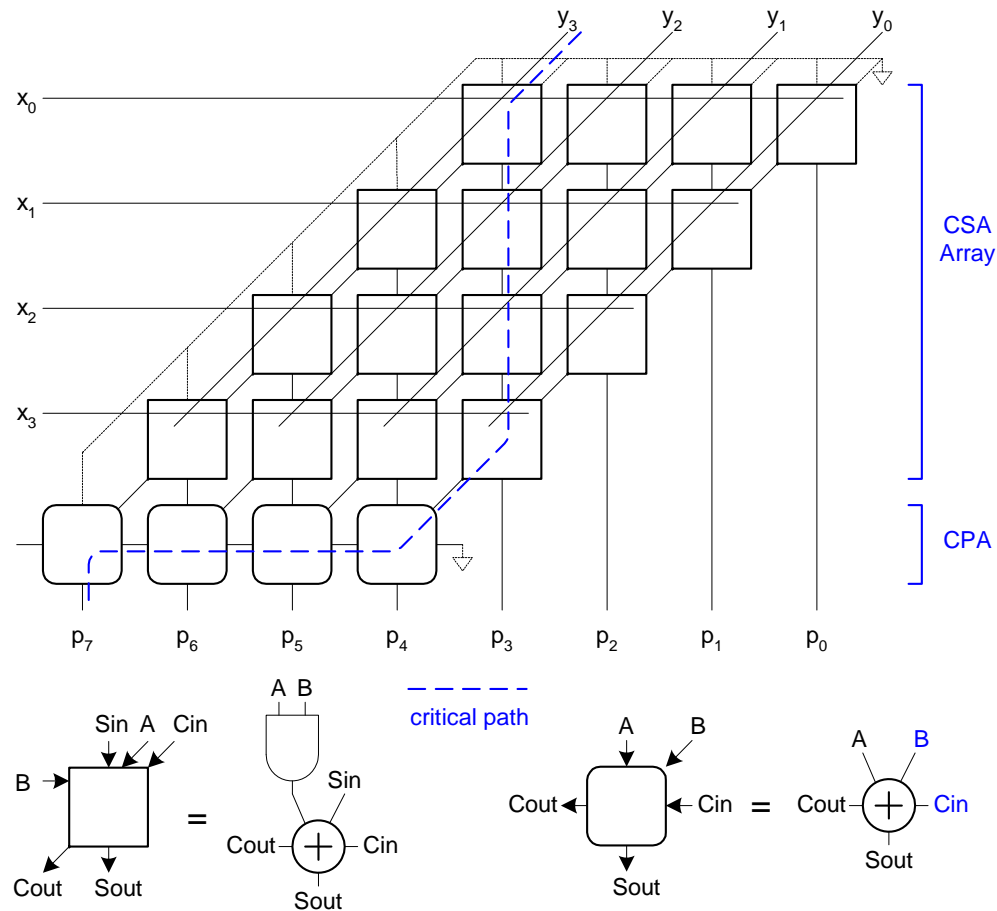
 
# Rectangular Array

- ❑ Squash array to fit rectangular floorplan





# Fewer Partial Products

- ❑ Array multiplier requires  $N$  partial products
- ❑ If we looked at groups of  $r$  bits, we could form  $N/r$  partial products.
  - Faster and smaller?
  - Called radix- $2^r$  encoding
- ❑ Ex:  $r = 2$ : look at pairs of bits
  - Form partial products of  $0, Y, 2Y, 3Y$
  - First three are easy, but  $3Y$  requires adder ☹


# Booth Encoding

- ❑ Instead of  $3Y$ , try  $-Y$ , then increment next partial product to add  $4Y$
- ❑ Similarly, for  $2Y$ , try  $-2Y + 4Y$  in next partial product

| Inputs     |          |            | Partial Product | Booth Selects |            |         |
|------------|----------|------------|-----------------|---------------|------------|---------|
| $x_{2i+1}$ | $x_{2i}$ | $x_{2i-1}$ | $PP_i$          | $SINGLE_i$    | $DOUBLE_i$ | $NEG_i$ |
| 0          | 0        | 0          | 0               | 0             | 0          | 0       |
| 0          | 0        | 1          | $Y$             | 1             | 0          | 0       |
| 0          | 1        | 0          |                 |               |            |         |
| 0          | 1        | 1          |                 |               |            |         |
| 1          | 0        | 0          |                 |               |            |         |
| 1          | 0        | 1          |                 |               |            |         |
| 1          | 1        | 0          |                 |               |            |         |
| 1          | 1        | 1          |                 |               |            |         |

 
# Booth Hardware

- Booth encoder generates control lines for each PP
  - Booth selectors choose PP bits



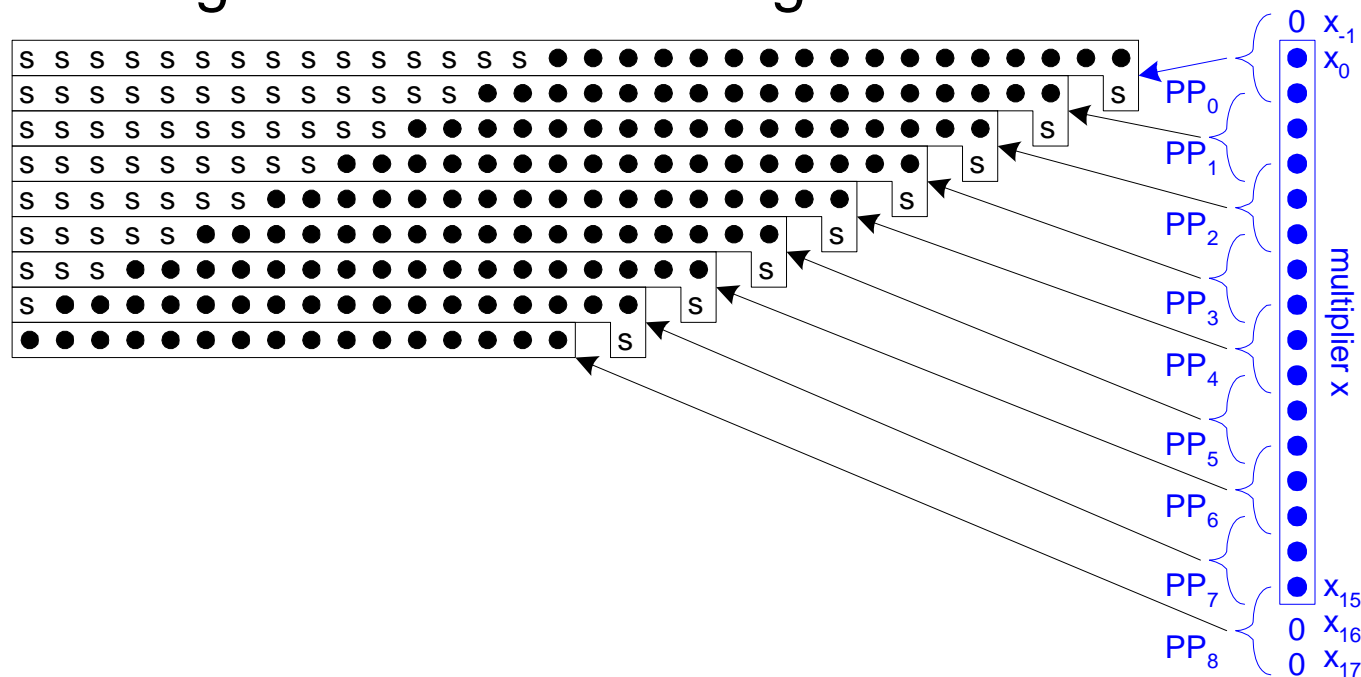
# Sign Extension

- ❑ Partial products can be negative
  - Require sign extension, which is cumbersome
  - High fanout on most significant bit



 
# Simplified Sign Ext.

- Sign bits are either all 0's or all 1's
  - Note that all 0's is all 1's + 1 in proper column
  - Use this to reduce loading on MSB


 
# Even Simpler Sign Ext.

- ❑ No need to add all the 1's in hardware
  - Precompute the answer!



# Advanced Multiplication

---

- ❑ Signed vs. unsigned inputs
- ❑ Higher radix Booth encoding
- ❑ Array vs. tree CSA networks