

Chapter 4 :: Hardware Description Languages

Digital Design and Computer Architecture

David Money Harris and Sarah L. Harris

Copyright © 2007 Elsevier

4-<1>



Chapter 4 :: Topics

- **Introduction**
- **Combinational Logic**
- **Structural Modeling**
- **Sequential Logic**
- **More Combinational Logic**
- **Finite State Machines**
- **Parameterized Modules**
- **Testbenches**

Copyright © 2007 Elsevier

4-<2>



Introduction

- **Hardware description language (HDL):** allows designer to specify logic function only. Then a computer-aided design (CAD) tool produces the optimized gates.
- **Most commercial designs built using HDLs**
- **Two leading HDLs:**
 - Verilog
 - developed in 1984 by Gateway Design Automation
 - became an IEEE standard (1364) in 1995
 - VHDL
 - Developed in 1981 by the Department of Defense
 - Became an IEEE standard (1076) in 1987

Copyright © 2007 Elsevier

4-<3>



HDL to Gates

- **Simulation**
 - Input values are applied to the circuit
 - Outputs checked for correctness
 - Millions of dollars saved by debugging in simulation instead of hardware
- **Synthesis**
 - Transforms HDL code into a *netlist* describing the hardware (i.e., a list of gates and the wires connecting them)

IMPORTANT:

When describing circuits using an HDL, it's critical to think of the **hardware the code should produce.**

Copyright © 2007 Elsevier

4-<4>



Verilog Modules



Two types of Modules:

- Behavioral: describe what a module does
- Structural: describe how a module is built from simpler modules

Copyright © 2007 Elsevier

4-<5>



Behavioral Verilog Example

Verilog:

```
module example(input a, b, c,
               output y);
    assign y = ~a & ~b & ~c | a & ~b & ~c | a & ~b & c;
endmodule
```

Copyright © 2007 Elsevier


4-<6>



Behavioral Verilog Simulation

Verilog:

```
module example(input a, b, c,
               output y);
    assign y = ~a & ~b & ~c | a & ~b & ~c | a & ~b & c;
endmodule
```

 

Copyright © 2007 Elsevier

4-<7>




Behavioral Verilog Synthesis

Verilog:

```
module example(input a, b, c,
               output y);
    assign y = ~a & ~b & ~c | a & ~b & ~c | a & ~b & c;
endmodule
```

Synthesis:

 

Copyright © 2007 Elsevier

4-<8>



Verilog Syntax

- Verilog is case sensitive. So, reset and Reset are not the same signal.
- Verilog does not allow you to start signal or module names with numbers. So, for example, 2mux is an invalid name.
- Verilog ignores whitespace.
- Comments come in single-line and multi-line varieties:
 - // single line comment
 - /* multiline comment */

Copyright © 2007 Elsevier

4-<9>



Structural Modeling - Hierarchy

```

module and3(input a, b, c,
            output y);
    assign y = a & b & c;
endmodule

module inv(input a,
           output y);
    assign y = ~a;
endmodule

module nand3(input a, b, c
             output y);
    wire n1; // internal signal

    and3 andgate(a, b, c, n1); // instance of and3
    inv inverter(n1, y); // instance of inverter
endmodule
    
```

Copyright © 2007 Elsevier


4-<10>



Bitwise Operators

```

module gates(input [3:0] a, b,
             output [3:0] y1, y2, y3, y4, y5);
    /* Five different two-input logic
       gates acting on 4 bit busses */
    assign y1 = a & b; // AND
    assign y2 = a | b; // OR
    assign y3 = a ^ b; // XOR
    assign y4 = ~(a & b); // NAND
    assign y5 = ~(a | b); // NOR
endmodule
    
```

 

```

// single line comment
/*...*/ multiline comment
    
```

Copyright © 2007 Elsevier


4-<11>



Reduction Operators

```

 module and8(input [7:0] a,
            output y);
    assign y = &a;
    // &a is much easier to write than
    // assign y = a[7] & a[6] & a[5] & a[4] &
    // a[3] & a[2] & a[1] & a[0];
endmodule
    
```



Copyright © 2007 Elsevier


4-<12>



Conditional Assignment

```

 module mux2(input  [3:0] d0, d1,
            input   s,
            output [3:0] y);
    assign y = s ? d1 : d0;
endmodule
    
```



? : is also called a *ternary operator* because it operates on 3 inputs: s, d1, and d0.

Copyright © 2007 Elsevier

4-<13>




Internal Variables

```

module fulladder(input a, b, cin, output s, cout);
    wire p, g; // internal nodes

    assign p = a ^ b;
    assign g = a & b;

    assign s = p ^ cin;
    assign cout = g | (p & cin);
endmodule
    
```

 

Copyright © 2007 Elsevier

4-<14>



Precedence

Defines the order of operations

Highest

~	NOT
*, /, %	mult, div, mod
+, -	add, sub
<<, >>	shift
<<<, >>>	arithmetic shift
<, <=, >, >=	comparison
==, !=	equal, not equal
&, ~&	AND, NAND
^, ~^	XOR, XNOR
, ~	OR, XOR
?:	ternary operator

Lowest

Copyright © 2007 Elsevier

4-<15>



Numbers

Format: N'Bvalue

N = number of bits, B = base

N'B is optional but recommended (default is decimal)

Number	# Bits	Base	Decimal Equivalent	Stored
3'b101	3	binary	5	101
'b11	unsized	binary	3	00...0011
8'b11	8	binary	3	00000011
8'b1010_1011	8	binary	171	10101011
3'd6	3	decimal	6	110
6'o42	6	octal	34	100010
8'hAB	8	hexadecimal	171	10101011
42	Unsize	decimal	42	00...0101010

Copyright © 2007 Elsevier

4-<16>



Bit Manipulations: Example 1

```
assign y = {a[2:1], {3{b[0]}}, a[0], 6'b100_010};

// if y is a 12-bit signal, the above statement produces:
y = a[2] a[1] b[0] b[0] b[0] a[0] 1 0 0 0 1 0

// underscores (_) are used for formatting only to make
it easier to read. Verilog ignores them.
```

Copyright © 2007 Elsevier

4-<17>




Bit Manipulations: Example 2

Verilog:

```
module mux2_8(input [7:0] d0, d1,
             input      s,
             output [7:0] y);

    mux2 lsbmux(d0[3:0], d1[3:0], s, y[3:0]); // from slide 12
    mux2 msbmux(d0[7:4], d1[7:4], s, y[7:4]); // from slide 12
endmodule
```

Synthesis:

 

Copyright © 2007 Elsevier

4-<18>




Z: Floating Output

Verilog:

```
module tristate(input [3:0] a,
               input      en,
               output [3:0] y);
    assign y = en ? a : 4'bz;
endmodule
```

Synthesis:

 


Copyright © 2007 Elsevier

4-<19>



Delays

```
module example(input a, b, c,
               output y);
    wire ab, bb, cb, n1, n2, n3;
    assign #1 {ab, bb, cb} = {a, b, c};
    assign #2 n1 = ab & bb & cb;
    assign #2 n2 = a & bb & cb;
    assign #2 n3 = a & bb & c;
    assign #4 y = n1 | n2 | n3;
endmodule
```

 


Copyright ©



Delays

```
module example(input a, b, c,
               output y);
  wire ab, bb, cb, n1, n2, n3;
  assign #1 {ab, bb, cb} =
    ~{a, b, c};
  assign #2 n1 = ab & bb & cb;
  assign #2 n2 = a & bb & cb;
  assign #2 n3 = a & bb & c;
  assign #4 y = n1 | n2 | n3;
endmodule
```

 

Copyright © 2007 Elsevier

4-21>



Sequential Logic

- Verilog uses certain idioms to describe latches, flip-flops and FSMs
- Other coding styles may simulate correctly but produce incorrect hardware

Copyright © 2007 Elsevier

4-22>



Always Statement

General Structure:

```
always @ (sensitivity list)
  statement;
```

Whenever the event in the sensitivity list occurs, the statement is executed

Copyright © 2007 Elsevier

4-23>




D Flip-Flop

```
module flop(input clk,
            input [3:0] d,
            output reg [3:0] q);
```

```
  always @ (posedge clk)
    q <= d; // pronounced "q gets d"
```

```
endmodule
```

 

Any signal on the left side of an always statement must be declared `reg`. In this case `q` is declared as `reg`

Beware: A variable declared `reg` is not necessarily a registered output. We will show examples of this later.

Copyright © 2007 Elsevier

4-24>




Resettable D Flip-Flop

```
module flopr(input      clk,
            input      reset,
            input [3:0] d,
            output reg [3:0] q);
```

```
// synchronous reset
always @ (posedge clk)
    if (reset) q <= 4'b0;
    else      q <= d;
```

```
endmodule
```

 

Copyright © 2007 Elsevier

4-<25>




Resettable D Flip-Flop

```
module flopr(input      clk,
            input      reset,
            input [3:0] d,
            output reg [3:0] q);
```

```
// asynchronous reset
always @ (posedge clk, posedge reset)
    if (reset) q <= 4'b0;
    else      q <= d;
```

```
endmodule
```

 

Copyright © 2007 Elsevier

4-<26>




D Flip-Flop with Enable

```
module flopren(input      clk,
              input      reset,
              input      en,
              input [3:0] d,
              output reg [3:0] q);
```

```
// asynchronous reset and enable
always @ (posedge clk, posedge reset)
    if (reset) q <= 4'b0;
    else if (en) q <= d;
```

```
endmodule
```

 

Copyright © 2007 Elsevier

4-<27>




Latch

```
module latch(input      clk,
            input [3:0] d,
            output reg [3:0] q);
```

```
always @ (clk, d)
    if (clk) q <= d;
```

```
endmodule
```

 

Warning: We won't use latches in this course, but you might write code that inadvertently implies a latch. So if your synthesized hardware has latches in it, this indicates an error.

Copyright © 2007 Elsevier

4-<28>



Other Behavioral Statements

- Statements that must be inside `always` statements:
 - `if/else`
 - `case, casez`
- **Reminder:** Variables assigned in an `always` statement must be declared as `reg` (even if they're not actually registered!)

Copyright © 2007 Elsevier

4-<29>



Combinational Logic using `always`

```
// combinational logic using an always statement
module gates(input    [3:0] a, b,
              output reg [3:0] y1, y2, y3, y4, y5);
  always @ (*)      // need begin/end because there is
  begin            // more than one statement in always
    y1 = a & b;    // AND
    y2 = a | b;    // OR
    y3 = a ^ b;    // XOR
    y4 = ~(a & b); // NAND
    y5 = ~(a | b); // NOR
  end
endmodule
```

This hardware could be described with `assign` statements using fewer lines of code, so it's better to use `assign` statements in this case.

Copyright © 2007 Elsevier

4-<30>



Combinational Logic using `case`

```
module sevensseg(input    [3:0] data,
                 output reg [6:0] segments);
  always @(*)
  case (data)
    //      abc_defg
    0: segments = 7'b111_1110;
    1: segments = 7'b011_0000;
    2: segments = 7'b110_1101;
    3: segments = 7'b111_1001;
    4: segments = 7'b011_0011;
    5: segments = 7'b101_1011;
    6: segments = 7'b101_1111;
    7: segments = 7'b111_0000;
    8: segments = 7'b111_1111;
    9: segments = 7'b111_1011;
    default: segments = 7'b000_0000; // required
  endcase
endmodule
```

Copyright © 2007 Elsevier

4-<31>



Combinational Logic using `case`

- In order for a `case` statement to imply combinational logic, all possible input combinations must be described by the HDL.
- Remember to use a `default` statement when necessary.

Copyright © 2007 Elsevier


4-<32>



Combinational Logic using `casez`

```
module priority_casez(input [3:0] a,
                    output reg [3:0] y);
```
 
```
    always @(*)
        casez(a)
            4'b1???: y = 4'b1000; // ? = don't care
            4'b01??: y = 4'b0100;
            4'b001?: y = 4'b0010;
            4'b0001?: y = 4'b0001;
            default: y = 4'b0000;
        endcase
endmodule
```



Copyright © 2007 Elsevier



4-<33>



Blocking vs. Nonblocking Assignments

- `<=` is a “nonblocking assignment”
 - Occurs simultaneously with others
- `=` is a “blocking assignment”
 - Occurs in the order it appears in the file
  
```
// Good synchronizer using // Bad synchronizer using
// nonblocking assignments // blocking assignments
module syncgood(input clk, module syncbad(input clk,
                    input d, output reg q);
                    output reg q);
    reg n1;
    always @(posedge clk)
    begin
        n1 <= d; // nonblocking
        q <= n1; // nonblocking
    end
endmodule
```



Copyright © 2007 Elsevier

4-<34>



Rules for Signal Assignment

- Use `always @ (posedge clk)` and nonblocking assignments to model synchronous sequential logic


```
always @ (posedge clk)
    q <= d; // nonblocking
```
- Use continuous assignments to model simple combinational logic.


```
assign y = a & b;
```
- Use `always @ (*)` and blocking assignments to model more complicated combinational logic where the `always` statement is helpful.
- Do not make assignments to the same signal in more than one `always` statement or continuous assignment statement.


Copyright © 2007 Elsevier

4-<35>



Finite State Machines (FSMs)

 - Three blocks:
 - next state logic
 - state register
 - output logic




Copyright © 2007 Elsevier

4-<36>



FSM Example: Divide by 3

 

The double circle indicates the reset state

Copyright © 2007 Elsevier

4-<37>



FSM in Verilog

```
module divideby3FSM (input clk,
                    input reset,
                    output y);
    reg [1:0] state, nextstate;

    parameter S0 = 2'b00;
    parameter S1 = 2'b01;
    parameter S2 = 2'b10;

    // state register
    always @ (posedge clk, posedge reset)
        if (reset) state <= S0;
        else state <= nextstate;
    // next state logic
    always @ (*)
        case (state)
            S0: nextstate = S1;
            S1: nextstate = S2;
            S2: nextstate = S0;
            default: nextstate = S0;
        endcase
    // output logic
    assign q = (state == S0);
endmodule
```

Copyright © 2007 Elsevier

4-<38>



Parameterized Modules

2:1 mux:

```
module mux2
    #(parameter width = 8) // name and default value
    (input [width-1:0] d0, d1,
     input s,
     output [width-1:0] y);
    assign y = s ? d1 : d0;
endmodule
```

Instance with 8-bit bus width (uses default):

```
mux2 mux1(d0, d1, s, out);
```

Instance with 12-bit bus width:

```
mux2 #(12) lowmux(d0, d1, s, out);
```

Copyright © 2007 Elsevier

4-<39>



Testbenches

- HDL code written to test another HDL module, the *device under test* (dut), also called the *unit under test* (uut)
- Not synthesizable
- Types of testbenches:
 - Simple testbench
 - Self-checking testbench
 - Self-checking testbench with testvectors

Copyright © 2007 Elsevier

4-<40>



Example

Write Verilog code to implement the following function in hardware:

$$y = \overline{bc} + a\overline{b}$$

Name the module sillyfunction

Copyright © 2007 Elsevier

4-<41>



Example

Write Verilog code to implement the following function in hardware:

$$y = \overline{bc} + a\overline{b}$$

Name the module sillyfunction

Verilog

```
module sillyfunction(input a, b, c,
                    output y);
    assign y = ~b & ~c | a & ~b;
endmodule
```

Copyright © 2007 Elsevier

4-<42>



Simple Testbench

```
module testbench1();
    reg a, b, c;
    wire y;
    // instantiate device under test
    sillyfunction dut(a, b, c, y);
    // apply inputs one at a time
    initial begin
        a = 0; b = 0; c = 0; #10;
        c = 1; #10;
        b = 1; c = 0; #10;
        c = 1; #10;
        a = 1; b = 0; c = 0; #10;
        c = 1; #10;
        b = 1; c = 0; #10;
        c = 1; #10;
    end
endmodule
```

Copyright © 2007 Elsevier

4-<43>



Self-checking Testbench

```
module testbench2();
    reg a, b, c;
    wire y;
    // instantiate device under test
    sillyfunction dut(a, b, c, y);
    // apply inputs one at a time
    // checking results
    initial begin
        a = 0; b = 0; c = 0; #10;
        if (y != 1) $display("000 failed.");
        c = 1; #10;
        if (y != 0) $display("001 failed.");
        b = 1; c = 0; #10;
        if (y != 0) $display("010 failed.");
        c = 1; #10;
        if (y != 0) $display("011 failed.");
        a = 1; b = 0; c = 0; #10;
        if (y != 1) $display("100 failed.");
        c = 1; #10;
        if (y != 1) $display("101 failed.");
        b = 1; c = 0; #10;
        if (y != 0) $display("110 failed.");
        c = 1; #10;
        if (y != 0) $display("111 failed.");
    end
endmodule
```

Copyright © 2007 Elsevier

4-<44>



Testbench with Testvectors

- Write testvectors file
- Testbench:
 1. Generate clock for assigning inputs, reading outputs
 2. Read testvectors file into array
 3. Assign inputs, expected outputs
 4. Compare outputs to expected outputs and report errors


Copyright © 2007 Elsevier

4-<45>



Testbench with Testvectors

 - Testbench clock is used to assign inputs (on the rising edge) and compare outputs with expected outputs (on the falling edge).



- The testbench clock may also be used as the clock source for synchronous sequential circuits.

Copyright © 2007 Elsevier

4-<46>



Testvectors File

File: example.tv - contains vectors of abc_yexpected

```
000_1
001_0
010_0
011_0
100_1
101_1
110_0
111_0
```

Copyright © 2007 Elsevier

4-<47>



Testbench: 1. Generate Clock

```
module testbench3();
    reg        clk, reset;
    reg        a, b, c, yexpected;
    wire       y;
    reg  [31:0] vectornum, errors; // bookkeeping variables
    reg  [3:0]  testvectors[10000:0]; // array of testvectors

    // instantiate device under test
    sillyfunction dut(a, b, c, y);

    // generate clock
    always // no sensitivity list, so it always executes
    begin
        clk = 1; #5; clk = 0; #5;
    end
end
```

Copyright © 2007 Elsevier

4-<48>



2. Read Testvectors into Array

```
// at start of test, load vectors
// and pulse reset

initial
begin
    $readmemb("example.tv", testvectors);
    vectornum = 0; errors = 0;
    reset = 1; #27; reset = 0;
end

// Note: $readmemb reads testvector files written in
// hexadecimal
```

Copyright © 2007 Elsevier

4-<49>



3. Assign Inputs and Expected Outputs

```
// apply test vectors on rising edge of clk
always @(posedge clk)
begin
    #1; {a, b, c, yexpected} = testvectors[vectornum];
end
```

Copyright © 2007 Elsevier

4-<50>



4. Compare Outputs with Expected Outputs

```
// check results on falling edge of clk
always @(negedge clk)
begin
    if (~reset) begin // skip during reset
        if (y != yexpected) begin
            $display("Error: inputs = %b", {a, b, c});
            $display(" outputs = %b (%b expected)", y, yexpected);
            errors = errors + 1;
        end
    end

// Note: to print in hexadecimal, use %h. For example,
// $display("Error: inputs = %h", {a, b, c});
```

Copyright © 2007 Elsevier

4-<51>



4. Compare Outputs with Expected Outputs

```
// increment array index and read next testvector
vectornum = vectornum + 1;
if (testvectors[vectornum] === 4'bx) begin
    $display("%d tests completed with %d errors",
        vectornum, errors);
    $finish;
end
end
endmodule

// Note: === and !== can compare values that are
// x or z.
```

Copyright © 2007 Elsevier

4-<52>

