

# Introduction to Computer Engineering (E85)


Harris

Fall 2007

## Problem Set 4

Due: Wednesday, October 3

**DOONESBURY** By Garry Trudeau

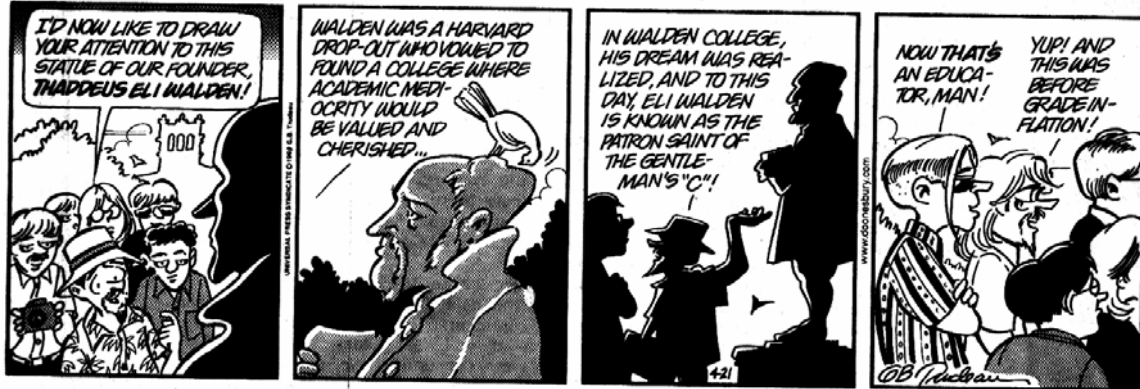

### 1) Textbook Problems

Do problems 3.34, 3.35, 4.2, and 4.18.

### 2) Blocking and nonblocking assignments

The lecture described a bad synchronizer built using blocking assignments that implies one flip-flop instead of two.

```
// Bad synchronizer using
// blocking assignments
module syncbad(input    clk,
               input    d,
               output reg q);
    reg n1;
    always @(posedge clk)
        begin
            n1 = d; // blocking
            q = n1; // blocking
        end
endmodule
```

- Show a different way of writing the always statement that still uses blocking assignments but implies a correct synchronizer.
- Describe a simple sequential circuit that cannot be correctly described with blocking assignments no matter how you write them.

### 3) Time

Please indicate how many hours you spent on this problem set. This will not affect your grade, but will be helpful for calibrating the workload for next semester's class.