

Chapter 4 :: Hardware Description Languages

Digital Design and Computer Architecture

David Money Harris and Sarah L. Harris

Copyright © 2007 Elsevier

4-<1>



Chapter 4 :: Topics

- **Introduction**
- **Combinational Logic**
- **Structural Modeling**
- **Sequential Logic**
- **More Combinational Logic**
- **Finite State Machines**
- **Parameterized Modules**
- **Testbenches**

Copyright © 2007 Elsevier

4-<2>



Introduction

- Hardware description language (HDL): allows designer to specify logic function only. Then a computer-aided design (CAD) tool produces or *synthesizes* the optimized gates.
- Most commercial designs built using HDLs
- Two leading HDLs:
 - **Verilog**
 - developed in 1984 by Gateway Design Automation
 - became an IEEE standard (1364) in 1995
 - **VHDL**
 - Developed in 1981 by the Department of Defense
 - Became an IEEE standard (1076) in 1987

Copyright © 2007 Elsevier

4-<3>



SystemVerilog

- These lecture notes cover SystemVerilog
 - An improved version of Verilog
 - Standardized in 2005
 - Widely used in industry
 - Backward compatible
 - Verilog examples from the text will work
 - Eliminates weird syntax artifacts of Verilog
 - Use `logic` type in place of `wire` and `reg`
 - Better ways to differentiate between combinational and sequential logic

Copyright © 2007 Elsevier

4-<4>



HDL to Gates

- **Simulation**
 - Input values are applied to the circuit
 - Outputs checked for correctness
 - Millions of dollars saved by debugging in simulation instead of hardware
- **Synthesis**
 - Transforms HDL code into a *netlist* describing the hardware (i.e., a list of gates and the wires connecting them)

IMPORTANT:

When describing circuits using an HDL, it's critical to think of the **hardware** the code should produce.

Copyright © 2007 Elsevier

4-<5>



Verilog Modules



Two types of Modules:

- Behavioral: describe what a module does
- Structural: describe how a module is built from simpler modules

Copyright © 2007 Elsevier

4-<6>



Behavioral Verilog Example

Verilog:

```
module example(input logic a, b, c,
               output logic y);
    assign y = ~a & ~b & ~c | a & ~b & ~c | a & ~b & c;
endmodule
```

Copyright © 2007 Elsevier


4-<7>



Behavioral Verilog Simulation

Verilog:

```
module example(input logic a, b, c,
               output logic y);
    assign y = ~a & ~b & ~c | a & ~b & ~c | a & ~b & c;
endmodule
```

 

Copyright © 2007 Elsevier

4-<8>




Behavioral Verilog Synthesis

Verilog:

```
module example(input logic a, b, c,
               output logic y);
    assign y = ~a & ~b & ~c | a & ~b & ~c | a & ~b & c;
endmodule
```

Synthesis:

 

Copyright © 2007 Elsevier

4-<9>



Verilog Syntax

- Case sensitive
 - Example: reset and Reset are not the same signal.
- No names that start with numbers
 - Example: 2mux is an invalid name.
- Whitespace ignored
- Comments:
 - // single line comment
 - /* multiline comment */
- logic represents a Boolean signal in SystemVerilog
 - 0, 1, x, z
 - Essentially replaces wire and reg data types from Verilog
 - Exception: use tri or trireg on nets with multiple drivers

Copyright © 2007 Elsevier

4-<10>



Structural Modeling - Hierarchy

```
module and3(input logic a, b, c,
           output logic y);
    assign y = a & b & c;
endmodule

module inv(input logic a,
          output logic y);
    assign y = ~a;
endmodule

module nand3(input logic a, b, c
            output logic y);
    logic n1; // internal signal
    and3 andgate(a, b, c, n1); // instance of and3
    inv inverter(n1, y); // instance of inverter
endmodule
```


Copyright © 2007 Elsevier

4-<11>



Bitwise Operators

```
module gates(input logic [3:0] a, b,
            output logic [3:0] y1, y2, y3, y4, y5);
    /* Five different two-input logic gates acting on 4 bit busses */
    assign y1 = a & b; // AND
    assign y2 = a | b; // OR
    assign y3 = a ^ b; // XOR
    assign y4 = ~(a & b); // NAND
    assign y5 = ~(a | b); // NOR
endmodule
```

 

```
// single line comment
/*...*/ multiline comment
```

Copyright © 2007 Elsevier

4-<12>




Reduction Operators

```

module and8(input logic [7:0] a,
           output logic      y);
  assign y = &a;
  // &a is much easier to write than
  // assign y = a[7] & a[6] & a[5] & a[4] &
  //           a[3] & a[2] & a[1] & a[0];
endmodule

```

 

Copyright © 2007 Elsevier

4-<13>




Conditional Assignment

```

module mux2(input logic [3:0] d0, d1,
           input logic      s,
           output logic [3:0] y);
  assign y = s ? d1 : d0;
endmodule

```

 

? : is also called a *ternary operator* because it operates on 3 inputs: s, d1, and d0.

Copyright © 2007 Elsevier

4-<14>



Internal Variables


```

module fulladder(input logic a, b, cin,
                output logic s, cout);
  logic p, g; // internal nodes

  assign p = a ^ b;
  assign g = a & b;

  assign s = p ^ cin;
  assign cout = g | (p & cin);
endmodule

```

 

Copyright © 2007 Elsevier

4-<15>



Precedence

Defines the order of operations

Highest

~	not
*, /, %	mult, div, mod
+, -	add, sub
<<, >>	shift
<<<, >>>	arithmetic shift
<, <=, >, >=	comparison
==, !=	equal, not equal
&, ~&	AND, NAND
^, ~^	XOR, XNOR
, ~	OR, NOR
?:	ternary operator

Lowest

Copyright © 2007 Elsevier

4-<16>



Numbers

Format: N'Bvalue

N = number of bits, B = base

N'B is optional but recommended (default is decimal)

Number	# Bits	Base	Decimal Equivalent	Stored
3'b101	3	binary	5	101
'b11	unsized	binary	3	00...0011
8'b11	8	binary	3	00000011
8'b1010_1011	8	binary	171	10101011
3'd6	3	decimal	6	110
6'o42	6	octal	34	100010
8'hAB	8	hexadecimal	171	10101011
42	Unsize	decimal	42	00...0101010

Copyright © 2007 Elsevier

4-<17>



Bit Manipulations: Example 1

```
assign y = {a[2:1], {3{b[0]}}, a[0], 6'b100_010};
```

// if y is a 12-bit signal, the above statement produces:
y = a[2] a[1] b[0] b[0] b[0] a[0] 1 0 0 0 1 0

// underscores (_) are used for formatting only to make it easier to read. Verilog ignores them.

Copyright © 2007 Elsevier

4-<18>




Bit Manipulations: Example 2

Verilog:

```
module mux2_8(input logic [7:0] d0, d1,
             input logic s,
             output logic [7:0] y);

    mux2 lsbmux(d0[3:0], d1[3:0], s, y[3:0]);
    mux2 msbmux(d0[7:4], d1[7:4], s, y[7:4]);
endmodule
```

Synthesis:

 

Copyright © 2007 Elsevier

4-<19>




Z: Floating Output

Verilog:

```
module tristate(input logic [3:0] a,
               input logic en,
               output tri [3:0] y);
    assign y = en ? a : 4'bz;
endmodule
```

Synthesis:

 

Copyright © 2007 Elsevier

4-<20>



Tristate Busses

- logic signals must have exactly one driver
- Tristate busses may have multiple drivers
 - Use tri or trireg
- Typically one driver is active at a time
 - If multiple drivers give conflicting values, bus gets x
 - If no driver is active:
 - tri floats (z)
 - trireg keeps its prior value


Copyright © 2007 Elsevier

4-<21>



Delays

```
module example(input logic a, b, c,
               output logic y);
  logic ab, bb, cb, n1, n2, n3;
  assign #1 {ab, bb, cb} = ~{a, b, c};
  assign #2 n1 = ab & bb & cb;
  assign #2 n2 = a & bb & cb;
  assign #2 n3 = a & bb & c;
  assign #4 y = n1 | n2 | n3;
endmodule
```

 


Copyrig

ELSEVIER

Delays

```
module example(input logic a, b, c,
               output logic y);
  logic ab, bb, cb, n1, n2, n3;
  assign #1 {ab, bb, cb} =
    ~{a, b, c};
  assign #2 n1 = ab & bb & cb;
  assign #2 n2 = a & bb & cb;
  assign #2 n3 = a & bb & c;
  assign #4 y = n1 | n2 | n3;
endmodule
```

 

Copyright © 2007 Elsevier

4-<23>



Sequential Logic

- Verilog uses certain idioms to describe latches, flip-flops and FSMs
- Other coding styles may simulate correctly but produce incorrect hardware

Copyright © 2007 Elsevier

4-<24>



Always Statement

General Structure:

```
always @ (sensitivity list)
    statement;
```

Whenever the event in the sensitivity list occurs, the statement is executed

Specialized Forms:

```
always_ff
always_latch
always_comb
```

Check for common mistakes in the always statement

Copyright © 2007 Elsevier

4-<25>




D Flip-Flop

```
module flop(input logic clk,
            input logic [3:0] d,
            output logic [3:0] q);
```

```
    always_ff @(posedge clk)
        q <= d; // pronounced "q gets d"
```

```
endmodule
```

 

Also could have written

```
always @(posedge clk)
    q <= d;
```

but `always_ff` checks for typos that don't imply a flip-flop.

Copyright © 2007 Elsevier

4-<26>




Resettable D Flip-Flop

```
module flopr(input logic clk,
             input logic reset,
             input logic [3:0] d,
             output logic [3:0] q);
```

```
    // synchronous reset
    always_ff @(posedge clk)
        if (reset) q <= 4'b0;
        else      q <= d;
```

```
endmodule
```

 

Copyright © 2007 Elsevier

4-<27>




Resettable D Flip-Flop

```
module flopr(input logic clk,
             input logic reset,
             input logic [3:0] d,
             output logic [3:0] q);
```

```
    // asynchronous reset
    always_ff @(posedge clk, posedge reset)
        if (reset) q <= 4'b0;
        else      q <= d;
```

```
endmodule
```

 

Copyright © 2007 Elsevier

4-<28>




D Flip-Flop with Enable

```
module flopren(input logic clk,
              input logic reset,
              input logic en,
              input logic [3:0] d,
              output logic [3:0] q);

// asynchronous reset and enable
always_ff @ (posedge clk, posedge reset)
  if (reset) q <= 4'b0;
  else if (en) q <= d;

endmodule
```

 

Copyright © 2007 Elsevier

4-<29>




Latch

```
module latch(input logic clk,
            input logic [3:0] d,
            output logic [3:0] q);
```

```
  always_latch
    if (clk) q <= d;
```

```
endmodule
```

 

```
Also could have written
  always @(clk or d)
    q <= d;
```

but `always_latch` checks for typos that don't imply a latch.

Warning: We won't use latches in this course, but you might write code that inadvertently implies a latch. So if your synthesized hardware has latches in it, this indicates an error.

Copyright © 2007 Elsevier

4-<30>



Other Behavioral Statements

- Statements that must be inside `always` statements:
 - `if/else`
 - `case, casez`

Copyright © 2007 Elsevier

4-<31>



Combinational Logic using `always`

```
// combinational logic using an always statement
module gates(input logic [3:0] a, b,
            output logic [3:0] y1, y2, y3, y4, y5);
  always_comb // need begin/end because there is
  begin // more than one statement in always
    y1 = a & b; // AND
    y2 = a | b; // OR
    y3 = a ^ b; // XOR
    y4 = ~(a & b); // NAND
    y5 = ~(a | b); // NOR
  end
endmodule
```

```
Also could have written
  always @(a or b) ...
  always @(*) ...
```

but `always_comb` checks for typos that don't imply comb logic.

This hardware could be described with `assign` statements using fewer lines of code, so it is better to use `assign` statements in this scenario.

Copyright © 2007 Elsevier

4-<32>



Combinational Logic using **case**

```

module sevenseg(input logic [3:0] data,
                output logic [6:0] segments);

always_comb
  case (data)
    //          abc_defg
    0: segments = 7'b111_1110;
    1: segments = 7'b011_0000;
    2: segments = 7'b110_1101;
    3: segments = 7'b111_1001;
    4: segments = 7'b011_0011;
    5: segments = 7'b101_1011;
    6: segments = 7'b101_1111;
    7: segments = 7'b111_0000;
    8: segments = 7'b111_1111;
    9: segments = 7'b111_1011;
    default: segments = 7'b000_0000; // required
  endcase
endmodule

```

Copyright © 2007 Elsevier

4-<33>



Combinational Logic using **case**

- In order for a **case** statement to imply combinational logic, all possible input combinations must be described by the HDL.
- Remember to use a **default** statement when necessary.

Copyright © 2007 Elsevier

4-<34>



Combinational Logic using **casez**

```


module priority_casez(input logic [3:0] a,
                    output logic [3:0] y);

always_comb
  casez(a)
    4'b1???: y = 4'b1000; // ? = don't care
    4'b01???: y = 4'b0100;
    4'b001?: y = 4'b0010;
    4'b0001?: y = 4'b0001;
    default: y = 4'b0000;
  endcase
endmodule

```

Copyright © 2007 Elsevier

<35>

 

Blocking vs. Nonblocking Assignments

- **<=** is a “nonblocking assignment”
 - Occurs simultaneously with others
- **=** is a “blocking assignment”
 - Occurs in the order it appears in the file

```



// Good synchronizer using // Bad synchronizer using
// nonblocking assignments // blocking assignments
module syncgood(input logic clk, input logic d,
                output logic q);
  logic n1;
  always_ff @(posedge clk)
  begin
    n1 <= d; // nonblocking
    q <= n1; // nonblocking
  end
endmodule

module syncgood(input logic clk, input logic d,
                output logic q);
  logic n1;
  always_ff @(posedge clk)
  begin
    n1 = d; // blocking
    q = n1; // blocking
  end
endmodule

```

Copyright © 2007 Elsevier

4-<36>

  

Rules for Signal Assignment

- Use `always_ff @(posedge clk)` and nonblocking assignments (`<=>`) to model synchronous sequential logic

```
always_ff @(posedge clk)
  q <= d; // nonblocking
```
- Use continuous assignments (`assign ...`) to model simple combinational logic.

```
assign y = a & b;
```
- Use `always_comb` and blocking assignments (`=`) to model more complicated combinational logic where the `always` statement is helpful.
- Do not make assignments to the same signal in more than one `always` statement or continuous assignment statement.

Copyright © 2007 Elsevier

4-<37>



Life Before SystemVerilog

- In the original Verilog standard, `logic` didn't exist
- `wire` and `reg` were used inside
 - `wire` used for signals driven in assign statements
 - `reg` used for signals driven in always blocks
 - Whether or not they are registers (!)
- SystemVerilog avoids this confusing issue
 - But old code with `wire` and `reg` still works


Copyright © 2007 Elsevier

4-<38>



Finite State Machines (FSMs)

 - Three blocks:
 - next state logic
 - state register
 - output logic




Copyright © 2007 Elsevier

4-<39>



FSM Example: Divide by 3

 

The double circle indicates the reset state

Copyright © 2007 Elsevier

4-<40>



FSM in Verilog

```
module divideby3FSM (input logic clk,
                    input logic reset,
                    output logic q);
    logic [1:0] state, nextstate;

    parameter S0 = 2'b00;
    parameter S1 = 2'b01;
    parameter S2 = 2'b10;

    // state register
    always_ff @(posedge clk, posedge reset)
        if (reset) state <= S0;
        else state <= nextstate;
    // next state logic
    always_comb
        case (state)
            S0: nextstate = S1;
            S1: nextstate = S2;
            S2: nextstate = S0;
            default: nextstate = S0;
        endcase
    // output logic
    assign q = (state == S0);
endmodule
```

Copyright © 2007 Elsevier

4-<41>



Parameterized Modules

2:1 mux:

```
module mux2
    #(parameter width = 8) // name and default value
    (input logic [width-1:0] d0, d1,
     input logic s,
     output logic [width-1:0] y);
    assign y = s ? d1 : d0;
endmodule
```

Instance with 8-bit bus width (uses default):

```
mux2 mux1(d0, d1, s, out);
```

Instance with 12-bit bus width:

```
mux2 #(12) lowmux(d0, d1, s, out);
```

Copyright © 2007 Elsevier

4-<42>



Testbenches

- HDL code written to test another HDL module, the *device under test* (dut), also called the *unit under test* (uut)
- Not synthesizable
- Types of testbenches:
 - Simple testbench
 - Self-checking testbench
 - Self-checking testbench with testvectors

Copyright © 2007 Elsevier

4-<43>



Example

Write Verilog code to implement the following function in hardware:

$$y = \overline{b}c + a\overline{b}$$

Name the module sillyfunction

Verilog

```
module sillyfunction(input logic a, b, c,
                    output logic y);
    assign y = ~b & ~c | a & ~b;
endmodule
```

Copyright © 2007 Elsevier

4-<44>



Simple Testbench

```
module testbench1();
  logic a, b, c;
  logic y;
  // instantiate device under test
  sillyfunction dut(a, b, c, y);
  // apply inputs one at a time
  initial begin
    a = 0; b = 0; c = 0; #10;
    c = 1; #10;
    b = 1; c = 0; #10;
    c = 1; #10;
    a = 1; b = 0; c = 0; #10;
    c = 1; #10;
    b = 1; c = 0; #10;
    c = 1; #10;
  end
endmodule
```

Copyright © 2007 Elsevier

4-<45>



Self-checking Testbench

```
module testbench2();
  logic a, b, c;
  logic y;
  // instantiate device under test
  sillyfunction dut(a, b, c, y);
  // apply inputs one at a time
  // checking results
  initial begin
    a = 0; b = 0; c = 0; #10;
    if (y != 1) $display("000 failed.");
    c = 1; #10;
    if (y != 0) $display("001 failed.");
    b = 1; c = 0; #10;
    if (y != 0) $display("010 failed.");
    c = 1; #10;
    if (y != 0) $display("011 failed.");
    a = 1; b = 0; c = 0; #10;
    if (y != 1) $display("100 failed.");
    c = 1; #10;
    if (y != 1) $display("101 failed.");
    b = 1; c = 0; #10;
    if (y != 0) $display("110 failed.");
    c = 1; #10;
    if (y != 0) $display("111 failed.");
  end
endmodule
```

Copyright © 2007 Elsevier

4-<46>



Testbench with Testvectors

- Write testvector file: inputs and expected outputs
- Testbench:
 1. Generate clock for assigning inputs, reading outputs
 2. Read testvectors file into array
 3. Assign inputs, expected outputs
 4. Compare outputs to expected outputs and report errors


Copyright © 2007 Elsevier

4-<47>



Testbench with Testvectors

 - Testbench clock is used to assign inputs (on the rising edge) and compare outputs with expected outputs (on the falling edge).



- The testbench clock may also be used as the clock source for synchronous sequential circuits.

Copyright © 2007 Elsevier

4-<48>



Testvectors File

File: example.tv - contains vectors of abc_yexpected

```
000_1
001_0
010_0
011_0
100_1
101_1
110_0
111_0
```

Copyright © 2007 Elsevier

4-<49>



Testbench: 1. Generate Clock

```
module testbench3();
  logic      clk, reset;
  logic      a, b, c, yexpected;
  logic      y;
  logic [31:0] vectornum, errors; // bookkeeping variables
  logic [3:0] testvectors[10000:0]; // array of testvectors

  // instantiate device under test
  sillyfunction dut(a, b, c, y);

  // generate clock
  always // no sensitivity list, so it always executes
  begin
    clk = 1; #5; clk = 0; #5;
  end
end
```

Copyright © 2007 Elsevier

4-<50>



2. Read Testvectors into Array

```
// at start of test, load vectors
// and pulse reset

initial
  begin
    $readmemb("example.tv", testvectors);
    vectornum = 0; errors = 0;
    reset = 1; #27; reset = 0;
  end
```

```
// Note: $readmemb reads testvector files written in
// hexadecimal
```

Copyright © 2007 Elsevier

4-<51>



3. Assign Inputs and Expected Outputs

```
// apply test vectors on rising edge of clk
always @(posedge clk)
  begin
    #1; {a, b, c, yexpected} = testvectors[vectornum];
  end
```

Copyright © 2007 Elsevier

4-<52>



4. Compare Outputs with Expected Outputs

```
// check results on falling edge of clk
always @(negedge clk)
  if (~reset) begin // skip during reset
    if (y !== yexpected) begin
      $display("Error: inputs = %b", {a, b, c});
      $display("  outputs = %b (%b expected)", y, yexpected);
      errors = errors + 1;
    end
  end

// Note: to print in hexadecimal, use %h. For example,
//       $display("Error: inputs = %h", {a, b, c});
```

Copyright © 2007 Elsevier

4-<53>



4. Compare Outputs with Expected Outputs

```
// increment array index and read next testvector
vectornum = vectornum + 1;
if (testvectors[vectornum] === 4'bx) begin
  $display("%d tests completed with %d errors",
    vectornum, errors);
  $finish;
end
end
endmodule

// Note: === and !== can compare values that are
// 1, 0, x, or z.
```

Copyright © 2007 Elsevier

4-<54>

