

Chapter 7 :: Microarchitecture

Digital Design and Computer Architecture

David Money Harris and Sarah L. Harris

Copyright © 2007 Elsevier

7-<1>



Chapter 7 :: Topics

- **Introduction**
- **Performance Analysis**
- **Single-Cycle Processor**
- **Multicycle Processor**
- **Pipelined Processor**
- **Exceptions**
- **Advanced Microarchitecture**

Copyright © 2007 Elsevier

7-<2>



Introduction

- Microarchitecture: how to implement an architecture in hardware
- Processor:
 - Datapath: functional blocks
 - Control: control signals

Application Software	programs
Operating Systems	device drivers
Architecture	instructions registers
Micro-architecture	datapaths controllers
Logic	adders memories
Digital Circuits	AND gates NOT gates
Analog Circuits	amplifiers filters
Devices	transistors diodes
Physics	electrons

Copyright © 2007 Elsevier

7-<3>



Microarchitecture

- Multiple implementations for a single architecture:
 - Single-cycle
 - Each instruction executes in a single cycle
 - Multicycle
 - Each instruction is broken up into a series of shorter steps
 - Pipelined
 - Each instruction is broken up into a series of steps
 - Multiple instructions execute at once.

Copyright © 2007 Elsevier

7-<4>



Processor Performance

- Program execution time

$$\text{Execution Time} = (\# \text{ instructions})(\text{cycles/instruction})(\text{seconds/cycle})$$

- Definitions:
 - Cycles/instruction = CPI
 - Seconds/cycle = clock period
 - $1/\text{CPI} = \text{Instructions/cycle} = \text{IPC}$
- Challenge is to satisfy constraints of:
 - Cost
 - Power
 - Performance

Copyright © 2007 Elsevier

7-<5>



MIPS Processor

- We consider a subset of MIPS instructions:
 - R-type instructions: and, or, add, sub, slt
 - Memory instructions: lw, sw
 - Branch instructions: beq
- Later consider adding addi and j

Copyright © 2007 Elsevier

7-<6>



Architectural State


- Determines everything about a processor:
 - PC
 - 32 registers
 - Memory

Copyright © 2007 Elsevier

7-<7>



MIPS State Elements

 

Copyright © 2007 Elsevier

7-<8>



Single-Cycle MIPS Processor

- Datapath
- Control


Copyright © 2007 Elsevier

7-<3>



Single-Cycle Datapath: 1w fetch

 - First consider executing 1w
- **STEP 1:** Fetch instruction




Copyright © 2007 Elsevier

7-<10>



Single-Cycle Datapath: 1w register read

 - **STEP 2:** Read source operands from register file




Copyright © 2007 Elsevier

7-<11>



Single-Cycle Datapath: 1w immediate

- **STEP 3:** Sign-extend the immediate

 


Copyright © 2007 Elsevier

7-<12>



Single-Cycle Datapath: 1w address

- **STEP 4:** Compute the memory address

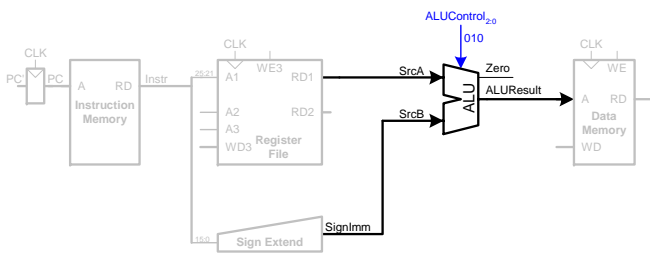


Copyright © 2007 Elsevier

7-<13>



Single-Cycle Datapath: 1w memory read

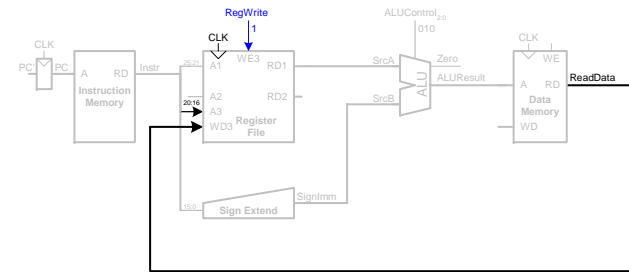- **STEP 5:** Read data from memory and write it back to register file




Copyright © 2007 Elsevier

7-<14>



Single-Cycle Datapath: 1w PC increment

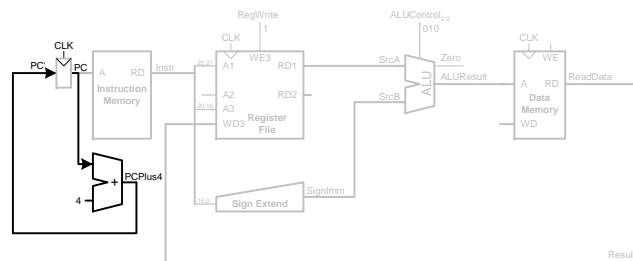- **STEP 6:** Determine the address of the next instruction




Copyright © 2007 Elsevier

7-<15>



Single-Cycle Datapath: sw

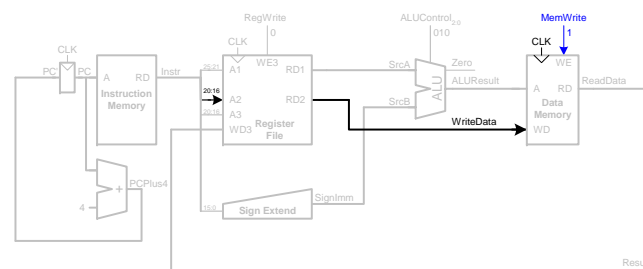- Consider sw
- Need to write data to memory




Copyright © 2007 Elsevier

7-<16>



Single-Cycle Datapath: R-type instructions

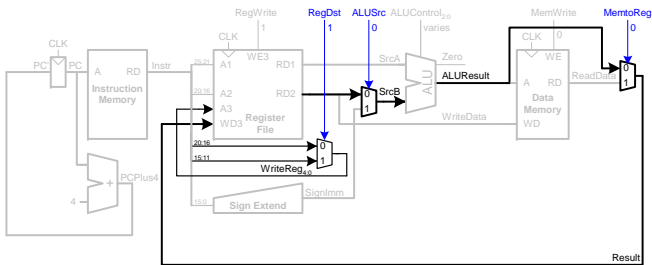- Consider R-type instructions: add, sub, and, or
- Write *ALUResult* to register file
- Writing to *rd* field of instruction (instead of *rt*)




Copyright © 2007 Elsevier

7-<17>



Single-Cycle Datapath: beq

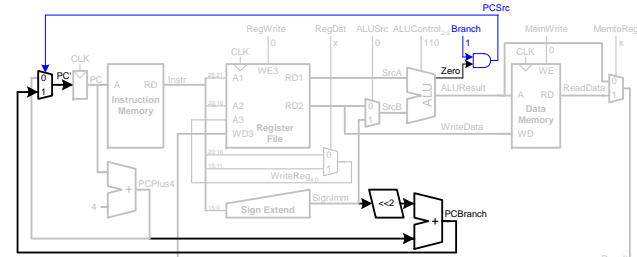- Consider branch instruction: beq
- Determine whether register values are equal
- Calculate branch target address (BTA) from sign-extended immediate and PC+4




Copyright © 2007 Elsevier

7-<18>



Complete Single-Cycle Processor

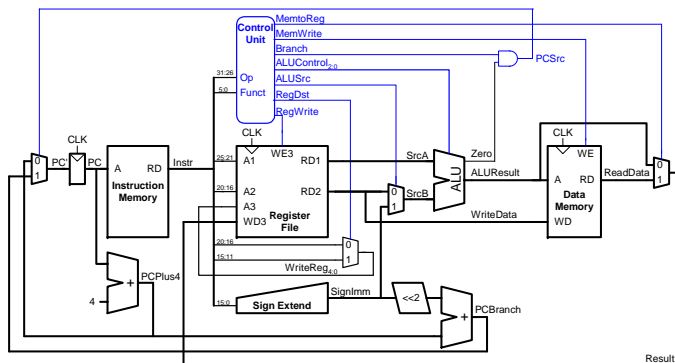


Copyright © 2007 Elsevier

7-<19>



Control Unit

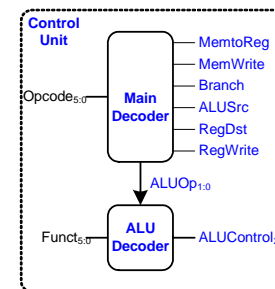


Copyright © 2007 Elsevier

7-<20>



Review: ALU

 


$F_{2:0}$	Function
000	A & B
001	A B
010	A + B
011	not used
100	A & B
101	A ~B
110	A - B
111	SLT

Copyright © 2007 Elsevier

7-<21>



Review: ALU

 

Copyright © 2007 Elsevier

7-<22>



Control Unit: ALU Decoder

ALUOp _{1:0}	Meaning
00	Add
01	Subtract
10	Look at Funct
11	Not Used

ALUOp _{1:0}	Funct	ALUControl _{2:0}
00	X	010 (Add)
X1	X	110 (Subtract)
1X	100000 (add)	010 (Add)
1X	100010 (sub)	110 (Subtract)
1X	100100 (and)	000 (And)
1X	100101 (or)	001 (Or)
1X	101010 (slt)	111 (SLT)


Copyright © 2007 Elsevier

7-<23>



Control Unit: Main Decoder

Instruction	Op _{5:0}	RegWrite	RegDst	AluSrc	Branch	MemWrite	MemoReg	ALUOp _{1:0}
R-type	000000							
lw	100011							
sw	101011							
beq	000100							

 

Copyright © 2007 Elsevier

7-<24>



Control Unit: Main Decoder


Instruction	Op _{5:0}	RegWrite	RegDst	AluSrc	Branch	MemWrite	MemoReg	ALUOp _{1:0}
R-type	000000	1	1	0	0	0	0	10
lw	100011	1	0	1	0	0	0	00
sw	101011	0	X	1	0	1	X	00
beq	000100	0	X	0	1	0	X	01

Copyright © 2007 Elsevier

7-25>



Single-Cycle Datapath Example: or

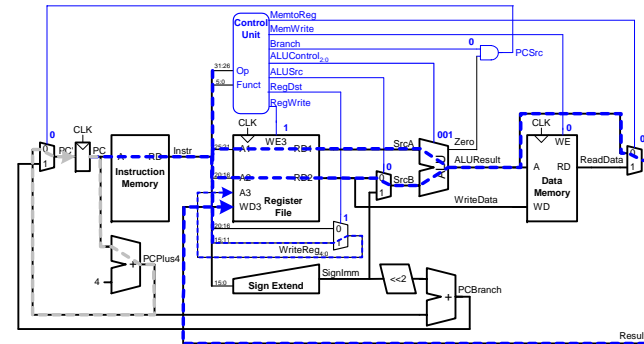


Copyright © 2007 Elsevier

7-26>



Extended Functionality: addi

- No change to datapath

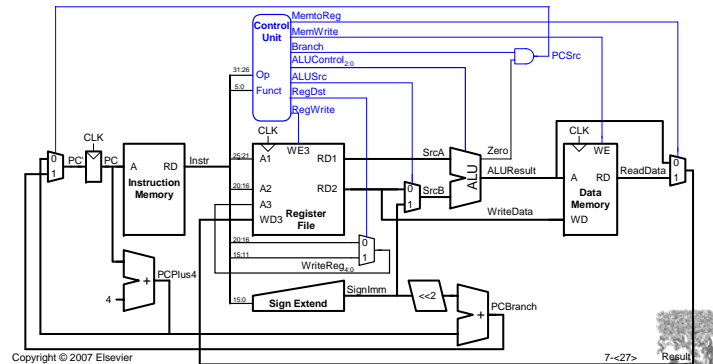

Copyright © 2007 Elsevier

7-27>



Control Unit: addi

Instruction	Op _{5:0}	RegWrite	RegDst	AluSrc	Branch	MemWrite	MemoReg	ALUOp _{1:0}
R-type	000000	1	1	0	0	0	0	10
lw	100011	1	0	1	0	0	1	00
sw	101011	0	X	1	0	1	X	00
beq	000100	0	X	0	1	0	X	01
addi	001000							

Copyright © 2007 Elsevier

7-28>



Control Unit: addi


Instruction	Op _{5:0}	RegWrite	RegDst	AluSrc	Branch	MemWrite	MemoReg	ALUOp _{1:0}
R-type	000000	1	1	0	0	0	0	10
lw	100011	1	0	1	0	0	1	00
sw	101011	0	X	1	0	1	X	00
beq	000100	0	X	0	1	0	X	01
addi	001000	1	0	1	0	0	0	00

Copyright © 2007 Elsevier

7-<29>



Extended Functionality: j

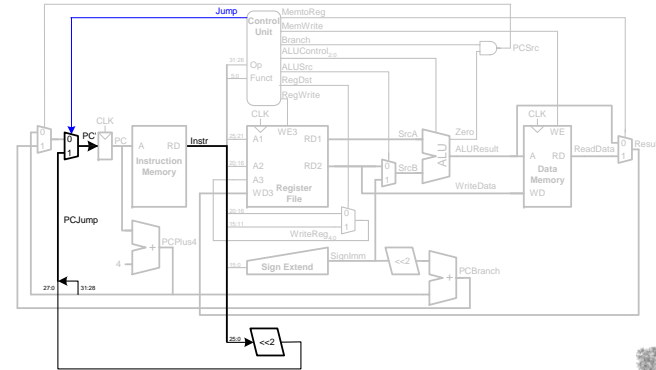

Copyright © 2007 Elsevier

7-<30>



Control Unit: Main Decoder

Instruction	Op _{5:0}	RegWrite	RegDst	AluSrc	Branch	MemWrite	MemoReg	ALUOp _{1:0}	Jump
R-type	000000	1	1	0	0	0	0	10	0
lw	100011	1	0	1	0	0	1	00	0
sw	101011	0	X	1	0	1	X	00	0
beq	000100	0	X	0	1	0	X	01	0
j	000100								

Copyright © 2007 Elsevier

7-<31>



Control Unit: Main Decoder

Instruction	Op _{5:0}	RegWrite	RegDst	AluSrc	Branch	MemWrite	MemoReg	ALUOp _{1:0}	Jump
R-type	000000	1	1	0	0	0	0	10	0
lw	100011	1	0	1	0	0	1	00	0
sw	101011	0	X	1	0	1	X	00	0
beq	000100	0	X	0	1	0	X	01	0
j	000100	0	X	X	X	0	X	XX	1


Copyright © 2007 Elsevier

7-<32>



Single-Cycle Performance

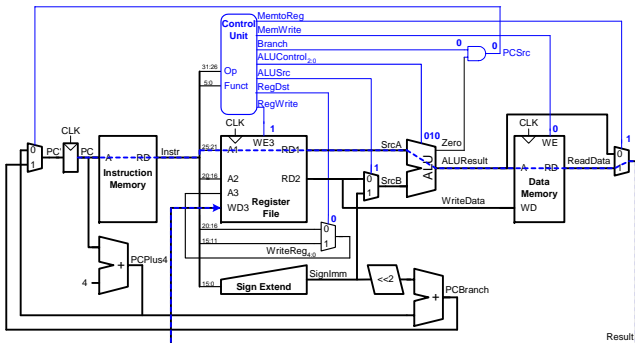- Clock cycle time is limited by the critical path (1w)



Copyright © 2007 Elsevier

7-<33>



Single-Cycle Performance

- Single-cycle critical path:

$$T_c = t_{pcq_PC} + t_{mem} + \max(t_{Rfread}, t_{setup}) + t_{mux} + t_{ALU} + t_{mem} + t_{mux} + t_{RFsetup}$$

- In most implementations, limiting paths are:

- memory, ALU, register file.
- $T_c = t_{pcq_PC} + 2t_{mem} + t_{Rfread} + 2t_{mux} + t_{ALU} + t_{RFsetup}$

Copyright © 2007 Elsevier

7-<34>



Single-Cycle Performance Example

Element	Parameter	Delay (ps)
Register clock-to-Q	t_{pcq_PC}	30
Register setup	t_{setup}	20
Multiplexer	t_{mux}	25
ALU	t_{ALU}	200
Memory read	t_{mem}	250
Register file read	t_{Rfread}	150
Register file setup	$t_{RFsetup}$	20

$$T_c =$$

Copyright © 2007 Elsevier

7-<35>



Single-Cycle Performance Example

Element	Parameter	Delay (ps)
Register clock-to-Q	t_{pcq_PC}	30
Register setup	t_{setup}	20
Multiplexer	t_{mux}	25
ALU	t_{ALU}	200
Memory read	t_{mem}	250
Register file read	t_{Rfread}	150
Register file setup	$t_{RFsetup}$	20

$$\begin{aligned} T_c &= t_{pcq_PC} + 2t_{mem} + t_{Rfread} + 2t_{mux} + t_{ALU} + t_{RFsetup} \\ &= [30 + 2(250) + 150 + 2(25) + 200 + 20] \text{ ps} \\ &= 950 \text{ ps} \end{aligned}$$

Copyright © 2007 Elsevier

7-<36>



Single-Cycle Performance Example

- For a program with 100 billion instructions executing on a single-cycle MIPS processor,

Execution Time =

Copyright © 2007 Elsevier

7-<37>



Single-Cycle Performance Example

- For a program with 100 billion instructions executing on a single-cycle MIPS processor,

$$\begin{aligned} \text{Execution Time} &= (\# \text{ instructions})(\text{cycles/instruction})(\text{seconds/cycle}) \\ &= (100 \times 10^9)(1)(950 \times 10^{-12} \text{ s}) \\ &= 95 \text{ seconds} \end{aligned}$$

Copyright © 2007 Elsevier

7-<38>



Multicycle MIPS Processor

- The single-cycle microarchitecture performs all steps in one cycle
 - + simple
 - cycle time limited by longest instruction (1w)
 - two adders and two memories
- Multicycle microarchitecture uses a variable number of shorter steps (ALU or memory)
 - + higher clock speed
 - + simpler instructions run faster
 - + reuse expensive hardware on multiple cycles
 - sequencing overhead paid many times
- Same design steps: datapath & control


Copyright © 2007 Elsevier

7-<39>



Multicycle State Elements

 - Replace Instruction and Data memories with a single unified memory
 - More realistic




Copyright © 2007 Elsevier

7-<40>



Multicycle Datapath: instruction fetch

 - First consider executing lw
- **STEP 1:** Fetch instruction




Copyright © 2007 Elsevier

7-<41>



Multicycle Datapath: 1w register read

 


Copyright © 2007 Elsevier

7-<42>



Multicycle Datapath: 1w immediate

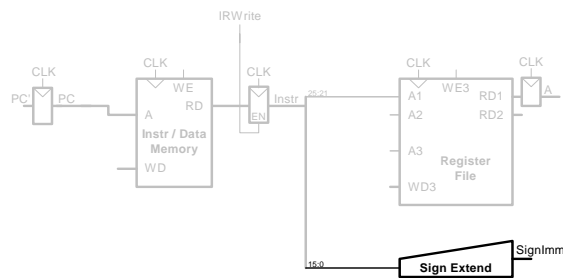


Copyright © 2007 Elsevier

7-<43>



Multicycle Datapath: 1w address

 


Copyright © 2007 Elsevier

7-<44>



Multicycle Datapath: 1w memory read

 


Copyright © 2007 Elsevier

7-<45>



Multicycle Datapath: 1w write register

 


Copyright © 2007 Elsevier

7-<46>



Multicycle Datapath: increment PC

 


Copyright © 2007 Elsevier

7-<47>



Multicycle Datapath: sw

 - Consider sw
- Need to write data to memory




Copyright © 2007 Elsevier

7-<48>



Multicycle Datapath: R-type Instructions

 - Consider R-type instructions: add, sub, and, or
- Write *ALUResult* to register file
- Writing to *rd* field of instruction (instead of *rt*)




Copyright © 2007 Elsevier

7-49>



Multicycle Datapath: beq

 - Consider branch instruction: beq
- Determine whether register values are equal
- Calculate branch target address (BTA) from sign-extended immediate and PC+4




Copyright © 2007 Elsevier

7-50>



Complete Multicycle Processor

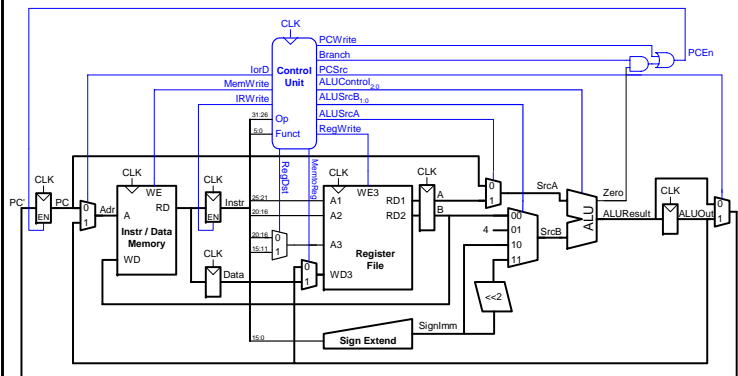


Copyright © 2007 Elsevier

7-51>



Control Unit


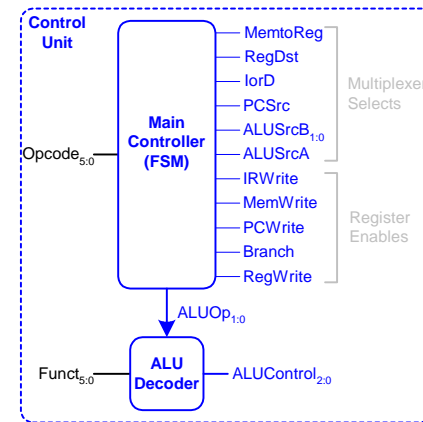


Copyright © 2007 Elsevier

7-52>



Main Controller FSM: Fetch

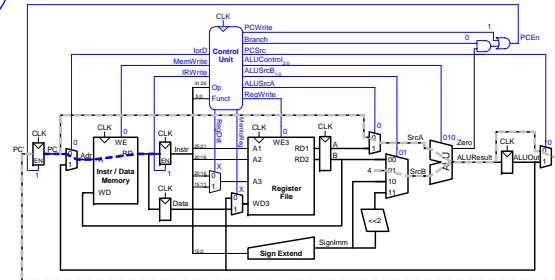
 


Copyright © 2007 Elsevier

7-<55>



Main Controller FSM: Fetch

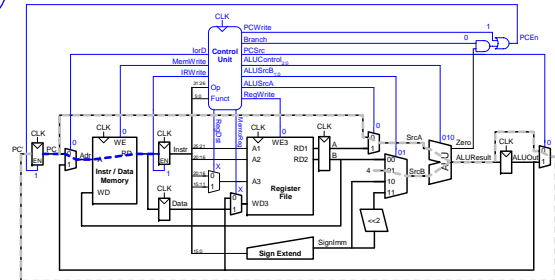
 


Copyright © 2007 Elsevier

7-<54>



Main Controller FSM: Decode

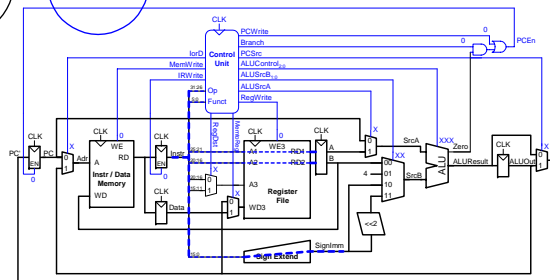
 


Copyright © 2007 Elsevier

7-<55>



Main Controller FSM: Address Calculation

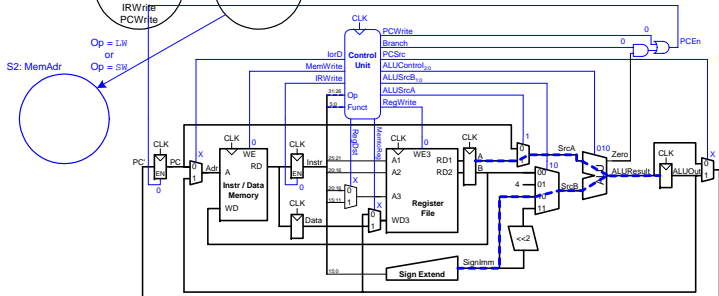 


Copyright © 2007 Elsevier


7-<56>




Main Controller FSM: Address Calculation

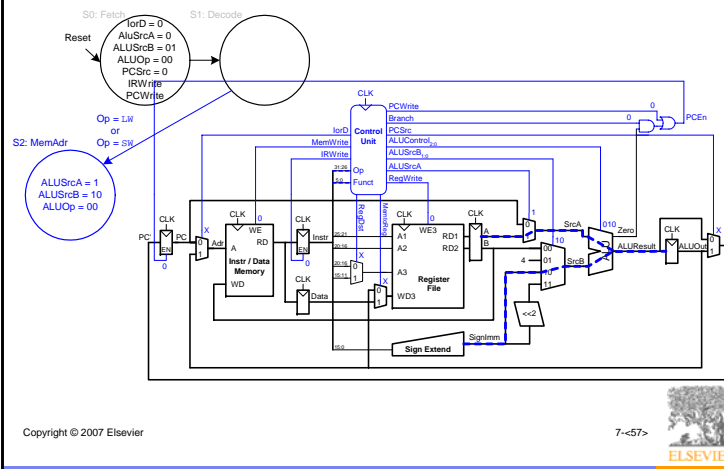


Main Controller FSM: 1w

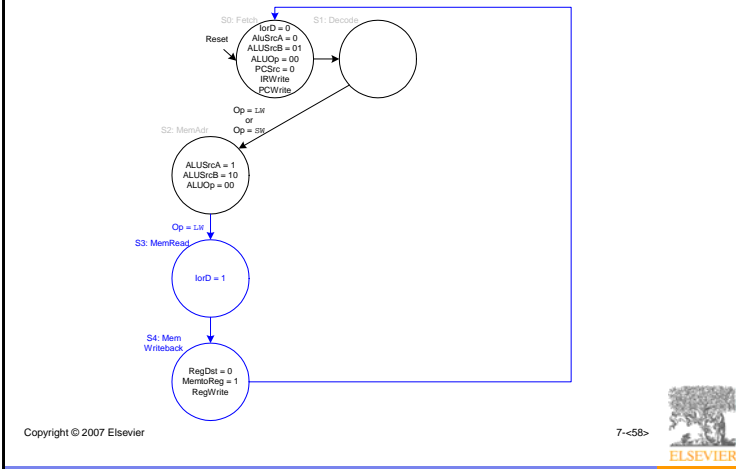


Main Controller FSM: sw

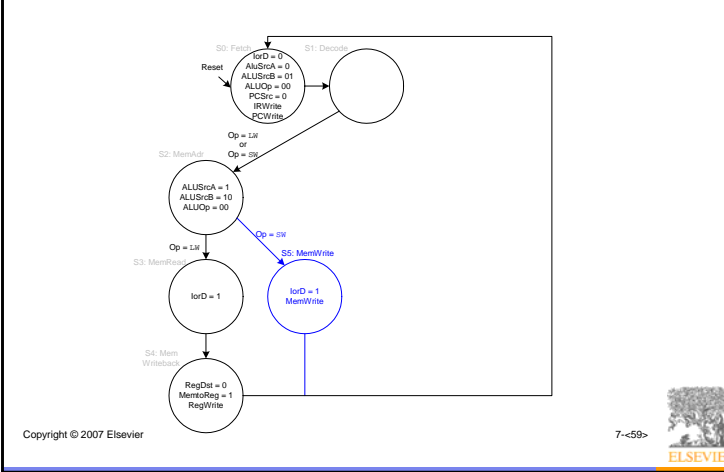

Main Controller FSM: R-Type

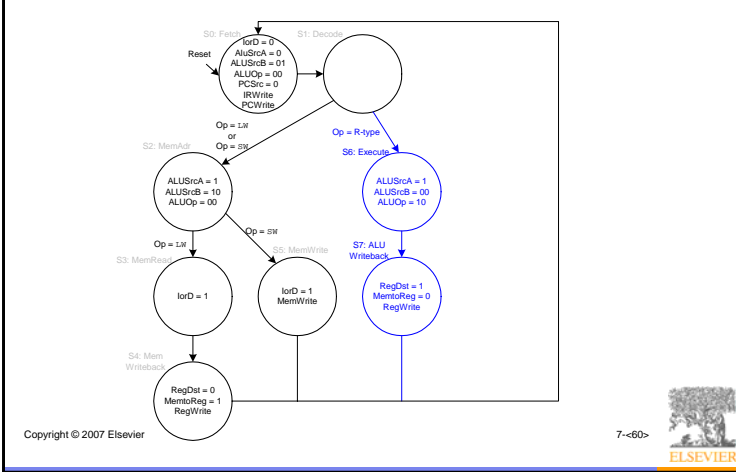

Main Controller FSM: beq

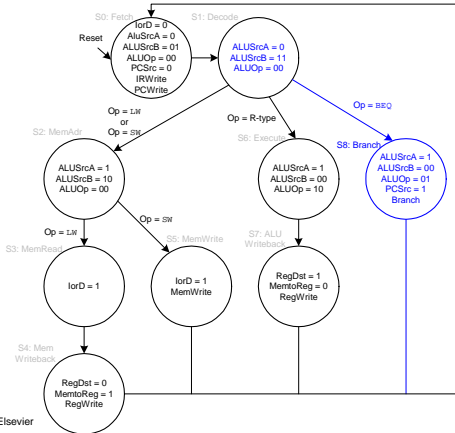


Copyright © 2007 Elsevier

7-61>



Complete Multicycle Controller FSM

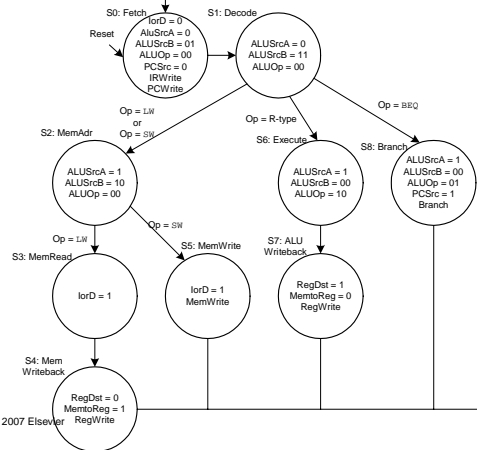


Copyright © 2007 Elsevier

7-62>



Main Controller FSM: addi

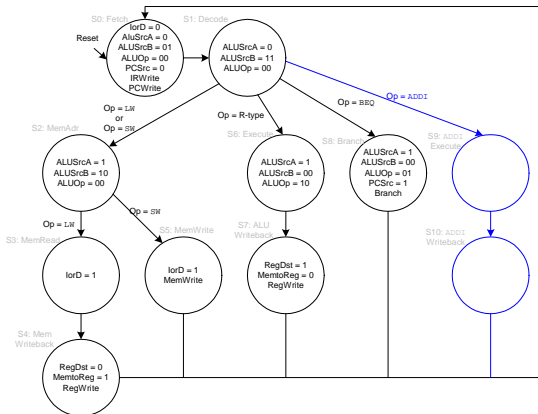


Copyright © 2007 Elsevier

7-63>



Main Controller FSM: addi

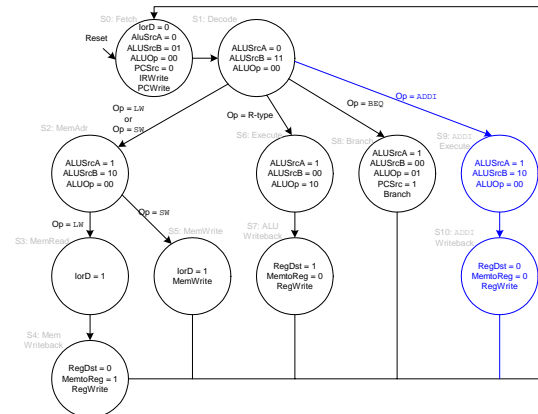


Copyright © 2007 Elsevier

7-64>



Extended Functionality: j

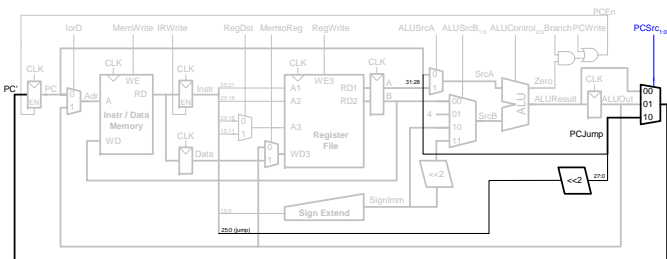


Copyright © 2007 Elsevier

7-65>



Control FSM: j

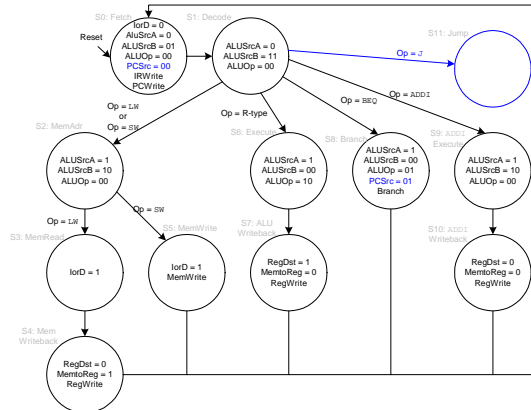


Copyright © 2007 Elsevier

7-66>



Control FSM: j

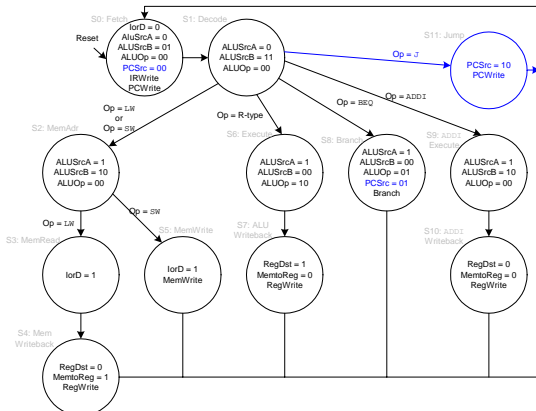

Copyright © 2007 Elsevier

7-67>



Multicycle Performance

- Instructions take different number of cycles:
 - 3 cycles: beq, j
 - 4 cycles: R-Type, sw, addi
 - 5 cycles: lw
- CPI is weighted average
- SPECINT2000 benchmark:
 - 25% loads
 - 10% stores
 - 11% branches
 - 2% jumps
 - 52% R-type

$$\text{Average CPI} = (0.11 + 0.2)(3) + (0.52 + 0.10)(4) + (0.25)(5) = 4.12$$

Copyright © 2007 Elsevier


7-68>



Multicycle Performance

- Multicycle critical path:

$$T_c =$$

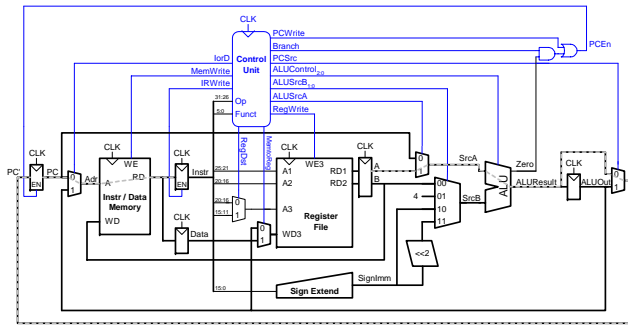

Copyright © 2007 Elsevier


7-69>



Multicycle Performance

- Multicycle critical path:
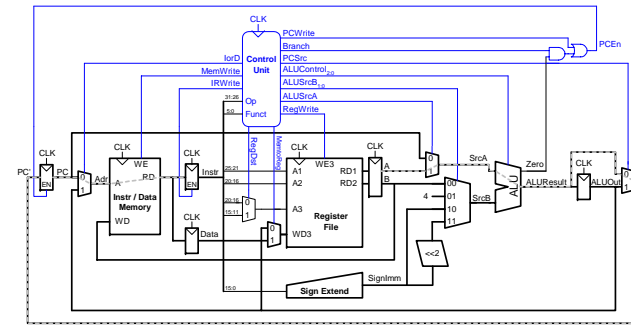
$$T_c = t_{pcq} + t_{mux} + \max(t_{ALU} + t_{mux}, t_{mem}) + t_{setup}$$



Copyright © 2007 Elsevier

7-70>



Multicycle Performance Example

Element	Parameter	Delay (ps)
Register clock-to-Q	t_{pcq}	30
Register setup	t_{setup}	20
Multiplexer	t_{mux}	25
ALU	t_{ALU}	200
Memory read	t_{mem}	250
Register file read	t_{RFread}	150
Register file setup	$t_{RFsetup}$	20

$$T_c =$$

Copyright © 2007 Elsevier

7-71>



Multicycle Performance Example

Element	Parameter	Delay (ps)
Register clock-to-Q	t_{pcq_PC}	30
Register setup	t_{setup}	20
Multiplexer	t_{mux}	25
ALU	t_{ALU}	200
Memory read	t_{mem}	250
Register file read	t_{RFread}	150
Register file setup	$t_{RFsetup}$	20

$$\begin{aligned} T_c &= t_{pcq_PC} + t_{mux} + \max(t_{ALU} + t_{mux}, t_{mem}) + t_{setup} \\ &= t_{pcq_PC} + t_{mux} + t_{mem} + t_{setup} \\ &= [30 + 25 + 250 + 20] \text{ ps} \\ &= 325 \text{ ps} \end{aligned}$$

Copyright © 2007 Elsevier

7-72>



Multicycle Performance Example

- For a program with 100 billion instructions executing on a multicycle MIPS processor
 - CPI = 4.12
 - $T_c = 325$ ps

Execution Time =

Copyright © 2007 Elsevier

7-<73>



Multicycle Performance Example

- For a program with 100 billion instructions executing on a multicycle MIPS processor
 - CPI = 4.12
 - $T_c = 325$ ps

$$\begin{aligned} \text{Execution Time} &= (\# \text{ instructions}) \times \text{CPI} \times T_c \\ &= (100 \times 10^9)(4.12)(325 \times 10^{-12}) \\ &= 133.9 \text{ seconds} \end{aligned}$$

- This is **slower** than the single-cycle processor (95 seconds). Why?

Copyright © 2007 Elsevier

7-<74>



Multicycle Performance Example

- For a program with 100 billion instructions executing on a multicycle MIPS processor
 - CPI = 4.12
 - $T_c = 325$ ps

$$\begin{aligned} \text{Execution Time} &= (\# \text{ instructions}) \times \text{CPI} \times T_c \\ &= (100 \times 10^9)(4.12)(325 \times 10^{-12}) \\ &= 133.9 \text{ seconds} \end{aligned}$$


- This is **slower** than the single-cycle processor (95 seconds). Why?
 - Not all steps the same length
 - Sequencing overhead for each step ($t_{pcq} + t_{\text{setup}} = 50$ ps)

Copyright © 2007 Elsevier

7-<75>



Review: Single-Cycle MIPS Processor

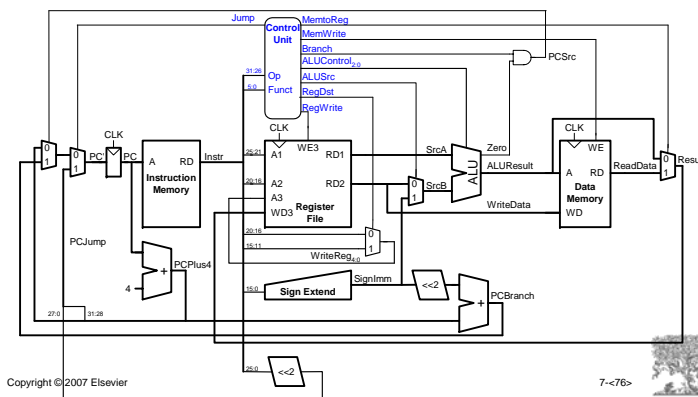


Copyright © 2007 Elsevier

7-<76>



Review: Multicycle MIPS Processor

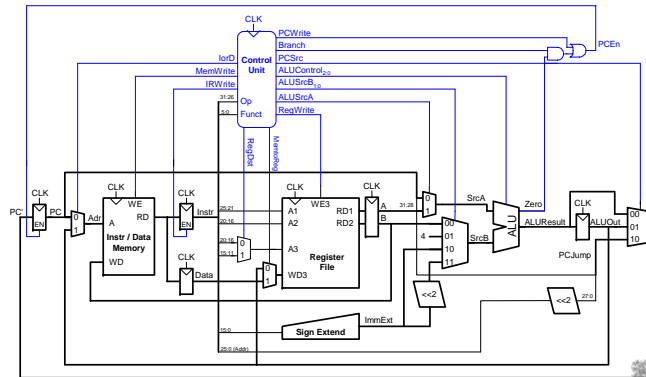

Copyright © 2007 Elsevier

7-477



Pipelined MIPS Processor


- Temporal parallelism
- Divide single-cycle processor into 5 stages:
 - Fetch
 - Decode
 - Execute
 - Memory
 - Writeback
- Add pipeline registers between stages

Copyright © 2007 Elsevier

7-478



Single-Cycle vs. Pipelined Performance

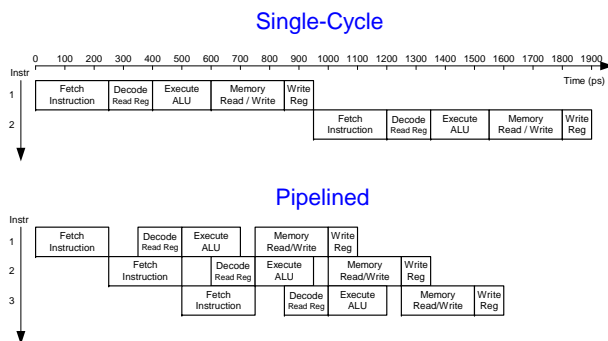


Copyright © 2007 Elsevier

7-479



Pipelining Abstraction

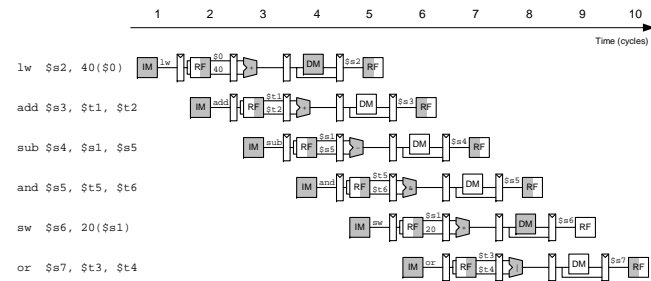


Copyright © 2007 Elsevier

7-480



Single-Cycle and Pipelined Datapath

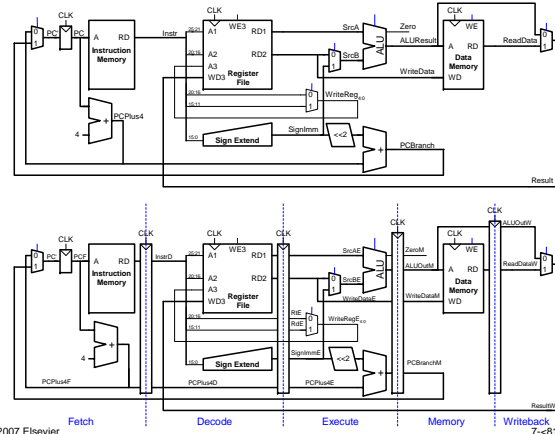


Copyright © 2007 Elsevier



Corrected Pipelined Datapath

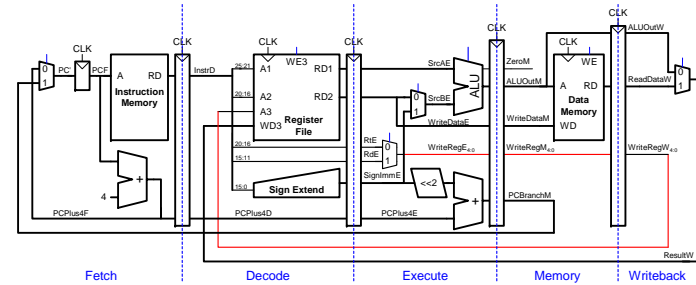- WriteReg must arrive at the same time as Result




Copyright © 2007 Elsevier

7-82>



Pipelined Control

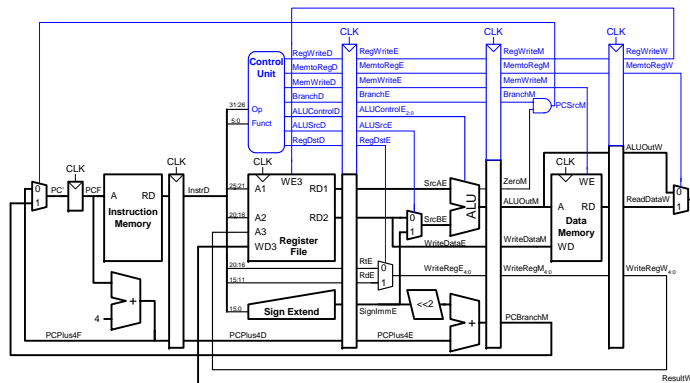

Same control unit as single-cycle processor

Control delayed to proper pipeline stage

Copyright © 2007 Elsevier

7-83>



Pipeline Hazard


- Occurs when an instruction depends on results from previous instruction that hasn't completed.
- Types of hazards:
 - **Data hazard:** register value not written back to register file yet
 - **Control hazard:** next instruction not decided yet (caused by branches)

Copyright © 2007 Elsevier

7-84>



Data Hazard

 

Copyright © 2007 Elsevier

7-<85>



Handling Data Hazards

- Insert nops in code at compile time
- Rearrange code at compile time
- Forward data at run time
- Stall the processor at run time


Copyright © 2007 Elsevier

7-<86>



Compile-Time Hazard Elimination

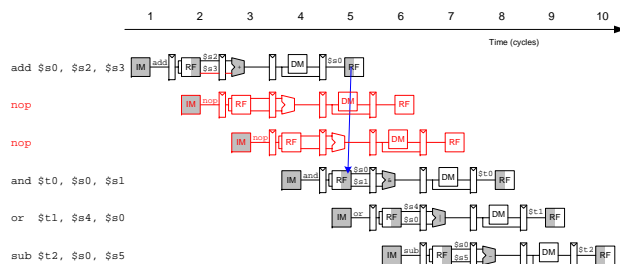- Insert enough nops for result to be ready
- Or move independent useful instructions forward




Copyright © 2007 Elsevier

7-<87>



Data Forwarding

 


Copyright © 2007 Elsevier

7-<88>



Data Forwarding

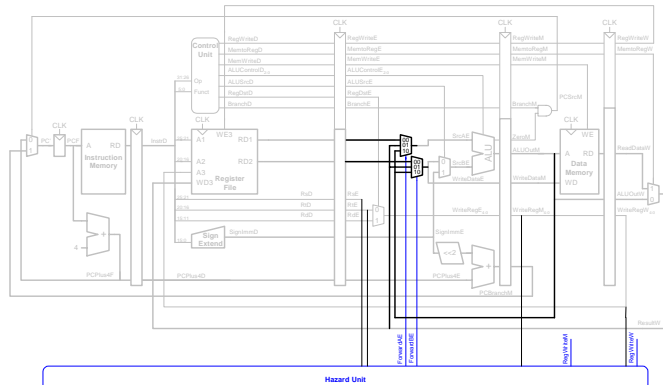

Copyright © 2007 Elsevier

7-89>



Data Forwarding

- Forward to Execute stage from either:
 - Memory stage or
 - Writeback stage

- Forwarding logic for *ForwardAE*:

```

if ((rsE != 0) AND (rsE == WriteRegM) AND RegWriteM)
then ForwardAE = 10
else if ((rsE != 0) AND (rsE == WriteRegW) AND RegWriteW)
then ForwardAE = 01
else ForwardAE = 00
    
```


- Forwarding logic for *ForwardBE* same, but replace *rsE* with *rtE*

Copyright © 2007 Elsevier

7-90>



Stalling

 


Copyright © 2007 Elsevier

7-91>



Stalling

 


Copyright © 2007 Elsevier

7-92>



Stalling Hardware

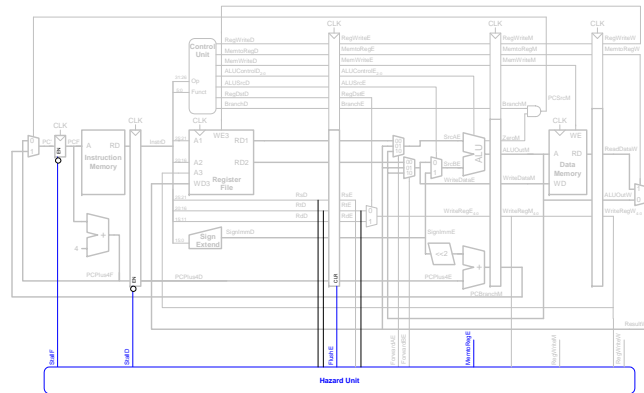

Copyright © 2007 Elsevier

7-93>



Stalling Hardware

- Stalling logic:

$$lwstall = ((rsD == rtE) \text{ OR } (rtD == rtE)) \text{ AND } MemtoRegE$$

$$StallF = StallD = FlushE = lwstall$$

Copyright © 2007 Elsevier

7-94>



Control Hazards


- beq:
 - branch is not determined until the fourth stage of the pipeline
 - Instructions after the branch are fetched before branch occurs
 - These instructions must be flushed if the branch happens
- Branch misprediction penalty
 - number of instruction flushed when branch is taken
 - May be reduced by determining branch earlier

Copyright © 2007 Elsevier

7-95>




Control Hazards: Original Pipeline

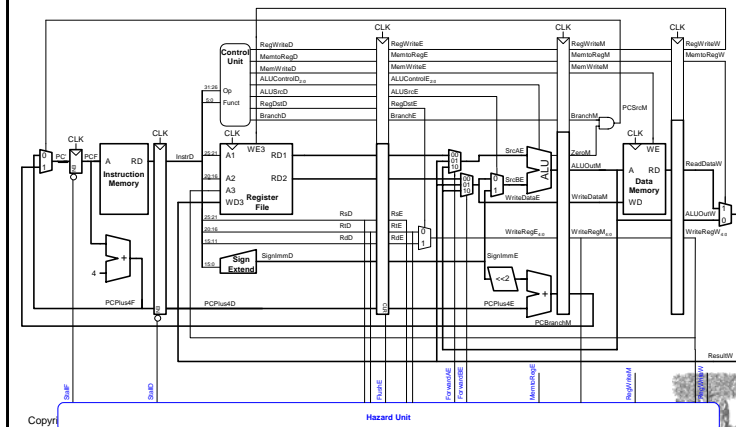

Copy



Control Hazards

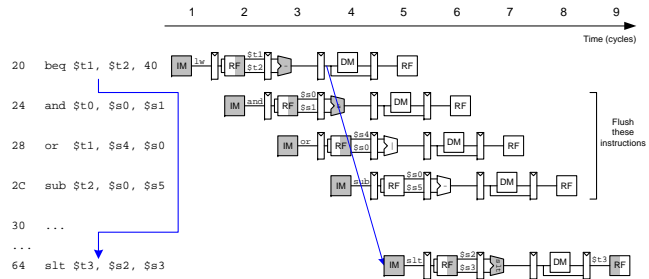


Copyright © 2007 Elsevier

7-69>




Control Hazards: Early Branch Resolution

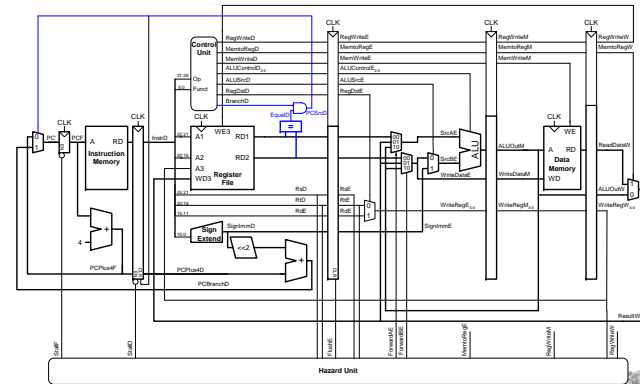

Copyright © 2007 Elsevier Introduced another data hazard in Decode stage 7-69>



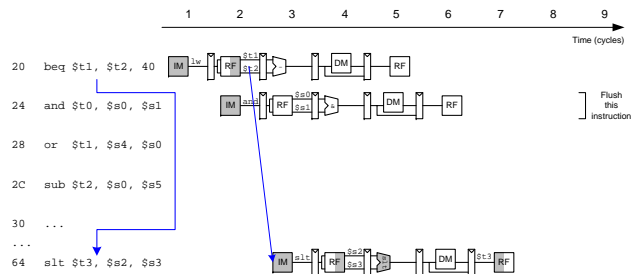Control Hazards with Early Branch Resolution




Copyright © 2007 Elsevier

7-69>



Handling Data and Control Hazards

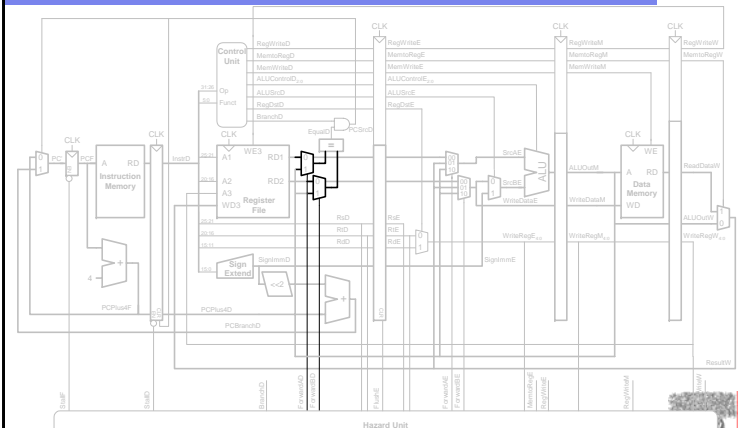

Copyright © 2007 Elsevier



Control Forwarding and Stalling Hardware

- Forwarding logic:

```
ForwardAD = (rsD != 0) AND (rsD == WriteRegM) AND RegWriteM  
ForwardBD = (rtD != 0) AND (rtD == WriteRegM) AND RegWriteM
```

- Stalling logic:

```
branchstall = BranchD AND RegWriteE AND  
              (WriteRegE == rsD OR WriteRegE == rtD)  
OR  
BranchD AND MemtoRegM AND  
              (WriteRegM == rsD OR WriteRegM == rtD)  
  
StallF = StallD = FlushE = lwstall OR branchstall
```

Copyright © 2007 Elsevier

7-<101>



Branch Prediction

- Guess whether branch will be taken
 - Backward branches are usually taken (loops)
 - Perhaps consider history of whether branch was previously taken to improve the guess
- Good prediction reduces the fraction of branches requiring a flush

Copyright © 2007 Elsevier

7-<102>



Pipelined Performance Example

- Ideally CPI = 1
- But need to handle stalling (caused by loads and branches)
- SPECINT2000 benchmark:
 - 25% loads
 - 10% stores
 - 11% branches
 - 2% jumps
 - 52% R-type
- Suppose:
 - 40% of loads used by next instruction
 - 25% of branches mispredicted
- **What is the average CPI?**

Copyright © 2007 Elsevier

7-<103>



Pipelined Performance Example

- SPECINT2000 benchmark:
 - 25% loads
 - 10% stores
 - 11% branches
 - 2% jumps
 - 52% R-type
- Suppose:
 - 40% of loads used by next instruction
 - 25% of branches mispredicted
 - All jumps flush next instruction
- **What is the average CPI?**
 - Load/Branch CPI = 1 when no stalling, 2 when stalling. Thus,
 - $CPI_{lw} = 1(0.6) + 2(0.4) = 1.4$
 - $CPI_{beq} = 1(0.75) + 2(0.25) = 1.25$
 - Thus,

$$\text{Average CPI} = (0.25)(1.4) + (0.1)(1) + (0.11)(1.25) + (0.02)(2) + (0.52)(1) = 1.15$$

Copyright © 2007 Elsevier

7-<104>



Pipelined Performance

- Pipelined processor critical path:

$$T_c = \max \{$$

$$t_{pcq} + t_{mem} + t_{setup}$$

$$2(t_{RFread} + t_{mux} + t_{eq} + t_{AND} + t_{mux} + t_{setup})$$

$$t_{pcq} + t_{mux} + t_{mux} + t_{ALU} + t_{setup}$$

$$t_{pcq} + t_{memwrite} + t_{setup}$$

$$2(t_{pcq} + t_{mux} + t_{RFwrite}) \}$$

Copyright © 2007 Elsevier

7-<105>



Pipelined Performance Example

Element	Parameter	Delay (ps)
Register clock-to-Q	t_{pcq_PC}	30
Register setup	t_{setup}	20
Multiplexer	t_{mux}	25
ALU	t_{ALU}	200
Memory read	t_{mem}	250
Register file read	t_{RFread}	150
Register file setup	$t_{RFsetup}$	20
Equality comparator	t_{eq}	40
AND gate	t_{AND}	15
Memory write	$T_{memwrite}$	220
Register file write	$t_{RFwrite}$	100 ps

$$T_c = 2(t_{RFread} + t_{mux} + t_{eq} + t_{AND} + t_{mux} + t_{setup})$$

$$= 2[150 + 25 + 40 + 15 + 25 + 20] \text{ ps} = \mathbf{550 \text{ ps}}$$

Copyright © 2007 Elsevier

7-<106>



Pipelined Performance Example

- For a program with 100 billion instructions executing on a pipelined MIPS processor,
- CPI = 1.15
- $T_c = 550 \text{ ps}$

$$\text{Execution Time} = (\# \text{ instructions}) \times \text{CPI} \times T_c$$

$$= (100 \times 10^9)(1.15)(550 \times 10^{-12})$$

$$= \mathbf{63 \text{ seconds}}$$

Processor	Execution Time (seconds)	Speedup (single-cycle is baseline)
Single-cycle	95	1
Multicycle	133	0.71
Pipelined	63	1.51

Copyright © 2007 Elsevier

7-<107>



Review: Exceptions

- Unscheduled procedure call to the *exception handler*
- Casued by:
 - Hardware, also called an *interrupt*, e.g. keyboard
 - Software, also called *traps*, e.g. undefined instruction
- When exception occurs, the processor:
 - Records the cause of the exception (Cause register)
 - Jumps to the exception handler at instruction address 0x80000180
 - Returns to program (EPC register)

Copyright © 2007 Elsevier

7-<108>





Example Exception

sequential circuits.]

Can we design a spiff

Figure 2.11 shows a
inputs, A and B, and on
box indicates that it is
this case, the function is

 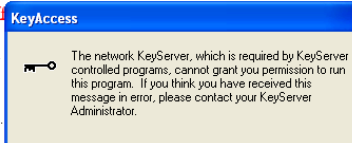

words, we say the output Y is a function of the two inputs A and B where
the function performed is A OR B.]

The implementation of the combinational circuit is independent of its
functionality Figure 2.1 and Figure 2.2 show two possible implementations.

Copyright © 2007 Elsevier

7-<109>



Exception Registers

- Not part of the register file.
 - Cause
 - Records the cause of the exception
 - Coprocessor 0 register 13
 - EPC (Exception PC)
 - Records the PC where the exception occurred
 - Coprocessor 0 register 14
- Move from Coprocessor 0
 - `mfc0 $t0, Cause`
 - Moves the contents of Cause into \$t0

mfc0

010000	00000	\$t0 (8)	Cause (13)	00000000000
31:26	25:21	20:16	15:11	10:0

Copyright © 2007 Elsevier

7-<110>



Exception Causes

Exception	Cause
Hardware Interrupt	0x00000000
System Call	0x00000020
Breakpoint / Divide by 0	0x00000024
Undefined Instruction	0x00000028
Arithmetic Overflow	0x00000030


We extend the multicycle MIPS processor
to handle the last two types of exceptions.

Copyright © 2007 Elsevier

7-<111>



Exception Hardware: EPC & Cause

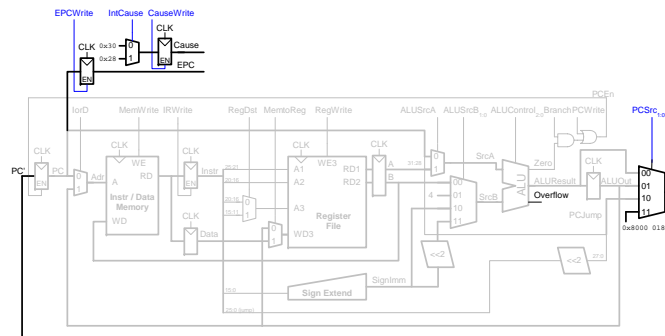


Copyright © 2007 Elsevier

7-<112>



Exception Hardware: mfc0

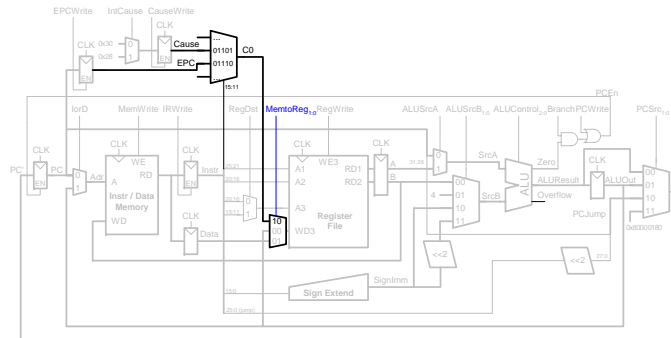


Copyright © 2007 Elsevier

7-<113>



Control FSM with Exceptions

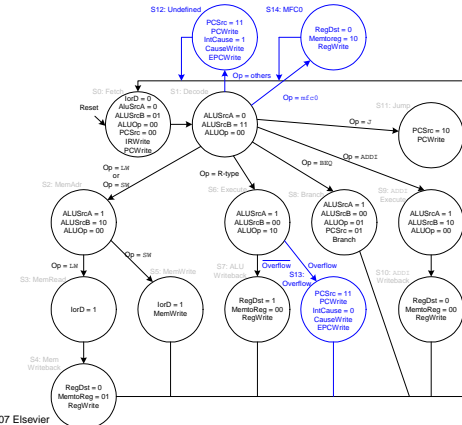

Copyright © 2007 Elsevier

7-<114>



Advanced MicroArchitecture

- Deep Pipelining
- Branch Prediction
- Superscalar Processors
- Out of Order Processors
- Register Renaming
- SIMD
- Multithreading
- Multiprocessors

Copyright © 2007 Elsevier

7-<115>



Deep Pipelining

- 10-20 stages typical
- Number of stages limited by:
 - Pipeline hazards
 - Sequencing overhead
 - Power
 - Cost

Copyright © 2007 Elsevier

7-<116>



Branch Prediction

- Ideal pipelined processor: CPI = 1
- Branch misprediction increases CPI
- Static branch prediction:
 - Check direction of branch (forward or backward)
 - If backward, predict taken
 - Otherwise, predict not taken
- Dynamic branch prediction:
 - Keep history of last (several hundred) branches in a *branch target buffer* which holds:
 - Branch destination
 - Whether branch was taken

Copyright © 2007 Elsevier

7-<117>



Branch Prediction Example

```
add $s1, $0, $0    # sum = 0
add $s0, $0, $0    # i = 0
addi $t0, $0, 10   # $t0 = 10
for:
  beq $t0, $t0, done # if i == 10, branch
  add $s1, $s1, $s0  # sum = sum + i
  addi $s0, $s0, 1   # increment i
  j    for
done:
```

Copyright © 2007 Elsevier

7-<118>



1-Bit Branch Predictor

- Remembers whether branch was taken the last time and does the same thing
- Mispredicts first and last branch of loop


Copyright © 2007 Elsevier

7-<119>



2-Bit Branch Predictor

- Only mispredicts last branch of loop

 


Copyright © 2007 Elsevier

7-<120>



Superscalar

 - Multiple copies of datapath execute multiple instructions at once
- Dependencies make it tricky to issue multiple instructions at once



Copyright © 2007 Elsevier


7-<121>



Superscalar Example

```
lw $t0, 40($s0)
add $t1, $t0, $s1
sub $t0, $s2, $s3
and $t2, $s4, $t0
or $t3, $s5, $s6
sw $s7, 80($t3)
```

Ideal IPC: 2
Actual IPC: 2

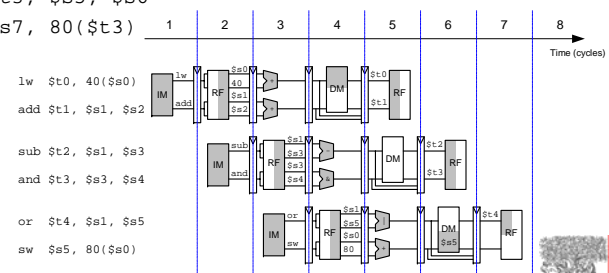

Copyright © 2007 Elsevier


7-<122>



Superscalar Example with Dependencies

```
lw $t0, 40($s0)
add $t1, $t0, $s1
sub $t0, $s2, $s3
and $t2, $s4, $t0
or $t3, $s5, $s6
sw $s7, 80($t3)
```

Ideal IPC: 2
Actual IPC: 6/5 = 1.17

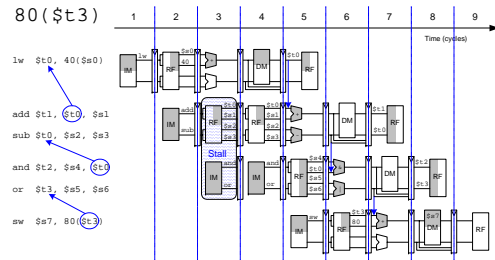

Copyright © 2007 Elsevier

7-<123>



Out of Order Processor

- Looks ahead across multiple instructions to issue as many as possible at once
- Issues instructions out of order as long as no dependencies
- Dependencies:
 - **RAW** (read after write): one instruction writes, and later instruction reads a register
 - **WAR** (write after read): one instruction reads, and a later instruction writes a register (also called an *antidependence*)
 - **WAW** (write after write): one instruction writes, and a later instruction writes a register (also called an *output dependence*)

Copyright © 2007 Elsevier

7-<124>



Out of Order Processor

- **Instruction level parallelism:** the number of instruction that can be issued simultaneously (in practice average < 3)
- **Scoreboard:** table that keeps track of:
 - Instructions waiting to issue
 - Available functional units
 - Dependencies

Copyright © 2007 Elsevier


7-<125>



Out of Order Processor Example

```
lw $t0, 40($s0)
add $t1, $t0, $s1
sub $t0, $s2, $s3
and $t2, $s4, $t0
or $t3, $s5, $s6
sw $s7, 80($t3)
```

Ideal IPC: 2
Actual IPC: 6/4 = 1.5

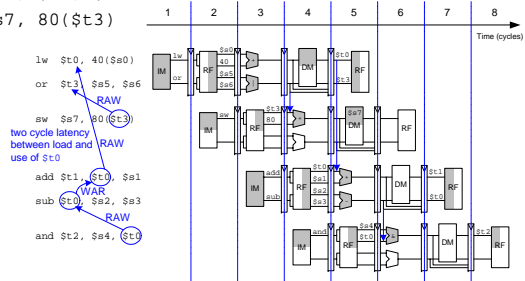

Copyright © 2007 Elsevier


7-<126>



Register Renaming

```
lw $t0, 40($s0)
add $t1, $t0, $s1
sub $t0, $s2, $s3
and $t2, $s4, $t0
or $t3, $s5, $s6
sw $s7, 80($t3)
```

Ideal IPC: 2
Actual IPC: 6/3 = 2

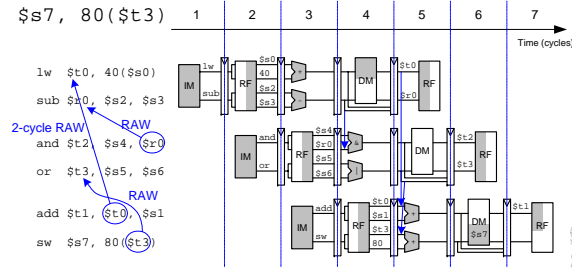

Copyright © 2007 Elsevier


7-<127>



SIMD

- **Single Instruction Multiple Data (SIMD)**
 - Single instruction acts on multiple pieces of data at once
 - Common application: graphics
 - Perform short arithmetic operations (also called *packed arithmetic*)
- For example, add four 8-bit elements
- Must modify ALU to eliminate carries between 8-bit values

```
padd8 $s2, $s0, $s1
```

 

Copyright © 2007 Elsevier

7-<128>



Multithreading: First Some Definitions

- **Process:** program running on a computer
- Multiple processes can run at once: e.g., surfing Web, playing music, writing a paper
- **Thread:** part of a program
- Each process has multiple threads: e.g., a word processor may have threads for typing, spell checking, printing
- In a conventional processor:
 - One thread runs at once
 - When one thread stalls (for example, waiting for memory):
 - Architectural state of that thread is stored
 - Architectural state of waiting thread is loaded into processor and it runs
 - Called **context switching**
 - But appears to user like all threads running simultaneously

Copyright © 2007 Elsevier

7-<129>



Multithreading

- Multiple copies of architectural state
- Multiple threads **active** at once:
 - When one thread stalls, another runs immediately (no need to store or restore architectural state)
 - If one thread can't keep all execution units busy, another thread can use them
- Does not increase ILP of single thread, but does increase throughput

Copyright © 2007 Elsevier

7-<130>



Multiprocessors

- Multiple processors (cores) with a method of communication between them
- Types of multiprocessing:
 - **Symmetric multiprocessing (SMT):** multiple cores with a shared memory
 - **Asymmetric multiprocessing:** separate cores for different tasks (for example, DSP and CPU in cell phone)
 - **Clusters:** each core has its own memory system

Copyright © 2007 Elsevier

7-<131>



Other Resources

- Patterson & Hennessy's: *Computer Architecture: A Quantitative Approach*
- Conferences:
 - www.cs.wisc.edu/~arch/www/
 - ISCA (International Symposium on Computer Architecture)
 - HPCA (International Symposium on High Performance Computer Architecture)

Copyright © 2007 Elsevier

7-<132>

