

Transmission Lines

Digital Design and Computer Architecture

David Money Harris and Sarah L. Harris

Copyright © 2007 Elsevier

TL-<1>



Transmission Lines :: Topics

- **Introduction**
- **Wave Propagation**
- **Termination**
- **Reflections**
- **Summary**

Copyright © 2007 Elsevier

TL-<2>



Introduction

- We have assumed wires are *equipotential* nodes
 - Same voltage along the entire length of wire
- Signals actually propagate at the speed of light
 - Voltage and current will vary along the line
 - Important for long wires or high speeds
- Transmission lines capture this behavior

Copyright © 2007 Elsevier

TL-<3>



Return Paths

- Current always flows in loops
- We usually think about the current flowing out along a wire
- But there must be a path for the current to return
- Often returns through the GND network
- If this is not well controlled, interesting things may happen


Copyright © 2007 Elsevier

TL-<4>



Transmission Lines

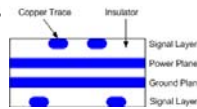- Many ways to provide a signal and a return path
- Printed Circuit Board
 - Typically use 4 or more multiple layers
 - Signal traces
 - Power/GND planes
- Coaxial Cable
 - Signal flows in the inner conductor
 - Returns in outer ground conductor
- Ad-Hoc
 - Current may return through unknown paths
 - May increase delay and cause unpredictable noise



Copyright © 2007 Elsevier

TL-<5>



Speed of Light in a Medium

- Speed of light in free space:

$$v = c = \frac{1}{\sqrt{\mu_0 \epsilon_0}} = 3 \times 10^8 \text{ m/s}$$

- Speed of light in a medium

$$v = \frac{1}{\sqrt{\mu \epsilon}} = \frac{1}{\sqrt{LC}}$$

- For a PCB with $\epsilon = 4 \epsilon_0$, $v = c/2 = 15 \text{ cm/ns}$

Copyright © 2007 Elsevier

TL-<6>



Transmission Time

- Flight time along a wire of length l

$$t_d = l / v$$

- Example: a 12" trace across a large board has a 2 ns flight time

Copyright © 2007 Elsevier


TL-<7>



Characteristic Impedance

- The *characteristic impedance* of a transmission line, Z_0 , is the ratio of voltage to current in a wave traveling along the wire
 - Not the resistance of the wire (typically close to 0)
- Depends on inductance and capacitance
 - Typically 50 to 75 Ω

$$Z_0 = \sqrt{\frac{L}{C}}$$

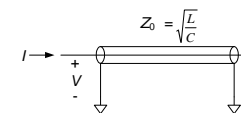

Copyright © 2007 Elsevier

TL-<8>



Transmission Line Behavior

- Visualize wave of voltage propagating along the line at the speed of light
 - When the wave hits the end, it may be absorbed or reflected, depending on the *termination*
 - Reflections travel back along the line, adding to the voltage already on the line
 - After all reflections die out, the voltage will be the same as if the line were a simple wire
- Terminations
 - Matched
 - Open
 - Short
 - Mismatched




Copyright © 2007 Elsevier

TL-<9>



Matched Termination

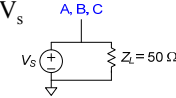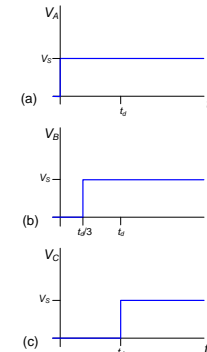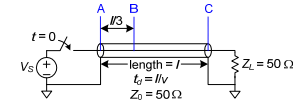- $Z_L = Z_0$
- Wave of $V = V_s$ begins flowing down line
- Wave travels at velocity v
- Wave is absorbed by Z_L
- Equivalent steady-state circuit
 - Final value = V_s






Copyright © 2007 Elsevier

TL-<10>



Matched Source and Load Termination

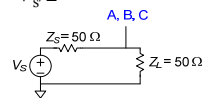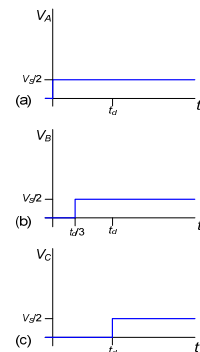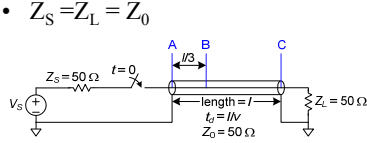- $Z_S = Z_L = Z_0$
- Voltage divider at source
- Wave of $V = V_s/2$ begins flowing down line
- Equivalent steady-state circuit
 - Final value = $V_s/2$





Copyright © 2007 Elsevier

TL-<11>



Open Termination

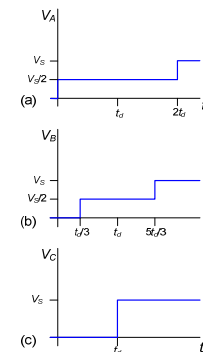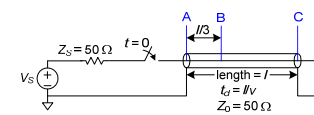- $Z_S = Z_0$ $Z_L = \infty$
- Wave of $V = V_s/2$ begins flowing down line
- Current flowing down the line has nowhere to go at the end and must reflect




Copyright © 2007 Elsevier

TL-<12>




Short Termination

- $Z_S = Z_0 \quad Z_L = 0$

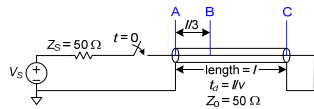

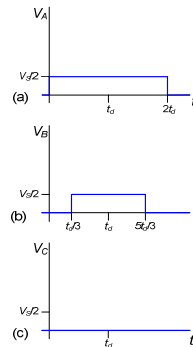- Wave of $V = V_S/2$ begins flowing down line
- Voltage at the end must be 0, so a negative wave must be reflected



Copyright © 2007 Elsevier

TL-<13>



Reflectance Coefficient

- When a wave of voltage V_i reaches either end of a transmission line, part (V_r) will be reflected if the termination impedance Z_T does not match the line impedance

$$V_r = k_r V_i$$

$$k_r = \frac{Z_T - Z_0}{Z_T + Z_0}$$

- Special cases

- $Z_T = Z_0$: $k_r = 0$ (matched load, wave absorbed)
- $Z_T = \infty$: $k_r = 1$ (open load, wave reflected)
- $Z_T = 0$: $k_r = -1$ (short load, negative wave reflected)


Copyright © 2007 Elsevier

TL-<14>





Mismatched Termination (Example 1)

- Load termination mismatched

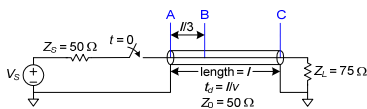

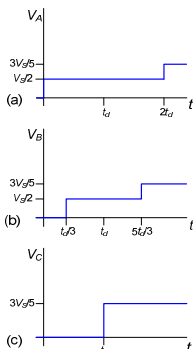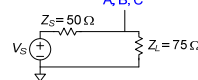- Wave of $V = V_S/2$ begins flowing down line
- $k_r = (75-50)/(75+50) = 1/5$
- Wave of $(1/5)V_S/2 = V_S/10$ reflects off end, bringing total to $3V_S/5$




Copyright © 2007 Elsevier

TL-<15>




Mismatched Termination (Example 2)

- Both terminations mismatched

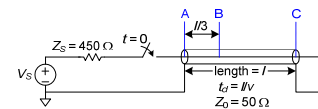

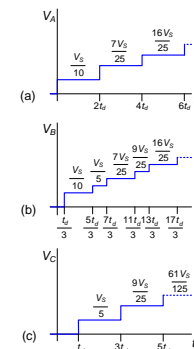- Wave of $V = V_S/10$ begins flowing down line
- $k_r = 1$ at end, $4/5$ at start
- Waves reflect off each end until line starts to approach its final value of V_S




Copyright © 2007 Elsevier

TL-<16>



Bounce Diagram

- Bounce diagram shows reflections

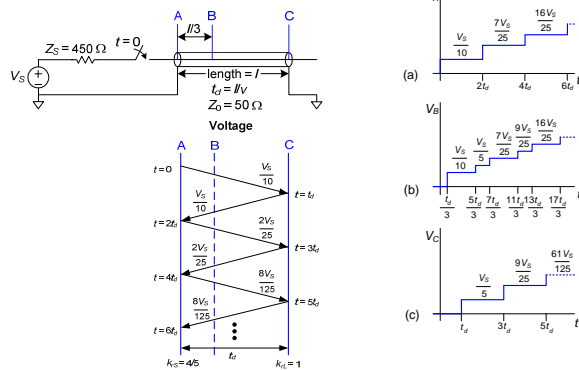

Copyright © 2007 Elsevier

TL<17>



When to use Transmission Line Models

- Wires should be modeled as transmission lines when $t_d > 20\%$ of the rise/fall time of the signal
 - i.e. when reflections don't dissipate while signal is transitioning
- Recall that signals on a PCB travel at 15 cm/ns
- For a TTL signal with a 10 ns edge rate, treat a wire as a transmission line if it exceeds 30 cm
- For a fast signal with a 2 ns edge rate, treat a wire as a transmission line if it exceeds 6 cm (2.5 inches)
- Don't make signals faster than necessary


Copyright © 2010 Elsevier

TL<18>



Proper Termination

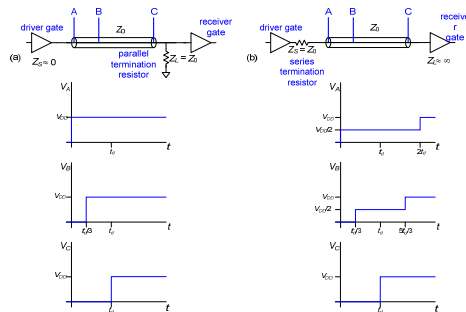- Transmission lines should be properly terminated at the load (parallel) or source (series)



Copyright © 2010 Elsevier

TL<19>



Comparison

- ### Parallel Termination
- All points on the line see valid logic levels
 - Good for busses with multiple receivers
 - Consumes lots of power (V^2/Z_0)
- ### Series Termination
- Consumes little power
 - Midpoint sees indeterminate logic level for a time
 - Only suitable for point-to-point links

Copyright © 2010 Elsevier

TL<20>

