 


# E85 Digital Design & Computer Engineering



## Lecture 19: Single Cycle Processor Datapath

**HARVEY  
MUDD  
COLLEGE**


# Lecture 19

- **Single Cycle Processor Datapath**


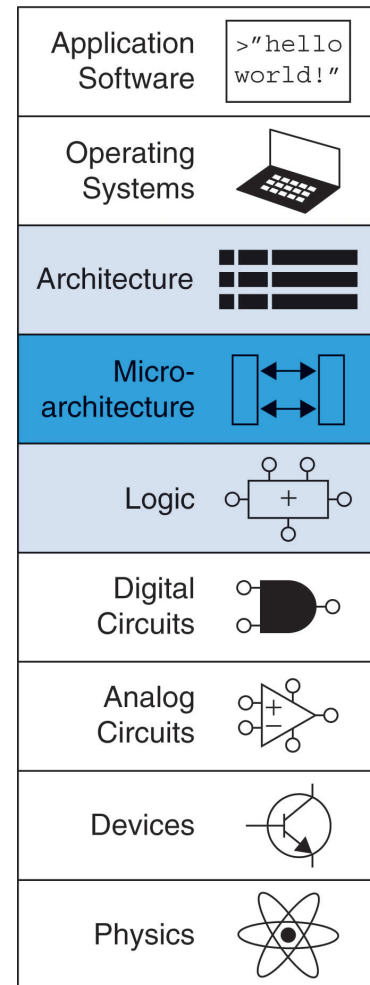
# Introduction

- **Microarchitecture:** how to implement an architecture in hardware
- **Processor:**
  - **Datapath:** functional blocks
  - **Control:** control signals



# Microarchitecture

- Multiple implementations for a single architecture:
  - **Single-cycle:** Each instruction executes in a single cycle
  - **Multicycle:** Each instruction is broken up into series of shorter steps
  - **Pipelined:** Each instruction broken up into series of steps & multiple instructions execute at once



# Processor Performance

- **Program execution time**

**Execution Time = (#instructions)(cycles/instruction)(seconds/cycle)**

- **Definitions:**

- CPI: Cycles/instruction
- clock period: seconds/cycle
- IPC: instructions/cycle = IPC

- **Challenge is to satisfy constraints of:**

- Cost
- Power
- Performance



# ARM Processor

- Consider **subset** of ARM instructions:
  - **Data-processing instructions:**
    - **ADD, SUB, AND, ORR**
    - with register and immediate Src2, but **no shifts**
  - **Memory instructions:**
    - **LDR, STR**
    - with **positive immediate offset**
  - **Branch instructions:**
    - **B**




# Architectural State Elements

## Determines everything about a processor:

- Architectural state:
  - 16 registers (including PC)
  - Status register
- Memory



# ARM Architectural State Elements

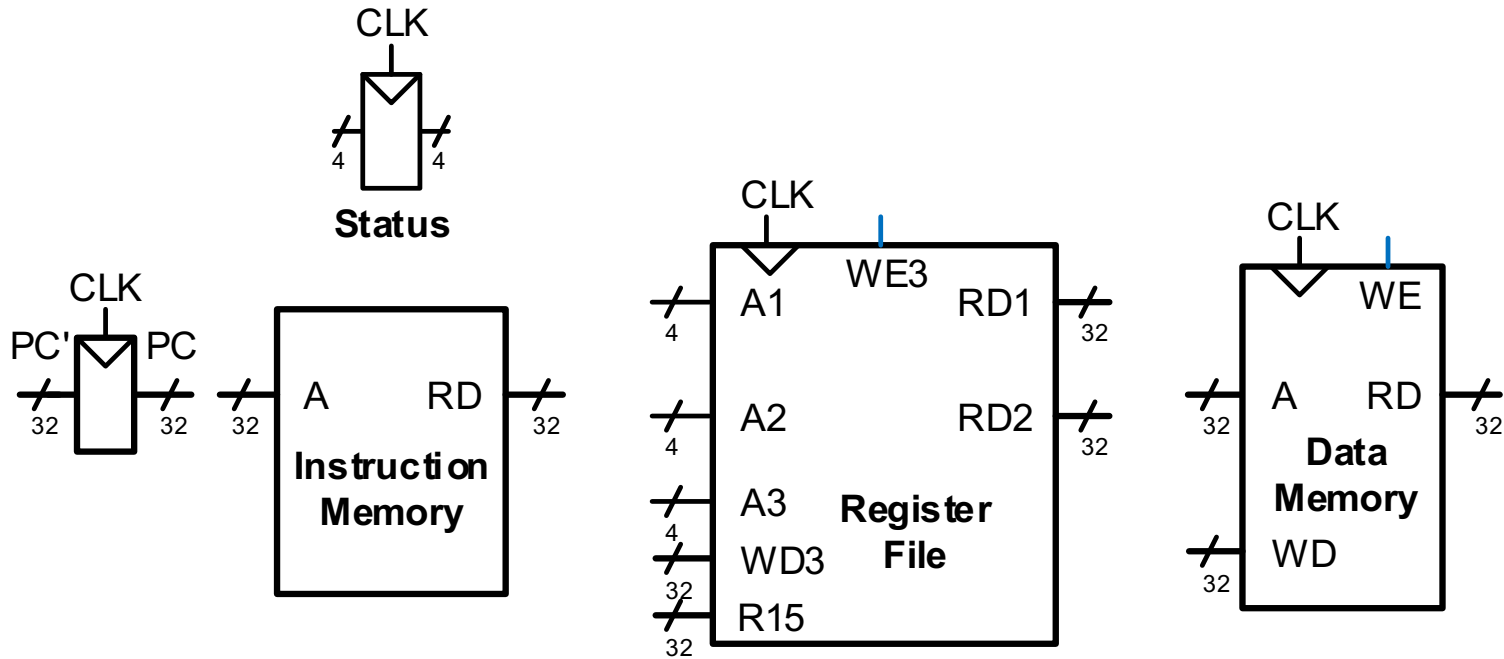



# Single-Cycle ARM Processor

- Datapath
- Control




# Single-Cycle ARM Processor

- **Datapath**
- Control



 
# Single-Cycle ARM Processor

- **Datapath:** start with LDR instruction
- **Example:** LDR R1, [R2, #5]  
LDR Rd, [Rn, imm12]





# Single-Cycle Datapath: LDR fetch

## STEP 1: Fetch instruction

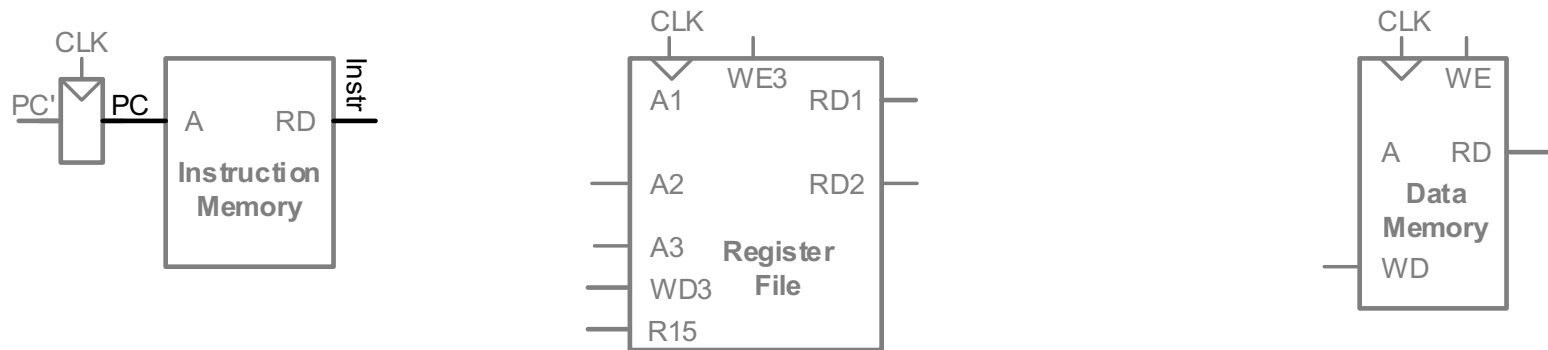



# Single-Cycle Datapath: LDR Reg Read

## STEP 2: Read source operands from RF

 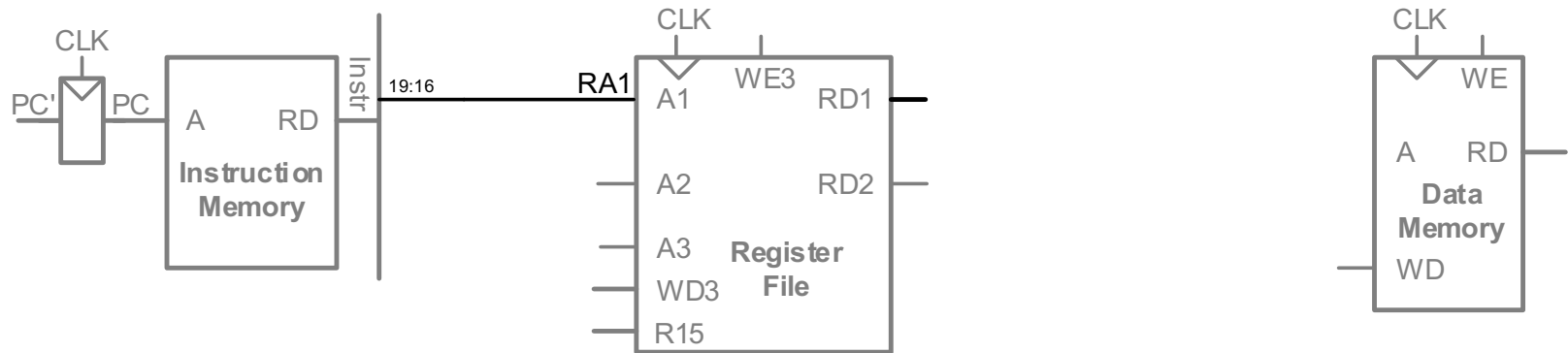



# Single-Cycle Datapath: LDR Immed.

## STEP 3: Extend the immediate

 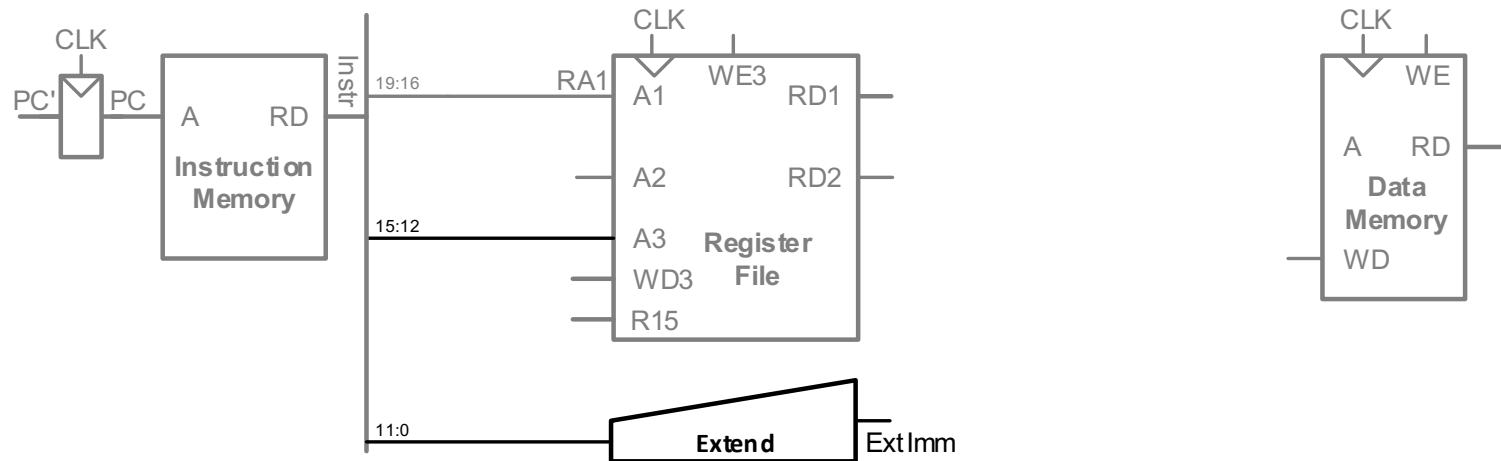



# Single-Cycle Datapath: LDR Address

## STEP 4: Compute the memory address

 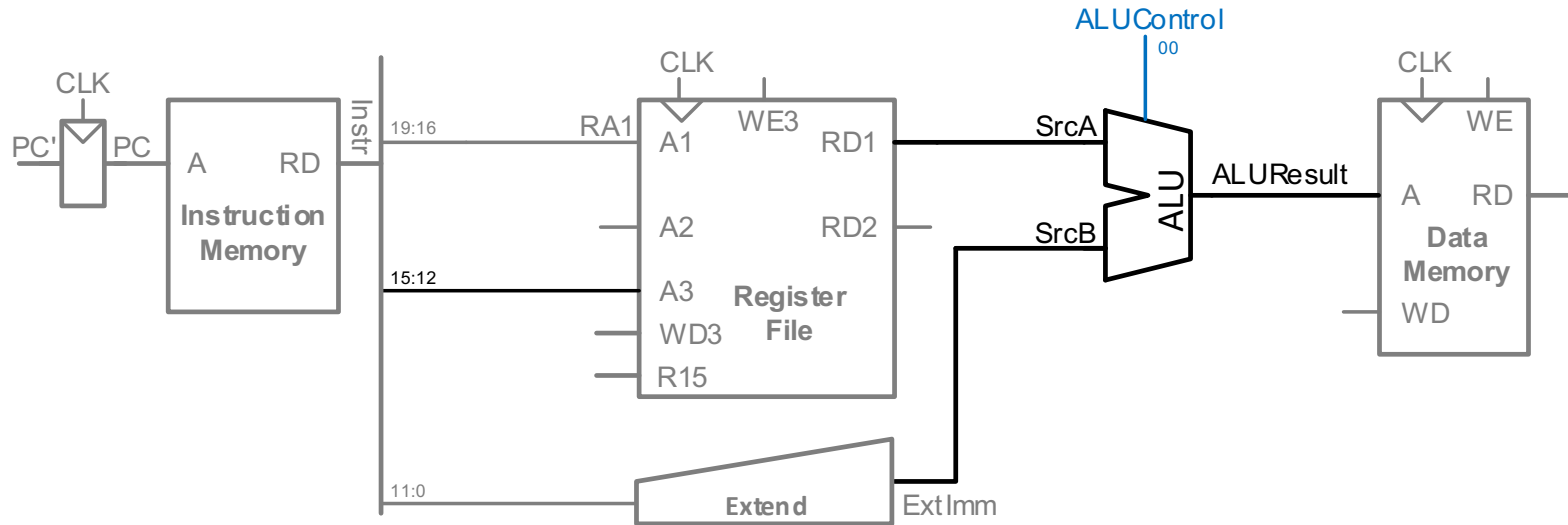
 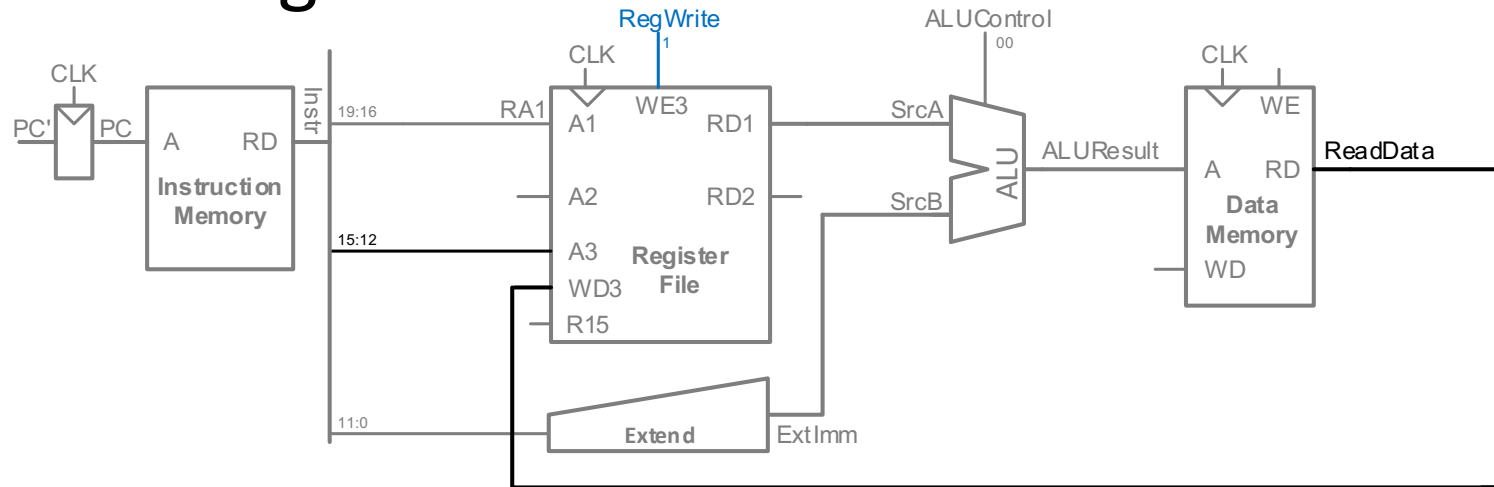
# Single-Cycle Datapath: LDR Mem Read


**STEP 5:** Read data from memory and write it back to register file






# Single-Cycle Datapath: PC Increment
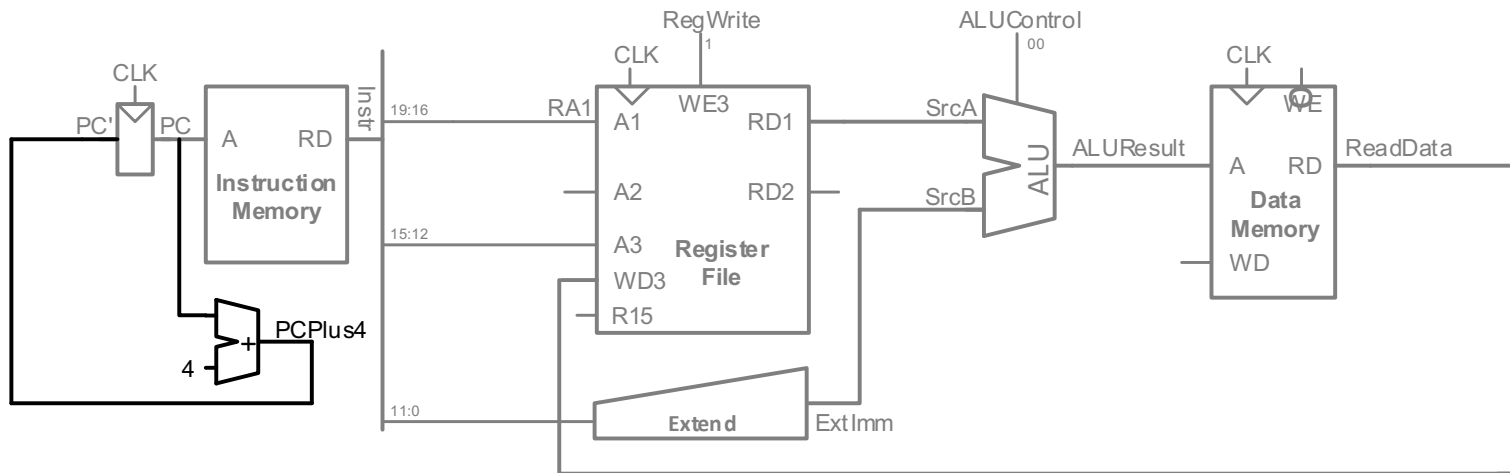
## STEP 6: Determine address of next instruction


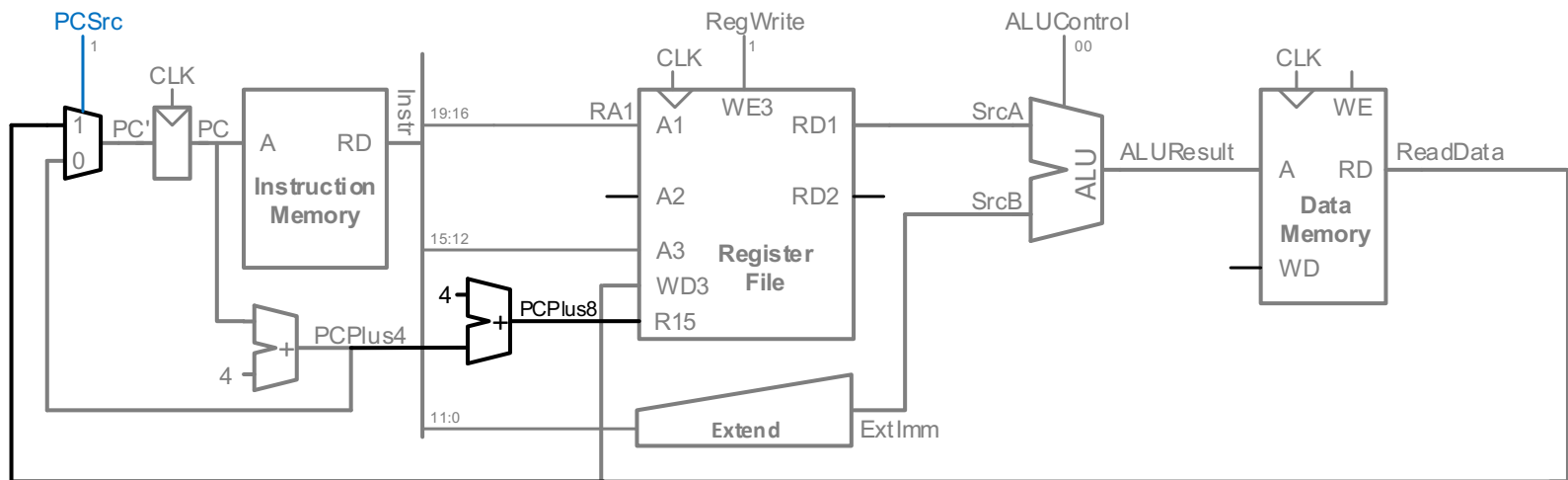
# Single-Cycle Datapath: Access to PC


PC can be source/destination of instruction


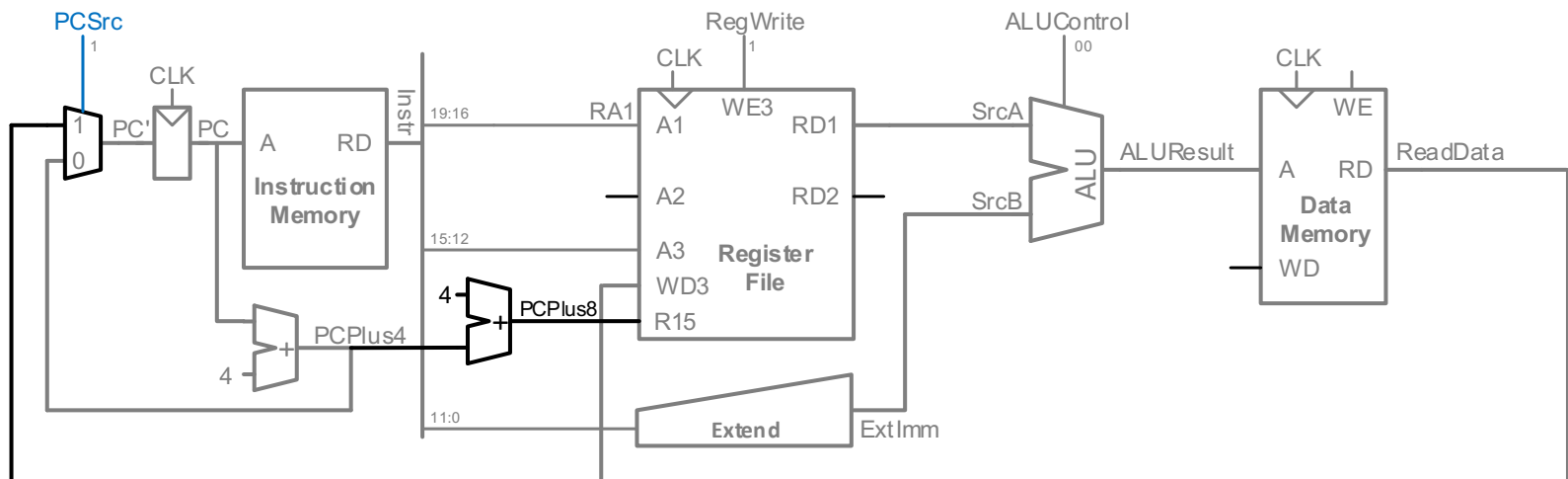
# Single-Cycle Datapath: Access to PC

PC can be source/destination of instruction


- **Source:** R15 must be available in Register File
  - **PC** is read as the current **PC plus 8**


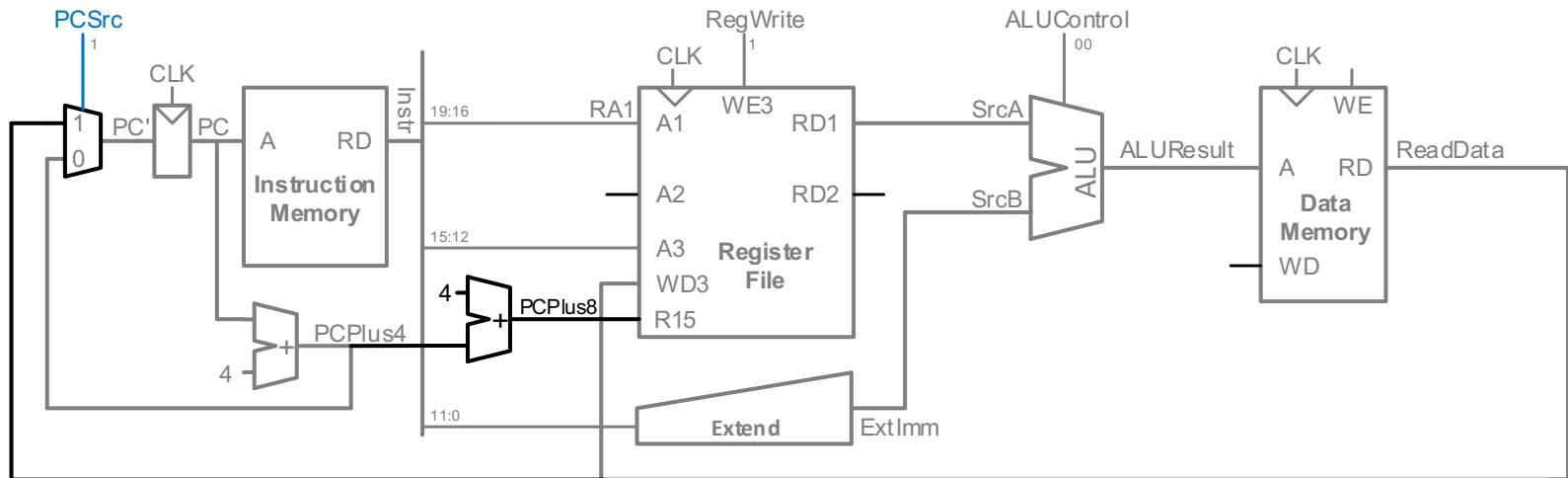
# Single-Cycle Datapath: Access to PC

PC can be source/destination of instruction



- **Source:** R15 must be available in Register File
  - **PC** is read as the current **PC plus 8**
- **Destination:** Be able to write result to PC



# Single-Cycle Datapath: STR

## Expand datapath to handle STR:


- Write data in Rd to memory

 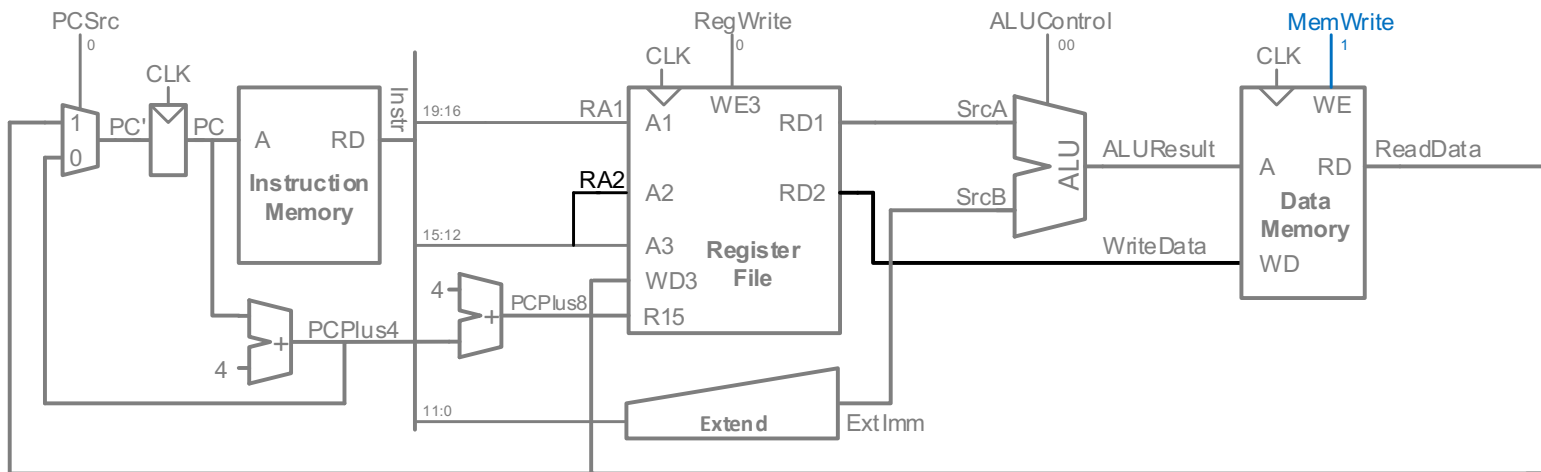

# Single-Cycle Datapath: Data-processing
 
## With **immediate Src2**:

- Read from  $R_n$  and  $Imm8$  (*ImmSrc* chooses the zero-extended  $Imm8$  instead of  $Imm12$ )
- Write *ALUResult* to register file
- Write to  $R_d$




**ADD  $R_d, R_n, imm8$**



# Single-Cycle Datapath: Data-processing
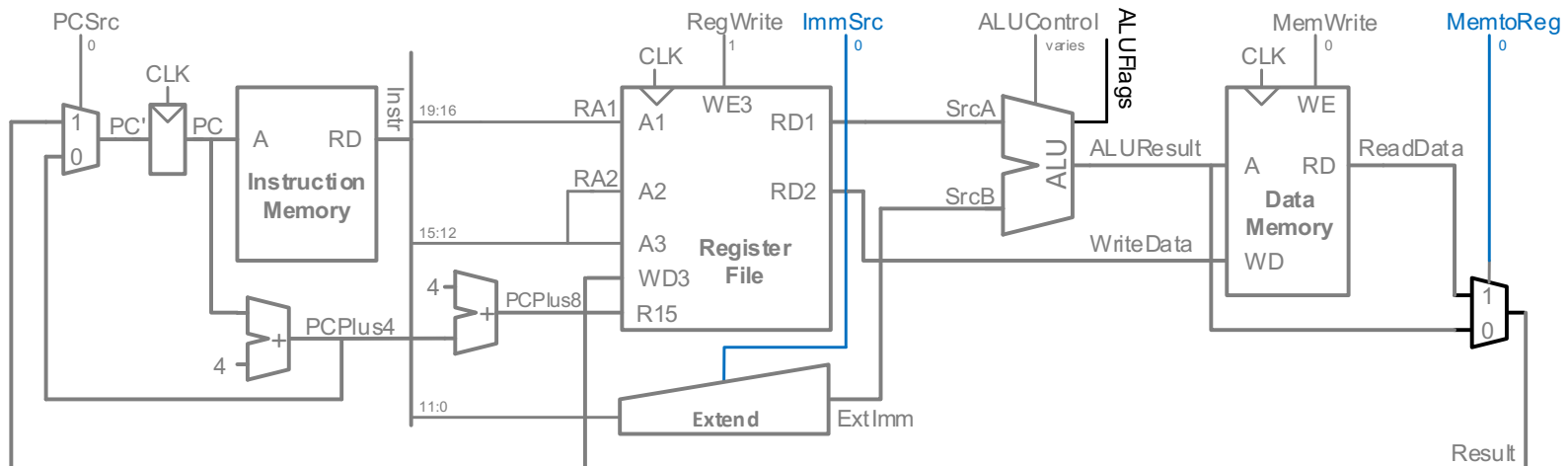
## With **immediate Src2**:

- Read from  $R_n$  and  $Imm8$  (*ImmSrc* chooses the zero-extended  $Imm8$  instead of  $Imm12$ )
- Write *ALUResult* to register file
- Write to  $R_d$




**ADD  $R_d, R_n, imm8$**

# Single-Cycle Datapath: Data-processing
 
## With register Src2:

- Read from  $R_n$  and  $R_m$  (instead of  $Imm8$ )
- Write  $ALUResult$  to register file
- Write to  $R_d$



**ADD  $R_d$ ,  $R_n$ ,  $R_m$**






# Single-Cycle Datapath: Data-processing
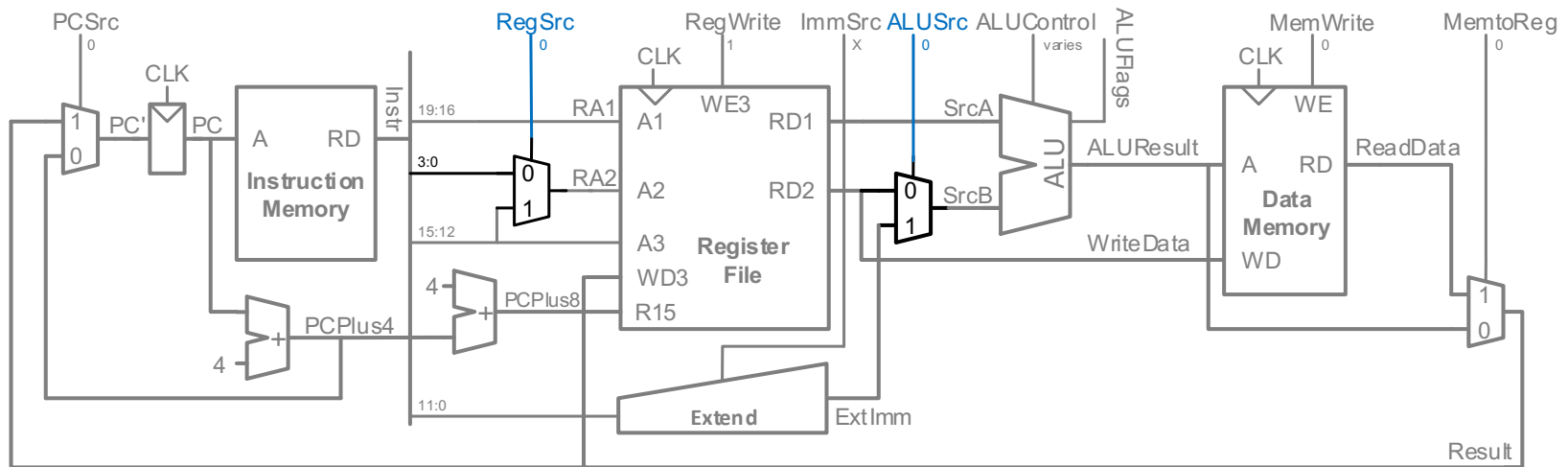
## With register Src2:

- Read from  $R_n$  and  $R_m$  (instead of  $Imm8$ )
- Write  $ALUResult$  to register file
- Write to  $R_d$



**ADD  $R_d$ ,  $R_n$ ,  $R_m$**




# Single-Cycle Datapath: B

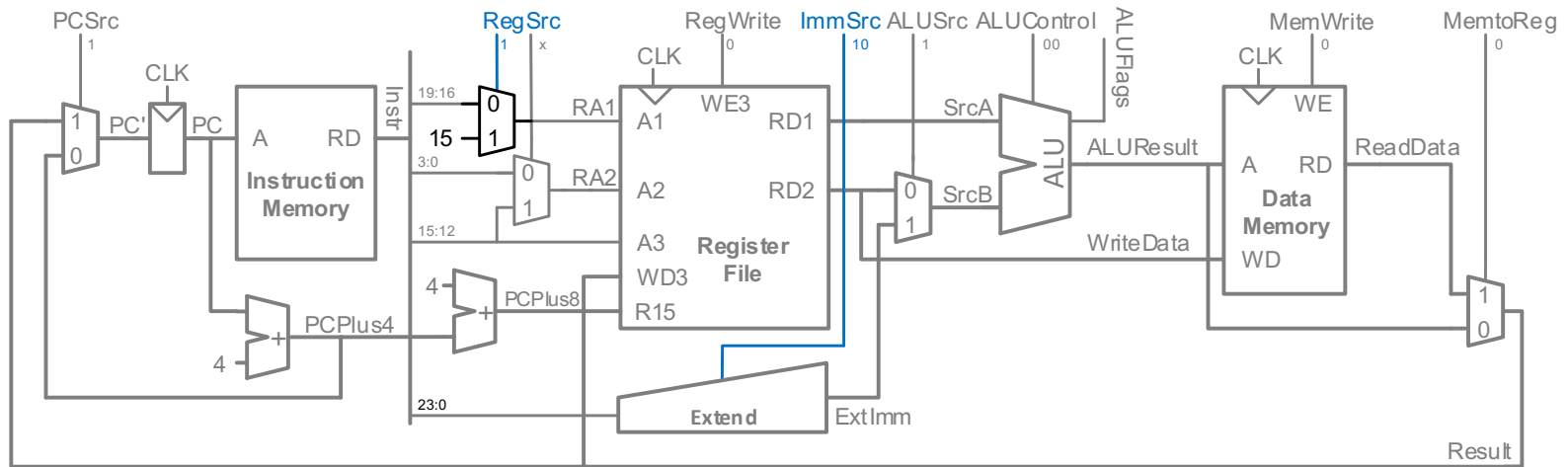
## Calculate branch target address:

$$\text{BTA} = (\text{ExtImm}) + (\text{PC} + 8)$$

$$\text{ExtImm} = \text{Imm24} \ll 2 \text{ and sign-extended}$$



Branch

 


funct

B Label



# Single-Cycle Datapath: ExtImm

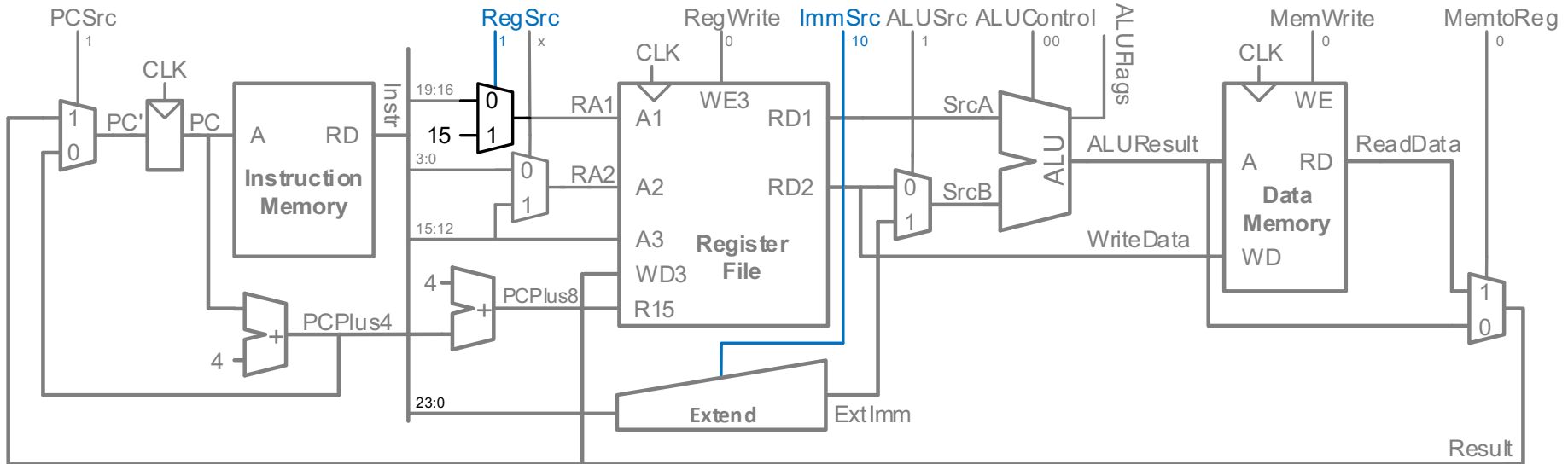

ImmSrc <sub>1:0</sub>	ExtImm	Description
00	{24'b0, Instr <sub>7:0</sub> }	Zero-extended <i>imm8</i>
01	{20'b0, Instr <sub>11:0</sub> }	Zero-extended <i>imm12</i>
10	{6{Instr <sub>23</sub> }, Instr <sub>23:0</sub> }	Sign-extended <i>imm24</i>



# Single-Cycle ARM Processor

