 


E85 Digital Design & Computer Engineering



Lecture 20: Single Cycle Processor Controller


**HARVEY
MUDD
COLLEGE**

Lecture 20


- **Single Cycle Processor Controller**




Single-Cycle ARM Processor

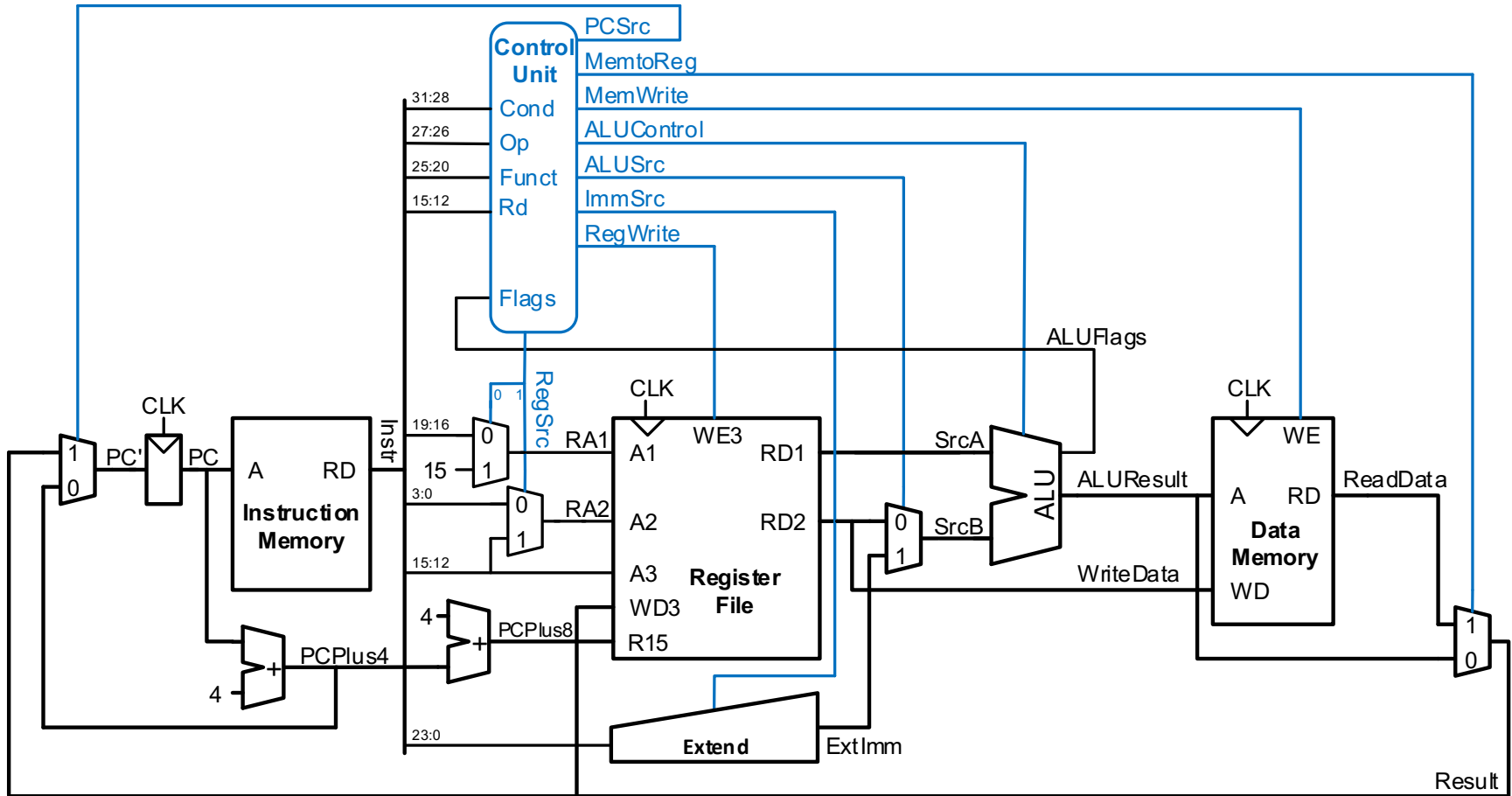


Single-Cycle Control

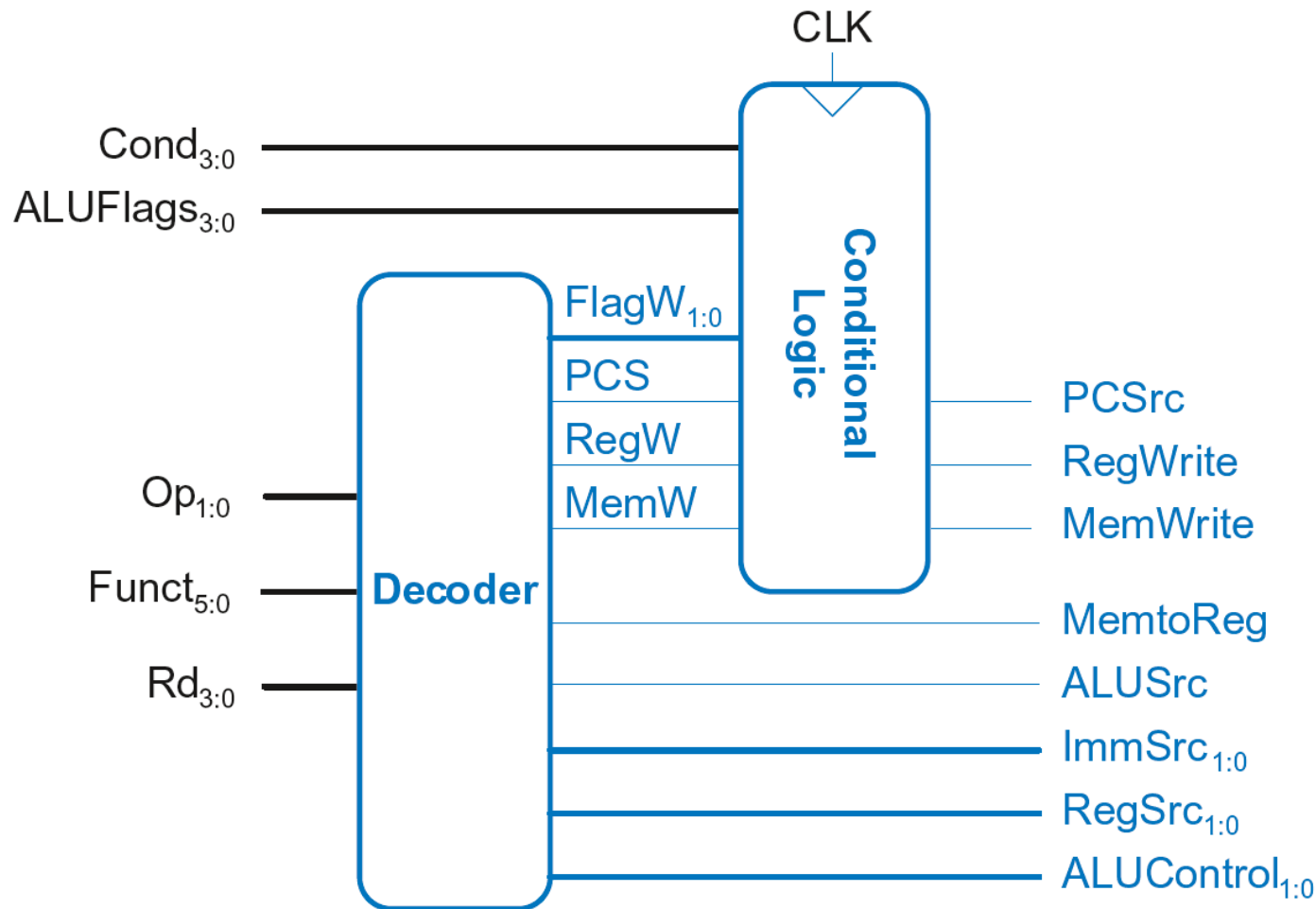


Single-Cycle Control

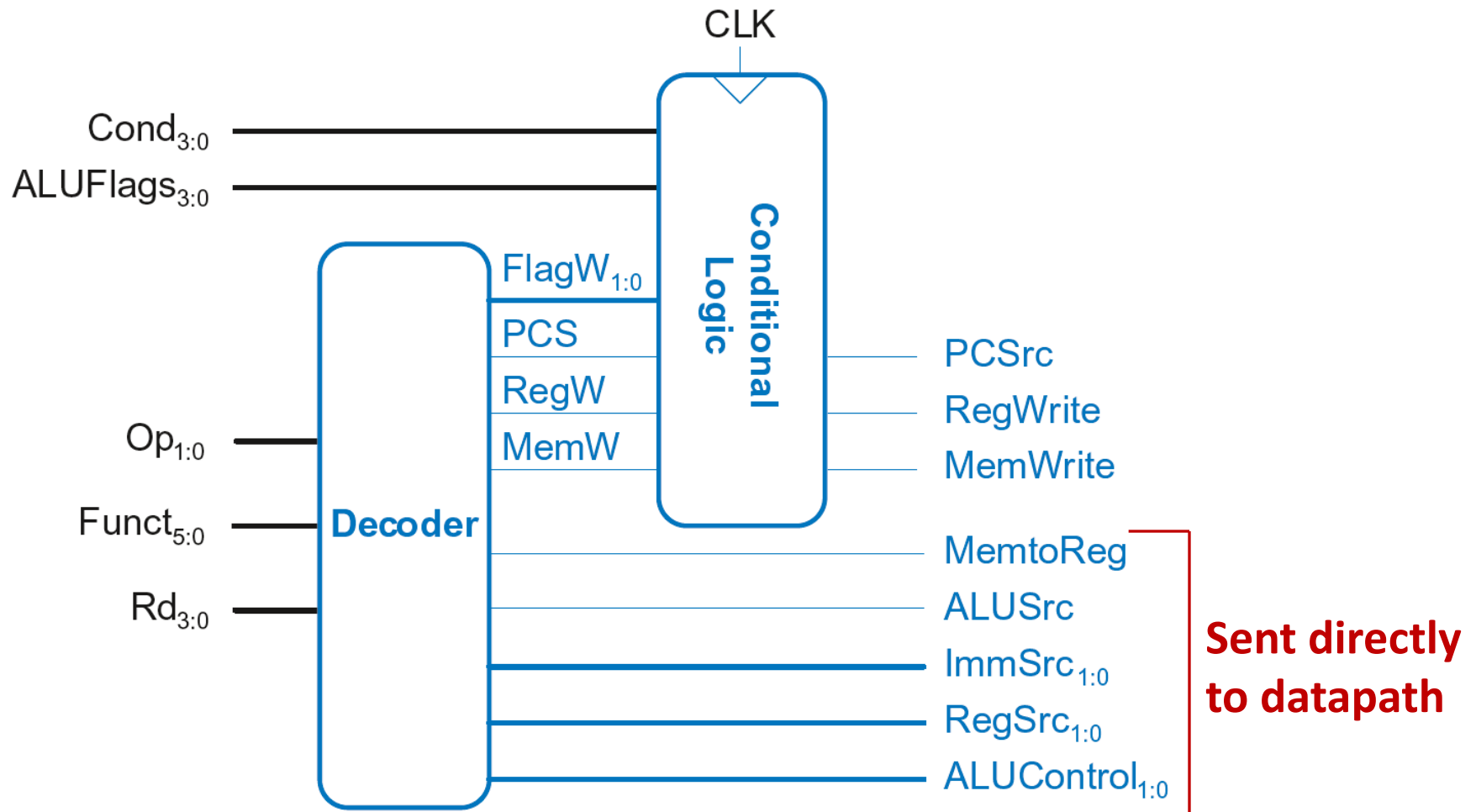


Single-Cycle Control

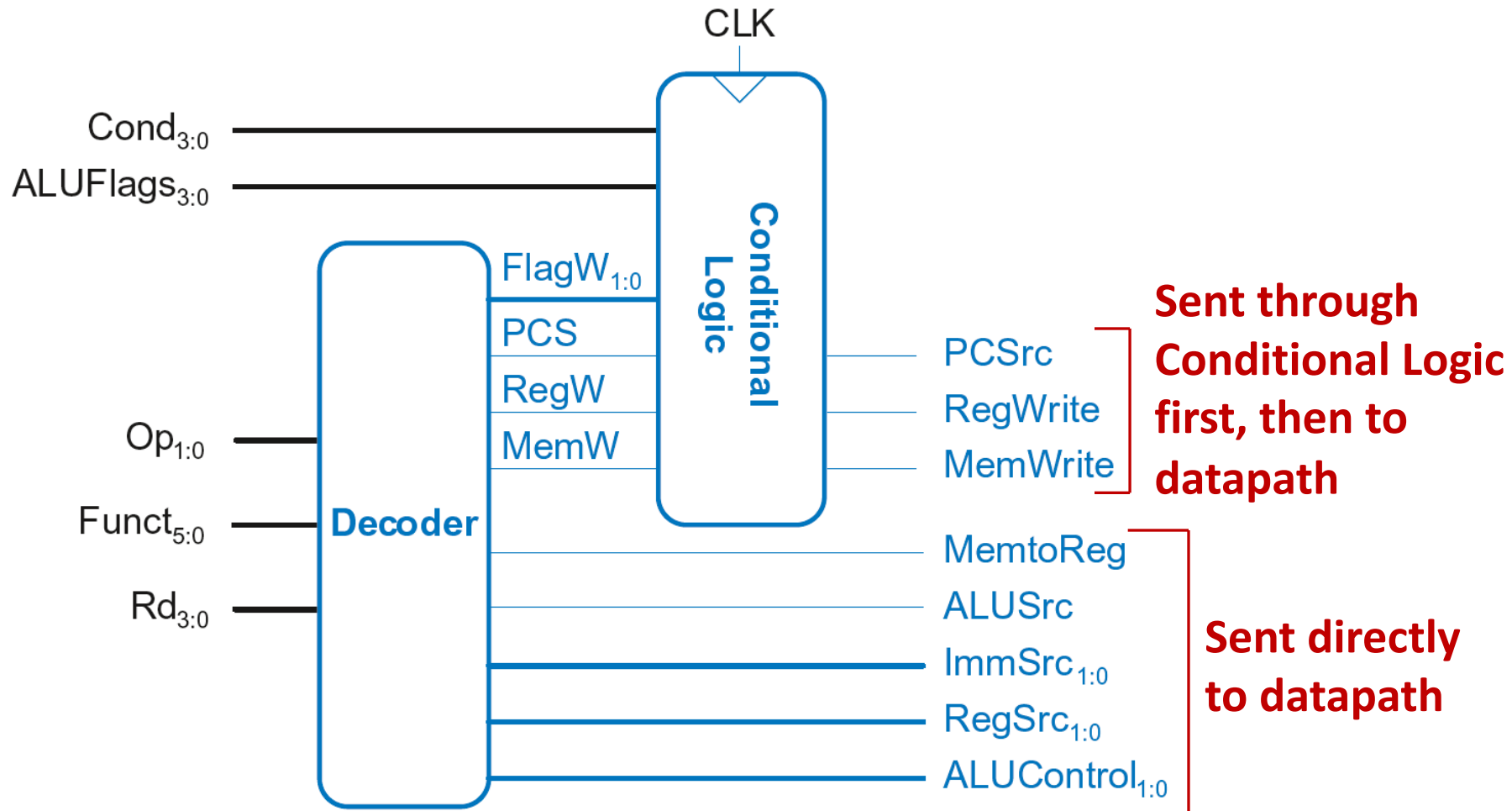

Single-Cycle Control

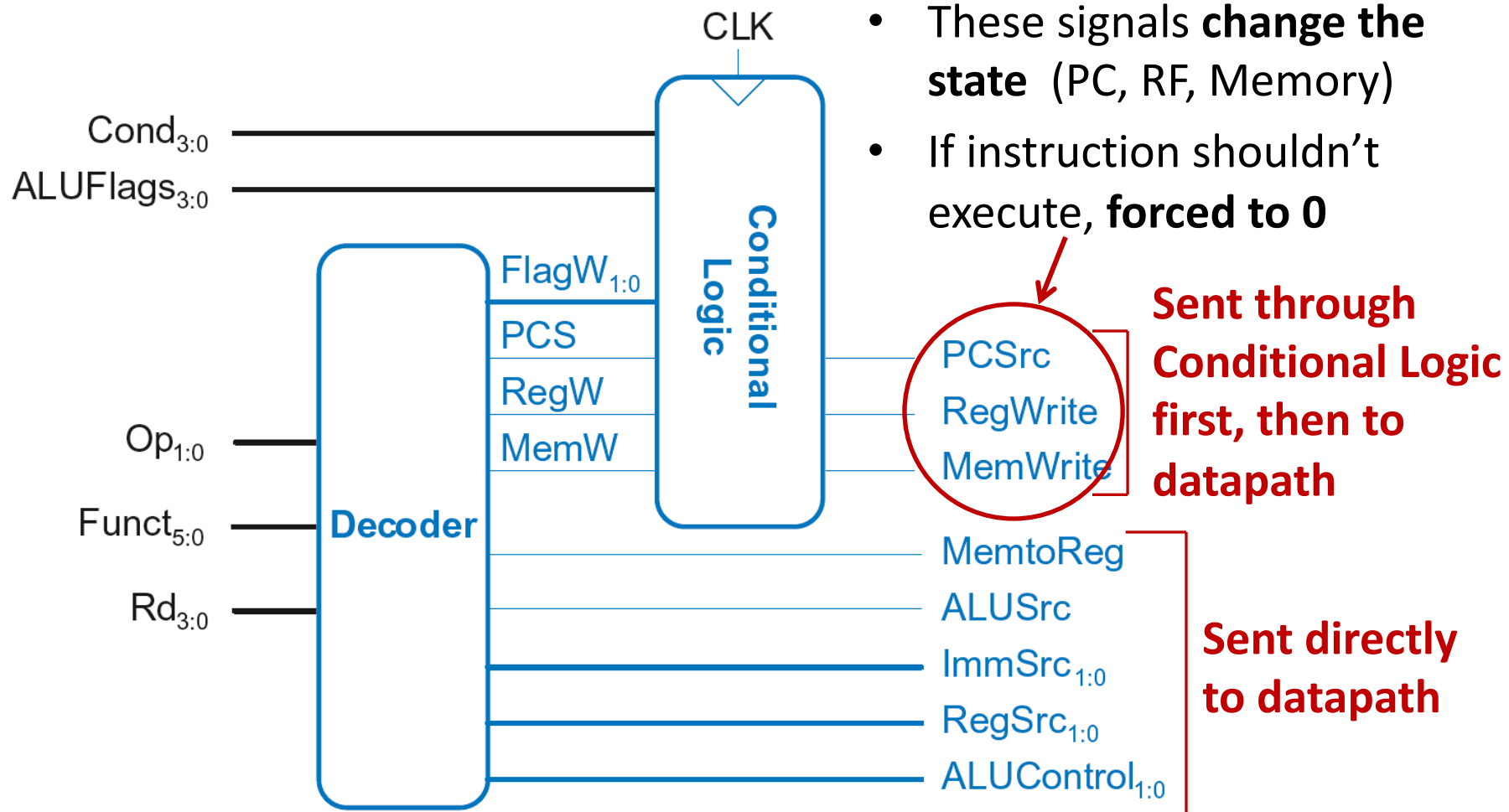


Single-Cycle Control

 

- **$FlagW_{1:0}$** : Flag Write signal, asserted when $ALUFlags$ should be saved (i.e., on instruction with $S=1$)




Single-Cycle Control

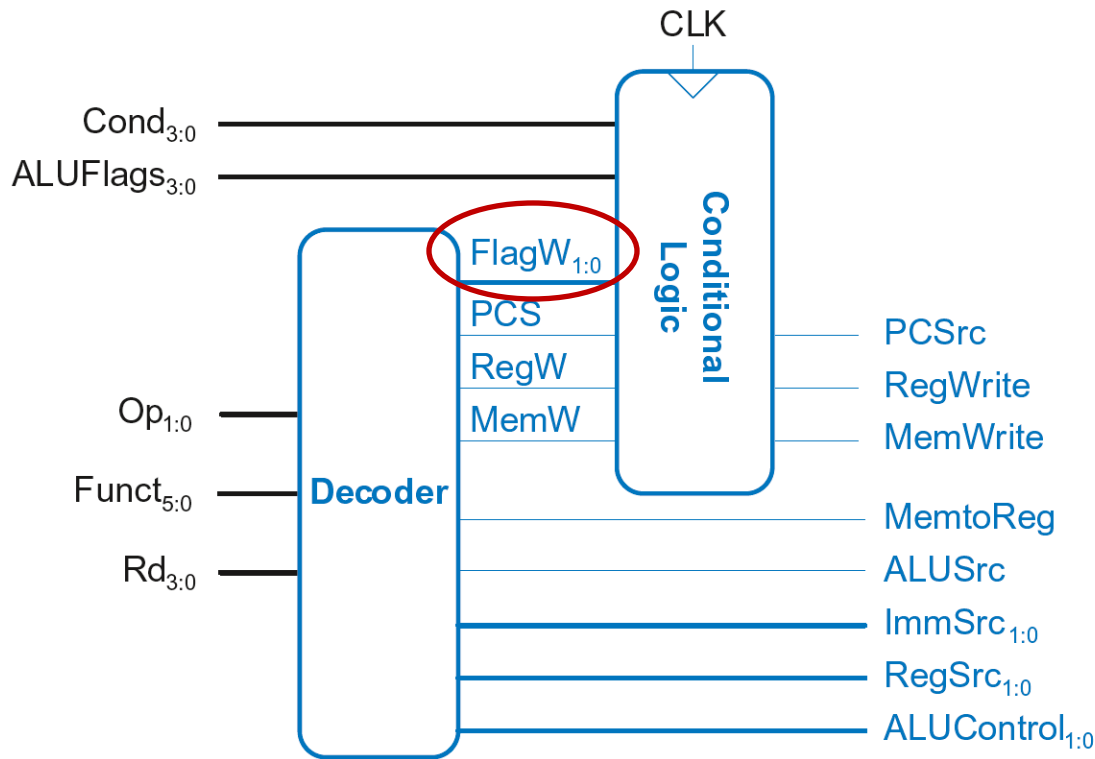

- **$FlagW_{1:0}$** : Flag Write signal, asserted when *ALUFlags* should be saved (i.e., on instruction with $S=1$)
- ADD, SUB update all flags (**NZCV**)
- AND, ORR only update **NZ** flags




Single-Cycle Control

 


- **$FlagW_{1:0}$** : Flag Write signal, asserted when $ALUFlags$ should be saved (i.e., on instruction with $S=1$)
- ADD, SUB update all flags (**NZCV**)
- AND, ORR only update **NZ** flags
- So, two bits needed:
 - **$FlagW_1 = 1$** : NZ saved ($ALUFlags_{3:2}$ saved)
 - **$FlagW_0 = 1$** : CV saved ($ALUFlags_{1:0}$ saved)



Single-Cycle Control

 


Single-Cycle Control: Decoder

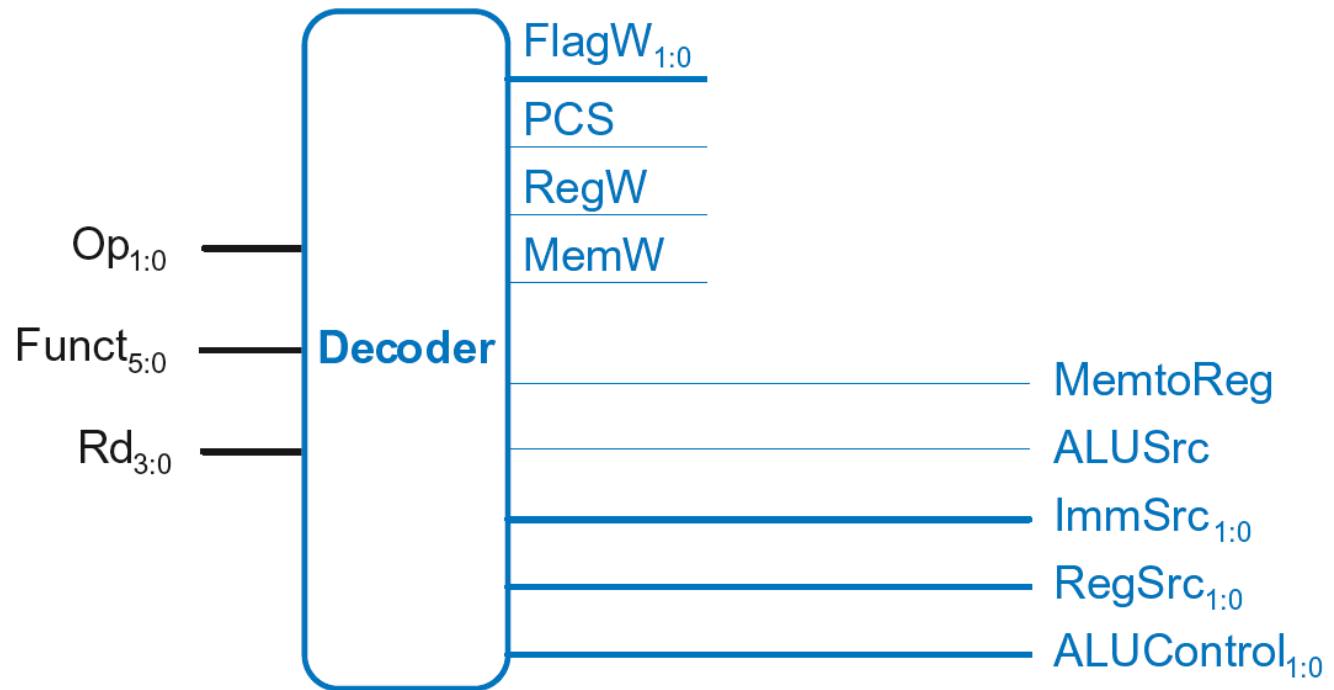

Single-Cycle Control: Decoder

Submodules:


- Main Decoder
- ALU Decoder
- PC Logic

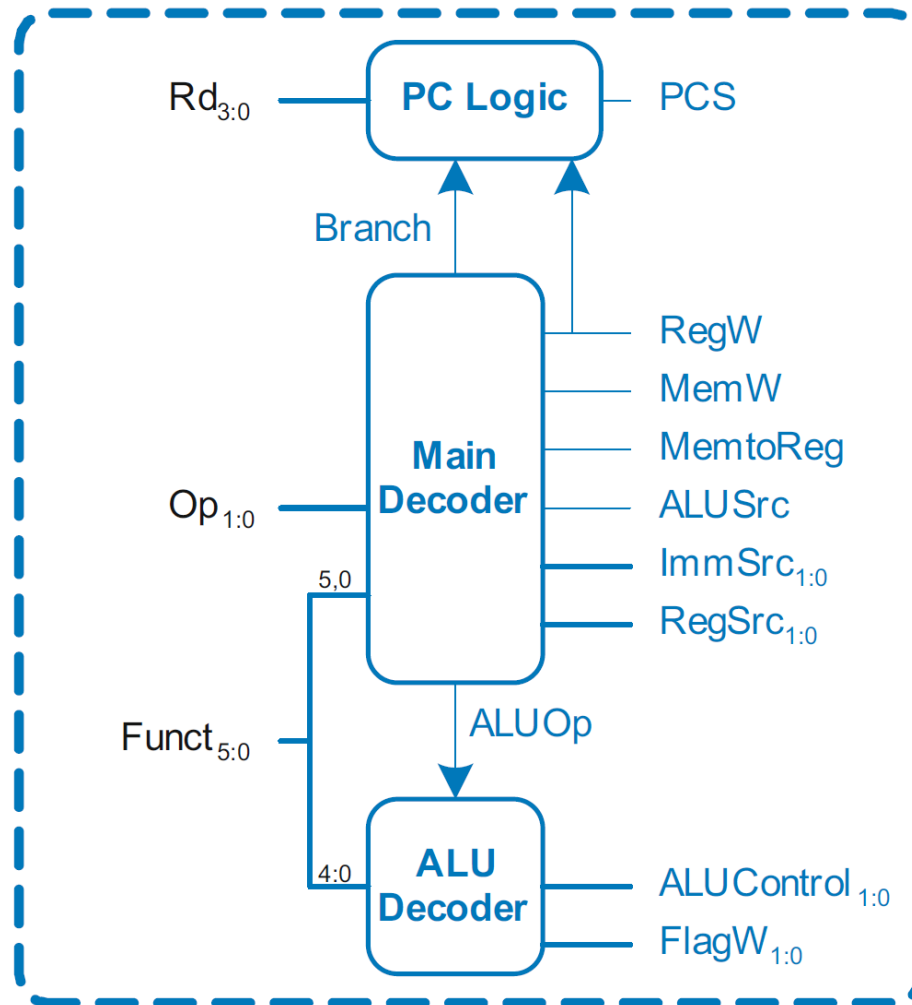

Single-Cycle Control: Decoder

Submodules:

 - **Main Decoder**
- ALU Decoder
- PC Logic



Control Unit: Main Decoder


Op	Funct _s	Funct ₀	Type	Branch	MemtoReg	MemW	ALUSrc	ImmSrc	RegW	RegSrc	ALUOp
00	0	X	DP Reg	0	0	0	0	XX	1	00	1
00	1	X	DP Imm	0	0	0	1	00	1	X0	1
01	X	0	STR	0	X	1	1	01	0	10	0
01	X	1	LDR	0	1	0	1	01	1	X0	0
10	X	X	B	1	0	0	1	10	0	X1	0



Single-Cycle Control: Decoder


Submodules:

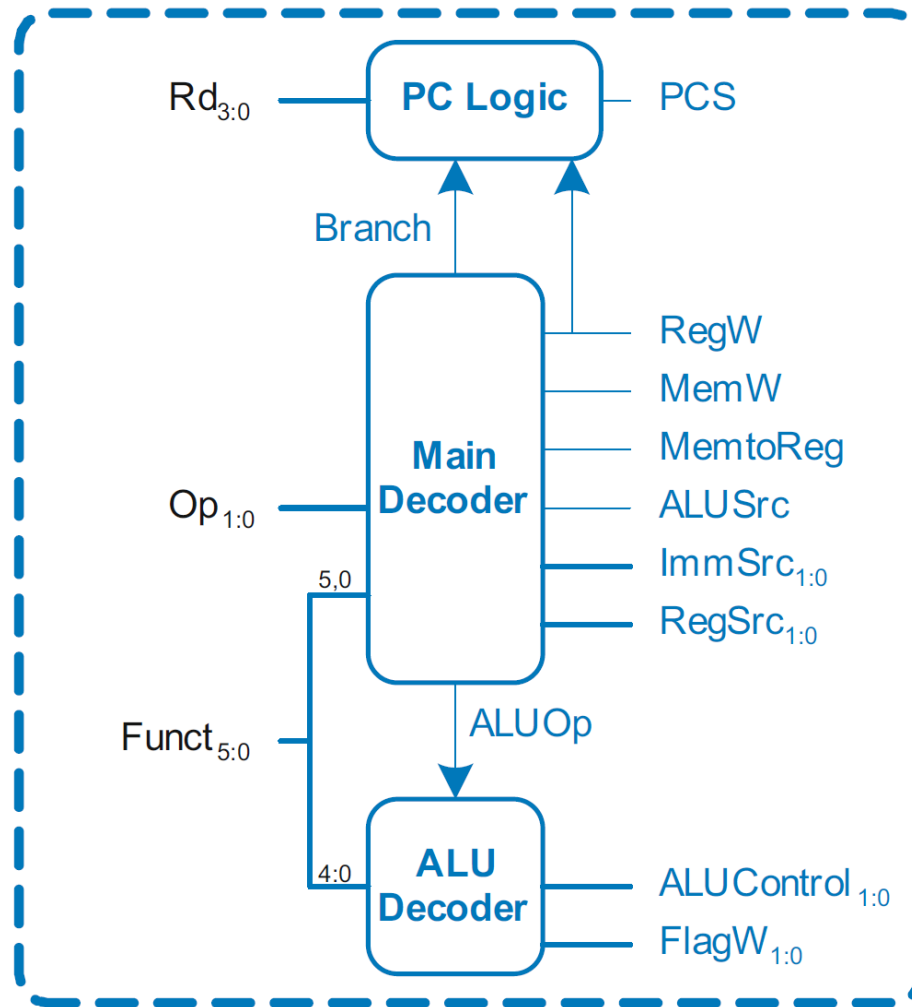- Main Decoder
- **ALU Decoder**
- PC Logic




Review: ALU

ALUControl _{1:0}	Function
00	Add
01	Subtract
10	AND
11	OR

 


Review: ALU

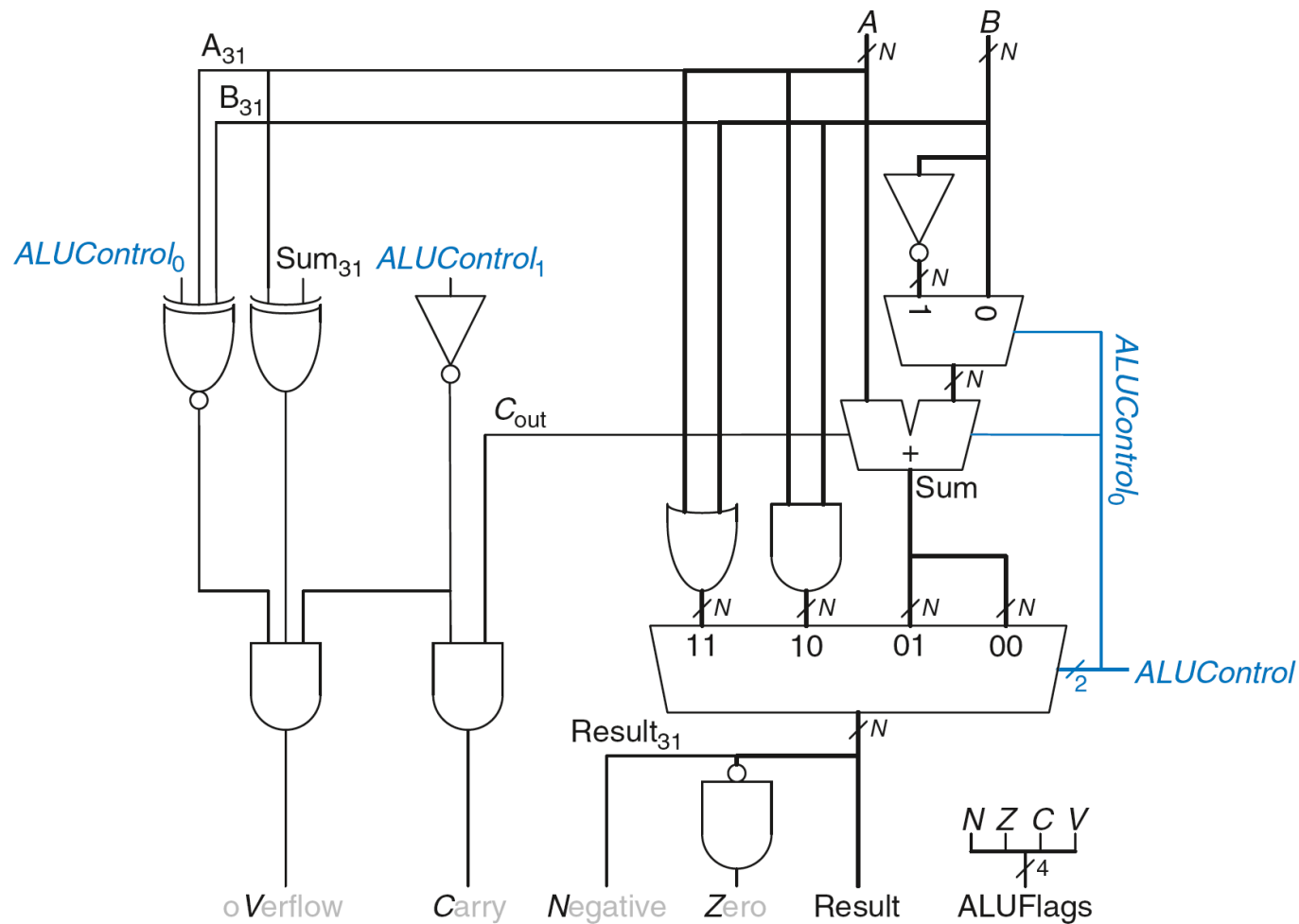

Single-Cycle Control: Decoder

Submodules:

 - Main Decoder
- **ALU Decoder**
- PC Logic



Control Unit: ALU Decoder

ALUOp	Funct _{4:1} (cmd)	Funct ₀ (S)	Type	ALUControl _{1:0}	FlagW _{1:0}
0	X	X	Not DP	00	00
1	0100	0	ADD	00	00
		1			11
	0010	0	SUB	01	00
		1			11
	0000	0	AND	10	00
		1			10
	1100	0	ORR	11	00
		1			10


- $FlagW_1 = 1$: NZ ($Flags_{3:2}$) should be saved
- $FlagW_0 = 1$: CV ($Flags_{1:0}$) should be saved




Single-Cycle Control: Decoder

Submodules:

 
- Main Decoder
- ALU Decoder
- **PC Logic**




Single-Cycle Control

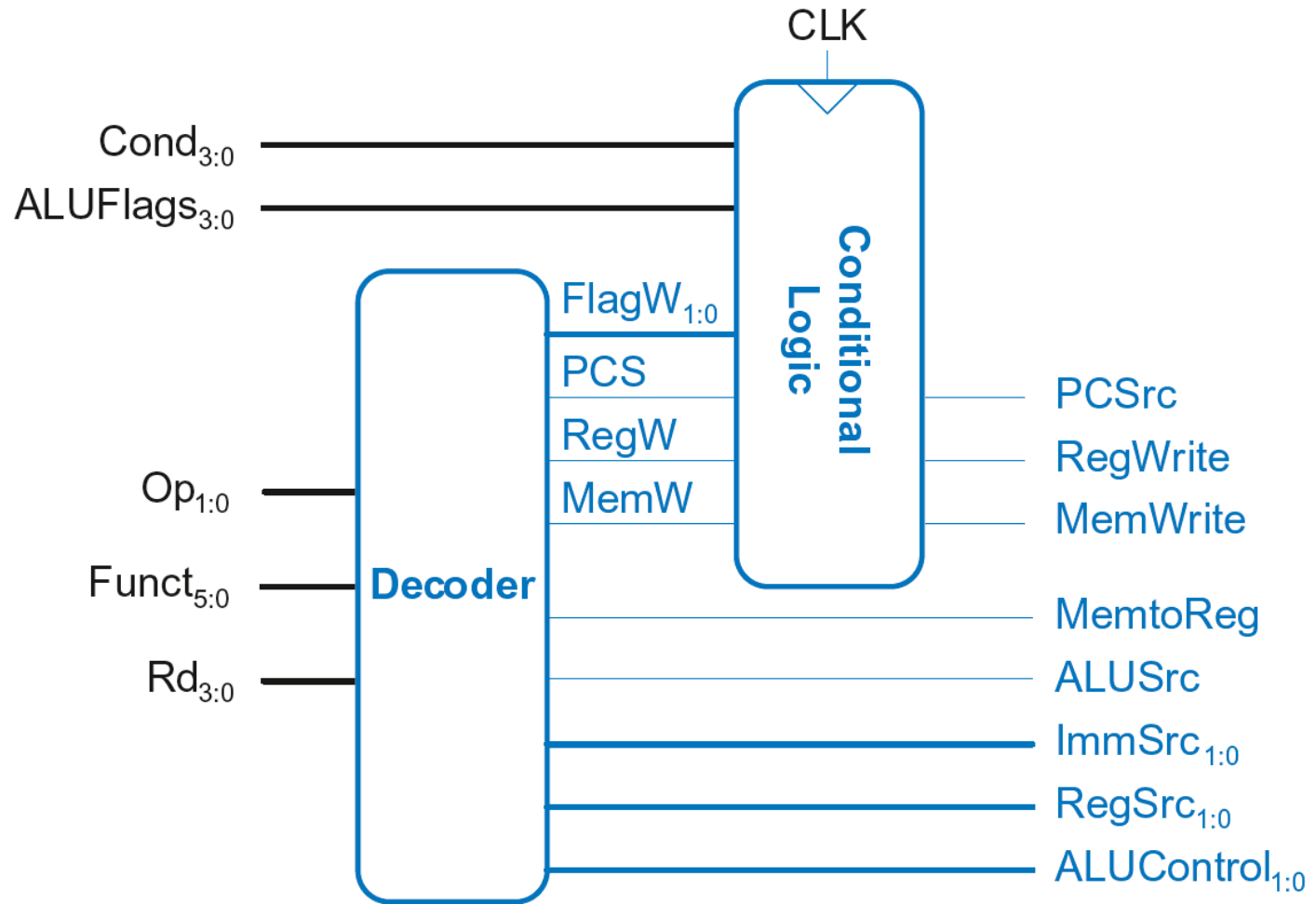

Single-Cycle Control: Cond. Logic

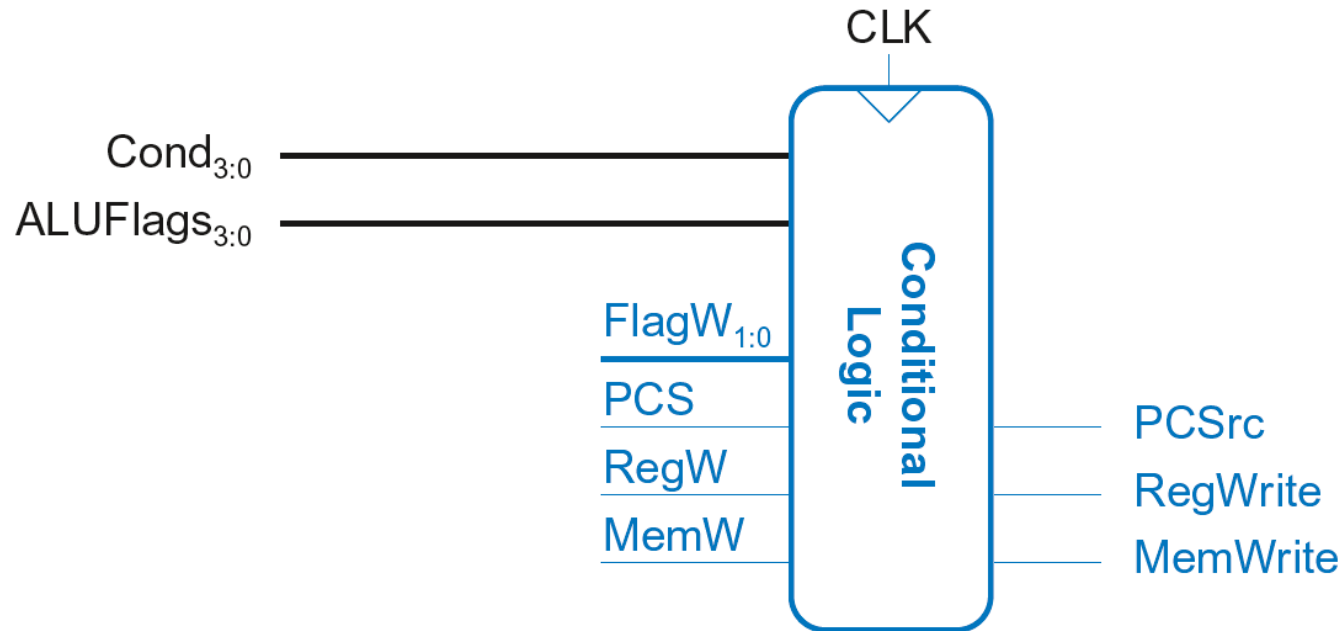

Conditional Logic

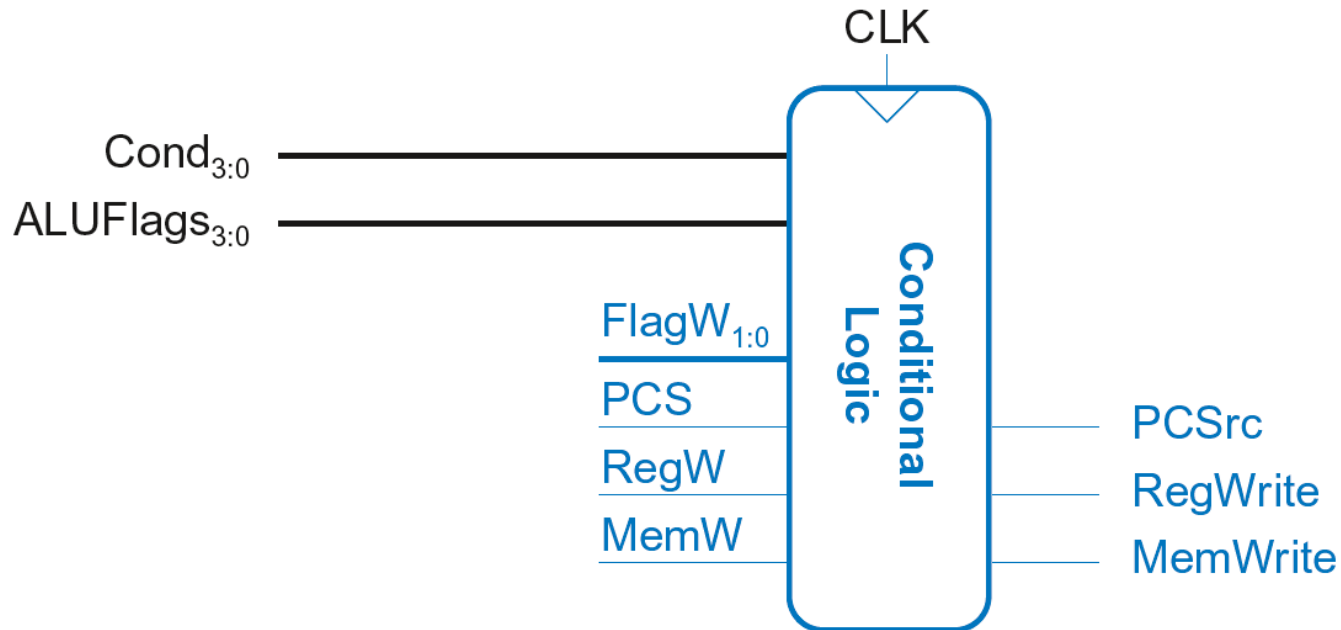


Function:

1. Check if instruction should execute (if not, force PCSrc, RegWrite, and MemWrite to 0)
2. Possibly update Status Register (Flags_{3:0})



Conditional Logic

 


Function:


1. Check if instruction should execute (if not, force PCSrc, RegWrite, and MemWrite to 0)
2. Possibly update Status Register (Flags_{3:0})



Single-Cycle Control: Conditional Logic

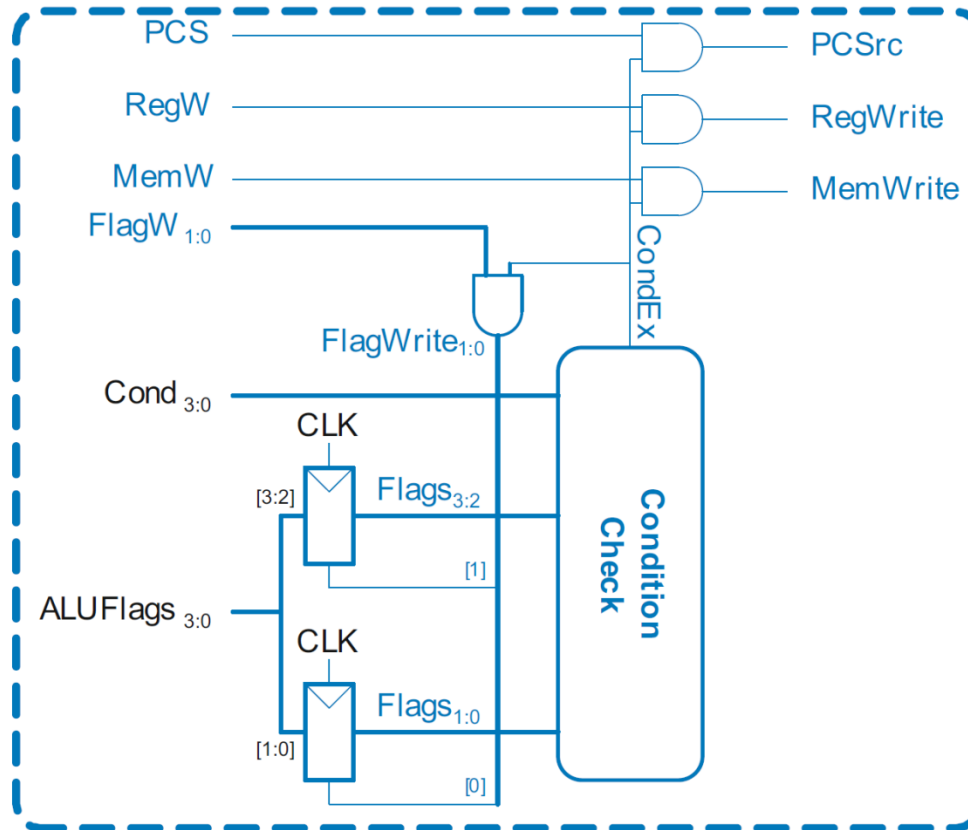

Conditional Logic: Conditional Execution

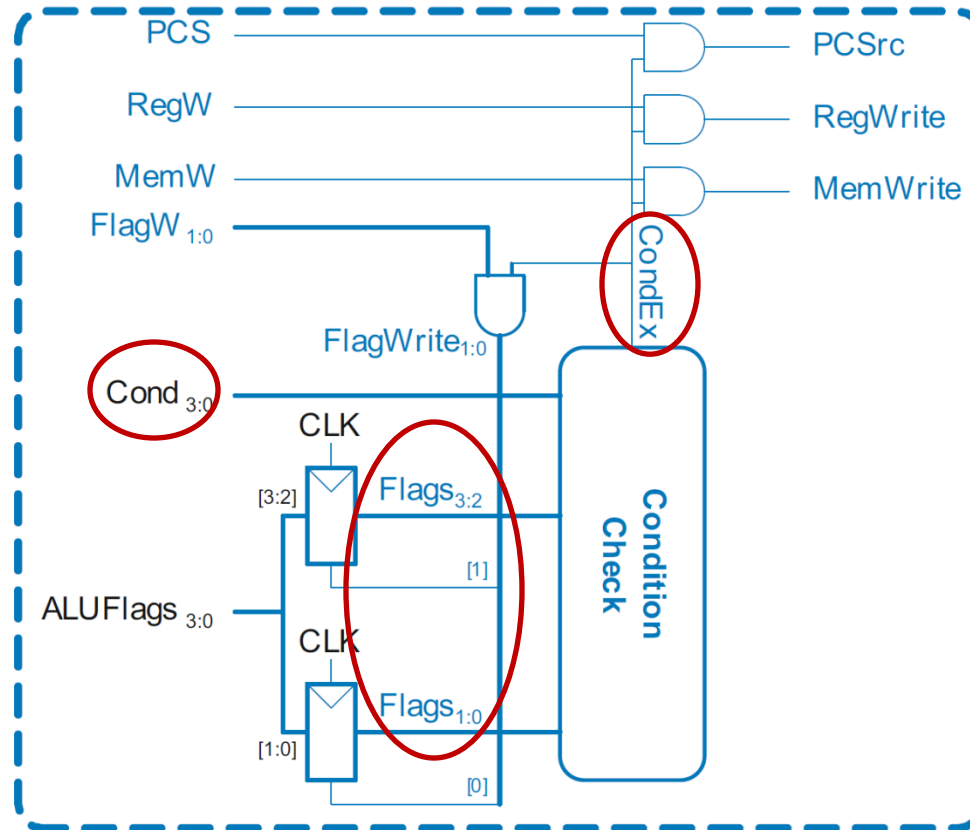


Depending on condition mnemonic (***Cond***_{3:0}) and condition flags (***Flags***_{3:0}) the instruction is executed (***CondEx*** = 1)



Conditional Logic: Conditional Execution

Flags_{3:0} is the status register

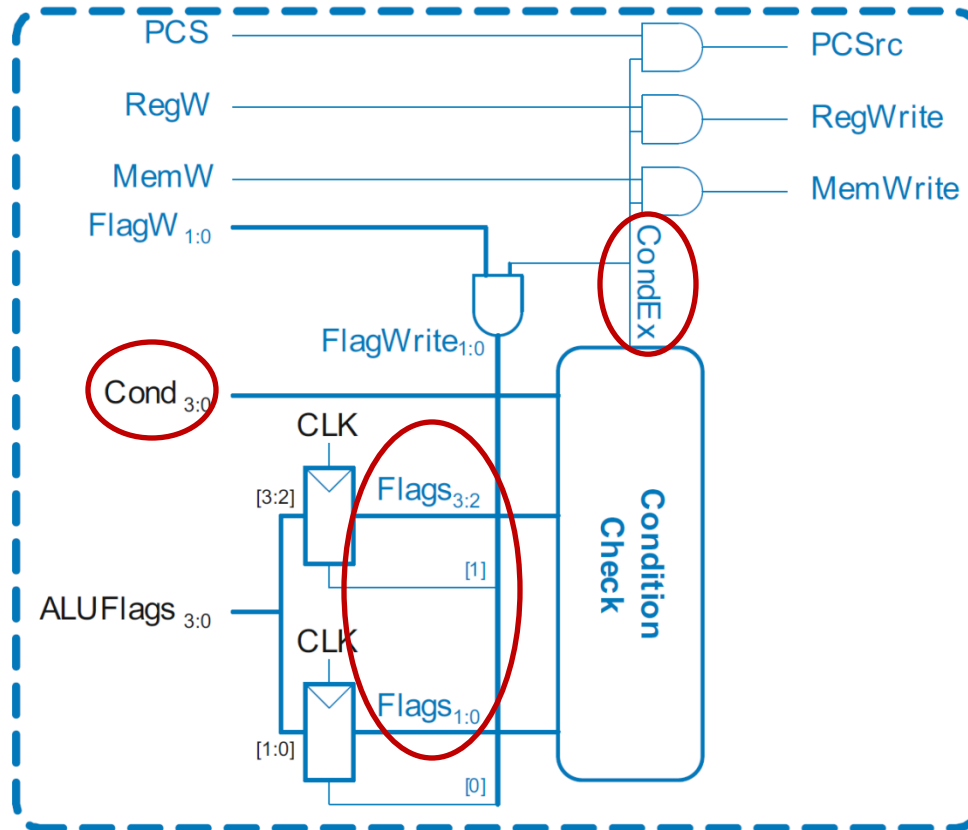

Depending on condition mnemonic (**Cond_{3:0}**) and condition flags (**Flags_{3:0}**) the instruction is executed (**CondEx = 1**)




Review: Condition Mnemonics

cond	Mnemonic	Name	CondEx
0000	EQ	Equal	Z
0001	NE	Not equal	\bar{Z}
0010	CS/HS	Carry set / unsigned higher or same	C
0011	CC/LO	Carry clear / unsigned lower	\bar{C}
0100	MI	Minus / negative	N
0101	PL	Plus / positive or zero	\bar{N}
0110	VS	Overflow / overflow set	V
0111	VC	No overflow / overflow clear	\bar{V}
1000	HI	Unsigned higher	$\bar{Z}C$
1001	LS	Unsigned lower or same	$Z \text{ OR } \bar{C}$
1010	GE	Signed greater than or equal	$\bar{N} \oplus \bar{V}$
1011	LT	Signed less than	$N \oplus V$
1100	GT	Signed greater than	$\bar{Z}(\bar{N} \oplus \bar{V})$
1101	LE	Signed less than or equal	$Z \text{ OR } (N \oplus V)$
1110	AL (or none)	Always / unconditional	Ignored



Conditional Logic: Conditional Execution

$\text{Flags}_{3:0} = \text{NZCV}$

 

Example:

AND R1, R2, R3


$\text{Cond}_{3:0} = 1110$ (unconditional)

$\Rightarrow \text{CondEx} = 1$



Conditional Logic: Conditional Execution

Flags_{3:0} = NZCV

 


Example:

EOREQ R5, R6, R7

Cond_{3:0}=0000 (EQ): if Flags = x1xx => **CondEx** = 1



Conditional Logic

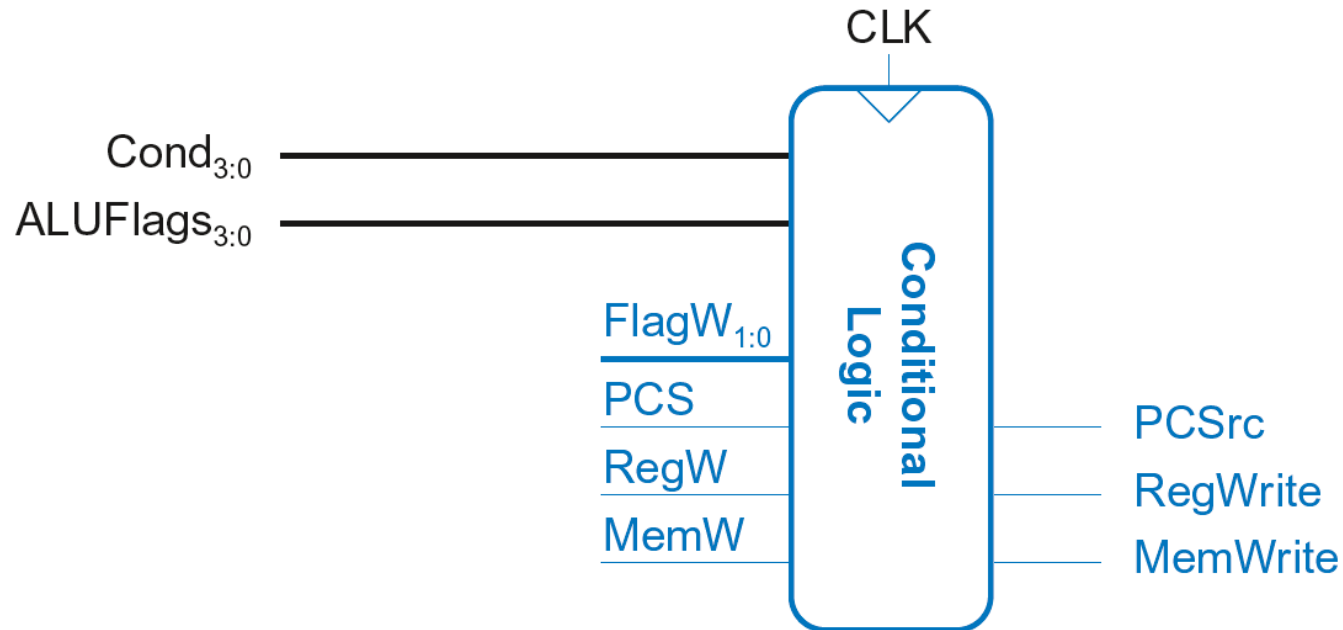


Function:

1. Check if instruction should execute (if not, force PCSrc, RegWrite, and MemWrite to 0)
2. **Possibly update Status Register (Flags_{3:0})**



Conditional Logic: Update (Set) Flags

$\text{Flags}_{3:0} = \text{NZCV}$

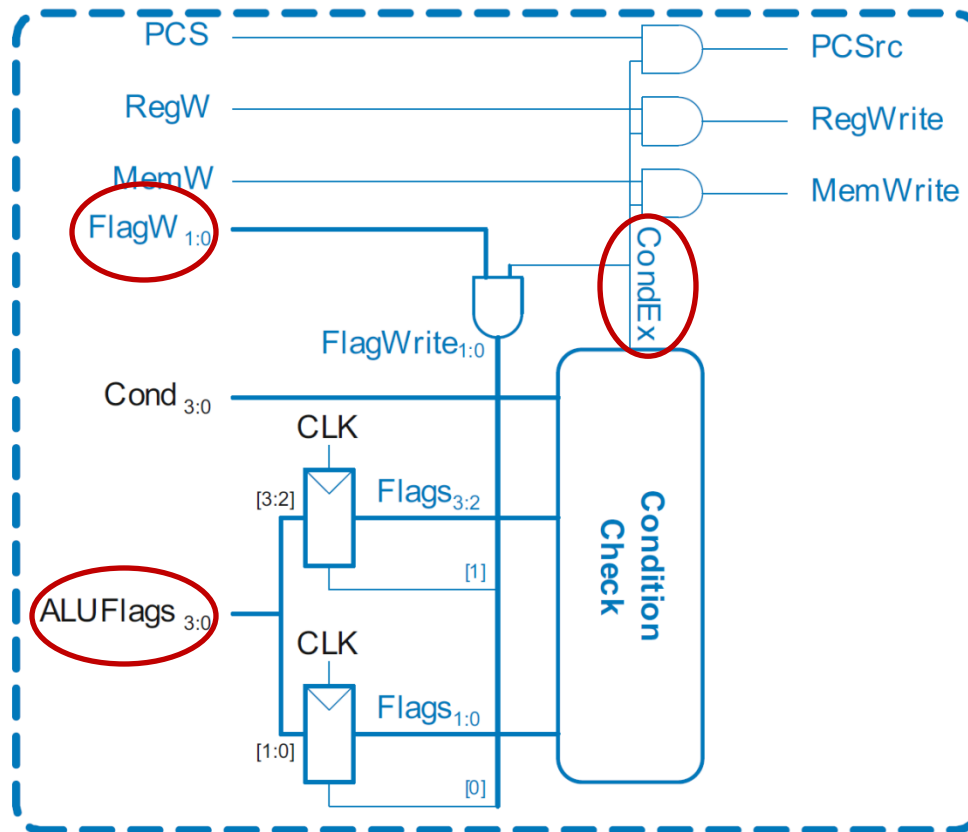


$\text{Flags}_{3:0}$ updated (with $\text{ALUFlags}_{3:0}$) if:

- **FlagW** is 1 (i.e., the instruction's S-bit is 1) AND
- **CondEx** is 1 (the instruction should be executed)



Conditional Logic: Update (Set) Flags

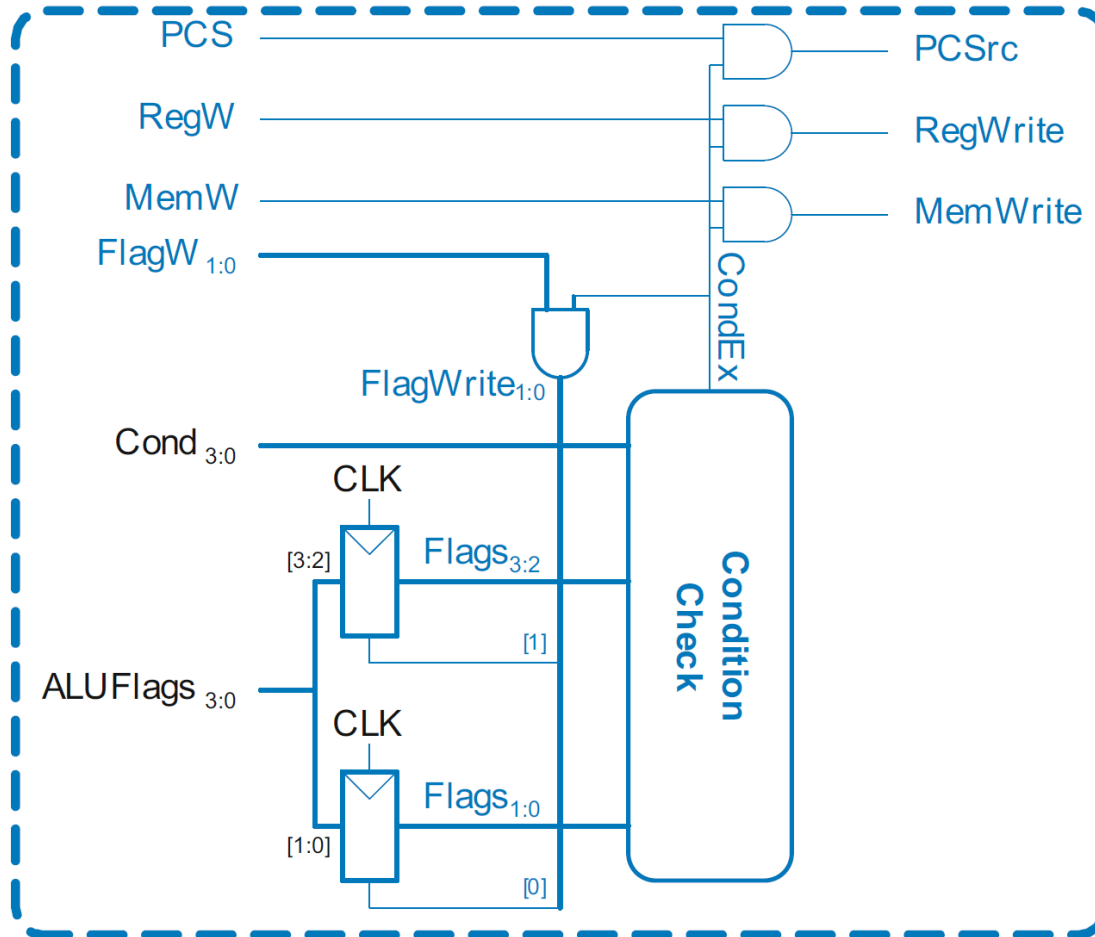

Recall:

- ADD, SUB update **all** Flags
- AND, OR update **NZ only**
- So Flags status register has two write enables:
FlagW_{1:0}



Review: ALU Decoder


ALUOp	Funct _{4:1} (cmd)	Funct ₀ (S)	Type	ALUControl _{1:0}	FlagW _{1:0}
0	X	X	Not DP	00	00
1	0100	0	ADD	00	00
		1			11
	0010	0	SUB	01	00
		1			11
	0000	0	AND	10	00
		1			10
	1100	0	ORR	11	00
		1			10

- $FlagW_1 = 1$: NZ ($Flags_{3:2}$) should be saved
- $FlagW_0 = 1$: CV ($Flags_{1:0}$) should be saved



Conditional Logic: Update (Set) Flags

All Flags updated

 

Example: SUBS R5, R6, R7


FlagW_{1:0} = 11 AND CondEx = 1 (unconditional) => FlagWrite_{1:0} = 11



Conditional Logic: Update (Set) Flags

$\text{Flags}_{3:0} = \text{NZCV}$

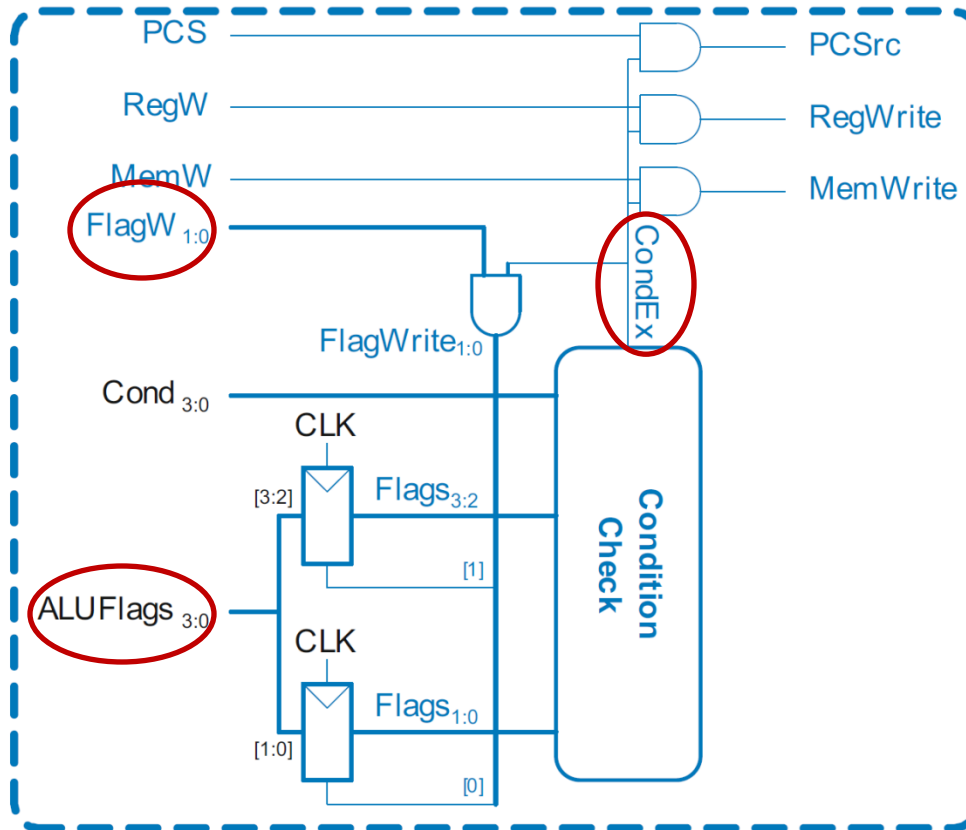- Only $\text{Flags}_{3:2}$ updated
- i.e., only **NZ** Flags updated




Example: `ANDS R7, R1, R3`

$\text{FlagW}_{1:0} = 10$ AND $\text{CondEx} = 1$ (unconditional) $\Rightarrow \text{FlagWrite}_{1:0} = 10$




Example: ORR


Op	Functs	Funct ₀	Type	Branch	MementoReg	Mem W	ALUSrc	ImmSrc	RegW	RegSrc	ALUOp
00	0	X	DP Reg	0	0	0	0	XX	1	00	1

 


Example: ORR

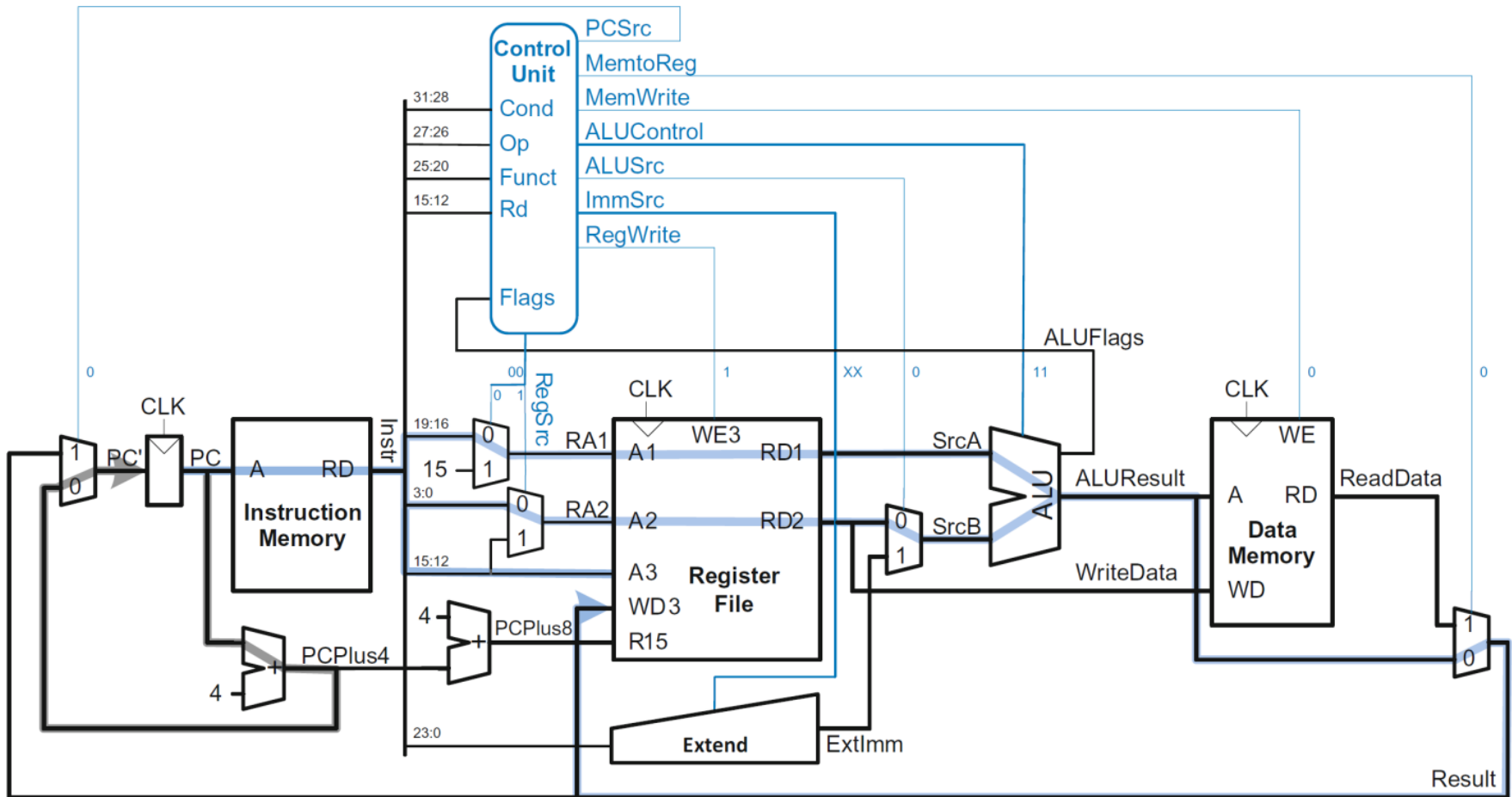

Extended Functionality: CMP

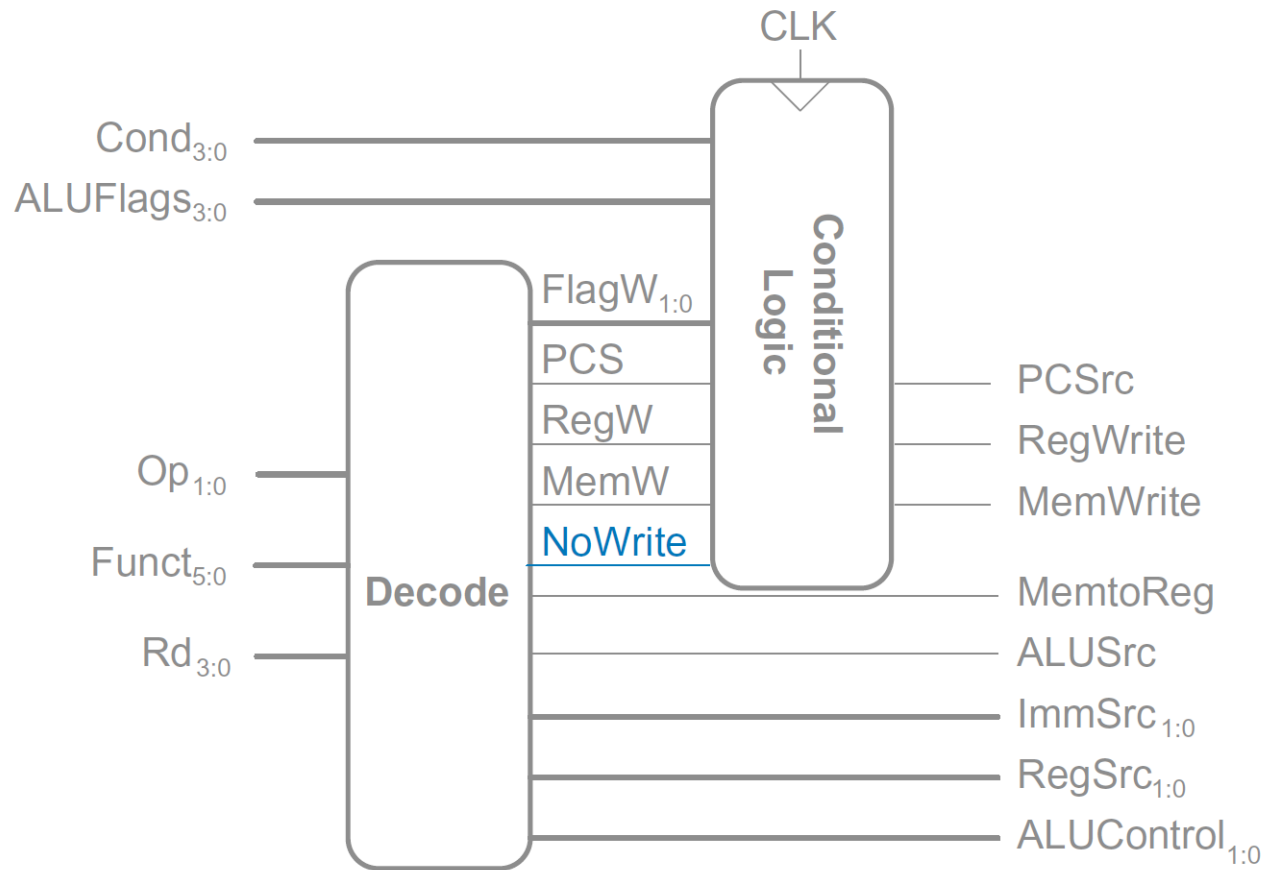


Extended Functionality: CMP

 

No change to datapath



Extended Functionality: CMP

 


Extended Functionality: CMP

ALUOp	Funct _{4:1} (cmd)	Funct ₀ (S)	Type	ALUControl _{1:0}	FlagW _{1:0}	NoWrite
0	X	X	Not DP	00	00	0
1	0100	0	ADD	00	00	0
		1			11	0
	0010	0	SUB	01	00	0
		1			11	0
	0000	0	AND	10	00	0
		1			10	0
	1100	0	ORR	11	00	0
		1			10	0
1010	1	1	CMP	01	11	1



Extended Functionality: Shifted Register

 


ADD R7, R2, R12, LSR #5

31:28	27:26	25	24:21	20	19:16	15:12	11:7	6:5	4	3:0	
14	0	0	4	0	2	7	5	01 ₂	0	12	
cond		op		I		cmd		S		rn	
		rd		shamt5		sh				rm	



Extended Functionality: Shifted Register

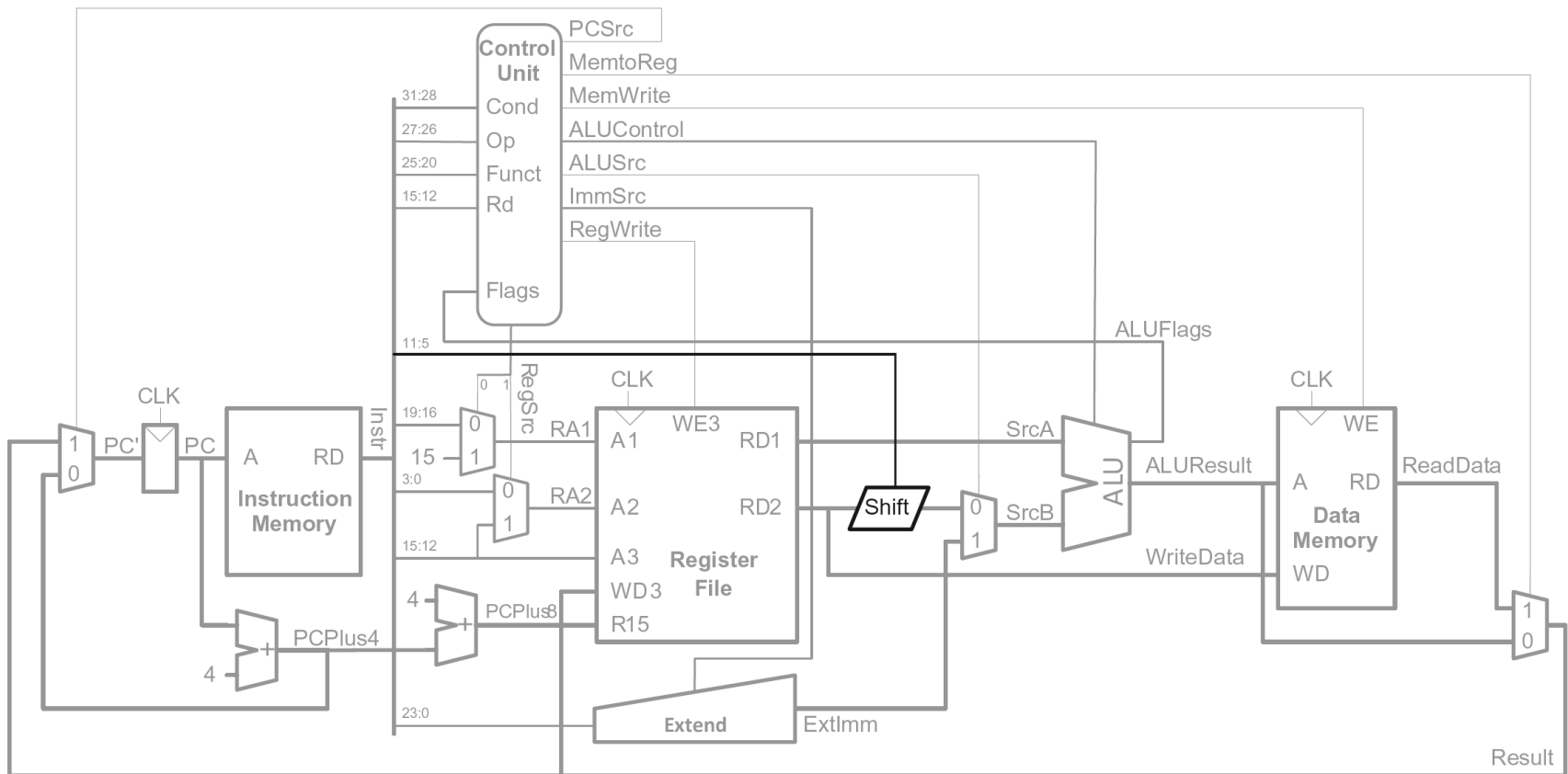

No change to controller



Review: Processor Performance


Program Execution Time

$$= (\# \text{instructions})(\text{cycles/instruction})(\text{seconds/cycle})$$

$$= \# \text{ instructions} \times \text{CPI} \times T_C$$



Single-Cycle Performance

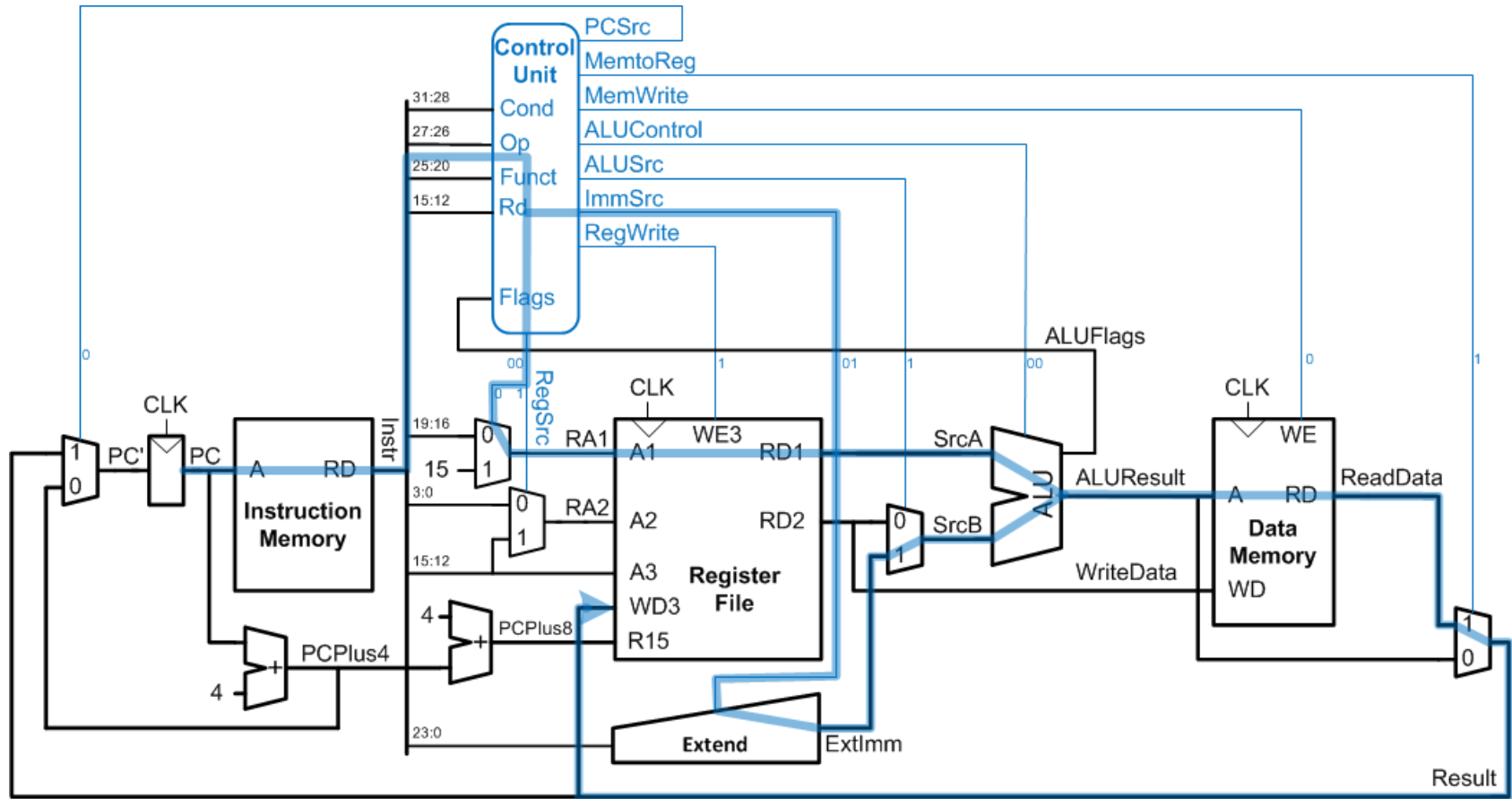

T_c limited by critical path (LDR)



Single-Cycle Performance

- **Single-cycle critical path:**

$$T_{cl} = t_{pcq_PC} + t_{mem} + t_{dec} + \max[t_{mux} + t_{RFread}, t_{sext} + t_{mux}] + t_{ALU} + t_{mem} + t_{mux} + t_{RFsetup}$$

- **Typically, limiting paths are:**

- memory, ALU, register file

- $T_{cl} = t_{pcq_PC} + 2t_{mem} + t_{dec} + t_{RFread} + t_{ALU} + 2t_{mux} + t_{RFsetup}$



Single-Cycle Performance Example

Element	Parameter	Delay (ps)
Register clock-to-Q	t_{pcq_PC}	40
Register setup	t_{setup}	50
Multiplexer	t_{mux}	25
ALU	t_{ALU}	120
Decoder	t_{dec}	70
Memory read	t_{mem}	200
Register file read	t_{RFread}	100
Register file setup	$t_{RFsetup}$	60

$$T_{cl} = ?$$



Single-Cycle Performance Example

Element	Parameter	Delay (ps)
Register clock-to-Q	t_{pcq_PC}	40
Register setup	t_{setup}	50
Multiplexer	t_{mux}	25
ALU	t_{ALU}	120
Decoder	t_{dec}	70
Memory read	t_{mem}	200
Register file read	t_{RFread}	100
Register file setup	$t_{RFsetup}$	60

$$\begin{aligned}T_{c1} &= t_{pcq_PC} + 2t_{mem} + t_{dec} + t_{RFread} + t_{ALU} + 2t_{mux} + t_{RFsetup} \\ &= [40 + 2(200) + 70 + 100 + 120 + 2(25) + 60] \text{ ps} \\ &= \mathbf{840 \text{ ps}}\end{aligned}$$



Single-Cycle Performance Example

Program with 100 billion instructions:

$$\begin{aligned}\text{Execution Time} &= \# \text{ instructions} \times \text{CPI} \times T_C \\ &= (100 \times 10^9)(1)(840 \times 10^{-12} \text{ s}) \\ &= \mathbf{84 \text{ seconds}}\end{aligned}$$

