 


# E85 Digital Design & Computer Engineering



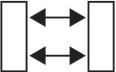
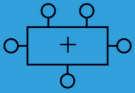

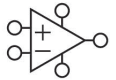




## Lecture 4: Finite State Machines

**HARVEY  
MUDD  
COLLEGE**

# Lecture 4

- **Finite State Machines**

Application Software	<code>&gt;"hello world!"</code>
Operating Systems	
Architecture	
Micro-architecture	
<b>Logic</b>	
Digital Circuits	
Analog Circuits	
Devices	
Physics	




# Synchronous Sequential Logic Design

- Breaks cyclic paths by **inserting registers**
- Registers contain **state** of the system
- State changes at clock edge: system **synchronized** to the clock
- **Rules** of synchronous sequential circuit composition:
  - Every circuit element is either a register or a combinational circuit
  - At least one circuit element is a register
  - All registers receive the same clock signal
  - Every cyclic path contains at least one register
- Two common synchronous sequential circuits
  - Finite State Machines (FSMs)
  - Pipelines


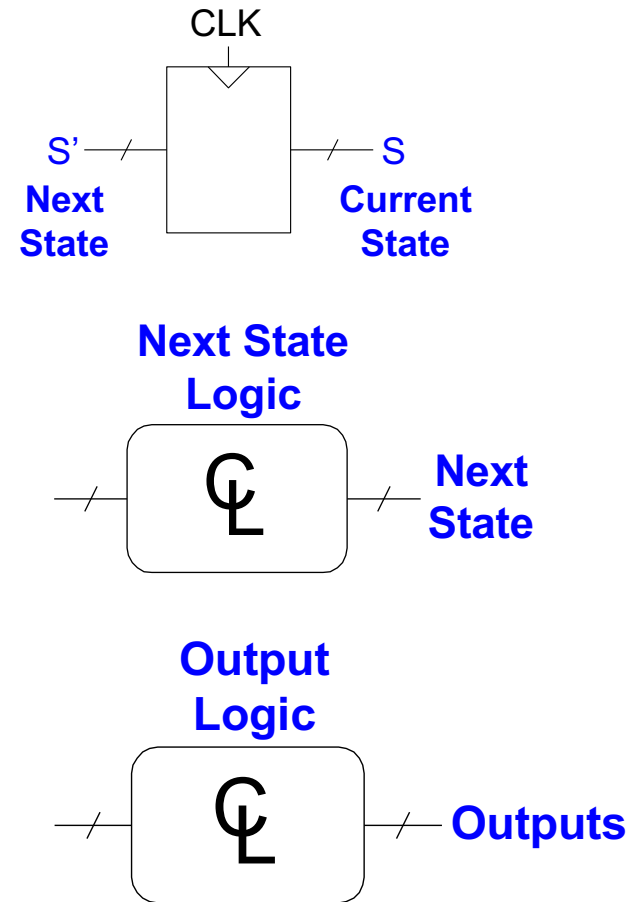
# Finite State Machine (FSM)


- Consists of:
  - **State register**
    - Stores current state
    - Loads next state at clock edge
  - **Combinational logic**
    - Computes the next state
    - Computes the outputs




# Finite State Machines (FSMs)

- **Next state** determined by current state and inputs
- Two types of finite state machines differ in **output logic**:
  - **Moore FSM**: outputs depend only on current state
  - **Mealy FSM**: outputs depend on current state *and* inputs

Moore FSM

 


Mealy FSM

 

 
# FSM Example

- Traffic light controller
  - Traffic sensors:  $T_A$ ,  $T_B$  (TRUE when there's traffic)
  - Lights:  $L_A$ ,  $L_B$



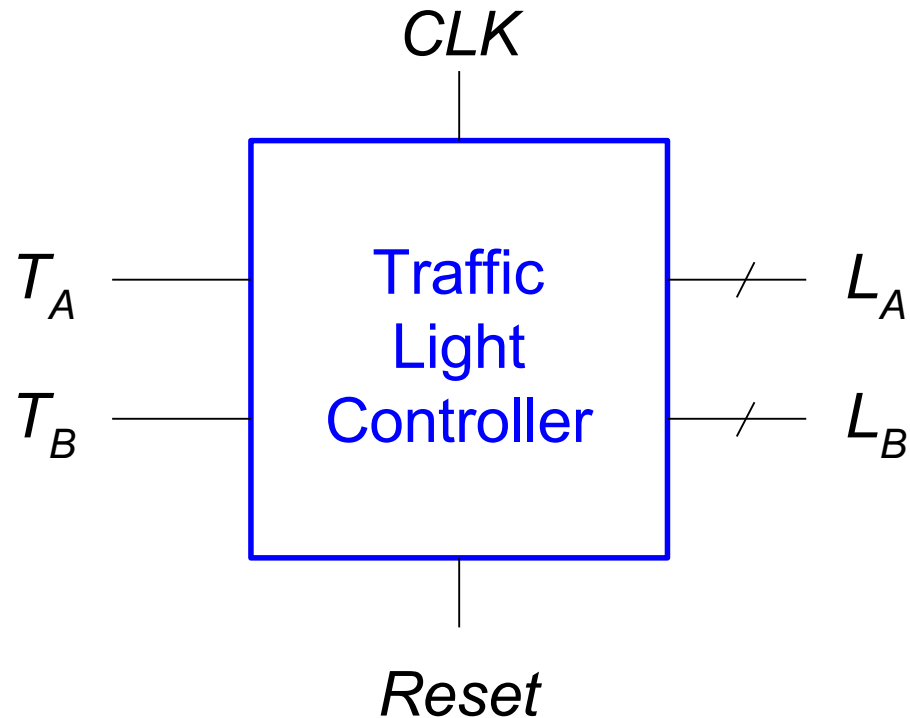
# FSM Black Box

- Inputs:  $CLK$ ,  $Reset$ ,  $T_A$ ,  $T_B$
- Outputs:  $L_A$ ,  $L_B$


 
# FSM State Transition Diagram


- **Moore FSM:** outputs labeled in each state
- **States:** Circles
- **Transitions:** Arcs





 
# FSM State Transition Diagram

- **Moore FSM:** outputs labeled in each state
- **States:** Circles
- **Transitions:** Arcs



# FSM State Transition Table

Current State	Inputs		Next State
	$T_A$	$T_B$	
S0	0	X	
S0	1	X	
S1	X	X	
S2	X	0	
S2	X	1	
S3	X	X	

 


# FSM Encoded State Transition Table

Current State		Inputs		Next State	
$S_1$	$S_0$	$T_A$	$T_B$	$S'_1$	$S'_0$
0	0	0	X		
0	0	1	X		
0	1	X	X		
1	0	X	0		
1	0	X	1		
1	1	X	X		

State	Encoding
S0	00
S1	01
S2	10
S3	11

$S'_1 =$

$S'_0 =$

 

# FSM Output Table

Current State		Outputs			
$S_1$	$S_0$	$L_{A1}$	$L_{A0}$	$L_{B1}$	$L_{B0}$
0	0				
0	1				
1	0				
1	1				


$L_{A1} =$

$L_{A0} =$


$L_{B1} =$

$L_{B0} =$


Output	Encoding
green	00
yellow	01
red	10

 


# FSM Schematic: State Register

 

# FSM Schematic: Next State Logic

 

# FSM Schematic: Output Logic

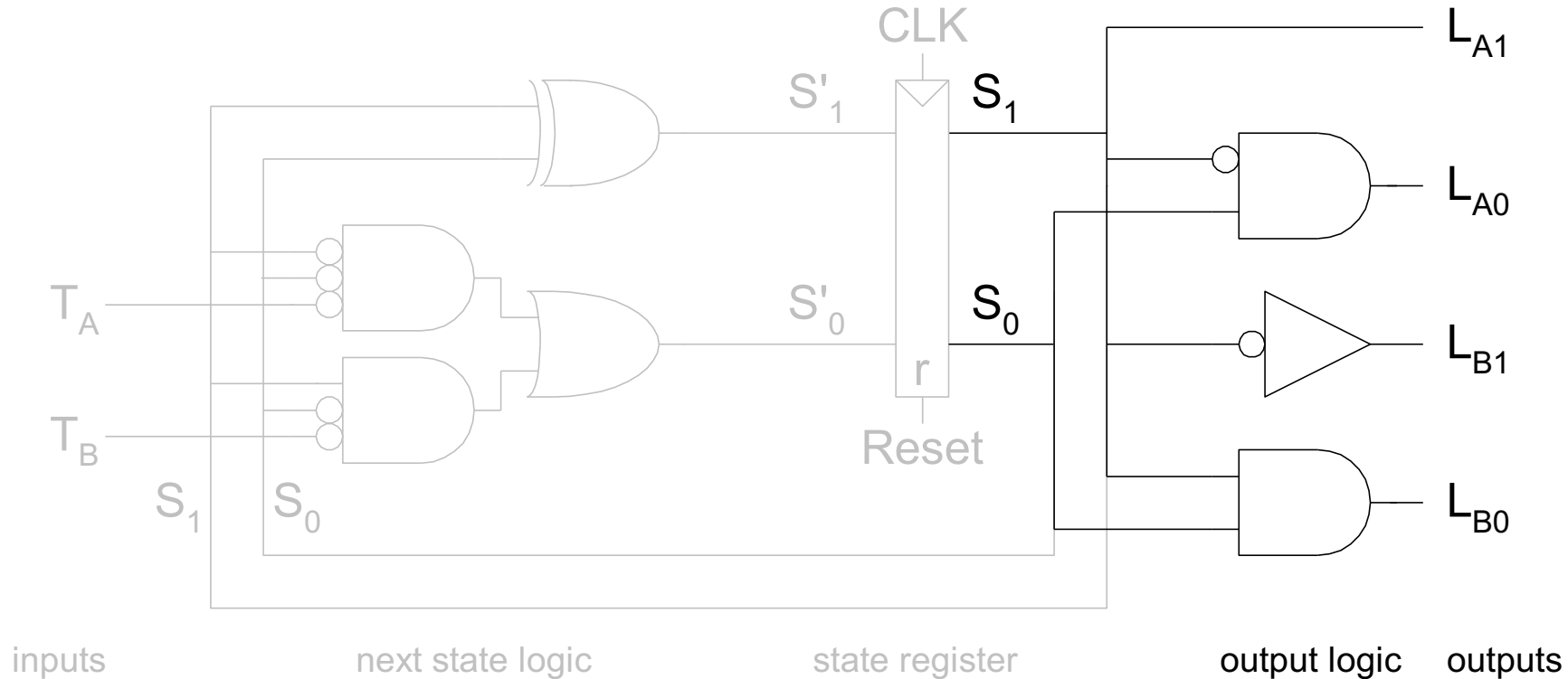

# SystemVerilog Description

```
module trafficFSM(input  logic      clk, reset,
                 input  logic      ta, tb,
                 output logic [1:0] la, lb);
    logic [1:0] state, nextstate, sb;
    logic      tab, tbb, p1, p2;

    // state register
    flopr #(2) statereg(clk, reset, nextstate, state);

    // next state logic
    not n0(sb[0], s[0]);
    not n1(sb[1], s[1]);
    not n2(tab, ta);
    not n3(tbb, tb);
    xor x1(nextstate[1], state[0], state[1]);
    and a1(p1, sb[0], sb[1], tab);
    and a2(p2, sb[0], s[1], tbb);
    or  o1(nextstate[0], p1, p2);



    // output logic
    buf b1(la[1], s[1]);
    and a3(la[0], s[0], sb[1]);
    inv n4(lb[1], s[1]);
    and a4(lb[0], s[0], s[1]);
endmodule
```

- Multi-input XOR: Odd parity





# FSM Timing Diagram

  

# FSM State Encoding


- **Binary** encoding:
  - i.e., for four states, 00, 01, 10, 11
- **One-hot** encoding
  - One state bit per state
  - Only one state bit HIGH at once
  - i.e., for 4 states, 0001, 0010, 0100, 1000
  - Requires more flip-flops
  - Often next state and output logic is simpler






# State Transition Diagrams

## Moore FSM

 

## Mealy FSM

 


Mealy FSM: arcs indicate input/output

# Moore FSM State Transition Table

Current State		Inputs	Next State	
$S_1$	$S_0$		$S'_1$	$S'_0$
0	0	0		
0	0	1		
0	1	0		
0	1	1		
1	0	0		
1	0	1		

State	Encoding
S0	00
S1	01
S2	10

Moore FSM

 

$S'_1 =$

$S'_0 =$




# Moore FSM Output Table

Current State		Output
$S_1$	$S_0$	$Y$
0	0	
0	1	
1	0	

$Y =$

## Moore FSM

 

# Mealy FSM State Transition & Output Table


Current State	Input	Next State	Output
$S_0$	$A$	$S'_0$	$Y$
0	0	-	-
0	1	-	-
1	0	-	-
1	1	-	-

State	Encoding
$S_0$	0
$S_1$	1


**Mealy FSM**

$$S'_0 =$$


$$Y =$$

 

# Moore

 


# Mealy

 



# Moore & Mealy Timing Diagram

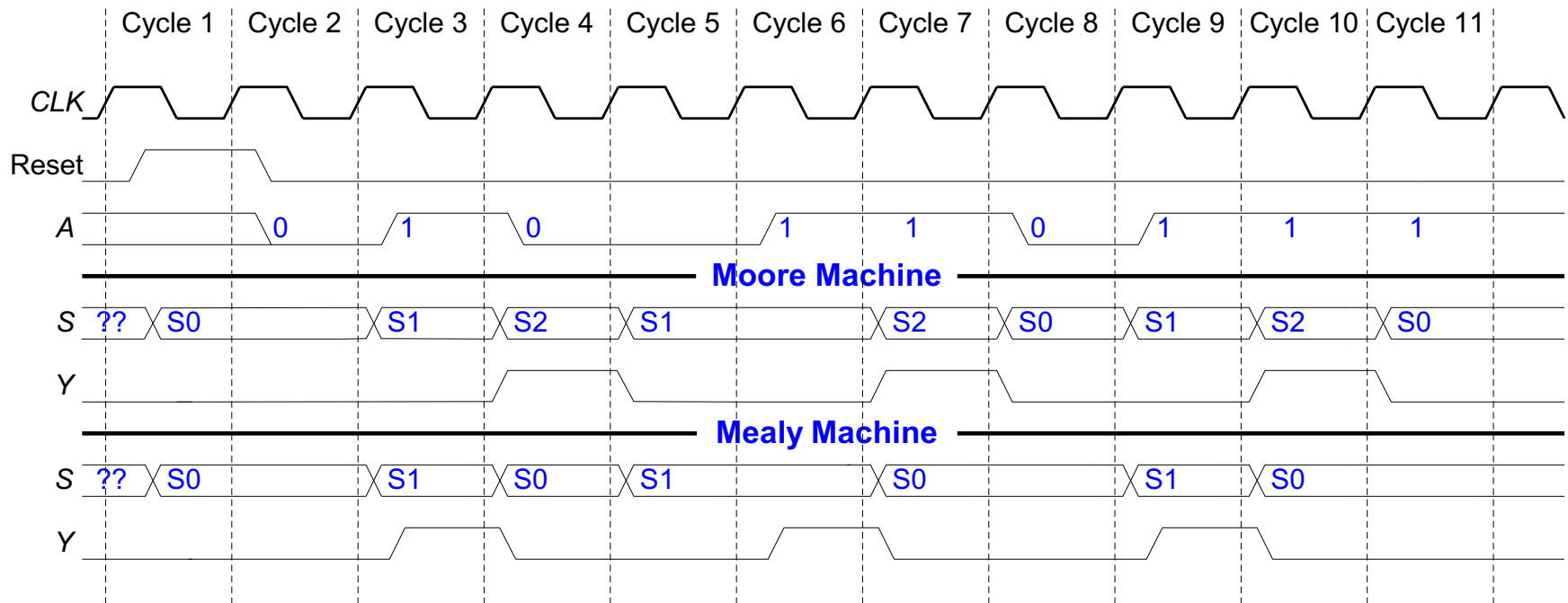

# Factoring State Machines

- Break complex FSMs into smaller interacting FSMs
- Example: Modify traffic light controller to have Parade Mode.
  - Two more inputs:  $P$ ,  $R$
  - When  $P = 1$ , enter Parade Mode & Bravado Blvd light stays green
  - When  $R = 1$ , leave Parade Mode




# Parade FSM


## Unfactored FSM




## Factored FSM

 


# Unfactored FSM

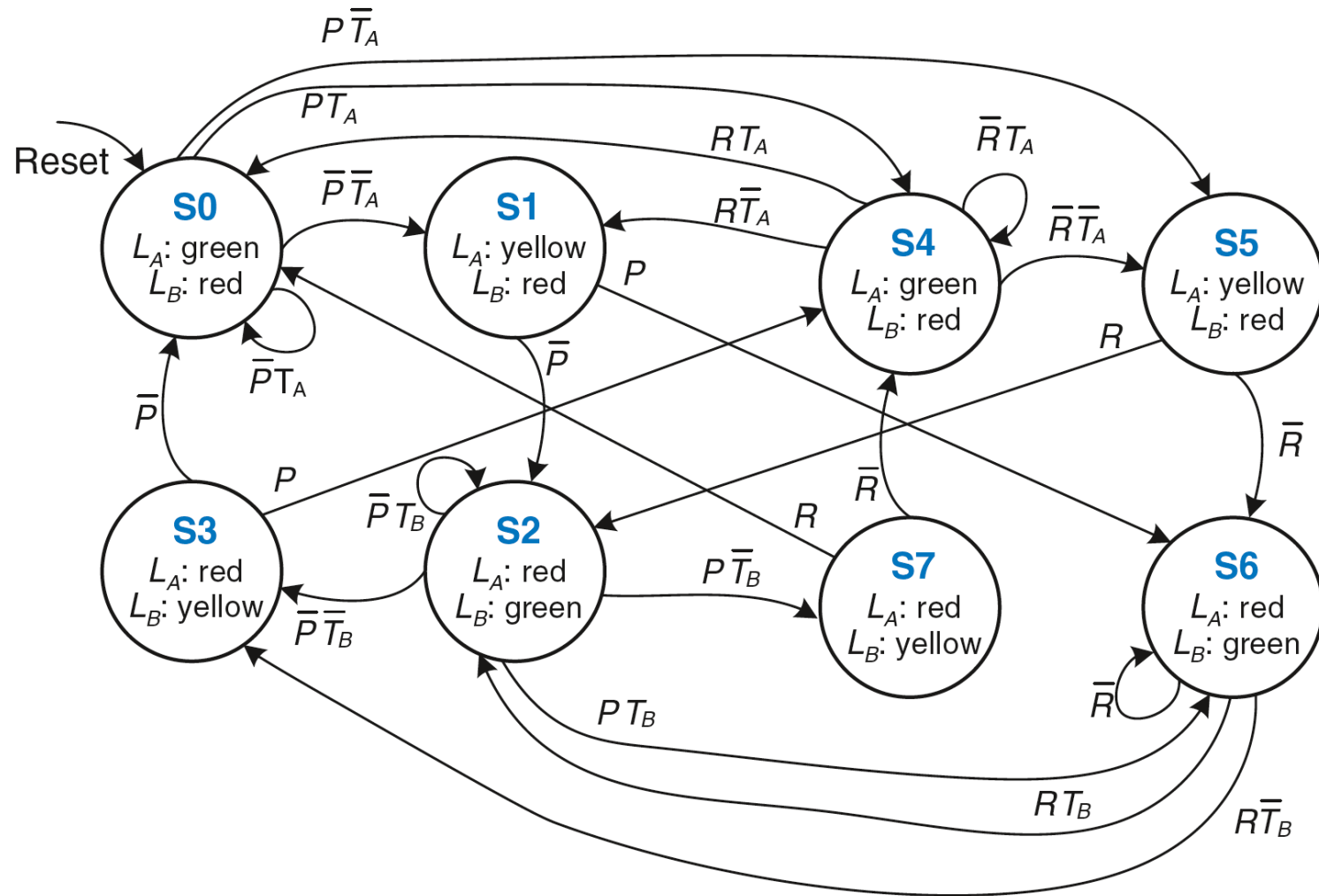

# Factored FSM

 

Lights FSM

 

Mode FSM



# FSM Design Procedure

1. Identify inputs and outputs
2. Sketch state transition diagram
3. Write state transition table
4. Select state encodings
5. For Moore machine:
  - a. Rewrite state transition table with state encodings
  - b. Write output table
5. For a Mealy machine:

Rewrite combined state transition and output table with state encodings
6. Write Boolean equations for next state and output logic
7. Sketch the circuit schematic

