 


E85 Digital Design & Computer Engineering



Lecture 6: Hardware Description Languages: Verilog

**HARVEY
MUDD
COLLEGE**

Lecture 6

- Introduction
- Combinational Logic
- Structural Modeling
- Sequential Logic

Application Software	
Operating Systems	
Architecture	
Micro-architecture	
Logic	
Digital Circuits	
Analog Circuits	
Devices	
Physics	



Introduction

- Hardware description language (HDL):
 - specifies logic function only
 - Computer-aided design (CAD) tool produces or *synthesizes* the optimized gates
- Most commercial designs built using HDLs
- Two leading HDLs:
 - **SystemVerilog**
 - developed in 1984 by Gateway Design Automation
 - IEEE standard (1364) in 1995
 - Extended in 2005 (IEEE STD 1800-2009)
 - **VHDL 2008**
 - Developed in 1981 by the Department of Defense
 - IEEE standard (1076) in 1987
 - Updated in 2008 (IEEE STD 1076-2008)



HDL to Gates

- **Simulation**

- Inputs applied to circuit
- Outputs checked for correctness
- Millions of dollars saved by debugging in simulation instead of hardware

- **Synthesis**

- Transforms HDL code into a *netlist* describing the hardware (i.e., a list of gates and the wires connecting them)



HDL to Gates

- **Simulation**

- Inputs applied to circuit
- Outputs checked for correctness
- Millions of dollars saved by debugging in simulation instead of hardware


- **Synthesis**

- Transforms HDL code into a *netlist* describing the hardware (i.e., a list of gates and the wires connecting them)

IMPORTANT: When using an HDL, think of the **hardware** the HDL should implies



SystemVerilog Modules

 

Two types of Modules:

- **Behavioral:** describe what a module does
- **Structural:** describe how it is built from simpler modules



Behavioral SystemVerilog

SystemVerilog:

```
module example(input  logic a, b, c,  
               output logic y);  
    assign y = ~a & ~b & ~c | a & ~b & ~c | a & ~b & c;  
endmodule
```



Behavioral SystemVerilog

SystemVerilog:

```
module example(input  logic a, b, c,
               output logic y);
    assign y = ~a & ~b & ~c | a & ~b & ~c | a & ~b & c;
endmodule
```


- module/endmodule: required to begin/end module
- example: name of the module
- Operators:
 - ~: NOT
 - &: AND
 - |: OR



HDL Simulation

SystemVerilog:

```
module example(input logic a, b, c,  
               output logic y);  
    assign y = ~a & ~b & ~c | a & ~b & ~c | a & ~b & c;  
endmodule
```

 


HDL Synthesis

SystemVerilog:

```
module example(input  logic a, b, c,  
               output logic y);  
    assign y = ~a & ~b & ~c | a & ~b & ~c | a & ~b & c;  
endmodule
```

Synthesis:

 

SystemVerilog Syntax

- Case sensitive
 - **Example:** `reset` and `Reset` are not the same signal.
- No names that start with numbers
 - **Example:** `2mux` is an invalid name
- Whitespace ignored
- Comments:
 - `//` single line comment
 - `/*` multiline
comment `*/`



Structural Modeling - Hierarchy

```
module and3(input  logic a, b, c,  
           output logic y);  
    assign y = a & b & c;  
endmodule
```

```
module inv(input  logic a,  
          output logic y);  
    assign y = ~a;  
endmodule
```


```
module nand3(input  logic a, b, c  
            output logic y);  
    logic n1;                // internal signal  
  
    and3 andgate(a, b, c, n1); // instance of and3  
    inv  inverter(n1, y);      // instance of inv  
endmodule
```



Bitwise Operators

```
module gates(input logic [3:0] a, b,  
            output logic [3:0] y1, y2, y3, y4, y5);  
    /* Five different two-input logic  
       gates acting on 4 bit busses */  
    assign y1 = a & b;      // AND  
    assign y2 = a | b;     // OR  
    assign y3 = a ^ b;     // XOR  
    assign y4 = ~(a & b); // NAND  
    assign y5 = ~(a | b); // NOR  
endmodule
```

Synthesis:

 

// single line comment

/*...*/ multiline comment




Reduction Operators

SystemVerilog:

```
module and8(input  logic [7:0] a,  
           output logic      y);  
    assign y = &a;  
    // &a is much easier to write than  
    // assign y = a[7] & a[6] & a[5] & a[4] &  
    //           a[3] & a[2] & a[1] & a[0];  
endmodule
```

Synthesis:

 


Conditional Assignment

SystemVerilog:

```
module mux2(input  logic [3:0] d0, d1,  
            input  logic      s,  
            output logic [3:0] y);  
    assign y = s ? d1 : d0;  
endmodule
```

Synthesis:

 

? : is also called a *ternary operator* because it operates on 3 inputs: `s`, `d1`, and `d0`.



Internal Variables

SystemVerilog:


```
module fulladder(input  logic a, b, cin,
                 output logic s, cout);

    logic p, g;    // internal nodes

    assign p = a ^ b;
    assign g = a & b;

    assign s = p ^ cin;
    assign cout = g | (p & cin);
endmodule
```

Synthesis:

 

Precedence

Highest

~	NOT
*, /, %	mult, div, mod
+, -	add, sub
<<, >>	shift
<<<, >>>	arithmetic shift
<, <=, >, >=	comparison
==, !=	equal, not equal
&, ~&	AND, NAND
^, ~^	XOR, XNOR
, ~	OR, NOR
? :	ternary operator

Lowest



Numbers

Format: N'Bvalue

N = number of bits, **B** = base

N'B is optional but recommended (default is decimal)

Number	# Bits	Base	Decimal Equivalent	Stored
3'b101	3	binary	5	101
'b11	unsized	binary	3	00...0011
8'b11	8	binary	3	00000011
8'b1010_1011	8	binary	171	10101011
3'd6	3	decimal	6	110
6'o42	6	octal	34	100010
8'hAB	8	hexadecimal	171	10101011
42	Unsized	decimal	42	00...0101010



Bit Manipulations: Example 1

```
assign y = {a[2:1], {3{b[0]}}, a[0], 6'b100_010};
```

```
// if y is a 12-bit signal, the above statement produces:
```

```
y = a[2] a[1] b[0] b[0] b[0] a[0] 1 0 0 0 1 0
```

```
// underscores (_) are used for formatting only to make
```

```
// it easier to read. SystemVerilog ignores them.
```




Bit Manipulations: Example 2

SystemVerilog:

```
module mux2_8(input  logic [7:0] d0, d1,
             input  logic      s,
             output logic [7:0] y);

    mux2 lsbmux(d0[3:0], d1[3:0], s, y[3:0]);
    mux2 msbmux(d0[7:4], d1[7:4], s, y[7:4]);
endmodule
```

Synthesis:

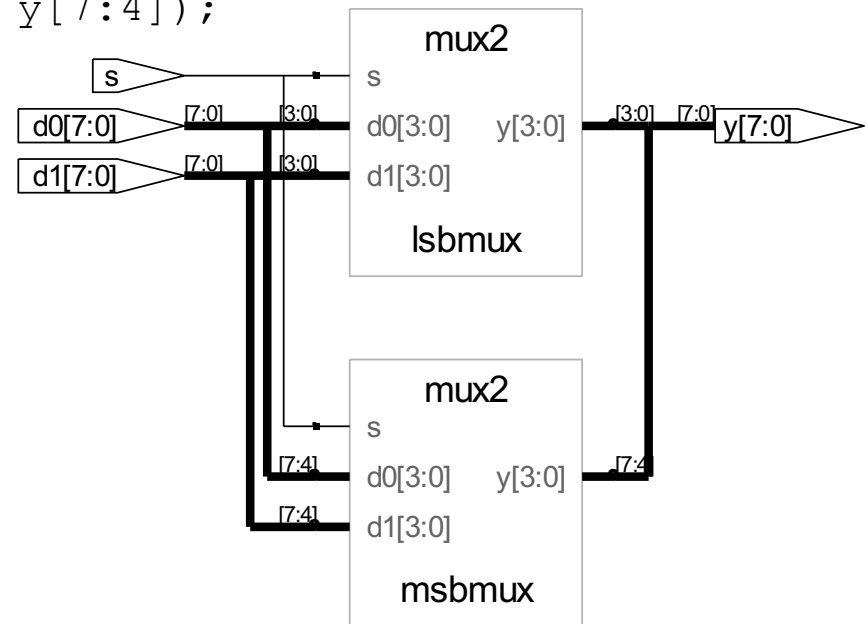


Z: Floating Output

SystemVerilog:


```
module tristate(input logic [3:0] a,  
               input logic      en,  
               output tri  [3:0] y);  
    assign y = en ? a : 4'bz;  
endmodule
```

Synthesis:

 


Delays

```
module example(input logic a, b, c,  
               output logic y);  
    logic ab, bb, cb, n1, n2, n3;  
    assign #1 {ab, bb, cb} = ~{a, b, c};  
    assign #2 n1 = ab & bb & cb;  
    assign #2 n2 = a & bb & cb;  
    assign #2 n3 = a & bb & c;  
    assign #4 y = n1 | n2 | n3;  
endmodule
```

 


Delays

```
module example(input logic a, b, c,  
               output logic y);  
    logic ab, bb, cb, n1, n2, n3;  
    assign #1 {ab, bb, cb} =  
             ~{a, b, c};  
    assign #2 n1 = ab & bb & cb;  
    assign #2 n2 = a & bb & cb;  
    assign #2 n3 = a & bb & c;  
    assign #4 y = n1 | n2 | n3;  
endmodule
```

 


Delays

```
module example(input logic a, b, c,  
               output logic y);  
    logic ab, bb, cb, n1, n2, n3;  
    assign #1 {ab, bb, cb} =  
        ~{a, b, c};  
    assign #2 n1 = ab & bb & cb;  
    assign #2 n2 = a & bb & cb;  
    assign #2 n3 = a & bb & c;  
    assign #4 y = n1 | n2 | n3;  
endmodule
```

 


Delays

```
module example(input logic a, b, c,  
               output logic y);  
    logic ab, bb, cb, n1, n2, n3;  
    assign #1 {ab, bb, cb} =  
             ~{a, b, c};  
    assign #2 n1 = ab & bb & cb;  
    assign #2 n2 = a & bb & cb;  
    assign #2 n3 = a & bb & c;  
    assign #4 y = n1 | n2 | n3;  
endmodule
```

 


Delays

```
module example(input logic a, b, c,  
               output logic y);  
    logic ab, bb, cb, n1, n2, n3;  
    assign #1 {ab, bb, cb} =  
             ~{a, b, c};  
    assign #2 n1 = ab & bb & cb;  
    assign #2 n2 = a & bb & cb;  
    assign #2 n3 = a & bb & c;  
    assign #4 y = n1 | n2 | n3;  
endmodule
```

 

Delays

```
module example(input logic a, b, c,  
               output logic y);  
    logic ab, bb, cb, n1, n2, n3;  
    assign #1 {ab, bb, cb} =  
             ~{a, b, c};  
    assign #2 n1 = ab & bb & cb;  
    assign #2 n2 = a & bb & cb;  
    assign #2 n3 = a & bb & c;  
    assign #4 y = n1 | n2 | n3;  
endmodule
```

 

Sequential Logic

- SystemVerilog uses **idioms** to describe latches, flip-flops and FSMs
- Other coding styles may simulate correctly but produce incorrect hardware



always Statement

General Structure:

```
always @(sensitivity list)
    statement;
```


Whenever the event in `sensitivity list` occurs,
statement is executed



D Flip-Flop

```
module flop(input logic clk,  
           input logic [3:0] d,  
           output logic [3:0] q);  
  
    always_ff @(posedge clk)  
        q <= d;           // pronounced "q gets d"  
  
endmodule
```

Synthesis:

 

Resettable D Flip-Flop


```
module flopr(input logic clk,  
            input logic reset,  
            input logic [3:0] d,  
            output logic [3:0] q);
```

```
// synchronous reset
```

```
always_ff @(posedge clk)  
    if (reset) q <= 4'b0;  
    else      q <= d;
```

```
endmodule
```


Synthesis:

 

Resettable D Flip-Flop

```
module flopr(input logic clk,  
            input logic reset,  
            input logic [3:0] d,  
            output logic [3:0] q);  
  
// asynchronous reset  
always_ff @(posedge clk, posedge reset)  
    if (reset) q <= 4'b0;  
    else      q <= d;  
  
endmodule
```

Synthesis:

 


D Flip-Flop with Enable

```
module flopren(input logic clk,  
               input logic reset,  
               input logic en,  
               input logic [3:0] d,  
               output logic [3:0] q);
```

```
// enable and asynchronous reset
```

```
always_ff @(posedge clk, posedge reset)  
    if (reset) q <= 4'b0;  
    else if (en) q <= d;
```


```
endmodule
```

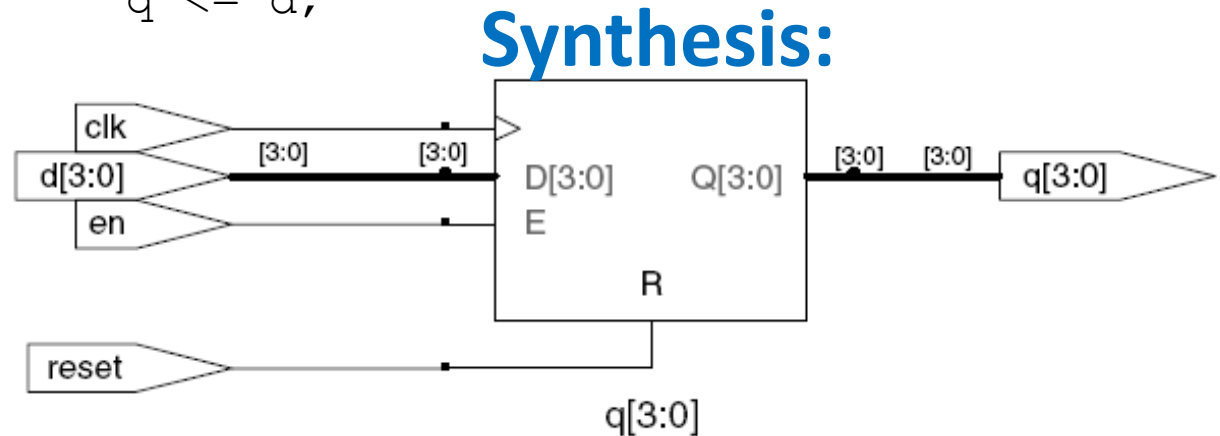

Latch

```
module latch(input logic clk,  
            input logic [3:0] d,  
            output logic [3:0] q);  
  
    always_latch  
        if (clk) q <= d;  
  
endmodule
```

Synthesis:

 

Warning: We don't use latches in this text. But you might write code that inadvertently implies a latch. Check synthesized hardware – if it has latches in it, there's an error.



Review

General Structure:

```
always @(sensitivity list)
    statement;
```

- **Flip-flop:** `always_ff`
- **Latch:** `always_latch` **(don't use)**

