


# ***Digital Design and Computer Architecture, RISC-V Edition***

---

David M. Harris and Sarah L. Harris

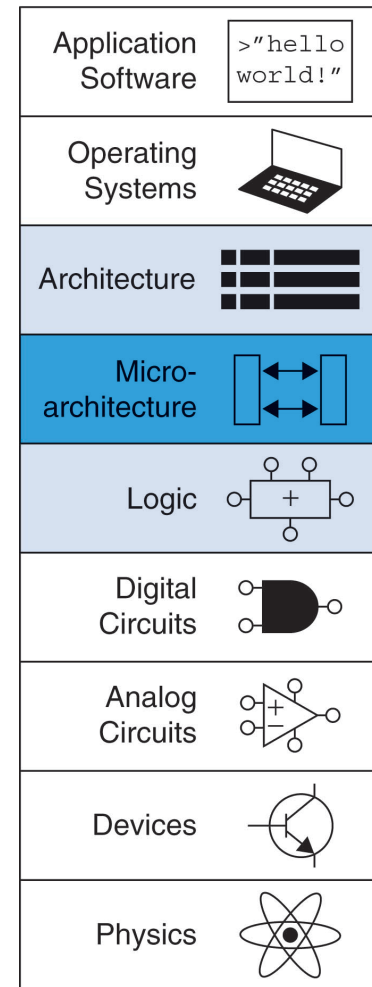
# Chapter 7 :: Microarchitecture

- Introduction
- Performance Analysis
- Single-Cycle Processor
- Multicycle Processor
- Pipelined Processor
- Advanced Microarchitecture


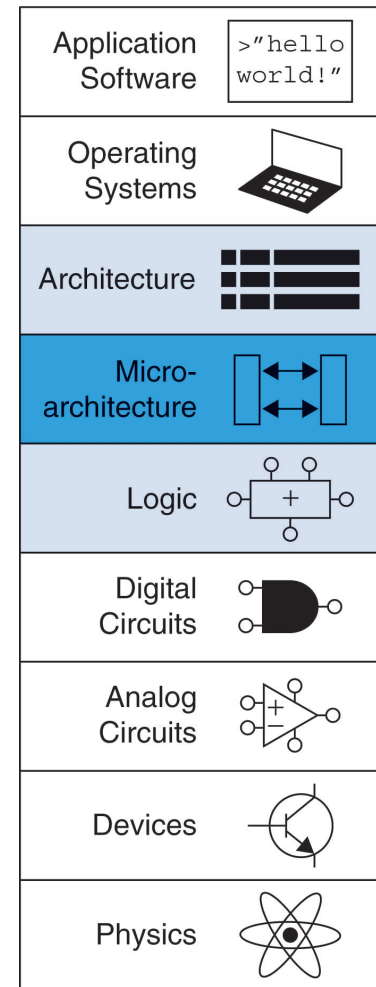
# Introduction

- **Microarchitecture:** how to implement an architecture in hardware
- Processor:
  - **Datapath:** functional blocks
  - **Control:** control signals



# Microarchitecture

- Multiple implementations for a single architecture:
  - **Single-cycle:** Each instruction executes in a single cycle
  - **Multicycle:** Each instruction is broken up into series of shorter steps
  - **Pipelined:** Each instruction broken up into series of steps & multiple instructions execute at once

# Processor Performance

- **Program execution time**

**Execution Time = (#instructions)(cycles/instruction)(seconds/cycle)**

- **Definitions:**

- CPI: Cycles/instruction
- clock period: seconds/cycle
- IPC: instructions/cycle = IPC

- **Challenge is to satisfy constraints of:**

- Cost
- Power
- Performance



# RISC-V Processor

- Consider **subset** of RISC-V instructions:
  - **R-type instructions:**
    - **add, sub, and, or, slt**
  - **I-type instruction:**
    - **lw**
  - **S-type instruction:**
    - **sw**
  - **B-type instructions:**
    - **beq**




# Architectural State Elements

## Determines everything about a processor:

– Architectural state:

- 32 registers
- PC
- Memory

# RISC-V Architectural State Elements

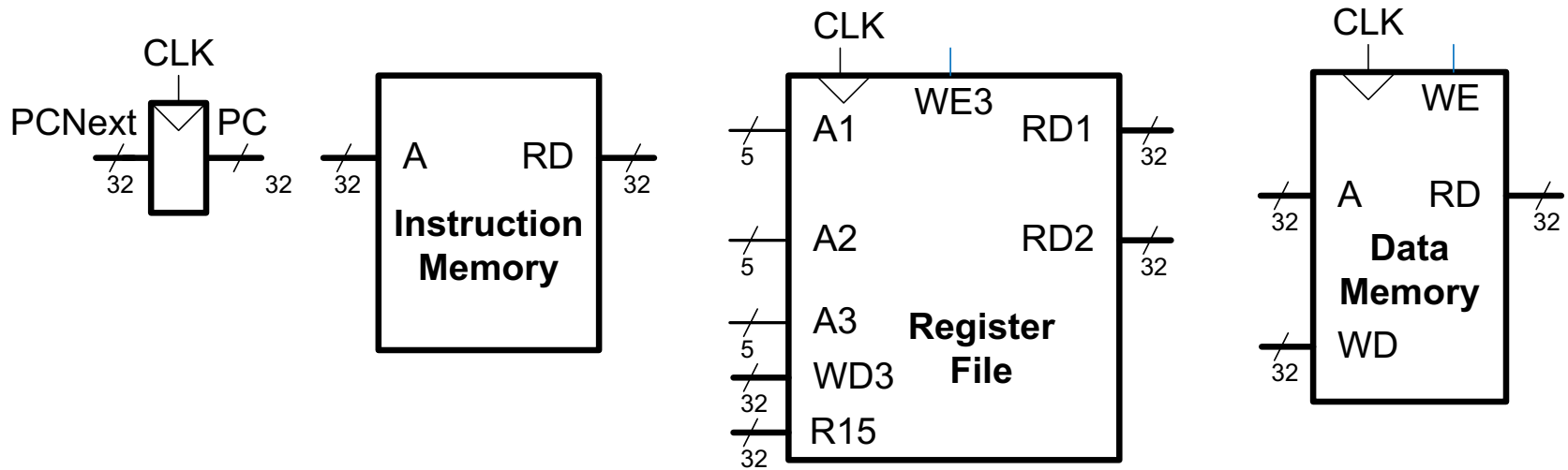



# Single-Cycle RISC-V Processor

- Datapath
- Control


# Single-Cycle RISC-V Processor

- **Datapath**
- Control


# RISC-V Processor

- **R-type instructions:**
  - `add`, `sub`, `and`, `or`, `slt`
- **I-type instruction:**
  - `lw`
- **S-type instruction:**
  - `sw`
- **B-type instructions:**
  - `beq`


## R-Type

 


## I-Type

 


## S-Type

 

## B-Type

 


# Single-Cycle RISC-V Datapath

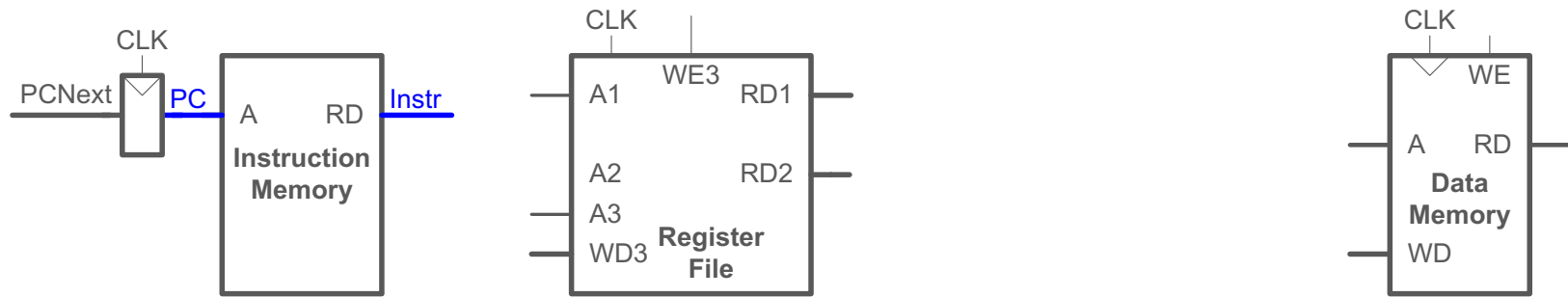

# Single-Cycle RISC-V Processor


- **Datapath:** start with `lw` instruction
- **Example:**  
`lw t2, -8(s3)`  
`lw rd, imm(rs1)`

## I-Type

 


# Single-Cycle Datapath: $1_w$ fetch

## STEP 1: Fetch instruction

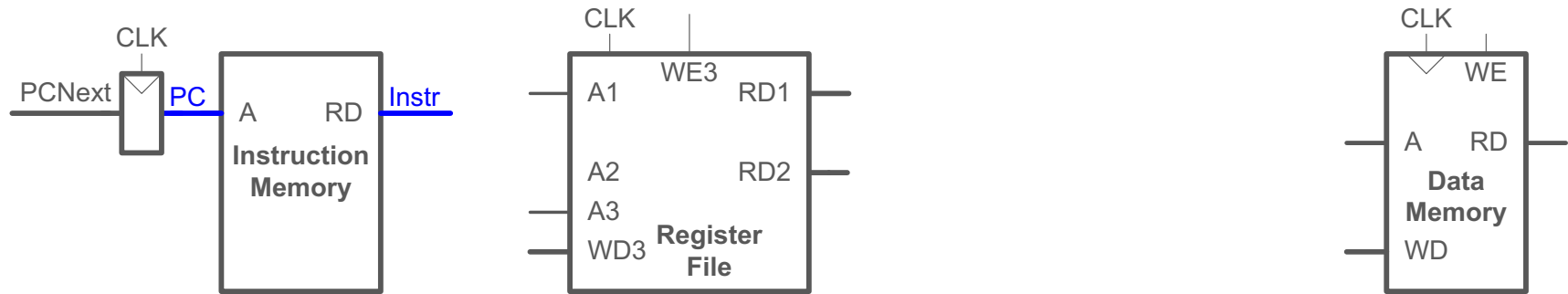

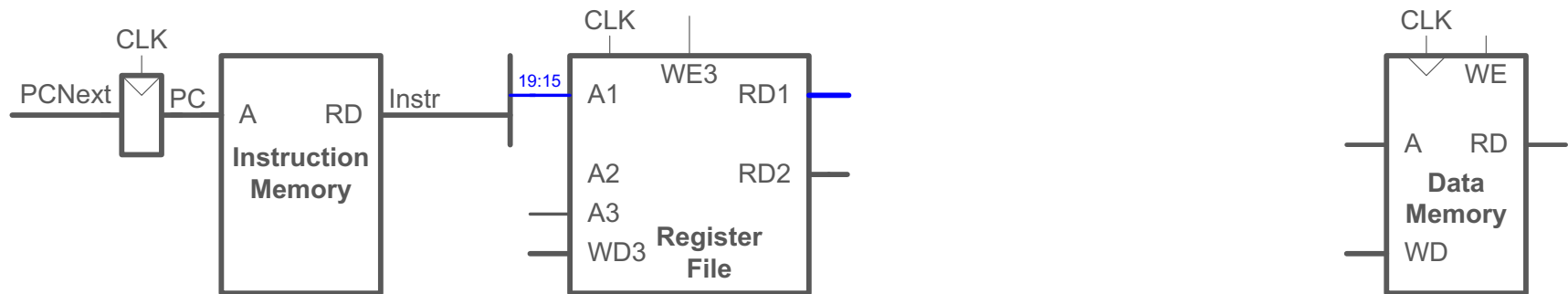
# Single-Cycle Datapath: $lw$ Reg Read

**STEP 2:** Read source operand (**rs1**) from RF




## I-Type

 

**$lw$  rd, imm(rs1)**

# Single-Cycle Datapath: $1_w$ Immediate


## STEP 3: Extend the immediate

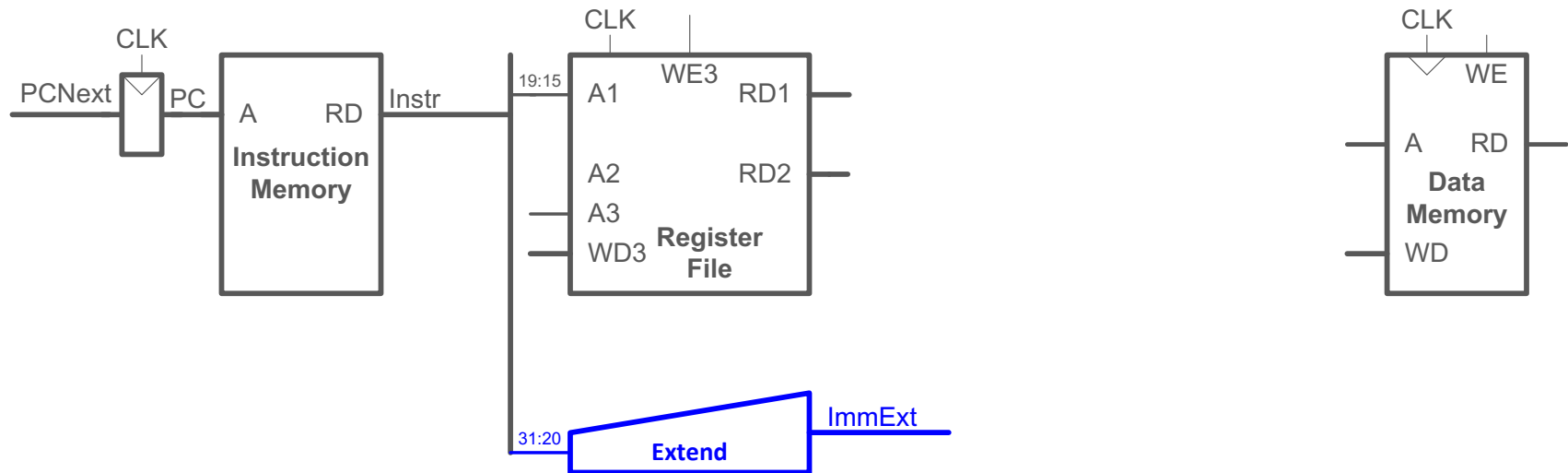




# Single-Cycle Datapath: $1_W$ Address

## STEP 4: Compute the memory address

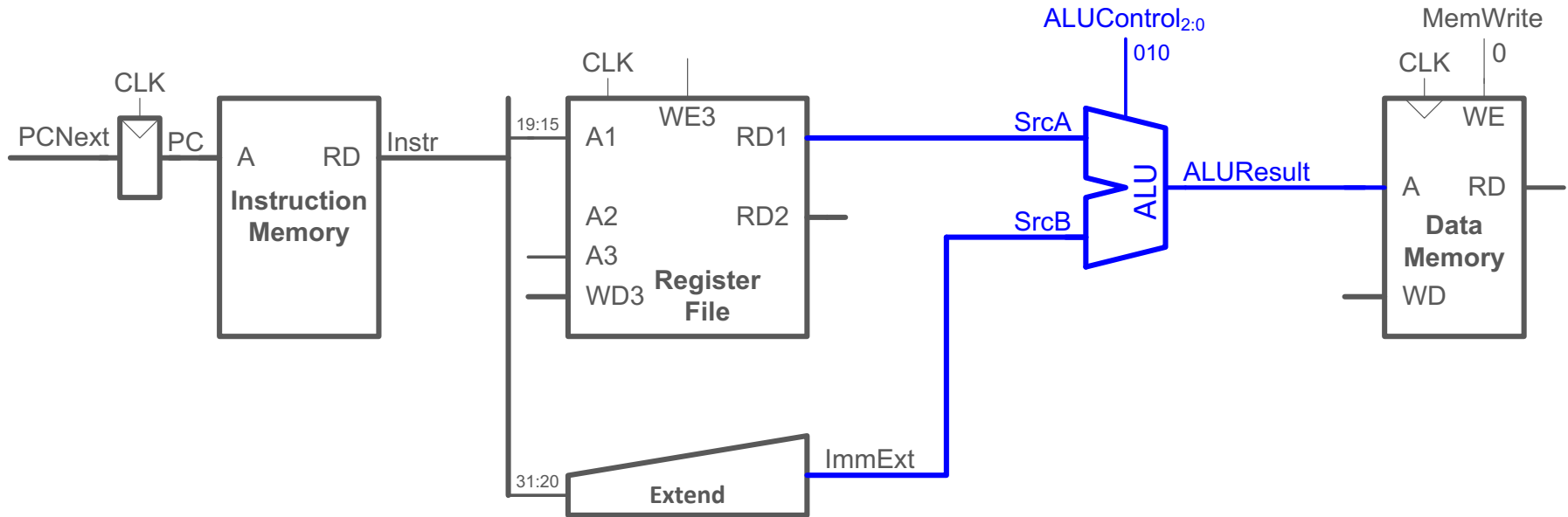

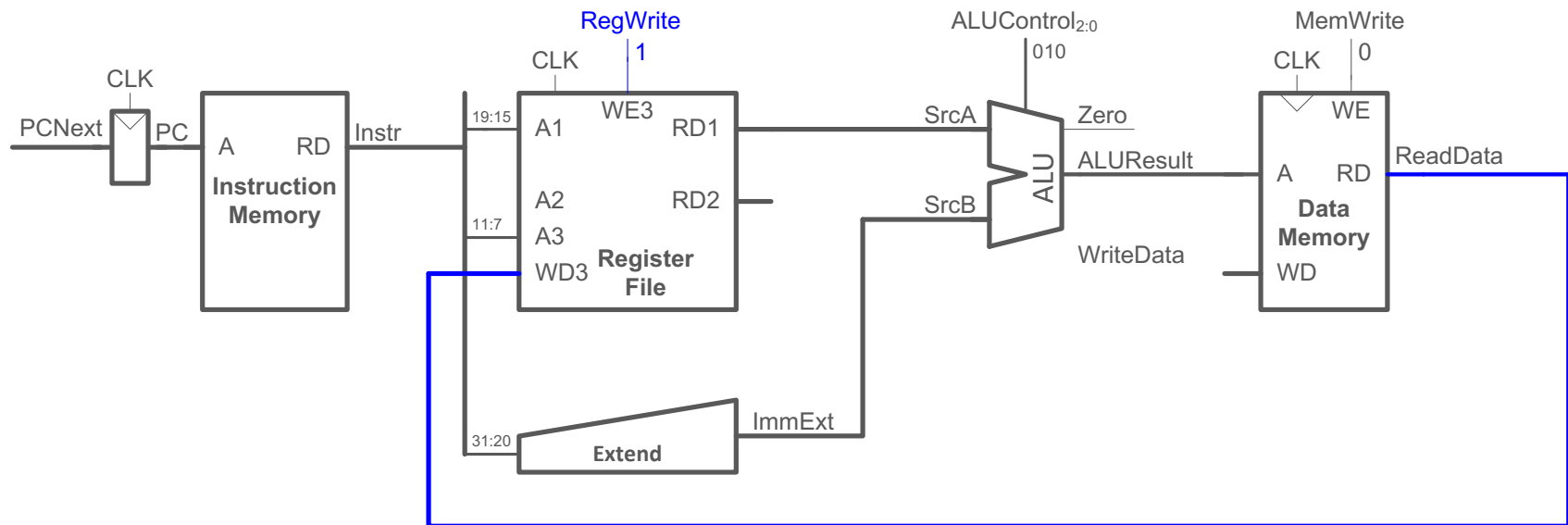
# Single-Cycle Datapath: LDR Mem Read

**STEP 5:** Read data from memory and write it back to register file



# Single-Cycle Datapath: PC Increment
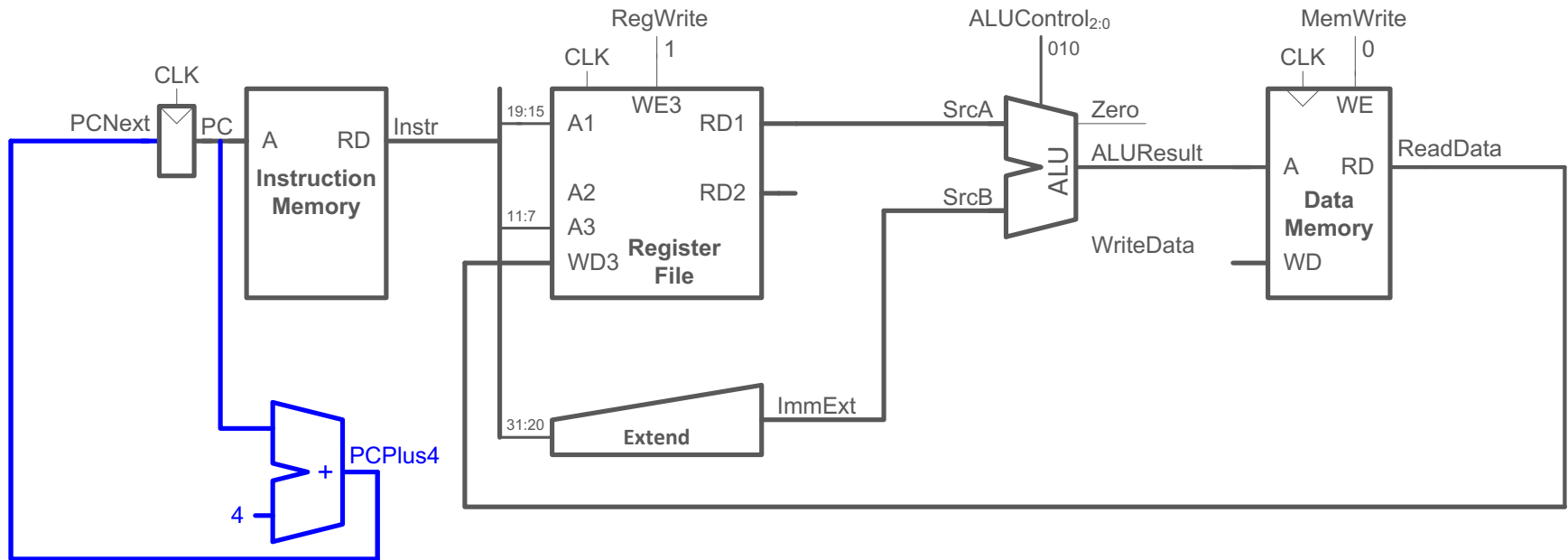
## STEP 6: Determine address of next instruction




# Single-Cycle Datapath: $sw$

**Expand datapath** to handle  $sw$ :


- Write data in  $rs2$  to memory
- **Example:**  $sw\ t2,\ 0xc(s3)$   
 $sw\ rs2,\ imm(rs1)$

## S-Type

 

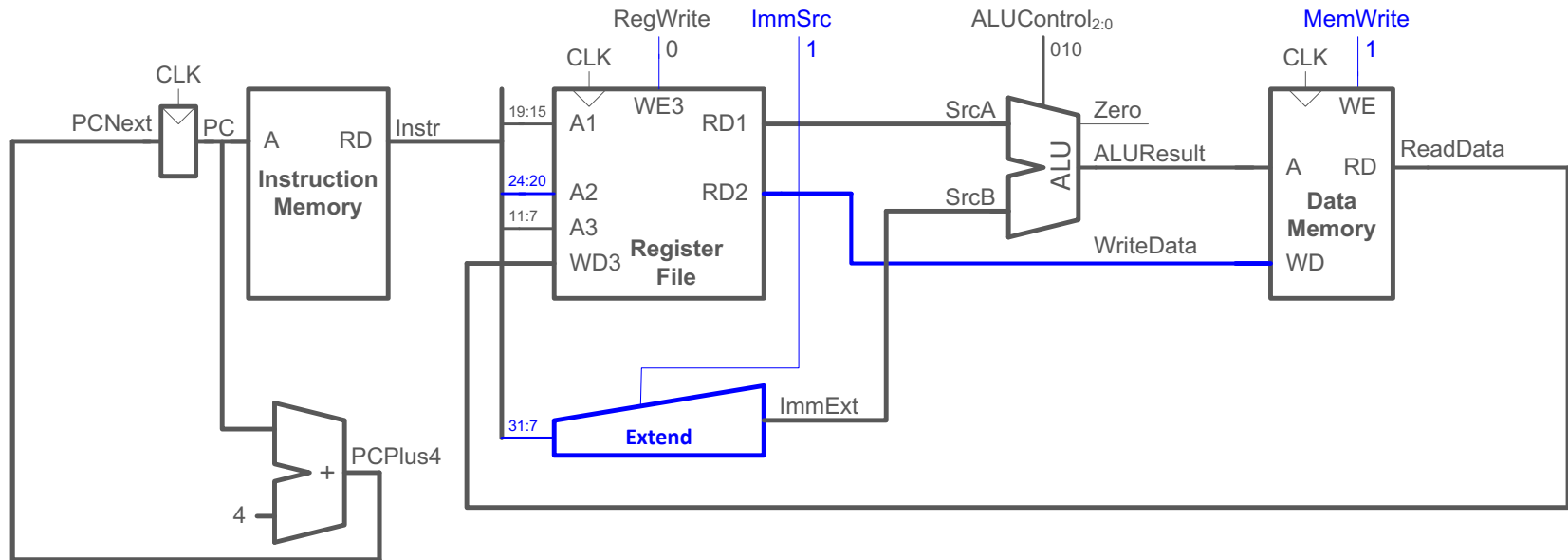
# Single-Cycle Datapath: Data-processing

- **Immediate:** now in {instr[31:25], instr[11:7]}
- **Add control signals:** ImmSrc, MemWrite



## S-Type

 


**sw rs2, imm(rs1)**


# Single-Cycle Datapath: Immediate

ImmSrc	ImmExt	Instruction Type
0	{{20{instr[31]}}, instr[31:20]}	I-Type
1	{{20{instr[31]}}, instr[31:25], instr[11:7]}	S-Type

## I-Type

 


## S-Type

 

# Single-Cycle Datapath: R-Type


- **Instructions:** add, sub, and, or, slt,
- **Example:**        add s1, s2, s3  
                      op  rd, rs1, rs2

## R-Type

 

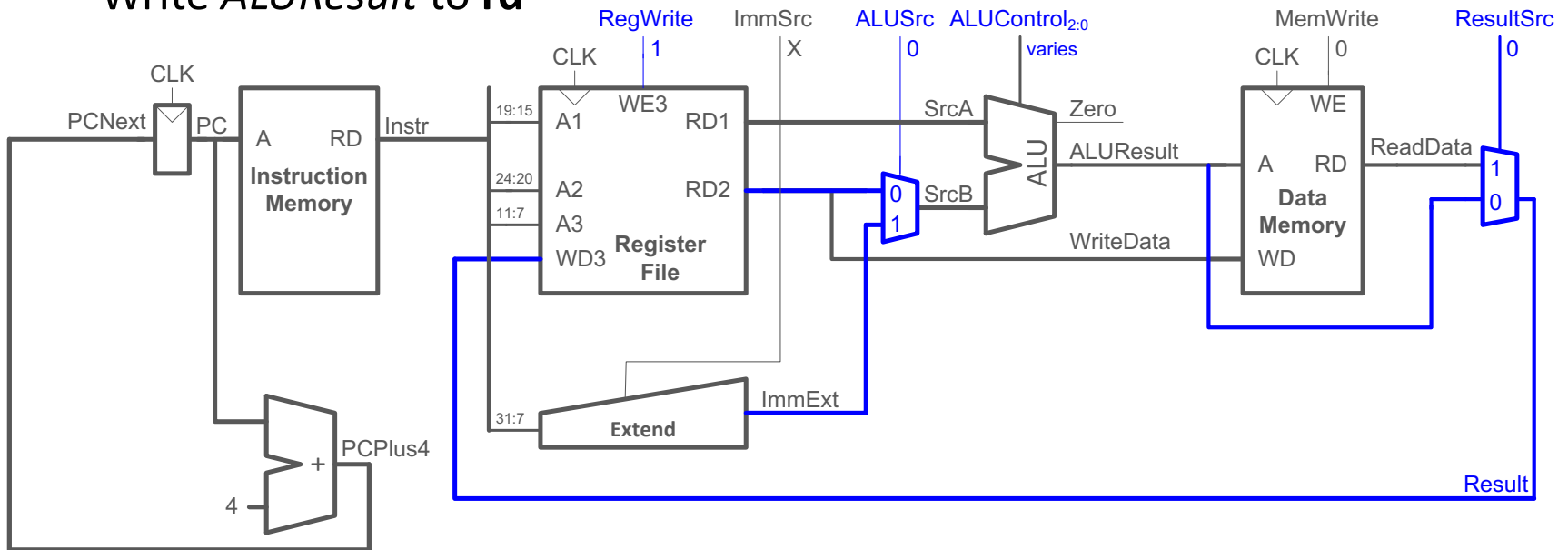
# Single-Cycle Datapath: R-Type

- Read from **rs1** and **rs2** (instead of **imm**)
- Write **ALUResult** to **rd**



## R-Type

 


**add rd, rs1, rs2**



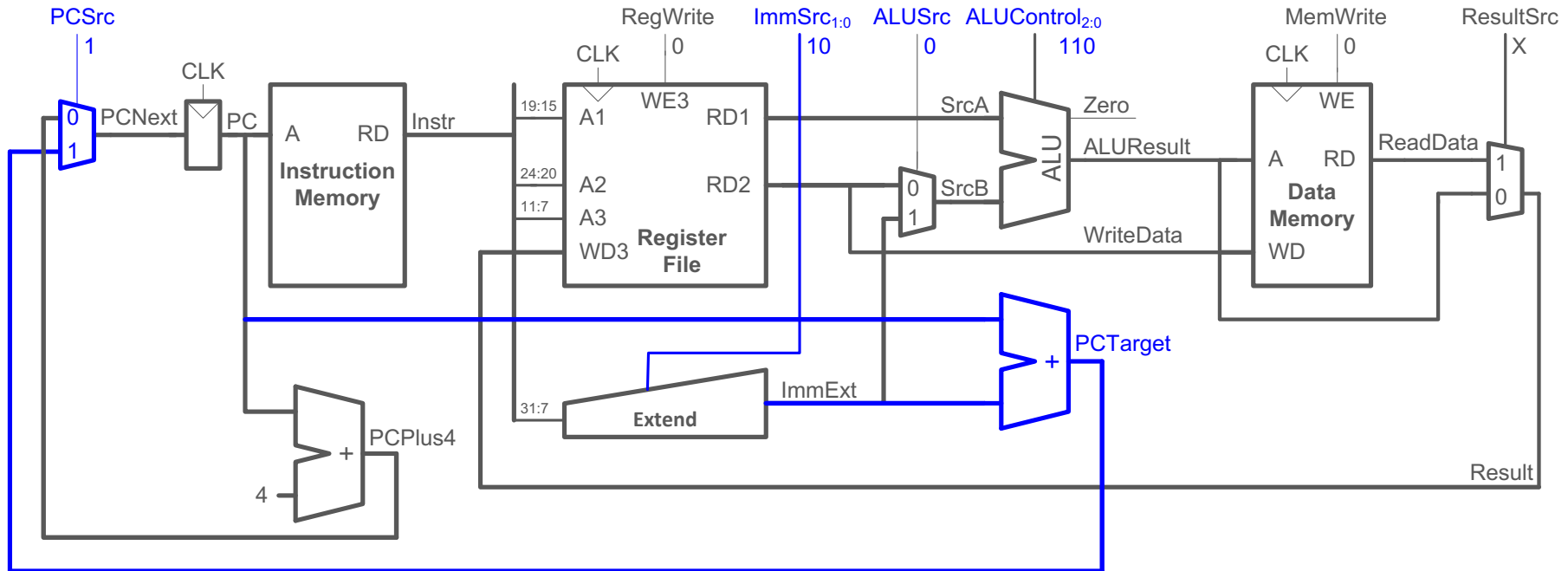
# Single-Cycle Datapath: beq

Calculate branch target address:  $PCTarget = PC + imm$



## B-Type

 


**beq rs1, rs2, Label**


# Single-Cycle Datapath: ImmExt

ImmSrc <sub>1:0</sub>	ImmExt	Instruction Type
00	{{20{instr[31]}}, instr[31:20]}	I-Type
01	{{20{instr[31]}}, instr[31:25], instr[11:7]}	S-Type
10	{{19{instr[31]}}, instr[31], instr[7], instr[30:25], instr[11:8], 1'b0}	B-Type


## I-Type

 


## S-Type

 


## B-Type

 

# Single-Cycle RISC-V Processor

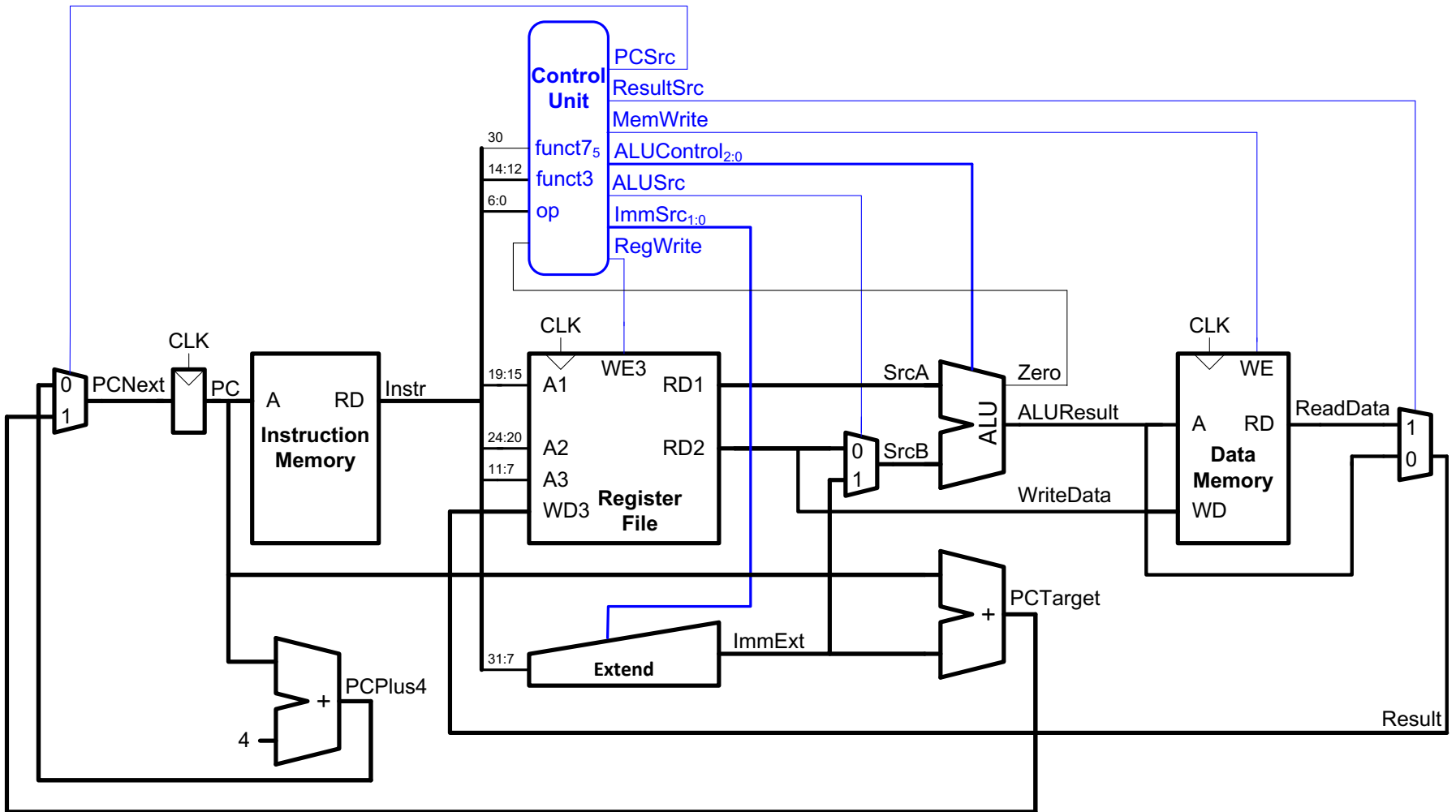


# Single-Cycle Control

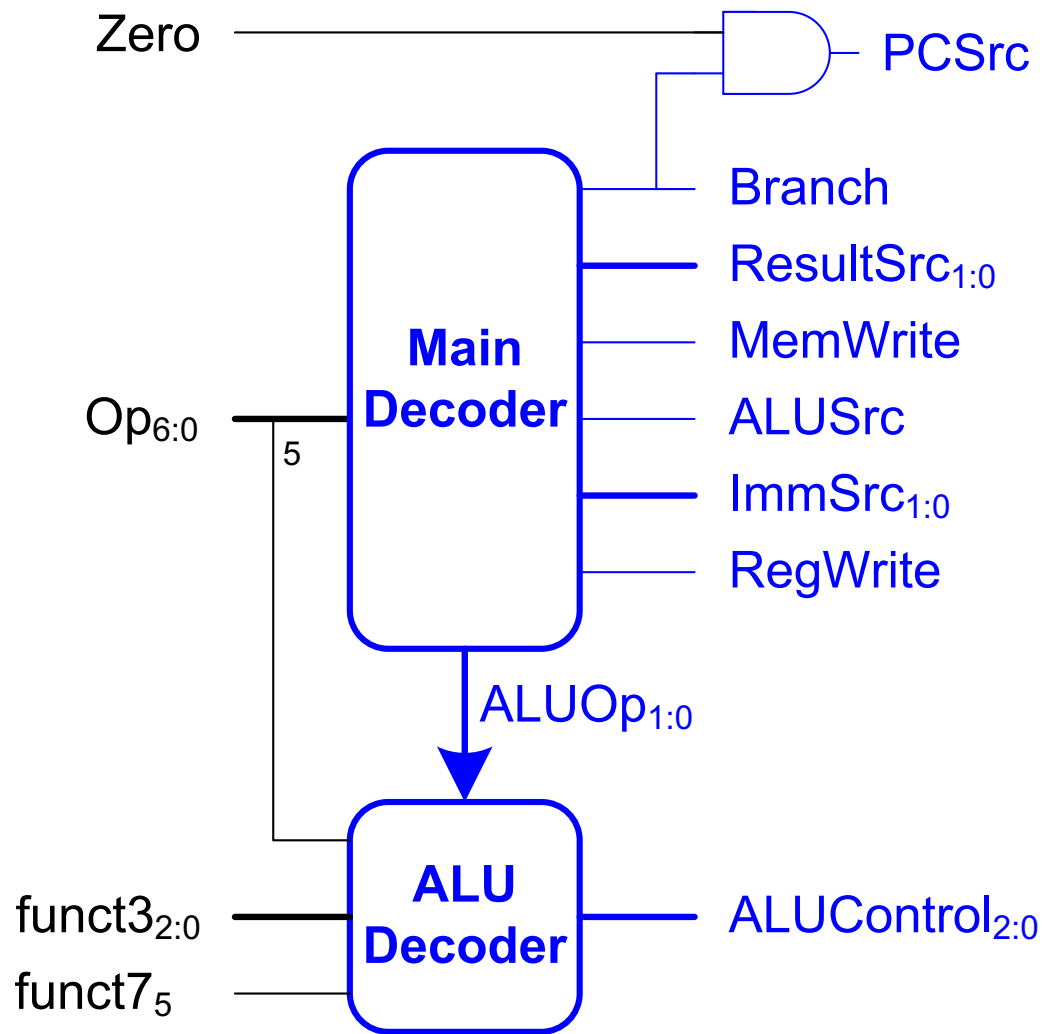


# Control Unit: Main Decoder

op	Instruct	RegWrite	ImmSrc	ALUSrc	MemWrite	ResultSrc	Branch	ALUOp
3	<b>lw</b>	1	00	1	0	1	0	00
35	<b>sw</b>	0	01	1	1	X	0	00
51	<b>R-type</b>	1	XX	0	0	0	0	10
99	<b>beq</b>	0	10	0	0	X	1	01

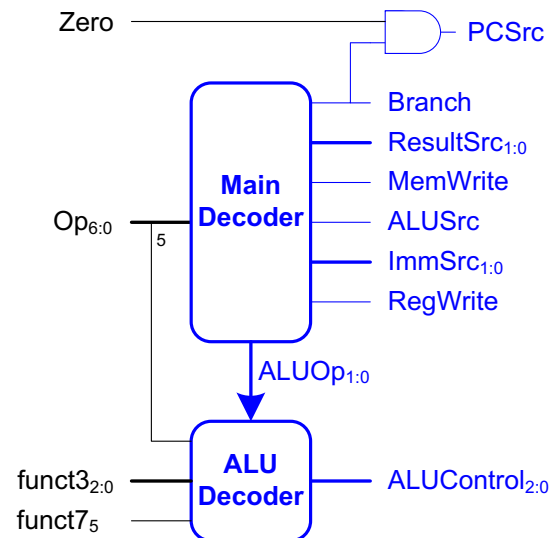


# Review: ALU

 


ALUControl <sub>2:0</sub>	Function
000	A & B
001	A   B
010	A + B
110	A - B
111	SLT

# Review: ALU

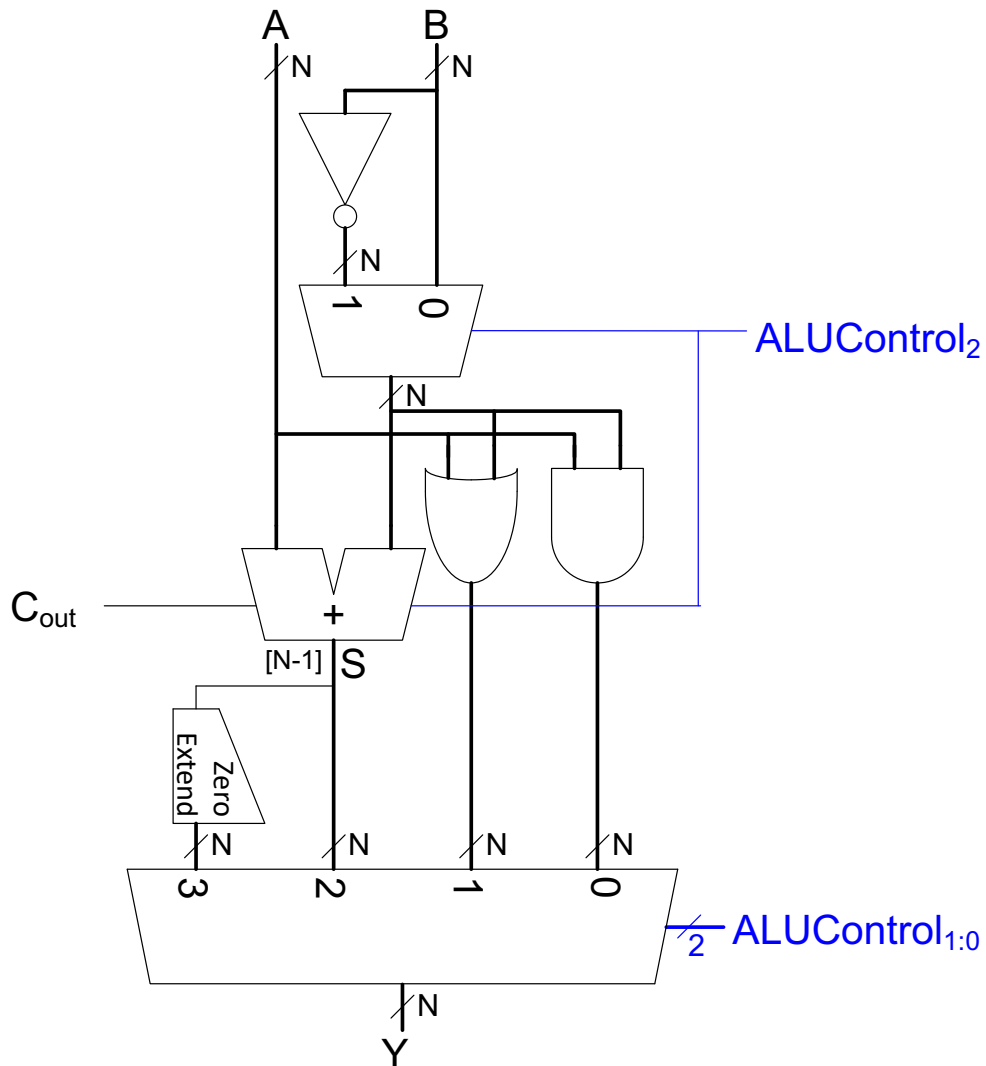

ALUControl <sub>2:0</sub>	Function
000	A & B
001	A   B
010	A + B
110	A - B
111	SLT


# Single-Cycle Control: ALU Decoder

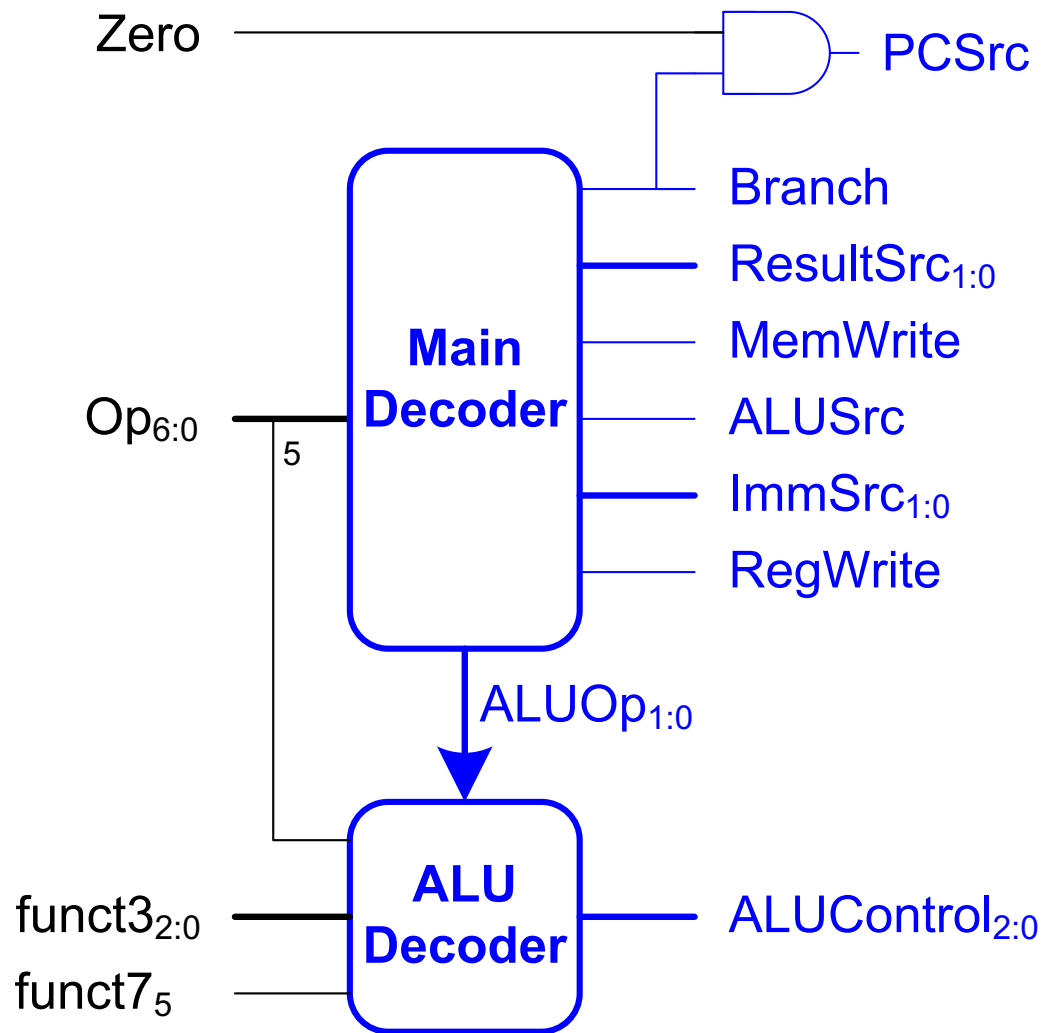




# Control Unit: ALU Decoder

ALUOp	op <sub>5</sub>	funct <sub>3</sub>	funct <sub>7_5</sub>	Instruction	ALUControl <sub>2:0</sub>
00	X	X	X	<b>lw, sw</b>	010 (add)
01	X	X	X	<b>beq</b>	110 (subtract)
10	X	000	0	<b>add</b>	010 (add)
	1	000	1	<b>sub</b>	110 (subtract)
	X	010	0	<b>slt</b>	111 (set less than)
	X	110	0	<b>or</b>	001 (or)
	X	111	0	<b>slt</b>	000 (and)

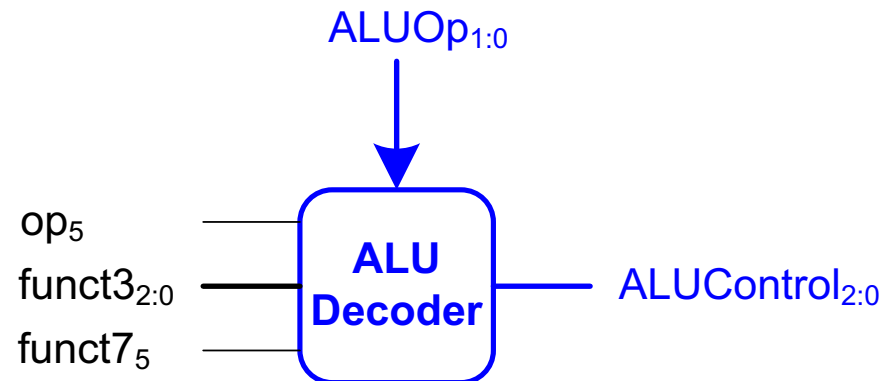


# Example: or

op	Instruct	RegWrite	ImmSrc	ALUSrc	MemWrite	ResultSrc	Branch	ALUOp
51	R-type	1	XX	0	0	0	0	10

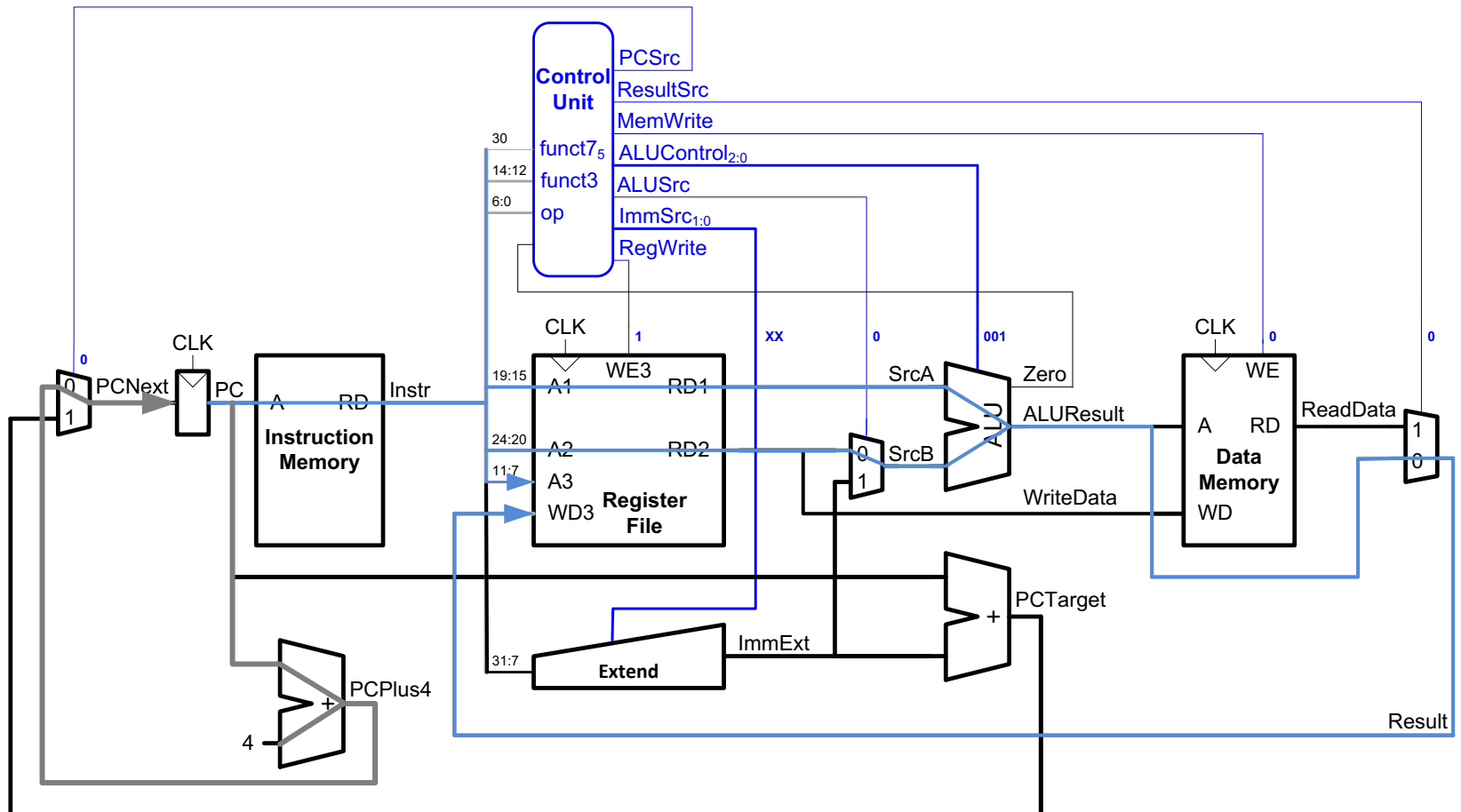

# Example: or

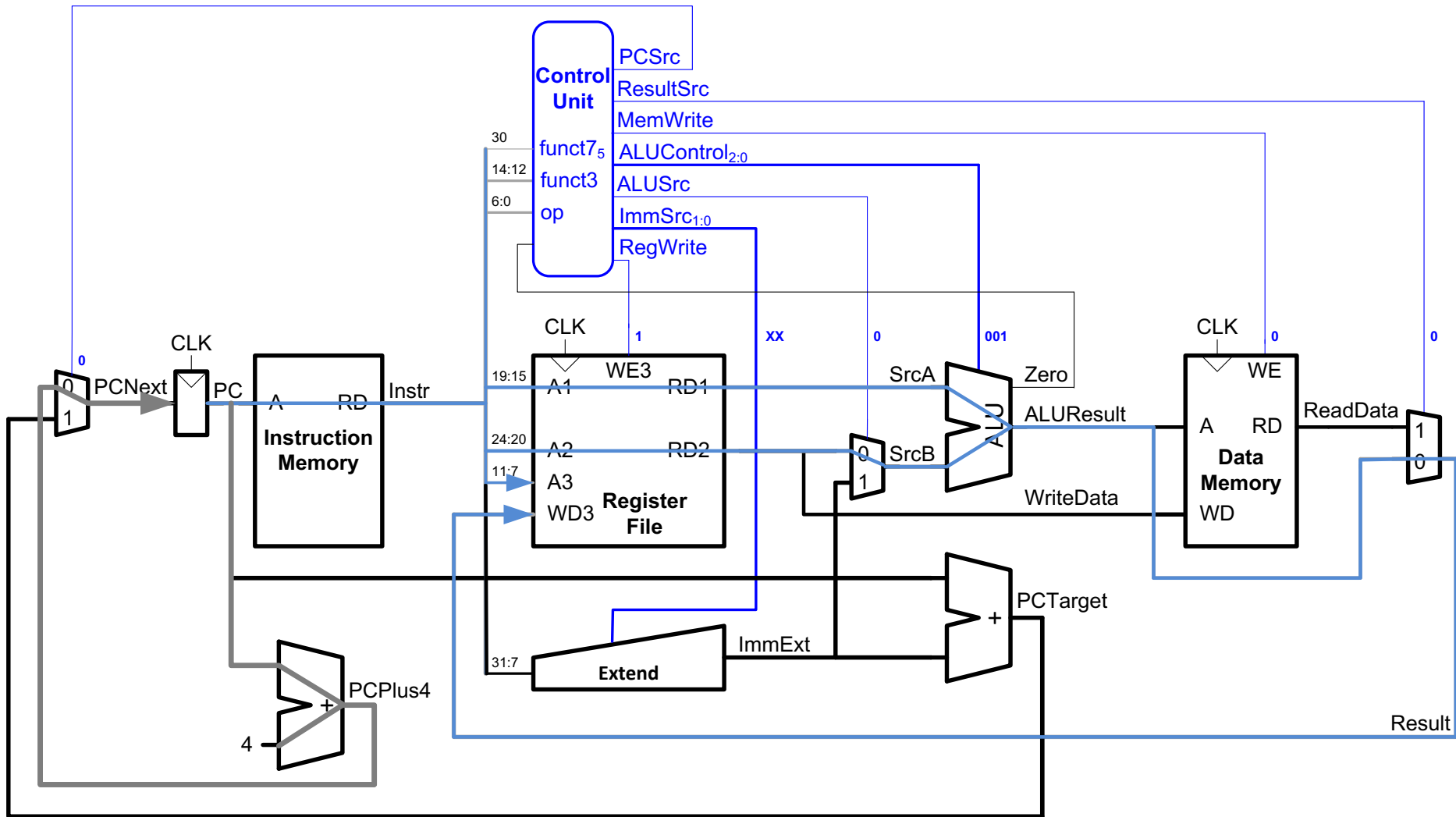


# Extended Functionality: `addi`


op	Instruct	RegWrite	ImmSrc	ALUSrc	MemWrite	ResultSrc	Branch	ALUOp
3	<code>lw</code>	1	00	1	0	1	0	00
35	<code>sw</code>	0	01	1	1	X	0	00
51	<b>R-type</b>	1	XX	0	0	0	0	10
99	<code>beq</code>	0	10	0	0	X	1	01
<b>19</b>	<b><code>addi</code></b>	<b>1</b>	<b>00</b>	<b>1</b>	<b>0</b>	<b>0</b>	<b>0</b>	<b>10</b>

# Extended Functionality: addi

op	Instruct	RegWrite	ImmSrc	ALUSrc	MemWrite	ResultSrc	Branch	ALUOp
19	addi	1	00	1	0	0	0	10

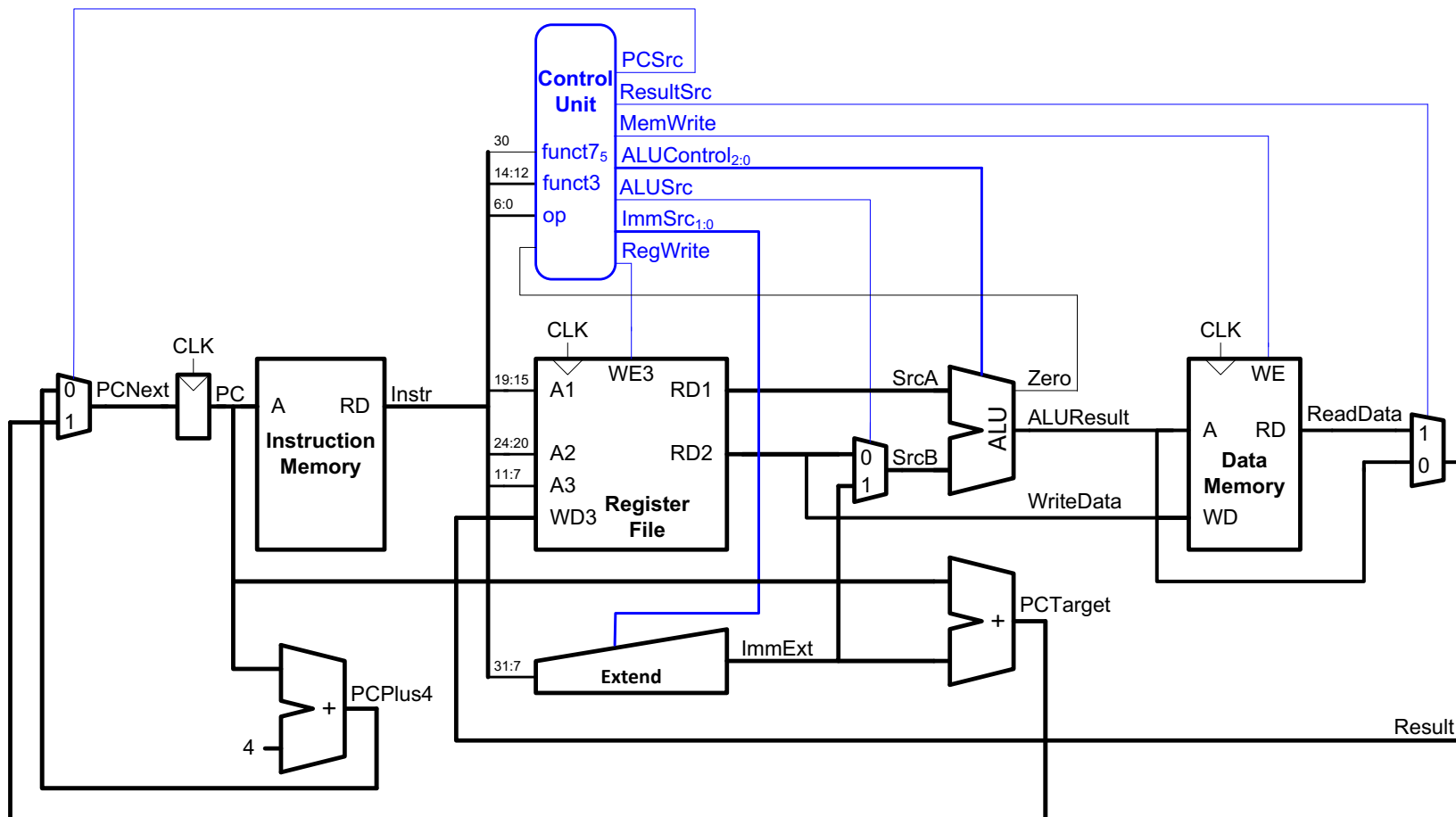


# Extended Functionality: jal

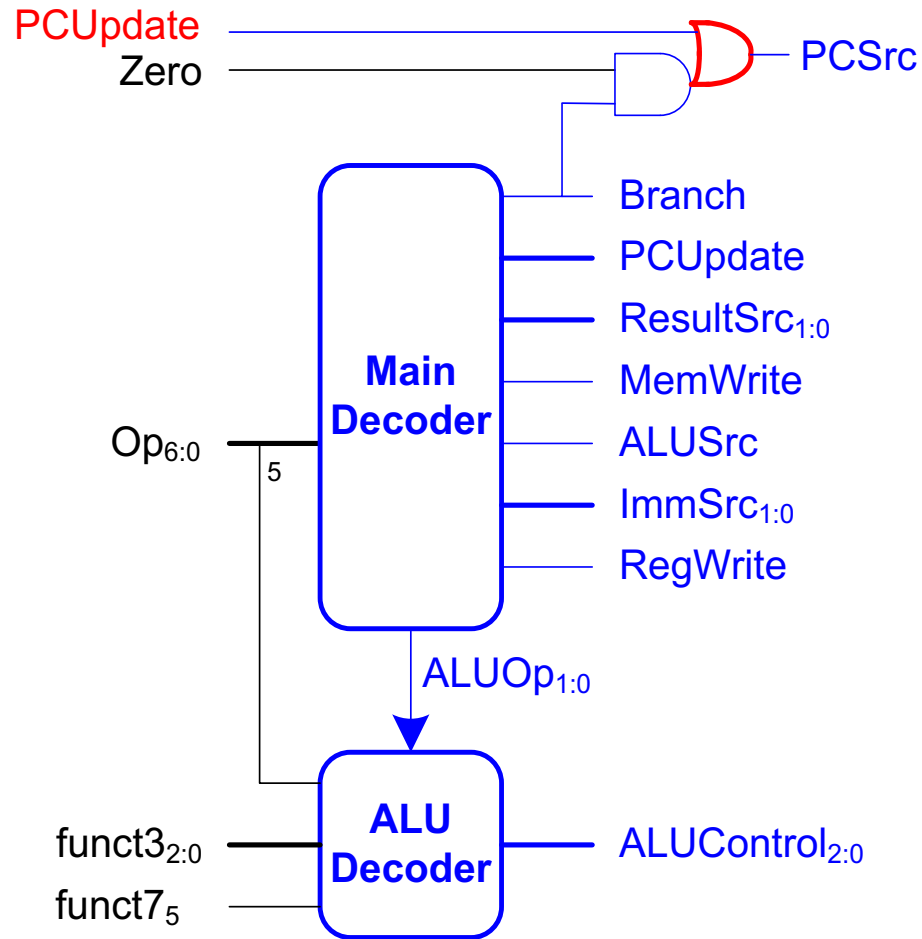


# Single-Cycle Datapath: ImmExt

ImmSrc <sub>1:0</sub>	ImmExt	Instruction Type
00	{{20{instr[31]}}, instr[31:20]}	I-Type
01	{{20{instr[31]}}, instr[31:25], instr[11:7]}	S-Type
10	{{19{instr[31]}}, instr[31], instr[7], instr[30:25], instr[11:8], 1'b0}	B-Type
11	{{12{instr[31]}}, instr[19:12], instr[20], instr[30:21], 1'b0}	J-Type


## I-Type

 


## B-Type

 

## S-Type

 

## J-Type

 


# Extended Functionality: jal

op	Instruct	RegWrite	ImmSrc	ALUSrc	MemWrite	ResultSrc	Branch	ALUOp	PCUpdate
3	lw	1	00	1	0	10	0	00	0
35	sw	0	01	1	1	XX	0	00	0
51	R-type	1	XX	0	0	01	0	10	0
99	beq	0	10	0	0	XX	1	01	0
19	addi	1	00	1	0	01	0	10	0
111	jal	0	11	X	0	00	0	XX	1



# Extended Functionality: jal

op	Instruct	RegWrite	ImmSrc	ALUSrc	MemWrite	ResultSrc	Branch	ALUOp	PCUpdate
111	jal	0	11	X	0	00	0	XX	1

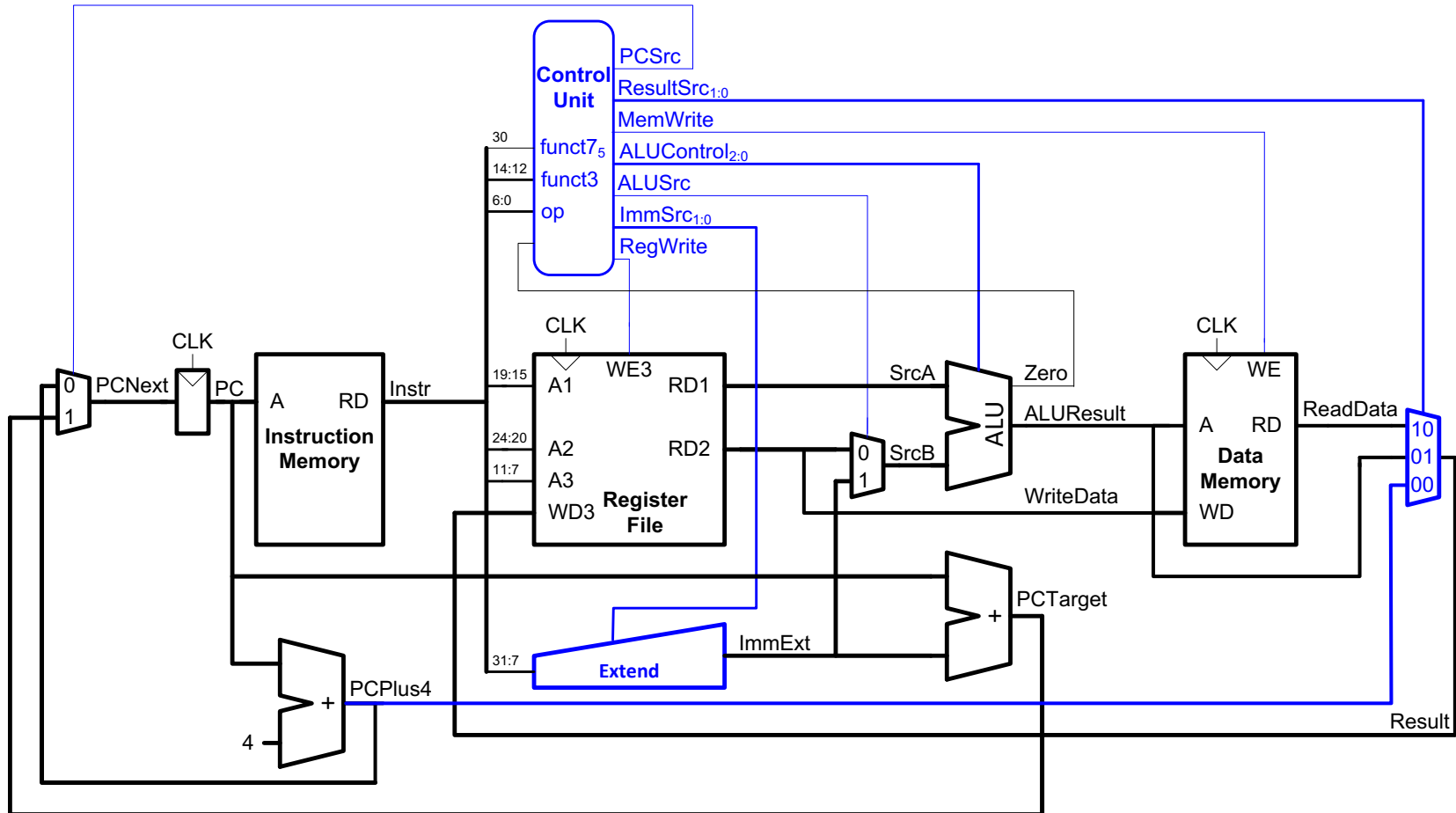


# Processor Performance

## Program Execution Time

= (#instructions)(cycles/instruction)(seconds/cycle)

= # instructions x CPI x  $T_C$

# Single-Cycle Performance

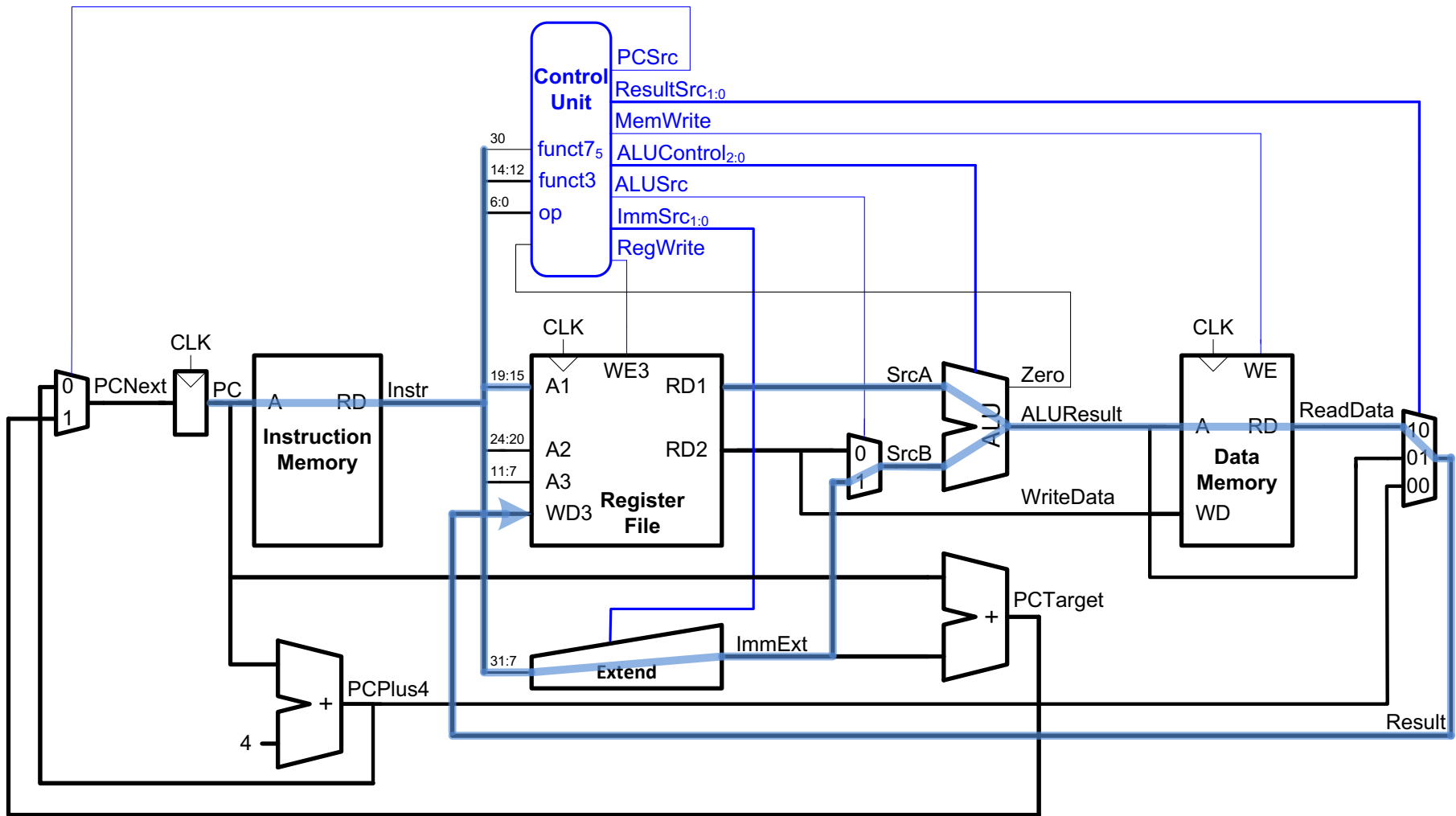

$T_C$  limited by critical path (1w)

# Single-Cycle Performance

- **Single-cycle critical path:**

$$T_{cl} = t_{pcq\_PC} + t_{mem} + \max[t_{mux} + t_{RFread}, t_{ext} + t_{mux}] + t_{ALU} + t_{mem} + t_{mux} + t_{RFsetup}$$

- **Typically, limiting paths are:**

- memory, ALU, register file

- $T_{cl} = t_{pcq\_PC} + 2t_{mem} + t_{RFread} + t_{ALU} + 2t_{mux} + t_{RFsetup}$

# Single-Cycle Performance Example

Element	Parameter	Delay (ps)
Register clock-to-Q	$t_{pcq\_PC}$	40
Register setup	$t_{setup}$	50
Multiplexer	$t_{mux}$	25
ALU	$t_{ALU}$	120
Decoder (Control Unit)	$t_{dec}$	70
Memory read	$t_{mem}$	200
Register file read	$t_{RFread}$	100
Register file setup	$t_{RFsetup}$	60

$$T_{cl} = ?$$

# Single-Cycle Performance Example

Element	Parameter	Delay (ps)
Register clock-to-Q	$t_{pcq\_PC}$	40
Register setup	$t_{setup}$	50
Multiplexer	$t_{mux}$	25
ALU	$t_{ALU}$	120
Decoder (Control Unit)	$t_{dec}$	70
Memory read	$t_{mem}$	200
Register file read	$t_{RFread}$	100
Register file setup	$t_{RFsetup}$	60

$$\begin{aligned}T_{cl} &= t_{pcq\_PC} + 2t_{mem} + t_{dec} + t_{RFread} + t_{ALU} + 2t_{mux} + t_{RFsetup} \\ &= [50 + 2(200) + 70 + 100 + 120 + 2(25) + 60] \text{ ps} \\ &= \mathbf{840 \text{ ps}}\end{aligned}$$

# Single-Cycle Performance Example

Program with 100 billion instructions:

$$\begin{aligned}\text{Execution Time} &= \# \text{ instructions} \times \text{CPI} \times T_C \\ &= (100 \times 10^9)(1)(840 \times 10^{-12} \text{ s}) \\ &= \mathbf{84 \text{ seconds}}\end{aligned}$$

# Multicycle RISC-V Processor

- **Single-cycle:**
  - + simple
  - cycle time limited by longest instruction ( $1_w$ )
  - separate memories for instruction and data
  - 3 adders/ALUs
- **Multicycle processor addresses these issues by breaking instruction into shorter steps**
  - shorter instructions take fewer steps
  - can re-use hardware
  - cycle time is faster



# Multicycle RISC-V Processor

- **Single-cycle:**
  - + simple
  - cycle time limited by longest instruction (LDR)
  - separate memories for instruction and data
  - 3 adders/ALUs
- **Multicycle:**
  - + higher clock speed
  - + simpler instructions run faster
  - + reuse expensive hardware on multiple cycles
  - sequencing overhead paid many times

# Multicycle RISC-V Processor

- **Single-cycle:**

- + simple
- cycle time limited by longest instruction (LDR)
- separate memories for instruction and data
- 3 adders/ALUs

- **Multicycle:**


- + higher clock speed
- + simpler instructions run faster
- + reuse expensive hardware on multiple cycles
- sequencing overhead paid many times

**Same design steps  
as single-cycle:**

- **first datapath**
- **then control**

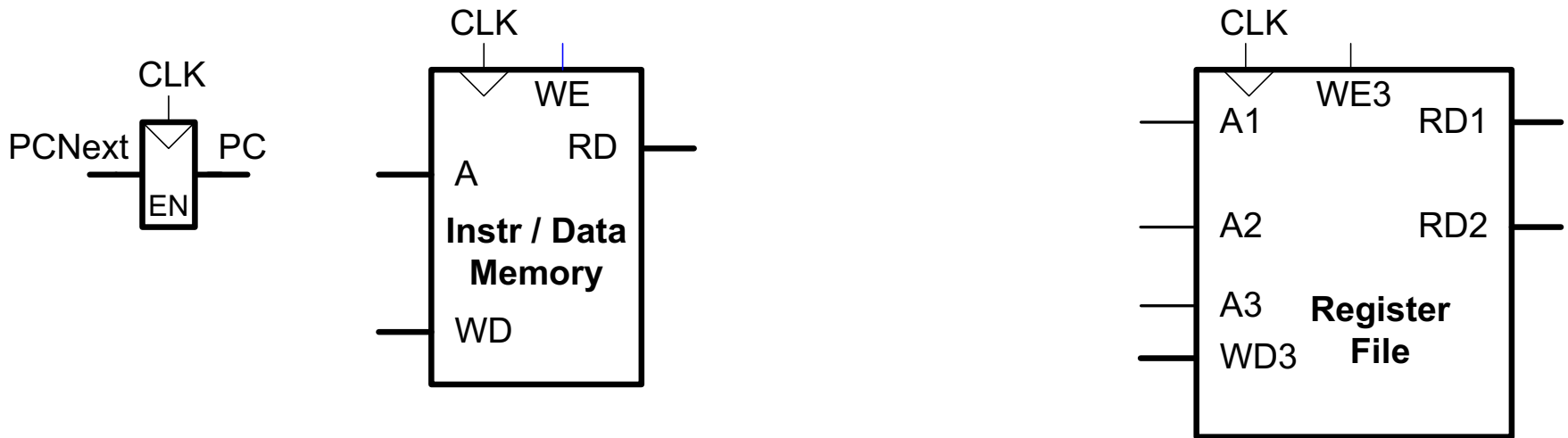
# Multicycle State Elements

Replace Instruction and Data memories with a single unified memory – more realistic




# Multicycle Datapath: Instruction Fetch

## STEP 1: Fetch instruction

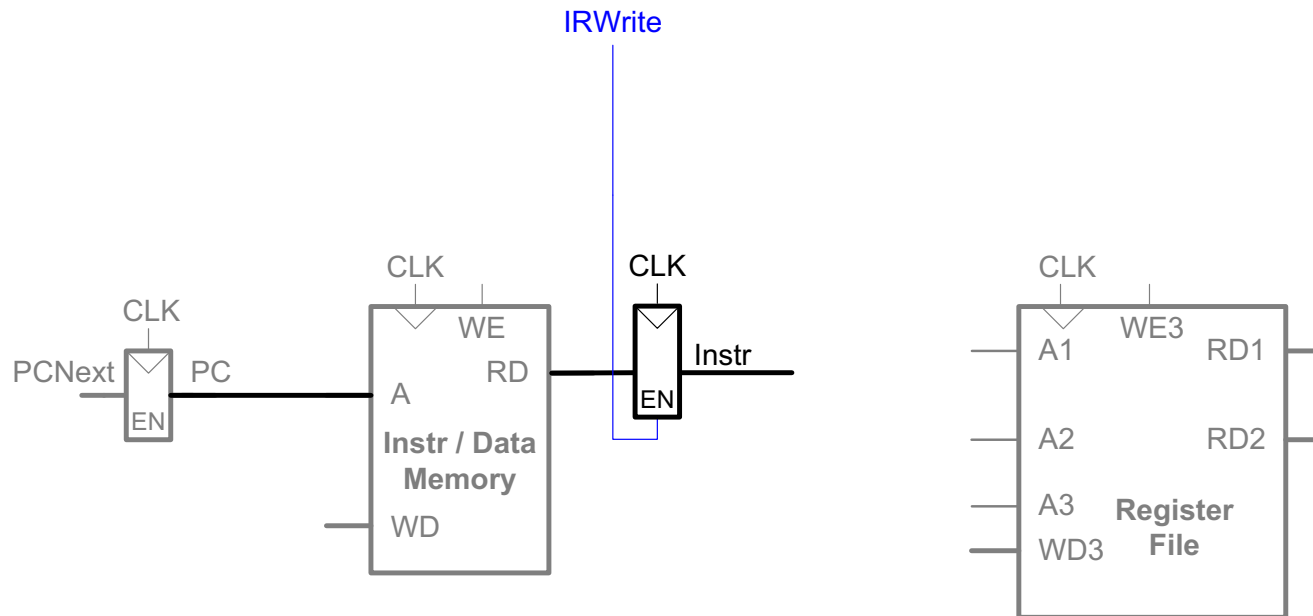

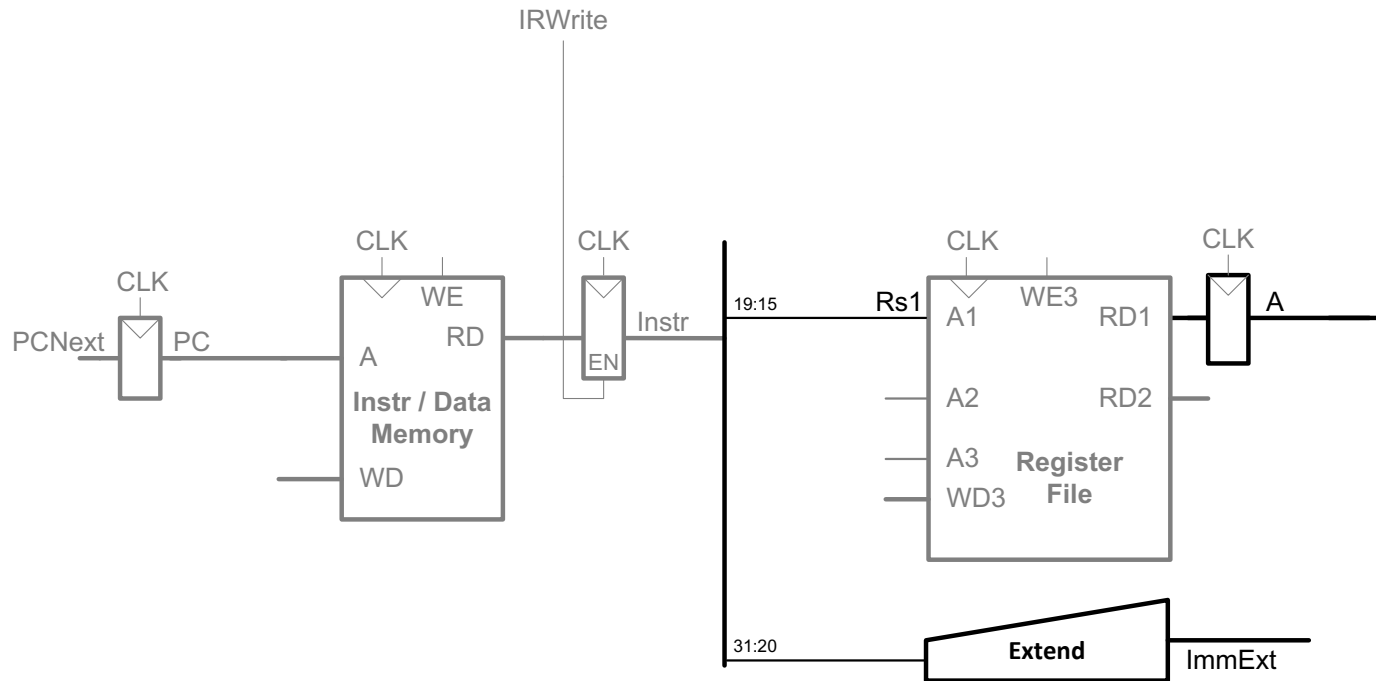
# Multicycle Datapath: $lw$ get sources

**STEP 2:** Read source operand from RF and extend immediate




**I-Type**

 


**$lw$  rd, imm(rs1)**

# Multicycle Datapath: $lw$ Address

## STEP 3: Compute the memory address

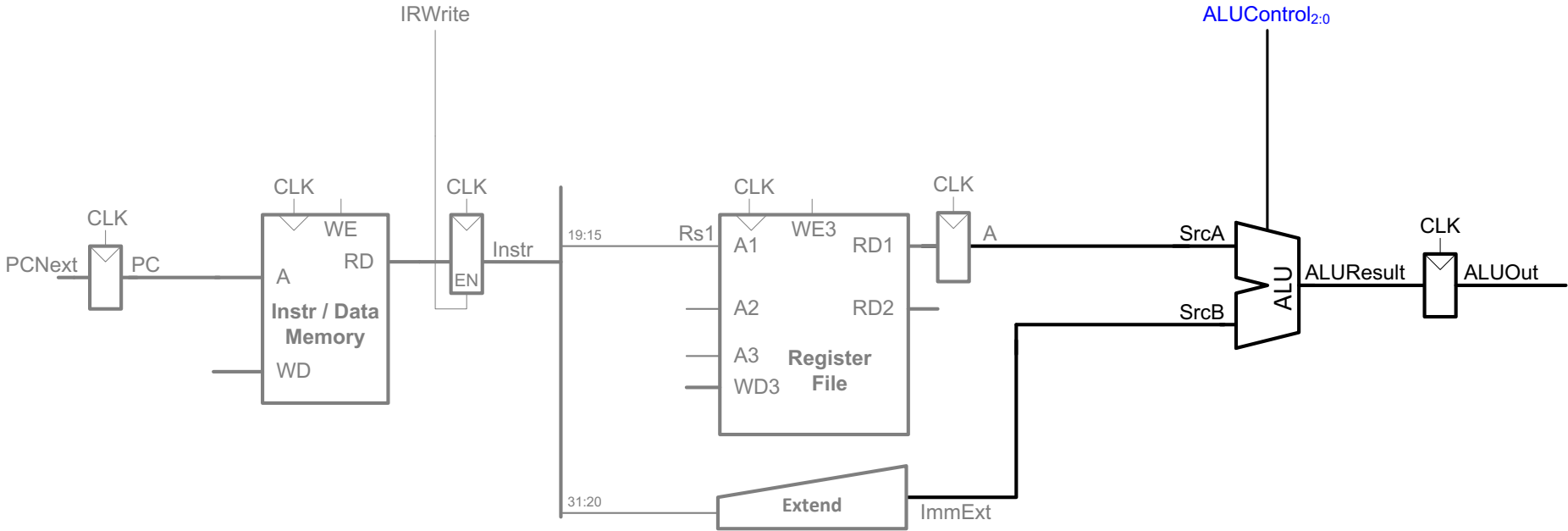


### I-Type

 


`lw rd, imm(rs1)`

# Multicycle Datapath: $lw$ Memory Read

## STEP 4: Read data from memory

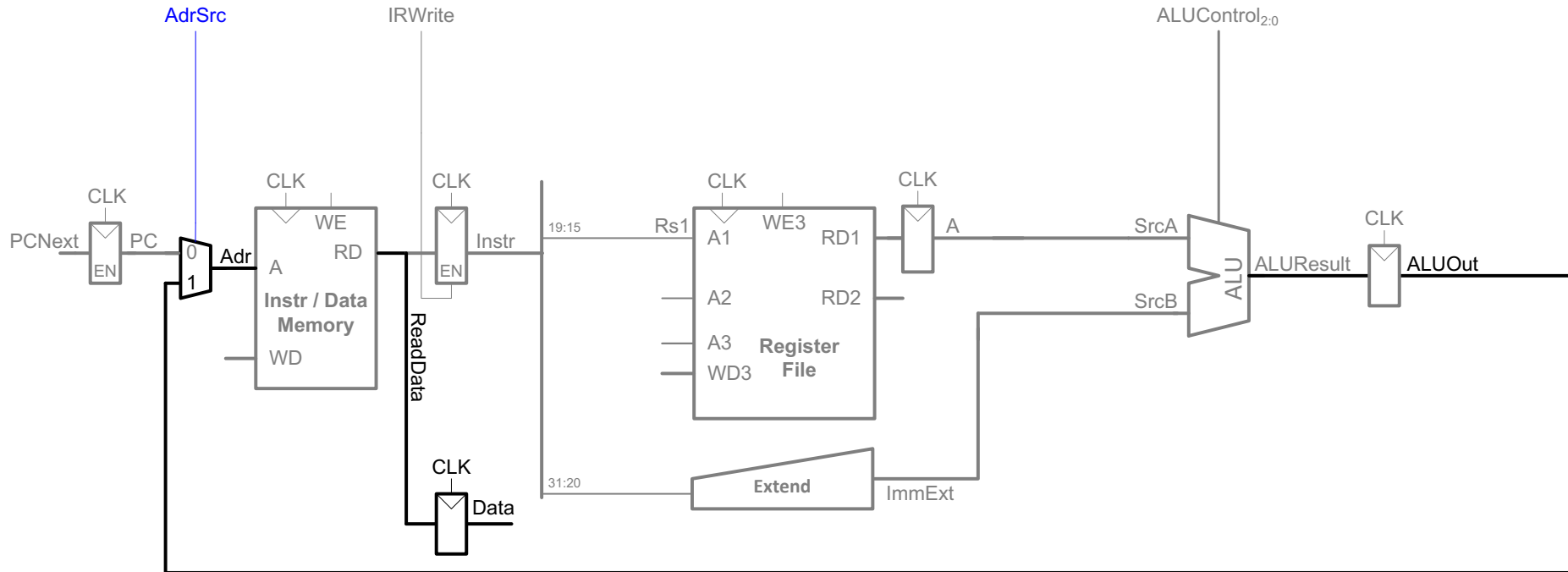


### I-Type

 


`lw rd, imm(rs1)`

# Multicycle Datapath: $lw$ Write Register
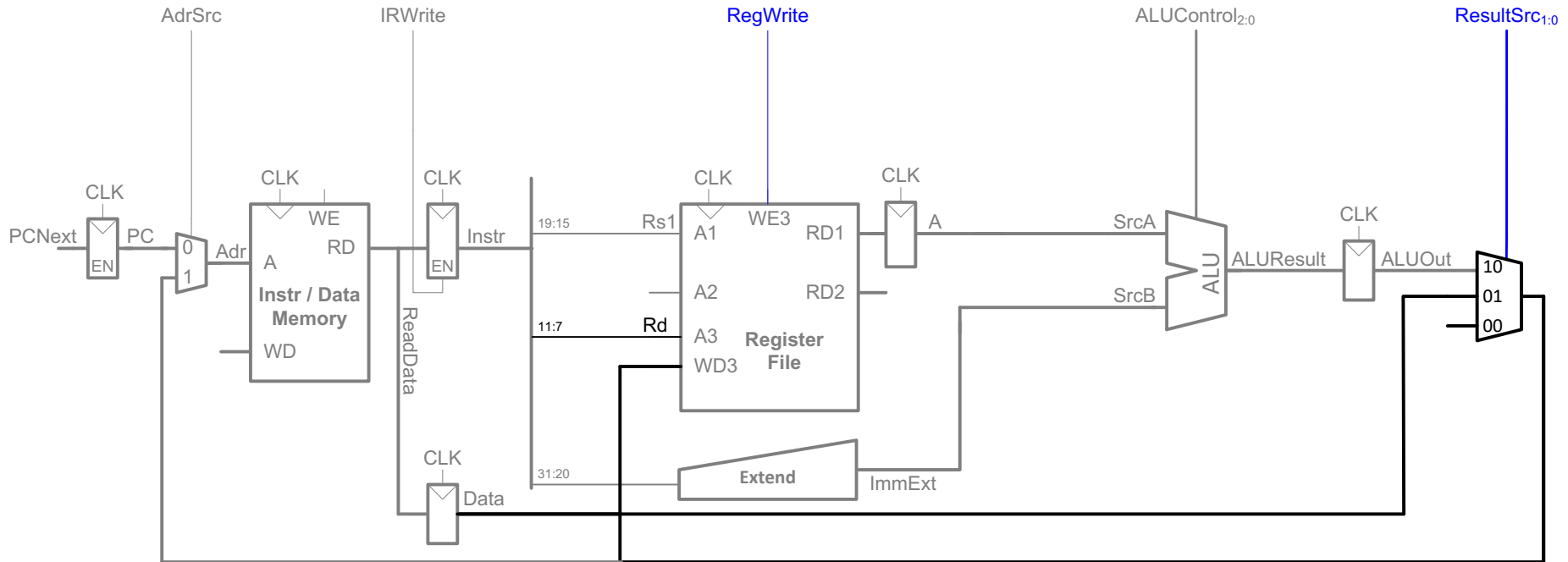
## STEP 5: Write data back to register file



### I-Type

 


`lw rd, imm(rs1)`




# Multicycle Datapath: Increment PC

## STEP 6: Increment PC: $PC = PC + 4$

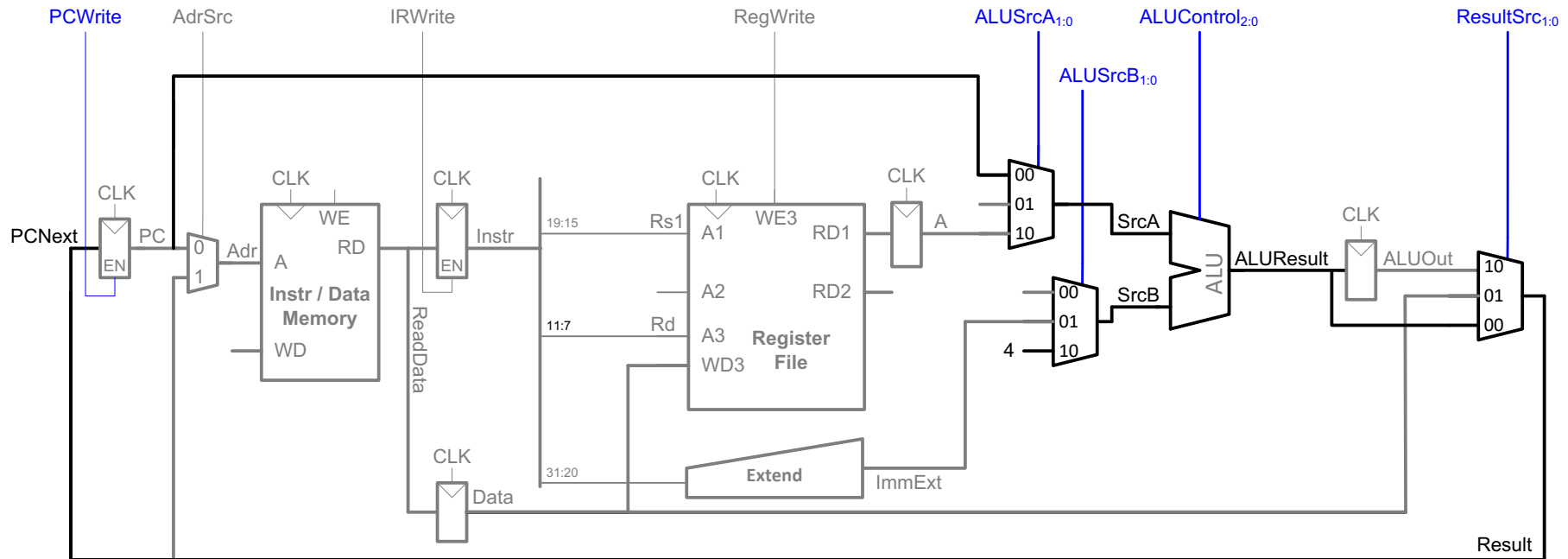


# Multicycle Datapath: $sw$

## Write data in $rs2$ to memory

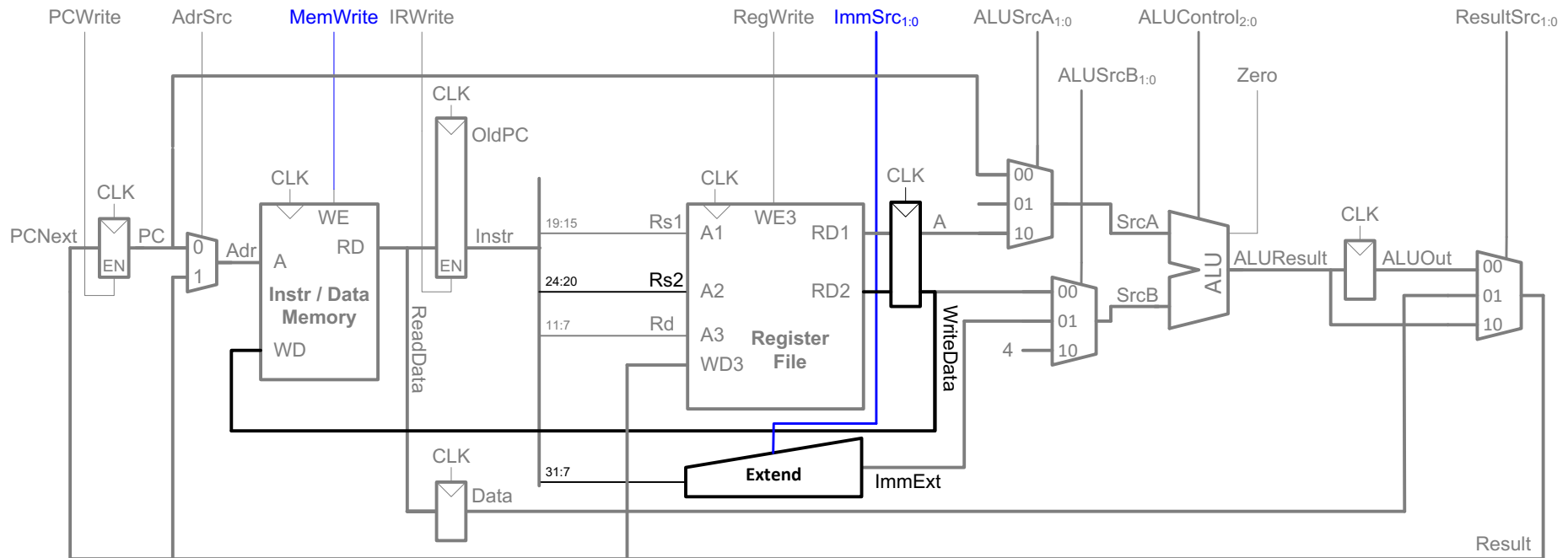

# Multicycle Datapath: $sw$


Write data in  $rs2$  to memory

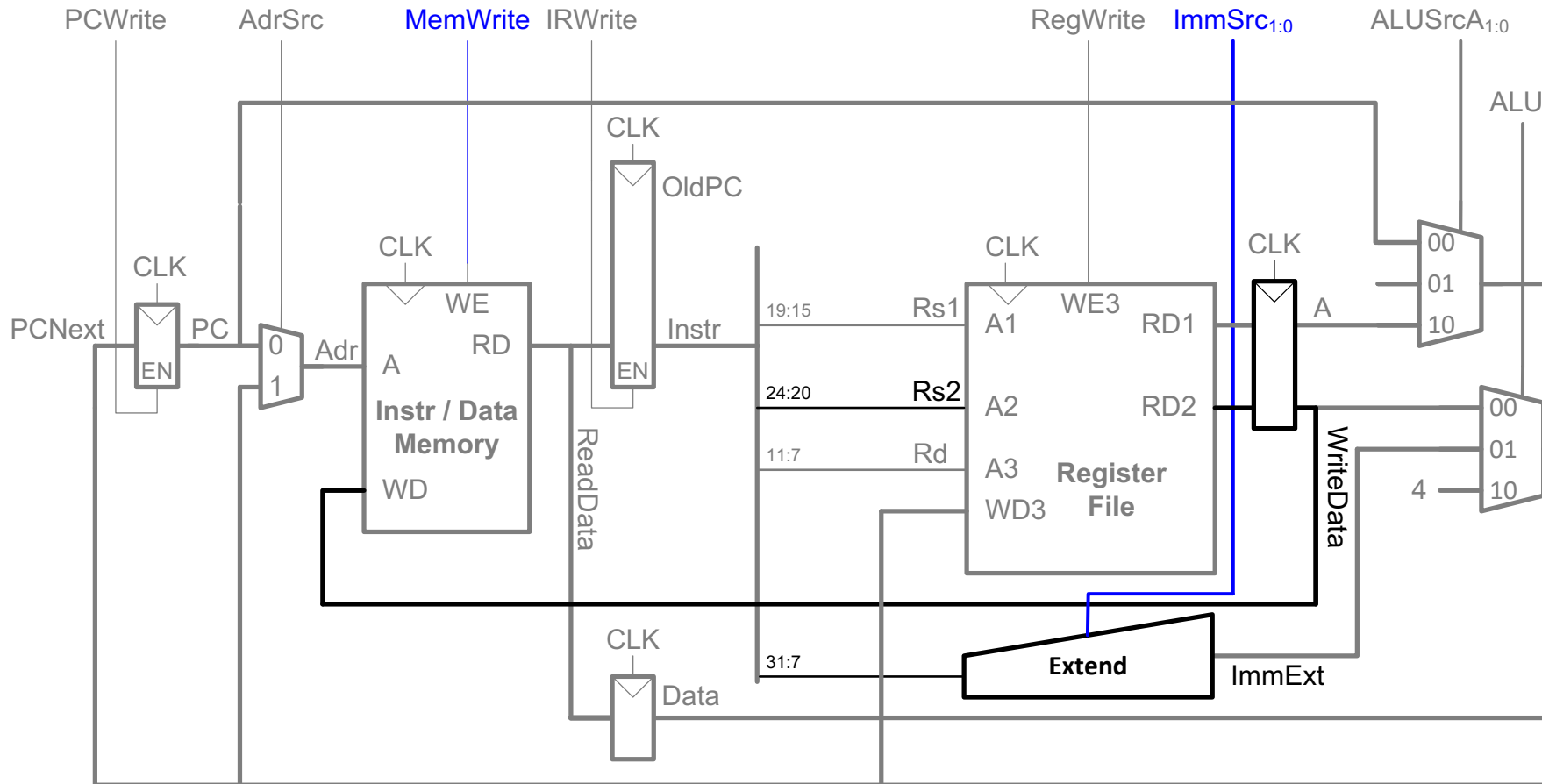

# Multicycle Datapath: beq


Calculate branch target address:

$$\text{BTA} = \text{PC} + \text{imm}$$

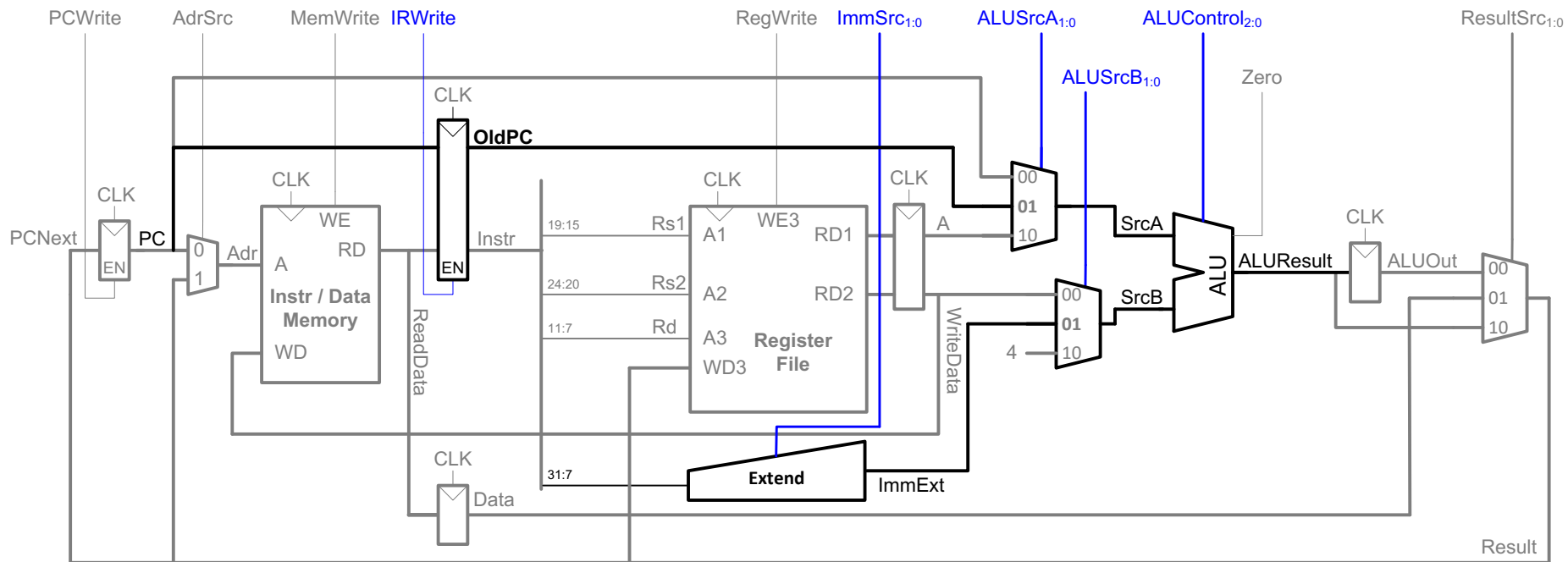


PC was already updated in Fetch stage, so need to save **old PC**


# Multicycle RISC-V Processor

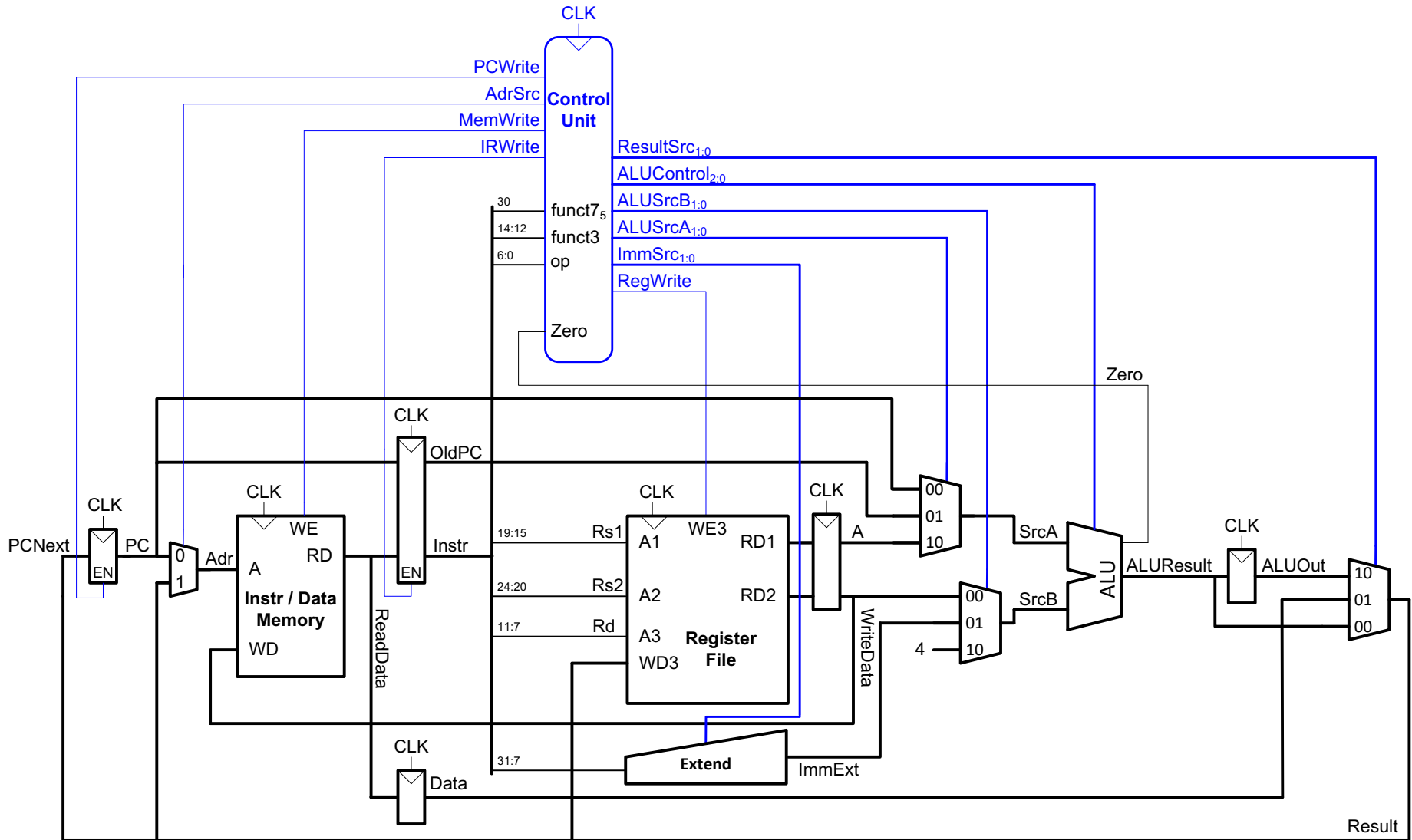

# Multicycle Control

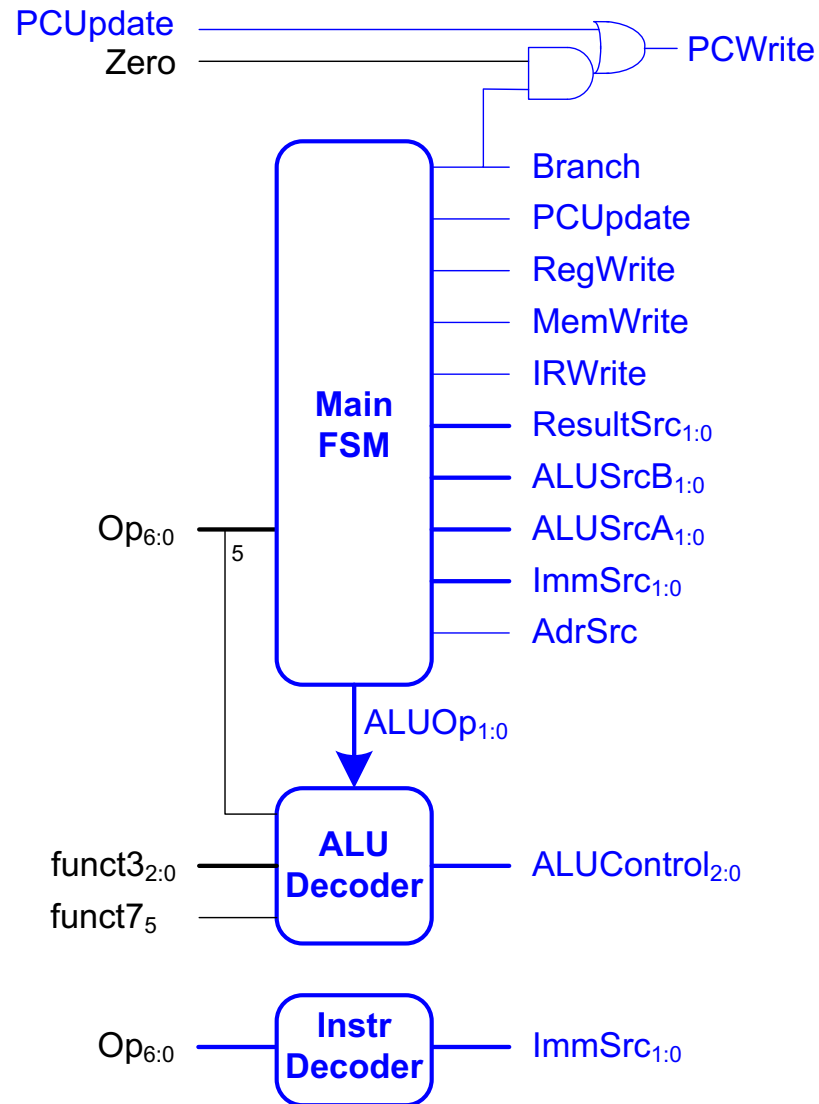


# Multicycle Control

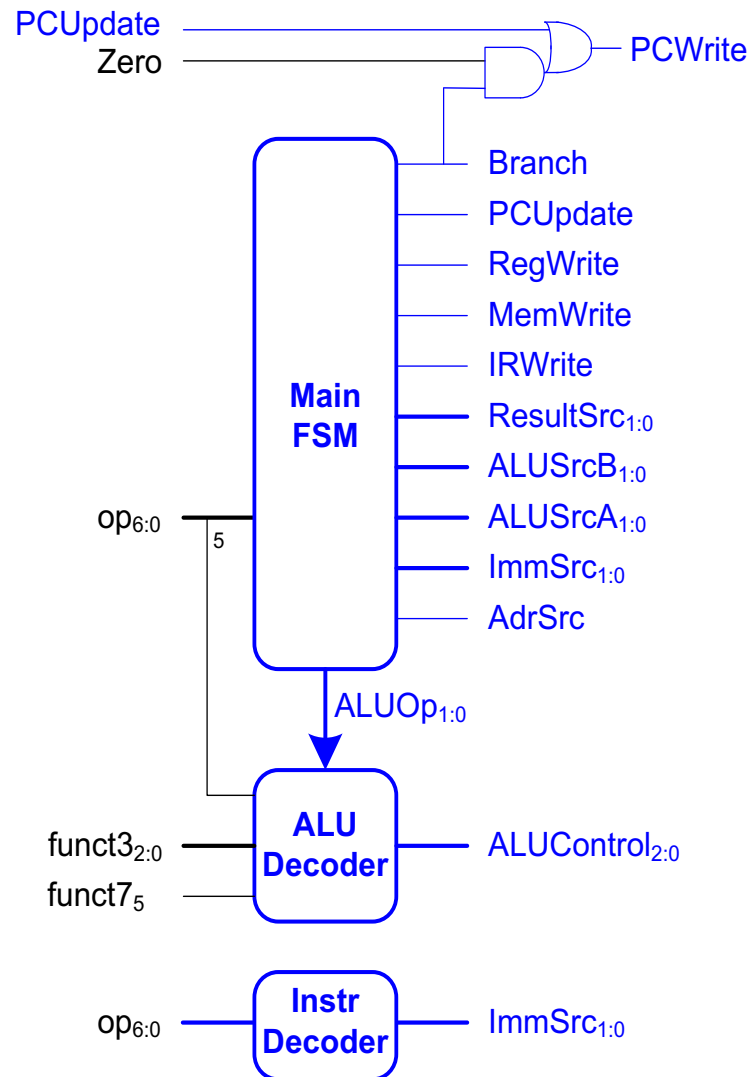

**ALU Decoder  
same as  
single-cycle**


# Multicycle Control: Instr Decoder

 


op	Instruction	ImmSrc
3	<b>lw</b>	00
35	<b>sw</b>	01
51	<b>R-type</b>	XX
99	<b>beq</b>	10



# Multicycle RISC-V Processor

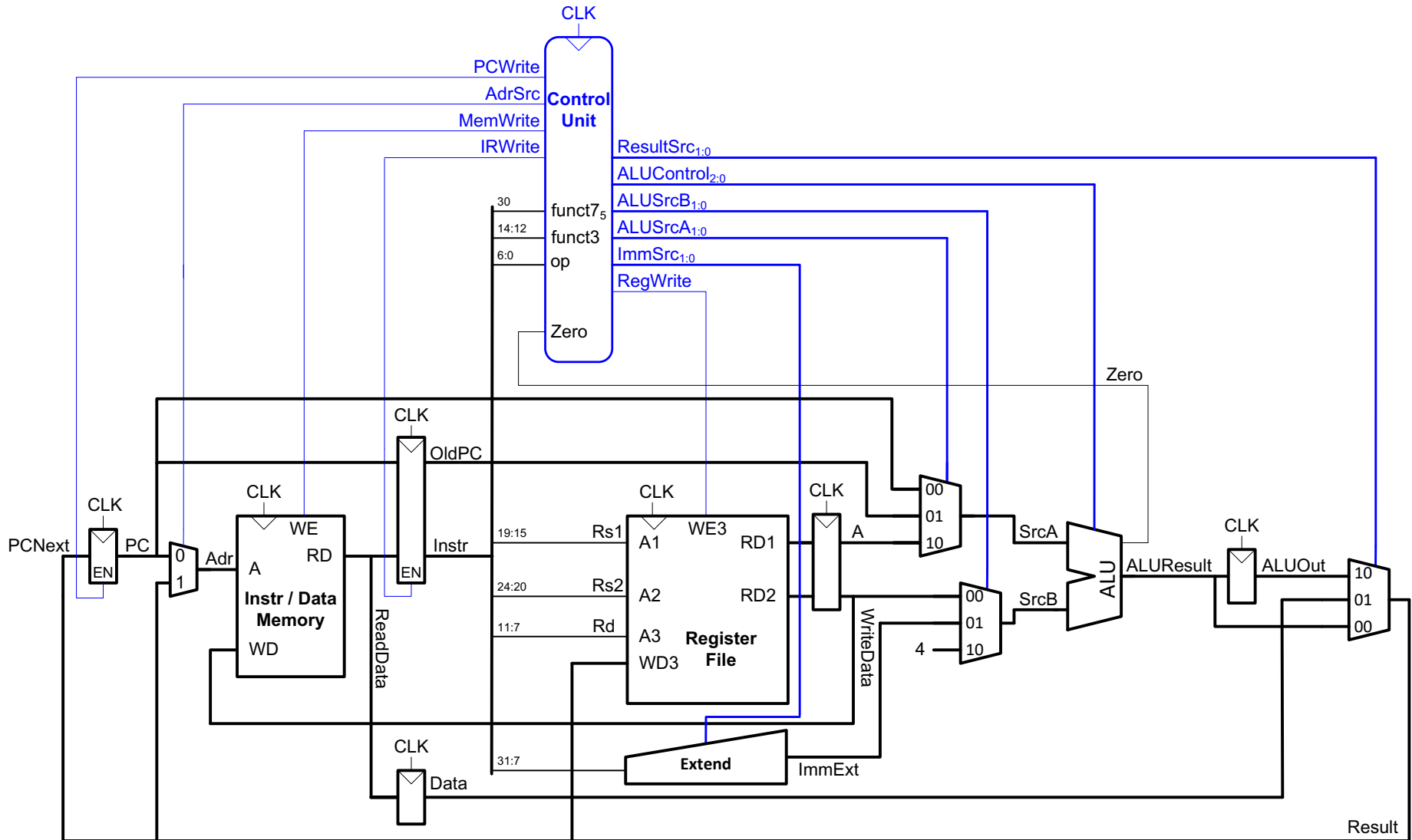


# Multicycle Control: Main FSM

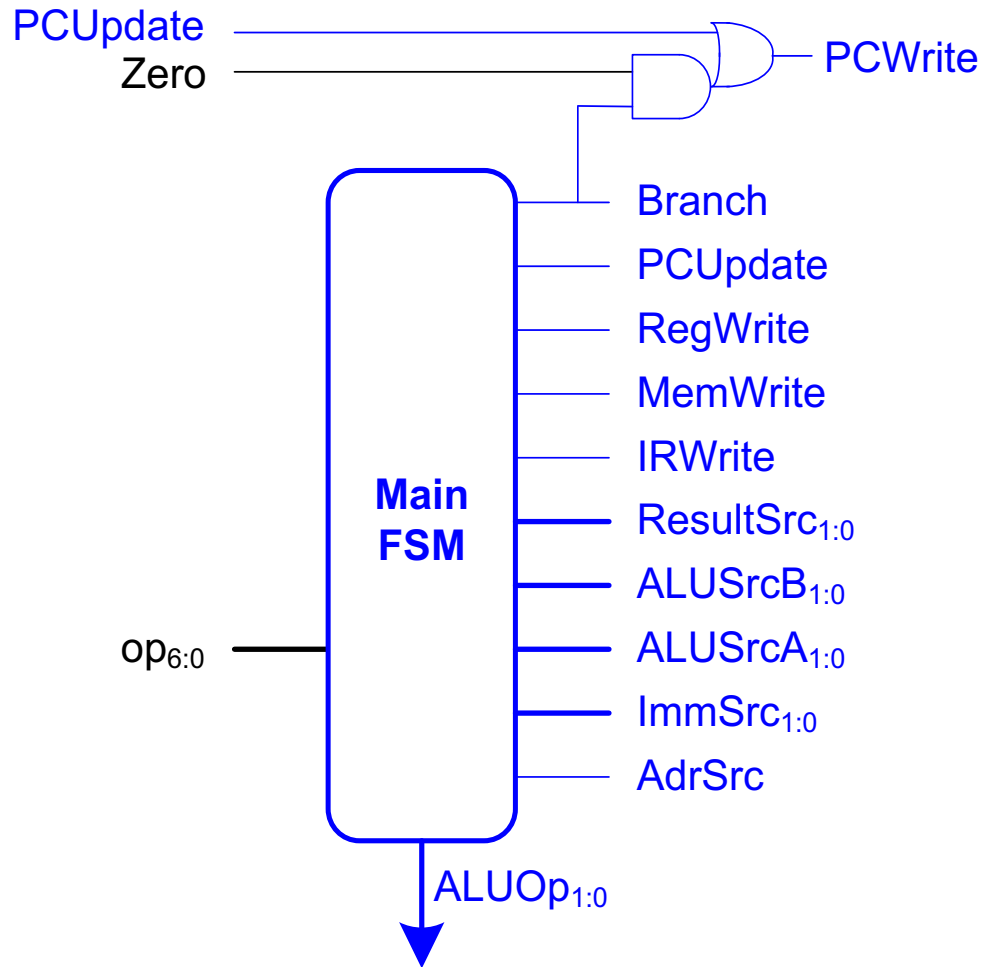


# Main Controller FSM: Fetch

Reset


**S0: Fetch**  
AdrSrc = 0  
IRWrite

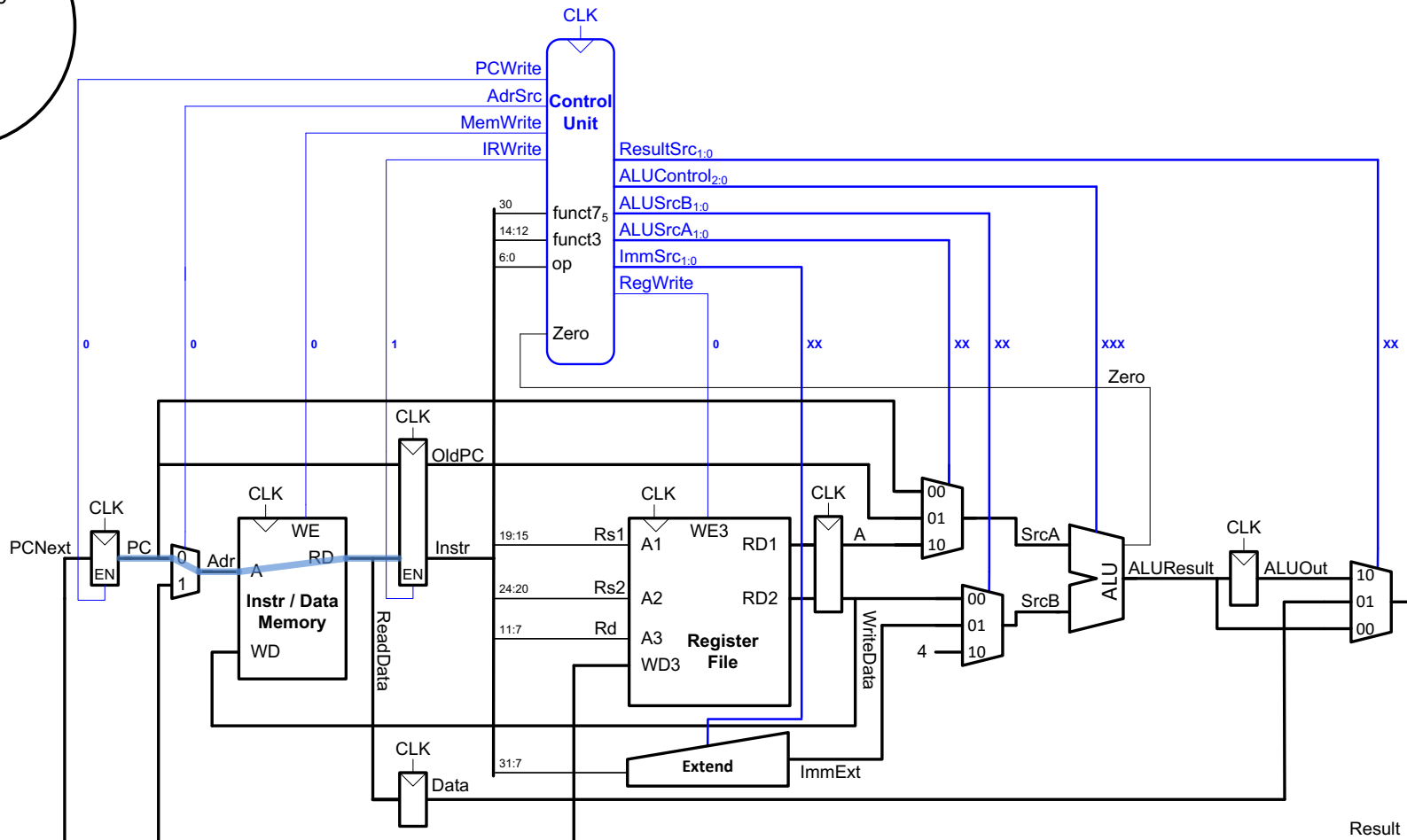


# Main Controller FSM: Decode

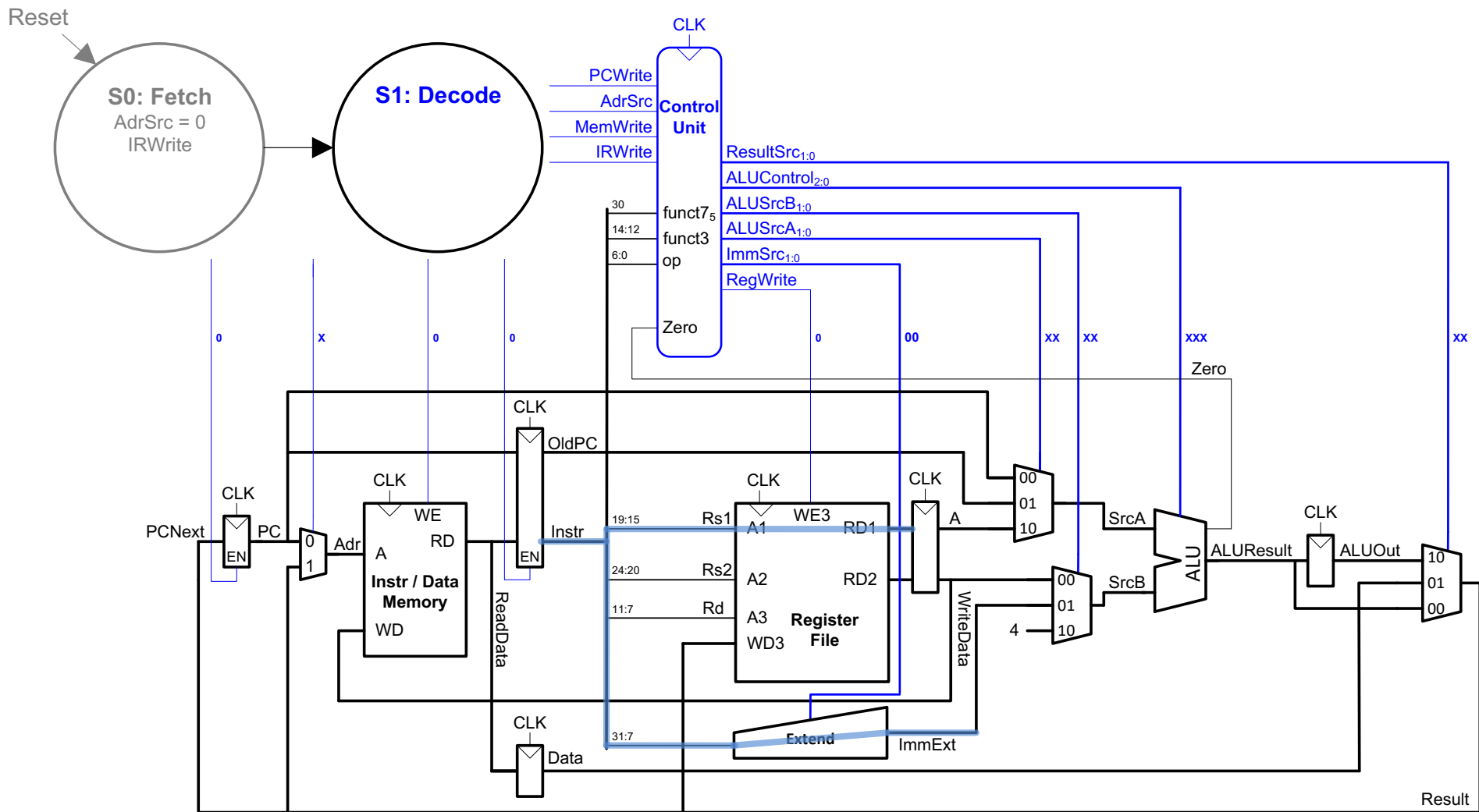


# Main Controller FSM: Address

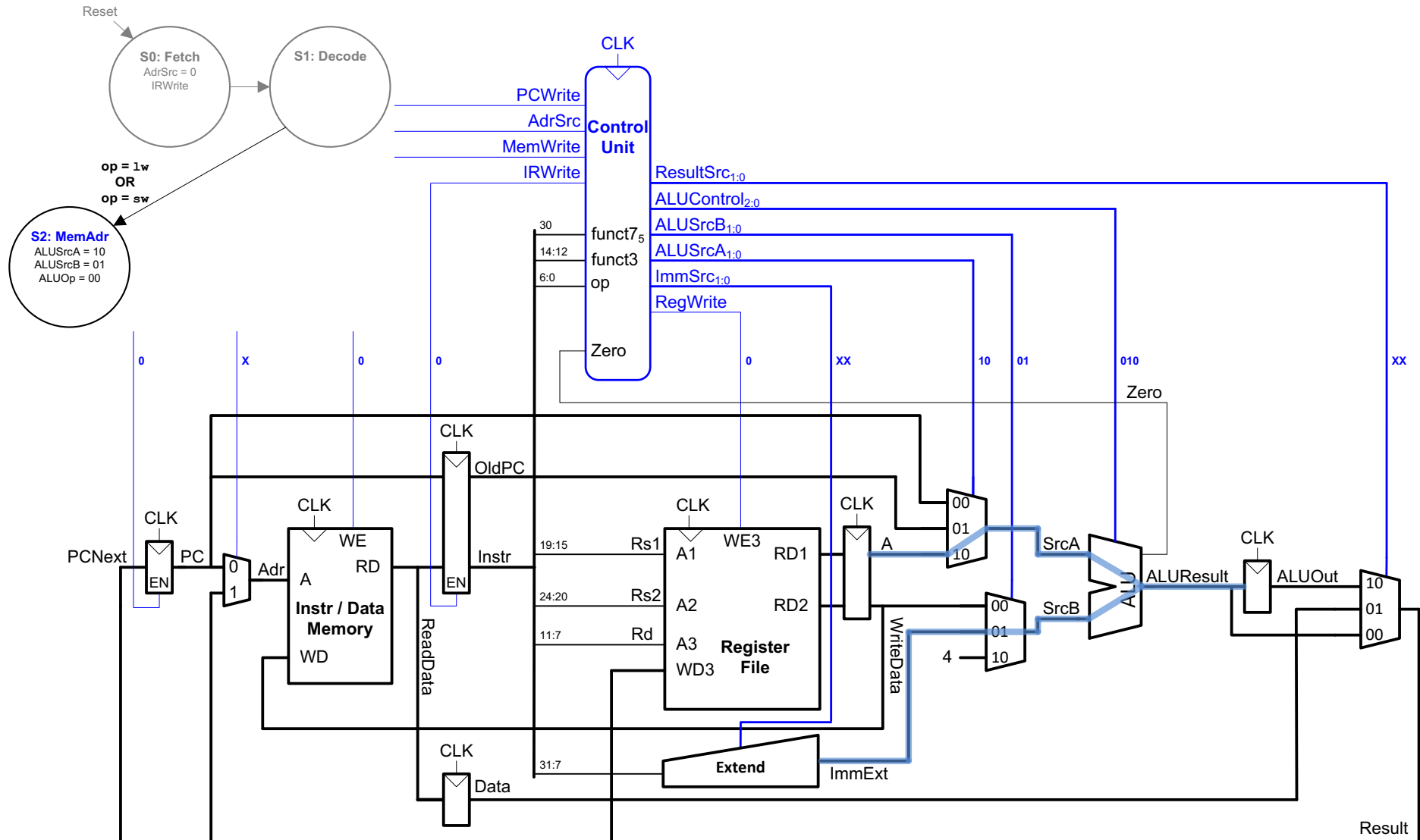


# Main Controller FSM: Read Memory

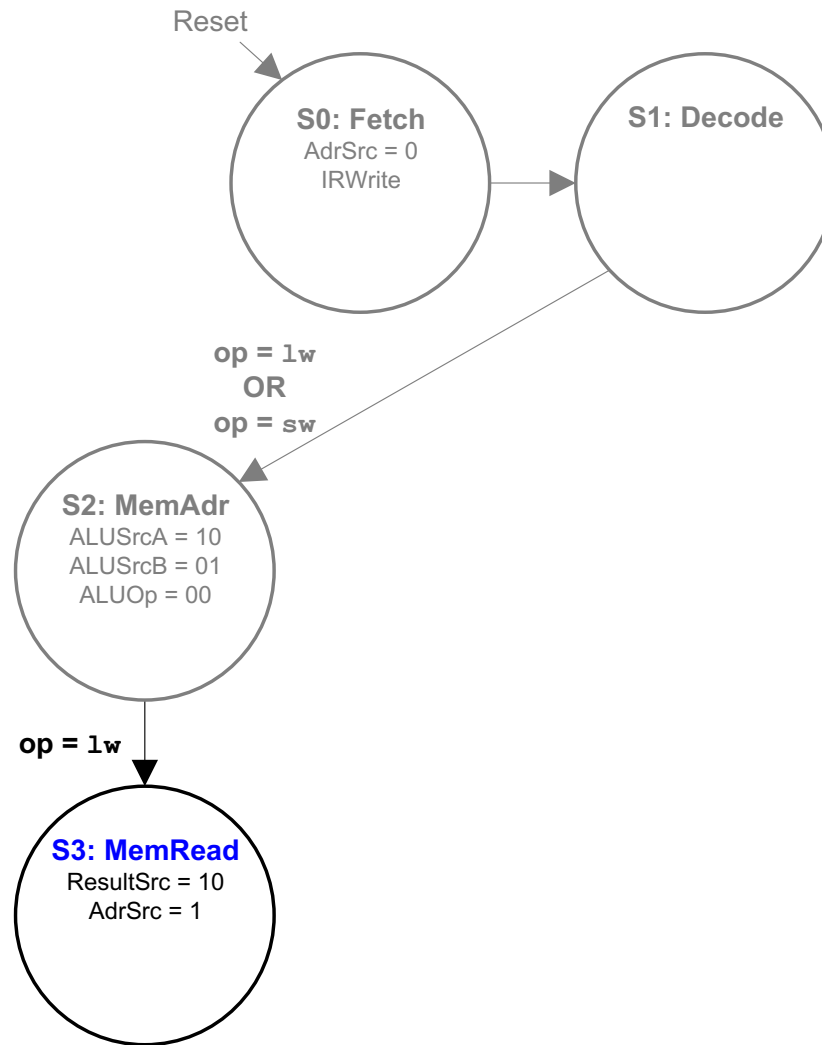

# Multicycle RISC-V Processor

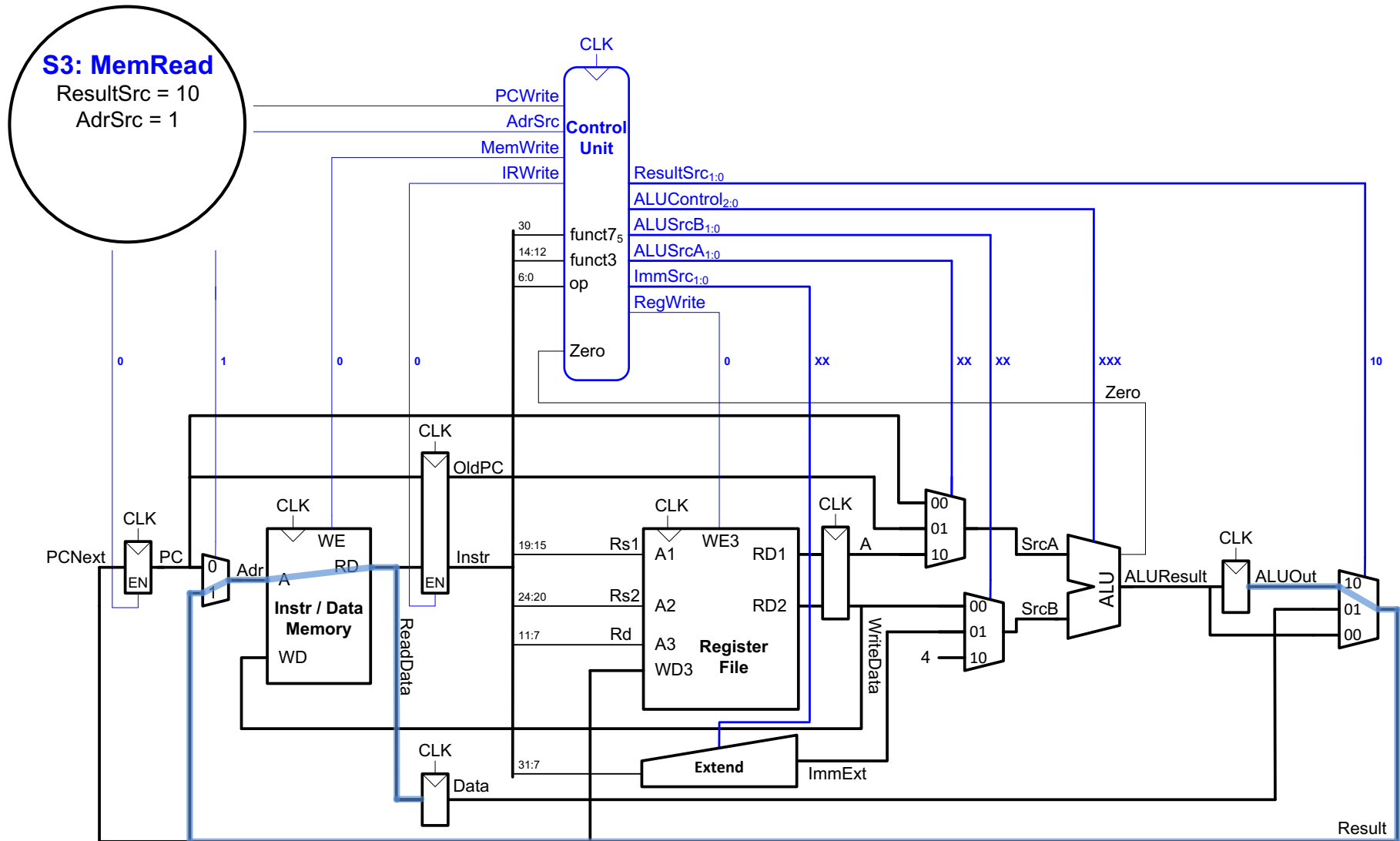


# Main Controller FSM: Write RF

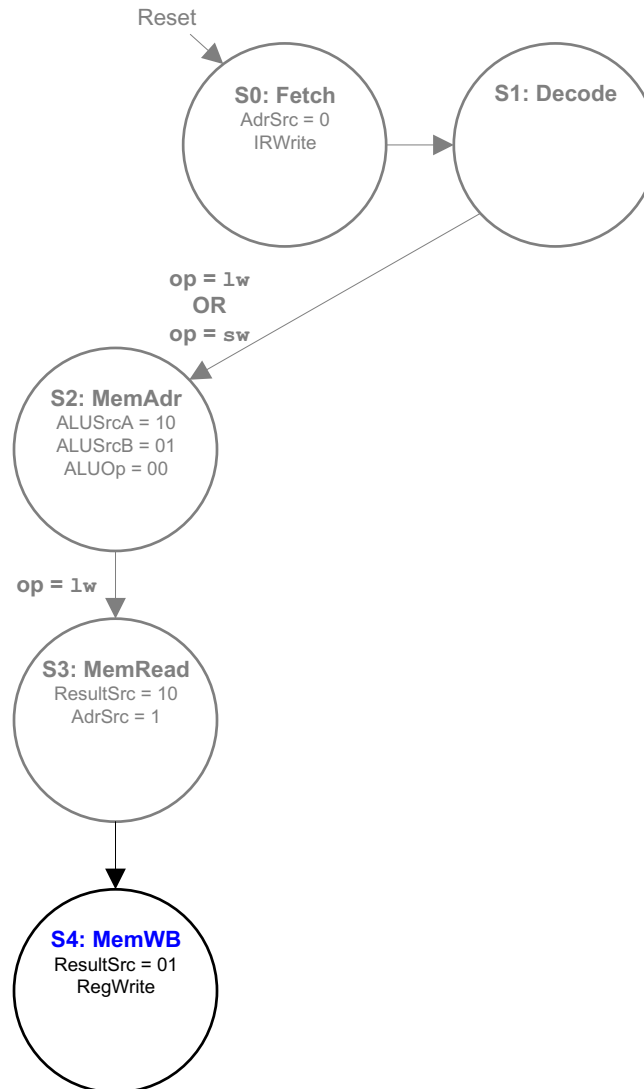



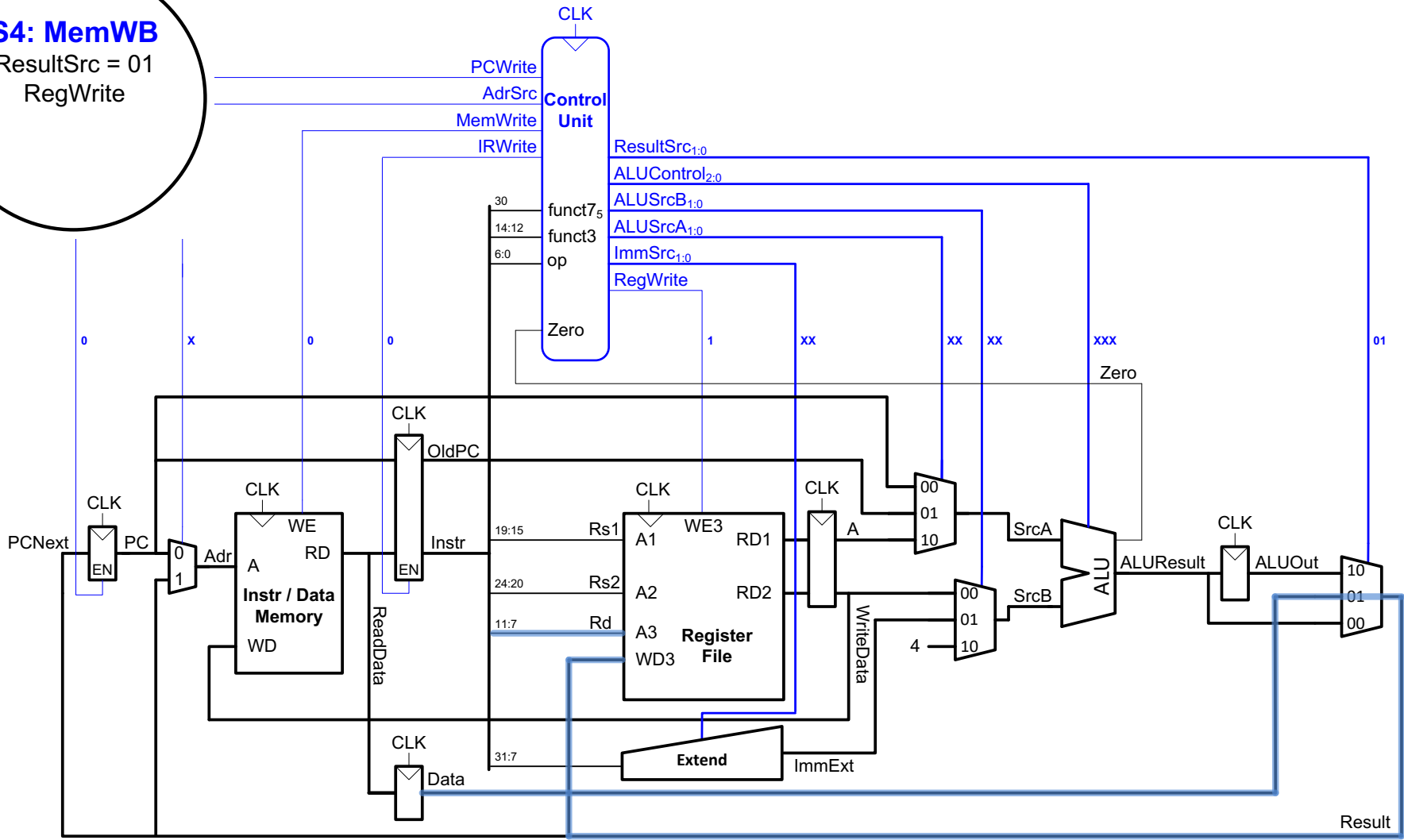
# Main Controller FSM: Write RF

**S4: MemWB**  
 ResultSrc = 01  
 RegWrite




# Main Controller FSM: Fetch Revisited

 


- **ALU** isn't being used
- Use ALU to calculate **PC+4**

# Main Controller FSM: Fetch Revisited

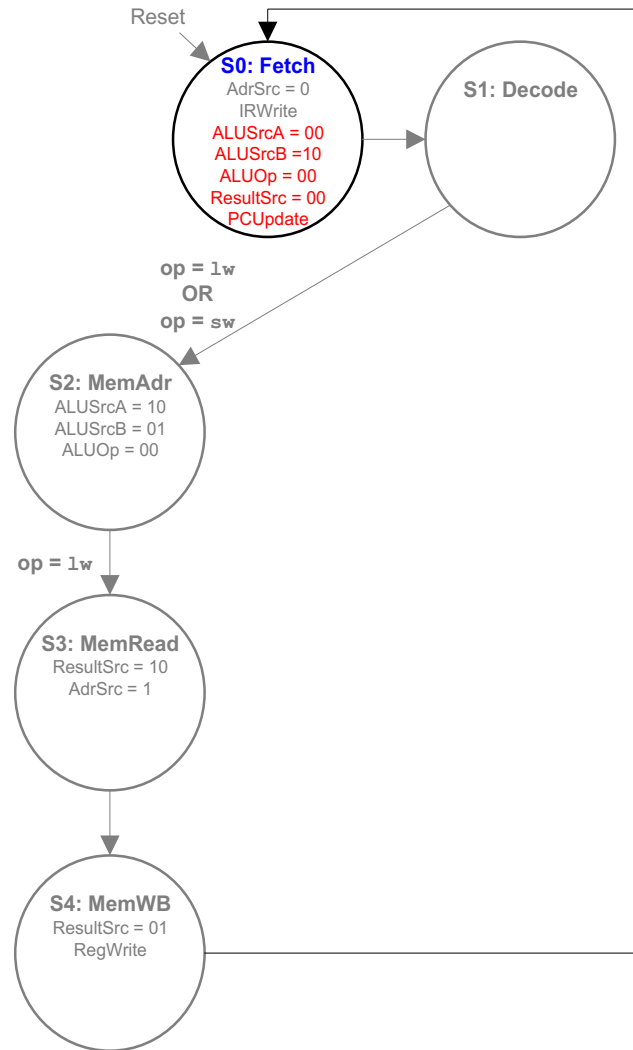

# Main Controller FSM: Fetch Revisited

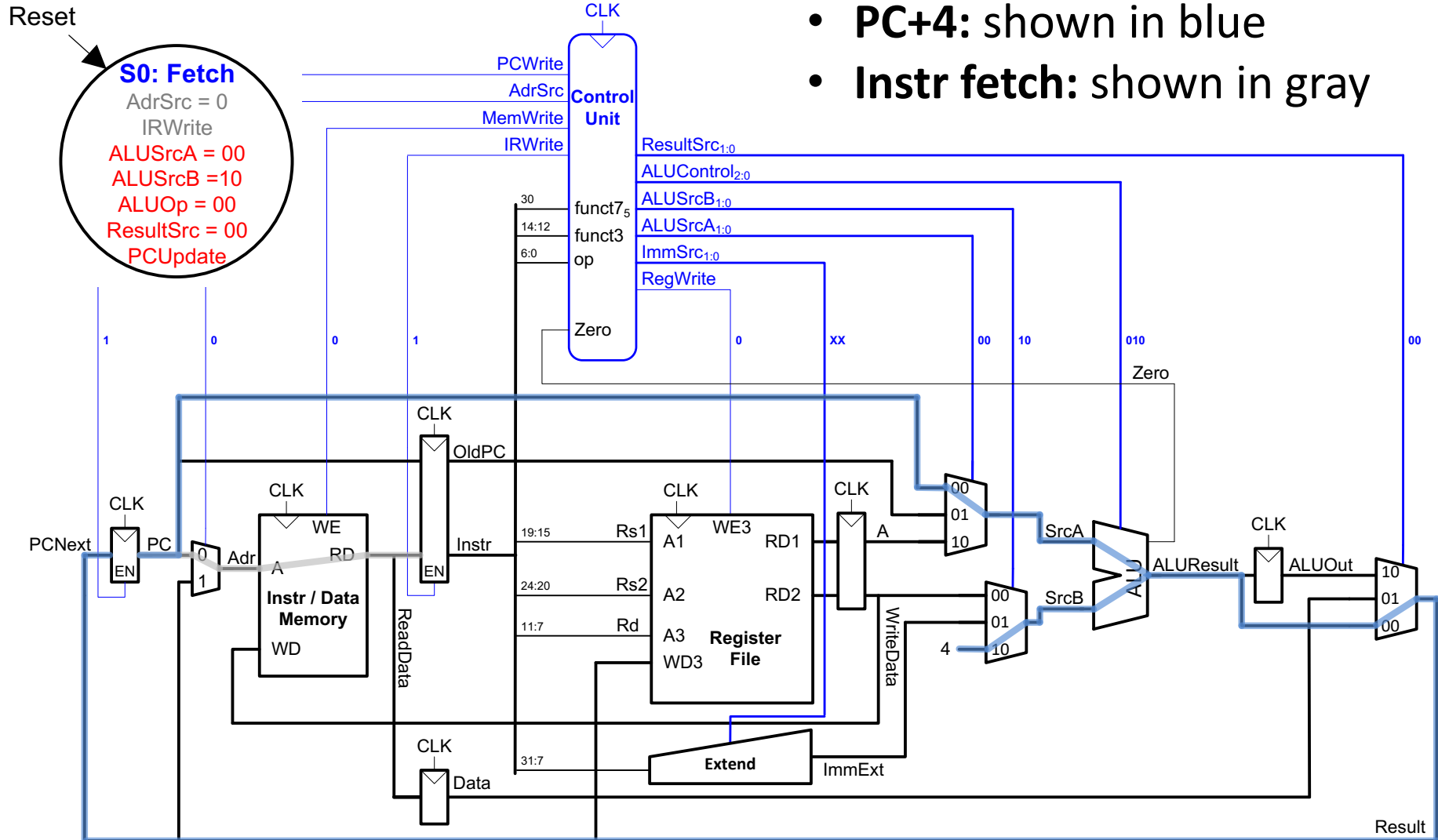

- **PC+4**: shown in blue
- **Instr fetch**: shown in gray