## **Digital Electronics & Computer Engineering (E85)**

Harris Fall 2019

#### **Final Exam**

This is a closed-book take-home exam. Electronic devices including calculators are not allowed, except on the computer question on the last page. You are permitted two 8.5x11" sheets of paper with notes.

You are bound by the HMC Honor Code while taking this exam.

The first part of the exam is written, while the final page is done on the computer based on your E85 Lab 11. The entire Lab 11 that you use (including datapath and controller) must be your own work; it cannot, for example, include somebody else's controller. The exam is intended to be doable in 3 hours if you have prepared adequately. However, there will be no limit on the time you are allowed except that the written portion must be completed in one contiguous block of time and the computer part must be completed in another contiguous block of time. A contiguous block of time is a period of time working at a desk without breaking for meals, naps, socializing, etc. You cannot study for E85 or consult E85 resources between the two blocks of time. Please manage your time wisely and do not let the exam expand to take more time than is justified.

Return the exam to the E85 box in the Engineering Department Office no later than Wednesday 12/18 at noon.

Alongside each question, the number of points is written in brackets. All work and answers should be written directly on this examination booklet, except for printouts. Use the backs of pages if necessary. Write neatly; illegible answers will be marked wrong. Show your work for partial credit.

Name:	
Do Not Write Below	v This Point
Page 2:	/ 4
Page 3:	/ 4
Page 4:	/7
Page 5:	/ 3
Page 6:	/ 5
Page 7:	/ 5
Page 9:	/ 4
Page 10:	/ 4
Page 11:	/ 8
Page 16:	/6
Total:	/ 50

number in hexac	-	c sum C = A	A + B, and write	e the result as	a floating-point
		1	Decimal Value	of A:	
		]	Decimal Value	of B:	
		1	Decimal Value	of C:	
	Hex	adecimal R	Representation (	of C:	

[4] Interpret A = 0x40D40000 and B = 0xC0C80000 as IEEE single-precision floating

An AND-OR-INVERT-22 (AOI22) gate computes  $Y = \sim (AB + CD)$ . The symbol is shown below. An AOI22 is considered one compound gate, not three individual gates.




[2] Using only an AOI22 gate and inverters, sketch a schematic for a 2:1 multiplexer. Let your inputs be S, D0, and D1, and your output be Y.

[2] Is it possible to perform any arbitrary function of 2 variables using a single AOI22 gate and as many inverters as you want? Explain why, or give a counterexample.

YES / NO

(explanation / counterexample)

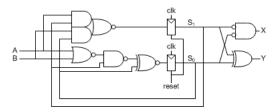Consider the circuit below. Notice that the circuit uses an AOI22 gate defined in the previous problem.




[4] Draw a state transition diagram for the circuit.

[3] Suppose the inputs below are applied. Sketch the behavior of the states and outputs.



reset

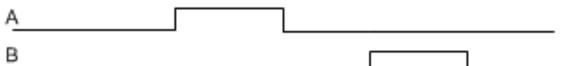

S1

S0


Х

Υ

[3] Write Behavioral Verilog code for the circuit based on your state transition diagram.

endmodule

 Consider the same circuit, repeated here for your convenience.



[2] How many logic elements are required to build this circuit on our Spartan FPGA?

Logic	Elements	

[3] Suppose that each input or clock pin of each gate or register has 3 fF of capacitance. (Note that the AOI22 has 4 input pins.) The X and Y outputs each drive 10 fF of capacitance. Suppose that the data signals have an average activity factor  $\alpha$  of 0.1, and reset has an activity factor of approximately 0. The power supply voltage is  $\sqrt{2}$  V, and the circuit operates at 1 GHz. Compute the power consumption of the circuit.

Power (Watts)

[5] Write an assembly language function to compare two strings. The answer should be 1 if the first string comes earlier in alphabetical (ASCII) order than the second, -1 if the first string comes later than the second, and 0 if the strings are identical. When the function is called, R0 and R1 contain the base address of two null-termianted strings. Return your result in R0. Hint: MVN R0, #0 puts -1 in R0.

Use ASCII order for comparison of nonalphabetic characters. For example,

```
strcmp("Alicia", "Ben") = 1
strcmp("MIT", "HMC") = -1
strcmp("Finals", "Finals") = 0
strcmp("E85A", "E85") = -1
strcmp("cash", "ca$h") = -1 because the ASCII value for s is 115 and for $ is 36.
```

[4] Refer to the memory maps below using the I2C1 Inter-integrated circuit port. Write a C function to set the 10-bit Own Address field (OA1) of the I2C\_OAR1 to 0x047 and then wait until the Receive Not Empty (RXNE) field of the I2\_ISR is true. Don't rely on any libraries; define the register addresses yourself.

Table 101. I2C register map and reset values

		_	_	_						_			_		-   -		<u> </u>									_	_						_
Offset	Register	31	30	29	78	27	56	52	24	23	22	21	20	19	18	17	16	12	14	13	12	11	10	6	∞	7	9	2	4	3	2	-	0
0x0	I2C_CR1	Res.	Res.	Res.	Res.	Res.	Res.	Res.	Res.	PECEN	ALERTEN	SMBDEN	SMBHEN	GCEN	WUPEN	NOSTRETCH	SBC	RXDMAEN	TXDMAEN	Res.	ANFOFF	С	ONF	[3:0	)]	ERRIE	TCIE	STOPIE	NACKIE	ADDRIE	RXIE	TXIE	PE
	Reset value									0	0	0	0	0	0	0	0	0	0		0	0	0	0	0	0	0	0	0	0	0	0	0
0x4	I2C_CR2	Res.	Res.	Res.	Res.	Res.	PECBYTE	AUTOEND	RELOAD			NB	ΥΤΙ	ES[7	7:0]			NACK	STOP	START	HEAD10R	ADD10	RD_WRN	SADD[9:0]									
	Reset value						0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0
0x8	I2C_OAR1	Res.	Res.	Res.	Res.	Res.	Res.	Res.	Res.	Res.	Res.	Res.	Res.	Res.	Res.	Res.	Res.	OA1EN	Res.	Res.	Res.	Res.	OA1MODE				(	DA1	[9:0	]			
	Reset value																	0					0	0	0	0	0	0	0	0	0	0	0
0xC	I2C_OAR2	Res.	Res.	Res.	Res.	Res.	Res.	Res.	Res.	Res.	Res.	Res.	Res.	Res.	Res.	Res.	Res.	OA2EN	Res.	Res.	Res.	Res.		DA2MS K [2:0] OA2[7:1]				Res.					
	Reset value																	0					0	0	0	0	0	0	0	0	0	0	
0x10	I2C_TIMINGR	PI	RES	SC[3	3:0]	Res.	Res.	Res.	Res.	sc	LD	EL[;	3:0	SI	DAE C	EL	3:			S	CLF	H[7:0	0]	SCLL[7:0]									
	Reset value	0	0	0	0					0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0
0x14	I2C_ TIMEOUTR	TEXTEN	Res.	Res.	Res.				Т	IME	OU	тв[	11:0	0]	•			TIMOUTEN	Doe	1000	TIDLE			TIMEOUTA[11:0]									
	Reset value	0				0	0	0	0	0	0	0	0	0	0	0	0	0			0	0	0	0	0	0	0	0	0	0	0	0	0
0x18	I2C_ISR	Res.	Res.	Res.	Res.	Res.	Res.	Res.	Res.		ΑĽ	DDC	OD	E[6	:0]		DIR	BUSY	Res.	ALERT	TIMEOUT	PECERR	OVR	ARLO	BERR	TCR	5	STOPF	NACKF	ADDR	RXNE	TXIS	TXE
	Reset value									0	0	0	0	0	0	0	0	0		0	0	0	0	0	0	0	0	0	0	0	0	0	1

Table 1. STM32F0xx peripheral register boundary addresses (continued)

Bus	Boundary address	Size	Peripheral	Peripheral register map
	0x4000 7C00 - 0x4000 7FFF	1 KB	Reserved	
	0x4000 7800 - 0x4000 7BFF	1 KB	CEC	Section 31.7.7 on page 910
	0x4000 7400 - 0x4000 77FF	1 KB	DAC	Section 14.10.15 on page 291
	0x4000 7000 - 0x4000 73FF	1 KB	PWR	Section 5.4.3 on page 92
	0x4000 6C00 - 0x4000 6FFF	1 KB	CRS	Section 7.6.5 on page 147
	0x4000 6800 - 0x4000 6BFF	1 KB	Reserved	
	0x4000 6400 - 0x4000 67FF	1 KB	CAN	Section 29.9.5 on page 854
	0x4000 6000 - 0x4000 63FF	1 KB	USB/CAN SRAM	Section 30.6.3 on page 890
	0x4000 5C00 - 0x4000 5FFF	1 KB	USB	Section 30.6.3 on page 890
	0x4000 5800 - 0x4000 5BFF	1 KB	I2C2	Section 26.7.12 on page 685
	0x4000 5400 - 0x4000 57FF	1 KB	I2C1	Section 26.7.12 on page 685

(put solution on next page)

```
void i2c_twiddling(void) {
```

}

Consider the following program. Initially, suppose R5 contains the value 0x0400 and memory location 0x420 contains the value 17.

LDR R6, [R5, #0x20]
ADD R7, R6, #1
SUBS R1, R5, #42
BNE AROUND
SUB R8, R5, #30
ADD R8, R8, R7
STR R8, [R5, #0x24]
AROUND
STR R7, [R5, #0x28]

The program is executed on our pipelined processor with the same hazard handling you considered in class and Problem Set 10. The behavior of the pipeline for the first instruction is illustrated below. For example, in cycle 2, the value 0x0400 is read from the first port of the register file.




- [1] What value is written to the register file on cycle 5?
- [1] What does the ALU do on cycle 6?
- [1] In which cycle is the memory written?
- [1] Which memory address is written?

The ARM LDR Rd, [Rn, imm]! is like an ordinary LDR but also updates the base address Rn = Rn + imm. This is called a pre-indexed load. For example, if R1 is initially 0x1000, and memory location 0x1008 contains 42, then LDR R2, [R1, #8] puts 42 in R2 and 0x1008 in R1. In ARM machine language, the W bit of the function field is 1 for pre-indexed loads and 0 for ordinary loads. Note that Ibar = 0, P = 1, U = 1, B = 0, and L = 1 for both kinds of loads. Modify the ARM multicycle processor to support the preindexed load instruction, using as little additional hardware as feasible.

- [3] Mark up the attached multicycle processor diagram and ALU to handle the new instructions.
- [2] Mark up the attached multicycle controller (including state transition diagram and truth tables) to handle the new instructions.
- [2] The attached multicycle memfile.s test code has highlighted modifications to test the new instruction. As compared to the memfile.s from Lab 11, it replaces the LDR instruction at 0x4C with an a pre-indexed load.

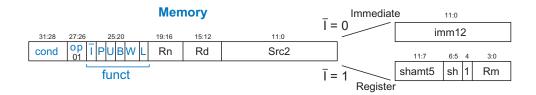Translate the pre-indexed command to machine language. Express your code in hexadecimal. The format for a memory instruction is given below. The cond field for ALWAYS is 1110. Hint:  $231_{10} = E7_{16}$ .



LDR R3, [R2, #231]!
---------------------

[1] Predict what value should be written to mem[248] at the last line of the program.

## Multicycle Processor


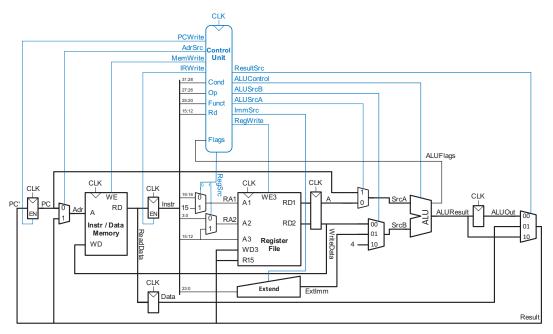


Figure 7.30 Complete multicycle processor

### ALU

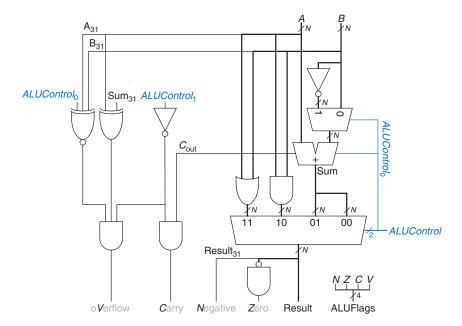

## Multicycle Controller


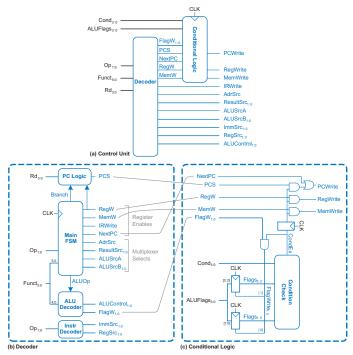


Figure 7.31 Multicycle control unit

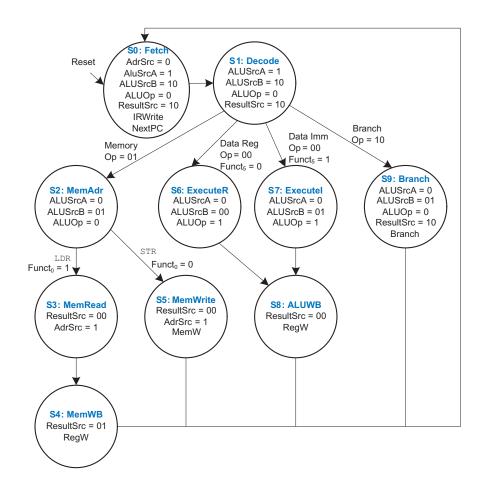

Page 13 of 16

Table 7.6 Instr Decoder logic for RegSrc and ImmSrc

Instruction	Op	Funct <sub>5</sub>	Funct <sub>0</sub>	RegSrc <sub>1</sub>	RegSrc <sub>0</sub>	$ImmSrc_{1:0}$
LDR	01	X	1	X	0	01
STR	01	X	0	1	0	01
DP immediate	00	1	X	X	0	00
DP register	00	0	X	0	0	00
В	10	X	X	X	1	10


ALUOp	Funct <sub>4:1</sub> (cmd)	Funct <sub>0</sub> (S)	Туре	$ALUControl_{1:0}$	$FlagW_{1:0}$
0	X	X	Not DP	00 (Add)	00
1	0100	0	ADD	00 (Add)	00
		1			11
	0010	0	SUB	01 (Sub)	00
		1			11
	0000	0	AND	10 (And)	00
		1			10
	1100	0	ORR	11 (Or)	00
		1			10


; memfile.dat


```
MATN
         ; R0 = 0
SUB RO, R15, R15
                   1110 000 0010 0 1111 0000 0000 0000 1111 E04F000F 0x00
ADD R2, R0, #5
          ; R2 = 5
                   1110 001 0100 0 0000 0010 0000 0000 0101 E2802005 0x04
ADD R3, R0, #12
          ; R3 = 12
                    1110 001 0100 0 0000 0011 0000 0000 1100 E280300C 0x08
SUB R7, R3, #9
          ; R7 = 3
                   1110 001 0010 0 0011 0111 0000 0000 1001 E2437009 0x0c
          ORR R4, R7, R2
AND R5, R3, R4
          ADD R5, R5, R4
SUBS R5, R5, #10
          ; R5 = 1 - 2 = -1
                   SUBSGT R5, R5, #2
ADD R5, R5, #12
          ; R5 = -1 + 12 = 11 1110 001 0100 0 0101 0101 0000 0000 1100 E285500C 0x24
SUBS R8, R5, R7
          BEO END
          ; not taken
                    0000 1010 0000 0000 0000 0000 1100 0A00000F 0x2c
          SUBS R8, R3, R4
BGE AROUND
          ADD R5, R0, #0
AROUND
          ; R8 = 3 - 5 = -2
SUBS R8, R7, R2
                   ADDLT R7, R5, #1
          ; R7 = 11+1 = 12
                    ; R7 = 12-5 = 7
SUB R7, R7, R2
                    STR R7, [R3, #224]
LDR R3, [R2, #231]!
          ; PC <- PC + 8
                    ADD R15, R15, R0
          ADD R2, R0, #14
B END
                    1110 1010 0000 0000 0000 0000 0001 EA000001 0x58
          ; alwavs taken
          ADD R2, R0, #13
ADD R2, R0, #10
         END
STR R2, [R0, #248]
         ; mem[248] = ?
                  1110 010 1100 0 0000 0010 0000 1111 1000 E58020F8 0x64
```

#### END OF WRITTEN PORTION OF EXAM
 
# DO NOT PROCEED PAST THIS POINT UNTIL YOU ARE PREPARED TO CEASE ALL WORK ON THE WRITTEN PORTION AND MOVE ON TO THE COMPUTER PORTION.



 

 



#### **COMPUTER PORTION OF EXAM**

Once you start this question, you may refer to the written portion of the exam, but may not spend any more time on the written portion or change any of your answers on that portion.

Modify your ARM multicycle processor from Lab 11 to support the pre-indexed load instruction. Modify your memfile.dat to replace the existing LDR instruction with the preindexed load.

[2] Print out your Verilog code and circle or highlight the lines you modified.

[4] Print out a simulation waveform showing at least the value being written to memory location 248 on the last cycle. Circle this value in the waveform.