 


E85 Digital Design & Computer Engineering




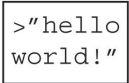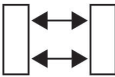
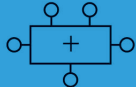

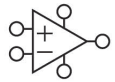




Lecture 3: Timing & Sequential Circuits

**HARVEY
MUDD
COLLEGE**

Lecture 3

- **Timing**
- **Sequential Circuits**
- **Latches and Flip-Flops**
- **Synchronous Logic Design**


Application Software	
Operating Systems	
Architecture	
Micro-architecture	
Logic	
Digital Circuits	
Analog Circuits	
Devices	
Physics	



Introduction


A logic circuit is composed of:

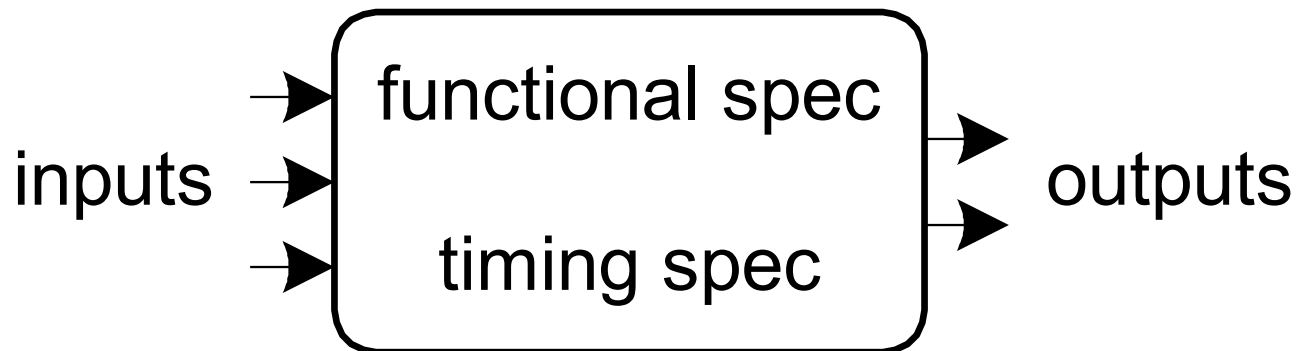- Inputs
- Outputs
- Functional specification
- Timing specification




Timing

 - **Delay:** time between input change and output changing
- How to build fast circuits?



Propagation & Contamination Delay

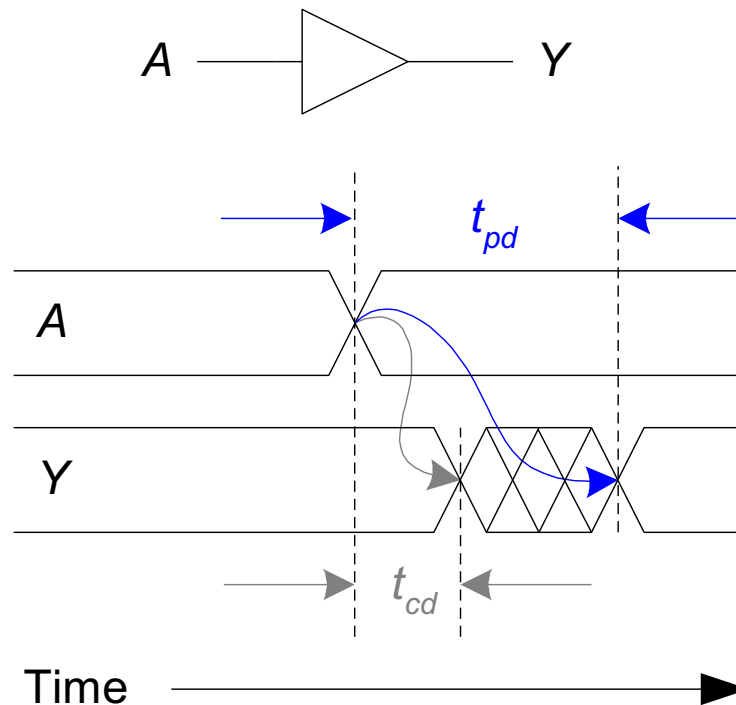- **Propagation delay:** t_{pd} = max delay from input to output
- **Contamination delay:** t_{cd} = min delay from input to output




Propagation & Contamination Delay

- Delay is caused by
 - Capacitance and resistance in a circuit
 - Speed of light limitation
- Reasons why t_{pd} and t_{cd} may be different:
 - Different rising and falling delays
 - Multiple inputs and outputs, some of which are faster than others
 - Circuits slow down when hot and speed up when cold



Critical (Long) & Short Paths

 

Critical (Long) Path: $t_{pd} = 2t_{pd_AND} + t_{pd_OR}$


Short Path: $t_{cd} = t_{cd_AND}$



Example: 8-input OR Delay

- Find the minimum and maximum delay of this 8-input OR


Cell	Propagation Delay (ps)	Contamination Delay (ps)
OR2	20	15
OR3	25	19
OR4	35	28

 

Solution: 8-input OR Delay

- Find the minimum and maximum delay of this 8-input OR

Cell	Propagation Delay (ps)	Contamination Delay (ps)
OR2	20	15
OR3	25	19
OR4	35	28

 

- Annotate each node with earliest and latest arrivals
- Min = 15 ps from A_7 to Y .
- Max = 140 ps from A_0 to Y .



Example: Optimized 8-input OR

- Redesign the 8-input OR to be as fast as possible.

Cell	Propagation Delay (ps)	Contamination Delay (ps)
OR2	20	15
OR3	25	19
OR4	35	28






Example: Optimized 8-input OR

- Redesign the 8-input OR to be as fast as possible.

Cell	Propagation Delay (ps)	Contamination Delay (ps)
OR2	20	15
OR3	25	19
OR4	35	28

- Try various possibilities:

   


Solution: Optimized 8-input OR

- Redesign the 8-input OR to be as fast as possible.

Cell	Propagation Delay (ps)	Contamination Delay (ps)
OR2	20	15
OR3	25	19
OR4	35	28

 - Annotate delays. OR3+OR3 is fastest (50 ps).



Sequential Logic Introduction

- Outputs of sequential logic depend on current *and* prior input values – it has ***memory***.
- Some definitions:
 - **State**: all the information about past inputs necessary to explain its future behavior
 - **Latches and flip-flops**: state elements that store one bit of state
 - **Synchronous sequential circuits**: combinational logic followed by a bank of flip-flops



Sequential Circuits

- Give sequence to events
- Have memory (short-term)
- Use feedback from output to input to store information





State Elements

- The state of a circuit influences its future behavior
- State elements store state
 - Bistable circuit
 - SR Latch
 - D Latch
 - D Flip-flop



Bistable Circuit

  - Fundamental building block of other state elements
- Two outputs: Q, \bar{Q}
- No inputs



Bistable Circuit Analysis



- Consider the two possible cases:

– $Q = 0$:

then $Q = 0, \bar{Q} =$

– $Q = 1$:

then $Q = 1, \bar{Q} =$

  


- Stores 1 bit of state in the state variable, Q (or \bar{Q})
- But there are **no inputs to control the state**



SR (Set/Reset) Latch

- SR Latch

 


- Consider the four possible cases:
 - $S = 1, R = 0$
 - $S = 0, R = 1$
 - $S = 0, R = 0$
 - $S = 1, R = 1$



SR Latch Analysis


– $S = 1, R = 0$:

then $Q = 1$ and $\bar{Q} = 0$

 

– $S = 0, R = 1$:



then $Q = 0$ and $\bar{Q} = 1$

 

SR Latch Analysis


– $S = 0, R = 0$:

then $Q = Q_{prev}$

  

– $S = 1, R = 1$:


then $Q = 0, \bar{Q} = 0$

 

SR Latch Symbol

- SR stands for Set/Reset Latch
 - Stores one bit of state (Q)
- Control what value is being stored with S , R inputs
 - **Set:** Make the output 1
($S = 1, R = 0, Q = 1$)
 - **Reset:** Make the output 0
($S = 0, R = 1, Q = 0$)
- **Avoid invalid state**
(when $S = R = 1$)


SR Latch
Symbol

 


D Latch

- Two inputs: CLK , D
 - CLK : controls *when* the output changes
 - D (the data input): controls *what* the output changes to
- Function
 - When $CLK = 1$,
 D passes through to Q (*transparent*)
 - When $CLK = 0$,
 Q holds its previous value (*opaque*)
- Avoids invalid case when
 $Q \neq \text{NOT } \bar{Q}$

D Latch
Symbol

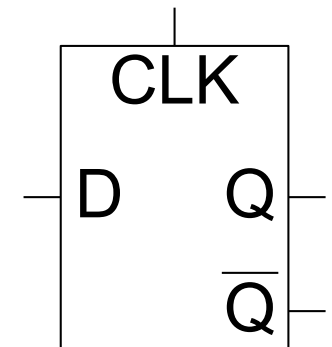

D Latch Internal Circuit

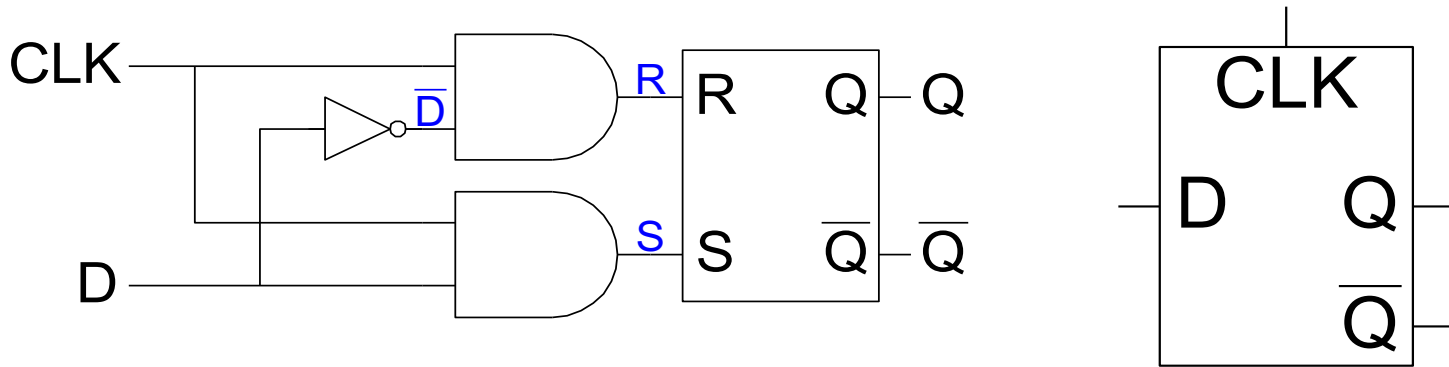


CLK	D	\overline{D}	S	R	Q	\overline{Q}
0	X					
1	0					
1	1					



D Flip-Flop


- **Inputs:** CLK , D
- **Function**
 - Samples D on rising edge of CLK
 - When CLK rises from 0 to 1, D passes through to Q
 - Otherwise, Q holds its previous value
 - Q changes only on rising edge of CLK
- Called *edge-triggered*
- Activated on the clock edge

D Flip-Flop Symbols


 


D Flip-Flop Internal Circuit

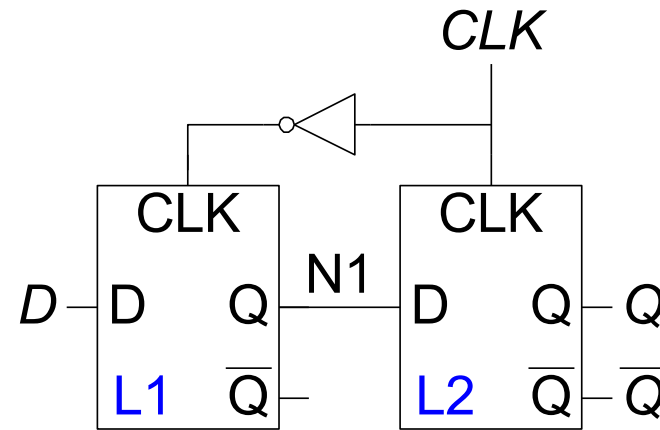
- Two back-to-back latches (L1 and L2) controlled by complementary clocks
- When $CLK = 0$
 - L1 is
 - L2 is
 - D passes through to N1
- When $CLK = 1$
 - L2 is
 - L1 is
 - N1 passes through to Q
- Thus, on the edge of the clock (when CLK rises from 0→1)
 - D passes through to Q



D Latch vs. D Flip-Flop

  


Registers: Multi-bit Flip-Flop

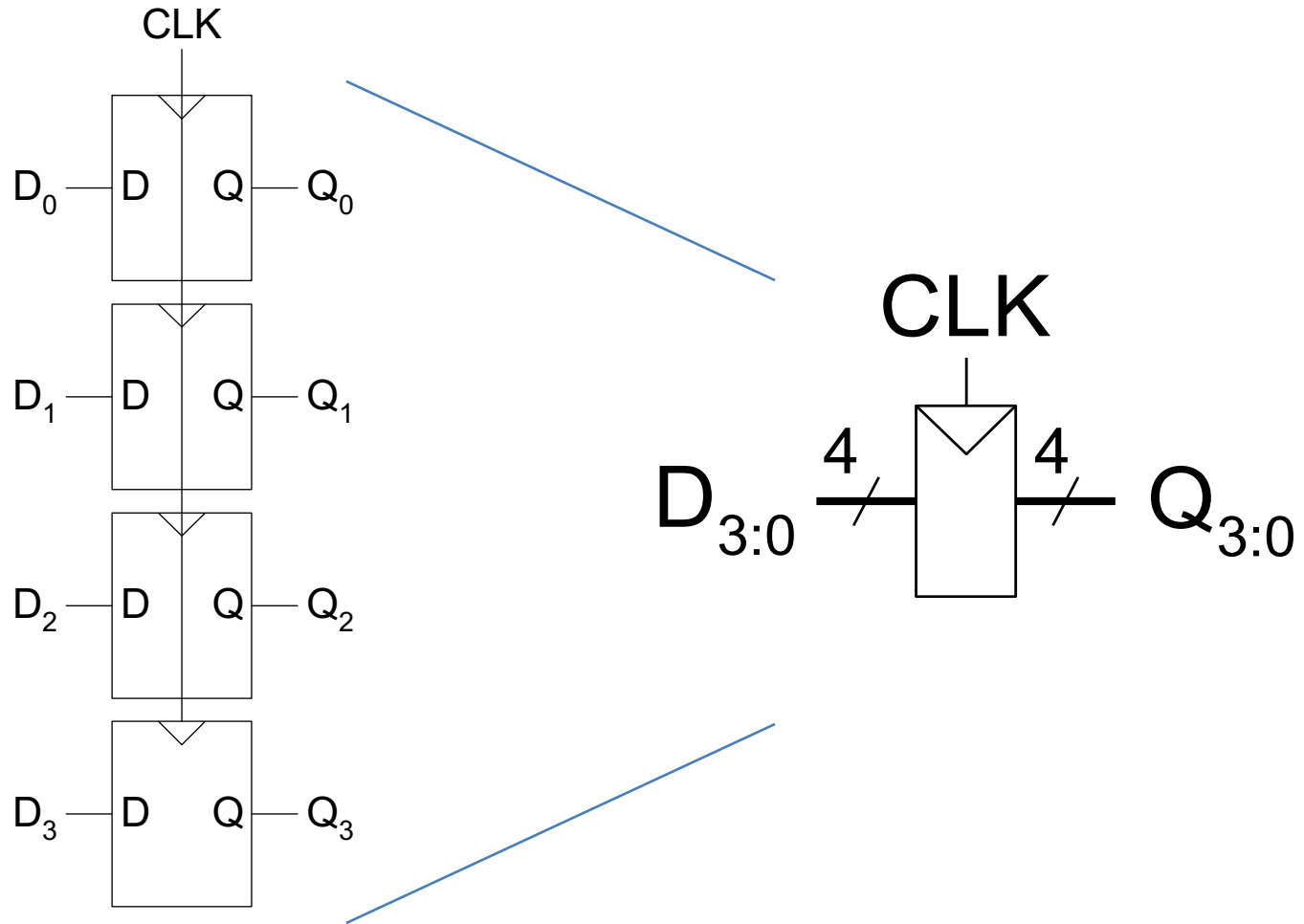

Enabled Flip-Flops


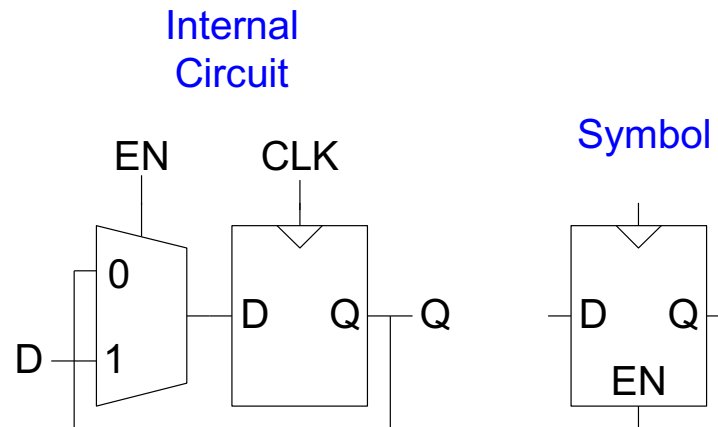
- **Inputs:** CLK , D , EN
 - The enable input (EN) controls when new data (D) is stored
- **Function**
 - $EN = 1$: D passes through to Q on the clock edge
 - $EN = 0$: the flip-flop retains its previous state



Resettable Flip-Flops

- **Inputs:** *CLK*, *D*, *Reset*
- **Function:**
 - **Reset = 1:** *Q* is forced to 0
 - **Reset = 0:** flip-flop behaves as ordinary D flip-flop

Symbols

  


Resettable Flip-Flops

- Two types:
 - **Synchronous:** resets at the clock edge only
 - **Asynchronous:** resets immediately when $Reset = 1$
- Asynchronously resettable flip-flop requires changing the internal circuitry of the flip-flop
- Synchronously resettable flip-flop?



Resettable Flip-Flops

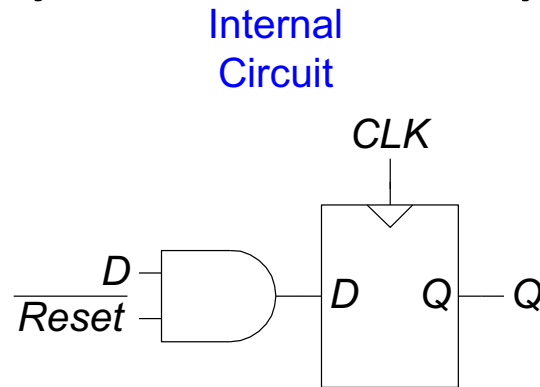
- Two types:
 - **Synchronous:** resets at the clock edge only
 - **Asynchronous:** resets immediately when $Reset = 1$
- Asynchronously resettable flip-flop requires changing the internal circuitry of the flip-flop
- Synchronously resettable flip-flop



Settable Flip-Flops



- **Inputs:** *CLK*, *D*, *Set*
- **Function:**
 - **Set = 1:** *Q* is set to 1
 - **Set = 0:** the flip-flop behaves as ordinary D flip-flop

Symbols

 

Sequential Logic

  - Sequential circuits: all circuits that aren't combinational
- A problematic circuit:



- No inputs and 1-3 outputs
- Astable circuit, oscillates
- Period depends on inverter delay
- It has a **cyclic path**: output fed back to input



SystemVerilog Description

```
module flop(input  logic clk, d,  
            output logic q);  
  
    always_ff @(posedge clk)  
        q <= d;  
endmodule
```

- Multi-input XOR: Odd parity




SystemVerilog Description

```
module flopenr(input  logic clk, en, reset, d,
               output logic q);

    always_ff @(posedge clk, posedge reset)
        if (reset)    q <= 0;
        else if (en)  q <= d;
endmodule
```

- Multi-input XOR: Odd parity

 

SystemVerilog Description

```
module flopenr #(parameter WIDTH = 4)
    (input  logic clk, reset, en,
     input  logic [WIDTH-1:0] d,
     output logic [WIDTH-1:0] q);
    always_ff @(posedge clk, posedge reset)
        if (reset) q <= 0;
        else if (en) q <= d;
endmodule
```

- Multi-input XOR: Odd parity



Synchronous Sequential Logic Design

- Breaks cyclic paths by **inserting registers**
- Registers contain **state** of the system
- State changes at clock edge: system **synchronized** to the clock
- **Rules** of synchronous sequential circuit composition:
 - Every circuit element is either a register or a combinational circuit
 - At least one circuit element is a register
 - All registers receive the same clock signal
 - Every cyclic path contains at least one register
- Two common synchronous sequential circuits
 - Finite State Machines (FSMs)
 - Pipelines

