 


E85 Digital Design & Computer Engineering

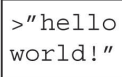



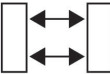
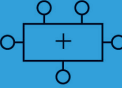
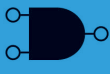


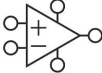

Lecture 7: Verilog Part II

**HARVEY
MUDD
COLLEGE**

Lecture 7

- **More Combinational Logic**
- **Finite State Machines**
- **Parameterized Modules**
- **Testbenches**

Application Software	
Operating Systems	
Architecture	
Micro-architecture	
Logic	
Digital Circuits	
Analog Circuits	
Devices	
Physics	



Other Behavioral Statements

- Statements that must be inside `always` statements:
 - `if / else`
 - `case, casez`



Combinational Logic using always

```
// combinational logic using an always statement
module gates(input logic [3:0] a, b,
             output logic [3:0] y1, y2, y3, y4, y5);
    always_comb // need begin/end because there is
    begin      // more than one statement in always
        y1 = a & b; // AND
        y2 = a | b; // OR
        y3 = a ^ b; // XOR
        y4 = ~(a & b); // NAND
        y5 = ~(a | b); // NOR
    end
endmodule
```

This hardware could be described with assign statements using fewer lines of code, so it's better to use assign statements in this case.



Combinational Logic using case

```
module sevenseg(input  logic [3:0] data,
                output logic [6:0] segments);

    always_comb
        case (data)
            //                abc_defg
            0: segments =    7'b111_1110;
            1: segments =    7'b011_0000;
            2: segments =    7'b110_1101;
            3: segments =    7'b111_1001;
            4: segments =    7'b011_0011;
            5: segments =    7'b101_1011;
            6: segments =    7'b101_1111;
            7: segments =    7'b111_0000;
            8: segments =    7'b111_1111;
            9: segments =    7'b111_0011;
            default: segments = 7'b000_0000; // required
        endcase
    endmodule
```



Combinational Logic using case


- case statement implies combinational logic **only if** all possible input combinations described
- Remember to use **default** statement



Combinational Logic using casez

```
module priority_casez(input logic [3:0] a,  
                    output logic [3:0] y);  
  
    always_comb  
        casez (a)  
            4'b1???: y = 4'b1000; // ?=don't care  
            4'b01??: y = 4'b0100;  
            4'b001?: y = 4'b0010;  
            4'b0001: y = 4'b0001;  
            default: y = 4'b0000;  
        endcase  
    endmodule
```

Synthesis:

 


Blocking vs. Nonblocking Assignment

- `<=` is **nonblocking** assignment
 - Occurs simultaneously with others
- `=` is **blocking** assignment
 - Occurs in order it appears in file


```
// Good synchronizer using
// nonblocking assignments
module syncgood(input logic clk,
                input logic d,
                output logic q);

     logic n1;
    always_ff @(posedge clk)
        begin
            n1 <= d; // nonblocking
            q <= n1; // nonblocking
        end
endmodule
```



```
// Bad synchronizer using
// blocking assignments
module syncbad(input logic clk,
               input logic d,
               output logic q);

     logic n1;
    always_ff @(posedge clk)
        begin
            n1 = d; // blocking
            q = n1; // blocking
        end
endmodule
```



Rules for Signal Assignment

- **Synchronous sequential logic:** use `always_ff @ (posedge clk)` and nonblocking assignments (`<=>`)

```
always_ff @(posedge clk)
    q <= d; // nonblocking
```

- **Simple combinational logic:** use continuous assignments (`assign...`)

```
assign y = a & b;
```


- **More complicated combinational logic:** use `always_comb` and blocking assignments (`=`)
- Assign a signal in **only one** `always` statement or continuous assignment statement.




Finite State Machines (FSMs)

- **Three blocks:**

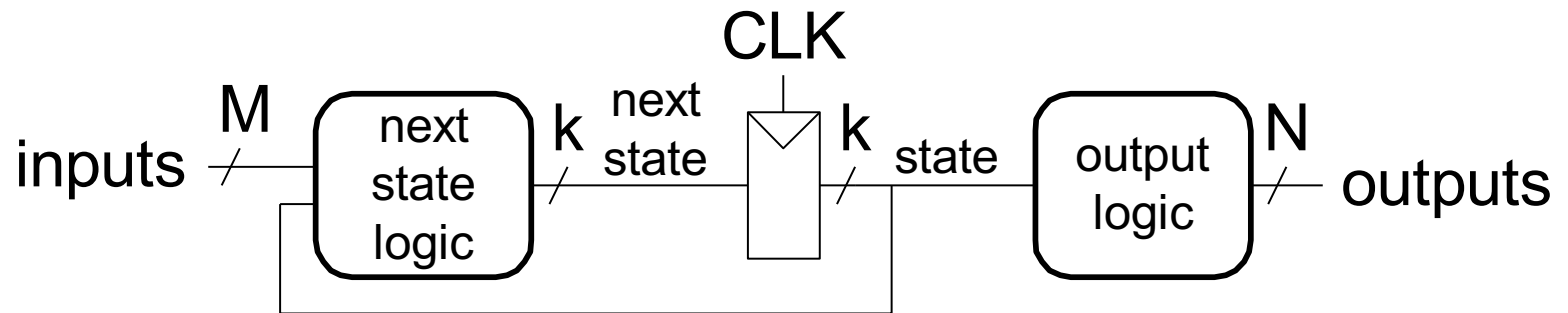- next state logic
- state register
- output logic



FSM Example: Divide by 3

 

The double circle indicates the reset state



FSM in SystemVerilog


```
module divideby3FSM(input  logic clk,
                   input  logic reset,
                   output logic q);

    typedef enum logic [1:0] {S0, S1, S2} statetype;
    statetype state, nextstate;

    // state register
    always_ff @(posedge clk, posedge reset)
        if (reset) state <= S0;
        else      state <= nextstate;

    // next state logic
    always_comb
        case (state)
            S0:    nextstate = S1;
            S1:    nextstate = S2;
            S2:    nextstate = S0;
            default: nextstate = S0;
        endcase

     // output logic
    assign q = (state == S0);
endmodule
```



FSM with Inputs


```
module fsmWithInputs(input  logic clk,
                    input  logic reset,
                    input  logic a,
                    output logic q);

typedef enum logic [1:0] {S0, S1, S2} statetype;
statetype state, nextstate;

// state register
always_ff @(posedge clk, posedge reset)
    if (reset) state <= S0;
    else      state <= nextstate;

// next state logic
always_comb
    case (state)
        S0:    if (a) nextstate = S1;
              else nextstate = S0;
        S1:    nextstate = S2;
        S2:    if (a) nextstate = S2;
              else nextstate = S0;
        default: nextstate = S0;
    endcase

 // output logic
assign q = (state == S2);
endmodule
```



Parameterized Modules

2:1 mux:

```
module mux2
    #(parameter width = 8) // name and default value
    (input logic [width-1:0] d0, d1,
     input logic s,
     output logic [width-1:0] y);
    assign y = s ? d1 : d0;
endmodule
```

Instance with 8-bit bus width (uses default):

```
mux2 myMux(d0, d1, s, out);
```

Instance with 12-bit bus width:

```
mux2 #(12) lowmux(d0, d1, s, out);
```



Testbenches

- HDL that tests another module: *device under test* (dut)
- Not synthesizable
- Uses different features of SystemVerilog
- Types:
 - Simple
 - Self-checking
 - Self-checking with testvectors



Testbench Example

- Write SystemVerilog code to implement the following function in hardware:

$$y = \overline{b}c + a\overline{b}$$

- Name the module `sillyfunction`



Testbench Example

- Write SystemVerilog code to implement the following function in hardware:

$$y = \overline{bc} + a\overline{b}$$

```
module sillyfunction(input  logic a, b, c,
                    output logic y);
    assign y = ~b & ~c | a & ~b;
endmodule
```



Simple Testbench

```
module testbench1();  
    logic a, b, c;  
    logic y;  
    // instantiate device under test  
    sillyfunction dut(a, b, c, y);  
    // apply inputs one at a time  
    initial begin  
        a = 0; b = 0; c = 0; #10;  
        c = 1; #10;  
        b = 1; c = 0; #10;  
        c = 1; #10;  
        a = 1; b = 0; c = 0; #10;  
        c = 1; #10;  
        b = 1; c = 0; #10;  
        c = 1; #10;  
    end  
endmodule
```



Self-checking Testbench

```
module testbench2();
  logic a, b, c;
  logic y;
  sillyfunction dut(a, b, c, y); // instantiate dut
  initial begin // apply inputs, check results one at a time
    a = 0; b = 0; c = 0; #10;
    if (y !== 1) $display("000 failed.");
    c = 1; #10;
    if (y !== 0) $display("001 failed.");
    b = 1; c = 0; #10;
    if (y !== 0) $display("010 failed.");
    c = 1; #10;
    if (y !== 0) $display("011 failed.");
    a = 1; b = 0; c = 0; #10;
    if (y !== 1) $display("100 failed.");
    c = 1; #10;
    if (y !== 1) $display("101 failed.");
    b = 1; c = 0; #10;
    if (y !== 0) $display("110 failed.");
    c = 1; #10;
    if (y !== 0) $display("111 failed.");
  end
endmodule
```




Testbench with Testvectors

- Testvector file: inputs and expected outputs
- Testbench:
 1. Generate clock for assigning inputs, reading outputs
 2. Read testvectors file into array
 3. Assign inputs, expected outputs
 4. Compare outputs with expected outputs and report errors



Testbench with Testvectors

 - Testbench clock:
 - assign inputs (on rising edge)
 - compare outputs with expected outputs (on falling edge).



- Testbench clock also used as clock for synchronous sequential circuits



Testvectors File

- **File:** `example.tv`
- contains vectors of `abc_yexpected`

```
000_1
001_0
010_0
011_0
100_1
101_1
110_0
111_0
```



1. Generate Clock

```
module testbench3();  
    logic        clk, reset;  
    logic        a, b, c, yexpected;  
    logic        y;  
    logic [31:0] vectornum, errors;    // bookkeeping variables  
    logic [3:0]  testvectors[10000:0]; // array of testvectors  
  
    // instantiate device under test  
    sillyfunction dut(a, b, c, y);  
  
    // generate clock  
    always        // no sensitivity list, so it always executes  
    begin  
        clk = 1; #5; clk = 0; #5;  
    end
```



2. Read Testvectors into Array

```
// at start of test, load vectors and pulse reset
```

```
initial
begin
    $readmemb("example.tv", testvectors);
    vectornum = 0; errors = 0;
    reset = 1; #27; reset = 0;
end
```

```
// Note: $readmemb reads testvector files written in
// hexadecimal
```



3. Assign Inputs & Expected Outputs

```
// apply test vectors on rising edge of clk
always @(posedge clk)
  begin
    #1; {a, b, c, yexpected} = testvectors[vectornum];
  end
```



4. Compare with Expected Outputs

```
// check results on falling edge of clk
```

```
always @(negedge clk)
```

```
    if (~reset) begin // skip during reset
```

```
        if (y !== yexpected) begin
```

```
            $display("Error: inputs = %b", {a, b, c});
```

```
            $display("  outputs = %b (%b expected)", y, yexpected);
```

```
            errors = errors + 1;
```

```
        end
```

```
// Note: to print in hexadecimal, use %h. For example,
```

```
//     $display("Error: inputs = %h", {a, b, c});
```



4. Compare with Expected Outputs

```
// increment array index and read next testvector
    vectornum = vectornum + 1;
    if (testvectors[vectornum] === 4'bx) begin
        $display("%d tests completed with %d errors",
                vectornum, errors);
        $stop;
    end
end
endmodule
```

```
// === and !== can compare values that are 1, 0, x, or z.
```

