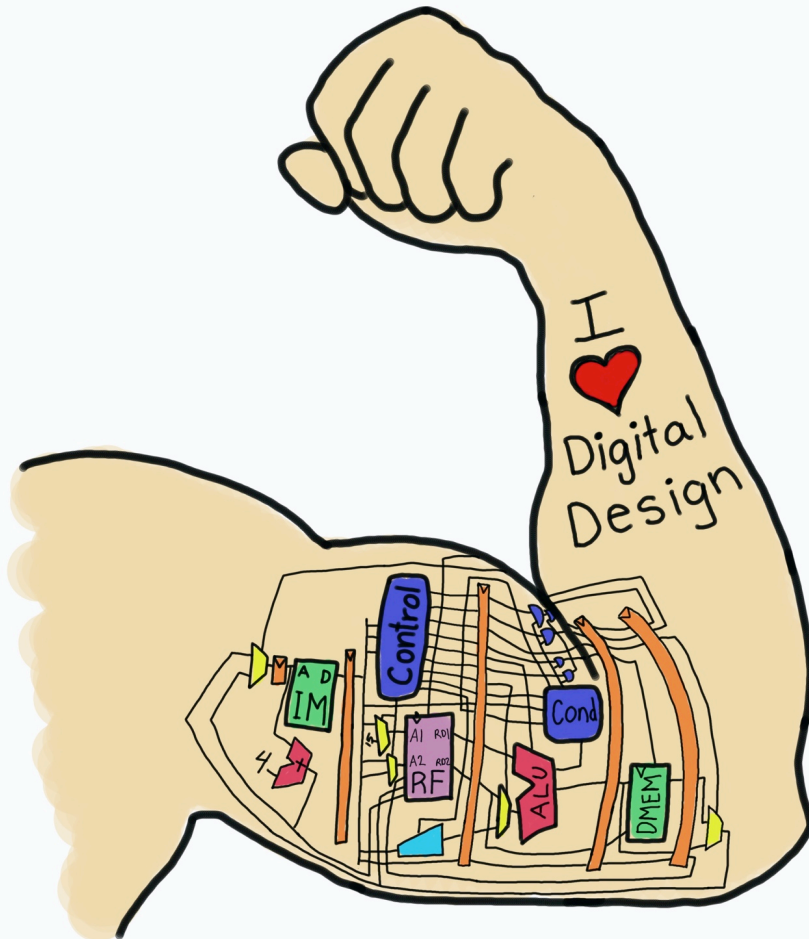


E85 Digital Design & Computer Engineering




Lecture 8: Arithmetic Circuits

**HARVEY
MUDD
COLLEGE**

Lecture 8

 - **Chapter 5 Introduction**
- **Arithmetic Circuits**
 - 1-bit Adders
 - N-bit Adders
 - Ripple Adders
 - Carry Lookahead Adders
 - Prefix Adders
 - Subtractors
 - Arithmetic/Logic Units




Chapter 5 Introduction

- **Digital building blocks:**
 - Gates, multiplexers, decoders, registers, arithmetic circuits, counters, memory arrays, logic arrays
- **Building blocks demonstrate hierarchy, modularity, and regularity:**
 - Hierarchy of simpler components
 - Well-defined interfaces and functions
 - Regular structure easily extends to different sizes
- **Will use these building blocks in Chapter 7 to build microprocessor**



1-Bit Adders

Half Adder

 


A	B	C_{out}	S
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

$$S = A \oplus B$$

$$C_{out} = A \cdot B$$

Full Adder

 

C_{in}	A	B	C_{out}	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	1	0
1	0	1	1	1
1	1	0	1	1
1	1	1	1	0


$$S = A \oplus B \oplus C_{in}$$

$$C_{out} = A \cdot B + C_{in} \cdot (A \oplus B)$$




Multibit Adders (CPAs)

 - Types of carry propagate adders (CPAs):
 - Ripple-carry (slow)
 - Carry-lookahead (fast)
 - Prefix (faster)
- Carry-lookahead and prefix adders faster for large adders but require more hardware



Ripple-Carry Adder

 - Chain 1-bit adders together
- Carry ripples through entire chain
- Disadvantage: **slow**



Ripple-Carry Adder Delay

$$t_{\text{ripple}} = Nt_{FA}$$

where t_{FA} is the delay of a 1-bit full adder



Carry-Lookahead Adder

Compute C_{out} for k -bit blocks using *generate* and *propagate* signals

Some definitions:

- Column i produces a carry out by either **generating** a carry out or **propagating** a carry in to the carry out
- Generate (G_i) and propagate (P_i) signals for each column:
 - **Generate:** Column i will generate a carry out if A_i and B_i are both 1.

$$G_i =$$

- **Propagate:** Column i will propagate a carry in to the carry out if A_i or B_i is 1.

$$P_i =$$

- **Carry out:** The carry out of column i (C_i) is:

$$C_i =$$



Block Propagate and Generate

Now use column Propagate and Generate signals to compute ***Block Propagate*** and ***Generate*** signals for k-bit blocks, i.e.:

- Compute if a k-bit group will **propagate** a carry in (to the block) to the carry out (of the block)
- Compute if a k-bit group will **generate** a carry out (of the block)



Block Propagate and Generate Signals

- **Example:** Block propagate and generate signals for 4-bit blocks ($P_{3:0}$ and $G_{3:0}$):

$$P_{3:0} = P_3 P_2 P_1 P_0$$

$$\begin{aligned} G_{3:0} &= G_3 + G_2 P_3 + G_1 P_2 P_3 + G_0 P_1 P_2 P_3 \\ &= G_3 + P_3 (G_2 + P_2 (G_1 + P_1 G_0)) \end{aligned}$$



Block Propagate and Generate Signals

- In general for a block spanning bits i through j ,



$$P_{i:j} = P_i P_{i-1} P_{i-2} \dots P_j$$

$$G_{i:j} = G_i + P_i (G_{i-1} + P_{i-1} (G_{i-2} + P_{i-2} \dots G_j))$$

$$C_i = G_{i:j} + P_{i:j} C_{j-1}$$



32-bit CLA with 4-bit Blocks

  

Carry-Lookahead Addition

- **Step 1:** Compute G_i and P_i for all columns
- **Step 2:** Compute G and P for k -bit blocks
- **Step 3:** C_{in} propagates through each k -bit propagate/generate logic (meanwhile computing sums)
- **Step 4:** Compute sum for most significant k -bit block



Carry-Lookahead Addition

- **Step 1:** Compute G_i and P_i for all columns

$$G_i = A_i B_i$$

$$P_i = A_i + B_i$$



Carry-Lookahead Addition

- **Step 1:** Compute G_i and P_i for all columns
- **Step 2:** Compute G and P for k -bit blocks


$$P_{3:0} = P_3 P_2 P_1 P_0$$

$$G_{3:0} = G_3 + P_3 (G_2 + P_2 (G_1 + P_1 G_0))$$




Carry-Lookahead Addition

 - **Step 1:** Compute G_i and P_i for all columns
- **Step 2:** Compute G and P for k -bit blocks
- **Step 3:** C_{in} propagates through each k -bit propagate/generate logic (meanwhile computing sums)



Carry-Lookahead Addition

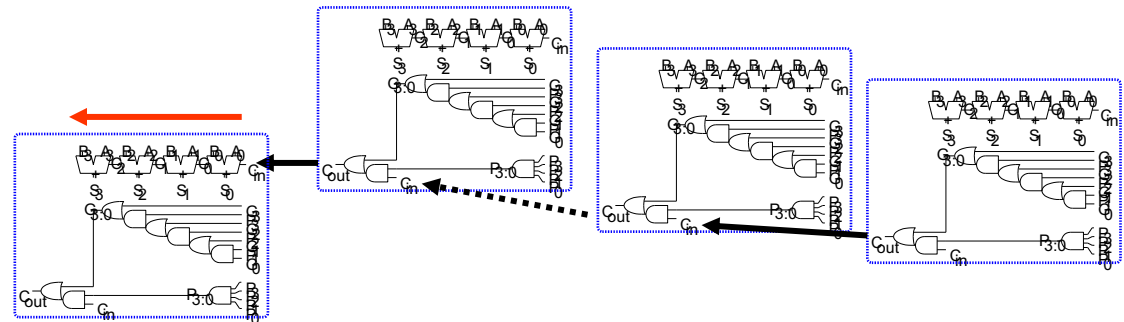- **Step 1:** Compute G_i and P_i for all columns
- **Step 2:** Compute G and P for k -bit blocks
- **Step 3:** C_{in} propagates through each k -bit propagate/generate logic (meanwhile computing sums)
- **Step 4:** Compute sum for most significant k -bit block



Carry-Lookahead Adder Delay

For N -bit CLA with k -bit blocks:

$$t_{CLA} = t_{pg} + t_{pg_block} + (N/k - 1)t_{AND_OR} + kt_{FA}$$

- t_{pg} : delay to generate all P_i, G_i
- t_{pg_block} : delay to generate all $P_{i:j}, G_{i:j}$
- t_{AND_OR} : delay from C_{in} to C_{out} of final AND/OR gate in k -bit CLA block

An N -bit carry-lookahead adder is generally much faster than a ripple-carry adder for $N > 16$



Prefix Adder

- Computes carry in (C_{i-1}) for each column, then computes sum:

$$S_i = (A_i \oplus B_i) \oplus C_{i-1}$$

- Computes G and P for 1-, 2-, 4-, 8-bit blocks, etc. until all G_i (carry in) known
- $\log_2 N$ stages



Prefix Adder

- Carry in either *generated* in a column or *propagated* from a previous column.
- Column -1 holds C_{in} , so

$$G_{-1} = C_{in}$$

- Carry in to column i = carry out of column $i-1$:

$$C_{i-1} = G_{i-1:-1}$$

$G_{i-1:-1}$: generate signal spanning columns $i-1$ to -1

- Sum equation:

$$S_i = (A_i \wedge B_i) \wedge G_{i-1:-1}$$

- **Goal:** Quickly compute $G_{0:-1}, G_{1:-1}, G_{2:-1}, G_{3:-1}, G_{4:-1}, G_{5:-1}, \dots$
(called *prefixes*) (= $C_0, C_1, C_2, C_3, C_4, C_5, \dots$)



Prefix Adder

- Generate and propagate signals for a block spanning bits $i:j$





$$G_{i:j} = G_{i:k} + P_{i:k} G_{k-1:j}$$

$$P_{i:j} = P_{i:k} P_{k-1:j}$$

- In words:
 - **Generate:** block $i:j$ will generate a carry if:
 - upper part ($i:k$) generates a carry or
 - upper part ($i:k$) propagates a carry generated in lower part ($k-1:j$)
 - **Propagate:** block $i:j$ will propagate a carry if *both* the upper and lower parts propagate the carry



16-Bit Prefix Adder Schematic

   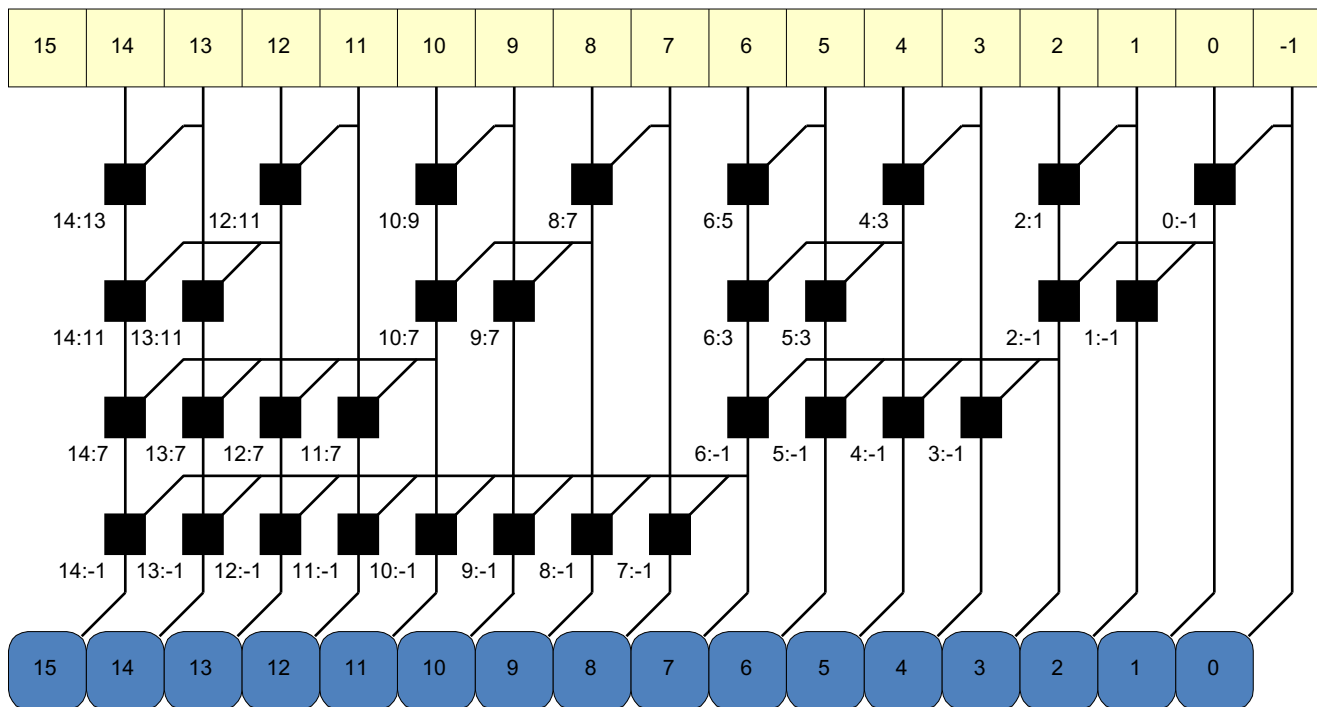

Prefix Adder Delay

$$t_{PA} = t_{pg} + \log_2 N (t_{pg_prefix}) + t_{XOR}$$

t_{pg} : delay to produce P_i, G_i (AND or OR gate)

t_{pg_prefix} : delay of black prefix cell (AND-OR gate)



Adder Delay Comparisons

Compare delay of: 32-bit ripple-carry, CLA, and prefix adders

- CLA has 4-bit blocks
- 2-input gate delay = 10 ps; full adder delay = 30 ps

$$\begin{aligned}t_{\text{ripple}} &= Nt_{FA} = 32(30 \text{ ps}) \\ &= \mathbf{960 \text{ ps}}\end{aligned}$$


$$\begin{aligned}t_{CLA} &= t_{pg} + t_{pg_block} + (N/k - 1)t_{AND_OR} + kt_{FA} \\ &= [10 + 60 + (7)20 + 4(30)] \text{ ps} \\ &= \mathbf{330 \text{ ps}}\end{aligned}$$

$$\begin{aligned}t_{PA} &= t_{pg} + \log_2 N(t_{pg_prefix}) + t_{XOR} \\ &= [10 + \log_2 32(20) + 10] \text{ ps} \\ &= \mathbf{120 \text{ ps}}\end{aligned}$$



Subtractor

Symbol

 

Implementation


A B

Y



Comparator: Equality

Symbol

 

Implementation

A_3

B_3

A_2

B_2

A_1

B_1


A_0

B_0

Equal



Comparator: Less Than

 

ALU: Arithmetic Logic Unit


ALU should perform:

- Addition
- Subtraction
- AND
- OR



ALU: Arithmetic Logic Unit

ALUControl _{1:0}	Function
00	Add
01	Subtract
10	AND
11	OR

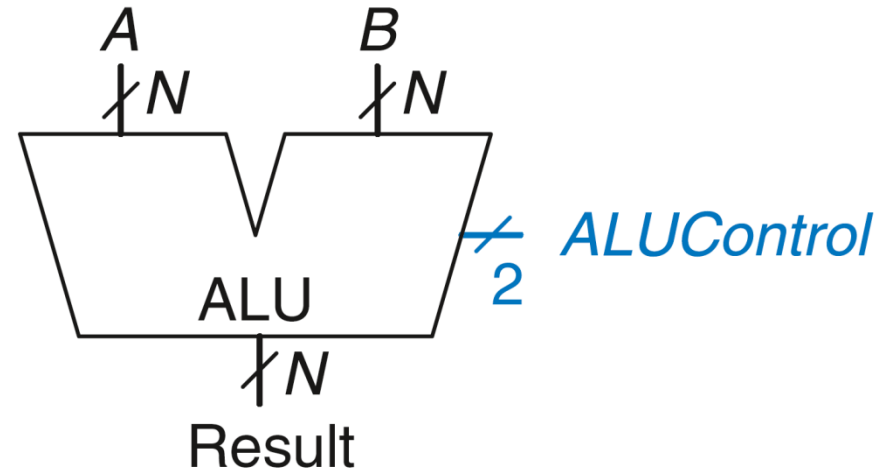

Example: Perform $A + B$

$ALUControl = 00$


$Result = A + B$



ALU: Arithmetic Logic Unit

ALUControl _{1:0}	Function
00	Add
01	Subtract
10	AND
11	OR

Example: Perform A OR B

 

ALU: Arithmetic Logic Unit


ALUControl _{1:0}	Function
00	Add
01	Subtract
10	AND
11	OR

Example: Perform $A \text{ OR } B$

$ALUControl_{1:0} = 11$

Mux selects output of OR gate as *Result*, so


Result = $A \text{ OR } B$

 

ALU: Arithmetic Logic Unit

ALUControl _{1:0}	Function
00	Add
01	Subtract
10	AND
11	OR

Example: Perform $A + B$

 

ALU: Arithmetic Logic Unit

ALUControl _{1:0}	Function
00	Add
01	Subtract
10	AND
11	OR

Example: Perform $A + B$

$ALUControl_{1:0} = 00$


$ALUControl_0 = 0$, so:

C_{in} to adder = 0

2nd input to adder is B


Mux selects *Sum* as *Result*, so

$Result = A + B$

 


ALU with Status Flags


Flag	Description
<i>N</i>	Result is N egative
<i>Z</i>	Result is Z ero
<i>C</i>	Adder produces C arry out
<i>V</i>	Adder o verflowed

 

ALU with Status Flags

 

ALU with Status Flags: **N**egative

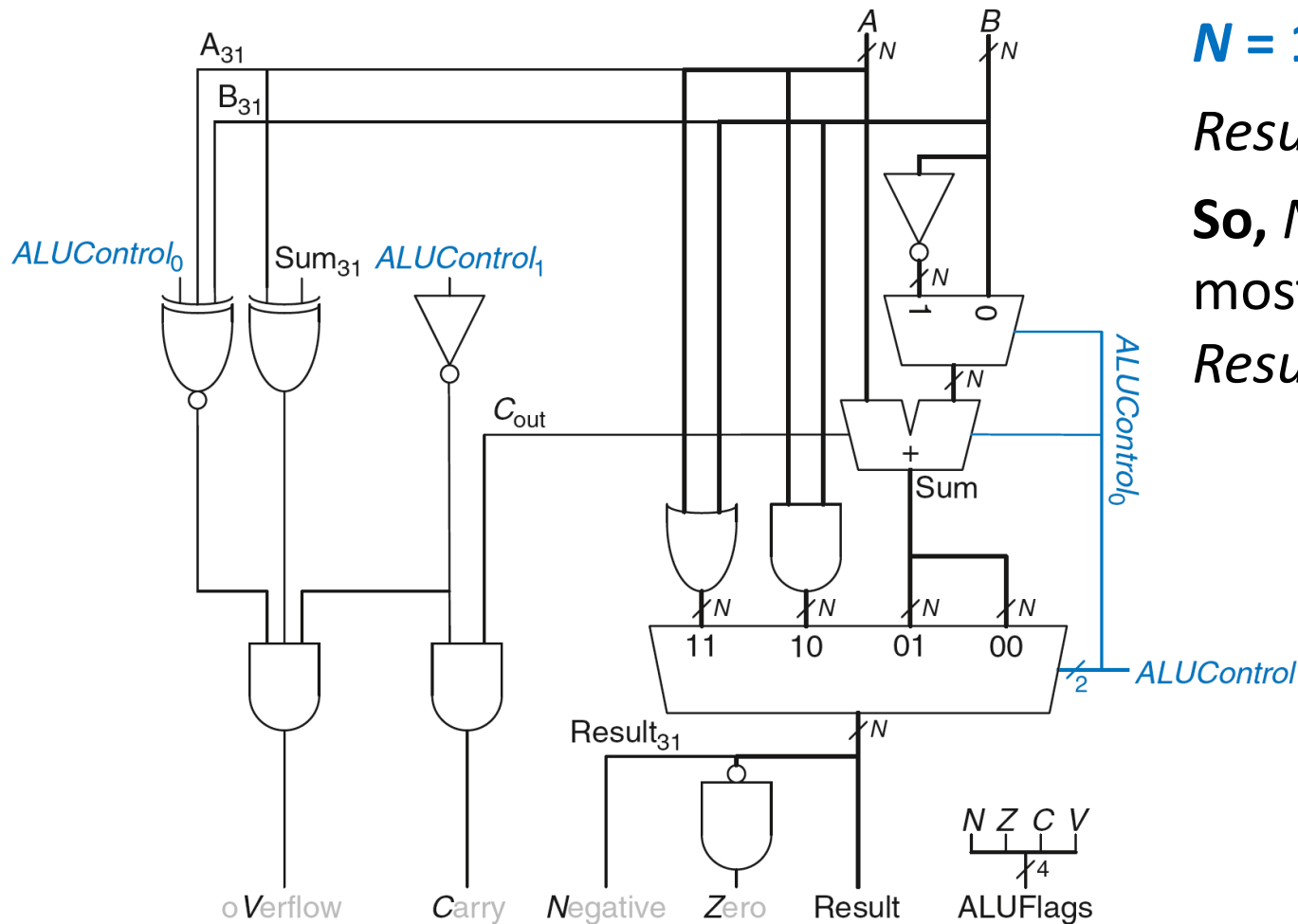

N = 1 if:

Result is negative


So, N is connected to most significant bit of *Result*



ALU with Status Flags: **Z**ero

Z = 1 if:

all of the bits of *Result*
are 0

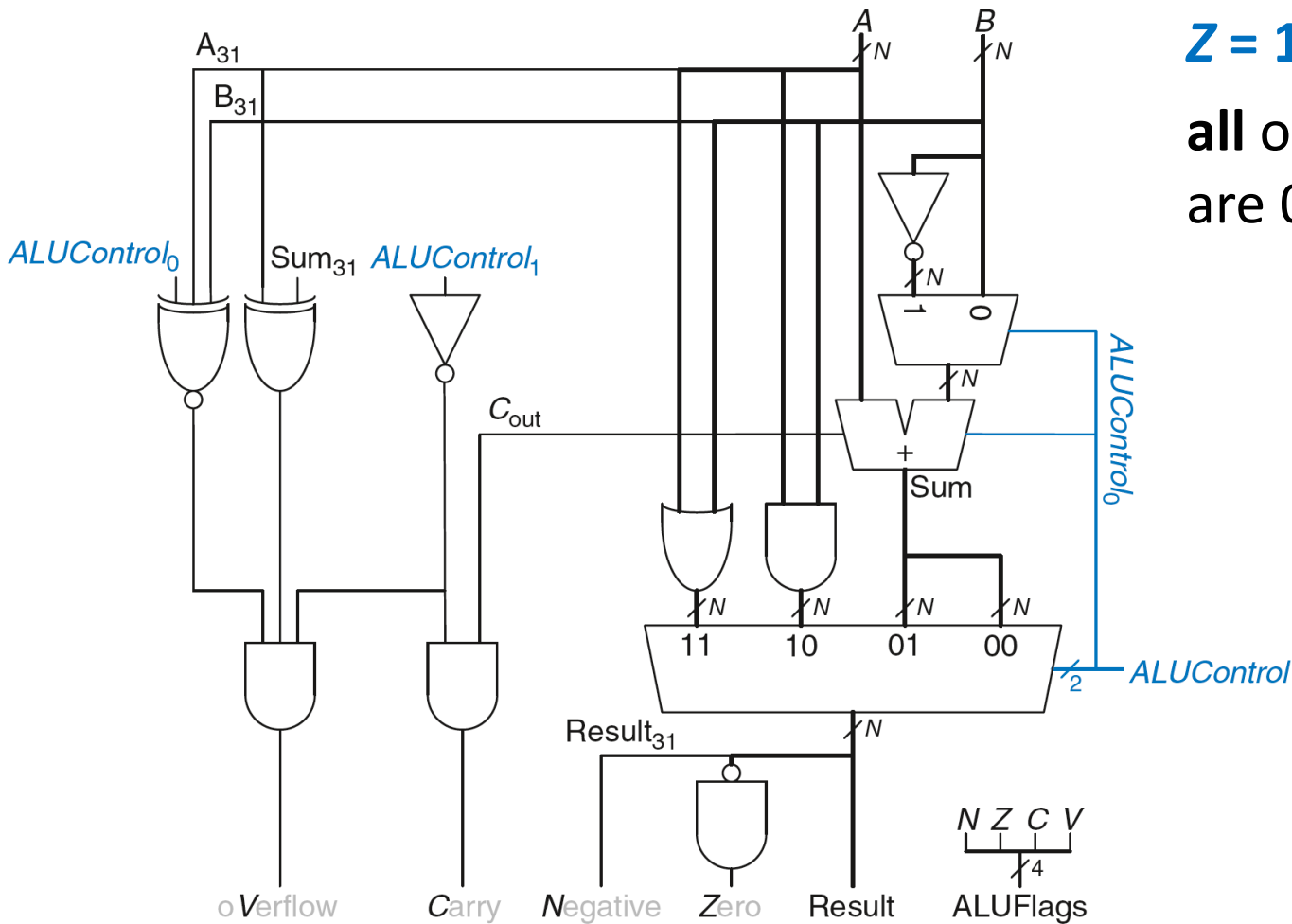


ALU with Status Flags: Carry

C = 1 if:

C_{out} of Adder is 1

AND

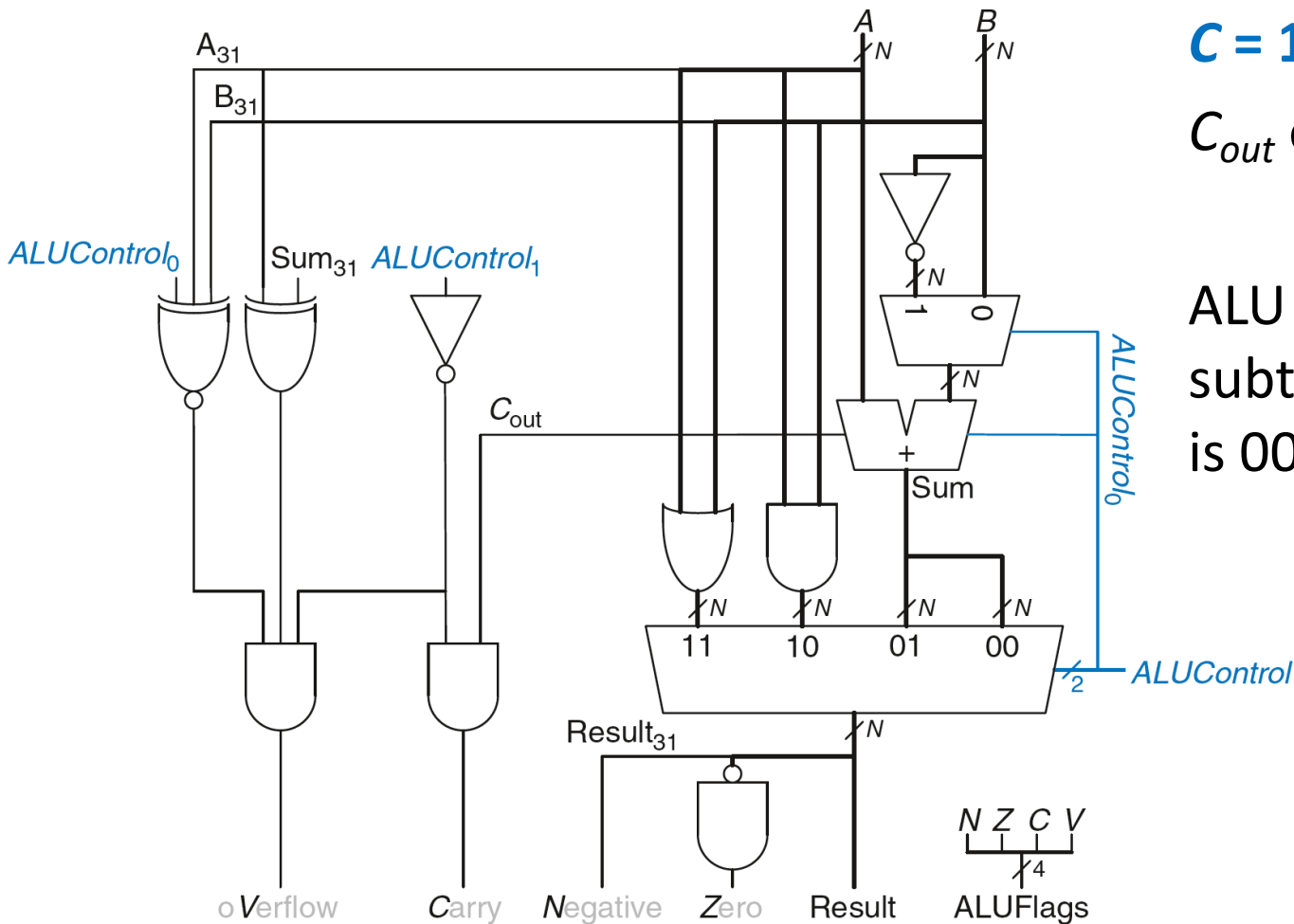
ALU is adding or subtracting (ALUControl is 00 or 01)




ALU with Status Flags: overflow

$V = 1$ if:

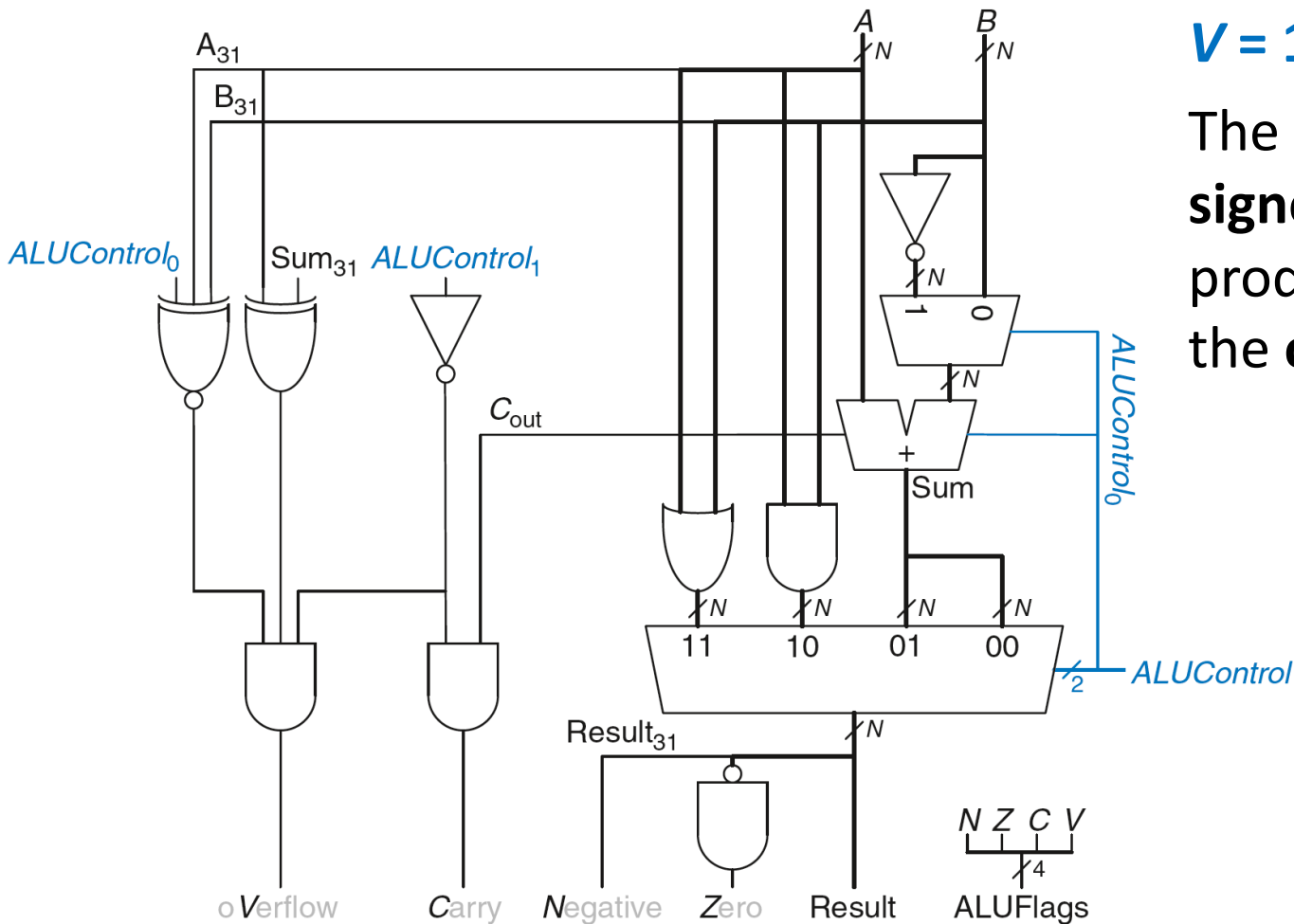The addition of 2 **same-signed numbers** produces a result with the **opposite sign**



ALU with Status Flags: overflow

 


$V = 1$ if:

ALU is performing addition or subtraction
($ALUControl_1 = 0$)



ALU with Status Flags: oVerflow

 

$V = 1$ if:


ALU is performing addition or subtraction
($ALUControl_1 = 0$)

AND

A and Sum have opposite signs



ALU with Status Flags: overflow

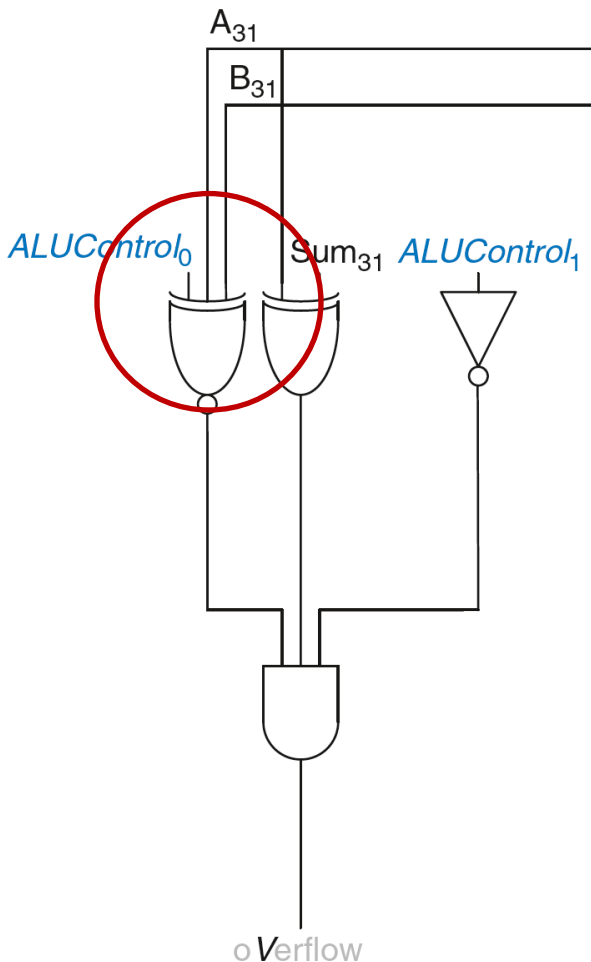

V = 1 if:

ALU is performing addition or subtraction
($ALUControl_1 = 0$)

AND

A and Sum have opposite signs


AND

A and B have same signs upon addition **OR**

A and B have different signs upon subtraction



ALU with Status Flags: overflow

 

V = 1 if:

ALU is performing addition or subtraction
($ALUControl_1 = 0$)

AND

A and Sum have opposite signs

AND

A and B have same signs upon addition
($ALUControl_0 = 0$)

OR

A and B have different signs upon subtraction
($ALUControl_0 = 1$)

