

E85: Digital Design and Computer Architecture

Lab 11: Multicycle Processor

Objective

In this lab, you will complete a multicycle ARM processor. You will need the working processor for your final exam.

1. Multicycle ARM Processor

Figure 7.30 of the textbook shows the complete multicycle processor. Write a hierarchical Verilog description of the processor. The processor should have the following module declaration. The memory signals are tapped out for testing purposes. Use your controller from Lab 10 and any Verilog building blocks you need from Section 7.6.2.

```
module top(input logic      clk, reset,
           output logic [31:0] WriteData, Adr,
           output logic      MemWrite);
```

2. Test Bench

The arm_testbench.sv and test code (in assembly and machine language) are on the class web page. Note that the test code has been enhanced somewhat beyond what is in Figure 7.60. Your memory should read the test code from the memory file at startup with the line:

```
initial $readmemh("memfile.dat", RAM);
```

Generate simulation waveforms at least for clk, reset, PC, Instr, state, SrcA, SrcB, ALUResult, Adr, WriteData, and MemWrite. Display the 32-bit signals in hexadecimal for ease of reading. You may wish to add other signals to help debug. Fix any problems you may find until your code executes the program as expected and the testbench reports success.

What to Turn In

1. Please indicate how many hours you spent on this lab. This will be helpful for calibrating the workload for next time the course is taught.
2. Hierarchical SystemVerilog for your top-level processor module (and submodules) matching the declaration given above.
3. Simulation waveforms (in this order) at least for the specified signals. Does your system pass your testbench?

If you have suggestions for further improvements of this lab, you're welcome to include them at the end of your lab.