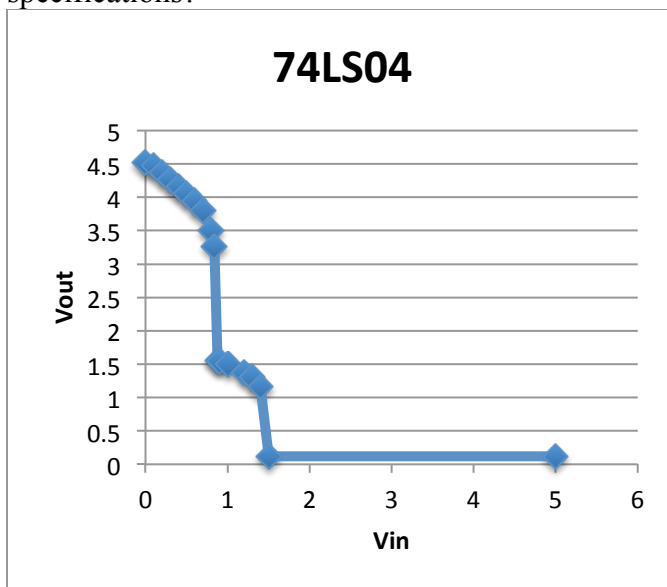



E85: Digital Design and Computer Architecture

Problem Set 2

- 1) The voltage transfer characteristics below are measured for a 74LS04 operating at 5V. Determine V_{IL} , V_{IH} , V_{OL} , V_{OH} , and the high and low noise margins. Compare your results to the 74LS specification in Table eA.2 of the textbook. Are they within the specifications?



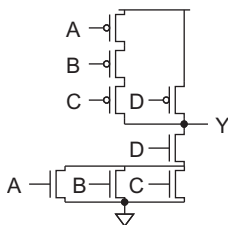- 2) Referring to the logic level specifications in Tables eA.2 and eA.3 of the textbook:
- What could go wrong if a 74LS04 inverter drives a 74HC08 AND gate?
 - In light of your answer to Part (a), why does the HCT family exist?
 - Can a 3.3V 74LVC32 gate reliably drive a 5V 74HC00?
 - Can a 3.3V 74LVC32 gate reliably drive a 5V 74HCT00?
 - Can a 74HC00 reliably drive a 3.3V 74LVC32?
- 3) Sketch a transistor-level implementation of a 3-input NAND gate.
- 4) Give the Boolean equation performed by the following gate.




- 5) Give a minimal sum of products Boolean equation for the following function. Show how to implement the function with logic gates and in Verilog.

A	B	C	Y
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	0

- 6) Give a minimal sum of products Boolean equation for the following function. Show how to implement the function with logic gates and in Verilog.

$$Y = \overline{AB} + \overline{BCD}$$

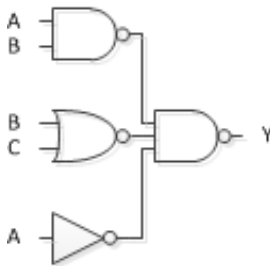- 7) Give the minimal sum-of-products equation for the following circuit.



- 8) Impact on Society: Integrated circuits have been following Moore's Law since 1965, with cost per transistor reducing approximately 30% per year. This progress is slowing as nanometer lithography is becoming extremely expensive. Supposing cost reduction grinds to a halt by 2020, write a thoughtful paragraph predicting a significant impact on society caused by the end of Moore's Law.
- 9) How long did you spend on this problem set? This will not count toward your grade but will help calibrate the workload.