


# Lecture 20: CAMs, ROMs, PLAs

# Outline

- ❑ Content-Addressable Memories
- ❑ Read-Only Memories
- ❑ Programmable Logic Arrays


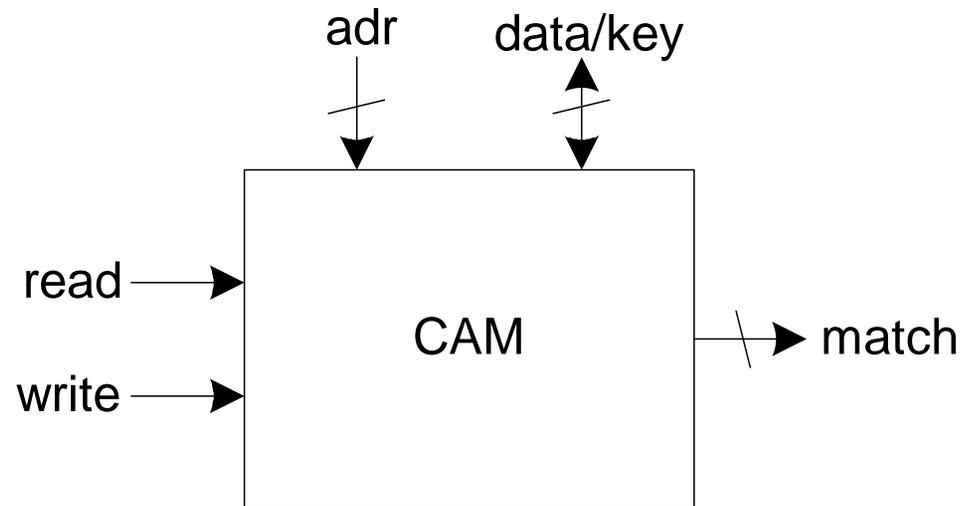
# CAMs

- ❑ Extension of ordinary memory (e.g. SRAM)
  - Read and write memory as usual
  - Also *match* to see which words contain a *key*


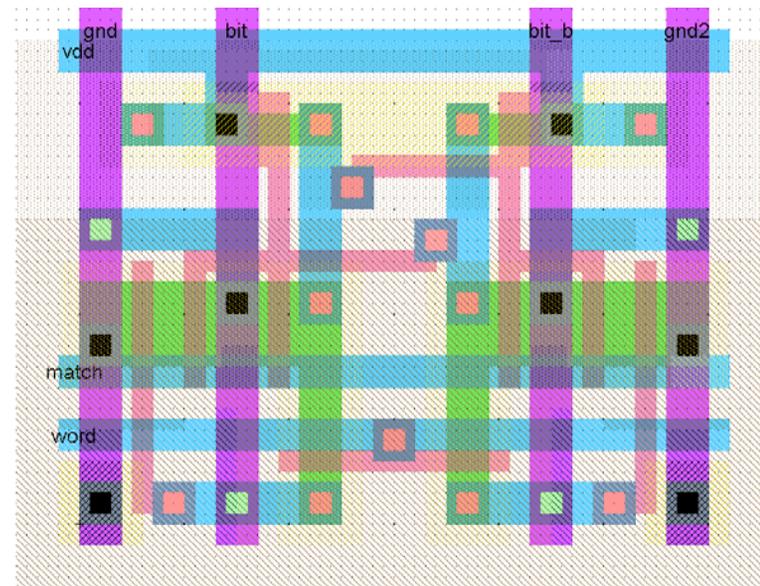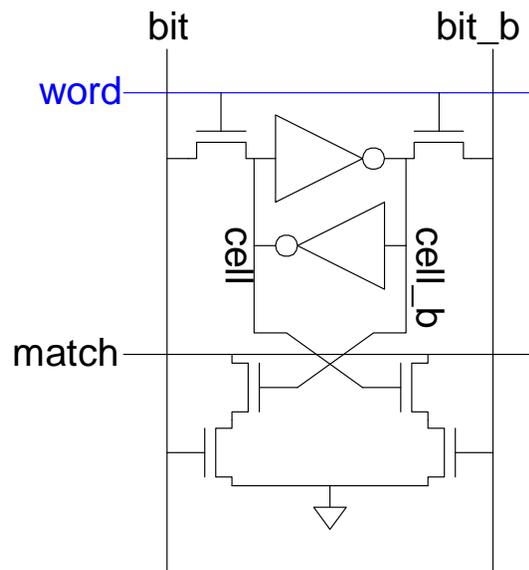
# 10T CAM Cell

- Add four match transistors to 6T SRAM
  - 56 x 43  $\lambda$  unit cell



# CAM Cell Operation


- ❑ Read and write like ordinary SRAM

- ❑ For matching:

- Leave wordline low
- Precharge matchlines
- Place key on bitlines
- Matchlines evaluate

- ❑ Miss line

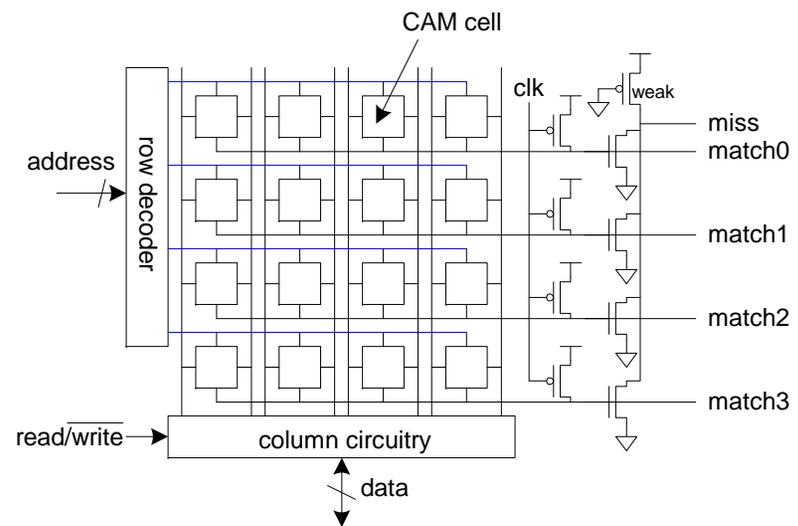- Pseudo-nMOS NOR of match lines
- Goes high if no words match



# Read-Only Memories

- ❑ Read-Only Memories are nonvolatile
  - Retain their contents when power is removed
- ❑ Mask-programmed ROMs use one transistor per bit
  - Presence or absence determines 1 or 0

# ROM Example

## 4-word x 6-bit ROM



- Represented with dot diagram
- Dots indicate 1's in ROM

Word 0: 010101

Word 1: 011001

Word 2: 100101


Word 3: 101010

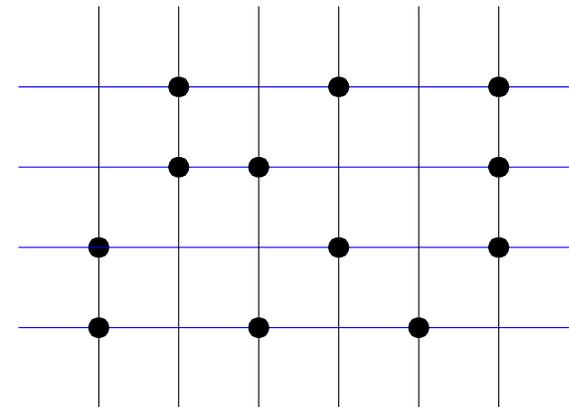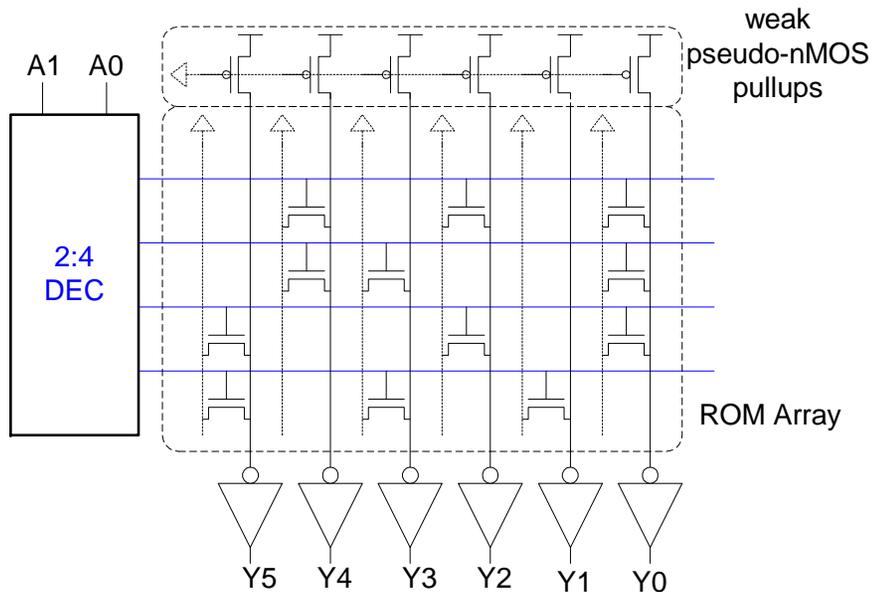

Looks like 6 4-input pseudo-nMOS NORs

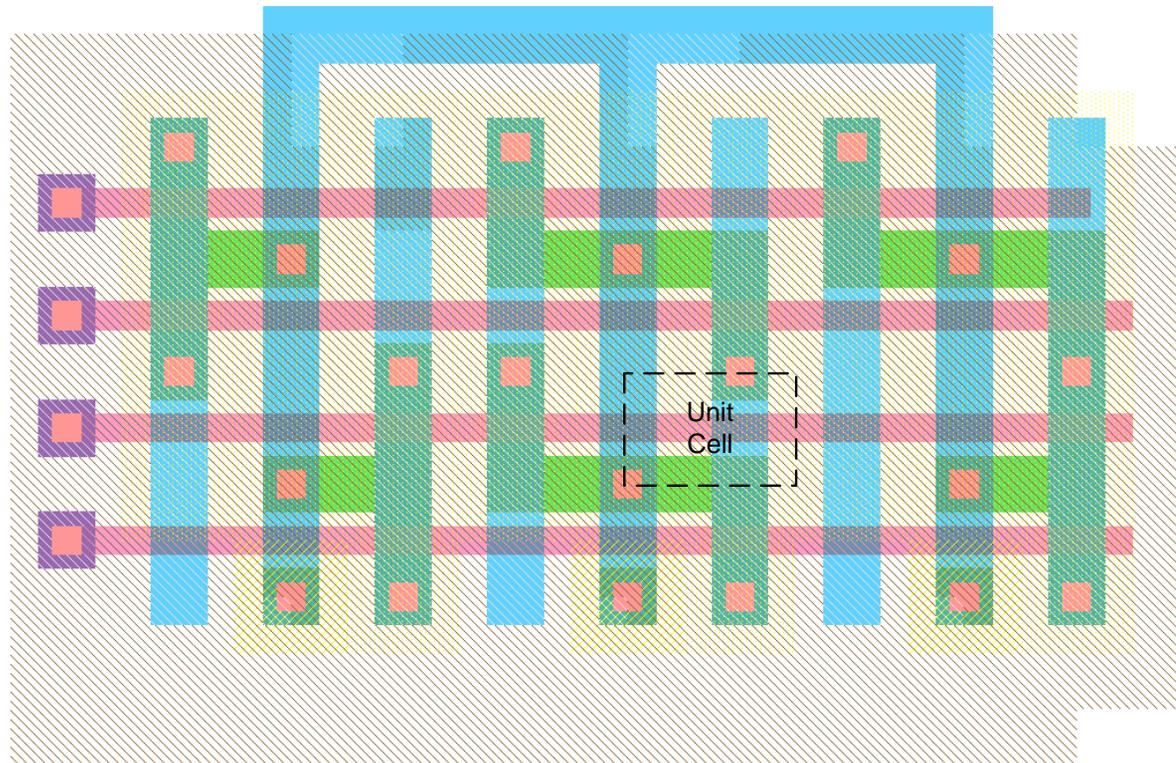
# ROM Array Layout

- Unit cell is  $12 \times 8 \lambda$  (about 1/10 size of SRAM)



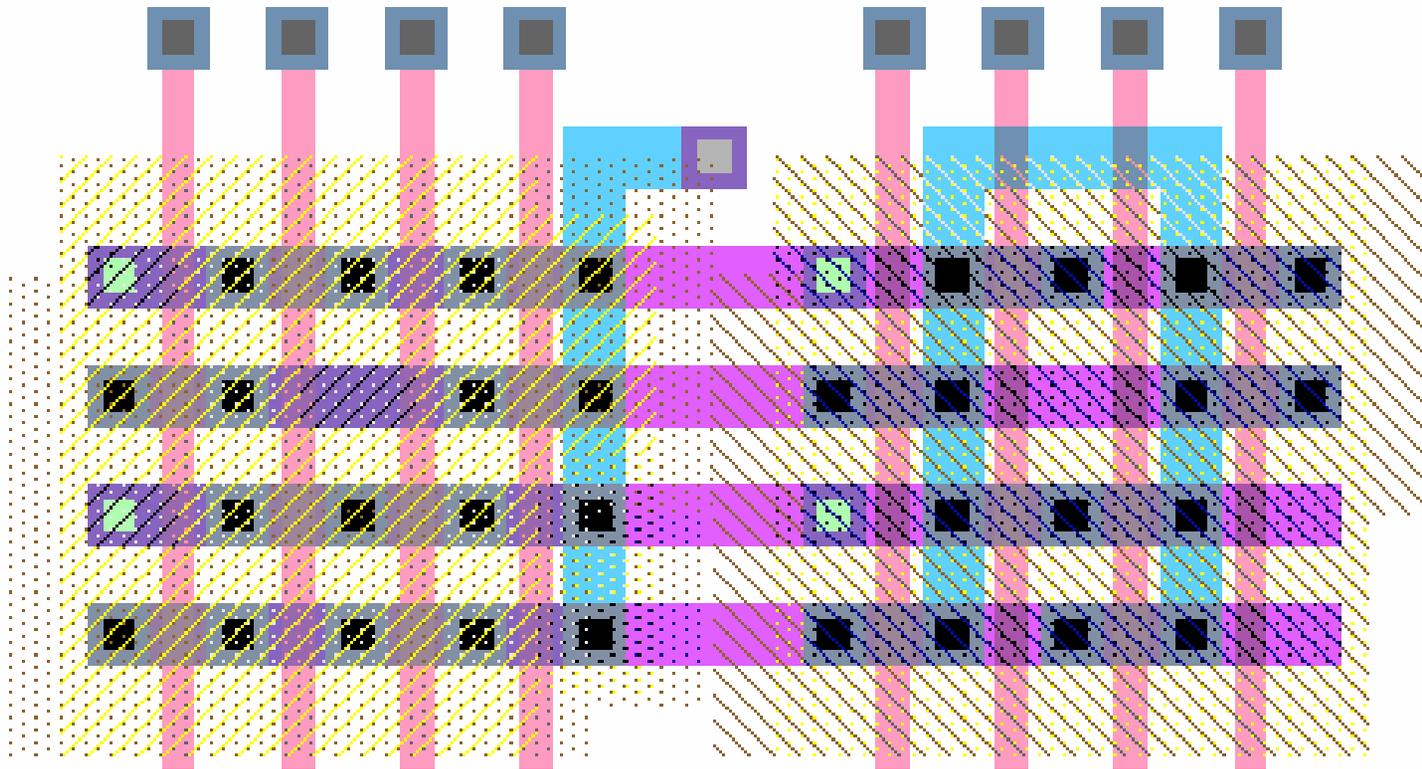
# Row Decoders

- ❑ ROM row decoders must pitch-match with ROM
  - Only a single track per word!




# Complete ROM Layout

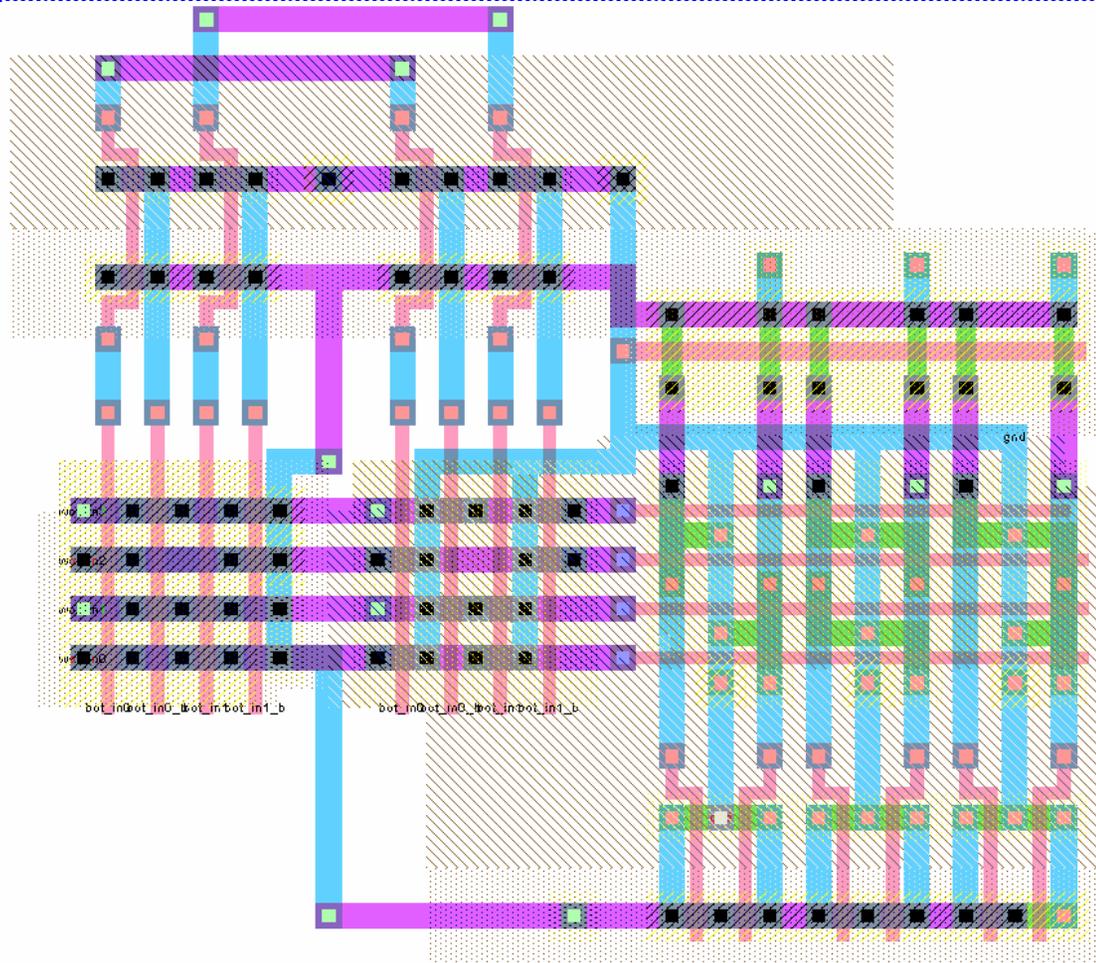

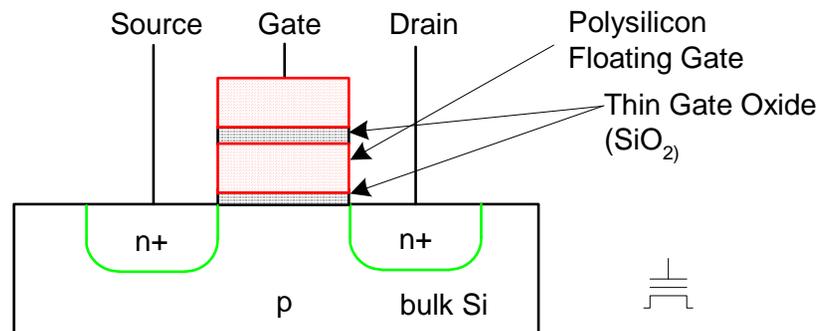
# PROMs and EPROMs

- ❑ Programmable ROMs
  - Build array with transistors at every site
  - Burn out fuses to disable unwanted transistors
- ❑ Electrically Programmable ROMs
  - Use floating gate to turn off unwanted transistors
  - EPROM, EEPROM, Flash



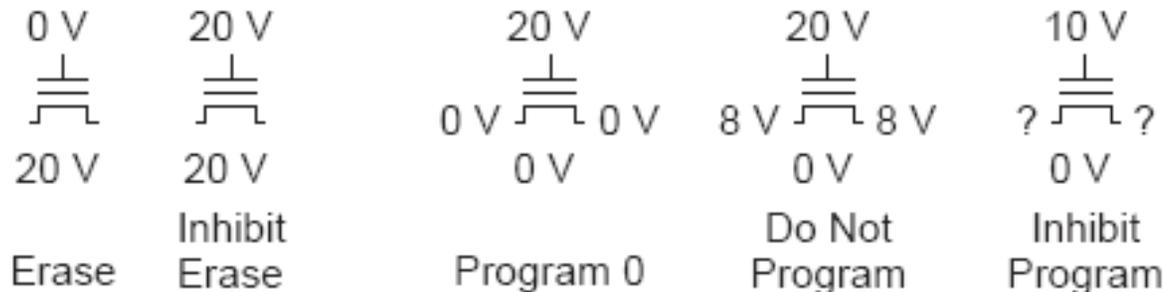
# Flash Programming

- ❑ Charge on floating gate determines  $V_t$
- ❑ Logic 1: negative  $V_t$
- ❑ Logic 0: positive  $V_t$
- ❑ Cells erased to 1 by applying a high body voltage so that electrons tunnel off floating gate into substrate
- ❑ Programmed to 0 by applying high gate voltage


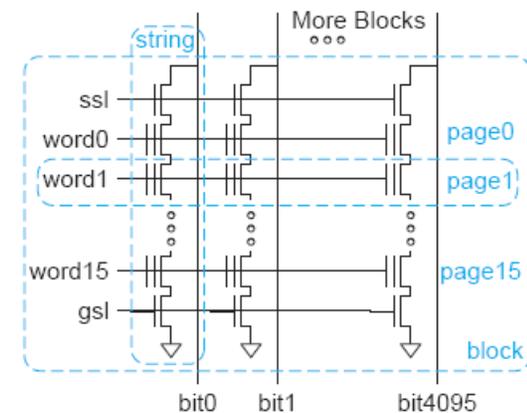
# NAND Flash

- ❑ High density, low cost / bit
  - Programmed one page at a time
  - Erased one block at a time
- ❑ Example:
  - 4096-bit pages
  - 16 pages / 8 KB block
  - Many blocks / memory



# 64 Gb NAND Flash



- ❑ 64K cells / page
- ❑ 4 bits / cell (multiple  $V_t$ )
- ❑ 64 cells / string
  - 256 pages / block
- ❑ 2K blocks / plane
- ❑ 2 planes



[Trinh09]
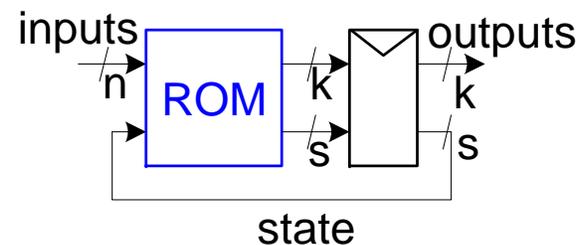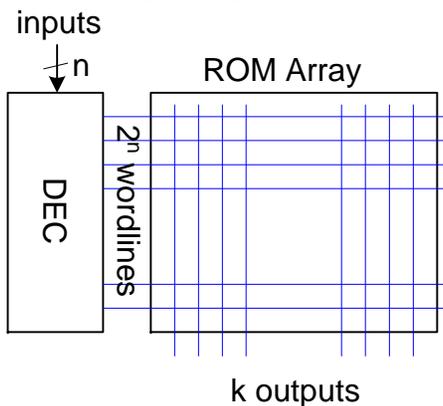
# Building Logic with ROMs

- ❑ Use ROM as lookup table containing truth table
  - $n$  inputs,  $k$  outputs requires  $2^n$  words x  $k$  bits
  - Changing function is easy – reprogram ROM
- ❑ Finite State Machine
  - $n$  inputs,  $k$  outputs,  $s$  bits of state
  - Build with  $2^n$  bit ROM and  $s$  bit reg



# Example: RoboAnt

Let's build an Ant


**Sensors:** Antennae

(L,R) – 1 when in contact

**Actuators:** Legs


Forward step F

Ten degree turns TL, TR

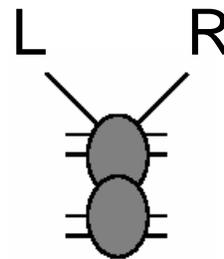


**Goal:** make our ant smart enough to get out of a maze

**Strategy:** keep right antenna on wall

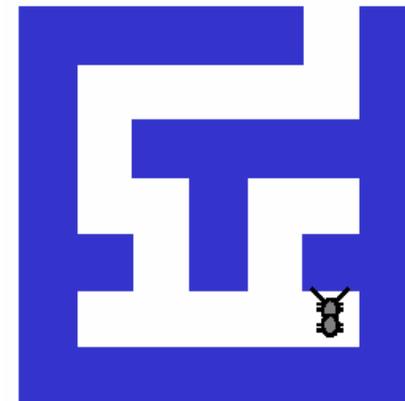


(RoboAnt adapted from MIT 6.004 2002 OpenCourseWare by Ward and Terman)


# Lost in space

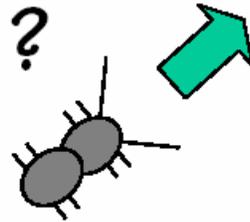

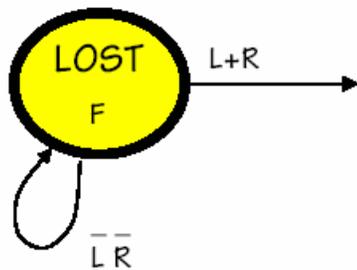
- ❑ Action: go forward until we hit something
  - Initial state




# Bonk!!!

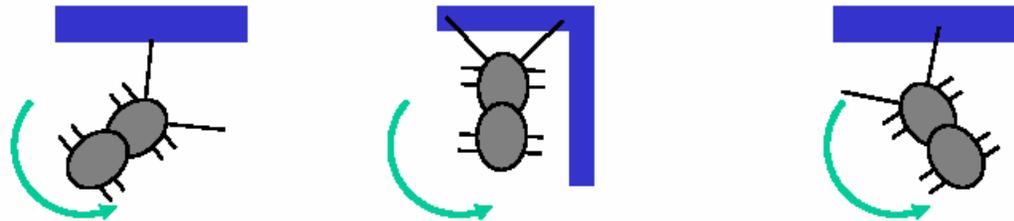

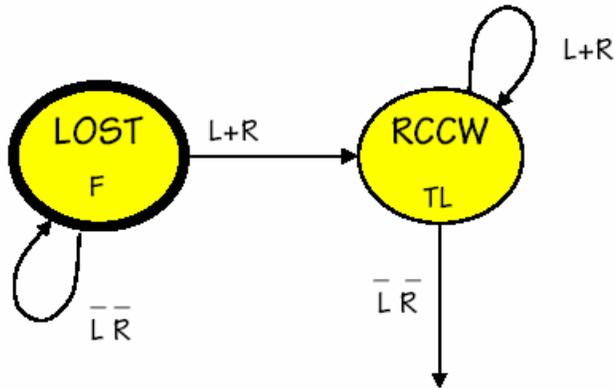
- Action: turn left (rotate counterclockwise)
  - Until we don't touch anymore




# A little to the right

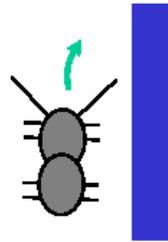

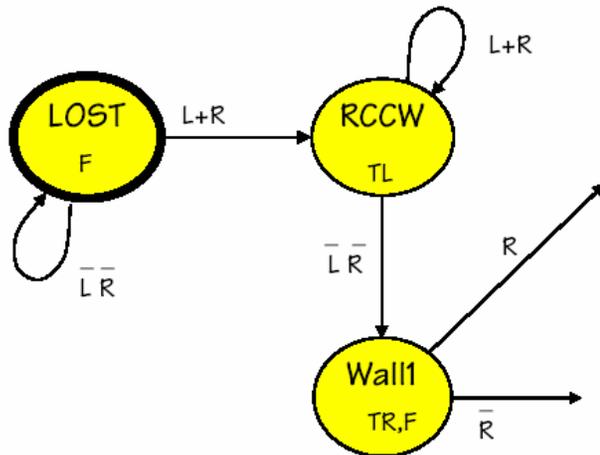
- Action: step forward and turn right a little
  - Looking for wall




# Then a little to the left

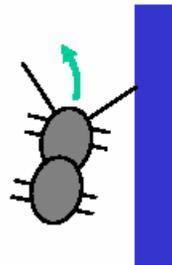

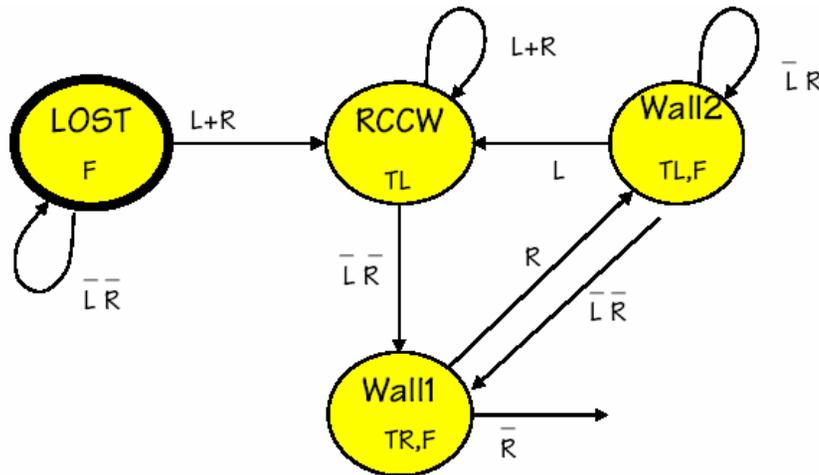
- Action: step and turn left a little, until not touching



# Whoops - a corner!

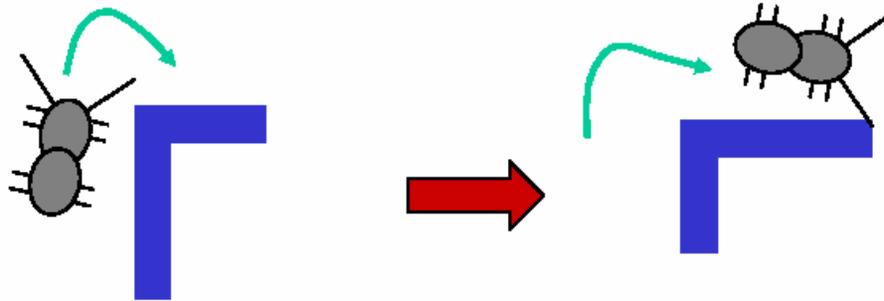


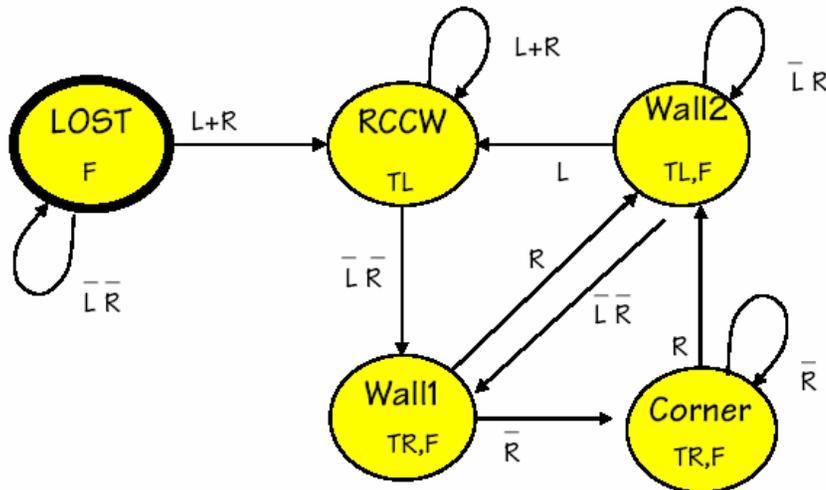- Action: step and turn right until hitting next wall



# Simplification

- Merge equivalent states where possible


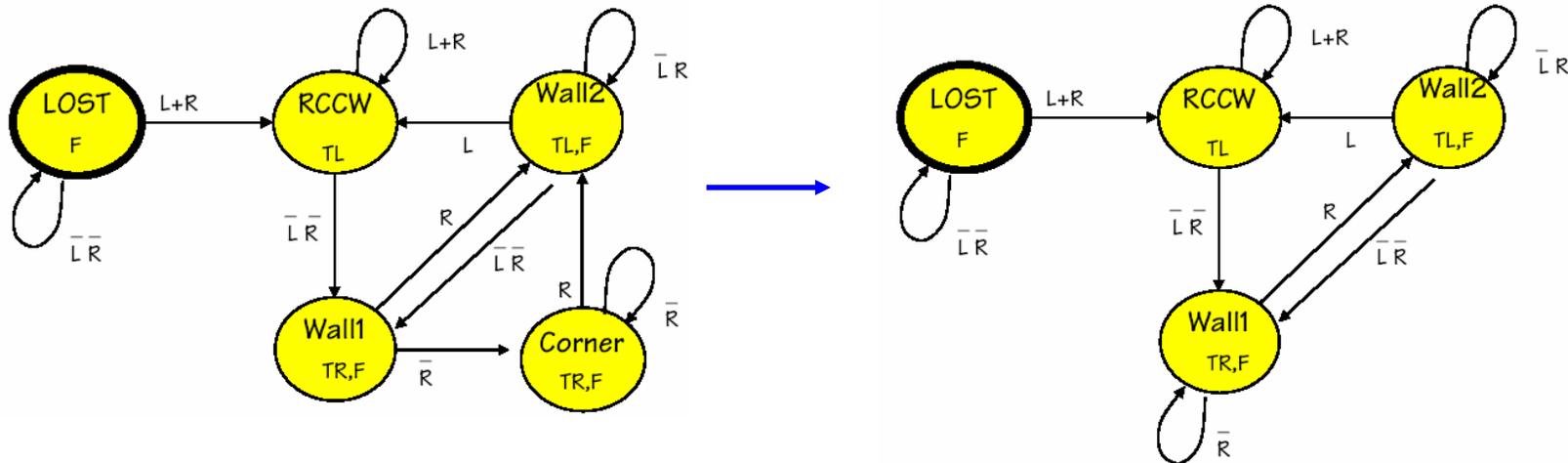


# State Transition Table

	$S_{1:0}$	L	R	$S_{1:0}'$	TR	TL	F
Lost	00	0	0	00	0	0	1
	00	1	X	01	0	0	1
	00	0	1	01	0	0	1
RCCW	01	1	X	01	0	1	0
	01	0	1	01	0	1	0
	01	0	0	10	0	1	0
Wall1	10	X	0	10	1	0	1
	10	X	1	11	1	0	1
Wall2	11	1	X	01	0	1	1
	11	0	0	10	0	1	1
	11	0	1	11	0	1	1



# ROM Implementation

## 16-word x 5 bit ROM

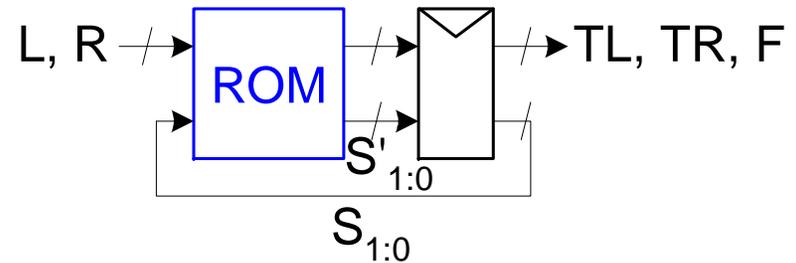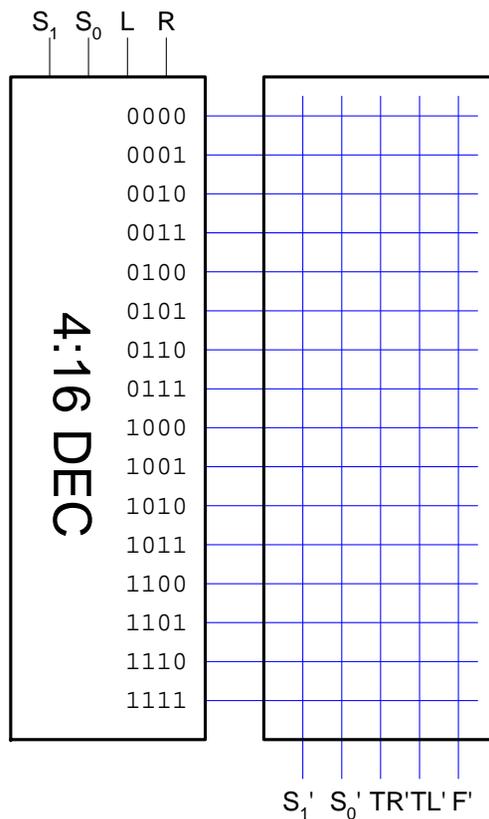

# ROM Implementation

## 16-word x 5 bit ROM

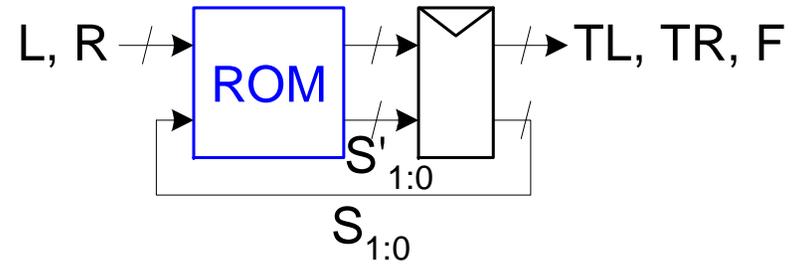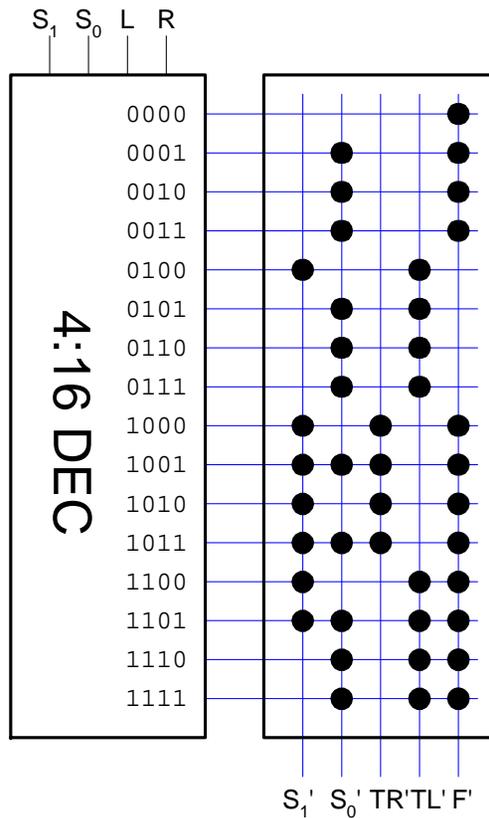


# PLAs

- ❑ A *Programmable Logic Array* performs any function in sum-of-products form.
- ❑ *Literals*: inputs & complements
- ❑ *Products / Minterms*: AND of literals
- ❑ *Outputs*: OR of Minterms
- ❑ Example: Full Adder


$$s = \bar{a}\bar{b}\bar{c} + \bar{a}b\bar{c} + \bar{a}bc + abc$$

$$c_{out} = ab + bc + ac$$


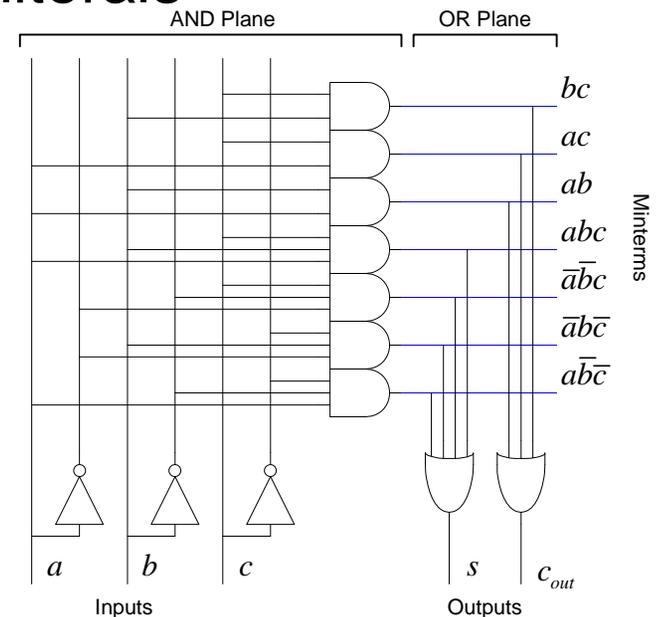

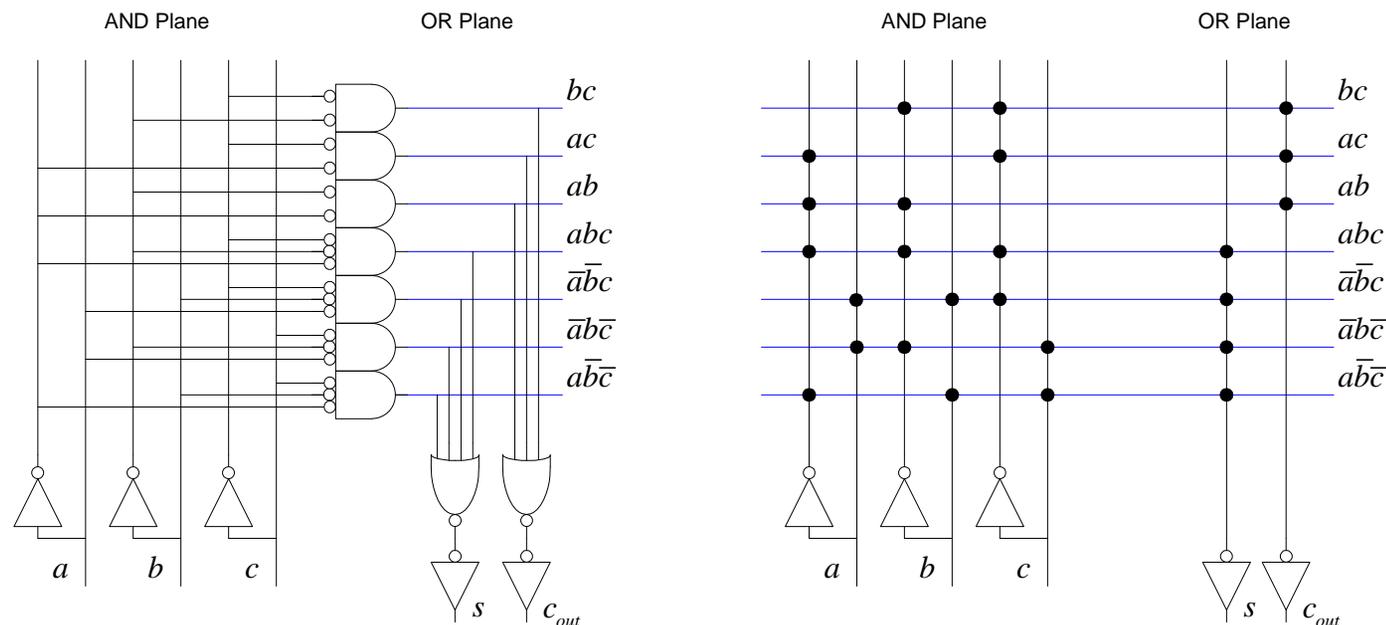
# NOR-NOR PLAs

- ❑ ANDs and ORs are not very efficient in CMOS
- ❑ Dynamic or Pseudo-nMOS NORs are very efficient
- ❑ Use DeMorgan's Law to convert to all NORs



# PLA Schematic & Layout

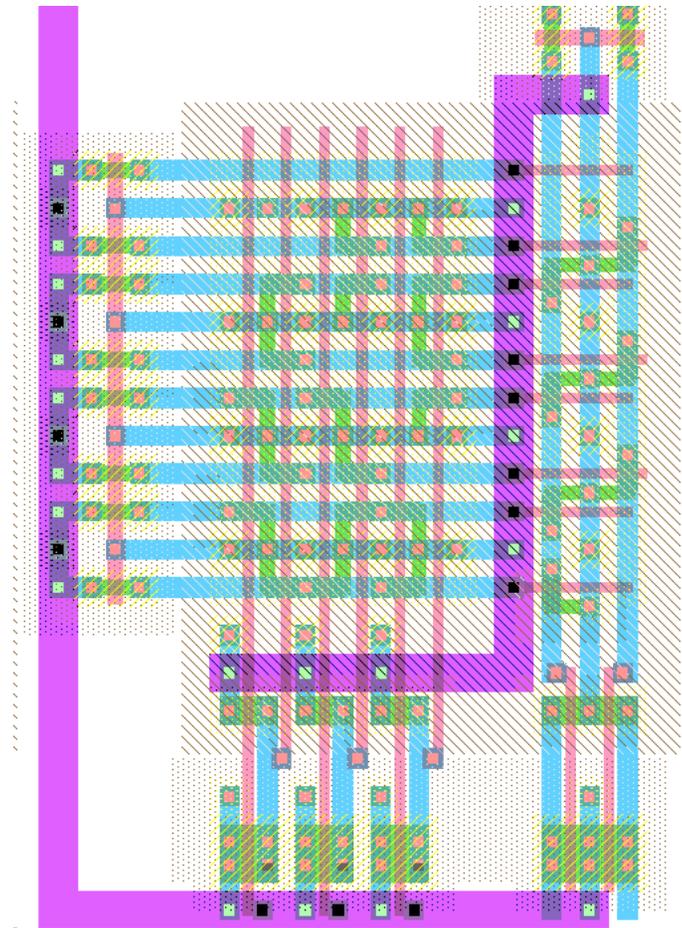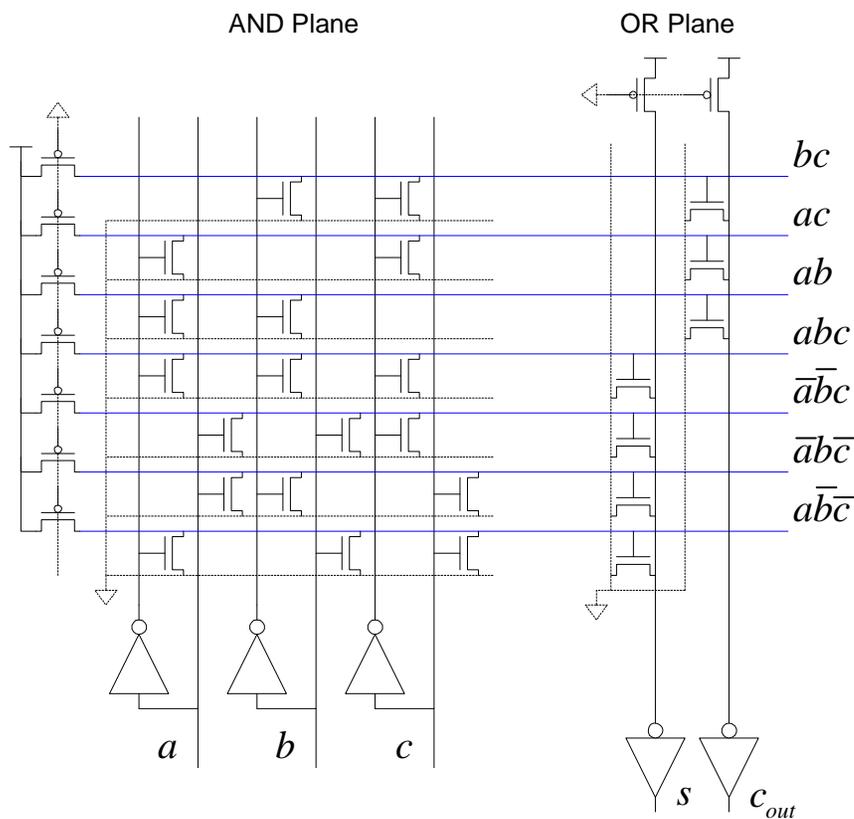

# PLAs vs. ROMs

- ❑ The OR plane of the PLA is like the ROM array
- ❑ The AND plane of the PLA is like the ROM decoder
- ❑ PLAs are more flexible than ROMs
  - No need to have  $2^n$  rows for  $n$  inputs
  - Only generate the minterms that are needed
  - Take advantage of logic simplification

# Example: RoboAnt PLA

□ Convert state transition table to logic equations

$S_{1:0}$	L	R	$S_{1:0}'$	TR	TL	F
00	0	0	00	0	0	1
00	1	X	01	0	0	1
00	0	1	01	0	0	1
01	1	X	01	0	1	0
01	0	1	01	0	1	0
01	0	0	10	0	1	0
10	X	0	10	1	0	1
10	X	1	11	1	0	1
11	1	X	01	0	1	1
11	0	0	10	0	1	1
11	0	1	11	0	1	1

$$\begin{array}{r}
 S_1' \\
 \begin{array}{cccc}
 & & S_1 S_0 & \\
 & 00 & 01 & 11 & 10 \\
 00 & 0 & 1 & 1 & 1 \\
 LR & 01 & 0 & 0 & 1 & 1 \\
 & 11 & 0 & 0 & 0 & 1 \\
 & 10 & 0 & 0 & 0 & 1
 \end{array} \\
 S_1' = S_1 \overline{S_0} + \overline{L} S_1 + \overline{L} R S_0
 \end{array}$$

$$\begin{array}{r}
 S_0' \\
 \begin{array}{cccc}
 & & S_1 S_0 & \\
 & 00 & 01 & 11 & 10 \\
 00 & 0 & 0 & 0 & 0 \\
 LR & 01 & 1 & 1 & 1 & 1 \\
 & 11 & 1 & 1 & 1 & 1 \\
 & 10 & 1 & 1 & 1 & 0
 \end{array} \\
 S_0' = R + \overline{L} S_1 + L S_0 \\
 TR = S_1 \overline{S_0} \\
 TL = S_0 \\
 F = S_1 + \overline{S_0}
 \end{array}$$

# RoboAnt Dot Diagram

$$S1' = S_1 \bar{S}_0 + \bar{L} S_1 + \bar{L} \bar{R} S_0$$

$$S0' = R + L \bar{S}_1 + L S_0$$

$$TR = S_1 \bar{S}_0$$

$$TL = S_0$$

$$F = S_1 + \bar{S}_0$$

