

Sequential Design


E155

Outline


- ❑ Sequential design
- ❑ Dynamic discipline
- ❑ Metastability
- ❑ Synchronizer

Sequencing

 - ❑ *Combinational logic*
 - output depends on current inputs
- ❑ *Sequential logic*
 - output depends on current and previous inputs
 - Requires separating previous, current, future
 - Called *state* or *tokens*
 - Ex: FSM, pipeline



Finite State Machine

 


Pipeline

Sequencing Overhead

- ❑ Use flip-flops to delay fast tokens so they move through exactly one stage each cycle.
- ❑ Inevitably adds some delay to the slow tokens
- ❑ Makes circuit slower than just the logic delay
 - Called sequencing overhead
- ❑ Some people call this clocking overhead
 - But it applies to asynchronous circuits too
 - Inevitable side effect of maintaining sequence

Sequencing Elements

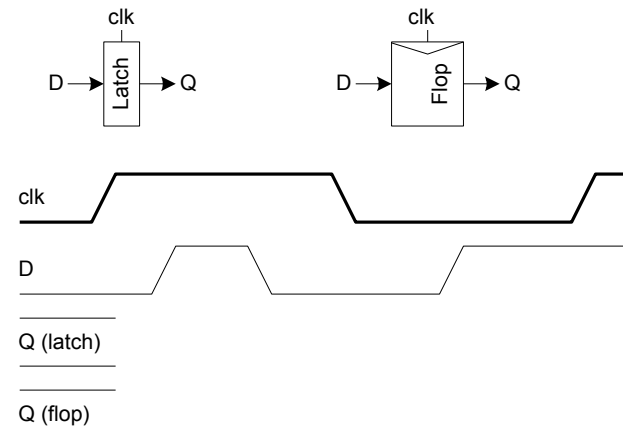- ❑ **Latch:** Level sensitive
 - a.k.a. transparent latch, D latch
- ❑ **Flip-flop:** edge triggered
 - A.k.a. master-slave flip-flop, D flip-flop, D register
- ❑ **Timing Diagrams**
 - Transparent
 - Opaque
 - Edge-trigger



Latch Design

- ❑ Pass Transistor Latch

- ❑ Pros

 - +

 - +

- ❑ Cons

 -


 -

 -

 -

 -

 -

 


Used in 1970's

Latch Design

□ Transmission gate

+

-

 

Latch Design

❑ Inverting buffer

+


+

+ Fixes either

•

•

-

 


Latch Design

❑ Tristate feedback

+

-

 ❑ Static latches are now essential because of leakage




Latch Design

□ Buffered input

+

+

 


Latch Design

❑ Buffered output

+

❑ Widely used in standard cells

 - + Very robust (most important)
- Rather large
- Rather slow (1.5 – 2 FO4 delays)
- High clock loading




Latch Design

□ Datapath latch

+


+

-

 

Flip-Flop Design


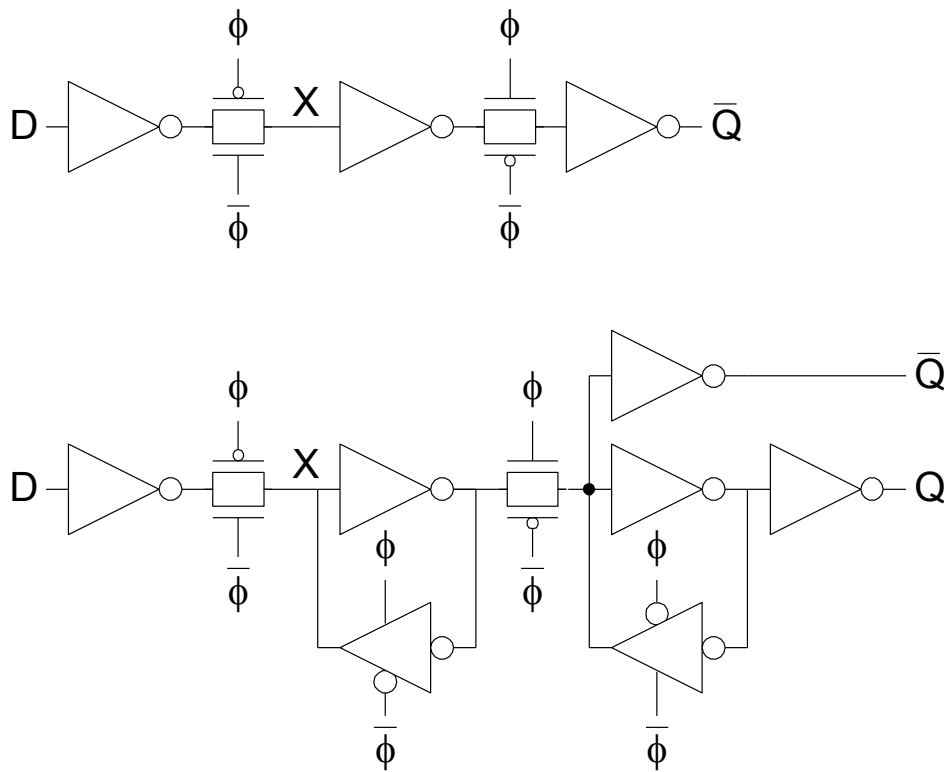
- ❑ Flip-flop is built as pair of back-to-back latches





Enable

- ❑ Enable: ignore clock when $en = 0$
 - Mux: increase latch D-Q delay
 - Clock Gating: increase en setup time, skew



Symbol

  

Multiplexer Design

  


Clock Gating Design

  


Reset

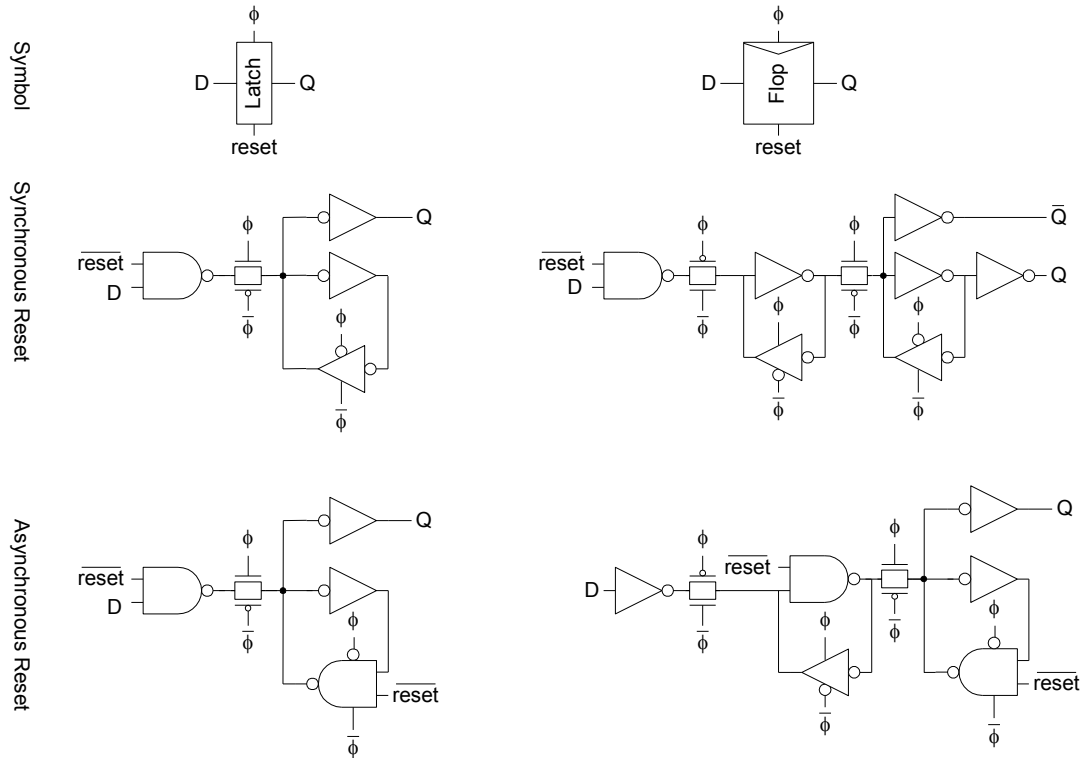- ❑ Force output low when reset asserted
- ❑ Synchronous vs. asynchronous




Set / Reset

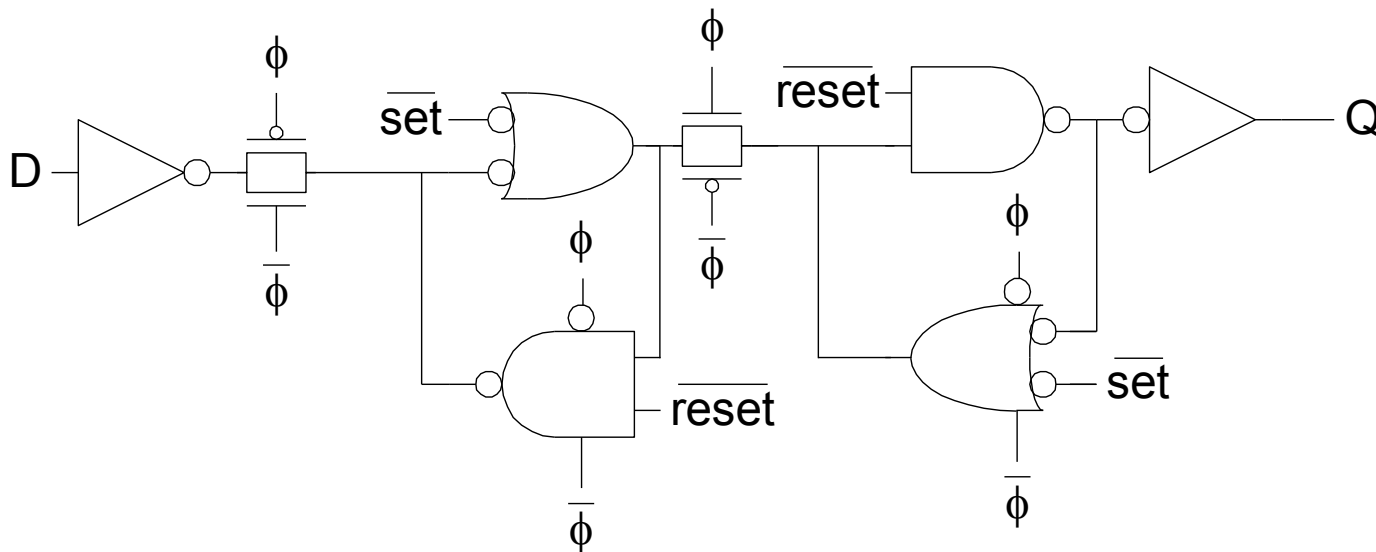- ❑ Set forces output high when enabled
- ❑ Flip-flop with asynchronous set and reset




Flip-Flop Design

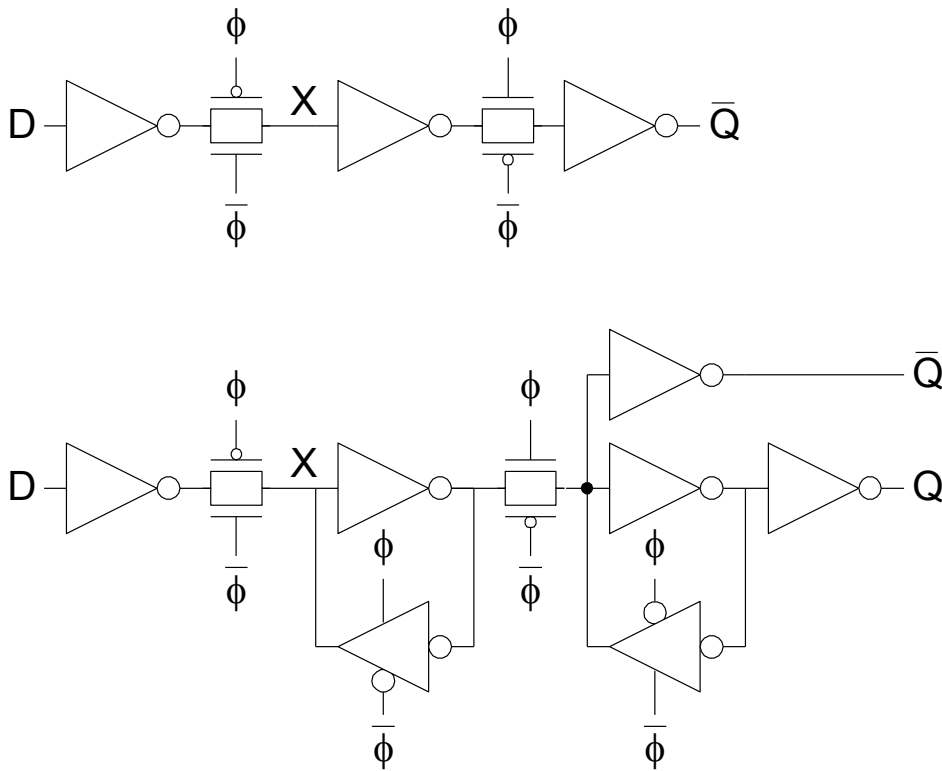- ❑ Flip-flop is built as pair of back-to-back latches





Max-Delay: Flip-Flops
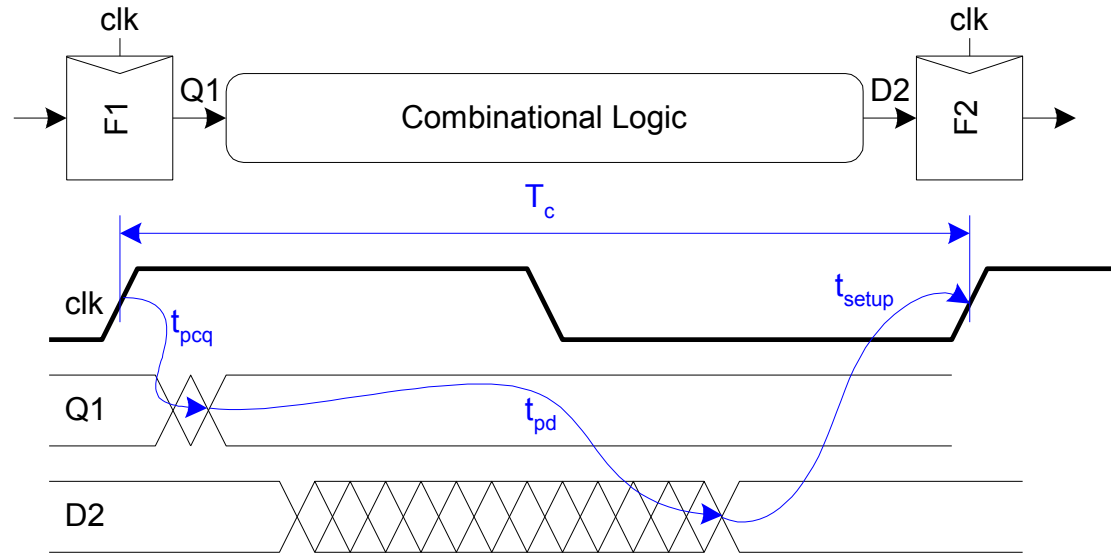
$$t_{pd} \leq T_c - \underbrace{(t_{\text{setup}} + t_{pcq})}_{\text{sequencing overhead}}$$



Min-Delay: Flip-Flops
  
$$t_{cd} \geq t_{\text{hold}} - t_{ccq}$$





Clock Skew

- ❑ We have assumed zero clock skew
- ❑ Clocks really have uncertainty in arrival time
 - Decreases maximum propagation delay
 - Increases minimum contamination delay

Skew: Flip-Flops

$$t_{pd} \leq T_c - \underbrace{(t_{pcq} + t_{setup} + t_{skew})}_{\text{sequencing overhead}}$$
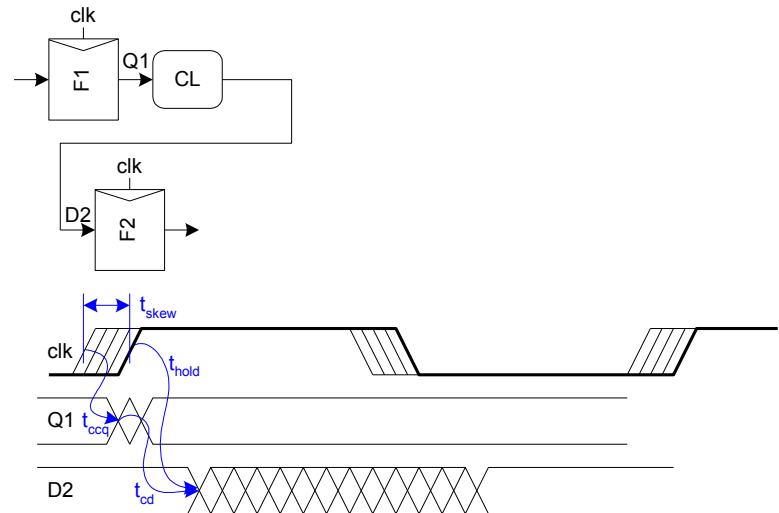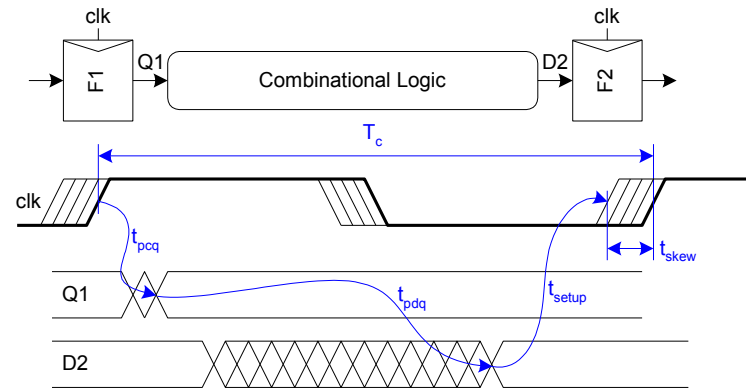
$$t_{cd} \geq t_{hold} - t_{ccq} + t_{skew}$$




Two-Phase Clocking

- ❑ If setup times are violated, reduce clock speed
- ❑ If hold times are violated, chip fails at any speed
- ❑ In this class, working chips are most important
 - No tools to analyze clock skew
- ❑ An easy way to guarantee hold times is to use 2-phase latches with big nonoverlap times
- ❑ Call these clocks ϕ_1 , ϕ_2 (ph1, ph2)


Safe Flip-Flop

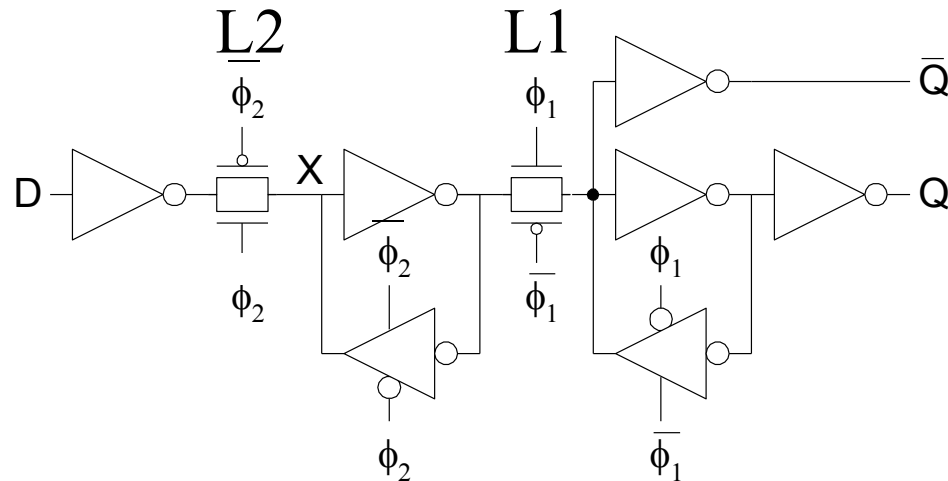- ❑ Safe designs use flip-flop with non-overlapping clocks
 - Slow – non-overlap adds to setup time
 - But no hold time problems
- ❑ In industry, use a better timing analyzer
 - Add buffers to slow signals if hold time is at risk




Max Delay: 2-Phase Latches
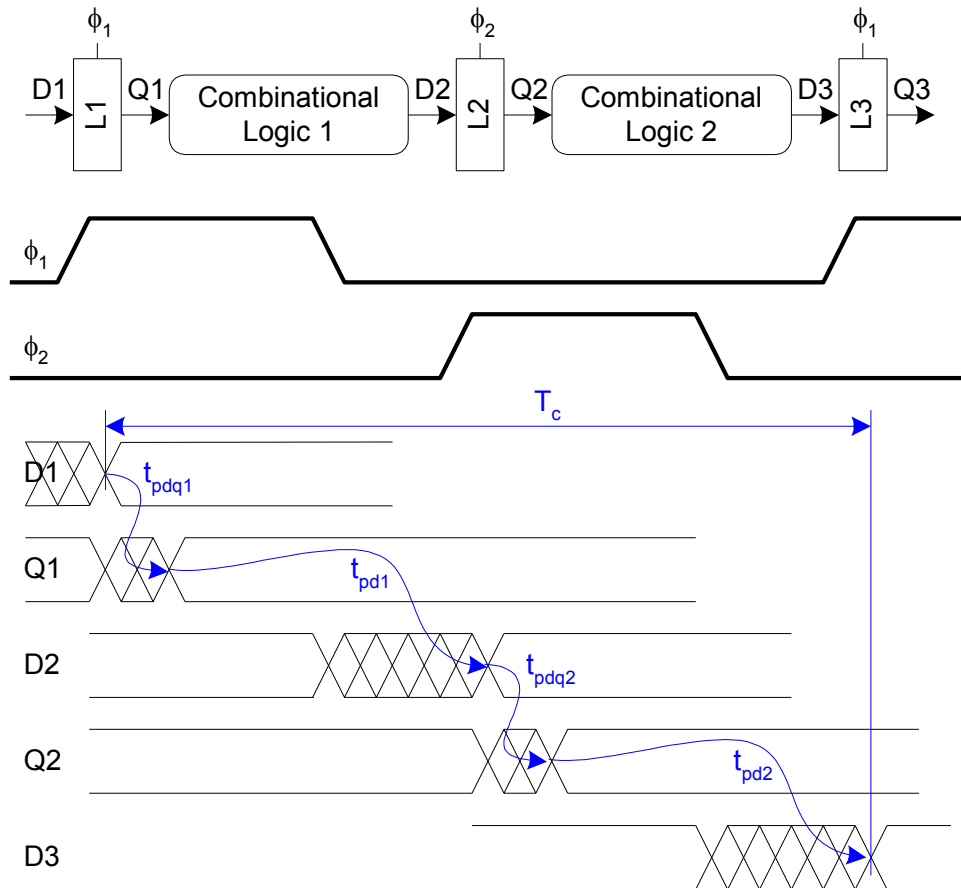
$$t_{pd} = t_{pd1} + t_{pd2} \leq T_c - \underbrace{\hspace{2cm}}_{\text{sequencing overhead}}$$





Min Delay 2-Phase Flip-Flop

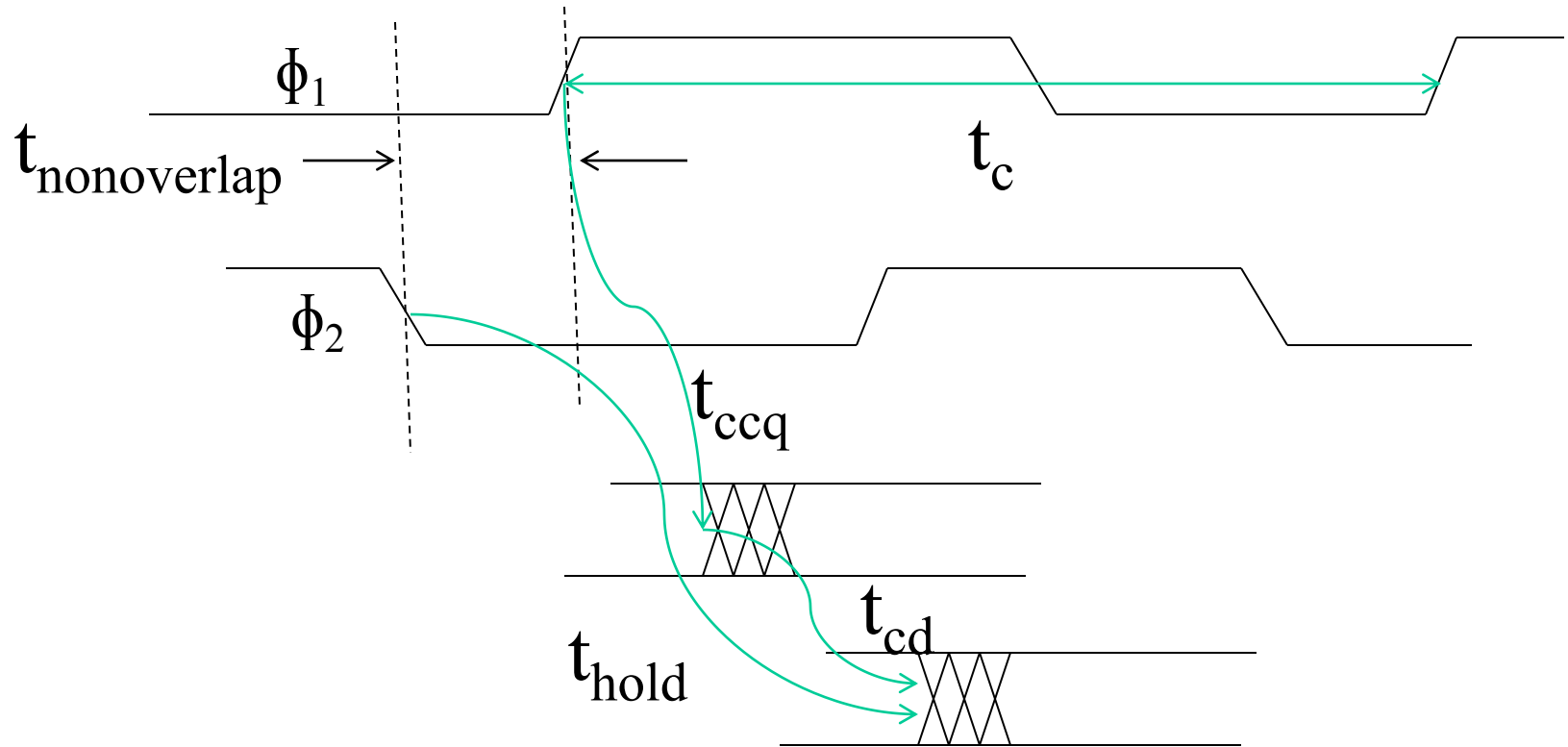

$$t_{\text{cd}} > t_{\text{hold}} - t_{\text{ccq}} - t_{\text{nonoverlap}}$$


Violation of Dynamic Discipline

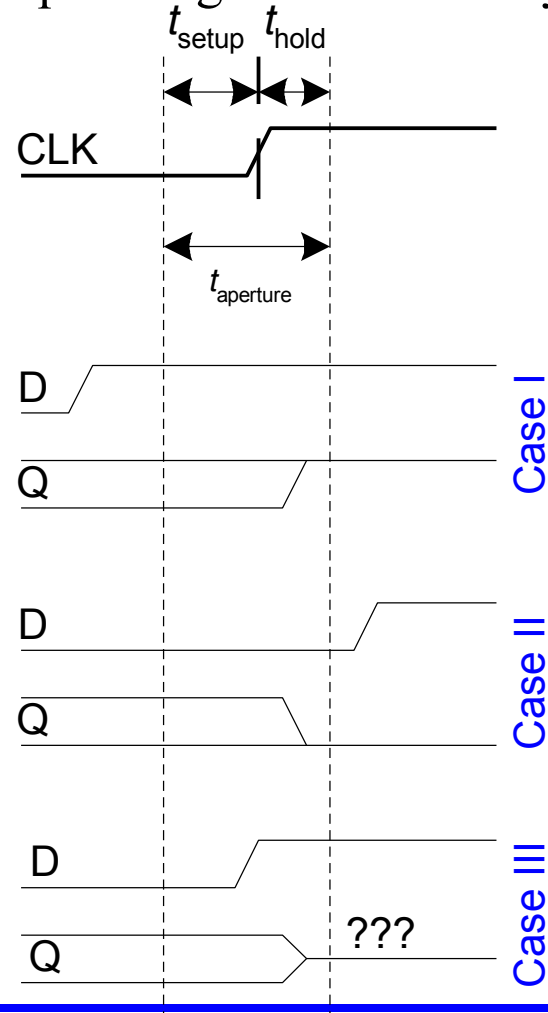 - Asynchronous (for example, user) inputs might violate the dynamic discipline




Metastability

 - Any bistable device has two stable states and a metastable state between them
- A flip-flop has two stable states (1 and 0) and one metastable state
- If a flip-flop lands in the metastable state, it could stay there for an undetermined amount of time



Synchronizer Internals

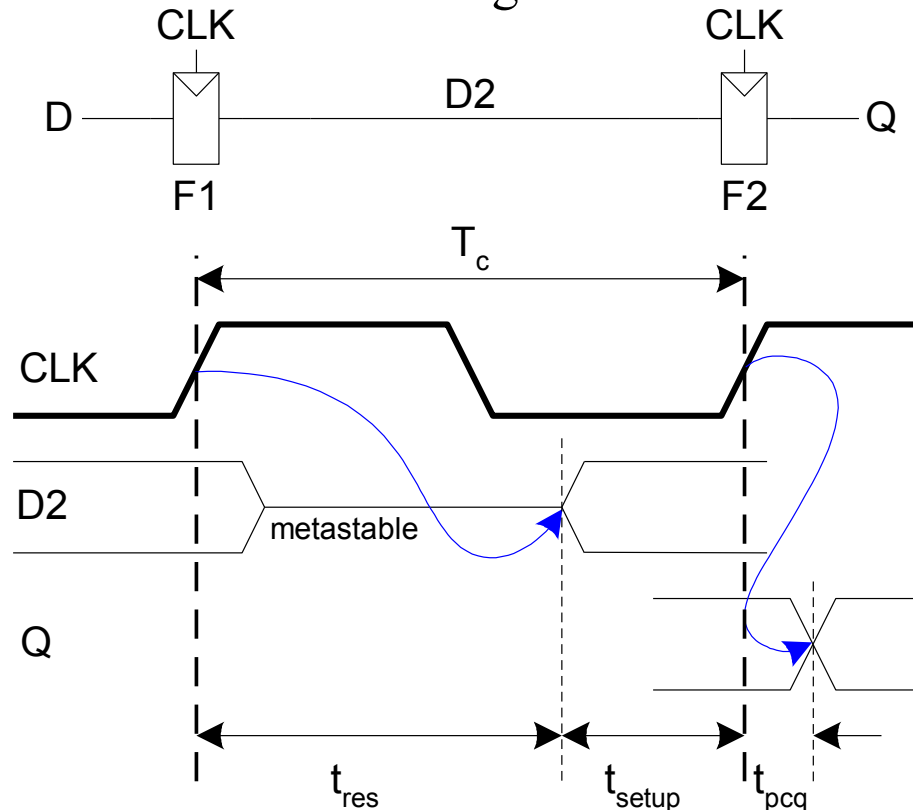
- ❑ A synchronizer can be built with two back-to-back flip-flops.
- ❑ Suppose the input D is transitioning when it is sampled by flip-flop 1, F1.
- ❑ The amount of time the internal signal D2 can resolve to a 1 or 0 is $(T_c - t_{\text{setup}})$.



Synchronizer Probability of Failure

For each sample, the probability of failure of this synchronizer is:
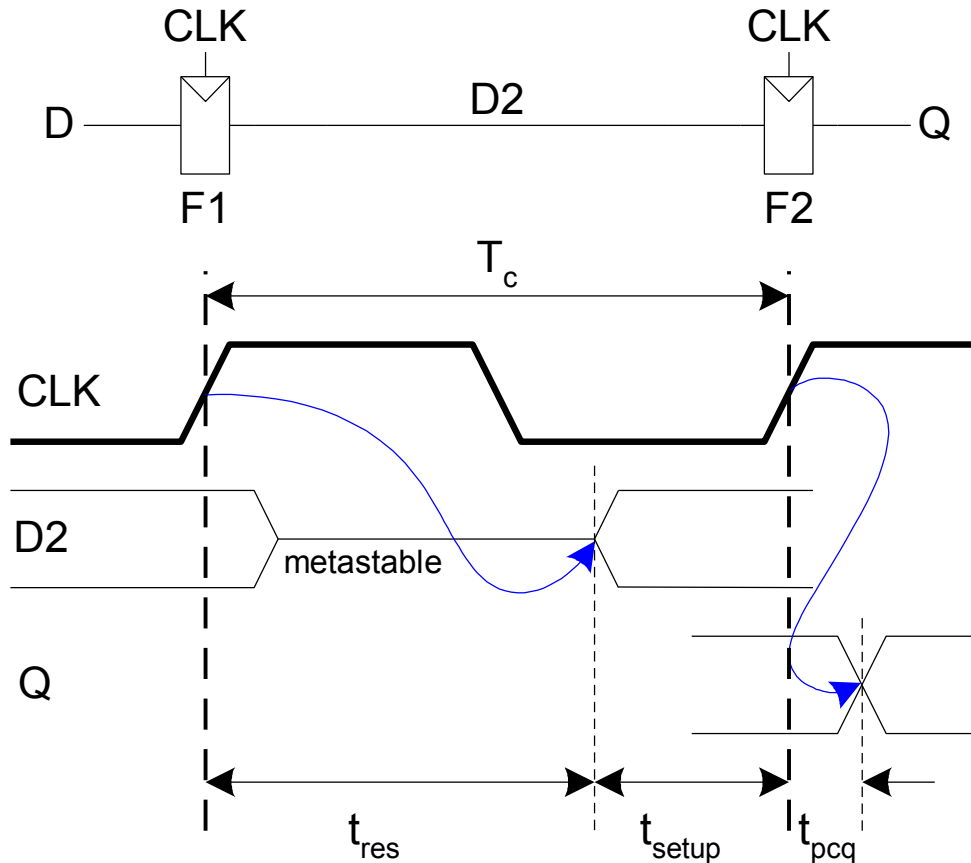
$$P(\text{failure}) = (T_0/T_c) e^{-(T_c - t_{\text{setup}})/\tau}$$



Synchronizer Mean Time Before Failure

- ❑ If the asynchronous input changes once per second, the probability of failure per second of the synchronizer is simply $P(\text{failure})$.
- ❑ In general, if the input changes N times per second, the probability of failure per second of the synchronizer is:

- ❑
$$P(\text{failure})/\text{second} = (NT_0/T_c) e^{-(T_c - t_{\text{setup}})/\tau}$$

- ❑ Thus, the synchronizer fails, on average, $1/[P(\text{failure})/\text{second}]$
- ❑ This is called the *mean time between failures*, MTBF:

$$\text{MTBF} = 1/[P(\text{failure})/\text{second}] = (T_c/NT_0) e^{(T_c - t_{\text{setup}})/\tau}$$