

Digital Devices

E155
9/16/2013

Outline



□ Combinational Logic


- 1-bit full adder
- 32-bit adder
- Priority decoder
- Days of month

□ Sequential Logic

- Counter
- Shift adder
- RAM

Combinational logic

```
module gates ( input logic [3:0] a, b,  
               output logic [3:0] y1, y2, y3, y4, y5);  
  
    assign y1 = a & b;  
    assign y2 = a | b;  
    assign y3 = ~y1;  
    assign y4 = ~y2;  
    assign y5 = a ^ b;  
  
endmodule
```

 


Flip Flop

```
module flopr(input logic      clk,
              input logic      reset, en,
              input logic [3:0] d,
              output logic [3:0] q);

    // asynchronous reset
    always_ff @ (posedge clk, posedge reset)
        if (reset) q <= 4'b0;
        else if (en) q <= d;

endmodule
```

 

Rules

- ❑ Use `always_ff` and `nonblocking <=` to model synchronous sequential logic.

```
always_ff @ (posedge clk)
    q <= d; // nonblocking
```


- ❑ Use `assign` to model simple combinational logic.

```
assign y = a & b;
```

- ❑ Use `always_comb` and `blocking =` to model complicated combinational logic.



1-bit Full Adder
 
```
module fulladder(input logic a, b, cin,  
                  output logic s, cout);  
  
endmodule
```





1-bit Full Adder

```
module fulladder(input logic a, b, cin,
                  output logic s, cout);
    logic p, g;           // internal nodes
    assign p = a ^ b;
    assign g = a & b;
    assign s = p ^ cin;
    assign cout = g | (p & cin);
endmodule
```

  


1-bit Full Adder

```
module fulladder(input logic a, b, cin,
                  output logic s, cout);
    logic p, g;           // internal nodes
    always_comb // equivalent to always@(a,b,cin)
    begin
        p = a ^ b;
        g = a & b;
        s = p ^ cin;
        cout = g | (p & cin);
    end
endmodule
```

  

32-bit Adder

 
```
Module addr ( input logic [31:0] a, b,  
              output logic [31:0] y);
```



```
endmodule
```

32-bit Adder
 
```
Module addr ( input logic [31:0] a, b,  
              output logic [31:0] y);  
    assign y= a+b;  
endmodule
```



Priority Decoder

```
module priority (input logic [3:0] a,  
                 output logic [3:0] y);  
  
    always_comb  
  
        4'b1????: y = 4'b1000;  
        4'b01???: y = 4'b0100;  
        4'b001?: y = 4'b0010;  
        4'b0001: y = 4'b0001;  
  
    endmodule
```

Priority Decoder

```
module priority (input logic [3:0] a,
                  output logic [3:0] y);  
  
    always_comb  
        if (a[3]) y = 4'b1000;  
        else if (a[2]) y = 4'b0100;  
        else if (a[1]) y = 4'b0010;  
        else if (a[0]) y = 4'b0001;  
        else y = 4'b0000;  
  
    endmodule
```

Priority Decoder

```
module priority (input logic [3:0] a,  
                  output logic [3:0] y);  
  
    always_comb  
        casez (a)  
            4'b1????: y = 4'b1000;  
            4'b01???: y = 4'b0100;  
            4'b001?: y = 4'b0010;  
            4'b0001: y = 4'b0001;  
  
        endcase  
    endmodule
```

Priority Decoder

```
module priority (input logic [3:0] a,
                  output logic [3:0] y);  
  
    always_comb  
        casez (a)  
            4'b1????: y = 4'b1000;  
            4'b01???: y = 4'b0100;  
            4'b001?: y = 4'b0010;  
            4'b0001: y = 4'b0001;  
            default: y = 4'b0000;  
        endcase  
    endmodule
```

Months with 31 Days

```
module month31days (input logic [3:0] a,  
                     output logic y);  
  
    always_comb  
        case (a)  
  
            endcase  
        endmodule
```

Months with 31 Days

```
module month31days (input logic [3:0] a,
                     output logic y);

    always_comb
        case (a)
            4'b0001: y = 1;
            4'b0011: y = 1;
            4'b0101: y = 1;
            4'b0111: y = 1;
            4'b1000: y = 1;
            4'b1010: y = 1;
            4'b1100: y = 1;
            default: y = 0;
        endcase
    endmodule
```


Counter

```
module flopr(input logic      clk,
              input logic      reset, en,
              output logic [3:0] q);

    // asynchronous reset

```

```
endmodule
```

 


Counter

```
module flopr(input logic      clk,
              input logic      reset, en,
              output logic [3:0] q);

    // asynchronous reset
    always_ff @ (posedge clk, posedge reset)
        if (reset) q <= 4'b0;
        else if (en) q <= q+1;

endmodule
```

 


Shift Register

```
module flopr(input logic      clk,
              input logic      reset, en, sdi
              output logic [3:0] q);

    // asynchronous reset

endmodule
```

 


Shift Register

```
module flopr(input logic      clk,
              input logic      reset, en, sdi
              output logic [3:0] q);

    // asynchronous reset
    always_ff @ (posedge clk, posedge reset)
        if (reset) q <= 4'b0;
        else if (en) q = {sdi, q[3:1]};


endmodule
```

 

RAM

```
module ram (input logic clk,  
           input logic we,  
           input logic [7:0] adr,  
           input logic [31:0] wd,  
           output logic [31:0] rd;  
  
endmodule
```

256 word x 32 bit RAM

 

RAM

```
module ram (input logic clk,  
           input logic we,  
           input logic [7:0] adr,  
           input logic [31:0] wd,  
           output logic [31:0] rd;  
  
logic [31:0] mem[255:0];  
  
always_ff @ @ posedge (clk)  
  if (we) mem[adr] <= wd;  
  assign rd = mem[adr];//note block assignment used  
                //so that rd is the updated memory  
                // data including after a write  
  
endmodule
```

256 word x 32 bit RAM

