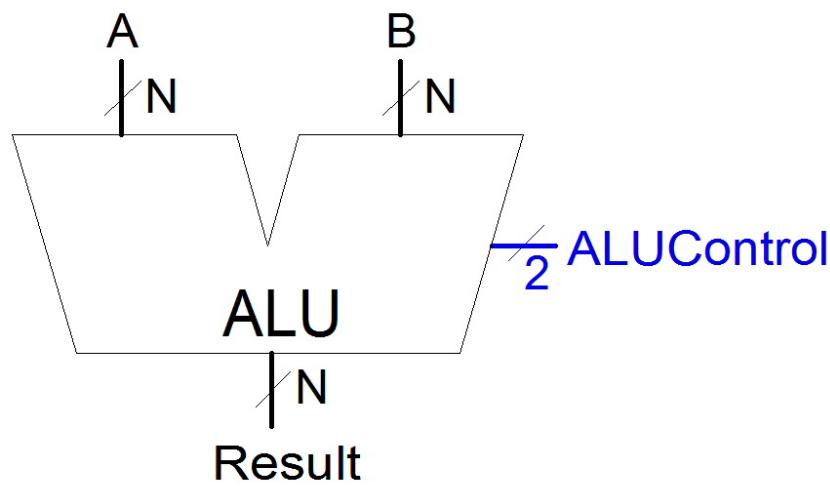


ALU Design


E85 Fall 2014

Arithmetic Logic Unit (ALU)




ALUControl _{2:0}	Function
00	A + B
01	A - B
10	A & B
11	A B

ALU Design

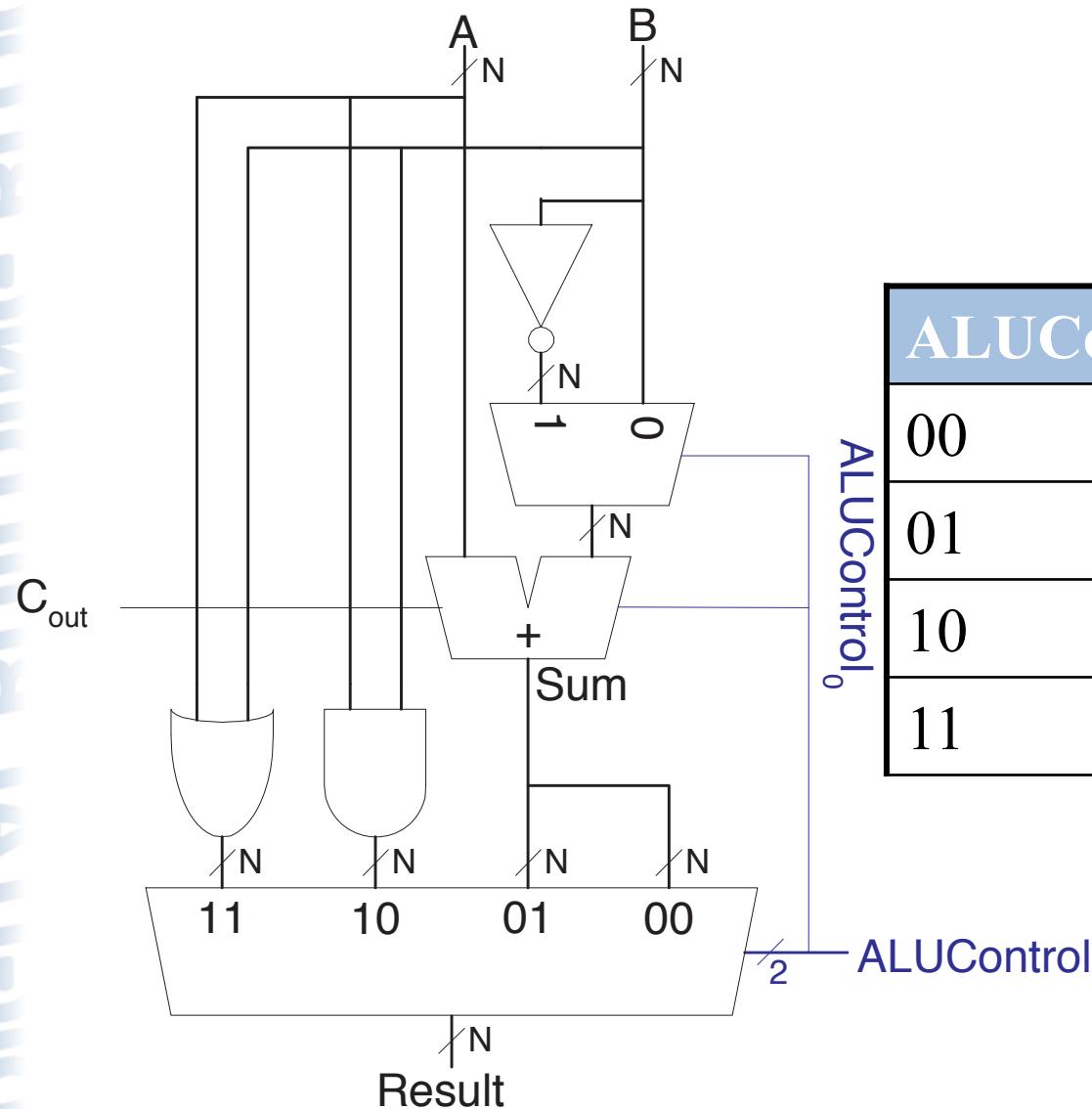


ALUControl _{2:0}	Function
00	A + B
01	A - B
10	A & B
11	A B

Subtraction Example

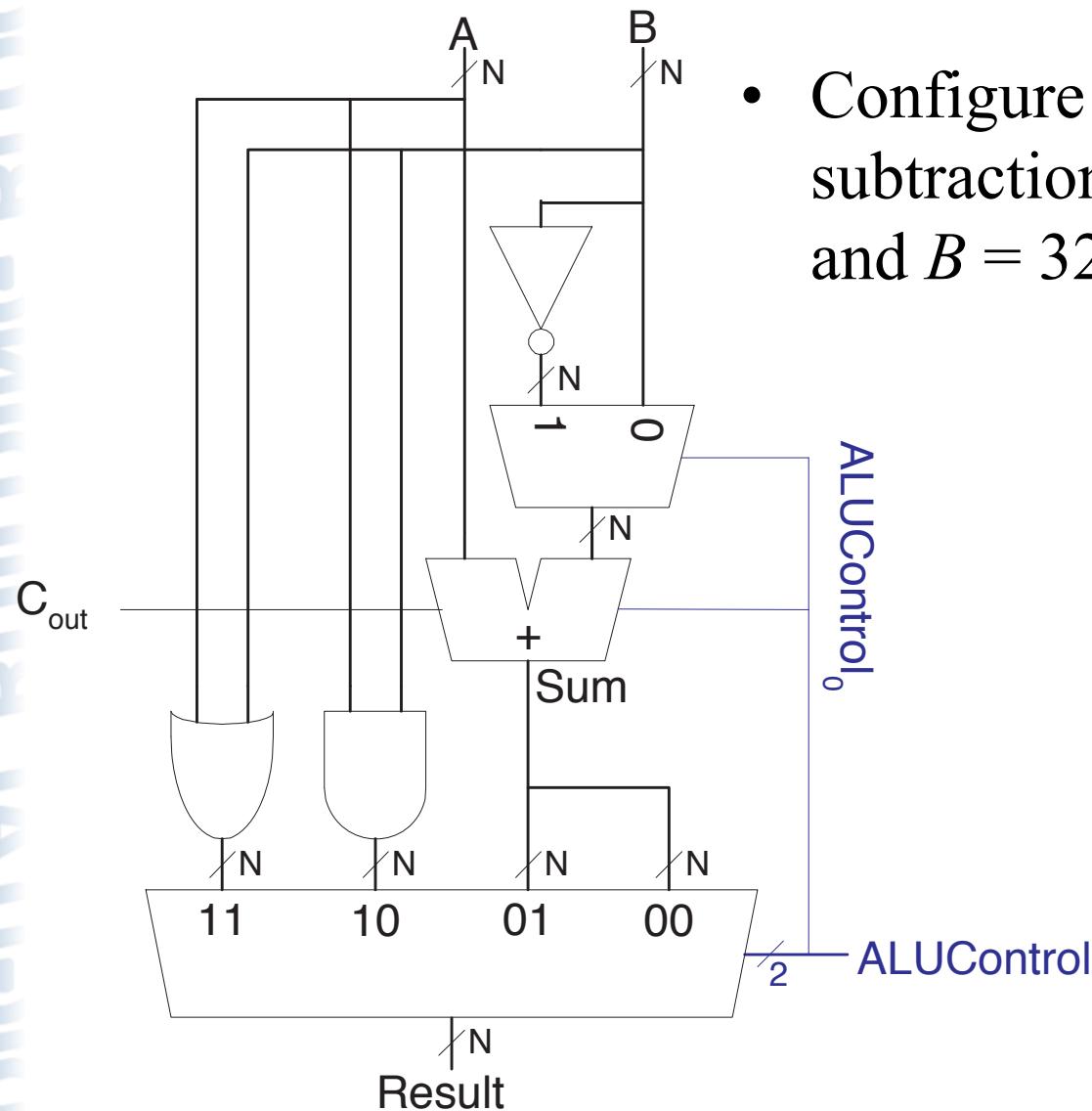

- Configure 32-bit ALU for subtraction operation: $A = 25$ and $B = 32$

Subtraction Example

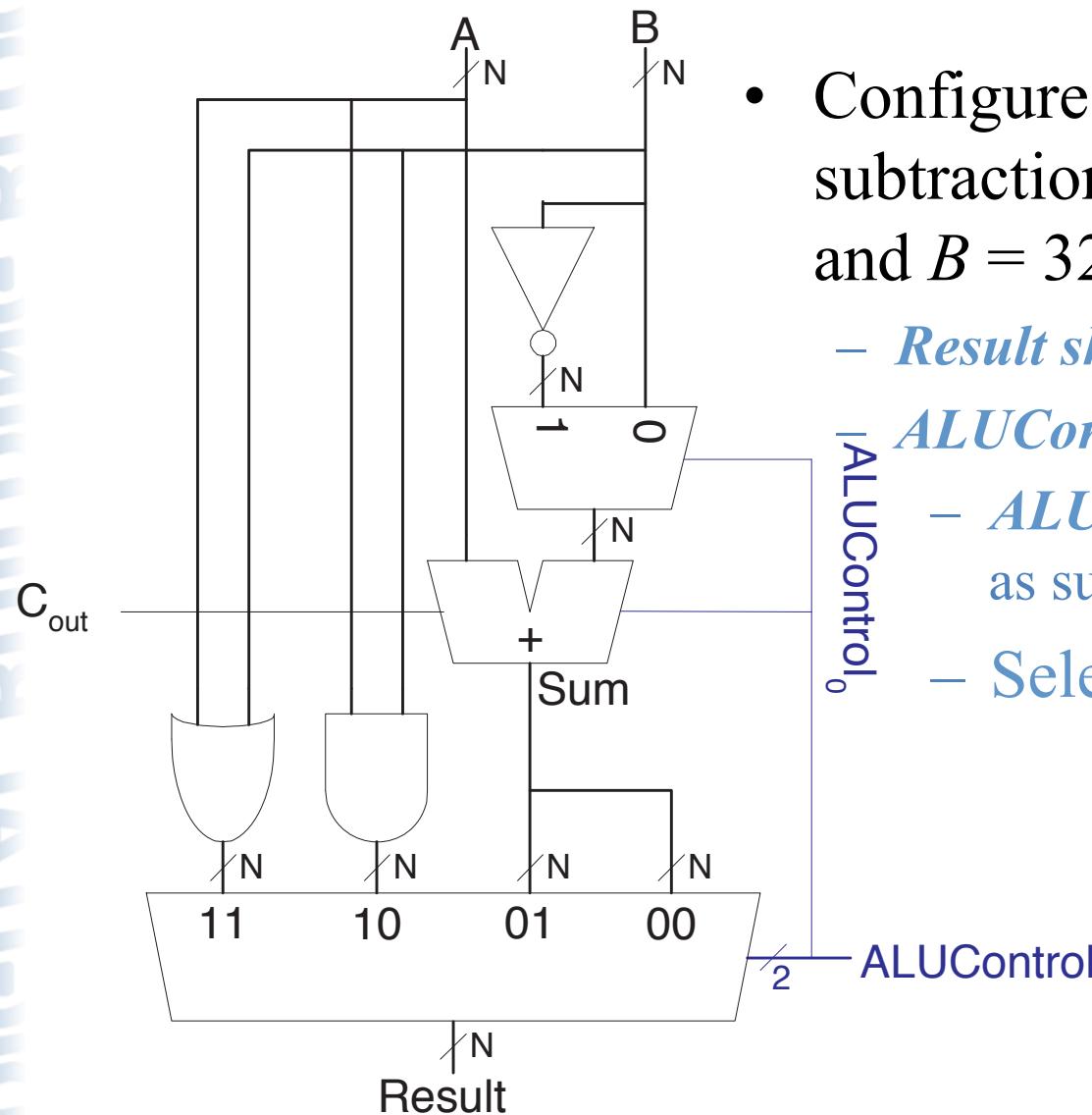

- Configure 32-bit ALU for subtraction operation: $A = 25$ and $B = 32$
 - Result should be -7 ($25 - 32$)*
 - $ALUControl_{1:0} = 01$
 - $ALUControl_0 = 1$ (adder acts as subtracter), so $25 - 32 = -7$
 - Select Sum for Result