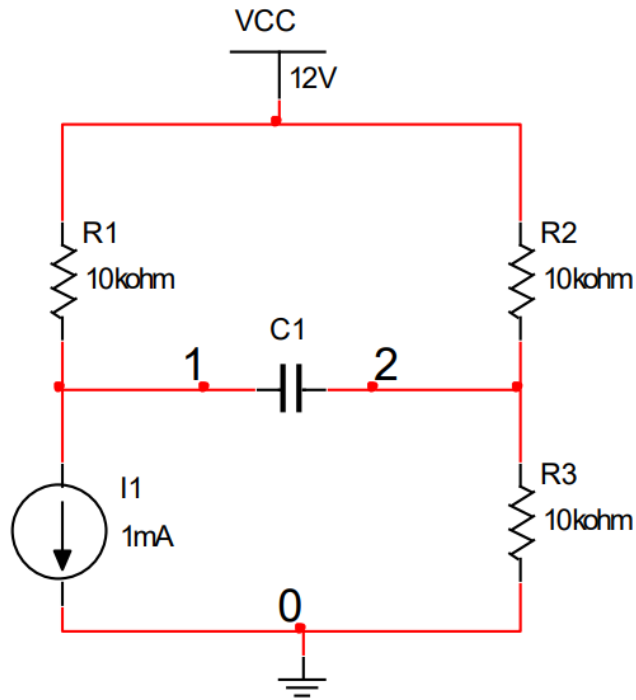


Lecture 1, Intro and Thevenin, Homework
E153 F17 - Spencer



(a) Find the effective resistance seen by the capacitor. (i.e.: the Thevenin resistance across the port between terminals 1 and 2). Call it R_{12} .

(b) Determine the Thévenin equivalent (i.e.: open circuit) voltage seen from a port between node 1 and ground. Call it $V_{oc-1,0}$.

(c) Determine the Thévenin equivalent (i.e.: open circuit) voltage seen from a port between node 2 and ground. Call it $V_{oc-2,0}$.

(d) What is the current between terminals 1 and 2? Be sure to explain why.

(e) If C_1 is changed to a resistor of $5k\Omega$, determine the current between terminals 1 and 2 and its direction. Hint: you already know R_{12} , what other quantity would make this easy to calculate?

(f) If I_1 is changed to a dependent current source with a current of $1mS \cdot v_2$, what is the effective resistance seen by the capacitor?