 


Lecture 16 and 17, Cascode Amplifier and MOS Capacitance  
E151/3 F17 – Matthew Spencer

 


**Figure 1:** A folded Cascode amplifier.

1. The amplifier pictured above is called a folded cascode amplifier. One aside that you don't need for the problem: the current sources in this amplifier are usually implemented as current mirrors, and we'll be studying how to incorporate them into amplifiers soon.

(a) Draw a small signal model for it and compare the small signal model to the cascode amplifier we studied in class (which is referred to as a telescopic cascode amplifier).

(b) Calculate the voltage swing of this folded cascode. Both npn and pnp transistors have a turn-on voltage of  $V_{be,on}$  and a saturation voltage of  $V_{ce,sat}$ . Assume the current at the emitter of the NPN is selected to maximize output swing.



**Figure 2:** An inverter.

2. Digital gates, like the inverter above, operate their transistors in a mix of operating regions. When the input voltage is transitioning from low to high, the NMOS device starts in cutoff, enters saturation as the input voltage rises above  $V_t$ , and finally ends in linear operation as the output voltage falls below the input voltage.

(a) What regions of operation does the PMOS device pass through during a low to high transition at the input and at what combinations of  $V_{in}$  and  $V_{out}$  does it switch between those regions? You may assume that the edge rate at the input is similar to the edge rate at the output; neither  $V_{in}$  nor  $V_{out}$  looks like an ideal step compared to the other quantity.

(b) What capacitance is seen at the input (i.e.: what is the sum of all capacitors with one terminal attached to the in node) during each combination of NMOS/PMOS device states? Assume both devices have length  $L$  and capacitance density  $C_{ox}$ .