

Lecture 22, References
E151/3 F17 – Matthew Spencer

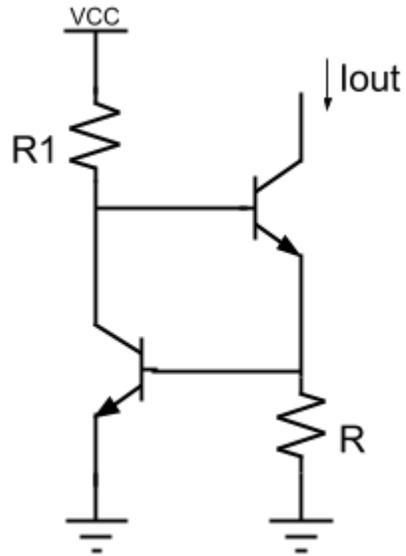


Figure 1: A vbe reference.

1. A vbe reference is pictured in Figure 1. Calculate the sensitivity of Iout to Vcc. This is in the notes, but try to do it on your own before checking them.