

Lecture 09 -- Emitter Degeneration, Emitter Followers, Multistage Amplifiers

Draw a modified common emitter amplifier which uses a capacitor to bypass the tradeoff between gain and offset voltage in the mid-band.

Draw a common emitter amplifier with an active load.

Draw an emitter degenerated common emitter amplifier.

What are R_{in} and A_v for an emitter degenerated common emitter amplifier?

What R_{out} for an emitter degenerated common emitter amplifier if r_o is ignored?

Draw 3 common patterns we find in small signal models and record their impedances

Draw a two port model for an amplifier which uses our amplifier parameters, compare it to a general 2-port Z parameter model