

E151 Lecture 1 – Intro and Linear Networks Review

Matthew Spencer
Harvey Mudd College
ENGR151

Disclaimer

These are note for Prof. Spencer to give the lecture, they were not intended as a reference for students. Students asked for them anyway, so I'm putting them up as a courtesy. Remember that they are not intended as a substitute for lecture.

Why Take This Class

- Teaching analog circuit design
- “Analog is dead and digital is king” – some strawman
- Used ADC in E80, why not apply to every analog problem? (board list)
 - Speed, noise, dynamic range, power ← All tightly linked
 - Expensive, complex to design and use, delicate
 - Why is outside the scope of this class ... but true
- What other analog tool do you know (op-amp). Why not? (board list)
 - Low power output
 - Limited bandwidth
 - We WILL learn why here ← YOU WILL BUILD ONE

What Makes Up Our Goals?

- Learning goals: you will learn how to build an op-amp (as list)
 - Really good at basics: RC dynamics and KVL/KCL
 - Basic semiconductor physics and intuition for how devices work in circuits
 - Single and multi-stage linear amplifiers
 - Analog building blocks and “talking the talk”
 - Fearless in lab and rational debugging
- Four major types of analysis (as list)
 - Large signal
 - Small signal
 - Dynamic
 - Other (mostly differential)

How Are We Doing This?

Mon	11:59PM	Turn in Lab Notebook & Problems
Tue	Lecture	Lab debrief
Wed		
Thu	12:01PM	Turn in self-graded problems
	Lecture	Quiz on lecture material (ind, + group)
	Afternoon	Lab + problems released
Fri	Lab	Oscope lesson & work time


- Lab deliverable is notebook: next slide
- Problems don't need to be done before lab, just related
- More later on design project, problems solo, DP + lab partners

Lab Notebook Demo

- My example posted
- Chronological – that helps you reference from boss qs
- Informal and handwritten – clear, but not a writeup, always evidence
- Correct – you need to get right measurements in this class, like 80
- This should help you both in and out of lab
- Lab password
- Break to gather partners, come back to tech work.

E84 was Linear Circuit Theory

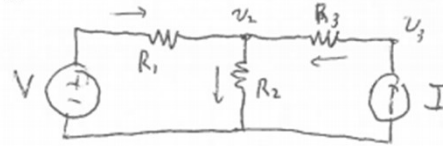- Small groups, find i_2 3 different ways for



① KCL $i_2 = \frac{V - u_2}{R_1} + I$ & $u_2 = i_2 R_2 \rightarrow i_2 = \frac{V}{R_1} - \frac{u_2}{R_1} + I$

$$I = \frac{u_3 - u_2}{R_3}$$

$$i_2 \left(1 + \frac{R_2}{R_1}\right) = \frac{V}{R_1} + I$$

$$i_2 = \frac{\frac{V}{R_1} + I}{1 + R_2/R_1}$$


② KVL

$$V = i_1 R_1 + (i_1 + I) R_2$$

$$i_1 = \frac{V - I R_2}{R_1 + R_2}$$

$$i_2 = \frac{V + I R_1}{R_1 + R_2} = \frac{V/R_1 + I}{1 + R_2/R_1}$$

③ Superposition

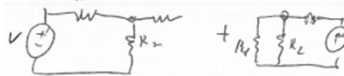

$$i_2 = \frac{V}{R_1 + R_2} + I \frac{R_1}{R_1 + R_2}$$

Split into "superposition subcircuits" and "turn off" supplies

- Split into equivalent summed circuits really common here
- Why the heck do we "turn off" sources

Matrix Picture of Circuit Linearity

- Split matrix into vectors and turn them off one at a time.

$$\begin{bmatrix} V \\ u_2 \\ u_3 \end{bmatrix} = \begin{bmatrix} R_1 & R_2 & 0 \\ 0 & R_2 & 0 \\ 0 & R_2 & R_3 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ I \end{bmatrix} = \begin{bmatrix} R_1 \\ 0 \\ 0 \end{bmatrix} i_1 + \begin{bmatrix} R_2 \\ R_2 \\ R_2 \end{bmatrix} i_2 + \begin{bmatrix} 0 \\ 0 \\ R_3 \end{bmatrix} I$$

Can find I contrib. Takept R_1 & R_2

① Make superpos subccts by "turning off" all but I src (short/open)

② Find i_2

③ Sum across all component subcct

Dependent Sources (I solve)

- V source or I source controlled by some other spot in circuit

Dependent Sources




- generate a voltage or current depending on some other v or i in ckt

→ like this, just have resistors, transformers

- Can't use superposition b/c depends on another source
↳ must be in all superpos sub ckt.

Solve

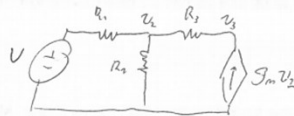

$$\frac{V - i_2 R_2}{R_1} + g_m R_2 i_2 = i_2$$

$$\frac{V}{R_1} = i_2 \left(1 + \frac{R_2}{R_1} - g_m R_2 \right)$$

$$i_2 = \frac{V/R_1}{1 + R_2/R_1 - g_m R_2}$$

- Can get crazy results (feedback)

- Can get hairy algebra