

E151 Lecture 7

Common Emitter Amplifier and Biasing BJTs

Matthew Spencer
Harvey Mudd College
ENGR151

Disclaimer

These are notes for Prof. Spencer to give the lecture, they were not intended as a reference for students. Students asked for them anyway, so I'm putting them up as a courtesy. Remember that they are not intended as a substitute for attending lecture.

Small Signal Derivation

- Graphical, Ebers-Moll Equation Based, Diode argument, i_c linear i_b !

) small signal model review in FAR

Don't forget to show $g_m \cdot r_p = \beta$

$i_c = \beta i_b$
 $i_e = i_c + i_b$
 $i_b = I_{ES} (e^{v_{BE}/\phi_{th}} - 1)$ ← on i_b → function of v_{BE}
 $i_c = \beta I_{ES} (e^{v_{BE}/\phi_{th}} - 1) (1 + \frac{v_{CE}}{V_A})$ ← $\frac{\partial i_c}{\partial v_{BE}} = \frac{I_C}{\phi_{th}} \approx g_m$
 we've been ignoring V_A in calc, but slowing on large signal plots
 $\frac{\partial i_c}{\partial v_{BE}} = \frac{I_C}{V_A}$ ← conductance
 $r_o = \frac{V_A}{I_C}$

conductance, $g_m = \frac{\phi_{th}}{I_B} \approx \frac{\beta}{g_m}$
 $\frac{\partial i_b}{\partial v_{BE}} = \frac{I_B}{\phi_{th}}$

$i_B = I_{ES} (e^{v_{BE}/\phi_{th}} - 1)$
 $i_C = \beta i_B$
 This slope "new" to our model
 - V_{CE} affects size of base
 - Q-m bias w/ V_A

What About PNP? Large signal negative

- Backwards from NPN, diodes point IN! (care w/ i direction)
- Region of operation table to emphasize
- Small signal is identical by diode/graphical argument

PNP $-I_E$, $+I_B$, $+I_C$

$-I_c$ vs $-V_{BE}$ graph showing exponential curves.
 - Identical but negative

BE	BC	
off	off	cut-off
fund	off	FAR
off	fund	RAR
fund	fund	SAT

 - Again, same as NPN but upside down
 By diode argument (graphical) ~ - Same! Good small signal model


PNP Exercise for Class

- Have them work example

— Recall that I find this all confusing. Just think of PNP

(in a circuit (or as junctions))

You guys

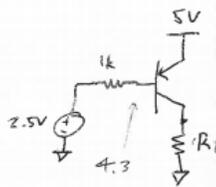

① — Find I_C

— For PNP, if we have emitter to supply & recall stuff turns on below supply it makes sense

$$\beta = 50$$

$$|U_{BE,ON}| = 0.7V$$

$$U_R = 1.8V \rightarrow I_b = 1.8\mu A \rightarrow I_C = 90\mu A$$

$$(U_{CB} = 0.5V)$$

② — What is max R_1 before we enter SAT? $U_{CE,SAT} = 0.1V$

$$U_{CE} = 5V - 90\mu A \cdot R_1 \quad U_C = 90\mu A \cdot R_1 \text{ must be } < 4.9V$$

$$R_1 < \sim 55\Omega$$