

E151 Lecture 8

Amplifier Design and Voltage Swing

Matthew Spencer
Harvey Mudd College
ENGR151

Disclaimer

These are notes for Prof. Spencer to give the lecture, they were not intended as a reference for students. Students asked for them anyway, so I'm putting them up as a courtesy. Remember that they are not intended as a substitute for attending lecture.

Built an Amplifier, Biasing Improvements

- Get to a_v , r_{in} and r_{out} indirectly
- Invoke voltage swing with final example
- We have been building up a sense of design specs for amps

Issues
- precise V_B and β
- stack V_B & V_b

negation is phase shift $\uparrow V_b$ asks $\downarrow V_o$

Issue
- Many V_B needed

see input loading, care about R_{in}

What if $I_C R_E > V_B$ in FAR?
Not just a divider? $I_C = \frac{V_B - V_{BE,ON}}{R_e}$

Bypass ground collector \rightarrow get same gain, changes?

Design Specifications for Amplifiers


- Suggests a generalized 2 port model for amplifiers ... no Z12, so easy

Sometimes care about a_i
 d_{io}/d_{ii} | out short = beta


Symbol	Name	Calc
a_v	Voltage gain	d_{vo}/d_{vi} out open
r_{in}	Input resistance	d_{ii}/d_{vi} out short
r_{out}	Output resistance	d_{io}/d_{vo} in short
V_{SW}	Voltage swing	$V_{O_MAX} - V_{O_MIN}$
I_{IN}	Input bias current	Large signal I_{IN}
f_{low}	Low f -3dB corner	Measure for now

Fall straight out of small signal,
Must measure with power on!
(small sig. open/short, not big)

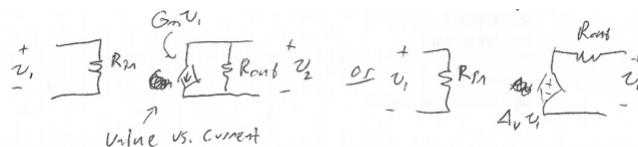Must find nominal V_O and
figure out allowed excursions
 $2 * \min(V_{O_MAX} - V_O, V_{O_MIN} - V_O)$




Output Swing Example

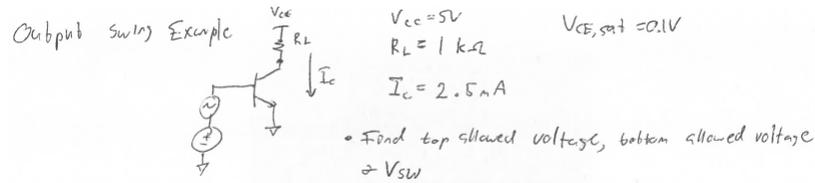

1. Find $V_O = V_{CC} - I_C \cdot R_L$
 2. If V_O down, when do we leave FAR? $V_{MIN} = V_{CE,SAT}$
 3. If V_O up, when do we leave FAR? $V_{MAX} = V_{CC}$ (cutoff)
 4. Check at input: $A_v = g_m \cdot R_L = 100$, so $+2.5V V_O/2$ is $\sim 25mV @in$
- Approximate: get distortion before sat/cutoff \rightarrow use FFT & 1-2V margin

Design Process: Specs to I_C / R values

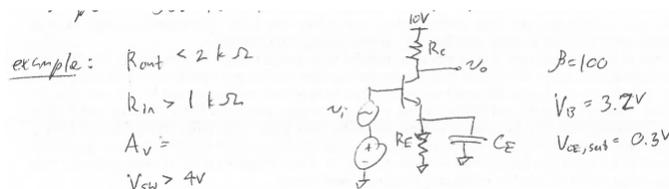

- Start w/ easy constraints:

• Eg: $r_{\pi} = \frac{\beta}{g_m} = \frac{\beta V_T}{I_C} = \frac{100 \cdot 25mV}{I_C} > 1k\Omega \rightarrow I_C > 2.5mA$

min power by setting $I_C = 2.5mA$
 $\approx 100mA$

- Unusual, easy constraints are usually at output: V_{SW} or r_{out} constraints

- Propagate

$V_{BE} = 3.2V$, so need $R_E = 1k$

- $V_{OMAX} = 10V, V_{OMIN} = V_E + V_{CE,SAT} = 2.8V, \frac{1}{2}$ way max swing $\rightarrow V_O = 6.4V$

$R_C = 1.6k$