



E151 Lecture 15 – References

Matthew Spencer
Harvey Mudd College
ENGR151

Disclaimer

These are notes for Prof. Spencer to give the lecture, they were not intended as a reference for students. Students asked for them anyway, so I'm putting them up as a courtesy. Remember that they are not intended as a substitute for attending lecture.

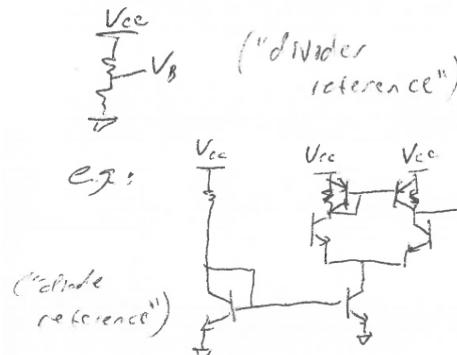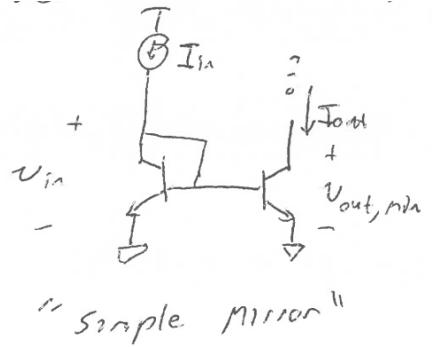How Do We Make Current Sources in Mirrors?




- Need analysis tools to measure "how good" V or I reference is
- References need to be supply and temperature invariant (PVT is big)

Measure Quality of Reference with Sensitivity


$$S_{\text{to } X} \equiv S_X \equiv \lim_{\Delta X \rightarrow 0} \frac{\Delta Y / Y}{\Delta X / X} = \frac{X}{Y} \frac{\partial Y}{\partial X} \quad \begin{matrix} \text{fractional change} \\ \text{of } Y \text{ w/rt } X \end{matrix}$$

e.g.: divider reference in simple mirror

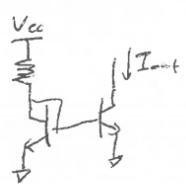

$$\begin{aligned} S_{V_{cc}}^{I_{out}} &= \frac{V_{cc}}{I_{out}} \cdot \frac{\partial}{\partial V_{cc}} \left[\left(\frac{\beta}{\beta+2} \right) \cdot \left(\frac{V_{cc} - V_{be,01}}{R} \right) \right] \\ &= \frac{\beta}{\beta+2} \cdot \frac{V_{cc}}{R} \\ &\quad \left(\frac{\beta}{\beta+2} \right) \left(\frac{V_{cc} - V_{be,01}}{R} \right) \end{aligned}$$

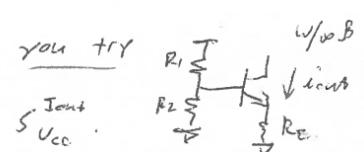
$$\approx \sqrt{\frac{V_{be,01}}{(1 - \frac{V_{be,01}}{V_{cc}})}} \approx 1 \quad \text{very sensitive!}$$



$$\frac{\partial I_{outb}}{\partial V_{cc}} = \frac{R_2}{R_E} \cdot \frac{V_{cc}}{R_1 + R_2}$$

$$S_{V_{cc}}^{I_{outb}} = \frac{1}{\left(1 - \left(1 + \frac{R_1}{R_2} \right) \frac{V_{be,01}}{V_{cc}} \right)} \approx 1$$

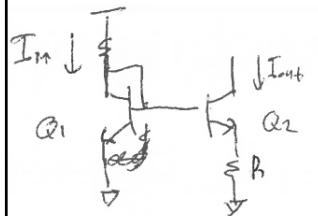“Widlar Current Source” Reference if Time



Interested in $I_{out}(I_{in})$

$$- V_{be1} = V_{be2} + I_{out} R - \frac{\beta}{\beta+1}$$

$$- I_{S1} e^{\frac{V_{be1}}{\phi_T}} = I_{S2} \rightarrow V_{be1} = \phi_T \ln \frac{I_{S2}}{I_{S1}}$$

Note can if
assume 0.7V
here

$$- \phi_T \ln \frac{I_{in}}{I_{out}} \approx I_{out} R$$

• Need an $\frac{1}{\beta}$ for V_{be}
Chg last lecture

- Logarithmic compression of I_{in} , so called a reference

“Widlar Current Source” Reference if Time

- Sensitivity w/ 1mA and 1k this is a factor of 40 better

$$\text{Sensitivity} \sim \phi_T \frac{\partial}{\partial V_{cc}} \ln \frac{I_{in}}{I_{out}} = R \frac{\partial I_{out}}{\partial V_{cc}}$$


$$\phi_T \left(\frac{i}{I_{out}} \frac{\partial I_{in}}{\partial V_{cc}} + \frac{I_{in}}{I_{out}} \frac{\partial I_{out}}{\partial V_{cc}} \right) = R \frac{\partial I_{out}}{\partial V_{cc}}$$

$$\frac{\partial I_{out}}{\partial V_{cc}} = \left(\frac{i}{1 + \frac{I_{out} R}{\phi_T}} \right) \circ \frac{I_{out}}{I_{in}} \circ \frac{\partial I_{in}}{\partial V_{cc}} \approx 1$$

$$S_{V_{cc}}^{I_{out}} = \frac{V_{cc}}{I_{out}} \circ \frac{\partial I_{out}}{\partial V_{cc}} = \left(\frac{1}{1 + \frac{I_{out} R}{\phi_T}} \right) \circ S_{V_{cc}}^{I_{in}} \approx \left(\frac{1}{1 + \frac{I_{out} R}{\phi_T}} \right)$$

Vbe Reference if Time

You \downarrow V_{be} reference

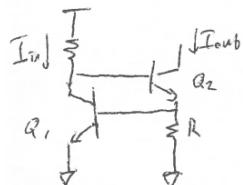

$$I_{out} = V_{be1}/R$$

$$= \frac{\phi_T}{R} I_n \frac{I_{in}}{I_{s1}}$$

$$\frac{\partial I_{out}}{\partial V_{cc}} = \frac{\phi_T}{R} \frac{I_n}{I_{in}} \cdot \frac{\partial V_{be1}}{\partial V_{cc}} \cdot \frac{1}{I_{s1}} \cdot \frac{\partial I_{in}}{\partial V_{cc}}$$

Note: pretty good vs V_{cc}




$$S = \frac{26 \text{ mV}}{300 \text{ mV}} = 3.7\%$$

$$S_{V_{cc}}^{I_{out}} = \frac{\phi_T}{R} \cdot \frac{1}{I_{in}} \cdot \frac{\partial I_{in}}{\partial V_{cc}} \cdot \frac{V_{cc}}{I_{out}} = \frac{\phi_T}{V_{be1, out}} \cdot S_{V_{cc}}^{I_{in}}$$

$$S_{V_{cc}}^{I_{out}} = \frac{V_{cc}}{I_{in}} \cdot \frac{\partial I_{in}}{\partial V_{cc}} = S_{V_{cc}}^{I_{in}}$$

- I like this one, easy to implement, easy to analyze, good vs. supply

Self-Biasing for Supply Insensitivity

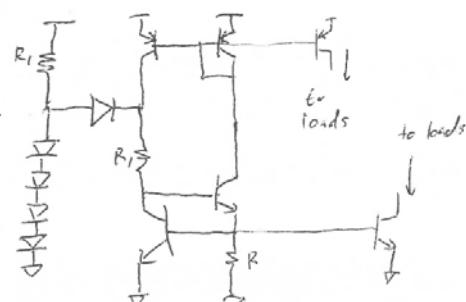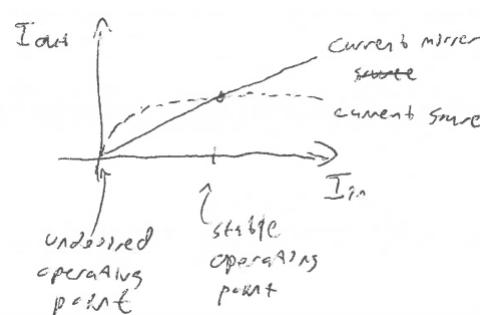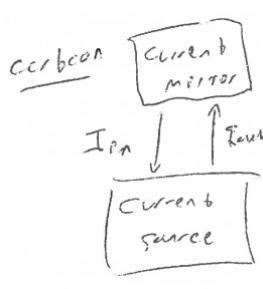


- Get away from dropping V_{cc} over R ... big sensitivity benefit
- Need startup circuit because undesired stable point (eg: 4Vbe vs. 3)
- Want startup circuits to shut themselves off (eg: rev. bias b/c of R_x)


Temperature Sensitivity

$$\text{TC}^{\text{Int}} = \frac{1}{I_{\text{out}}} \frac{\partial I_{\text{out}}}{\partial T}$$

- Model w/ temperature coefficient (sensitivity to temp, % change/deg)
- Big issues: Resistors (+1100 ppm/C), Vbe (-2mV/C), ϕ_T (3300 ppm/C)
- Cancel OK in Widlar, bad issue in Vbe, assorted self-bias tricks
- Sometimes need reference V constant w/ both supply and temp (eg: regulators) → Band Gap

Band Gap Reference

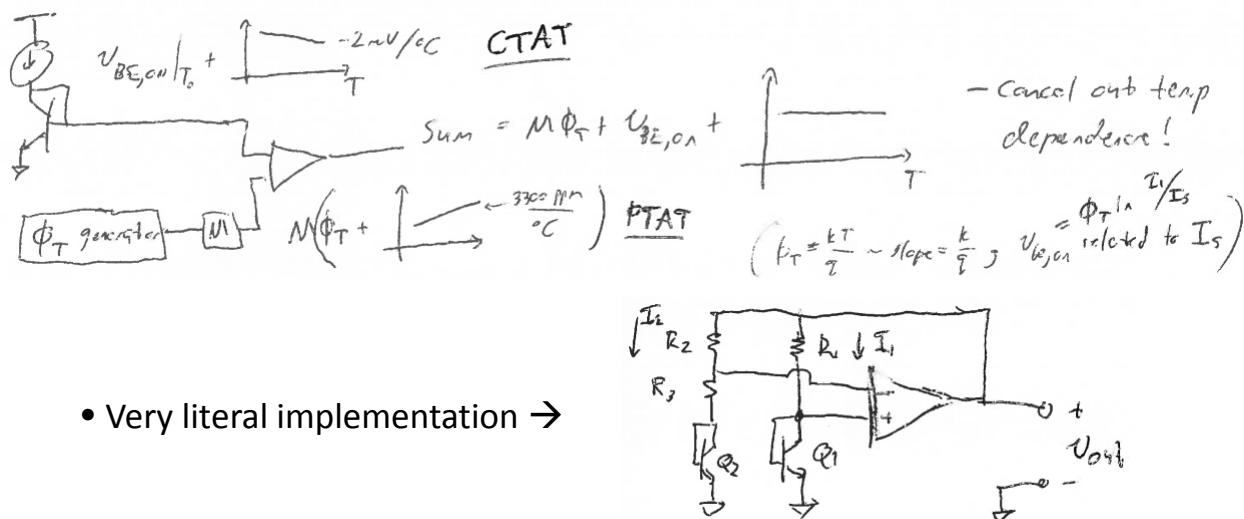

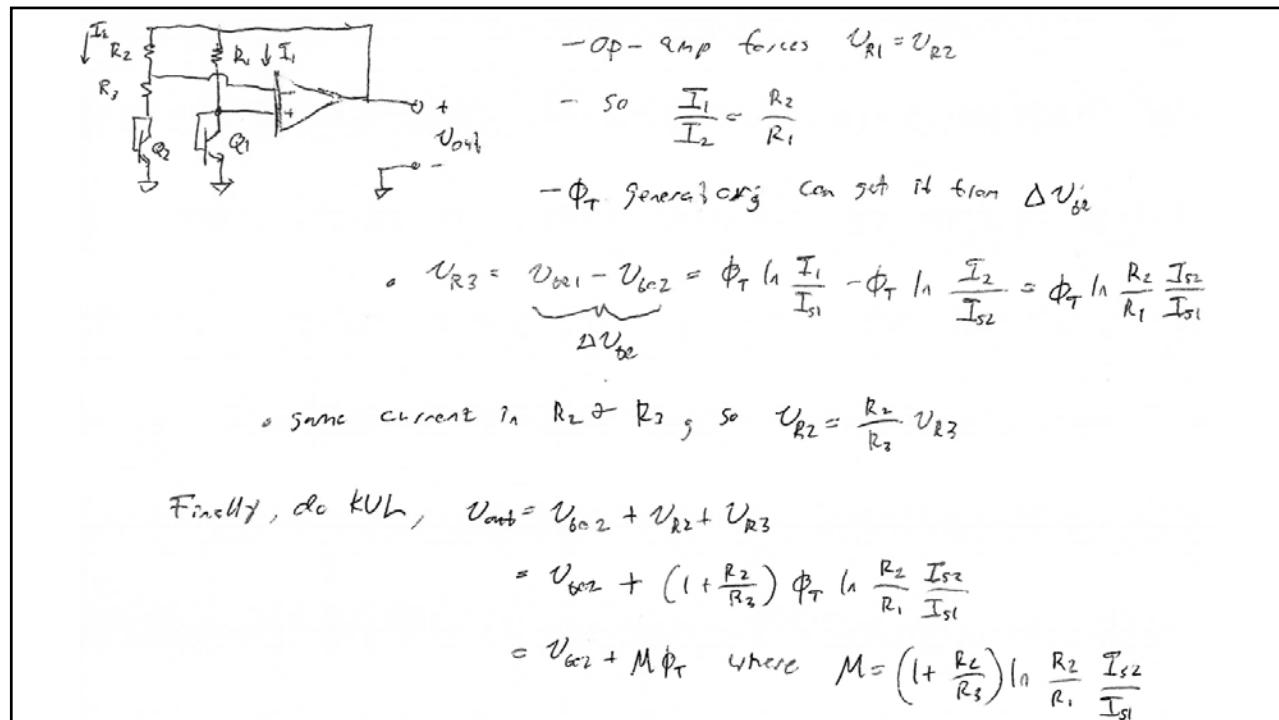

Band Gap Details

- $V_{OUT} = 1.26V$, about the band gap of silicon in eV (but unrelated)
- Temperature variation: parabolic, concave down, a few mV over 100C
- Implement in CMOS w/ parasitic substrate PNP

