

E151 Lecture 16

Matthew Spencer
Harvey Mudd College
ENGR151

Disclaimer



These are notes for Prof. Spencer to give the lecture, they were not intended as a reference for students. Students asked for them anyway, so I'm putting them up as a courtesy. Remember that they are not intended as a substitute for attending lecture.

PN Junctions Have Capacitance

→ physically came from growing & shrinking PN junction dep. region

$$\frac{1}{C_J} = \frac{C_{J0}}{\sqrt{1 - V_{bi}^2}}$$

Sometimes use cube root

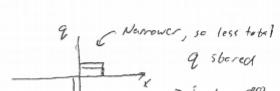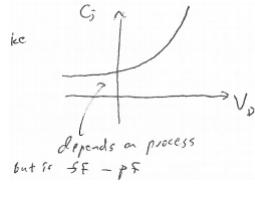

Narrower, so less total
q stored
→ implies $\frac{dq}{dv}$
 $\frac{dq}{dv}$ is a cap
(non-linear in this case)

Charge voltage, charge
total E is backed!


This can be included in small signal model

$$\frac{1}{C_J(v)} \approx \frac{1}{C_{J0}} e^{-\frac{q}{kT}}$$

- Change in width results in more "space charge"

Optional: Should I fwd/rev Bias Photodiodes?

— Photodiode design application

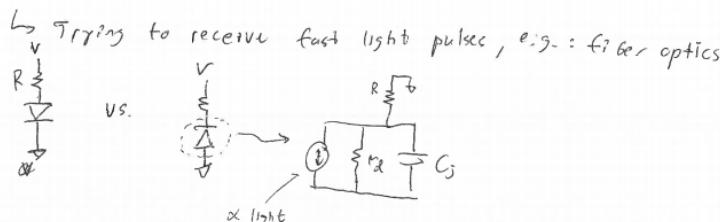


— You suff. find max light frequency & decide which config to use

$$Z = C_J (R_L \parallel R) \quad V_o = I \frac{R_L \parallel R}{1 + (R_L \parallel R) C_J s}$$

Want rev. bias → C_J smaller
→ R_L bigger b/c less current
→ No offset voltage b/c no current

doesn't matter
if large signal &
slow → see E80

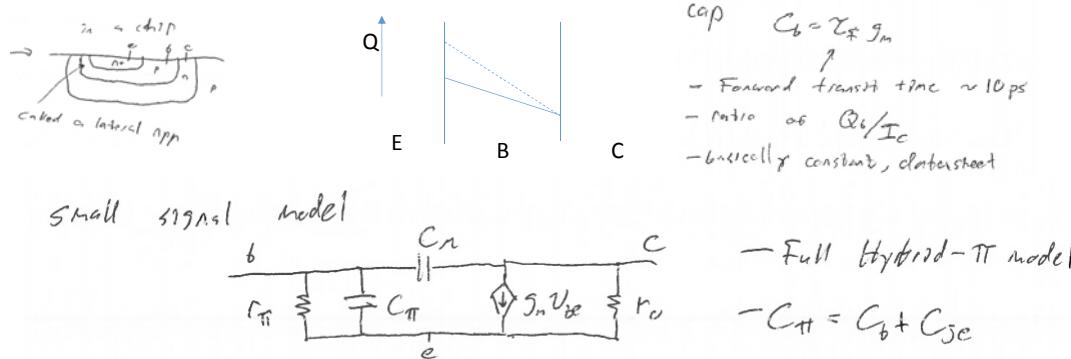BJTs Have Two PN Junctions + Base Current




- BE junction usually forward biased, BC usually reverse biased (small)
- Charge is in transit through the base all the time, need to supply more
 - Emitter charge goes to collector, so comes from base. Changing river level ...

Describe BJT Small Signal Speed Limit with fT

How fast can we go?

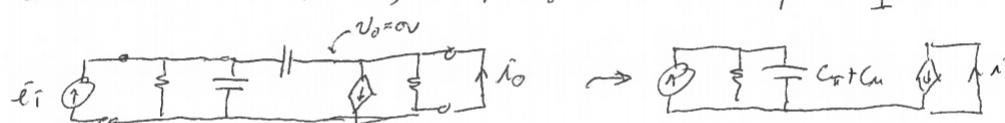- often measured w/ f_T , frequency where A_i drops to 1



$$V_o = g_m V_{be}$$

$$V_o = I_i \cdot \frac{R/(C_{be}+C_{bc})s}{R + 1/(C_{be}+C_{bc})s} = \frac{r_\pi}{1 + r_\pi(C_{be}+C_{bc})s}$$

$$\text{So } A_f = \frac{\beta}{1 + \beta \left(\frac{C_{be}+C_{bc}}{g_m} \right) s} \quad \Rightarrow f_T \approx \frac{1}{2\pi} \frac{g_m}{r_\pi + r_{in}}$$