

# E151 Lecture 20 – Differential Pairs

Matthew Spencer  
Harvey Mudd College  
ENGR151

## Disclaimer

These are notes for Prof. Spencer to give the lecture, they were not intended as a reference for students. Students asked for them anyway, so I'm putting them up as a courtesy. Remember that they are not intended as a substitute for attending lecture.


## What is Differential

- Op-amps:  $A(v_+ - v_-)$  ... how do we do that?
- Can represent any two signals as a common & differential mode
- Often useful b/c lots of noise (and distortion) is common mode

$$v_{dm} = v_1 - v_2 \quad \text{or} \quad v_{cm} = \frac{v_1 + v_2}{2} \quad \begin{matrix} \text{instantaneous} \\ \text{(average value)} \end{matrix}$$

(usually small signal)

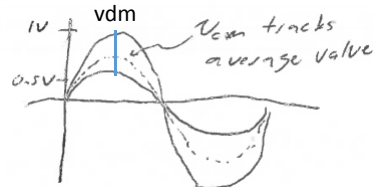
can express  $v_1 = v_{cm} + \frac{v_{dm}}{2}$  ( $v_2 = v_{cm} - \frac{v_{dm}}{2}$ )



- EG:  $v_1 = 1V \cdot \sin(\omega t)$   
 $v_2 = 0.5V \cdot \sin(\omega t)$


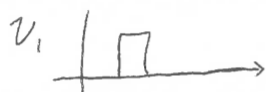
## Example of Differential Signals

You try ~~pseudo~~ <sup>pseudo</sup> - diff signaling ~ a common digital technique



- You draw  $v_{cm}$  &  $v_{dm}$


- from this com link

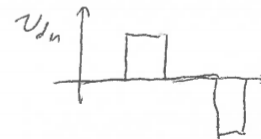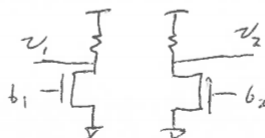

- This isn't called purely differential signaling b/c there is some CM
- How would you measure  $r_{in\_cm}$  of an amp?  $r_{in\_dm}$ ?
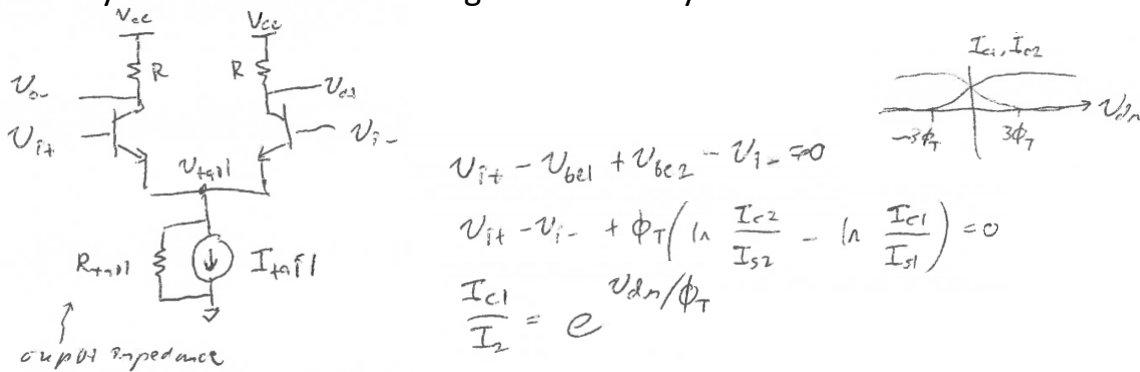
# Emitter Coupled Pair + Large Signal Behavior




- The most common circuit that amplifies DM but not CM is ECP
- Big picture: works by current steering ... DM does and CM doesn't
- Maybe a derivation later ... gets at linearity and other cool stuff


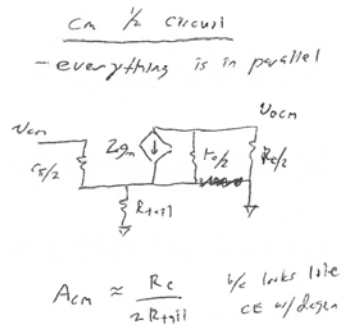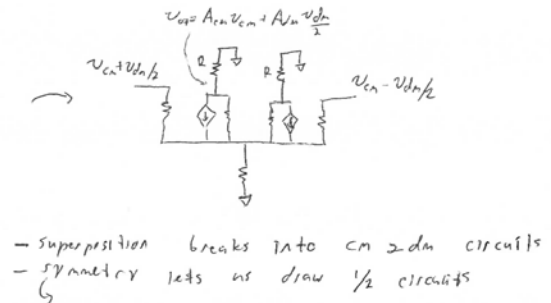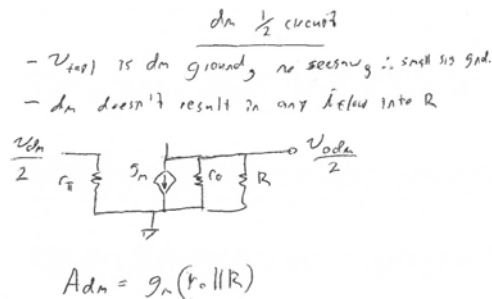
## 1/2 Circuit Analysis


- Analyze the small signal model w/ symmetry and superposition.

- dm vs cm parameters – av, rin, rout, etc.
- CMRR=adm/acm


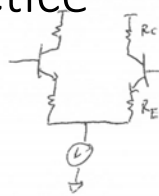
# 1/2 Circuit Practice

- Extends linear input range to  $I_{tail} * R_E$  (same as linear design)




- Draw  $d_m$  1/2 circuit & find  $A_v$





- looks like CE w/ degen  
 -  $A_v \approx -\frac{R_C}{R_E}$

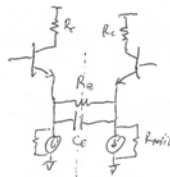- An equalizer, CTLE, gain boost at high freq.
- Note 1/2 ckt OCTC and SCTC



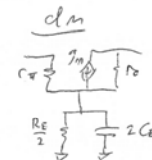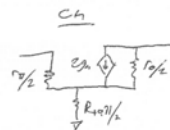- Find  $d_m$  &  $c_m$  1/2 ckt. Assume  $Q_1 = Q_2$  identical



An equalizer, CTLE, experiences gain boost & we'll see why

-  $R_E$  &  $C_E$  shunted by tail nodes @ same voltage

- differential ground in middle of  $R_E$ , can't be shunt  
 - Parallel Impedance  $\rightarrow \frac{R_E}{2}, 2C_E$