

E151 Lecture 24 – Feedback in Amplifiers

Matthew Spencer
Harvey Mudd College
ENGR151

Disclaimer

These are notes for Prof. Spencer to give the lecture, they were not intended as a reference for students. Students asked for them anyway, so I'm putting them up as a courtesy. Remember that they are not intended as a substitute for attending lecture.

Lab Debrief


- Base current supply for class AB can limit swing
- 100 ohms in class AB is for r_{in} , bias branch design affects it
- Efficiency very low because load is non-optimal: can't get through cap
- Distortion is especially audible in audio

Why Feedback?


- Risk of stability is bad! What do we get from this?
- Linearity & offset reduction ← not going over it b/c hard to draw
- Repeatable gain
- Input/output impedance modulation
- (This can work w/ single ended amps instead of diff or within a stage)
 - Single ended amps → Miller example
 - Within a stage → EF example (optional, if time)

→ Fwd. path / $(1 + \beta)$ is magic!

$$\frac{v_o}{v_i} = \frac{r_{o||R_E} (g_m + 1/r_{\pi})}{1 + r_{o||R_E} (g_m + 1/r_{\pi})} \quad \frac{i_c}{v_i} = \frac{1/r_{\pi}}{1 + r_{o||R_E} (g_m + 1/r_{\pi})}$$

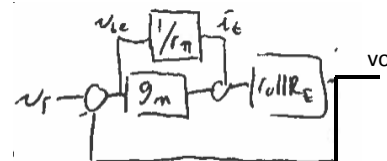

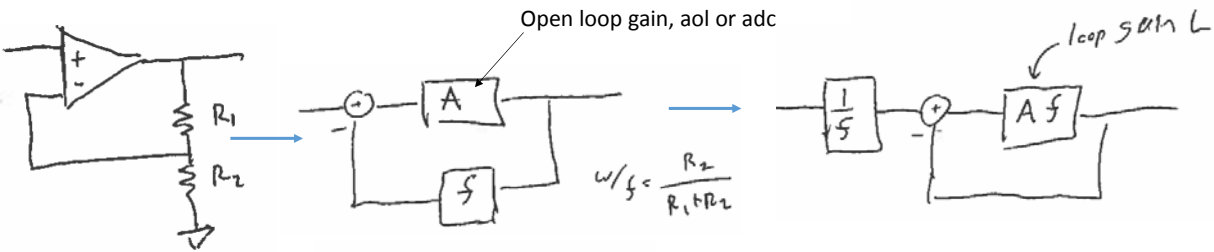Example of Repeatable Gain (also Static Error)



Closed loop gain, acl


$$\frac{V_o}{V_i} = \frac{1}{s} \cdot \frac{L}{1+L}$$

target gain set only by R

causes steady state error $\epsilon \approx 1/L$

$(1 - \frac{1}{1+L})$


Examples of Impedance Modulation

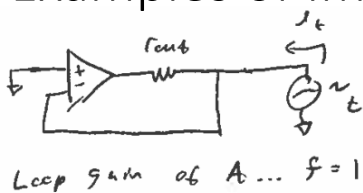

$$i_t = \frac{V_t - (-AV_t)}{R_{out}}$$

$$R_{out, eff} = \frac{V_t}{i_t} = \frac{R_{out}}{1+A}$$

lowered by loop gain!

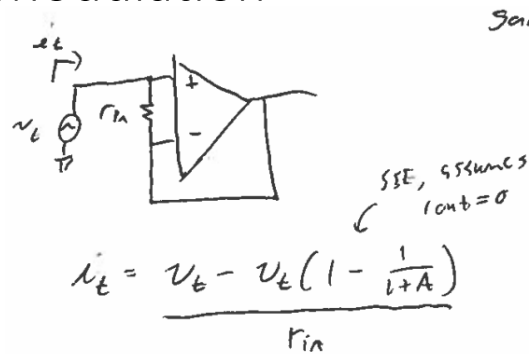

$$i_t = \frac{V_t - V_t(1 - \frac{1}{1+A})}{R_{in}}$$

$$R_{in, eff} = \frac{V_t}{i_t} = R_{in}(1+A)$$


- r_{in} or r_{out} can be raised or lowered by loop gain
- Recognize raised/lowered by looking at boosted/reduced swing

What's Stability?

- Definition of stability
 - Circuit designers usually use BIBO, but breaks down for large signals
 - Lyapunov always works, but it's a bit out of scope for most designs
 - I like spectral content for bounded inputs –only have output f where input f
- Instability comes from RHP poles in the in closed loop Xfer function
 - That's the same as $1+L(s)=0$
 - Often simplify analysis to look at $L(j\omega)=-1$ (mag=1, phase=-180) \rightarrow Nyquist/PM
- What about the instability we've seen? Our amps have LHP poles?
 - Undesired in \rightarrow out coupling: breadboard or cabling cap, power supply
 - Bypass cap is important for suppressing supply coupling

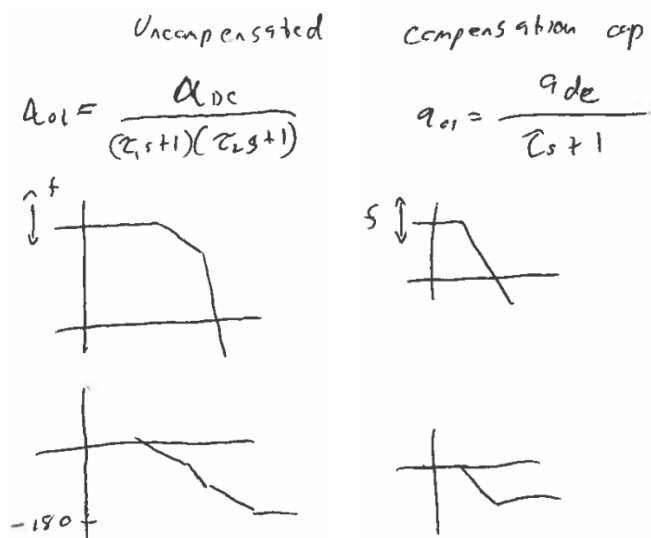
Examples of Using Phase Margin

- Uncompensated op-amp often has poor phase margin
- Compensation cap \rightarrow 90° PM
- 2nd pole in comp amp pushed to higher f by $1/g_m$, so omit
- Least stable with $f=1$, more stable with small f (big a_{cl})
- PM= 45° if 2nd pole located at crossover \rightarrow reasonable Q



Origin of Gain-Bandwidth Product

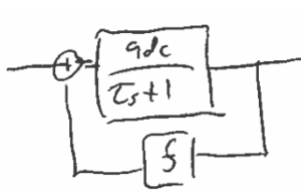- Gain-bandwidth product is not fundamental to op-amps
- GBW originates with dominant pole compensation & big aol



$$\begin{aligned} \frac{v_o}{v_i} &= \frac{a_{dc}/(s+1)}{1 + a_{dc}s/(s+1)} \\ &= \frac{a_{dc}}{s + \frac{1}{\tau} + a_{dc}s} \\ &= \frac{1}{s} \cdot \frac{a_{dc}}{1 + a_{dc}\tau s} = \frac{1}{1 + \frac{\tau}{1 + a_{dc}\tau s}} \end{aligned}$$

$$G \cdot BW \approx \frac{1}{s} \cdot \frac{1 + a_{dc}\tau s}{\tau} \approx \frac{a_{dc}}{\tau}$$

Fails if $a_{dc}\tau s \not\gg 1$
or if not dominant pole