

E151 Lecture 25 – Oscillators

Matthew Spencer
Harvey Mudd College
ENGR151

Disclaimer

These are notes for Prof. Spencer to give the lecture, they were not intended as a reference for students. Students asked for them anyway, so I'm putting them up as a courtesy. Remember that they are not intended as a substitute for attending lecture.

Quiz Follow Up Mini-Review

- Output and input swing calculations may be rusty, esp class B/AB
- Bandwidth and/or transfer function estimation is a good skill
- Natural followup would be to use Xfer function to ask about stability
- DC coupling didn't require a level shift here, but PNP better
- Must degenerate CE stage because emitter bypass doesn't work at DC
- r_{in} of the class AB is small ... careful of loading

Final Exam Next Friday

- Logistics: 3 hours from 9-12 on 5/3 in B445, B454 and B470
- Coverage
 - Material up to today covered, some stuff on review counts
 - Emphasis on back $\frac{1}{2}$ of class, but analysis from front $\frac{1}{2}$ matters
 - Special topics lecture just for fun (no quiz) ~ PLL, power converters, devices ...
- Resources
 - Allowed two crib sheets (8.5x11 2-sided) and otherwise no resources
 - Use them well: back $\frac{1}{2}$ of class has many odds and ends to note down
 - I've posted last year's final & solutions, also blank quizzes.
 - Honor code violation to share these review materials in future
- Important that you attend review ... assessment & feedback there too


Stability Analysis Practice

- Consider an uncompensated amplifier with two poles at $p_1=1\text{MHz}$ and $p_2=10\text{MHz}$. What is the maximum open loop gain the amplifier can have and still be unity gain stable?
- Answer:
 - reach 180deg phase at 100MHz.
 - Have 1 decade (1MHz-10MHz) of 20dB rolloff
 - Have 1 decade (10MHz-100MHz) of 40dB rolloff
 - Therefore max stable gain is 60dB \rightarrow 1000

Knowing Stability Let's us Design Instability


- Oscillate if closed loop poles on $j\omega$ axis \rightarrow design $L(j\omega)=-1$ (in -ve fb)
- Can this oscillate? (Note that all R and C are the same in each stage)

Phase shift oscillator

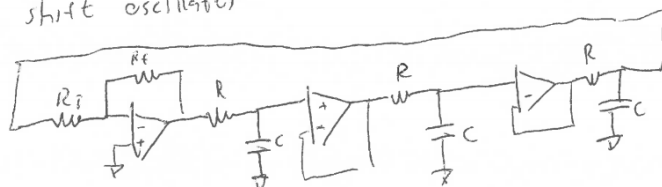

Yes!
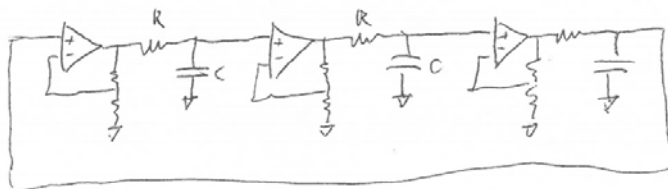
$$L(s) = + \frac{R_f}{R_i} \frac{1}{(RCs+1)^3} \quad \begin{matrix} \text{in -ve} \\ \text{fb} \\ (-R_f/R_i \text{ is +ve}) \end{matrix}$$



No!



$$L(s) = \frac{\left(1 + \frac{R_1}{R_2}\right)^3}{(RCs+1)^3} \quad \text{BUT evaluate } \frac{L(s)}{1-L(s)} \text{ in +fb}$$

Deeper Dive into Phase Shift Oscillator


- Frequency of Oscillation
 - Oscillate where $L(j\omega) = -1$ (phase=180) and total phase = $3 \cdot \text{atan}(\omega RC)$
 - In other words: need 60 deg of phase from each pole
 - $\text{atan}(\sqrt{3}) = 60 \rightarrow \omega_{osc} = \frac{\sqrt{3}}{RC}$ (Recall 30 60 90 triangle $\rightarrow x, \sqrt{3}x, 2x$)
- Required gain for oscillation
 - Oscillate where $L(j\omega) = -1$ (mag = 1)
 - $\frac{R_f}{R_i} \left| \frac{1}{\sqrt{\left(\frac{RC\sqrt{3}}{RC}\right)^2 + 1^2}} \right|^3 = 1 \rightarrow \frac{R_f}{R_i} = 8$
- Finding frequency of osc and loop gain are standard osc problems

Colpitts Oscillator

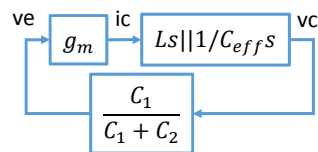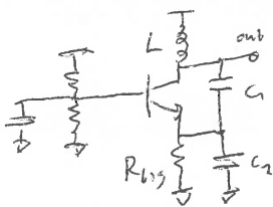- Many similar LC oscillator varieties: Pierce, Clapp, Hartley, etc ...
- Colpitts very easy to implement, so much so you do it by accident
- Capacitive divider feedback from b to e \rightarrow eg: $C_{pi} + \text{big } C_l + \text{long wire}$
- Can Analyze w/ 1 port impedance too



OR

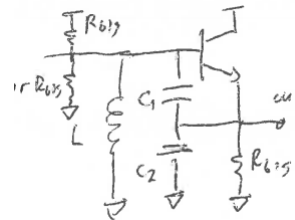

Basically the same, trickier analysis, inductor is wire from last stage

$$C_{eff} = \frac{C_1 C_2}{C_1 + C_2}, \omega_{osc} = \frac{1}{\sqrt{L C_{eff}}}, \frac{C_1}{C_1 + C_2} = \frac{1}{g_m}$$

Describing Functions

- All practical amplifiers are non-linear
- Linear 2 pole systems respond forever in response to a kick
- Real oscillators poles start RHP then non-linearity reduces loop gain
- Capture w/ describing functions → useful to evaluate osc. Spectra
 - Map gain vs. input amplitude of non-linearity for fundamental & harmonics
 - Assume system is essentially low pass so that only one tone, ω , matters
 - Find amplitude at which loop gain satisfies $L(j\omega)=-1$, could vary ω / frequency
- Describing function is $H(A,j\omega)$ from non-linear $F(x)$ w/ $x=A*\sin(j\omega t)$