

E151 Lecture 26 – Review

Matthew Spencer
Harvey Mudd College
ENGR151

Disclaimer

These are notes for Prof. Spencer to give the lecture, they were not intended as a reference for students. Students asked for them anyway, so I'm putting them up as a courtesy. Remember that they are not intended as a substitute for attending lecture.



Topics Since the Midterm



- Dynamics
 - Caps in BJT model
 - Exact CE Xfer function
 - Miller effect & approximation
 - OCTC & Cascodes
 - Step Responses
- Differential Analysis
 - CM and DM signals
 - CM and DM $\frac{1}{2}$ Circuits
 - CMRR and PSRR
 - Offsets
- References
 - Sensitivity analysis
 - Examples
- Output Stages
 - Large signal analysis
 - Examples
- Op-amp design
 - Basics: 3 stages, etc.
 - Design specs: I_B , V_{ICM} , ...
 - Compensation & Xfer fn.
- Stability & Feedback Effects



Topics before the Midterm (Digging Deep)



- Thevenin review and basics of dynamics
- Amplifier model and input/output impedance
- Diode and BJT equations, survey of physics, small signal models
- Going from small signal models to amplifier models
- Examples of single-stage amplifiers: CE, CB, EF, Cascode
- Multistage analysis, Current Mirrors, Active Loads

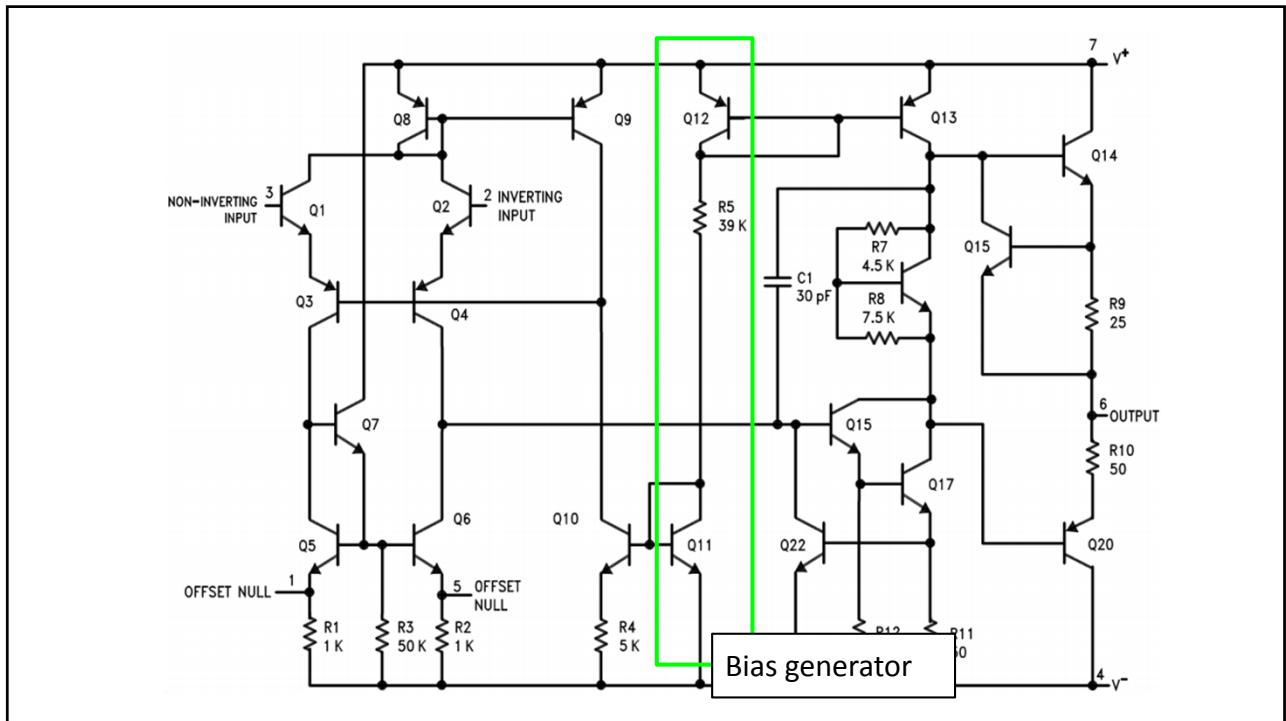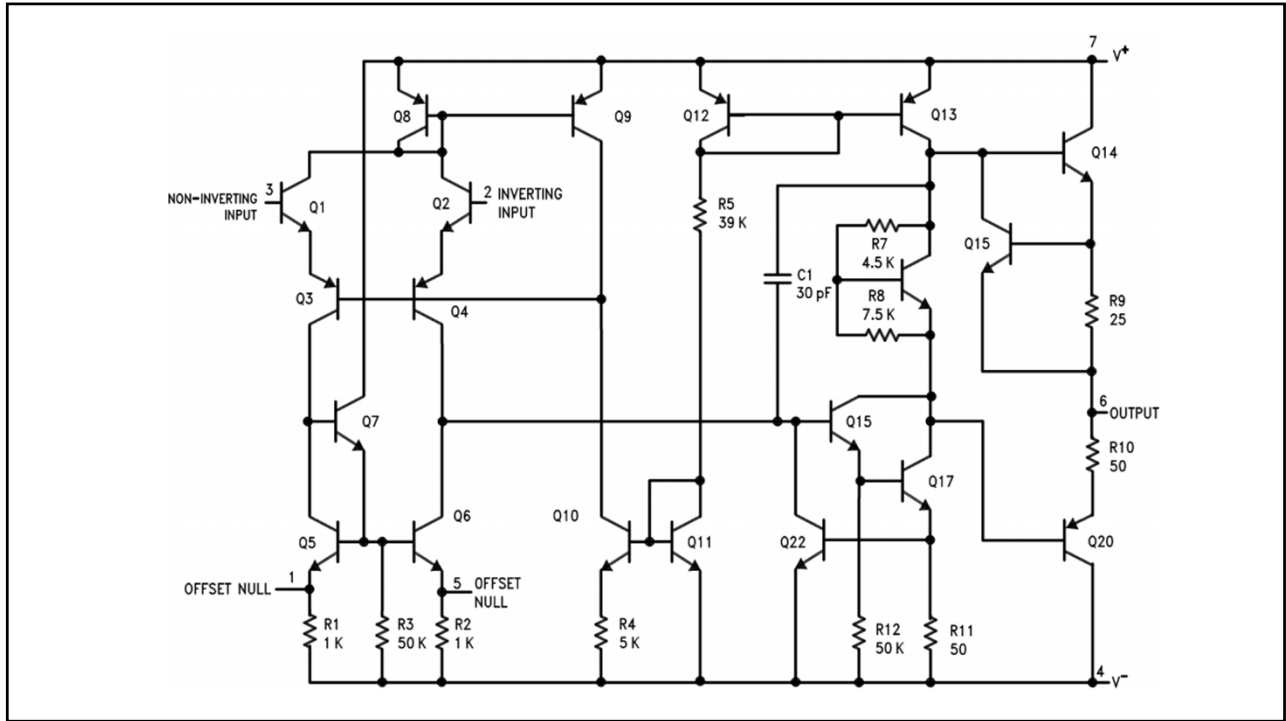- All of this together lets us understand real op-amps!



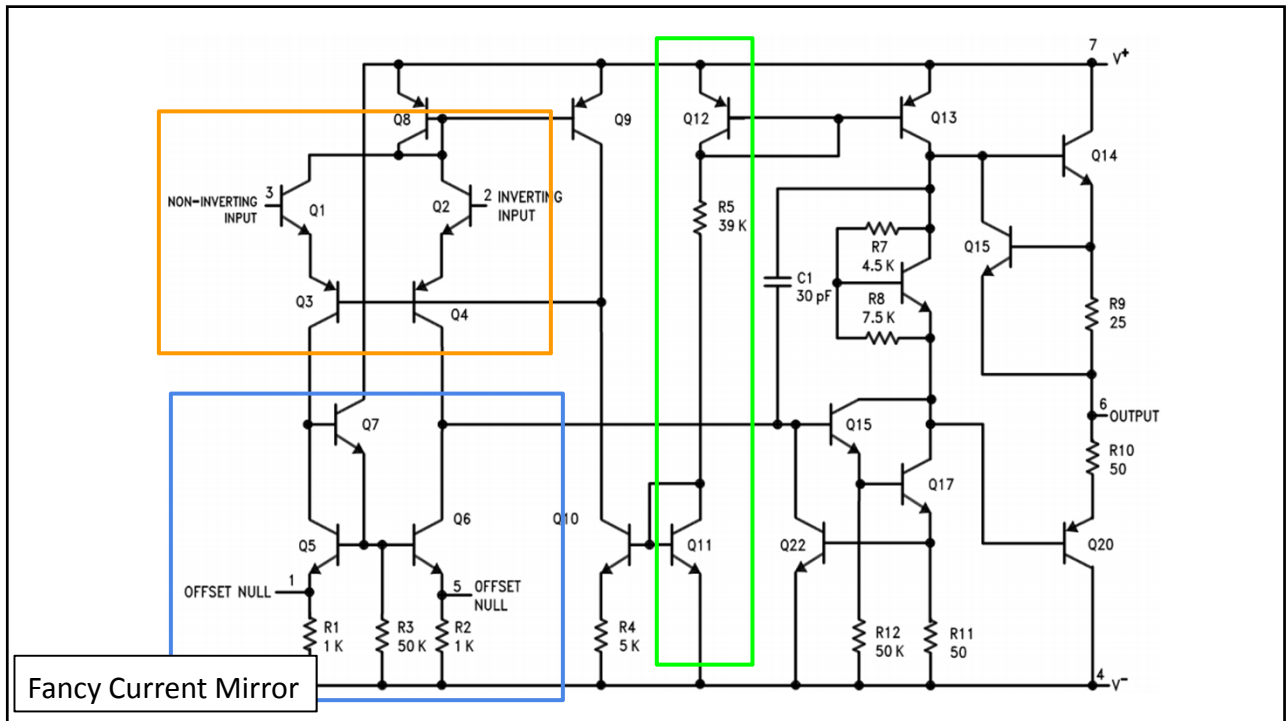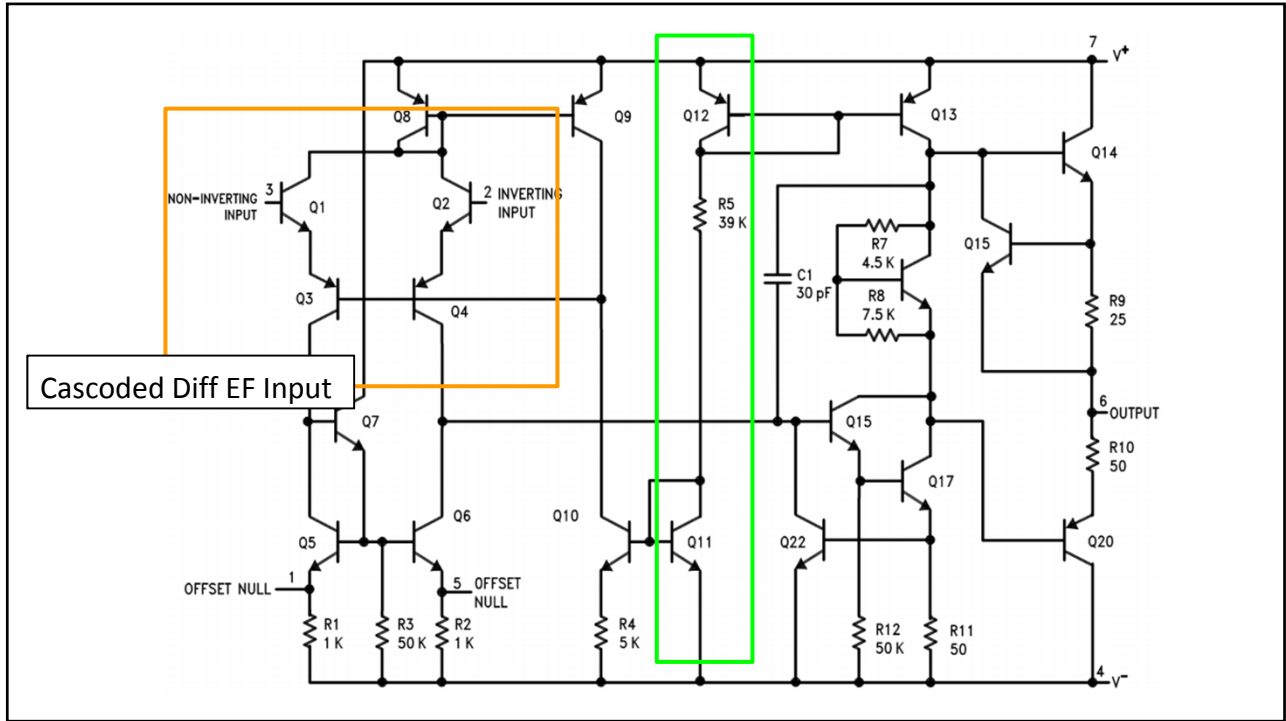

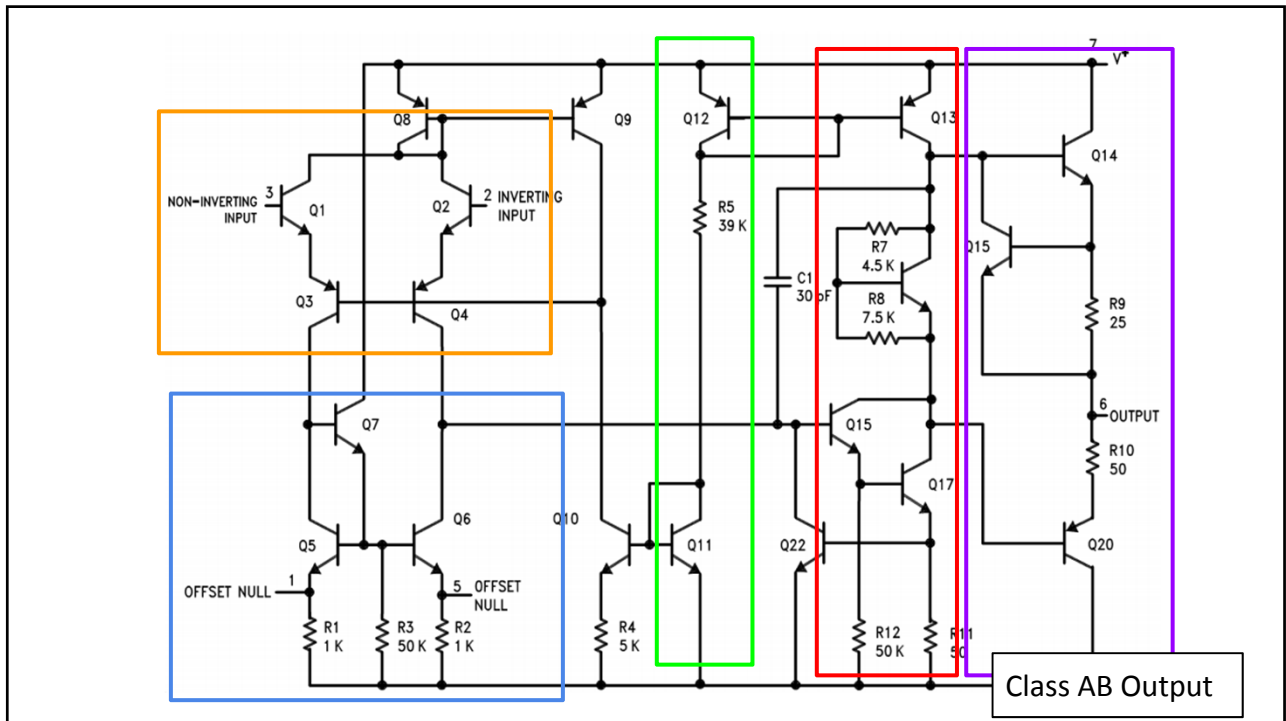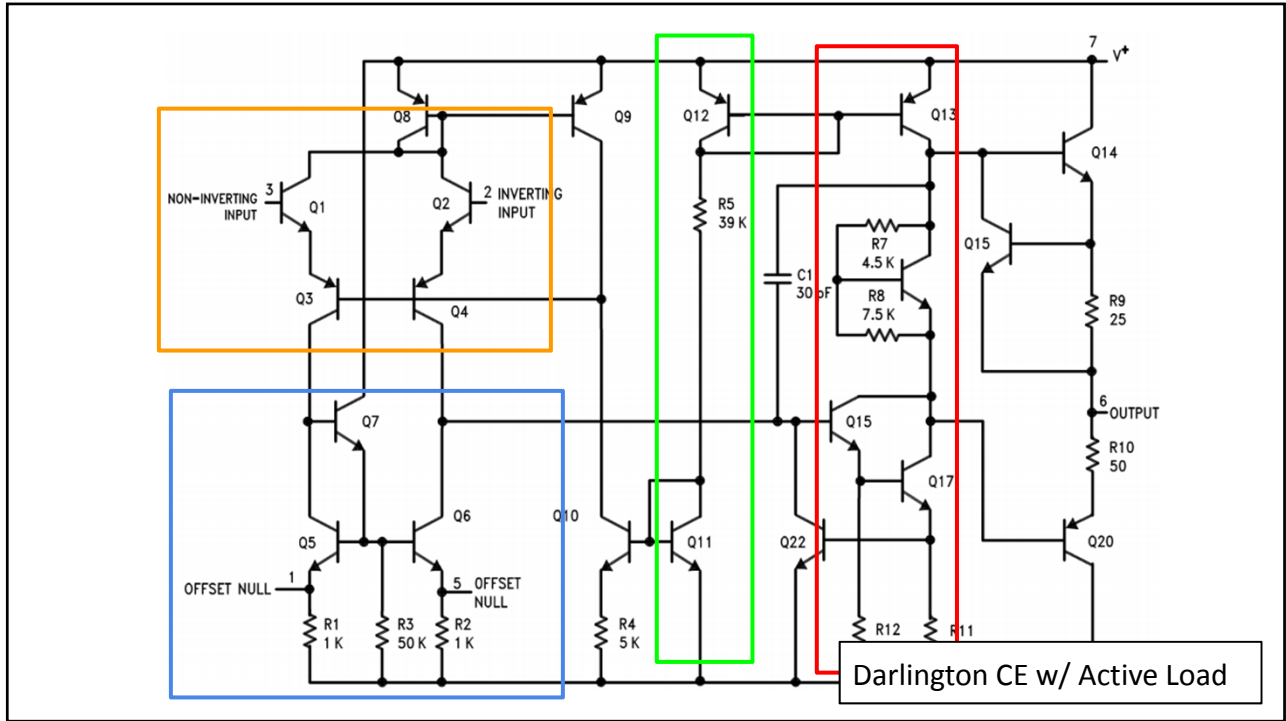

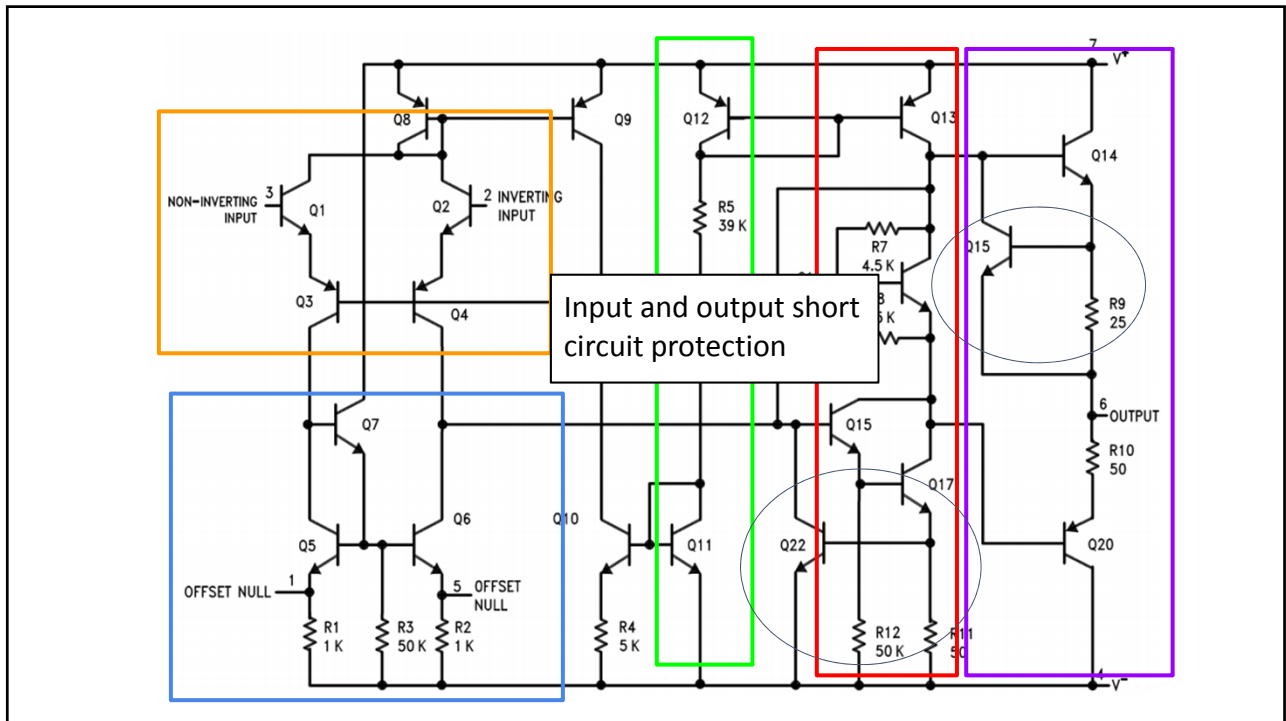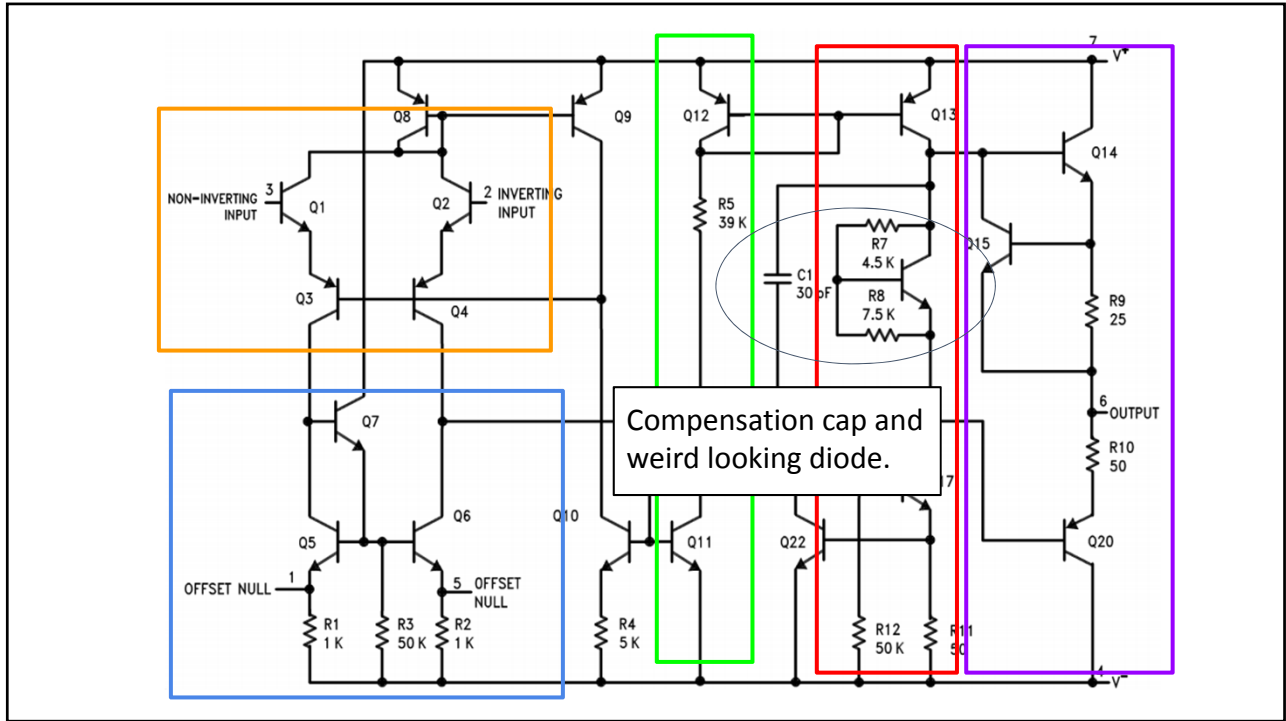

Analyze Mirror Loaded Emitter Coupled Pair

- $r_{in,dm}$ unaffected by load, whew. Both sides help $a_{v,dm}$.
- r_o is a fundamentally single ended quantity ... involved. Anecdote.

