

- What are they
- Brainstorm clock replication
 - Vs. DLL & FLL

- Basic Model
- PD
 - CP
 - LF
 - VCO
 - Linearization (of a very nonlinear thing)



- Phase as a signal
- $\phi = \int \omega dt$
 - accumulation
 - pictures of controlling ϕ w/ f

- Implementing
- mult PD
 - XOR PD
 - J/K PD
 - ring osc.
 - LC osc.
 - dividers

- Control
- Jitter
 - PLL as filter
 - N and loop gain

How do we make a clock! → oscillators

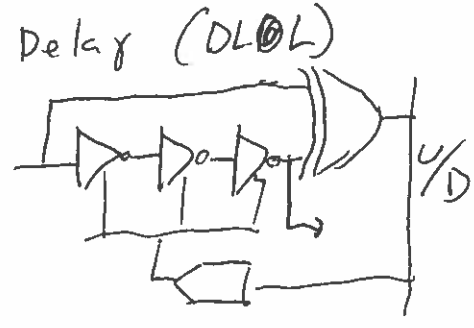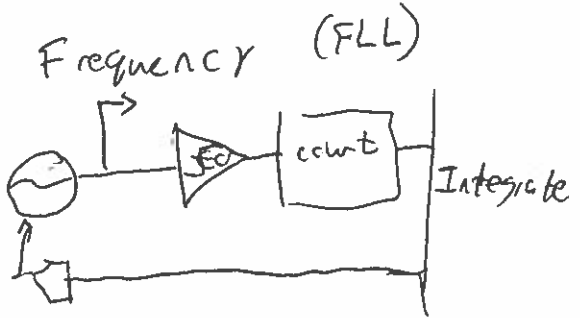If we have a clock, how do we replicate it? → PLL





But we want phase & freq locked simultaneously


- Do so w/ a PLL --- many possible implementations (highly digital)
- interesting b/c linear models work in v. non-linear

Big trick: control ϕ as a variable

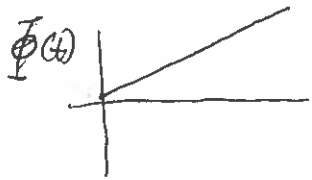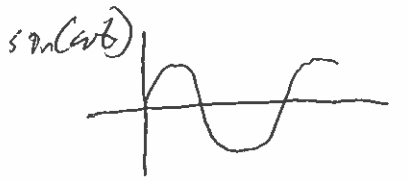- Interpret $\sin(\omega(t)t)$ as $\sin(\Phi(t))$



simple example

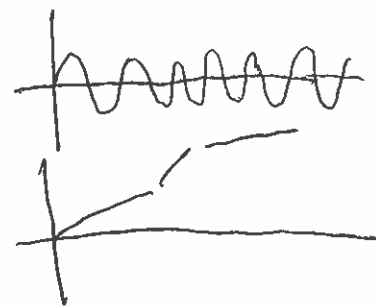


FSK example

Back & forth to ω :


$$\Phi(t) = \int \omega(t) dt$$

$$\omega(t) = \frac{d\Phi(t)}{dt} + \phi_0$$

- Coarse way to make it:

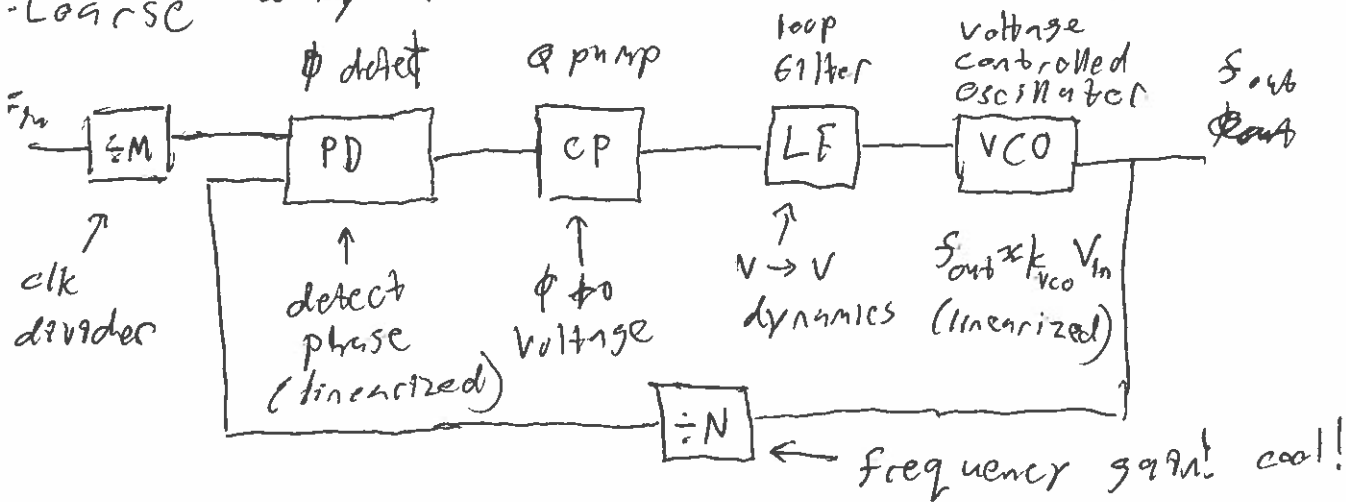


Lends itself to a linear model

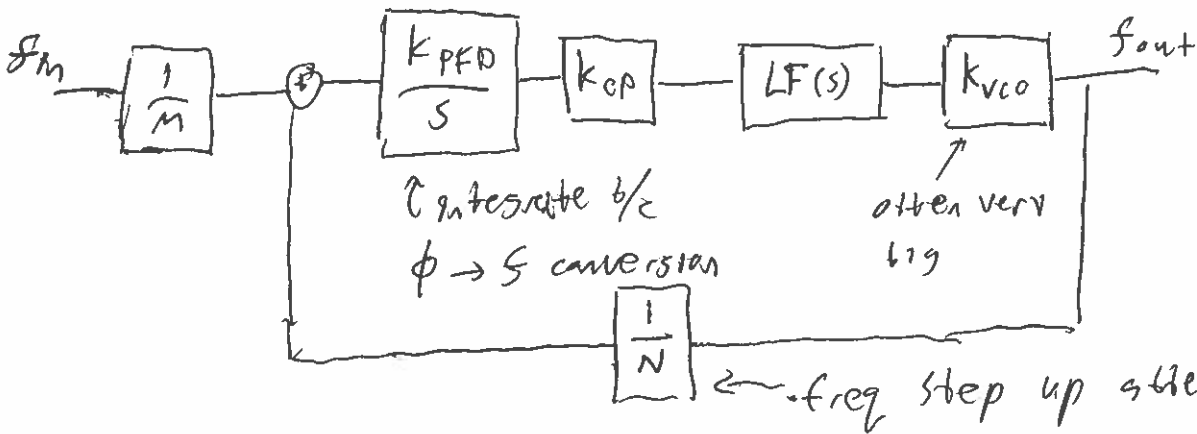


- Big BW & stability implications (eg: can it respond to input noise)
- cleanup/filter

Implementation:

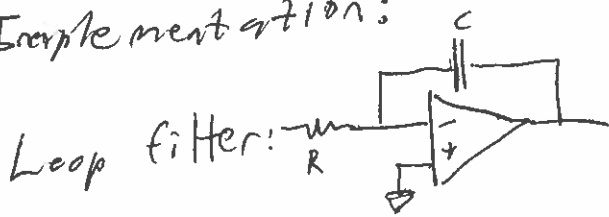

- Voltage to voltage, we know that
- Often GBW sensitive

VCO:

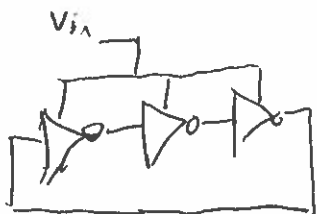


- big K_{VCO}
- non-linear
- noisy (jitter)
- quad. out
- easy to build
- Ring Oscillator



- LC tank filters
- ϕ noise
- power hog & touchy
- Varactors hard

PD + CP:

Analog multiplier

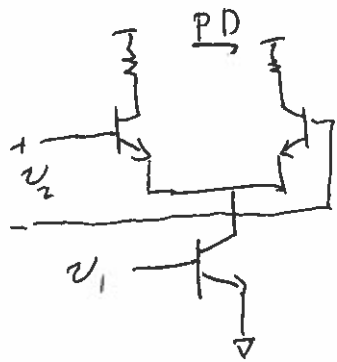

CP

none

editorial

$$V_o = V_1 \sin(\omega t + \phi) \cdot V_2 \sin(\omega t)$$


=

- touchy in a lot of way

XOR



pulse width $\approx \Delta\phi$

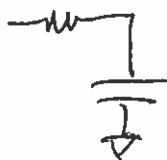



Make into avg. value

- slow 6/c LPF

- ripple

- no direction info

JK Flop

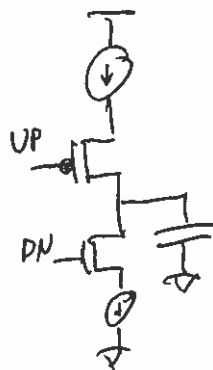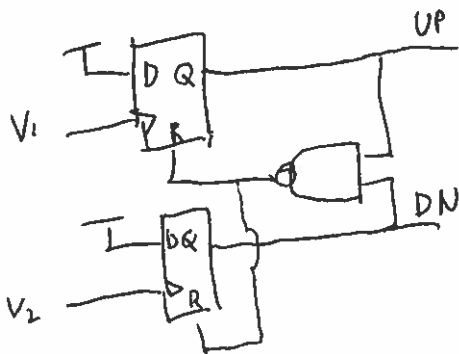

- commonly used

- prone to misastd

Divider:

Just use a digital counter