

E151 Lecture 2 – Thevenin and 2 Port Hacks


Matthew Spencer
Harvey Mudd College
ENGR151

Disclaimer


These are note for Prof. Spencer to give the lecture, they were not intended as a reference for students. Students asked for them anyway, so I'm putting them up as a courtesy. Remember that they are not intended as a substitute for lecture.

Thevenin

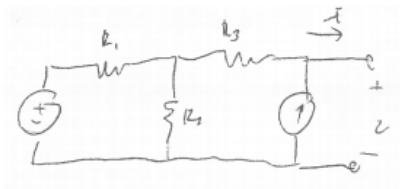
- Connect circuits to the world at ports, model w/ 1 line b/c linear
- Note that Norton is literally slope intercept form of line



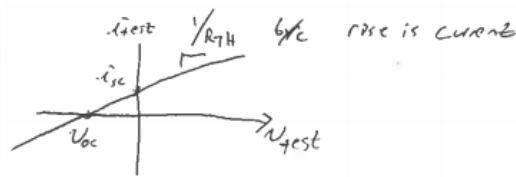what is $i-v$ relation across ports?
 - must be linear
 - model may have DC value
 - model w/ $i_{sc} + r_{th}$



Norton is V-I curve instead of I-V

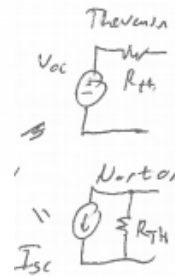


Example Find Thevenin Impedance 2 Ways

- Options: v_{oc}/i_{sc} (slope), simplify network (test source / derivative)
- Then I show 3rd way: test sources (derivative of circuit)

① $v_{oc} = v_3 = I(R_3 + R_1 || R_2) + V \frac{R_2}{R_1 + R_2}$ by super pos $i_{sc} = I + \frac{V}{R_3 + R_1 || R_2} \cdot \frac{R_2}{R_1 + R_2}$

② $R_{TH} = R_3 + R_1 || R_2$ w/ shorted & opened sources

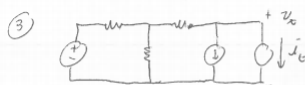

$v_{test} = V \frac{R_2}{R_1 + R_2} + (I + i_{test})(R_3 + R_1 || R_2)$

$\frac{dv_{test}}{di_{test}} = R_3 + R_1 || R_2$ (eg to small signal model, setting v_{test} to 0)

(super handy for ignoring tricky circuit details!)


- can pick current or voltage test
- ask how much i or v out (find dv/di)
- i easy here b/c $||$ w/ I
- MUST use this technique of dept. sig.

MUST SHUT OFF SOURCES for di/dv . (Small wiggles go to die)

Odds and Ends

- Non-resistive impedances?

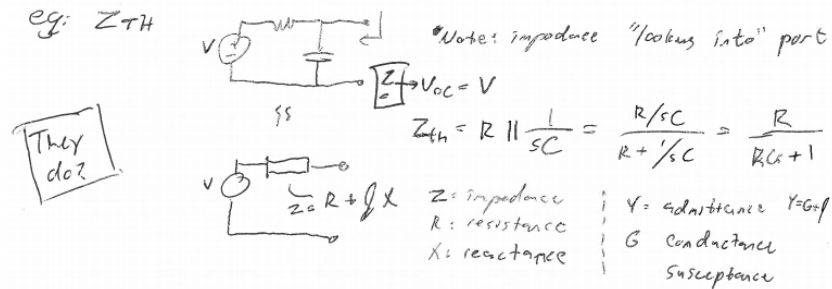- Just fine, have a Z_{th} (general case) rather than R_{th} (like homework)



- What if no sources? In quadrants 1&4, dissipative, called "passive"

Dynamics Review – Initial and Final Values

- What do we want to know dynamics responses to?

- Sines \rightarrow transfer functions work great
- Steps \rightarrow ... time domain, need some trick
- Ramps \rightarrow integrated steps, next
- Exponentials \rightarrow basically ramps, next

- We can get time domain responses from xfer fn with IVT/FVT


- IVT

$$\lim_{t \rightarrow 0} f(t) = \lim_{s \rightarrow \infty} sF(s) \quad \text{- FVT} \quad \lim_{t \rightarrow \infty} f(t) = \lim_{s \rightarrow 0} F(s)$$

Don't forget that LT $F(s)$ implicitly involves initial condition, so the IC is added to IVT/FVT value

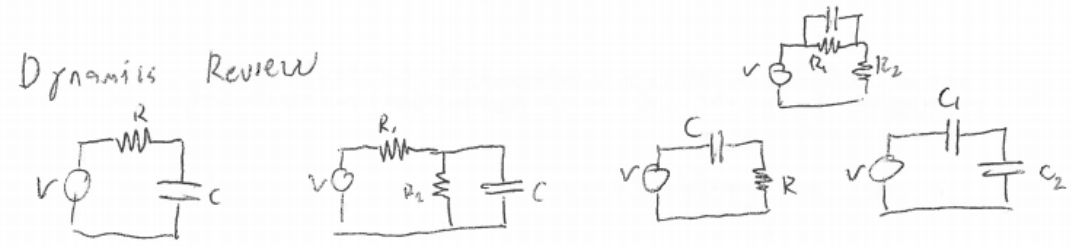
Exercise: sketch vo step for these circuits

- Break room into groups and each group does 1, I do 1st & 2nd ?



- Main points: IVT/FVT practice, tau is same in t and f, AC vs. DC ckt. To find Vi and Vf, Thevenize from cap to find tau (if only 1 cap)
- Original solutions on next few pages, often drop some details

Exercise answers

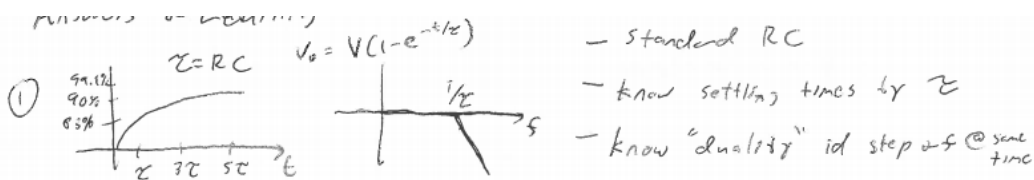

② $V_{DC} = \frac{R_2}{R_1 + R_2} V$
 $V_{AC} = 0V$
 $\tau = C \cdot R_{th} = C \cdot \frac{R_1 R_2}{R_1 + R_2}$
 $\hookrightarrow v_o = \frac{R_2}{R_1 + R_2} V (1 - e^{-t/\tau})$

or $v_o = \frac{R_2 \parallel \frac{1}{Cs}}{R_1 + R_2 \parallel \frac{1}{Cs}}$
 $= \frac{R_2 / Cs}{R_1(R_2 + 1/Cs) + R_2 / Cs}$
 $= \frac{R_2}{R_1 R_2 Cs + R_1 + R_2}$
 $= \frac{R_2}{R_1 + R_2} \cdot \frac{1}{R_{th} Cs + 1}$


- can thevenize storage elements to find τ
 - can fall back on impedance if stuck

Non-interacting!
 - separate DC & AC behavior!

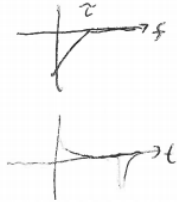Exercise Answers

⑤ $V_o = \frac{\sqrt{\omega} C_2}{\sqrt{\omega} C_1 + \sqrt{\omega} C_2} = \frac{C_1}{C_1 + C_2}$

③ $V_{BE} = 0V$
 $V_{AC} = V$
 $\tau = RC$
 $V_o = V e^{-t/RC}$




- Value on far side of cap already has an "average" value
- AC coupled signals are transient
- ↳ interesting behavior turning bursts on & off

④ $V_{DC} = \frac{R_2}{R_1 + R_2} V$
 $V_{AC} = V$
 $\tau = R_1 R_2 \cdot C$
 $V_o = V \left(\frac{R_1}{R_1 + R_2} + \frac{R_2}{R_1 + R_2} e^{-t/\tau} \right)$

$$\frac{R_2}{R_1 + R_2 + sRC}$$
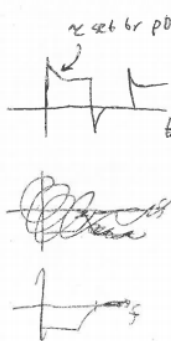
$$\frac{R_2}{R_1 R_2} \frac{1 + R_1 C s}{1 + \frac{R_1 R_2}{R_1 R_2} C s}$$



- τ set by pole, not zero
- capacitive feedthrough
- ac part is transient
- parallel forward paths means oblique zero
- ↳ change from gain A to gain B
- Change in gain & change in f
- Intek is still 1st order



- capacitive divider
- output is DC floating but will stay to coupling or input (scope probe)
- frequency independent!