

# E151 Lecture 8

## Amplifier Design and Voltage Swing

Matthew Spencer  
Harvey Mudd College  
ENGR151

### Disclaimer

These are notes for Prof. Spencer to give the lecture, they were not intended as a reference for students. Students asked for them anyway, so I'm putting them up as a courtesy. Remember that they are not intended as a substitute for attending lecture.

# Built an Amplifier, Biasing Improvements

- Get to  $a_v$ ,  $r_{in}$  and  $r_{out}$  indirectly
- Invoke voltage swing with final example
- We have been building up a sense of design specs for amps

$I_C = \beta I_B (e^{V_{be}/kT} - 1)$   
 $V_{ce} = 0 - g_m V_i (r_o || R_L)$   
 $I_{CQ} = \frac{V_{BB} - V_{BE,ON}}{R_B}$   
 $V_o = -g_m (r_o || R_L) \cdot \frac{R_B || r_{\pi}}{R_B + R_B || r_{\pi}}$   
 Bypass ground collector  $\rightarrow$  get same gain, changes?

# Design Specifications for Amplifiers


- Suggests a generalized 2 port model for amplifiers ... no Z12, so easy

Sometimes care about  $a_i$   $d_{io}/d_{ii}$  | out short = beta


Symbol	Name	Calc
$a_v$	Voltage gain	$d_{vo}/d_{vi}$   out open
$r_{in}$	Input resistance	$d_{ii}/d_{vi}$   out load
$r_{out}$	Output resistance	$d_{io}/d_{vo}$   in load
$V_{SW}$	Voltage swing	$V_{O\_MAX} - V_{O\_MIN}$
$I_{IN}$	Input bias current	Large signal $I_{IN}$
$f_{low}$	Low f -3dB corner	Measure for now

Fall straight out of small signal, **Must measure with power on!** (small sig. open/short, not big)

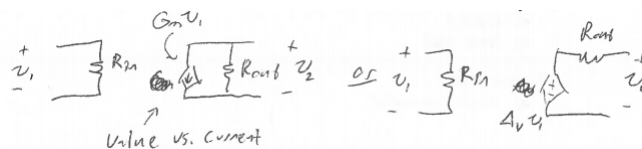Must find nominal  $V_O$  and figure out allowed excursions  $2 * \min(V_{O\_MAX} - V_O, V_{O\_MIN} - V_O)$



## Output Swing Example

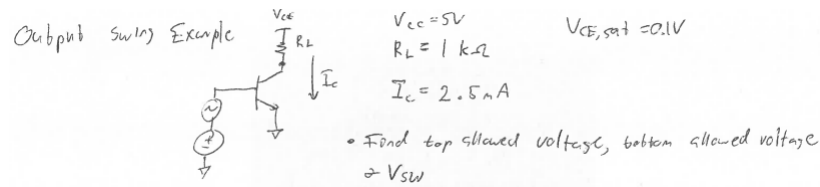

1. Find  $V_O = V_{CC} - I_C \cdot R_L$
  2. If  $V_O$  down, when do we leave FAR?  $V_{MIN} = V_{CE,SAT}$
  3. If  $V_O$  up, when do we leave FAR?  $V_{MAX} = V_{CC}$  (cutoff)
  4. Check at input:  $A_v = g_m \cdot R_L = 100$ , so  $+2.5V$   $V_O/2$  is  $\sim 25\text{mV}$  @in
- Approximate: get distortion before sat/cutoff  $\rightarrow$  use FFT & 1-2V margin