

# E151 Lecture 10 – Emitter Follower and Multistage

Matthew Spencer  
Harvey Mudd College  
ENGR151


## Disclaimer

These are notes for Prof. Spencer to give the lecture, they were not intended as a reference for students. Students asked for them anyway, so I'm putting them up as a courtesy. Remember that they are not intended as a substitute for attending lecture.

## CE with Degen

- Find  $r_{in}$ ,  $r_{out}$ ,  $a_v$

ke Rin



- Note  $V_{in} \neq V_{be}$   
 - leads to feedback  
 (could do  $f_{in}$  (or  $shv$ )

$V_{be} = i_i \cdot r_{\pi}$   
 $V_E = (g_m r_{\pi} i_i + i_i) R_E$  *really big!*  
 $V_i = V_E + V_{be} = i_i (r_{\pi} + R_E + \beta R_E)$

You Try Av


$V_{be} = r_{\pi} i_i / R_{in}$   
 $V_o = -g_m (r_{\pi} i_i / R_{in}) \cdot R_L$   
 $= \frac{-g_m r_{\pi} R_L}{r_{\pi} + R_E + \beta R_E} i_i$   
 $A_v = \frac{-\beta R_L}{r_{\pi} + (\beta + 1) R_E} \approx -\frac{R_L}{R_E}$

- $r_{out} = R_L$  if  $r_o$  presumed infinite, you will do more on your HW

## Emitter Follower (Common Collector)

- We don't yet have the ability to generate a small  $r_{out}$
- Need a new amplifier topology. I do  $r_{in}$ , they do  $a_v$ , I do  $r_{out}$
- $r_{in}$  follows same patterns as CE w/ degen,  $r_{out}$  is a new pattern ( $1/g_m$ )

→ Emitter follower!

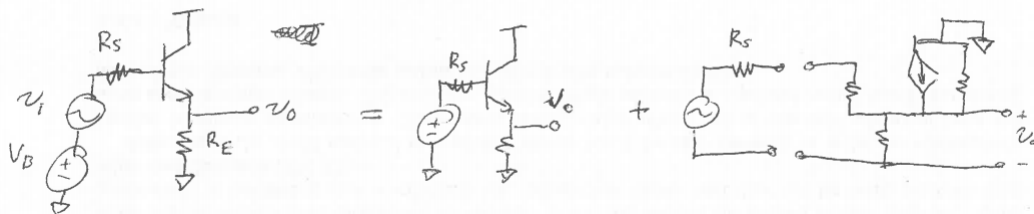


# rin

- Same pattern as CE with degen


$$\begin{aligned}
 v_{be} &= r_{\pi} i_i \\
 i_i &= \frac{v_o}{R_E \parallel r_o} - g_m v_{be} \\
 &= \frac{v_o}{R_E \parallel r_o} - g_m r_{\pi} i_i \\
 v_o &= (R_E \parallel r_o) (1 + \beta) i_i
 \end{aligned}$$

$$v_i = v_o + v_{be}$$
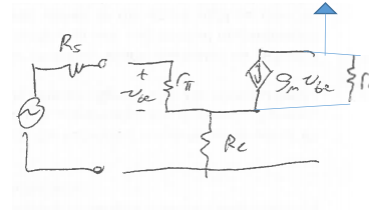
$$R_{in} = r_{\pi} + (\beta + 1)(R_E \parallel r_o) \approx \beta R_E$$



OR

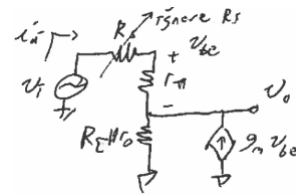

## Exercise: you find av


- Gain of 1 isn't very high, level shift is nice interpretation

Calc Av  $v_o = i_i (\beta + 1) (R_E \parallel r_o)$  from above

$$A_v = \frac{(\beta + 1)(R_E \parallel r_o)}{r_{\pi} + (\beta + 1)(R_E \parallel r_o)} v_i \quad \text{b/c } i_i = v_i / R_{in}$$

$$\rightarrow A_v \approx 1$$

Let's look @ large signal to check this

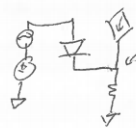

$$v_E = v_B - 0.7$$

- Gain is 1, level shifted down
- Used to get DC voltages right
- $v_{BE}$  stays  $\approx 0.7$ , small sig captures changes

## rout – a new small signal pattern (1/gm)

- Need to include Rs b/c not pure 1 directional
- Breaks our 2 port model a bit
- The reason why we measure rout w/ "input sourced":

calc Rout

- Need to include Rs - start w/  $V_{be}$  this time!

$$i_b = \frac{V_b}{R_E} + \frac{V_b}{r_o} + \frac{V_b}{r_{\pi} + R_s} - g_m V_{be}$$

and  $V_{be} = -\frac{R_{\pi}}{r_{\pi} + R_s} V_b$

so  $i_b = V_b \left( \frac{1}{R_E} + \frac{1}{r_o} + \frac{1}{r_{\pi} + R_s} + \frac{g_m r_{\pi}}{r_{\pi} + R_s} \right)$

$$R_{out} = R_E \parallel r_o \parallel \left. \frac{r_{\pi} + R_s}{\beta + 1} \right\} \approx \frac{1}{\beta} + \frac{R_s}{\beta + 1}$$

$\approx \frac{1}{g_m}$

- Backwards gain of  $\frac{r_{\pi}}{R_s + r_{\pi}}$ , we ignore in 2 port model

- say it's small --

- why  $\frac{1}{g_m}$ ? Voltage applied directly across gm control terminals & receives controlled current

↳ watch for this pattern!

## Small Signal Patterns

- We've just seen two common small signal models that are used a lot
- Here are more, can analyze fast if you understand / memorize
  - Thevenize aggressively, can remove from circuit
- Watch for variations: dividers to vbe, parallel stuff, ro, care w/ signs.

$$R_{in} = R_E \parallel R_T + g_m R_E R_T$$

$$R_{in} = r_{\pi} \parallel \left( \frac{1}{\beta} + \frac{R_c}{\beta} + \frac{R_s}{\beta} \right)$$

You try

$$R_{in} = R_E (\beta + 1) + r_{\pi}$$

These are Rth and not rin