

E151 Lecture 13 – Active Loads and Current Mirrors

Matthew Spencer
Harvey Mudd College
ENGR151

Disclaimer


These are notes for Prof. Spencer to give the lecture, they were not intended as a reference for students. Students asked for them anyway, so I'm putting them up as a courtesy. Remember that they are not intended as a substitute for attending lecture.

Midterm is Coming Up

- Lab on Friday, but stays in 3 hour lab time, gentle grading
- Practice problems and maybe solutions on Sakai
- In class, 1 hr 15 min, no calculator, book, notes
- Get 1 page cheat sheet, must make your own
- Note that tour through MOS physics & amplifiers is kind of a review


What's a Current Mirror and Why?

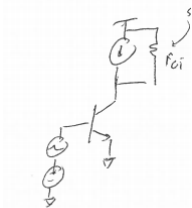- Active loads are pretty cool, but tough to bias
- Amount to biasing w/ a current source ... ideal load (inf. Z, inf. Vsw)
- Fix biasing by using current mirrors



$A_v = g_m (r_{o1} || R_C)$ → unrelated to DC value of V_{out} (both in FAR)
Cool!

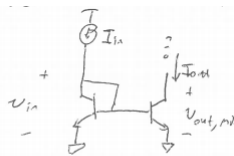- ISSUE 1: How to make
- ISSUE 2: What's large signal V_o



"simple mirror"

$$i_c = T(V_{be}) \text{ on left}$$

$$i_c = T^{-1}(V_{be}) \text{ on right}$$

$$= T(T^{-1}(i_c))$$

What do we care about w/ mirrors?

- Mirror design specifications – functions of I_c , compare @ same I_c

- V_{IN}
- V_{MIN}
- Error = $\epsilon = I_{OUT}/I_{IN}$
- r_{out}

V_{BEON}



V_{CESAT}

$\beta/(\beta+2)$

r_o


$$I_{in} = I_{b1} + I_{c1} \stackrel{I_{c1} = \beta I_{b1}}{=} (\beta+1) I_{b1}$$

$$I_{out} = \beta I_{b1}$$

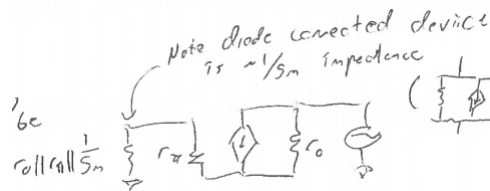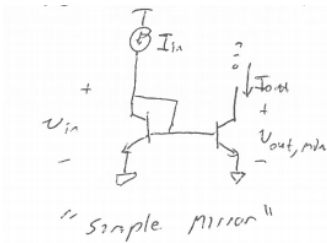


Use Mirrors to Make Active Loads

- $a_v = g_m \cdot (r_{o1} || r_{o2})$ – very high! (~1/2 of what we saw w/ isrc load)
- Need to pick V_B st we're in FAR, do w/ load line or another mirror

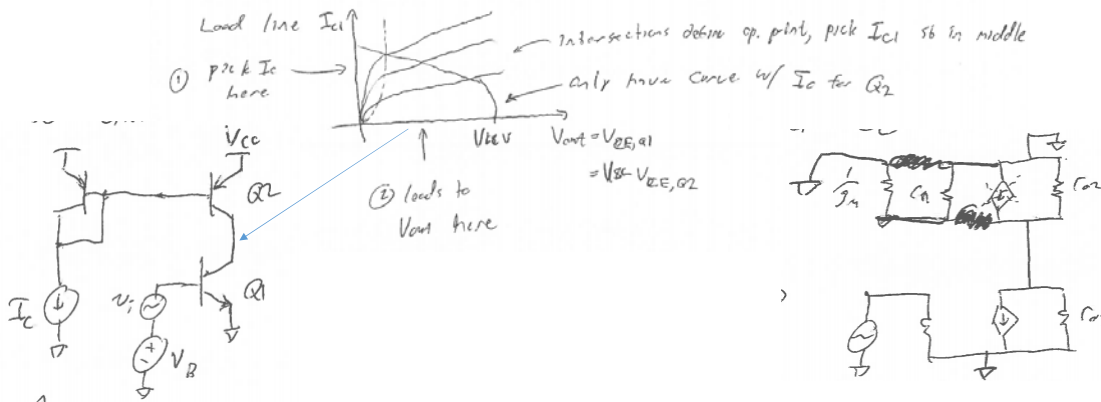

Current Mirror Reminder and Error

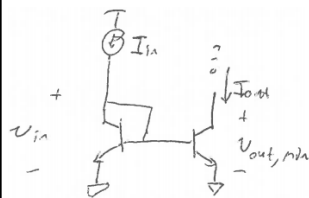
- Error example here, not commonly calculated b/c MOSFETs different
- Similarly, lots of cool types of mirrors ~ Widlar has feedback for low ϵ
- But cascode mirror commonly used in MOS b/c big rout
- Reminder: FOM are V_{IN} , V_{MIN} , ϵ , rout



"Simple Mirror"

$$I_{in} = I_{b1} + I_{c1} \stackrel{I_{c1}}{=} (\beta + 1) I_{b1} \quad \left. \vphantom{I_{in}} \right\} \epsilon = \frac{\beta}{\beta + 1}$$

$$I_{out, mir} = \beta I_{b1}$$

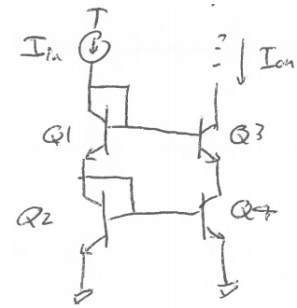

$$V_{in} = 2 \cdot V_{be, on}$$

$$V_{out, mir} = 2 \cdot V_{ce, sat}$$